

TI Designs: PMP9806

TPS61088昇圧コンバータ用の高精度な出力電流制限回路のリファレンス・デザイン



概要

PMP9806リファレンス・デザインは、TPS61088昇圧コンバータ用の高精度な出力電流制限ソリューションです。出力電流感知抵抗とオペアンプを活用して、低コストのアプリケーション向けのソリューションを実現しています。出力電流が電流制限ポイントを超えると、オペアンプの出力がTPS61088の1.204V基準電圧よりも高い電位に上昇し、出力電圧の低下を引き起こします。出力電流が増加し続ける場合は、応答として出力電圧がさらに低下します。この構成により、最大出力電力が常に一定レベルより低く保たれることを保証できます。

リソース

PMP9806

デザイン・フォルダ

TPS61088

プロダクト・フォルダ

TLV2314

プロダクト・フォルダ





E2Eエキスパートに質問

特長

- 入力電圧範囲: 2.7V~4.2V
- 5V/3A、9V/2A、12V/1.5Aの出力能力
- 高精度の出力電流制限
- 最大出力電力の制限
- 小さなサイズのソリューション、簡単な実装

アプリケーション

- 外付けバッテリー
- 昇圧コンバータ・アプリケーションでの最大出力電力の制限

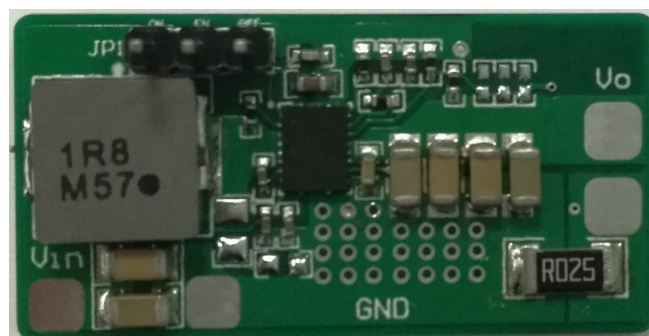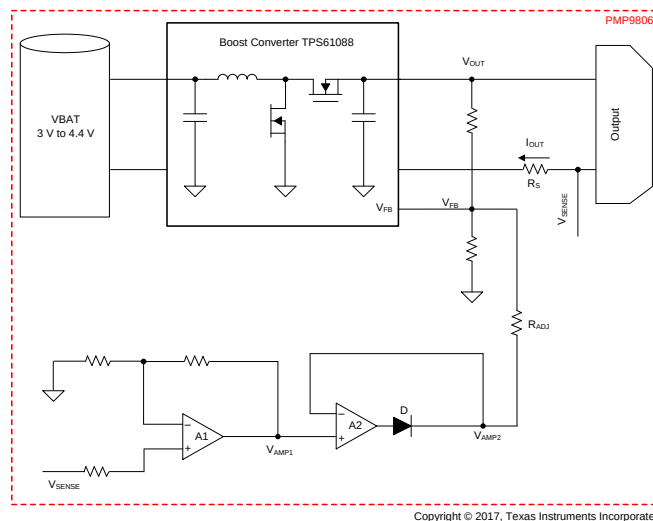

使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、www.ti.comで閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

1 System Description

The latest generation power banks must utilize output power limit functions to avoid the overpower and overheating problems that occur during usage. Overheating is not allowable per Quick Charge 3.0 requirements.

The synchronous boost converter TPS61088 is widely used in quick charge power bank applications. This converter implements cycle-by-cycle current limit to protect the device from overload conditions during boost switching. This current limit function is realized by detecting the current flowing through the low-side MOSFET and has an approximate $\pm 10\%$ precision. The maximum output power varies significantly if designers utilize the current limit function of the TPS61088 itself. The part with a higher current limit threshold generates more heat in the overload conditions and some parts encounter overheating problems.

The PMP9806 reference design delivers an accurate output current-limit solution for the TPS61088 boost converter. This feature is made possible by utilizing an output current sense resistor and an operational amplifier for low cost applications. When the output current exceeds the current limit point, the output of the operational amplifier increases to a voltage higher than the TPS61088 1.204-V reference voltage and causes the output voltage to drop. If the output current continues to increase, the output voltage decreases further in response. This configuration ensures that the maximum output power is always limited below a certain level. The TLV2314 is a low-cost, small packaged operational amplifier. The PMP9806 reference design offers a cost effective and compact solution for power bank applications.

1.1 Key System Specifications

表 1 provides the performance specification of this reference design. When the output current is higher than the setting point, the output voltage drops.

表 1. Performance Specifications

INPUT VOLTAGE	OUTPUT VOLTAGE AND OUTPUT CURRENT	OUTPUT CURRENT LIMIT POINT
3 V to 4.2 V	9 V, 2 A	$I_o \geq 2.1 \text{ A}$
	5 V, 3 A	$I_o \geq 3.15 \text{ A}$
	12 V, 1.5 A	$I_o \geq 1.575 \text{ A}$


2 System Overview

2.1 Block Diagram

Figure 1 shows the block diagram of the PMP9806 reference design. A shunt resistor, R_S , is placed in the output return and this resistor converts the output current to a voltage signal V_{SENSE} . The operational amplifier, A1, senses the voltage V_{SENSE} across the shunt resistor R_S and provides a magnified voltage, V_{AMP1} , to the amplifier A2.

When the output current is lower than the current limit point, V_{AMP1} is lower than the 1.204-V reference voltage of the TPS61088 device, the diode D cannot conduct, and resistor R_{ADJ} is floating. The boost converter functions per usual.

When the output current is higher than the current limit point, V_{AMP1} exceeds the 1.204-V reference voltage of the TPS61088 device and diode D conducts. Voltage V_{AMP2} is equal to the voltage V_{AMP1} ; so, V_{FB} increases and the output voltage V_{OUT} drops. If the output current continues to increase, the output voltage decreases further. Thus the maximum output power always remains limited below a certain level.

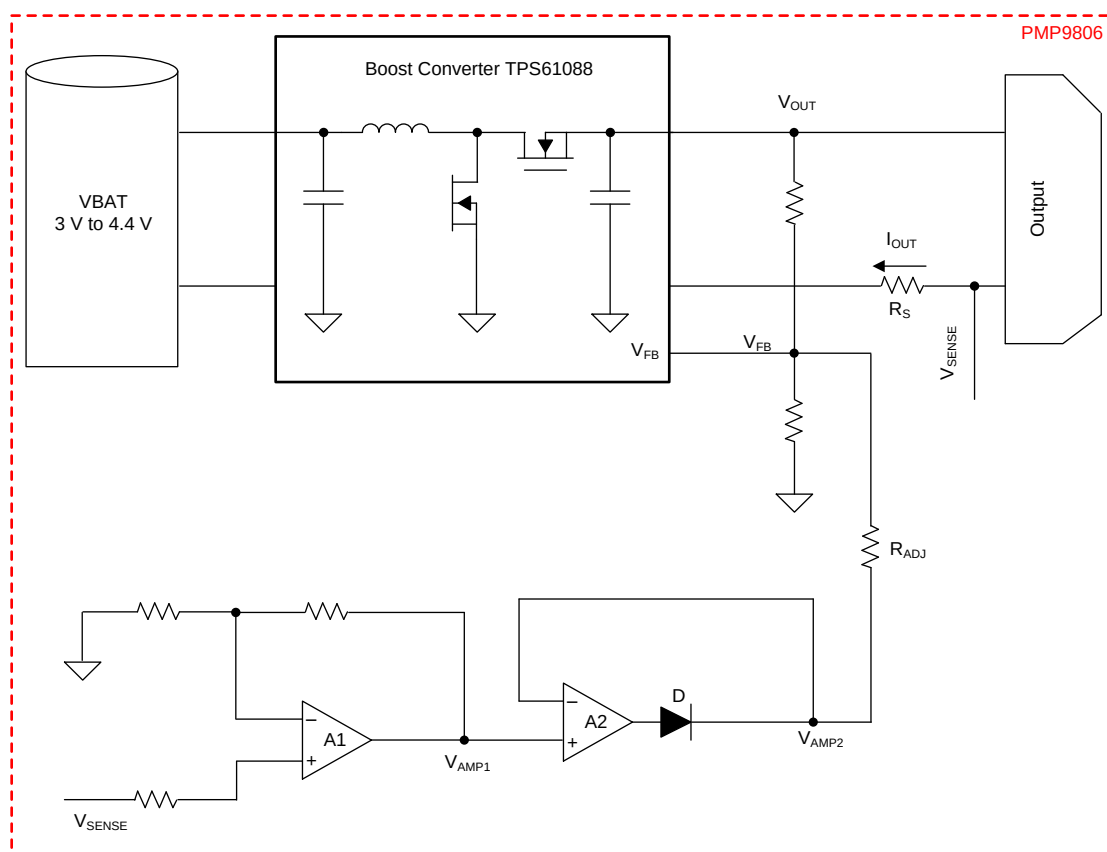

Copyright © 2017, Texas Instruments Incorporated

図 1. PMP9806 Block Diagram

2.2 System Design Theory

This section provides the PMP9806 output current limit circuit design. For the power components and compensation network calculation, see the [TPS61088 10-A Fully-Integrated Synchronous Boost Converter](http://www.ti.com/sc/techlit/TPS61088_10-A_Fully-Integrated_Synchronous_Boost_Converter_datasheet) datasheet[1].

2.2.1 Setting Current Limit Point

The output current limit point must be higher than the maximum output current. In this reference design, the maximum output current is 3 A when $V_O = 5\text{-V}$ condition, 2 A when $V_O = 9\text{-V}$ condition, and 1.5 A when $V_O = 12\text{-V}$ condition. Set the output current limit point to 3.15 A, 2.1 A, and 1.575 A, respectively, to avoid the current limit circuit from false triggering during normal output current conditions.

2.2.2 Shunt Resistor Selection

The use of a shunt resistor is the most versatile and cost-effective means to measure the current. The voltage across this resistor must be kept to a low value to reduce the power loss. In this reference design, the shunt resistor value, R_S , has been selected as 25 mΩ. The maximum continuous current, I_{O_MAX} , which flows through the shunt resistor is 3.15 A when $V_O = 5\text{-V}$ condition. So the maximum shunt voltage, V_{SENSE_MAX} , can be calculated using the following 式 1:

$$V_{SENSE_MAX} = R_S \times I_{O_MAX} \quad (1)$$


The minimum power rating, P_{RATING} , of the shunt resistor can be calculated using the following 式 2:

$$P_{RATING} = V_{SENSE_MAX} \times I_{O_MAX} \quad (2)$$

Using the previous equation, the minimum power rating of the shunt resistor is calculated as 0.248 W in this reference design. A general rule of thumb is to multiply this minimum power rating by 2. Therefore, TI recommends that the designer choose a $\geq 0.5\text{-W}$ resistor in this reference design to make it more robust in the overload or output short-circuit condition.

2.2.3 Output Current Limit Circuit Design

図 2 shows the output current limit circuit in this reference design. The current sense signal V_{SENSE} is connected to the non-inverting input of A1 through R15.

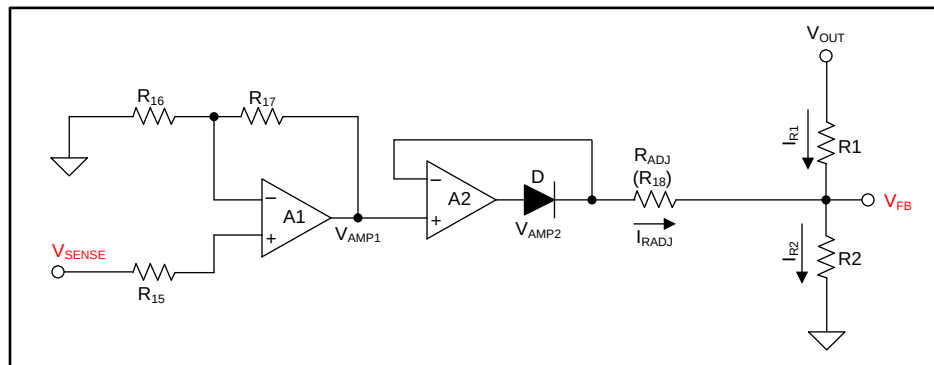

Copyright © 2017, Texas Instruments Incorporated

図 2. Output Current Limit Circuit

During the theoretical calculation (using the 9-V, 2-A output condition for example) of this reference design, the designer sets the operational amplifier A1 output voltage (V_{AMP1}) to 1.204 V when the output current is 2.1 A. This setting is 5% higher than the 2-A maximum normal output current.

When the output current increases to the targeted transition point of 2.1 A, the voltage V_{SENSE} at the non-inverting positive input of A1 is calculated as the following 式 3 shows:

$$V_{SENSE} = R_S \times I_{O_MAX} = 52.5 \text{ mV} \quad (3)$$

To make V_{AMP1} equal to 1.204 V, the designer must rearrange the equation as follows in 式 4:

$$V_{\text{SENSE}} \times \frac{R_{17} + R_{16}}{R_{16}} = V_{\text{AMP1}} \quad (4)$$

This rearrangement results in the following 式 5:

$$\frac{R_{17} + R_{16}}{R_{16}} = \frac{V_{AMP1}}{V_{SENSE}} = \frac{1.204}{0.0525} = 22.93 \quad (5)$$

So select $R_{17} = 232 \text{ k}\Omega$ and $R_{16} = 10.5 \text{ k}\Omega$ in this reference design.

When the output current is higher than 2.1 A, V_{AMP1} exceeds the 1.204-V reference voltage of the TPS61088 device, the diode D conducts. This action causes V_{FB} to increase and the output voltage V_{OUT} to drop. The output voltage dropout is controlled by the resistor R_{ADJ} . The relationship between the output voltage V_{OUT} to the resistor R_{ADJ} can be deduced by the following 式 6 through 式 9:

$$I_{RADJ} + I_{R1} = I_{R2} \quad (6)$$

$$I_{RADJ} = \frac{(V_{AMP2} - V_{FB})}{R_{ADJ}} \quad (7)$$

$$I_{R1} = \frac{V_O - V_{FB}}{R1} \quad (8)$$

$$I_{R2} = \frac{V_{FB}}{R2} \quad (9)$$

Insert 式 7, 式 8, and 式 9 into 式 6 to obtain the following 式 10:

$$V_O = V_{FB} + \left(\frac{V_{FB}}{R2} - \frac{(V_{AMP2} - V_{FB})}{R_{ADJ}} \right) \times R1 \quad (10)$$

Set the V_O to 6.5 V at a 3-A output current condition to limit the output power below a certain level, which results in the following 式 11:

$$R_{ADJ} = \frac{(V_{AMP2} - V_{FB})}{\frac{V_{FB}}{R2} - \frac{(V_O - V_{FB})}{R1}} \approx 169 \text{ k} \quad (11)$$

where,

- $V_{AMP2} = V_{AMP1} = V_{SENSE} \times (R_{17} + R_{16}) / R_{16} = 1.73 \text{ V}$ when $I_O = 3 \text{ A}$
- $R1 = 768 \text{ k}$
- $R2 = 120 \text{ k}$.

If set the V_O to 5.5 V when at a 3-A output current condition, $R_{ADJ} = 121 \text{ k}$.

3 Test Results

3.1 Start-Up Waveforms

Figure 3 shows the start-up waveforms of the inductor current and the output voltage at $V_{IN} = 3.3\text{ V}$ and $I_O = 2\text{ A}$ condition.

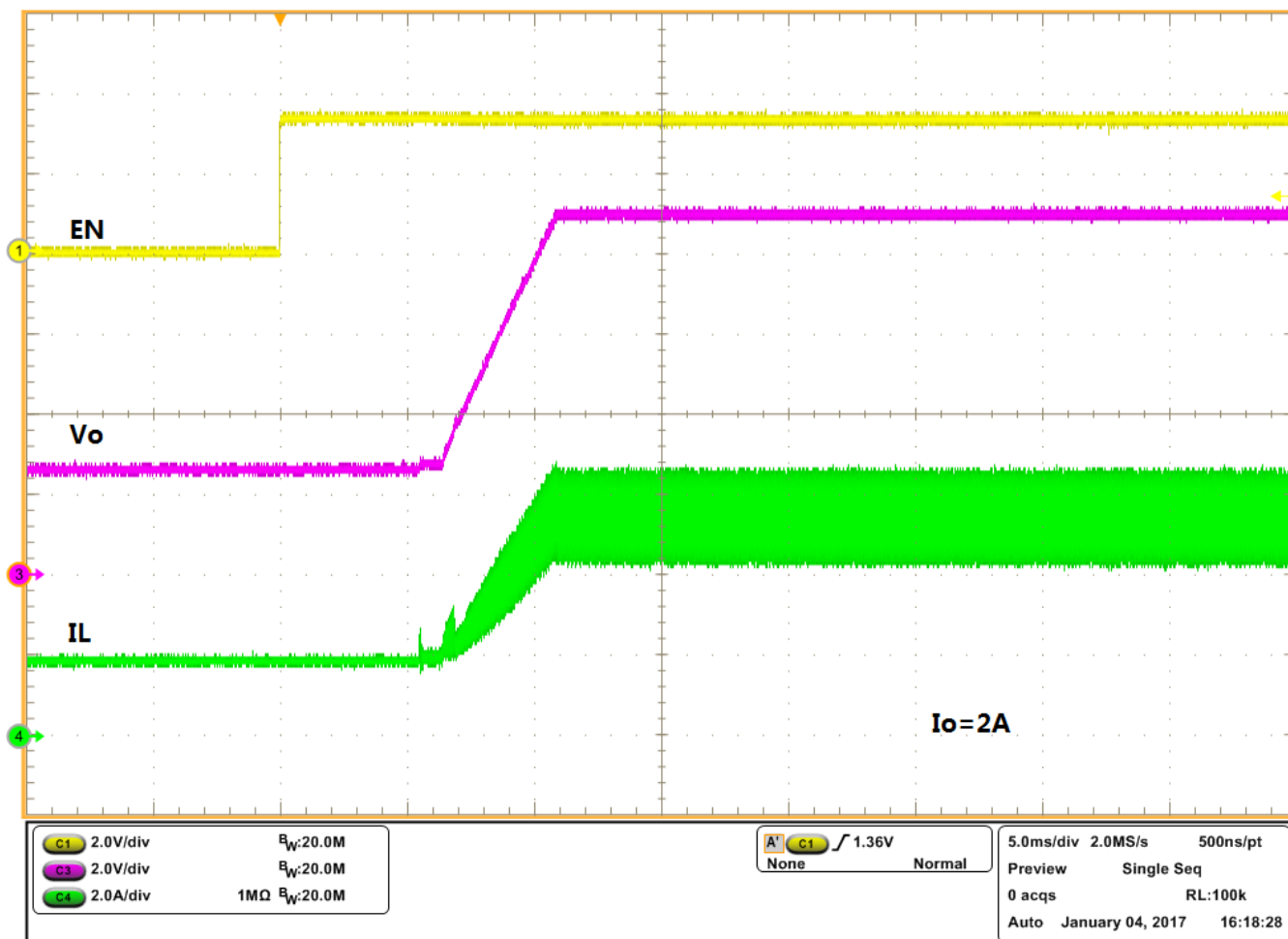


図 3. Start-up Waveforms at $I_O = 2\text{ A}$ ($V_O = 9\text{ V}$)

Figure 4 shows the start-up waveforms of the inductor current and the output voltage at $V_{IN} = 3.3\text{ V}$ and $I_O = 3\text{ A}$ condition. As the output current is higher than the current limit point, the boost converter enters into the current limit mode after start-up. The output voltage after start-up is 6.2 V .

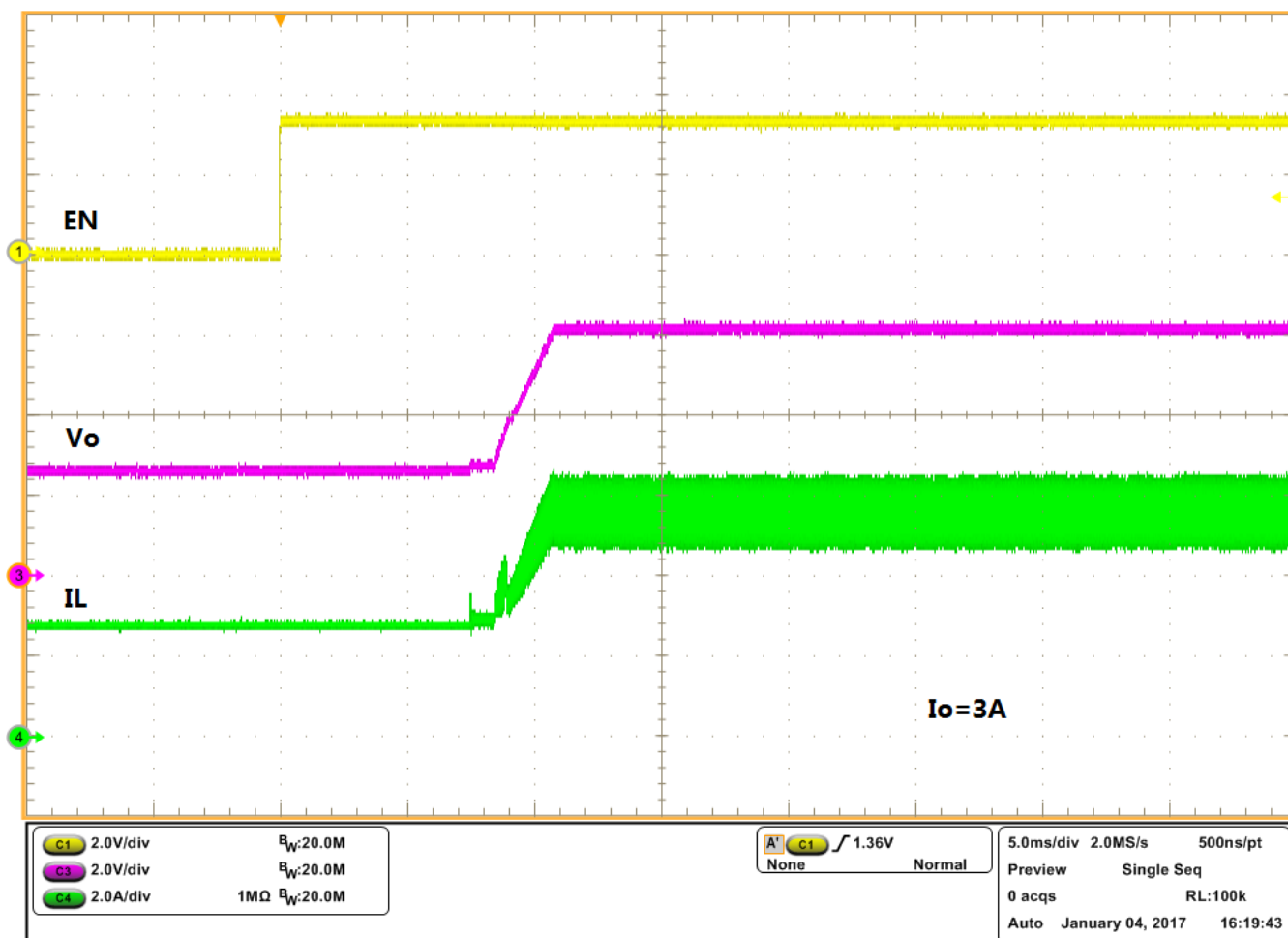


図 4. Start-up Waveforms at $I_O = 3\text{ A}$ ($V_O = 9\text{ V}$)

3.2 Output Current Limit Waveforms

Figure 5 shows the output current limit waveforms at $V_o = 9\text{ V}$ condition. From the waveforms of the output voltage, output current, and the inductor current, the designer can observe that the output voltage drops from 9 V to 6.2 V within 50 μs when the output current suddenly increases from 2 A to 3 A.

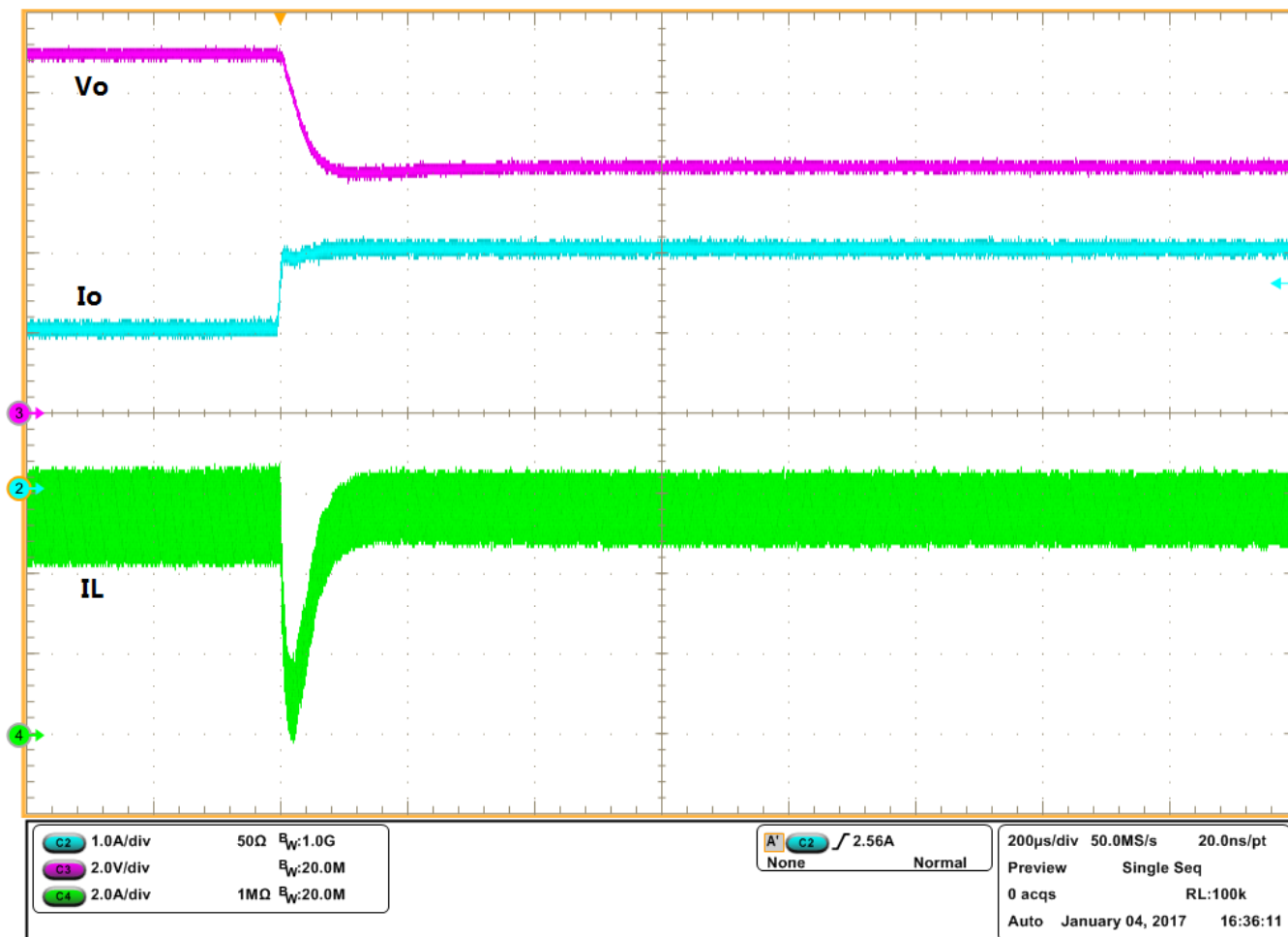


図 5. Output Current Limit Waveforms at $V_o = 9\text{ V}$ ($I_o = 2\text{ A}$ to 3 A)

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [PMP9806](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [PMP9806](#).

4.3 Altium Project

To download the Altium project files, see the design files at [PMP9806](#).

4.4 Gerber Files

To download the Gerber files, see the design files at [PMP9806](#).

4.5 Assembly Drawings

To download the assembly drawings, see the design files at [PMP9806](#).

5 Related Documentation

1. Texas Instruments, [TPS61088 10-A Fully-Integrated Synchronous Boost Converter](#), TPS61088 Datasheet (SLVSCM8)

5.1 商標

All trademarks are the property of their respective owners.

6 About the Author

HELEN CHEN is an application engineer on the Texas Instruments BMC-BCS team. She brings more than 12 years of experience in power supply product design. Helen started her career as an AC-DC server power design engineer in Delta Power Electronics before joining TI in 2014. Helen specializes in various circuit topologies such as buck, boost, RCC, buck-boost, full-bridge, half-bridge, fly-back, CCM PFC, and DCMB PFC. She also has experience in the magnetic components design, PCB layout, and EMI solutions.

重要なお知らせと免責事項

TI は、技術データと信頼性データ (データシートを含みます)、設計リソース (リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Web ツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の黙示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または黙示的にかかわらず拒否します。

これらのリソースは、TI 製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1) お客様のアプリケーションに適した TI 製品の選定、(2) お客様のアプリケーションの設計、検証、試験、(3) お客様のアプリケーションが適用される各種規格や、その他のあらゆる安全性、セキュリティ、またはその他の要件を満たしていることを確実にする責任を、お客様のみが単独で負うものとします。上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されている TI 製品を使用するアプリケーションの開発の目的でのみ、TI はその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TI や第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TI およびその代理人を完全に補償するものとし、TI は一切の責任を拒否します。

TI の製品は、TI の販売約款 (<https://www.tij.co.jp/ja-jp/legal/terms-of-sale.html>)、または [ti.com](https://www.ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TI がこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

日本語版 日本テキサス・インスツルメンツ合同会社
Copyright © 2021, Texas Instruments Incorporated