

## TI Designs: TIDA-01350

# 高速、リニア・トランシスインピーダンス・アンプのリファレンス・デザイン



## 概要

このトランシスインピーダンス・アンプのデザインは、LMH5401完全差動アンプ(FDA)を使用する高速、リニアの2段トランシスインピーダンス・アンプ(TIA)アプリケーションです。このリファレンス・デザインには、ファイバー・ピグテール付きのフォトダイオードが含まれます。提供されるフォトダイオードは、ほぼ理想的な電流ソースとなるため、テストが簡単になります。

## リソース

[TIDA-01350](#)

デザイン・フォルダ

[LMH5401](#)

プロダクト・フォルダ

[TINA-TI™](#)

ツール・フォルダ

## 特長



- 帯域幅: 500MHz超
- 電流を電圧に変換
- フォトダイオード内蔵
- 2段によるゲインの増大

## アプリケーション

- [リニア光受信機](#)
- [マシン・ビジョン](#)
- [近接検出器](#)



[E2Eエキスパートに質問](#)

  

使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、[www.ti.com](http://www.ti.com)で閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

## 1 System Description

The TIDA-01350 TI Design is a fixed-gain, high-bandwidth, fully-differential, current-to-voltage conversion circuit designed for high-speed applications. This reference design includes the full optical-to-electrical conversion gain circuit, including two stages of electrical gain for improved sensitivity and bandwidth.

Optical proximity detectors use a photodiode receiver to measure the return time of an optical pulse. The TIDA-01350 has a very-high-speed response and the sufficient level of sensitivity required to measure a reflected light pulse.

Machine vision applications, such as linear measurement or edge detection, require high-speed optical power measurements. The TIDA-01350 enables high-speed optical power detection.

Multi-bit modulation patterns such as PAM-4 or QPSK require receiver circuits with a linear response. The TIDA-01350 has very-high-fidelity linearity performance, which allows high-order modulation schemes that enable more data to be sent in the same bandwidth.

### 1.1 Key System Specifications


表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Supply voltage	5- V external supply
Current-to-voltage gain	500 $\Omega$ to 10000 $\Omega$
Differential-output common-mode voltage	0 V
Target bandwidth	> 500 MHz
Onboard photo diode	AC Photonics PTD0075A2211
Fiber connector	FC/APC

## 2 System Overview

### 2.1 Block Diagram

図 1 shows a block diagram of the system. The main portion of the design is two fully-differential amplifiers (FDAs). An onboard photo diode is provided to facilitate high-speed testing. The board is populated for a transimpedance of 10000  $\Omega$  by default.

 

Copyright © 2017, Texas Instruments Incorporated

図 1. System Block Diagram


## 2.2 Highlighted Products

### 2.2.1 THS4131

The TIDA-01350 design features the [LMH5401](#) fully differential amplifier (FDA).

The LMH5401 is a very-high-performance differential amplifier optimized for radio frequency (RF), intermediate frequency (IF), or high-speed, DC-coupled, time-domain applications. The device is ideal for DC- or AC-coupled applications that may require a single-ended-to-differential (SE-DE) conversion when driving an analog-to-digital converter (ADC). The LMH5401 generates very low levels of second- and third-order distortion when operating in SE-DE or differential-to-differential (DE-DE) mode.

The amplifier is optimized for use in both SE-DE and DE-DE systems. The device has unprecedented usable bandwidth from DC to 2 GHz. The LMH5401 can be used for SE-DE conversions in the signal chain without external baluns in a wide range of applications such as test and measurement, broadband communications, and high-speed data acquisition. [図 2](#) shows the LMH5401 block diagram.

 


**図 2. LMH5401 Functional Block Diagram**
 
## 2.3 System Design Theory

The TIDA-01350 is a linear, high-speed transimpedance amplifier (TIA) reference design. 図 3 shows the system block diagram. TIAs are very sensitive to input diode capacitance. As diode capacitance increases, the bandwidth of the circuit decreases. In the same manner, increasing the value of the feedback resistor decreases the bandwidth of the amplifier. Weighing both the required gain and bandwidth is very important because there is a gain bandwidth relationship in TIAs. Two stages are used in this reference design to achieve high gain as well as high bandwidth.

The other key component of the reference design is the photo diode. The PTD0075A2211 diode has been chosen for two primary specifications. The first key specification is the junction capacitance of 0.6 pF and the second key specification is the reverse bias voltage of 5 V. The 5-V bias voltage is chosen to keep the system design very simple because the amplifiers and the diode operate from the same supply voltage. The diode is specified for a 1550-nm optical wavelength but it operates very well at the 1310-nm test frequency, as well. The sensitivity of the diode is 0.9 A/W, which means for every watt of illumination power the diode allows 0.9 A of current to flow. This design has been tested at power levels of 5 mW and below.



Copyright © 2017, Texas Instruments Incorporated

**図 3. Frequency Shaping Components Shown in Red**

### 3 Design Options

#### 3.1 Diode Bias

There are two ways to apply the bias voltage to the photo diode. This first option is the use of inductors. The benefit of inductors is that the voltage applied to the diode is independent of the diode current. The drawback of using bias inductors is that inductors short out low-frequency optical currents. Inductors are also more expensive than resistors, which are the other option for diode bias.

In [图 1](#), inductors L1 and L2 are used to provide reverse bias to the photo diode. The diode used in TIDA-01350 is designed for a 5-V bias voltage, which is also the recommended supply voltage for the LMH5401 amplifier, so the bias inductors connect to the same supplies that are used for the amplifiers. Key parameters to consider when choosing the bias inductors are the inductance, parasitic capacitance, and series resistance. This design uses 1- $\mu$ H inductors, which provide a good balance of high impedance at low frequencies while maintaining low parasitic resistance. A larger value inductor improves the low-frequency response.

The photo diode can also be biased with resistors, as the previous [图 3](#) shows. If resistors are desired for providing the diode bias, make sure that the diode DC current does not reduce the DC bias voltage to the point that the diode performance suffers. Note that the diode junction capacitance increases as the bias voltage on the diode decreases. This increase in diode junction capacitance causes a decrease in system bandwidth.

Given a diode sensitivity of 0.9 A/W and an average illumination power of 1 mW, the average diode current is 0.9 mA. With two 1-k bias resistors, the diode bias voltage is reduced by  $2 \times (0.0009 \times 1000) = 1.8$  V, which leaves a bias voltage of  $5\text{ V} - 1.8\text{ V} = 3.2$  V.

Even though many electrical signals are zero-referenced, it is rare for optical signals to be fully modulated. Typically, a modulated optical signal only has modulation which is specified as an extinction ratio (ER). The ER is defined as the ratio of the one power to the zero power and is usually specified in dB. For example, if the one power is 1 mW and the zero power is 0.5 mw, the ER is  $10 \times \log(1 / 0.5) = 3.0$  dB. A fully-modulated signal where the zero level is 0 mW would have an infinite ER.

The standing bias current required by the photo diode is determined by both the modulation current and the ER of the diode. The current consumed by the diode in the zero logic state is basically waste current. When using inductive bias, this waste current does not dissipate nearly as much power. In contrast, when using a resistive bias, the waste current contributes to voltage loss in the bias resistors. Using small-value bias resistors keeps this loss low, but then the signal current is diverted from the TIA and into the bias resistors. This dilemma makes selection of the bias resistor value difficult. A high-value resistor is desired for maximum system gain, so if possible, use a high ER modulator for the signal source.

#### 3.2 AC Coupling and Stability

The capacitors labeled CIn are required to isolate the bias voltage from the amplifier inputs. These capacitors are not optional if a reverse-biased diode is used. While it is possible to use a photo diode with no reverse bias, that application is not addressed in this reference design.


TIAs can be unstable when the input capacitance is too large. Place capacitors in parallel with the feedback resistors to stabilize the circuit. These capacitors are shown as CF1. These resistors are not required for the chosen photo diode, as discovered during characterization of the circuit.

The second-stage amplifier is a voltage amplifier. The LMH5401 device is specified for a minimum stable gain of 3 V/V. The unmarked resistors at the input of stage 2 are used to add gain to stage 2 for stability. These resistors are not required for any of the configurations detailed in this reference design.

[5.1.1](#) provides further detail on the capacitors labeled as Cb1, Cb2, and Peaking Caps.
 
## 4 Getting Started Hardware

The performance of the TIDA-01350 has been evaluated using TINA-TI™ simulation software as well as in the lab using an optical-to-electrical vector network analyzer. 図 4 shows the hardware setup diagram for evaluating the reference design frequency response. The optical unit is capable of -2-dBm to 5-dBm laser power. Use optical attenuators to test smaller input signals and reduce the optical power to the desired level.



Copyright © 2017, Texas Instruments Incorporated

図 4. Hardware Setup Diagram


## 4.1 Applying Power and Basic Setup

The following subsections cover the two main test configurations for the TIDA-01350 reference design. The first configuration is for frequency response (see [図 4](#)). The second configuration is for time domain testing (see [図 9](#)).

### 4.1.1 Board Power Supply Setup

The TIDA-01350 reference design supports a supply voltage range of 4.5 V to 5.25 V. The recommended supply voltages are +2.5 V and –2.5 V with the output common-mode voltages set to 0 V. The setup procedure is as follows:

1. With the supplies disconnected, set the voltage on the DC power supply (capable of sourcing 300-mA current) between 4.5 V to 5.25 V. Also, set the current compliance limit to approximately 200 mA on the DC power supply.
2. Keeping the supplies turned OFF, connect the positive supply lead of the DC power supply to the red V+ test point.
3. Connect the negative power supply lead to the yellow V– test point.
4. When using split-supply supplies, connect the black GND connector to the supply common. When using single supplies, connect the black GND connector to V–.
5. When using single supplies, the Vcm pin must be set to an appropriate voltage as detailed in [4.2](#). See [LMH5401 8-GHz, Low-Noise, Low-Power, Fully-Differential Amplifier \(SBOS710\)](#) for the voltage limits of this pin.
6. Enable the power supplies. The supply current must be approximately 120 mA.

 

**図 5. Board Layout Bottom Showing Supply Connections**

#### 4.1.2 Connecting Optical Input

1. Make sure the optical source is disabled.
2. The photodiode has an attached fiber optic cable with an angled physical contact (APC) connector. APC connectors are typically green in color. Check the owner's manual to determine what kind of connector the test equipment uses by default.
3. Connect the diode optical fiber to the optical source.
4. Enable the optical source.

#### 4.1.3 Connecting AC Test Equipment

1. The +OUT and –OUT connectors (J1 and J2) are 50- $\Omega$  SMA connectors. Use a 50- $\Omega$  cable to connect these two connectors to test equipment that supports differential signaling, or use math as detailed in the following steps to extract the proper signal.
2. For differential signal measurement, an oscilloscope should be set to CHA – CHB to show a differential signal when +OUT and –OUT are connected to CHA and CHB, respectively.
3. For common-mode signal measurement, an oscilloscope should be set to (CHA + CHB) / 2 to show a differential signal when +OUT and –OUT are connected to CHA and CHB, respectively.

### 4.2 Output Common-Mode Voltage Option

The LMH5401 amplifier features an output common-mode control pin. This pin allows a small amount of voltage adjustment in the amplifier output common-mode voltage ( $V_{cm} = (+OUT - -OUT) / 2$ ). For small output voltage levels (2 V<sub>PP</sub> or lower), the amplifier output common-mode can be offset from mid supply by 0.5 V. For large output signals, the amplifier output common-mode must be set exactly to mid supply.

By default, the TIDA-01350 board has a 1-k $\Omega$  resistor from the Vcm test point to ground. This configuration is appropriate for split supplies that are symmetrical about ground. All testing for this design guide has been performed using split 2.5-V power supplies and  $V_{cm} = 0$  V.

Two options are available for single supplies or for supply voltages that are not symmetrical. The first option is to connect a bench power supply with the desired Vcm voltage to the Vcm test point. With a 1-k $\Omega$  resistor to ground, it is very easy to overdrive this pin to the desired voltage with no changes to the board. The second option is to remove R14 and use resistors R1 and R2 to set a voltage divider to set the proper Vcm voltage using the existing supplies. This option does not require an additional bench supply, but does require board modifications.

## 5 Testing and Results

### 5.1 Frequency Response

図 4 details the setup procedure for frequency response testing. 図 6 shows the frequency response for several input optical power levels. This graph covers signals from  $-2 \text{ dBm}$  to  $-27 \text{ dBm}$ . The ER is approximately 5 dB.

 


図 6. Optical Input Frequency Response

Note that in 図 6 the gain shown includes losses in the optical modulator, so the gain is not directly correlated to the board gain. 表 2 lists the calculations for board gain.

#### 5.1.1 Shaping Frequency Response

The addition of a few components enables the user to shape the frequency response to eliminate the gradual amplitude loss shown in the previous 5.1. The response in 図 7 is flat out to 600 MHz. 図 8 shows the additional components used to generate this frequency response. The trade-off for the increased flat-band response is a faster drop of amplitude above the flat-band frequency.


 


図 7. Frequency Response With Frequency Shaping

 


Copyright © 2017, Texas Instruments Incorporated

**図 8. Schematic Showing Frequency-Shaping Capacitors**

## 5.2 Digital Data Testing

図 9 shows the hardware configuration for the digital data testing.

 

Copyright © 2017, Texas Instruments Incorporated

**図 9. Test Setup for Digital Testing**

図 10 and 図 11 show the results of the time domain measurements.

 


図 10. Small Signal Response:  $f = 700$  MHz

 


図 11. Large Signal Response:  $f = 700$  MHz

### 5.3 Overall Transimpedance Gain

For high-speed circuits, the capacitance of the photo diode together with the gain of the amplifier limits the bandwidth. Reducing the diode capacitance increases bandwidth and reducing the TIA gain also increases bandwidth. Obtaining the desired bandwidth in one stage may not be possible for a given diode and gain. The TIDA-01350 reference design uses two stages of LMH5401 amplifiers to achieve bandwidths approaching 1 GHz along with transimpedances of 1 k $\Omega$  or higher. 表 2 lists the component selections for a variety of gain configurations. Note the 10  $\Omega$  in the interstage and output termination resistor columns. This occurrence is to indicate that there is an addition to the  $\Omega$  of resistance internal to the LMH5410 device. This resistance must be included in the gain calculations.

表 2. Transimpedance Gain for Various Resistor Values<sup>(1)</sup>

STAGE 1 FEEDBACK RESISTORS	INTERSTAGE RESISTANCE	STAGE 2 FEEDBACK RESISTORS	OUTPUT TERMINATION RESISTORS	TOTAL SYSTEM TRANSIMPEDANCE GAIN
499 $\Omega$	24.9 $\Omega$ + 10 $\Omega$	499 V	40 $\Omega$ + 10 $\Omega$	3567 $\Omega$
300 $\Omega$	24.9 $\Omega$ + 10 $\Omega$	499 V	40 $\Omega$ + 10 $\Omega$	2144 $\Omega$
300 $\Omega$	24.9 $\Omega$ + 10 $\Omega$	300 V	40 $\Omega$ + 10 $\Omega$	1289 $\Omega$
200 $\Omega$	24.9 $\Omega$ + 10 $\Omega$	300 V	40 $\Omega$ + 10 $\Omega$	859 $\Omega$

<sup>(1)</sup> Transimpedance gain =  $RF_1 \times (RF_2 / RG_2) / 2$

図 12 shows the relationship between gain and bandwidth. Similarly, 図 13 shows the gain for both a single-stage- and two-stage circuit. The performance gained by using two stages is clear.

 


図 12. Bandwidth versus Gain for  $3567\ \Omega$  and  $859\ \Omega$

 



図 13. Bandwidth One Stage versus Two Stage

## 5.4 Noise

表 3 lists the primary amplifier noise terms. See *Analysis of fully differential amplifiers* for a full explanation of amplifier error terms. For this reference design, the noise of the first stage is amplified by the second stage, so the first stage noise dominates. Using a 500- $\Omega$  feedback resistor for the first stage, the voltage noise and current noise are both significant. The voltage noise is 1.25 nV/ $\sqrt{\text{Hz}}$  and the current noise multiplied by the transimpedance gain is 1.75 nV/ $\sqrt{\text{Hz}}$ . These two noise sources are uncorrelated, so add in a root sum of squares (RSS) manner. The RSS sum of these sources are, in turn, added to the second-stage noise terms. Unlike the first stage, where the voltage and current noise are both significant, only the voltage noise is significant in the second stage. As it turns out, the total system noise is significantly higher than the amplifier contributions. 図 14 shows the output noise for two different diode bias circuits.

**表 3. Input Referred Error Terms**

PARAMETER	VOLTAGE NOISE	CURRENT NOISE
Stage 1 input noise	1.25 nV/ $\sqrt{\text{Hz}}$	3.5 pA/ $\sqrt{\text{Hz}}$
Stage 1 output noise, $R_{F1} = 499$	1.25 nV/ $\sqrt{\text{Hz}}$	$3.5 \text{ pA}/\sqrt{\text{Hz}} \times 500 = 1.75 \text{ nV}/\sqrt{\text{Hz}}$
Stage 2 input noise (at 100 MHz)	2.66 nV/ $\sqrt{\text{Hz}}$	$3.5 \text{ pA}/\sqrt{\text{Hz}} \times (500 \parallel 34.9) = 0.122 \text{ nV}/\sqrt{\text{Hz}}$
Stage 2 output noise $R_{F2} = 499$ , $R_{G2} = 34.9$	19 nV/ $\sqrt{\text{Hz}}$	—

 

**図 14. Output Referred Noise**

The graph of output voltage noise in 図 14 shows curves for both inductive bias and resistive bias (1-k $\Omega$  resistors) circuits. As expected, the inductive bias provides slightly lower noise because an inductor is ideally noiseless. The reason that the curves converge at higher frequencies is due to the amplifier voltage noise and the diode capacitance. 式 1 shows the equation for the amplifier noise gain. Notice that the amplifier noise gain is a function of the input capacitance, the feedback resistor, and frequency. What is unique for a TIA is that there is no  $R_G$  or gain set resistor, which is a key attribute of the TIA applications. At higher frequencies, the amplifier noise gain grows larger; and so at high frequencies, this noise term dominates the other terms. The rolloff in noise that starts at 900 MHz is due to the frequency-shaping capacitors Cb1 and Cb2.

$$\sqrt{1 + (2\pi f \times C_{IN} \times R_f)^2} \quad (1)$$

One important thing to note about high-frequency circuits is that there are no ideal components. As previously noted, there is no discrete or schematic value for  $R_G$ . Employing a careful PCB design to minimize parasitic resistance is essential to obtaining a reasonably accurate value for  $R_G$ . This task is especially important at high frequencies because of the RF skin effect, which causes resistance of circuit components to increase with increasing frequency. Likewise, the parasitic capacitance and inductance of the circuit elements can be large enough to cause performance changes. For example, this reference design does not use a feedback capacitor; however, the capacitance of the PCB traces is enough to provide sufficient capacitance on the feedback resistor to ensure stability. Due to this reason, 式 1 is only accurate at frequencies up to approximately 1.5 GHz.

## 6 Design Files

### 6.1 Schematics

To download the schematics, see the design files at [TIDA-01350](#).

### 6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01350](#).

### 6.3 PCB Layout Recommendations

#### 6.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01350](#).

#### 6.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01350](#).

### 6.5 Layout Guidelines

図 15 shows the layout guidelines for this reference design. The design features a six-layer board with a Rogers RO4350 dielectric under the top layer. Note that the signal path is confined to the top layer. The other layers of the printed-circuit board (PCB) use standard FR406 dielectric. The other layers include ground and power planes. To maximize the interplane capacitance, the positive and negative power supply planes are adjacent on layers 3 and 4, respectively. The overall stack up is: Signal, Ground, V+, V-, Ground, and back.

See the layout section in [LMH5401 8-GHz, Low-Noise, Low-Power, Fully-Differential Amplifier](#) for layout guidelines related to the LMH5401.

 


図 15. Example Layout (Top Layer)

## 6.6 Gerber Files

To download the Gerber files, see the design files at [TIDA-01350](#).

## 6.7 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01350](#).

## 7 Related Documentation

1. Texas Instruments, [\*LMH5401 8-GHz, Low-Noise, Low-Power, Fully-Differential Amplifier\*](#),
2. Texas Instruments, [\*Analysis of fully differential amplifiers\*](#)
3. Texas Instruments, [\*Op amp stability and input capacitance\*](#)

### 7.1 商標

TINA-TI is a trademark of Texas Instruments.

すべての商標および登録商標はそれぞれの所有者に帰属します。

## 8 About the Author

**LOREN SIEBERT** is an applications engineer with TI in the High-Speed Amplifier division in Fort Collins, Colorado. He supports high speed amplifier applications ranging from 4G and 5G radio base stations to Optical Networking.

## TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに合意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任をお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的での、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または默示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものではありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、あるいはTIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的かにかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、統発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する默示の保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁護または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際的、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知られていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかつたために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/samptersms.htm>)についてのTIの標準条項が含まれますが、これらに限られません。