

Powering the TMS320DM368 With TPS650061

This document details the design considerations of a low-cost power solution for the TMS320DM368 low-power application processor with a TPS650061, three-rail Power Management Unit (PMU) or Power Management Integrated Circuit (PMIC).

Portable application solution size demands a high level of integration and the TMS320DM368 requires at least three different voltage rails with specific sequencing and reset requirements. The TPS650061 is a highly integrated, low-cost power solution providing the 1.35-, 1.8-, and 3.3-V rails and RESET signals required by the TMS320DM368. The TPS650061 has a single, step-down converter, two low-dropout regulators, and a voltage supervisor.

Included in this document is a power solution for the TMS320DM368. Power requirements, schematic, operational waveforms, and a bill of materials are provided.

Contents

1	Power	Requirements	2
		Power-On Sequence	
		Power-Off Sequence	
		Power Solution	
2	natic, Waveforms, and Bill of Materials	4	
	2.1	Schematic	4
	2.2	Waveforms	5
	2.3	Bill of Materials	9
3	Conclu	usion	9
4	References		

List of Figures

1	TPS650061 and TMS320DM368 Block Diagram	2
2	TPS650061 External Components and Sequencing Circuit for the 'DM368	4
3	Power-Up Sequence With System Enable HIGH	5
4	Power-Up Sequence and Reset Release	6
5	Power-Down Sequence With System Enable LOW	7
6	Power-Down Sequence and Reset Pulled LOW	8

List of Tables

1	'DM368 Power Requirements	2
2	Bill of Materials	9

1 Power Requirements

Figure 1 presents the block diagram for the TPS650061 and the TMS320DM368 (also referred to as 'DM368).

The 'DM368 power requirements are listed in Table 1.

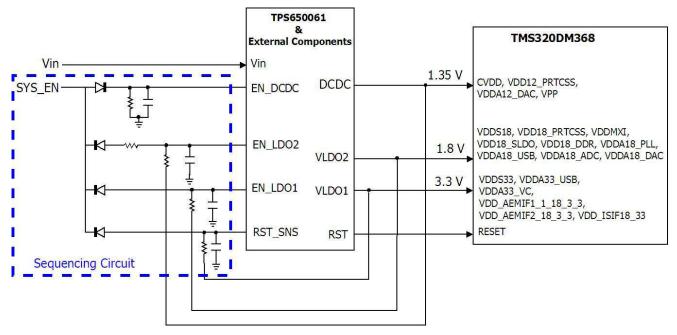




Table 1.	'DM368	Power	Red	uirements
		1 0 11 0 1	1100	

Rail Name	Voltage (V)	Imax (mA)	Tolerance (%)	Power On	Power Off	
CVDD, VDD12_PRTCSS, VDDA12_DAC, VPP	1.35	1000	±5	First	Third	
VDDS18, VDD18_PRTCSS, VDDMXI, VDD18_SLDO, VDD18_DDR, VDDA18_PLL, VDDA18_USB, VDDA18_ADC, VDDA18_DAC	1.8	125	±5	Second	Second	
VDDS33, VDDA33_USB, VDDA33_VC, VDD_AEMIF1_1_18_3_3, VDD_AEMIF2_18_3_3, VDD_ISIF18_33	3.3	146	±5	Third	First	

The TPS650061 meets these power requirements. Power sequencing is implemented using a simple sequencing circuit that controls the order at which the power supplies in the TPS650061 are enabled.

1.1 Power-On Sequence

2

Meet the 'DM368 power-on requirements by powering on the 1.35-V rail first, then both the 1.8-V rail and the 3.3-V rail power on. After all three rails are powered on, RESET is released.

Per the excerpt from the <u>TMS320DM368</u> data sheet for simple power-on, the device must be powered on in the following order:

- 1. Power on PRTCSS/Main Core (1.35 V)
- 2. Power on PRTCSS/Main I/O (1.8 V)
- 3. Power on the Main/Analog I/O (3.3 V)

RESET must be low until all supplies are ramped up.



1.2 Power-Off Sequence

The 'DM368 power-down requirements state that the supplies must power off in the reverse order from which they are powered on. These requirements are described in the <u>TMS320DM368</u> data sheet for simple power-off:

- 1. Power off Main/Analog I/O (3.3 V)
- 2. Power off PRTCSS/Main I/O (1.8 V)
- 3. Power off PRTCSS/Main Core (1.35 V)

If **RESET** is low, steps 2 and 3 may be performed simultaneously.

If **RESET** is not low, these steps must be followed sequentially.

1.3 Power Solution

The proper connections for the power-on and power-off sequence are shown in Figure 2.

For power-on, an external system enable signal SYS_EN is enabled HIGH. Diodes D2, D3, and D4 are reversed biased. Diode D1 is forward biased and EN1.35 is HIGH. This turns ON the 1.35-V DCDC rail. The output voltage of the DCDC converter, VO_1.35, is filtered into the enable of the LDO2 converter, EN1.8, and creates an RC (R8 and C12) delay before turning ON the 1.8-V rail. When EN1.8 reaches the turn-on threshold of the converter, VO_1.8 ramps up to nominal voltage. The output voltage of the LDO2, VO_1.8, is filtered into the enable of the LDO1 converter, EN3.3, and creates an RC (R4 and C10) delay before turning ON the 3.3-V rail. When EN3.3 reaches the turn ON threshold of the converter, VO_3.3 ramps up to nominal voltage. Lastly, the output voltage of the LDO1 converter, VO_3.3, is coupled into the reset sense-fail pin of the TPS650061, RSTSNS. The RST_SNS signal is sensed through an internal comparator in the TPS650061 and triggers the RST signal HIGH when RSTSNS reaches 0.6 V and after a time delay dictated by C4. Power-on sequence is complete.


For power-off, SYS_EN is LOW. D2, D3, and D4 are forward biased. RSTSNS becomes LOW to pull RST LOW. EN3.3 becomes LOW and VO_3.3 ramps down. The EN1.8 signal is filtered to create an RC (R7 and C12) delay between VO_3.3 ramping down and VO_1.35 ramping down. Lastly, D1 is reversed biased and capacitor C11 discharges through resistor R1 with a delay longer than the ramping down of VO_3.3 and VO_3.3 and VO_1.8 are off, the 1.35-V rail ramps down. Power-off sequence is complete.



2 Schematic, Waveforms, and Bill of Materials

2.1 Schematic

Figure 2 shows the circuit schematic detailing the external components required by the TPS650061 to achieve the 1.35-, 1.8-, and 3.3-V power rails required by the 'DM368. In addition, Figure 2 shows the sequencing circuit that achieves the proper power-on, power-off, and reset sequencing required by the 'DM368.

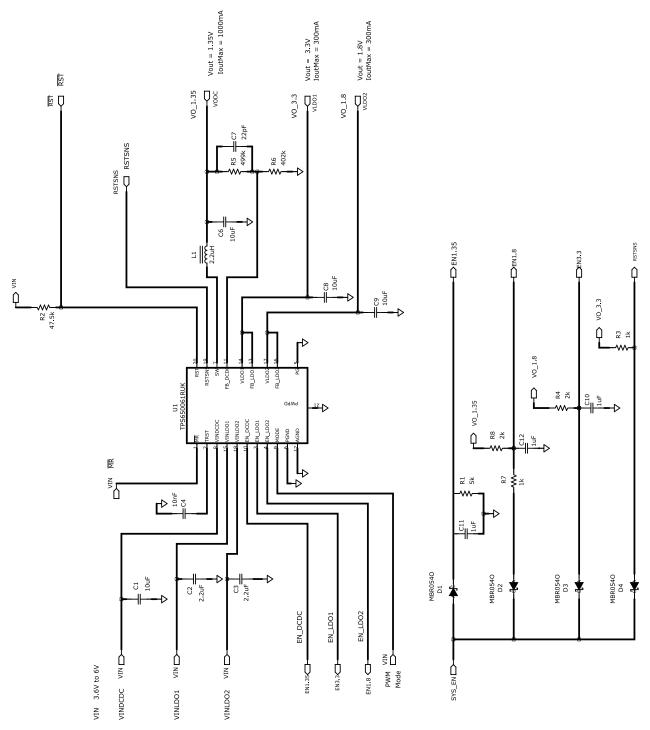





2.2 Waveforms

The following waveforms demonstrate the power-up and power-down sequence of the TPS650061 as required by the 'DM368. Figure 3 shows the TPS650061 power-on sequence where 1.35-V, then 1.8-V, and then 3.3-V rails ramp up when the system enable is HIGH.

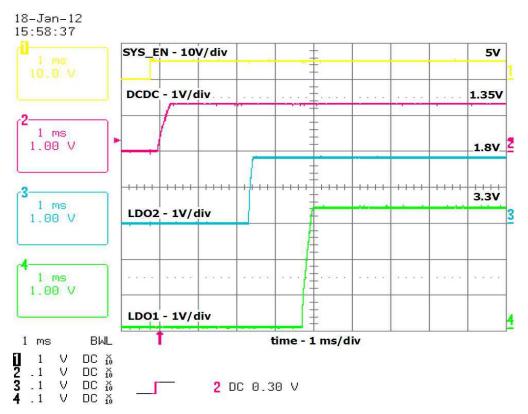


Figure 3. Power-Up Sequence With System Enable HIGH



Schematic, Waveforms, and Bill of Materials

www.ti.com

Figure 4 shows the reset pin, RST, being released after the rails have ramped up and after the reset recovery time, t_{RST} , is exceeded. The measurements were taken under a 1000-mA load on 1.35 V, 125-mA load on 1.8 V, and 146-mA load on 3.3 V.

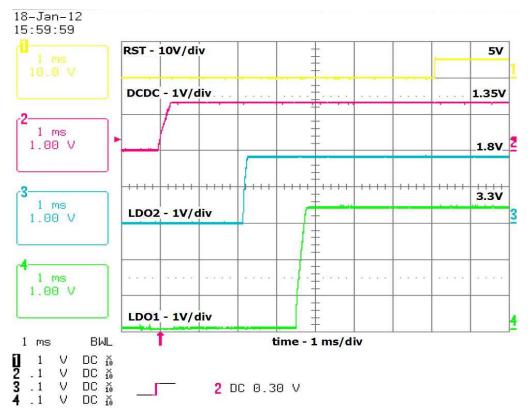


Figure 4. Power-Up Sequence and Reset Release

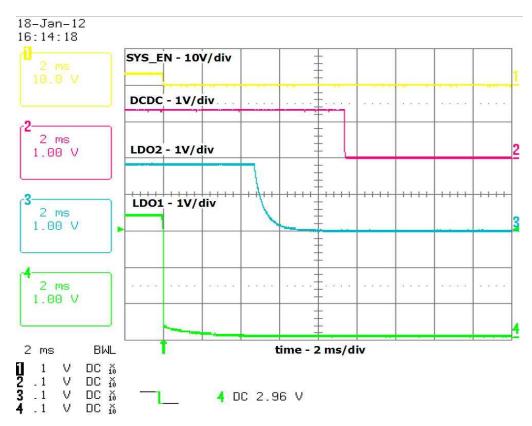


Figure 5. Power-Down Sequence With System Enable LOW

Figure 5 shows the power-down sequence of the 3.3-V, then 1.8-V, and then 1.35-V rails ramping down after system enable SYS_EN is pulled low. Figure 6 shows the reset pin being pulled low during power-off. The measurements were taken under a 1000-mA load at 1.35 V, 125-mA load at 1.8 V, and 146-mA load at 3.3 V.

Texas

www.ti.com

STRUMENTS



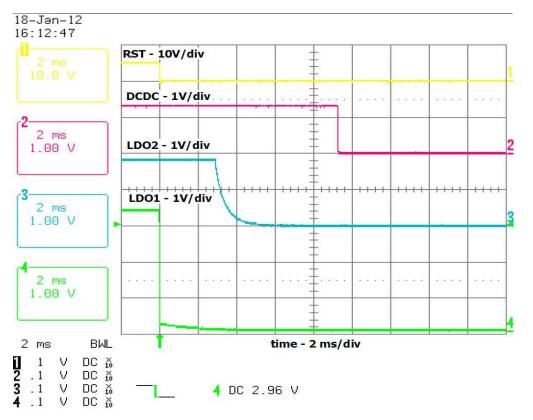


Figure 6. Power-Down Sequence and Reset Pulled LOW



2.3 Bill of Materials

The bill of materials is displayed in Table 2.

Table 2. Bill of Materials

Count	RefDes	Value	Description	Size	Part Number	MFR
1	C1	10 µF	Capacitor, ceramic, 10 V, X5R, 10%,	0805	GRM21BR61A106KE19L	Murata
1	C2	2.2 µF	Capacitor, ceramic, 10 V, X5R, 10%	0603	GRM188R61C225KE15D	Murata
1	C3	2.2 µF	Capacitor, ceramic, 10 V, X5R, 10%	0603	GRM188R61C225KE15D	Murata
1	C4	10 nF	Capacitor, ceramic, 16 V, X7R, 10%	0603	Std	Std
1	C6	10 µF	Capacitor, ceramic, 10 V, X5R, 10%,	0805	GRM21BR61A106KE19L	Murata
1	C7	22 pF	Capacitor, ceramic, 50 V, C0G, 5%	0603	Std	Std
1	C8	10 µF	Capacitor, ceramic, 10 V, X5R, 10%	0805	GRM21BR61A106KE19L	Murata
1	C9	10 µF	Capacitor, ceramic, 10 V, X5R, 10%	0805	GRM21BR61A106KE19L	Murata
1	C10	1 µF	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	TDK	TDK
1	C11	1 µF	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	TDK	TDK
1	C12	1 µF	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	TDK	TDK
1	D1	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Ser
1	D2	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Ser
1	D3	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Ser
1	D4	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Ser
1	L1	2.2 µH	Inductor, SMT, 2.0 A, 110 mΩ	0.118 x 0.118 inch	LPS3015-222ML	Coilcraft
1	R1	5 kΩ	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R2	47.5 kΩ	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R3	1 kΩ	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R4	2 kΩ	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R5	499 kΩ	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R6	402 kΩ	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R7	1 kΩ	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R8	2 kΩ	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	U1	TPS650061RUK	IC, 2.25-MHz step-down converter with dual LDOs and SVS	QFN	TPS650061RUK	ті

Notes: 1. These assemblies are ESD sensitive, ESD precautions shall be observed.

2. These assemblies must be clean and free from flux and all contaminants. Use of no clean flux is not acceptable.

3. These assemblies must comply with workmanship standards IPC-A-610 Class 2.

4. Ref designators marked with an asterisk (***) cannot be substituted. All other components can be substituted with equivalent MFG's components.

3 Conclusion

The TPS650061 provides a low-cost, comprehensive power solution for the 'DM368. A simple logic circuit controls the sequencing for each power rail. A 1.35-V rail (capable of supplying 1 A) is powered on, followed by a 1.8-V rail (300 mA), and then a 3.3-V rail (300 mA). Once all three supplies have reached regulation, RESET goes high (that is, rises to its pullup voltage). For power-down, the 3.3-V rail turns off, then the 1.8-V, and lastly the 1.35-V rail. This meets the power requirements of the 'DM368.

4 References

- 1. TMS320DM368, Digital Media System-on-Chip data sheet (SPRS668)
- 2. TPS650061, 2.25 MHz Step Down Converter with Dual LDOs and SVS data sheet (SLVS810)

EVALUATION BOARD/KIT/MODULE (EVM) ADDITIONAL TERMS

Texas Instruments (TI) provides the enclosed Evaluation Board/Kit/Module (EVM) under the following conditions:

The user assumes all responsibility and liability for proper and safe handling of the goods. Further, the user indemnifies TI from all claims arising from the handling or use of the goods.

Should this evaluation board/kit not meet the specifications indicated in the User's Guide, the board/kit may be returned within 30 days from the date of delivery for a full refund. THE FOREGOING LIMITED WARRANTY IS THE EXCLUSIVE WARRANTY MADE BY SELLER TO BUYER AND IS IN LIEU OF ALL OTHER WARRANTIES, EXPRESSED, IMPLIED, OR STATUTORY, INCLUDING ANY WARRANTY OF MERCHANTABILITY OR FITNESS FOR ANY PARTICULAR PURPOSE. EXCEPT TO THE EXTENT OF THE INDEMNITY SET FORTH ABOVE, NEITHER PARTY SHALL BE LIABLE TO THE OTHER FOR ANY INDIRECT, SPECIAL, INCIDENTAL, OR CONSEQUENTIAL DAMAGES.

Please read the User's Guide and, specifically, the Warnings and Restrictions notice in the User's Guide prior to handling the product. This notice contains important safety information about temperatures and voltages. For additional information on TI's environmental and/or safety programs, please visit www.ti.com/esh or contact TI.

No license is granted under any patent right or other intellectual property right of TI covering or relating to any machine, process, or combination in which such TI products or services might be or are used. TI currently deals with a variety of customers for products, and therefore our arrangement with the user is not exclusive. TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein.

REGULATORY COMPLIANCE INFORMATION

As noted in the EVM User's Guide and/or EVM itself, this EVM and/or accompanying hardware may or may not be subject to the Federal Communications Commission (FCC) and Industry Canada (IC) rules.

For EVMs **not** subject to the above rules, this evaluation board/kit/module is intended for use for ENGINEERING DEVELOPMENT, DEMONSTRATION OR EVALUATION PURPOSES ONLY and is not considered by TI to be a finished end product fit for general consumer use. It generates, uses, and can radiate radio frequency energy and has not been tested for compliance with the limits of computing devices pursuant to part 15 of FCC or ICES-003 rules, which are designed to provide reasonable protection against radio frequency interference. Operation of the equipment may cause interference with radio communications, in which case the user at his own expense will be required to take whatever measures may be required to correct this interference.

General Statement for EVMs including a radio

User Power/Frequency Use Obligations: This radio is intended for development/professional use only in legally allocated frequency and power limits. Any use of radio frequencies and/or power availability of this EVM and its development application(s) must comply with local laws governing radio spectrum allocation and power limits for this evaluation module. It is the user's sole responsibility to only operate this radio in legally acceptable frequency space and within legally mandated power limitations. Any exceptions to this are strictly prohibited and unauthorized by Texas Instruments unless user has obtained appropriate experimental/development licenses from local regulatory authorities, which is responsibility of user including its acceptable authorization.

For EVMs annotated as FCC – FEDERAL COMMUNICATIONS COMMISSION Part 15 Compliant

Caution

This device complies with part 15 of the FCC Rules. Operation is subject to the following two conditions: (1) This device may not cause harmful interference, and (2) this device must accept any interference received, including interference that may cause undesired operation.

Changes or modifications not expressly approved by the party responsible for compliance could void the user's authority to operate the equipment.

FCC Interference Statement for Class A EVM devices

This equipment has been tested and found to comply with the limits for a Class A digital device, pursuant to part 15 of the FCC Rules. These limits are designed to provide reasonable protection against harmful interference when the equipment is operated in a commercial environment. This equipment generates, uses, and can radiate radio frequency energy and, if not installed and used in accordance with the instruction manual, may cause harmful interference to radio communications. Operation of this equipment in a residential area is likely to cause harmful interference in which case the user will be required to correct the interference at his own expense.

FCC Interference Statement for Class B EVM devices

This equipment has been tested and found to comply with the limits for a Class B digital device, pursuant to part 15 of the FCC Rules. These limits are designed to provide reasonable protection against harmful interference in a residential installation. This equipment generates, uses and can radiate radio frequency energy and, if not installed and used in accordance with the instructions, may cause harmful interference to radio communications. However, there is no guarantee that interference will not occur in a particular installation. If this equipment does cause harmful interference to radio or television reception, which can be determined by turning the equipment off and on, the user is encouraged to try to correct the interference by one or more of the following measures:

- Reorient or relocate the receiving antenna.
- Increase the separation between the equipment and receiver.
- · Connect the equipment into an outlet on a circuit different from that to which the receiver is connected.
- Consult the dealer or an experienced radio/TV technician for help.

For EVMs annotated as IC – INDUSTRY CANADA Compliant

This Class A or B digital apparatus complies with Canadian ICES-003.

Changes or modifications not expressly approved by the party responsible for compliance could void the user's authority to operate the equipment.

Concerning EVMs including radio transmitters

This device complies with Industry Canada licence-exempt RSS standard(s). Operation is subject to the following two conditions: (1) this device may not cause interference, and (2) this device must accept any interference, including interference that may cause undesired operation of the device.

Concerning EVMs including detachable antennas

Under Industry Canada regulations, this radio transmitter may only operate using an antenna of a type and maximum (or lesser) gain approved for the transmitter by Industry Canada. To reduce potential radio interference to other users, the antenna type and its gain should be so chosen that the equivalent isotropically radiated power (e.i.r.p.) is not more than that necessary for successful communication.

This radio transmitter has been approved by Industry Canada to operate with the antenna types listed in the user guide with the maximum permissible gain and required antenna impedance for each antenna type indicated. Antenna types not included in this list, having a gain greater than the maximum gain indicated for that type, are strictly prohibited for use with this device.

Cet appareil numérique de la classe A ou B est conforme à la norme NMB-003 du Canada.

Les changements ou les modifications pas expressément approuvés par la partie responsable de la conformité ont pu vider l'autorité de l'utilisateur pour actionner l'équipement.

Concernant les EVMs avec appareils radio

Le présent appareil est conforme aux CNR d'Industrie Canada applicables aux appareils radio exempts de licence. L'exploitation est autorisée aux deux conditions suivantes : (1) l'appareil ne doit pas produire de brouillage, et (2) l'utilisateur de l'appareil doit accepter tout brouillage radioélectrique subi, même si le brouillage est susceptible d'en compromettre le fonctionnement.

Concernant les EVMs avec antennes détachables

Conformément à la réglementation d'Industrie Canada, le présent émetteur radio peut fonctionner avec une antenne d'un type et d'un gain maximal (ou inférieur) approuvé pour l'émetteur par Industrie Canada. Dans le but de réduire les risques de brouillage radioélectrique à l'intention des autres utilisateurs, il faut choisir le type d'antenne et son gain de sorte que la puissance isotrope rayonnée équivalente (p.i.r.e.) ne dépasse pas l'intensité nécessaire à l'établissement d'une communication satisfaisante.

Le présent émetteur radio a été approuvé par Industrie Canada pour fonctionner avec les types d'antenne énumérés dans le manuel d'usage et ayant un gain admissible maximal et l'impédance requise pour chaque type d'antenne. Les types d'antenne non inclus dans cette liste, ou dont le gain est supérieur au gain maximal indiqué, sont strictement interdits pour l'exploitation de l'émetteur.

[Important Notice for Users of this Product in Japan]

This development kit is NOT certified as Confirming to Technical Regulations of Radio Law of Japan

If you use this product in Japan, you are required by Radio Law of Japan to follow the instructions below with respect to this product:

- Use this product in a shielded room or any other test facility as defined in the notification #173 issued by Ministry of Internal Affairs and Communications on March 28, 2006, based on Sub-section 1.1 of Article 6 of the Ministry's Rule for Enforcement of Radio Law of Japan,
- 2. Use this product only after you obtained the license of Test Radio Station as provided in Radio Law of Japan with respect to this product, or
- 3. Use of this product only after you obtained the Technical Regulations Conformity Certification as provided in Radio Law of Japan with respect to this product. Also, please do not transfer this product, unless you give the same notice above to the transferee. Please note that if you could not follow the instructions above, you will be subject to penalties of Radio Law of Japan.

Texas Instruments Japan Limited (address) 24-1, Nishi-Shinjuku 6 chome, Shinjuku-ku, Tokyo, Japan

http://www.tij.co.jp

【ご使用にあたっての注】

本開発キットは技術基準適合証明を受けておりません。

本製品のご使用に際しては、電波法遵守のため、以下のいずれかの措置を取っていただく必要がありますのでご注意ください。

- 1. 電波法施行規則第6条第1項第1号に基づく平成18年3月28日総務省告示第173号で定められた電波暗室等の試験設備でご使用いただく。
- 2. 実験局の免許を取得後ご使用いただく。
- 3. 技術基準適合証明を取得後ご使用いただく。

なお、本製品は、上記の「ご使用にあたっての注意」を譲渡先、移転先に通知しない限り、譲渡、移転できないものとします。

上記を遵守頂けない場合は、電波法の罰則が適用される可能性があることをご留意ください。

日本テキサス・インスツルメンツ株式会社 東京都新宿区西新宿6丁目24番1号 西新宿三井ビル http://www.tij.co.jp

EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMERS

For Feasibility Evaluation Only, in Laboratory/Development Environments. Unless otherwise indicated, this EVM is not a finished electrical equipment and not intended for consumer use. It is intended solely for use for preliminary feasibility evaluation in laboratory/development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical mechanical components, systems and subsystems. It should not be used as all or part of a finished end product.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

- 1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
- 2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
- 3. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.
- 4. You will take care of proper disposal and recycling of the EVM's electronic components and packing materials.

Certain Instructions. It is important to operate this EVM within TI's recommended specifications and environmental considerations per the user guidelines. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output are maintained at a normal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch. As with all electronic evaluation tools, only qualified personnel knowledgeable in electronic measurement and diagnostics normally found in development environments should use these EVMs.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of the agreement. This obligation shall apply whether Claims arise under law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate the components for possible use in safety critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2012, Texas Instruments Incorporated

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Security	www.ti.com/security
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com		
OMAP Mobile Processors	www.ti.com/omap		
Wireless Connectivity	www.ti.com/wirelessconnectivity		
	TI 505 0		

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2012, Texas Instruments Incorporated