

# Achieving high-DC Precision and Wide Large Signal Bandwidth with Hi-Z Buffers

---



Leapfar Castro


To reliably capture high-frequency signals and fast transient pulses, wide-bandwidth data acquisition systems like oscilloscopes and active probes require high-performance analog front-end (AFE) signal chains that must be able to:

- Support 1 V<sub>PP</sub> signals (at least) to ensure a high signal-to-noise ratio.
- Support DC to 500 MHz of high input-impedance (Hi-Z) to prevent loading of the device under test.
- Offer low noise and distortion to maintain high signal fidelity.
- Deliver high DC precision.

One way to overcome these design challenges is to create a composite loop-based approach that interleaves the low- and high-frequency signal chain in order to get DC precision and a wide large signal bandwidth.

---

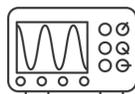
## Achieve ASIC-level performance with the BUF802



Learn how to more reliably capture high-frequency signals and fast transient pulses in wide-bandwidth acquisition systems in the video, "[BUF802: Wide-bandwidth, high-input impedance JFET buffer.](#)"

---

Given the complexity of implementing a composite loop-based circuit that meets system requirements, engineers usually have to either design custom application-specific integrated circuits (ASICs) or use multiple discrete components, as shown in [Figure 1](#). Both options have drawbacks, including the need for specialized expertise with ASICs and additional design complexity. The two approaches also have trade-offs in terms of performance and cost: discrete implementations are less expensive than ASICs but cannot match their level of performance.

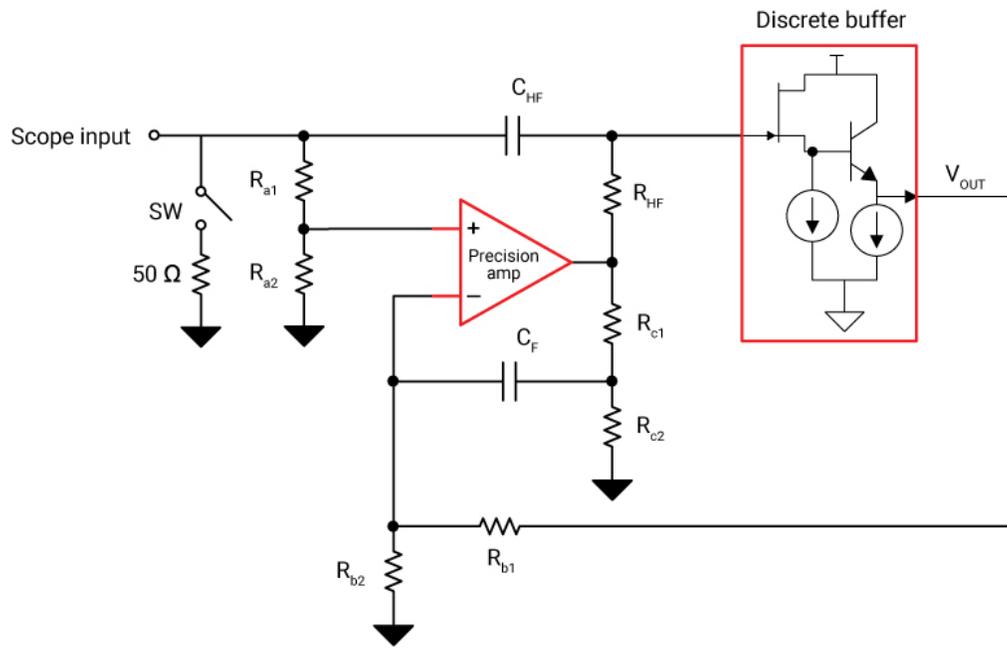


**Figure 1. Discrete Buffer Composite Loop with a Precision Amplifier AFE**

In this article, I'll explore the design challenges of discrete buffer composite loop implementations versus a single-chip implementation with the [BUF802](#) Hi-Z buffer.

### A Discrete Buffer Composite Loop Architecture

The discrete implementation of the Hi-Z AFE in [Figure 1](#) uses a precision amplifier and a discrete junction field-effect transistor (JFET)-based source follower circuit configured in a composite loop. The loop splits the input signal into low- and high-frequency components, taking both components to the output through two different circuits (transfer functions) and recombining them to reproduce a net output signal, as shown in [Figure 2](#).

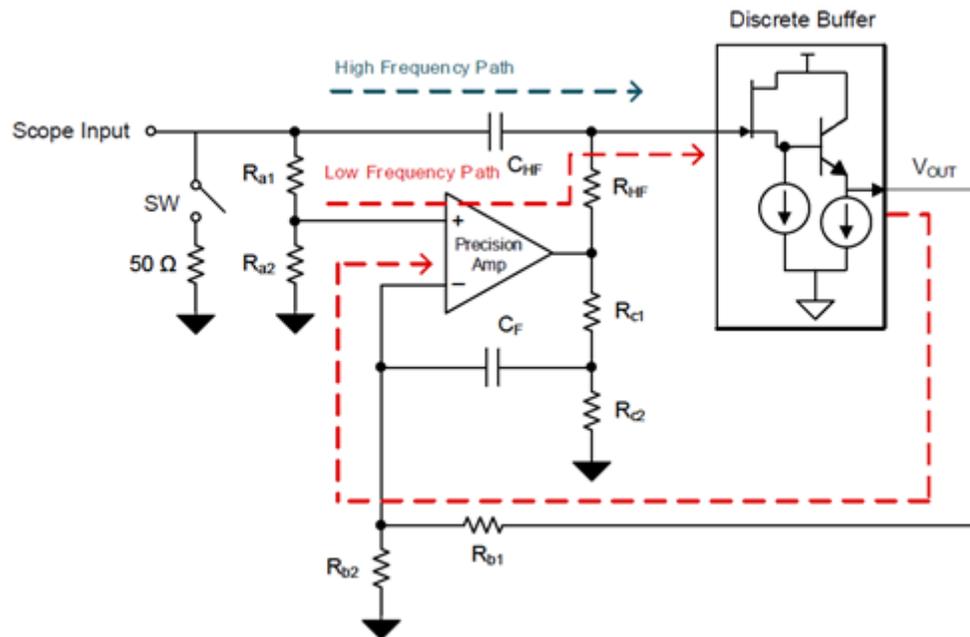


**Figure 2. Discrete Composite Loop Low- and High-frequency Paths**

The low-frequency path gives the net transfer function good DC precision, whereas the JFET source follower-based high-frequency path enables the net transfer function to have a wide large signal bandwidth, as well as low noise and distortion. One of the main challenges with the circuit shown in Figure 2 is achieving smooth interleaving of the two paths to ensure a flat frequency response. Any mismatch in the transfer function of the two paths will lead to discontinuity in the net transfer function frequency response resulting in a loss of signal fidelity.

### The Goal of a Composite Loop Architecture


At DC or low frequencies,  $C_{HF}$  (high-frequency capacitor) is open and the voltage output ( $V_{OUT}$ ) is controlled by the precision amplifier in the low-frequency path. The ratio of the alpha and beta resistor network controls the DC or low-frequency gain.

At high frequencies,  $C_{HF}$  short circuits, and the precision amplifier runs out of bandwidth given the limited gain- bandwidth product. The discrete buffer operates as a JFET source and a negative-positive-negative emitter follower determines  $V_{OUT}$ . The discrete buffer stage, referred to as gain (G) in Figure 3, determines the high-frequency path gain.

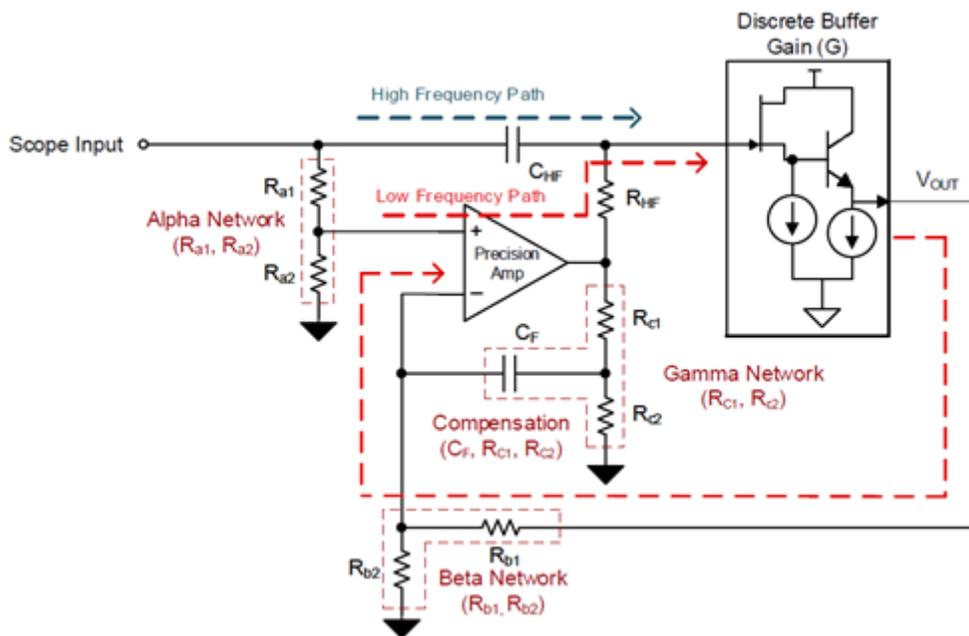

**Figure 3. Discrete Buffer Composite Loop Architecture**

At mid-frequencies, since both the low- and high-frequency paths determine the output, careful tuning of individual gain and interaction of poles and zeros is important to ensure a flat frequency response. Gain equalization at mid-frequencies is challenging to implement since the same components,  $C_{HF}$  and  $R_{HF}$  (high-frequency resistor) determine the poles of the low- and high frequency paths, as shown in Figure 4.

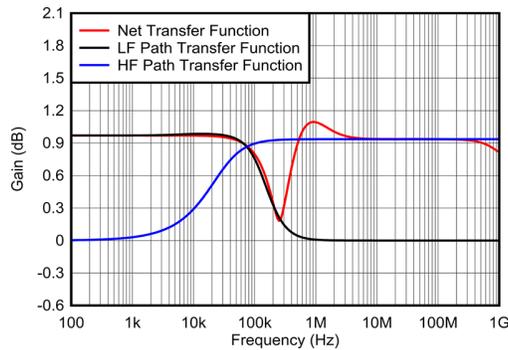


**Figure 4. Discrete Buffer Frequency Response**

The composite loop should have a flat frequency response and a high crossover frequency region in order to achieve low  $1/f$  noise and fast overdrive recovery.

### The Complexities of a Discrete Implementation

Given the interdependency of the low- and high-frequency paths, as shown in Figure 5, the values of  $C_{HF}$  and  $C_F$  (compensation capacitor) are in tens of nanofarads in order to achieve a flat frequency response. But these values cause a crossover frequency range of tens to hundreds of hertz, which can limit the DC noise performance of the signal chain.

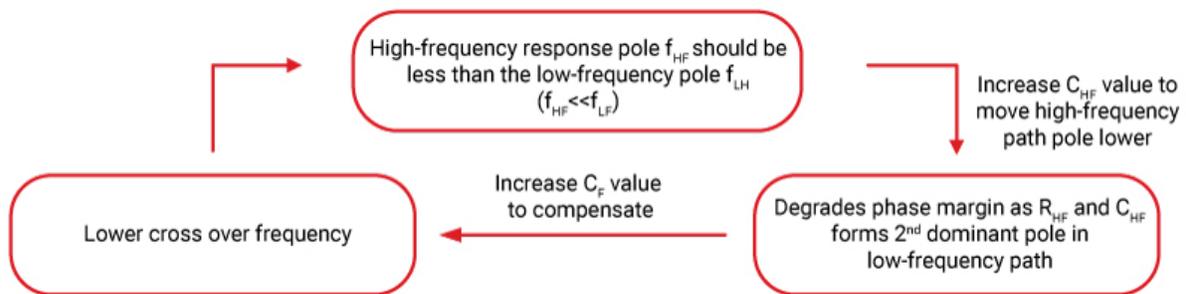


**Figure 5. Interdependency of the Low- and High-frequency Paths**

Another challenge when implementing the composite loop discretely is that the pole from the precision amplifier's open-loop gain and the pole from the resistor-capacitor network of  $R_{HF}$  and  $C_{HF}$  contributes to the two-pole network in the low-frequency path, resulting in instability. The implementation of an additional network across the precision amplifier (labeled the gamma network in Figure 3) will compensate for that instability, but will require tuning in order to achieve a flatter frequency response, further adding to the complexity of creating a smooth frequency response across the operating range.

### Implementing a Composite Loop with the BUF802

Since one of the major limitations of implementing a discrete composite loop is the interdependency between the low- and high-frequency paths and the need for an additional gamma network for compensation, the BUF802 has an auxiliary path internal to the device. Connecting the output of the precision amplifier to the auxiliary path creates a composite loop while ensuring isolation between the low- and high-frequency paths. Isolating the different frequency paths creates a higher crossover frequency region and eliminates the gamma network and compensation circuitry. The low- and high-frequency signal components recombine inside the BUF802 and are reproduced at the OUT pin, as shown in Figure 6.

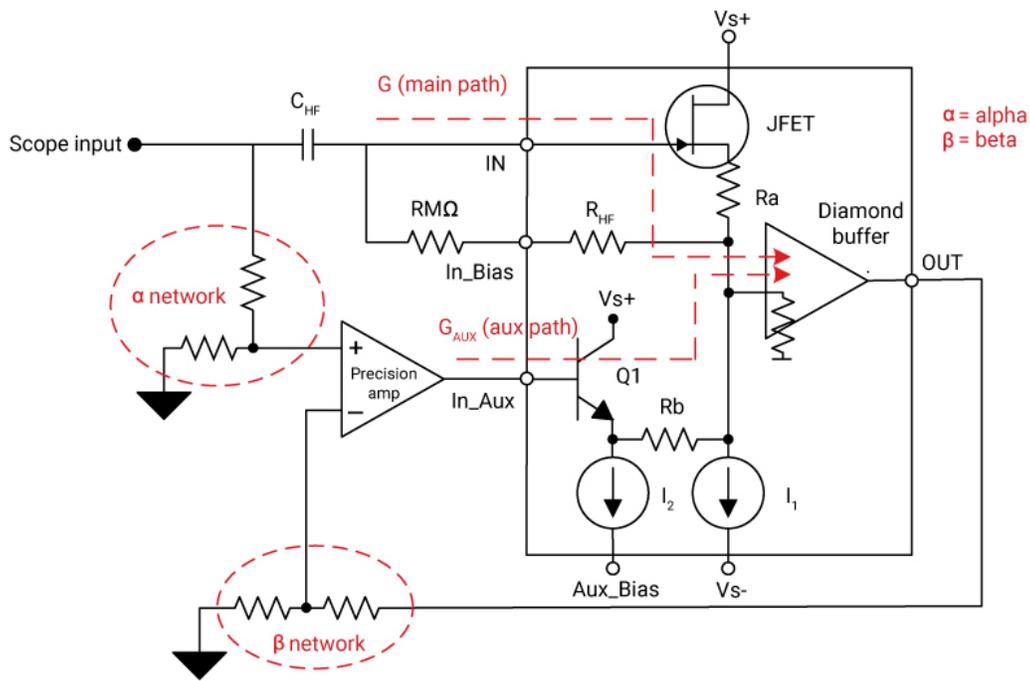

**Figure 6. Composite loop precision amplifier with an internal BUF802**

### Conclusion

An integrated Hi-Z buffer such as the BUF802 helps solve the complex challenges of a composite loop-based implementations. The BUF802's integrated protection features like input/output clamps help protect subsequent stages in the signal chain, reduce overdrive recovery time and input capacitance, and increase system reliability.

When considering an AFE for today's applications, you must also keep in mind future measurement needs, which usually require additional bandwidth. This bandwidth can go a long way in both measurement accuracy and ensuring system design investments stay relevant for future test requirements.

### Additional Resources

- [The Application Information section of the BUF802 data sheet](#) has detailed analysis and calculations for discrete component selection to achieve a flat frequency response.
- Read the application note, "[How to Tune the S-Parameters of Your Analog Front-End Signal Chain.](#)"

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated