

Eric Faraci

When I first got into cooking, I preferred to do it alone, thinking that having anyone else in the kitchen was a distraction. But as I started to cook more complicated recipes with multiple steps, I found that having a second pair of hands was invaluable and made the experience more fun. The saying is true: if you can't beat them, join them.

The same principle applies with the active clamp flyback.

Everyone wants a smaller AC/DC converter, especially when it's for their phone or tablet charger. Due to its simplicity, the flyback converter is the topology of choice, since it effectively converts AC to DC with few components. But there are limits to how small a flyback can be, since the losses associated with the leakage inductance of the transformer limit the practical size. Until now, every design has fought it by minimizing this leakage inductance. But the active clamp flyback breaks this cycle.

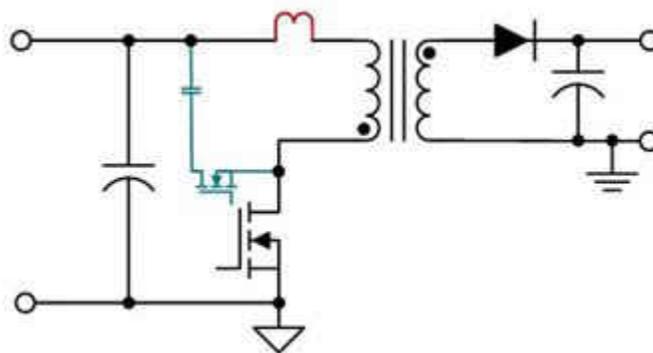


Figure 1. Active Clamp Flyback with Leakage Inductance in Red and Active Clamp in Blue

Rather than fighting the leakage inductance by dissipating the energy in a resistor-capacitor-diode (RCD) or Zener clamp, an active clamp stores the energy and delivers it to the output. Intelligently controlling the clamp also provides zero voltage switching. This eliminates two major sources of loss, enabling the size to be drastically reduced. If you were to use gallium nitride (GaN) field-effect transistors (FETs) with their lower output capacitance and on-state resistance, the size of the adapter can be cut in half!

But the devil is in the details, since if the active clamp is not intelligently controlled, it will actually make the efficiency worse. The active clamp flyback had been only a pipe-dream, since there was no controller intelligent enough to enable this topology. But this has changed with the UCC28780. This active clamp flyback controller is specifically designed to work with silicon (Si)- or GaN-based power stages, making this topology a reality for any design. The UCC24612 synchronous rectifier enables compliance with U.S. Department of Energy (DoE) Level VI or Code of Conduct (CoC) Tier 2.

Additional Resources

- Learn more about TI's new active clamp flyback controller by checking out the:
 - [UCC28780EVM-002](#), a 45W GaN-based evaluation module with a power density of 22.5W/in³ and a peak efficiency above 94%.
 - [High Efficiency, High Power Density Active Clamp Flyback Adapter with SJ FET Reference Design](#), a USB Power Delivery programmable power supply-compliant design with a 6.2V/5A to 9V/5A output.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated