

# Why a Wide VIN DC/DC Converter Is a Good Fit for High-cell-count Battery-powered Drones



Lujian Huang

More and more [drone](#) applications require high-cell-count [battery packs](#) to support longer flying distances and flight times. For example, consider a 14-series lithium-ion (Li-ion) battery pack architecture where the working voltage is 50V to 60V. When designing a DC/DC power supply for such a system, one of the challenges is how to select the maximum input voltage rating. Some engineers see an oversized voltage excursion at the node designated  $V_M$  in [Figure 1](#), but may not be aware of its origin or how to deal with it.

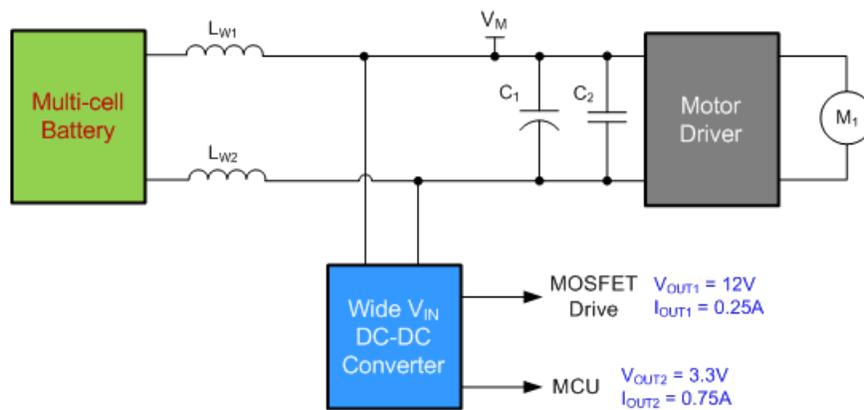


Figure 1. Drone System Block Diagram

First, let me explain the modes of operation of a [motor driver](#). As shown schematically in [Figure 2](#), the battery stack powers a brushed-DC (BDC) motor,  $M_1$ , through the forward current path designated as loop 1, and electric power converts to the motor's rotational kinetic energy during this period. Conversely, when the motor decelerates or changes its direction of rotation, it acts as a generator; the resulting [back electromotive force \(EMF\)](#) returns energy to the input through the driver via current loop 2.

Although this action may seem advantageous in terms of improving overall system efficiency, the regenerative behavior can result in a large reverse current and consequent voltage overshoot at the supply input.

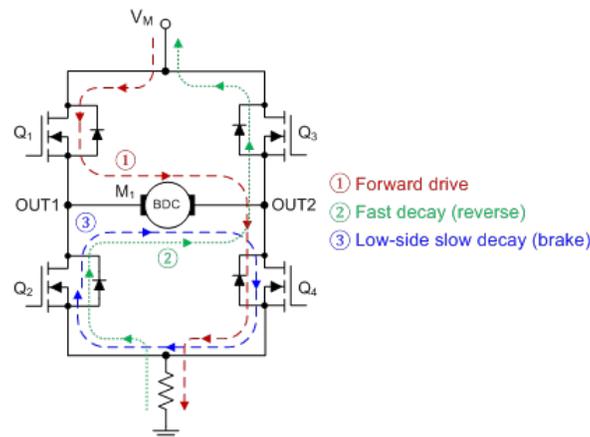


Figure 2. Forward Current Paths of a BDC Motor H-bridge Driver

Table 1 outlines typical voltage-rating margins for different motor types. The overshoot voltage range (relative to the nominal battery operating voltage) also depends on the drone’s flight dynamics and control algorithm for the thrust and direction change of each propeller.

**Table 1. Motor Driver Voltage Rating Requirements**


| Motor type    | Voltage rating margin        | Remarks  |
|---------------|------------------------------|--|
| BDC motor     | 1.5x to 2x $V_{BATT(nom)}$   | $V_M$ pumping effect may occur during deceleration, stop or direction change   |
| BLDC motor    | 1.5x to 2.5x $V_{BATT(nom)}$ | $V_M$ pumping is higher given that a brushless DC (BLDC) motor usually has higher power density than an equivalent BDC motor |
| Stepper motor | 1.2x to 2x $V_{BATT(nom)}$   | $V_M$ pumping exists when a motor stall is missed and the motor loses its synchronization with the controller                |

In order to manage this voltage overshoot and ensure that the system runs safely, you can use an electrolytic bulk capacitor for  $C_1$  to absorb the energy or, alternatively, add a transient voltage suppressor (TVS) diode to clamp the voltage to a safe range.

Take the [Rubycon 2200µF/63V](#) electrolytic capacitor, for example. Its diameter and height are 18mm and 33mm, respectively – quite large to go in a drone implementation where footprint and profile are important constraints. The 1,000-unit price of this capacitor is more than \$1.00 from a distributor such as Digi-Key. More important is that this electrolytic capacitor, with its finite rated lifetime, represents an acknowledged limitation in terms of system reliability and robustness. A TVS clamp also creates space, cost and reliability concerns for the whole system.

Another option is to use a [DC/DC converter solution](#) with a wide input voltage range and high-line transient immunity to accommodate the full voltage excursion during the motor’s regenerative action.

Selecting a converter with a wide  $V_{IN}$  range, such as the [LM5161 100V, 1A synchronous buck converter](#) from TI (see [Figure 3](#)) enables you to eliminate the bulk energy storage or TVS clamp, saving time, cost and board space. Moreover, the LM5161 converter offers a large degree of flexibility in terms of platform design. Not only does it support a non-isolated output, but the converter can also deliver one or more isolated outputs – using a [Fly-Buck™](#) circuit implementation – if it’s necessary to break a ground loop or decouple different voltage domains in the drone system. If a VCC bias rail between 9V and 13V is available, the LM5161’s input quiescent current reduces to 325µA at a 50V input to uphold battery life during standby operating conditions.

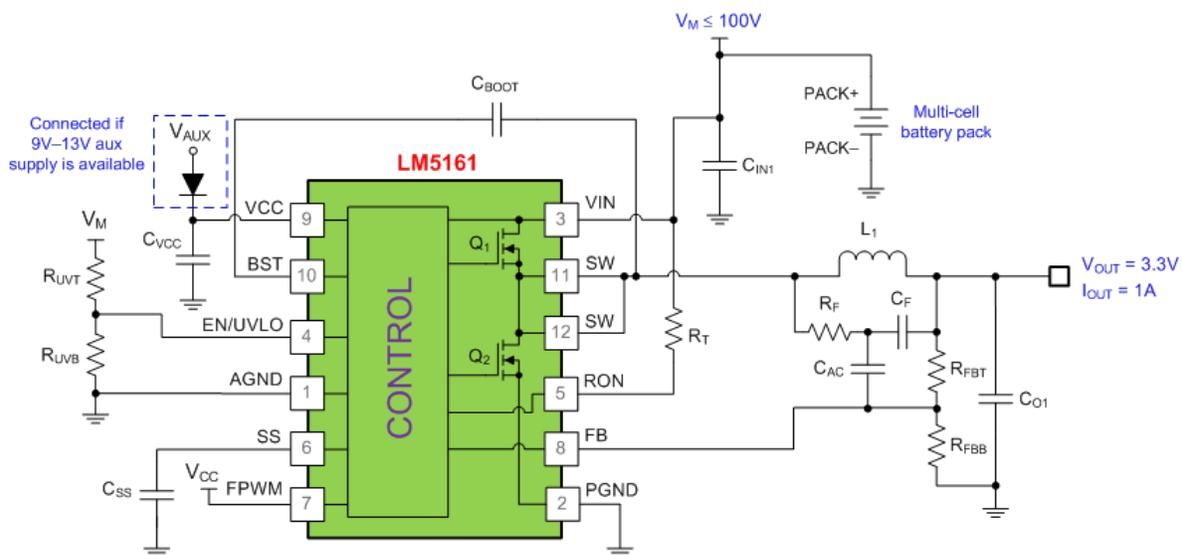

**Figure 3. LM5161 Step-down Converter Schematic**

## Summary

Amid a continual focus on high reliability, small size and low overall bill-of-materials cost, a wide  $V_{IN}$  synchronous buck converter dovetails seamlessly into a variety of power-management circuits for drone applications. A proposed DC/DC converter conveniently provides high efficiency performance, topology flexibility and increased circuit robustness during transient voltage events when mechanical energy from the motor cycles back to the input supply.

## Additional Resources

- Order the [evaluation module](#) for the LM5161 100V synchronous buck converter.
- Download the LM5161 [quickstart calculator](#).
- Peruse these reference designs for drones:
  - [Non-Military Drone, Robot or RC 2S1P Battery Management Solution Reference Design](#).
  - [Sensorless High-Speed FOC Reference Design for Drone ESC](#).
  - [4.4 V to 30 V, 15 A, High Performance Brushless DC Drone Propeller Controller Reference Design](#).
  - [High Density Efficient Solution for Main Aux As Well As Back Up Aux Power in Drones](#).”
- Review the white paper, “[Valuing wide  \$V\_{IN}\$ , low EMI synchronous buck circuits for cost-driven, demanding applications](#).”

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated