

Crafty Idea: Create a 150V Non Synchronous Buck Solution with a Lower VIN Rated Controller



David Baba

Many applications today require an input-voltage rating beyond the V_{IN} max ratings of many DC-to-DC controllers. Traditional options include using expensive front-end protection or implementing a low-side gate-drive device, which means employing an isolated topology such as a flyback converter. Isolated topologies often require custom magnetics and increase design complexity and cost compared to a nonisolated approach.

But another alternative exists that enables you to resolve the issue by using a simple buck controller with a V_{IN} max less than the system input voltage. How is this possible?

Buck controllers typically derive a bias supply referenced from ground potential (0V) (Figure 1a). The bias supply is derived from the input; therefore, the device needs to withstand the full V_{IN} potential. However, P-channel buck controllers have the gate-drive supply referenced to V_{IN} (Figure 1b), because the gate-drive voltage required to turn on the P-channel metal-oxide semiconductor field-effect transistor (MOSFET) is at V_{GS} below V_{IN} . To turn off the P-channel MOSFET, the gate voltage simply goes to V_{IN} (0V V_{GS}) (Figure 2).

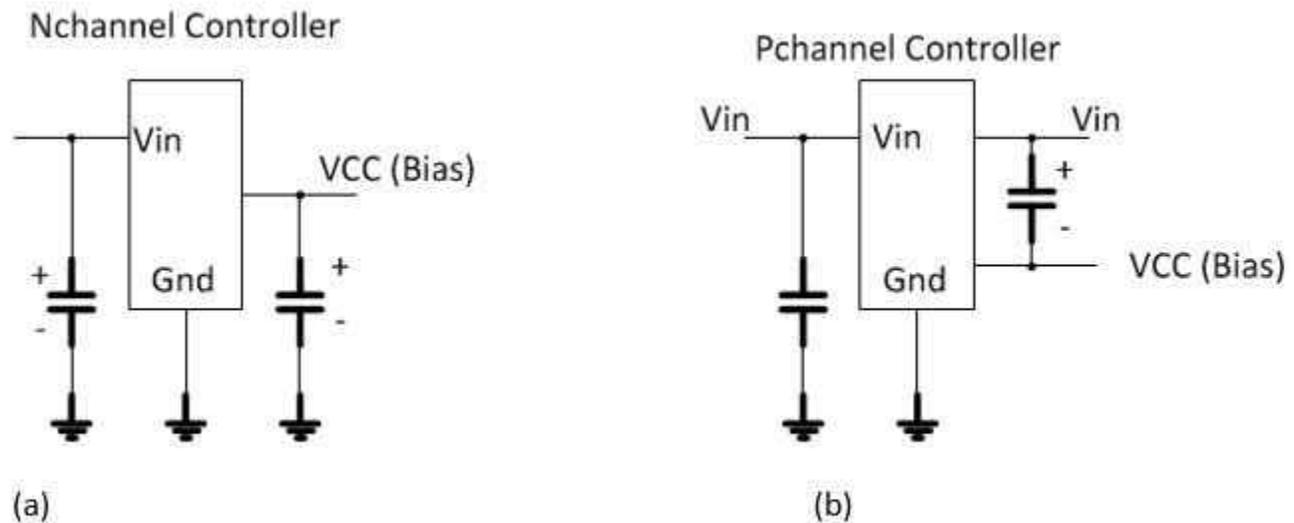


Figure 1. VCC Bias Generation for N-channel (a); and P-channel Controllers (b)

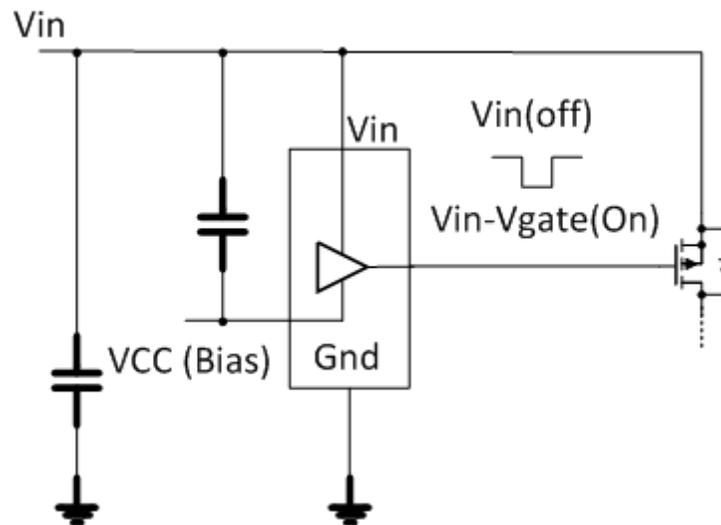


Figure 2. Gate Drive for a P-Channel Controller

The fact that the nonsynchronous P-channel controller derives its bias supply to drive the P-channel gate in this way is a huge benefit and makes it possible to supply a virtual ground that floats above a 0V potential. For an N-channel high side MOSFET the voltage is derived from a supply that is referenced to ground. This is charge pumped using a boot capacitor and diode to supply a gate voltage higher than its source potential of V_{IN} . With a P-channel high side MOSFET, things are a lot simpler. To turn on the P-channel MOSFET, the gate potential needs to be lower than its source potential of V_{IN} . Therefore the supply is referenced to V_{IN} only and not V_{IN} and ground as described above.

Floating Ground

How can you create a floating ground for the controller? It's quite simple: by using an emitter follower. [Figure 3](#) shows a basic implementation of such a scheme. The emitter of the P-channel N-channel P-channel (PNP) will sit at a potential that is V_{be} ($\sim 0.7V$) below the Zener diode voltage potential (V_z). In essence, you're floating the controller to V_{IN} and regulating the reference of the controller to limit the voltage between V_{IN} and the device ground.

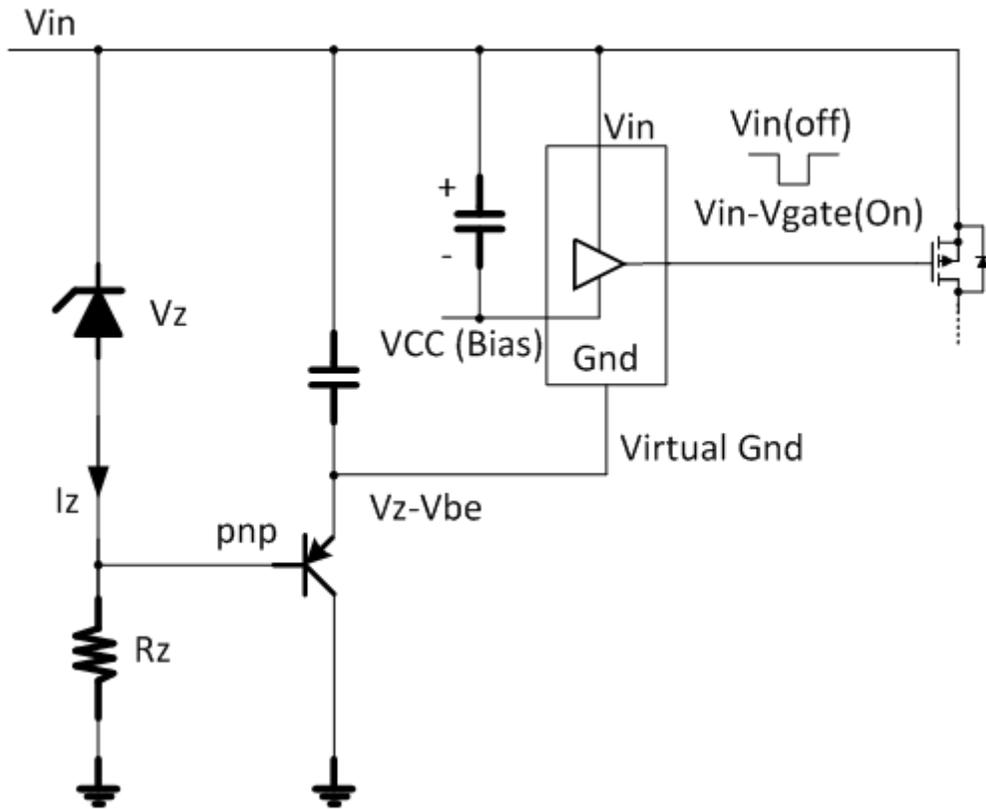


Figure 3. Creating a Virtual Ground Using a Simple Emitter Follower Scheme

Output-voltage Translation

There is one challenge to overcome. Because the controller is sitting on a virtual ground ($V_z - V_{be}$) and generating a step-down output voltage that is referenced to ground (0V) potential, how are you going to translate the output-voltage signal to a feedback voltage (typically between 0.8V and 1.25V) sitting above a virtual ground? Figure 4 illustrates the challenge.

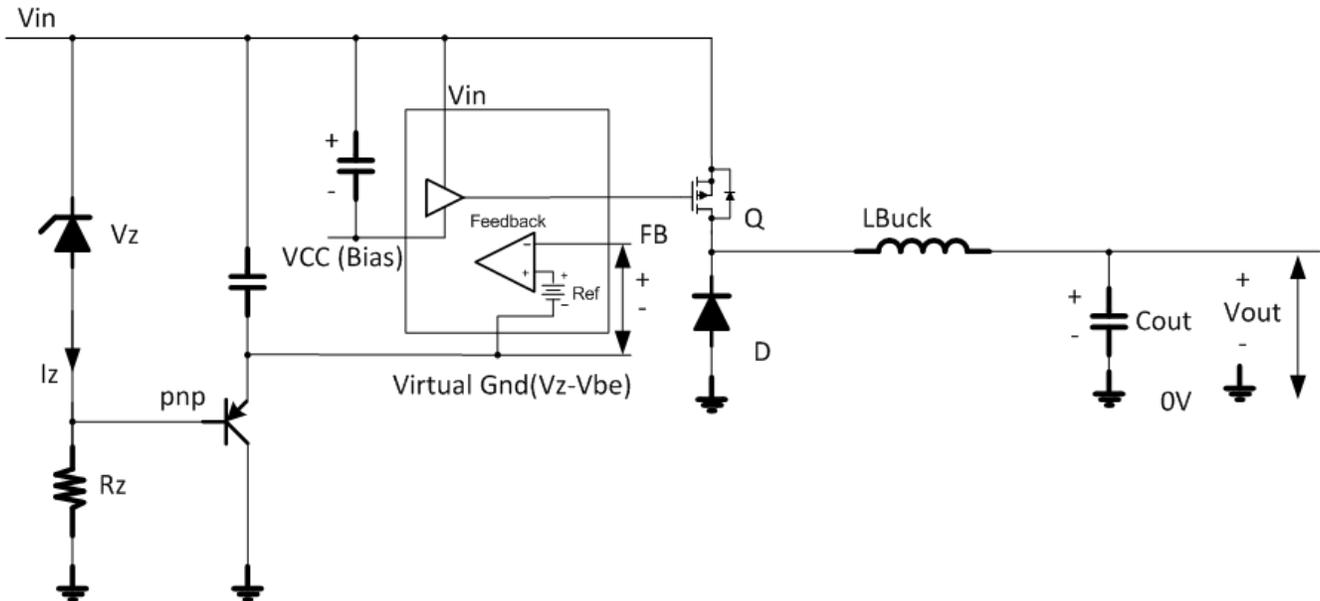


Figure 4. Schematic Showing the Difference in Voltage Potential between v_{OUT} (Referenced to 0V Ground) and the Feedback Voltage of a Controller (Referenced to Virtual Ground)

To close the loop, you can implement [Figure 5](#) by using a couple of matched-pair transistors. One pair sends the feedback signal to V_{IN} ; the other matched pair generates a current from V_{IN} to a potential above the virtual ground.

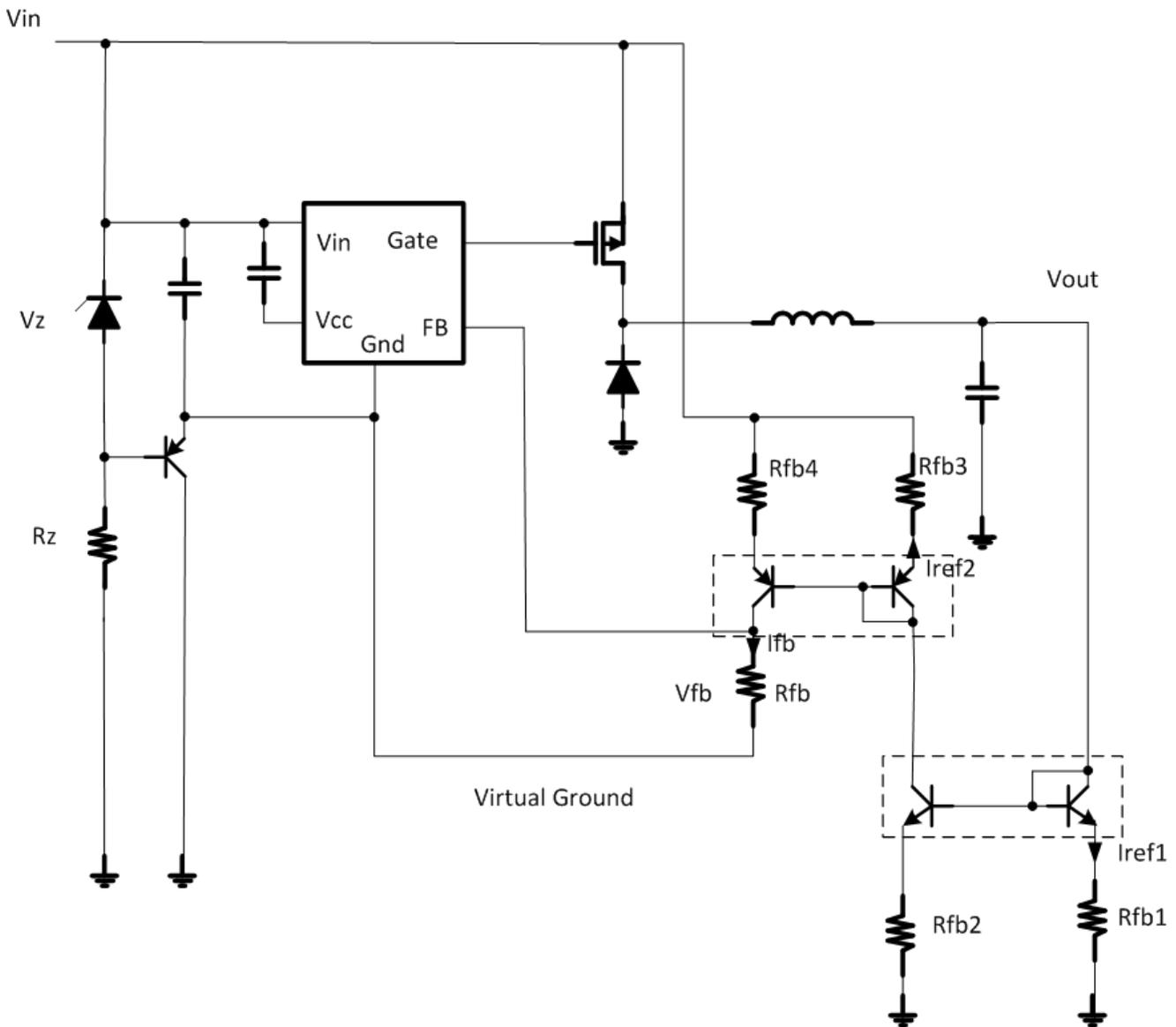


Figure 5. High-level Schematic of a Nonsynchronous Controller and Feedback Implementation Using Matched-pair Transistors

Putting It All Together

The LM5085 is ideal for the application I've described because it is a P-channel nonsynchronous controller whose VCC bias supply is referenced to V_{IN} . The LM5085 can withstand input voltages up to $75V_{IN}$ in traditional applications. For applications with input transient voltages much higher than $75V$, consider the solution presented here, specified for an output of 12V.

Starting from the controller feedback voltage of 1.25V and using a current to generate the feedback (I_{fb}) set to 1mA, calculate the R_{fb} value using [Equation 1](#):

$$R_{fb} = \frac{V_{fb}}{I_{fb}} \quad (1)$$

(1)

where $R_{fb} = 1.25k$.

R_{fb1} sets the reference current for the current mirrors. Once again, with 1mA as the reference current and using Equation 2, calculate R_{fb1} to set the output voltage:

$$R_{fb1} = \frac{V_{out} - V_{be}}{I_{fb1}} \quad (2)$$

where $V_{OUT} = 12V$, $R_{fb1} = 11.3k$ and V_{be} is $\sim 0.7V$.

With 1mA flowing into R_{fb2} and the emitter current being approximately equal to the collect current ($I_e \sim I_c$), this sets the reference current I_{ref2} . The loop is closed and the voltage will regulate to the set voltage described.

Output Voltage Regulation

One possible application this idea is suitable for is when voltage transients are significantly higher than the absolute maximum of the LM5085. The LM5085 is a constant on-time (COT) controller; as such, its on-time (T_{on}) is inversely proportional to V_{IN} . However, when clamping the V_{IN} to the LM5085, T_{on} will no longer adjust with increasing V_{IN} (to the power stage) because the device will have a fixed voltage set by the Zener diode while the V_{in} to the power stage is increasing. This will cause the frequency to drop as the input voltage to the power stage increases beyond the clamping voltage to the LM5085; the regulation voltage may begin to increase slightly as a result. Therefore, take care to size the ripple-injection voltage using a Type 1 ripple-injection scheme, thus ensuring that the ripple is set within acceptable limits to maintain stability and minimize error on the output from increasing ripple.

Example Schematic

Figure 6 shows an example schematic of a 48V supply with an absolute maximum V_{IN} rating of 150V. The example board can deliver $12V_{OUT}$ at 3A.

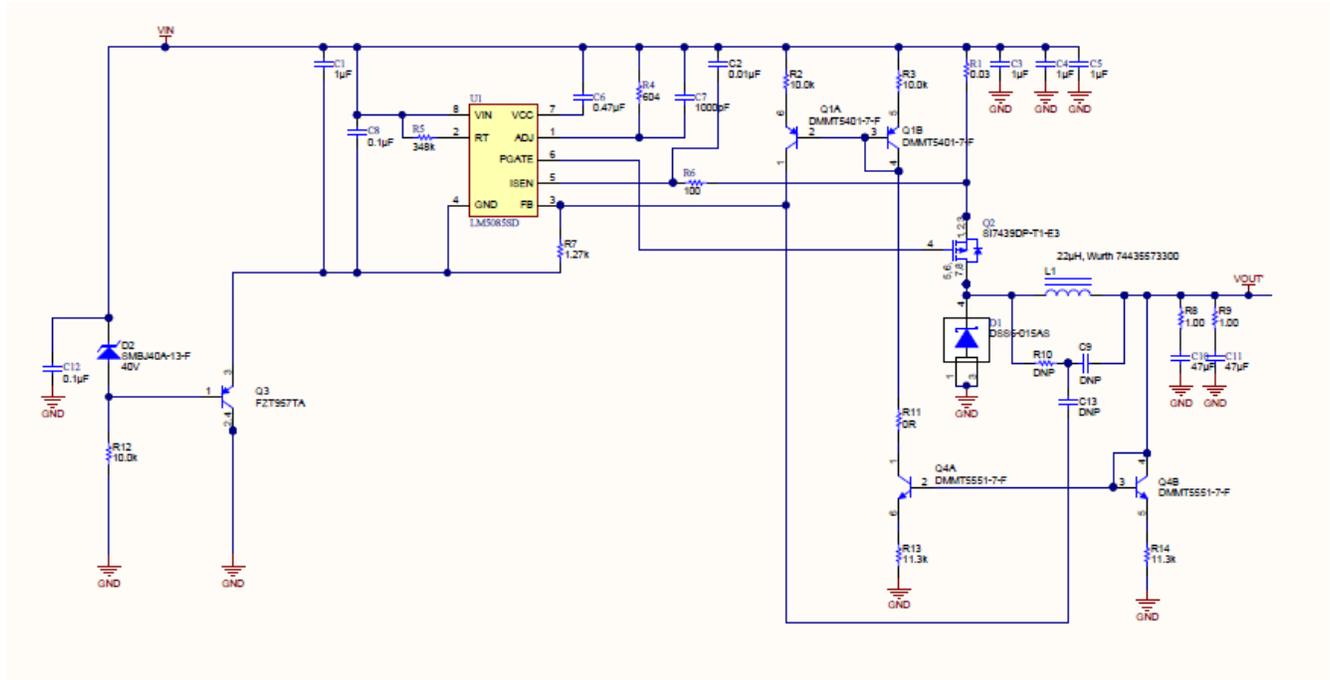


Figure 6. A 24V to 150V_{IN} (Max)/12V_{OUT} At 3A Design Using the LM5085

Figure 7 shows an efficiency plot taken from a prototype board, with efficiency (%) vs. load current (A).

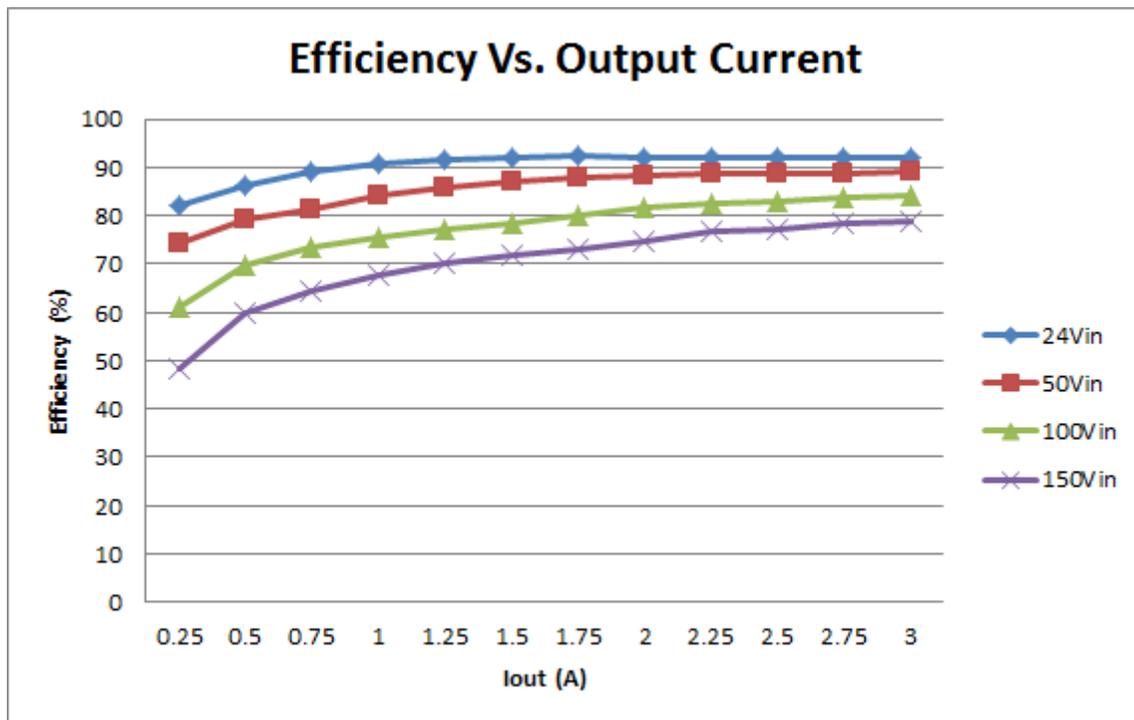


Figure 7. Efficiency (%) vs. Load Current (a) at Various Input Voltages

Figure 8 shows the switch-node voltage and inductor ripple current at 150V_{IN}.

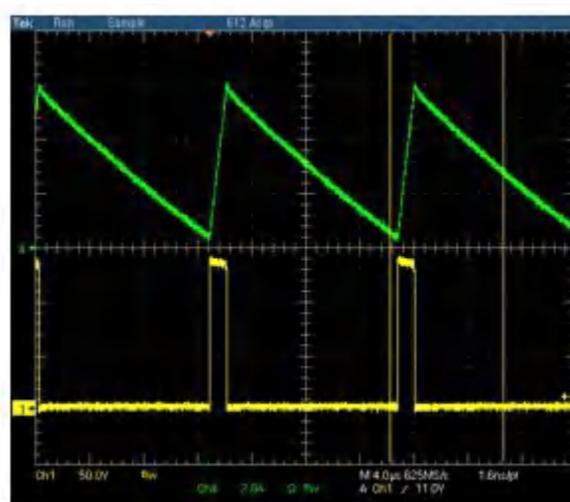


Figure 8. Channel 1 Switch-node Voltage, Channel 4 Inductor Ripple Current

Conclusion

You can use a P-channel nonsynchronous buck controller in applications where the input voltage of the system exceeds the maximum input-voltage rating of the device. This application has the benefit of using a lower-cost controller with minimal component count. For design guidance on the power stage of the buck converter, please see the application information in the [LM5085 data sheet](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated