

Technical Article

LDO Basics: Dropout



Aaron Paxton

The quintessential characteristic of a **low-dropout (LDO) linear voltage regulator** has to be dropout. After all, that is the source of its name and acronym.

At the most basic level, dropout describes the minimum delta between V_{IN} and V_{OUT} required for proper regulation. However, it quickly becomes more nuanced when you incorporate variables. Dropout, as you'll see, is essential to obtaining efficient operation and generating voltage rails with limited headroom.

What Is Dropout?

Dropout voltage, V_{DO} , refers to the minimum voltage differential that the input voltage, V_{IN} , must maintain above the desired output voltage, $V_{OUT(nom)}$, for proper regulation. See [Equation 1](#):

$$V_{IN} \geq V_{OUT(nom)} + V_{DO} \quad (1)$$

Should V_{IN} fall below this value, the linear regulator will enter dropout operation and no longer regulate the desired output voltage. In this case, the output voltage, $V_{OUT(dropout)}$, will track V_{IN} minus the dropout voltage ([Equation 2](#)):

$$V_{OUT(dropout)} = V_{IN} - V_{DO} \quad (2)$$

As an example, consider an LDO like the [TPS799](#) regulating 3.3V. When sourcing 200mA, the [TPS799's](#) maximum dropout voltage is specified at 175mV. As long as the input voltage is 3.475V or greater, regulation is not affected. However, dropping the input voltage to 3.375V will cause the LDO to enter dropout operation and cease regulation, as shown in [Figure 1](#).

 


Figure 1. The [TPS799](#) Operating in Dropout

Although it's supposed to regulate 3.3V, the [TPS799](#) does not have the headroom required to maintain regulation. As a result, the output voltage begins to track the input voltage.

What Determines Dropout?

The architecture of the LDO primarily determines dropout. To see why, let's look at PMOS and NMOS LDOs and compare their operation.

PMOS LDO

Figure 2 shows a PMOS LDO architecture. In order to regulate the desired output voltage, the feedback loop controls the drain-to-source resistance, or R_{DS} . As V_{IN} approaches $V_{OUT(nom)}$, the error amplifier will drive the gate-to-source voltage, or V_{GS} , more negative in order to lower R_{DS} and maintain regulation.

 


Figure 2. A PMOS LDO

At a certain point, however, the error-amplifier output will saturate at ground and cannot drive V_{GS} more negative. R_{DS} has reached its minimum value. Multiplying this R_{DS} value against the output current, or I_{OUT} , will yield the dropout voltage.

Bear in mind that the more negative the value of V_{GS} , the lower R_{DS} achieved. By increasing the input voltage, you can achieve a more negative V_{GS} . Therefore, PMOS architectures will have lower dropout at higher output voltages. Figure 3 illustrates this behavior.

 


Figure 3. Dropout Voltage vs. Input Voltage for the TPS799

As shown in Figure 3, the TPS799 has a lower dropout voltage as the input voltage (and output voltage, for that matter) increases. That is because a higher input voltage yields a more negative V_{GS} .

Nmos Ldo

In the case of an NMOS architecture, as shown in [Figure 4](#), the feedback loop still controls R_{DS} . As V_{IN} approaches $V_{OUT(nom)}$, however, the error amplifier will **increase** V_{GS} in order to lower the R_{DS} and maintain regulation.

 


Figure 4. An Nmos Ldo

At a certain point, V_{GS} cannot increase any more, since the error-amplifier output will saturate at the supply voltage, or V_{IN} . When this condition is met, R_{DS} is at its minimum value. Multiplying this value against the output current, or I_{OUT} , derives the dropout voltage.

This presents a problem though, because as V_{IN} approaches $V_{OUT(nom)}$, V_{GS} will also decrease, since the error-amplifier output saturates at V_{IN} . This prevents ultra-low dropout.

Biasing the LDO

Many NMOS LDOs employ an auxiliary rail known as a bias voltage, or V_{BIAS} , as shown in [Figure 5](#).

 


Figure 5. An NMOS LDO with a Bias Rail

This rail serves as the positive supply rail for the error amplifier and allows its output to swing all the way up to V_{BIAS} , which is higher than V_{IN} . This type of configuration enables the LDO to maintain a high V_{GS} , and therefore achieve ultra-low dropout at low output voltages.

Sometimes an auxiliary rail is not available but low dropout at a low output voltage is still desired. In such a situation, an internal charge pump can be substituted in place of V_{BIAS} , as shown in [Figure 6](#).

 


Figure 6. An NMOS LDO with an Internal Charge Pump

The charge pump will boost V_{IN} so that the error amplifier may generate a larger V_{GS} value despite the lack of an external V_{BIAS} rail.

Other Variables

In addition to architecture, dropout is also affected by a few other variables, as outlined in [Table 1](#).

Table 1. Variables Affecting Dropout

Variable	Impact on dropout
PMOS LDO	↓ V_{DO} when ↑ V_{OUT}
NMOS LDO with bias	↓ V_{DO} when ↓ V_{OUT}
Pass element size	↓ V_{DO} when ↑ pass element size
Output current	↑ V_{DO} when ↑ I_{OUT}
Temperature	↑ V_{DO} when ↑ T_J
Output accuracy	↑ V_{DO} when ↑ tolerance

It's clear that dropout is not a static value. Rather than just complicating your LDO choice, though, these variables should help you choose the optimal LDO for your specific set of conditions. Learn more about LDO dropout in the application note, [Understanding LDO Dropout](#).

Additional resources:

- Read more [LDO blogs](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated