

# How an eFuse Can Help Provide Robust Industrial Power Path Protection



Abhishek Kumar

Any electronic systems are often subjected to harsh environments and threats such as electrostatic discharge (ESD), electrical fast transient (EFT) and lightning surges. Power designers must prioritize circuit protection to prevent system failure, especially for [industrial applications](#) with a 24V supply rail.

Circuit protection schemes are capable of protecting the power supply and the overall system from events such as overcurrent, short circuit, input inrush current, overvoltage, undervoltage, input reverse polarity protection (commonly known as miswiring) and reverse current blocking.

In this blog I will give an overview of several approaches to robust industrial power path protection including discrete implementation, hot-swap plus ORing controller approach and integrated implementation.

## Discrete Implementation

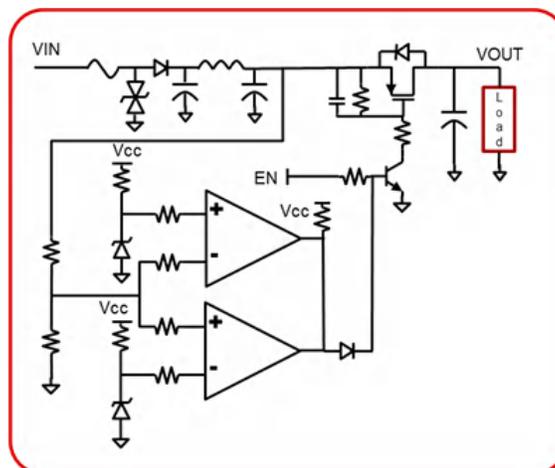


Figure 1. Discrete Protection Scheme


Discrete implementation schemes are the most traditional way of power path protection using a protection scheme in the power path one example is shown in [Figure 1](#).

A discrete implementation utilizes a power diode in series to protect the system from reverse polarity (miswiring) and reverse current. If a circuit draws 2A of current, it dissipates ~1W of power across the diode, which will increase the board temperature. Resonant circuit (L-C) filters and multiple TVS diodes control the input line transients during surge test (International Electrotechnical Commission (IEC) 61000-4-5).

The implementation utilizes a PFET (high-side switch) along with bi-polar junction transistor BJTs, operational amplifiers, Zener diodes, resistors and capacitors to fulfill all protection requirements. This system solution is bulky and has a larger bill of materials (BOM) count. Additionally, this implementation does not address thermal shutdown protection and current-limit accuracy variations with temperature.

By utilizing a traditional fuse, a discrete implementation protects against short-circuit events. The fuse takes milliseconds to seconds to break during short circuit, which can damage the load. Be sure to check out [my colleague's blog](#) for more information on upgrading your fuse.


## Hot-swap plus ORing Controller Approach

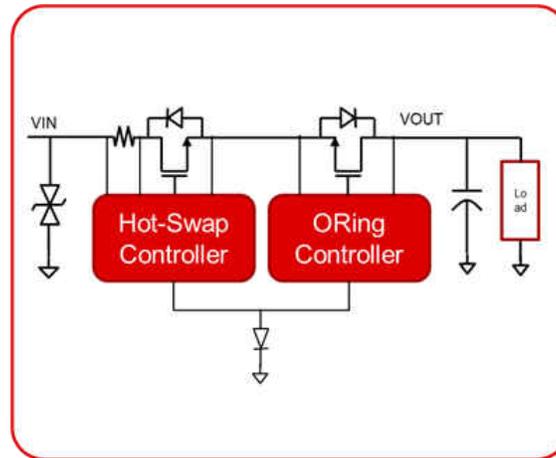

**Figure 2. Controller + MOSFET Protection Scheme**

Another common approach, as shown in [Figure 2](#), to power protection is through a hot-swap controller and an ORing controller. This scheme uses external FETs to make the design more efficient and reliable. Unfortunately, this implementation still has challenges, such as controlling external FETs, external sense resistance and implementing an additional circuit for input reverse-polarity protection. This implementation struggles to manage thermal and safe operating area (SOA) protections due to the external FET architecture. Even though this solution is better than a discrete implementation, it is not suitable for space-constrained systems such as input/output (I/O) modules.

## Integrated Implementation (eFuse)

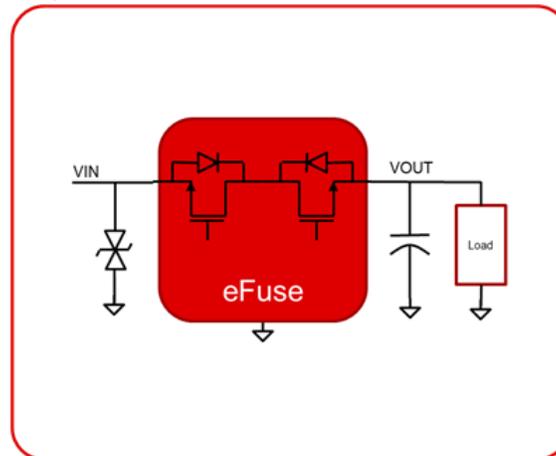

**Figure 3. Integrated Protection Scheme**

On the other hand, imagine that your entire discrete implementation vanishes into a single integrated device, barring a few components like Transient Voltage Suppressor (TVS) diodes, resistors and capacitors, as shown in [Figure 3](#). That would be really cool, right? An **eFuse** typically integrates all of the protection features mentioned above into single device, efficiently and with minimal design efforts. eFuses also incorporate features like voltage, current monitoring and fault indication for system diagnosis – apart from power path protection.

The SOA protection of FETs and robust thermal protection ensures the protection of the eFuse, as well as the load in harsh environments. It is also suitable for space-constrained applications, as integration helps reduce the system solution by more than half.

One of these types of solutions is the [TPS2660](#), the industry's first 60V back-to-back FET integrated eFuse. The device is definitely worth considering for your new designs as it supports protection against inrush current, overcurrent, short circuit, input reverse polarity protection (miswiring), overvoltage and undervoltage conditions. It also provides current monitoring and fault indication for system diagnosis. The integrated 60V back-to back-

FET architecture lets you design robust circuits and protect loads against industry-standard tests such as surge (IEC 61000-4-5), EFT (IEC 61000-4-4), and voltage dips and interruption tests in accordance with IEC 61131-2.

A robust and efficient power supply protection scheme is essential for electronic system design. With integrated protection devices, designers can create their system more simply, , efficiently and get to market faster. If you have a design which uses power path protection for 24V power supply rail, stay a step ahead and start designing today with the [Input Protection and Backup Supply Reference Design for a 25W PLC Controller Unit](#).

#### **Additional Resources**

- For more details on how the [TPS2660](#) helps during industry-standard testing:
  - Read the application note, “[The TPS2660 Simplifies Surge and Power-Fail Protection Circuits in PLC Systems.](#)”
  - Learn more about [TI's eFuse products](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated