

What Do CAN Bus Signals Look like?

John Griffith

Welcome to the second post in this series on the controller area network (CAN), which is increasingly being used in industrial applications. In this post, I'll focus on the signaling levels found on a CAN bus, so that designers will understand the origin of CAN's reputation for noise immunity.

As stated in my first [post](#), CAN is a serial, two-wire, differential bus technology. This means that data is sent one bit at a time through two complementary signals on the controller area network high (CANH) and controller area network low (CANL) bus wires.

To effectively explain the different types of signals, it's useful to first understand a typical CAN application. Every CAN application consists of a microcontroller with built-in CAN controller and a transceiver that is tied to the bus. A discrete implementation of this is shown in [Figure 1](#). The two types of signals that are processed by the CAN transceiver are single-ended signals (TXD and RXD) and differential signals (CANH and CANL). During normal operation, the CAN transceiver converts the single-ended logic-level output signal (TXD) from the CAN controller to a differential signal. It also converts the differential signal on the bus back to a single-ended logic signal (RXD) for input into the CAN controller. Essentially, the transceiver provides differential drive and differential receive capability to and from the CAN bus.

 


Figure 1. CAN Controller and CAN Transceiver

The CAN bus has two logical states: dominant and recessive. The dominant state occurs when a logic low level is applied to the transmit input pin (usually called TXD) of the transceiver. The recessive state corresponds to a logic high level on the transmit input pin of the transceiver. [Figure 2](#) shows these two states.

 


Figure 2. CAN Bus Signal Levels

As you can see, in the recessive state both the CANH and CANL bus pins are biased to the same level: approximately 2.5V. During the dominant state, the CANH bus pin is biased to a higher voltage potential (approximately 3.5V) and the CANL bus pin is biased to a lower voltage potential (approximately 1.5V). By subtracting the voltage potential of the two bus pins, you can determine the logical state of the bus using the equation below. When the V_{diff} value on the bus is less than 0.5V, the bus is considered to be in a recessive state. Alternately, V_{diff} values greater than 0.9V indicate that the bus is in a dominant state. Lastly, for V_{diff} values between 0.5V and 0.9V, the bus state is undefined. Since the difference between the two signals is used to define the state of the bus, this signaling type is known as differential signaling. Additionally, the CANH and CANL signals are commonly referred to as complementary singles since you need to know the voltage potential of both signals to determine the logical state of the bus.

$$V_{diff} = V_{CANH} - V_{CANL}$$

The recessive state will only exist on the bus if all transceivers connected to the bus are transmitting a recessive state, because the recessive state is weakly biased, while the dominant state is strongly biased. This is analogous to a wired logical AND connection. All transceivers must be transmitting a logical high signal for the bus output to be logical high. If even one transceiver transmits a logical 0, the entire bus will follow this state and will be in the dominant state.

Now that you know what the differential bus signals on a CAN bus look like, stay tuned for my next post which will describe the typical driver topology that is used to create these bus signals. Feel free to post any questions or comments below.

Additional Resources:

- Read Part 1 of this series: [“CAN we start at the very beginning?”](#)
- Check out the new [CAN page](#) with information on our products, support resources and technical documents.
- [Polarity Correcting Isolated CAN Reference Design](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated