



## **LM27403 Synchronous Buck Converter**

**TI reference design number: PMP8000**

**Input: 12V**

**Output: 5V @ 30A**

**DC – DC Test Results**

---

## Table of Contents

1	Circuit Description.....	3
2	Photos .....	3
3	Efficiency .....	5
4	Thermal Tests.....	6
4.1	Test Setup .....	6
4.2	30A Load, No Airflow .....	7
5	Startup and Shutdown Behavior .....	8
5.1	Turn-on and Turn-off from Vin .....	8
5.2	Turn-on and Turn-off from EN .....	9
6	Switching and Ripple .....	10
6.1	Switching and Ripple .....	10
7	Load Transient Response.....	11
7.1	Load Transient Response.....	11

# PMP8000 Test Results


## 1 Circuit Description


PMP8000 is a single-phase synchronous buck converter rated for 5V output at 30A from an input voltage of 12V. This design uses the LM27403 synchronous buck controller at a switching frequency of 500 kHz. CSD87350Q5D power block MOSFETs provide maximum efficiency when combined with a 250nH ferrite output inductor. The design solution uses all ceramic capacitors to fit into a minimum board area.

All tests were performed at room temperature on an open bench. A 470 $\mu$ F, 25V aluminum electrolytic input capacitor was used for input filter damping.
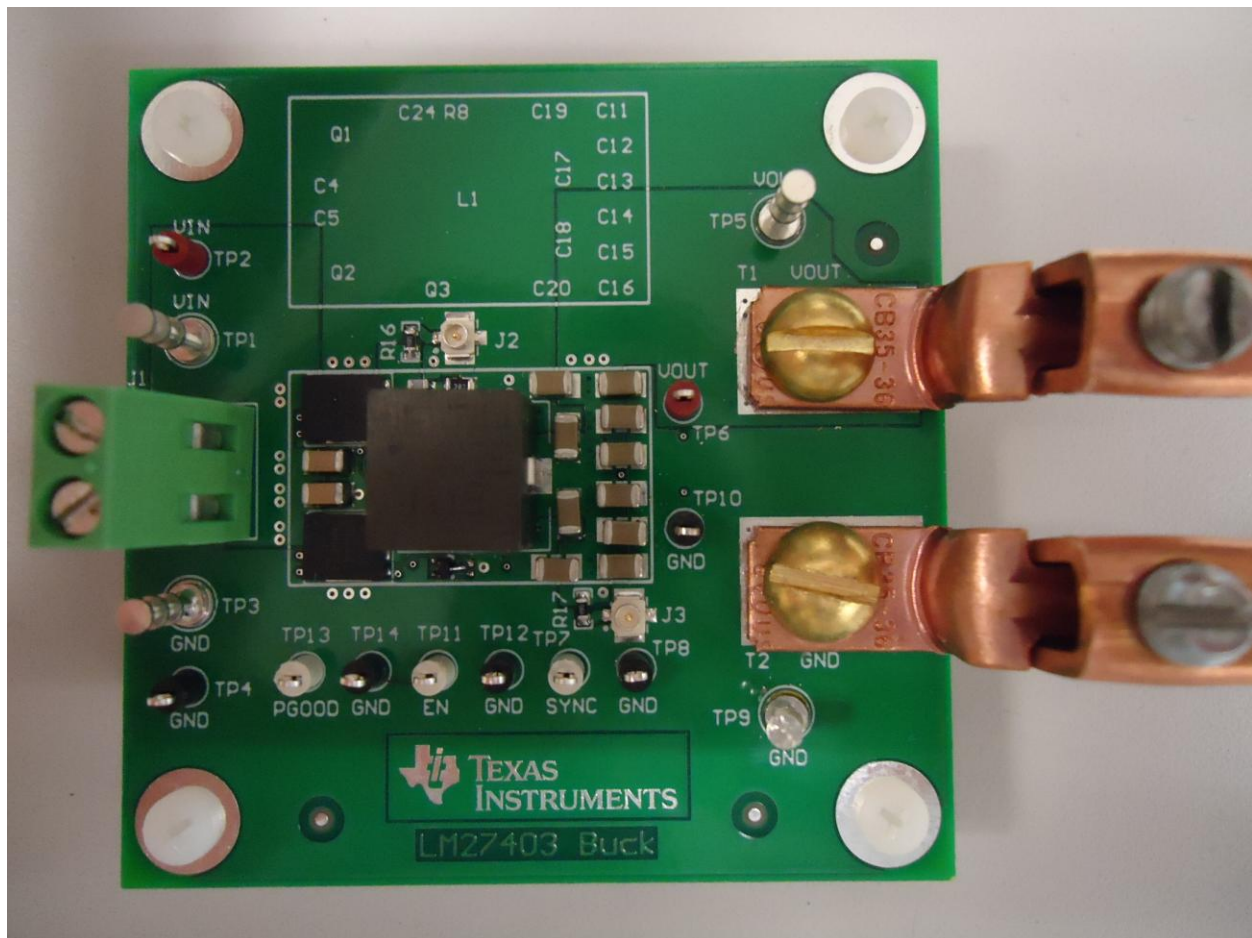
## 2 Photos

The photographs below show the PMP8000 Rev A assembly as built on PMP7935-A printed circuit board. This is a 4 layer board using 2 ounce copper on external layers and 1 ounce copper on internal layers. Power components are mounted on the top side of the board, with the control circuit on the bottom. The overall board dimensions are 2.5" x 2.5". The solution size component area is 1.1" x 0.65". The maximum component height is set by the inductor at 9.4 mm.




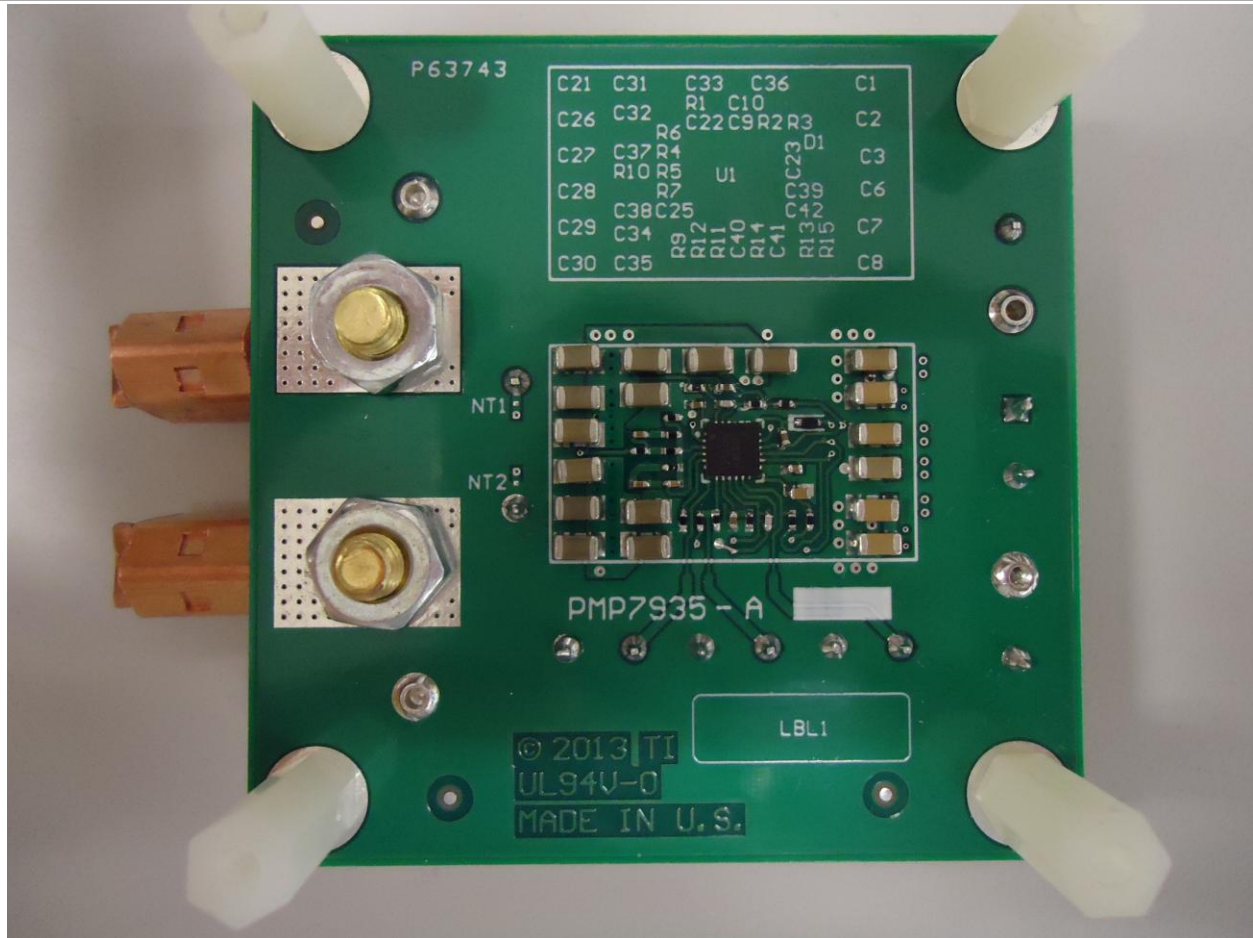

# PMP8000 Test Results
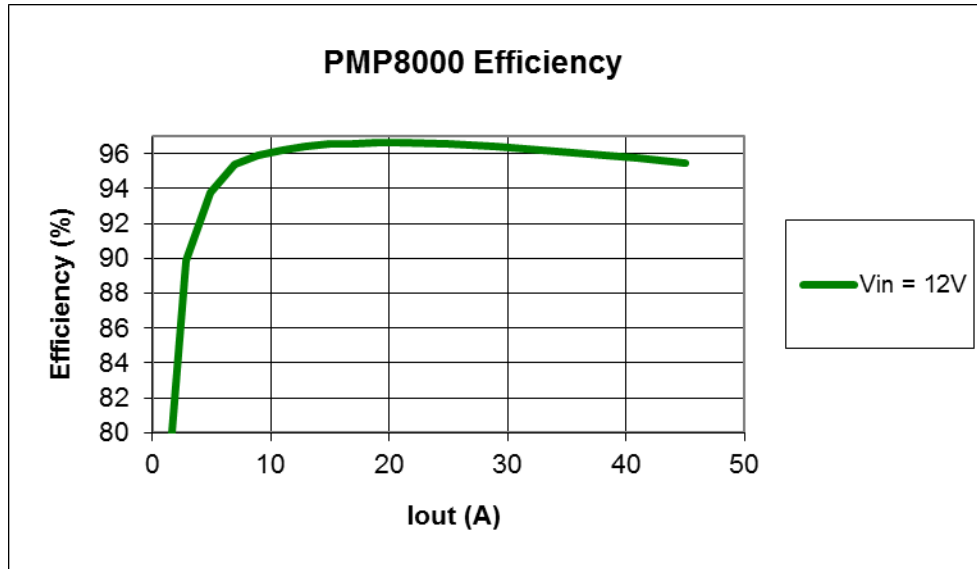
## 3 Efficiency

The efficiency data is shown in the tables and graph below.




Vin(V)	Iin(A)	Vout(V)	Iout(A)	Efficiency(%)	Pin(W)	Pout(W)	Pdis(W)
12.000	0.135	5.017	0.00	0.000	1.62	0.00	1.62
12.000	0.510	5.018	0.90	73.794	6.12	4.52	1.60
12.000	1.350	5.020	2.90	89.864	16.20	14.56	1.64
12.000	2.195	5.021	4.92	93.786	26.34	24.70	1.64
12.000	3.045	5.024	6.94	95.420	36.54	34.87	1.67
12.000	3.905	5.026	8.94	95.887	46.86	44.93	1.93
12.0000	4.755	5.028	10.92	96.225	57.06	54.91	2.15
11.999	5.625	5.030	12.94	96.435	67.49	65.09	2.41
11.999	6.495	5.031	14.96	96.574	77.93	75.26	2.67
11.999	7.365	5.032	16.96	96.571	88.37	85.34	3.03
11.999	8.240	5.033	18.98	96.616	98.87	95.53	3.35
11.998	9.100	5.034	20.96	96.639	109.18	105.51	3.67
11.998	10.865	5.038	24.98	96.541	130.36	125.85	4.51
11.997	12.635	5.043	28.98	96.414	151.58	146.15	5.44
11.996	14.44	5.051	33.00	96.225	173.22	166.68	6.54
11.995	16.265	5.057	37.02	95.957	195.10	187.21	7.89
11.995	18.08	5.061	41.02	95.727	216.87	207.60	9.27
11.993	19.92	5.063	45.04	95.453	238.90	228.04	10.86

## 4 Thermal Tests

All tests were performed at room temperature on an open bench.

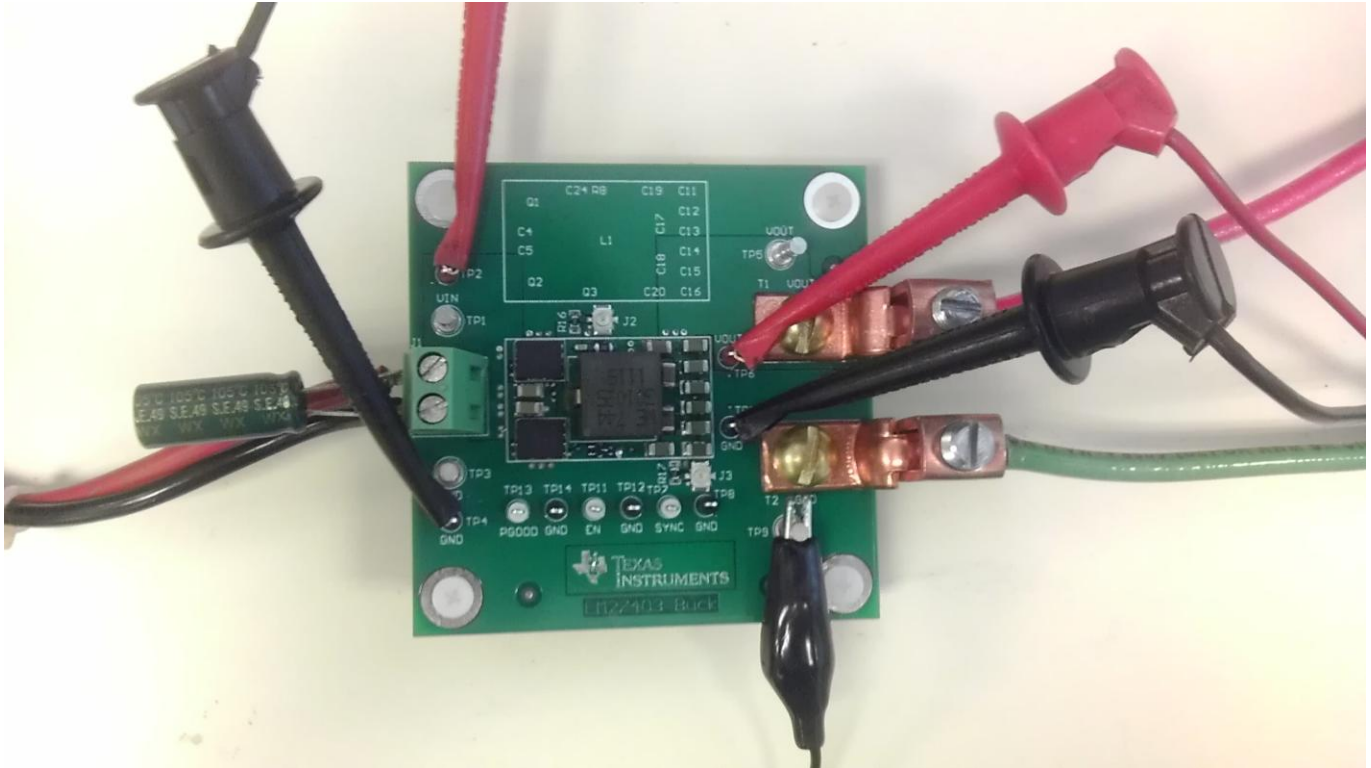
### 4.1 Test Setup

Thermal data was taken with a Fluke handheld thermal camera.







## 4.2 30A Load, No Airflow

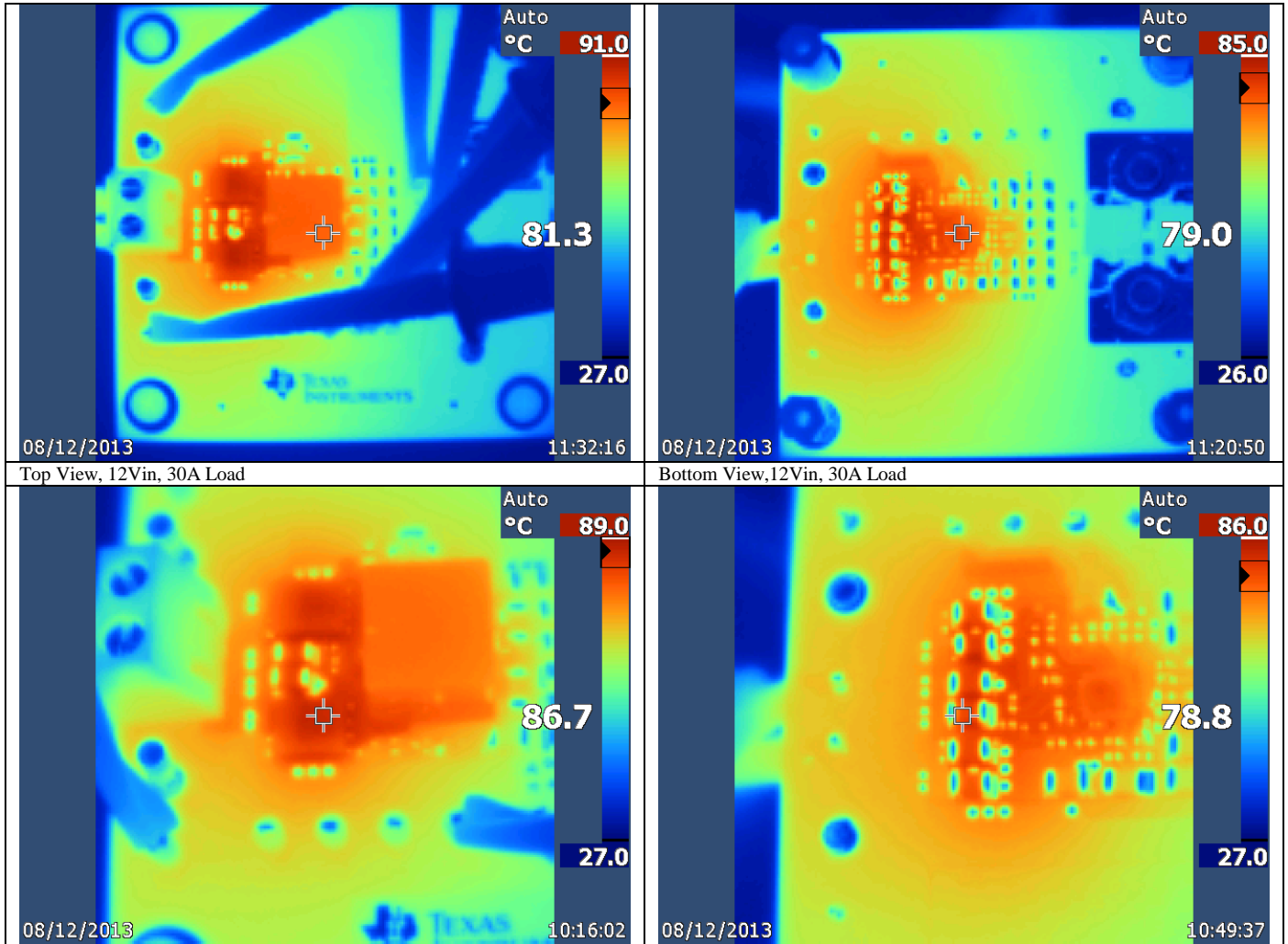

## 5 Startup and Shutdown Behavior
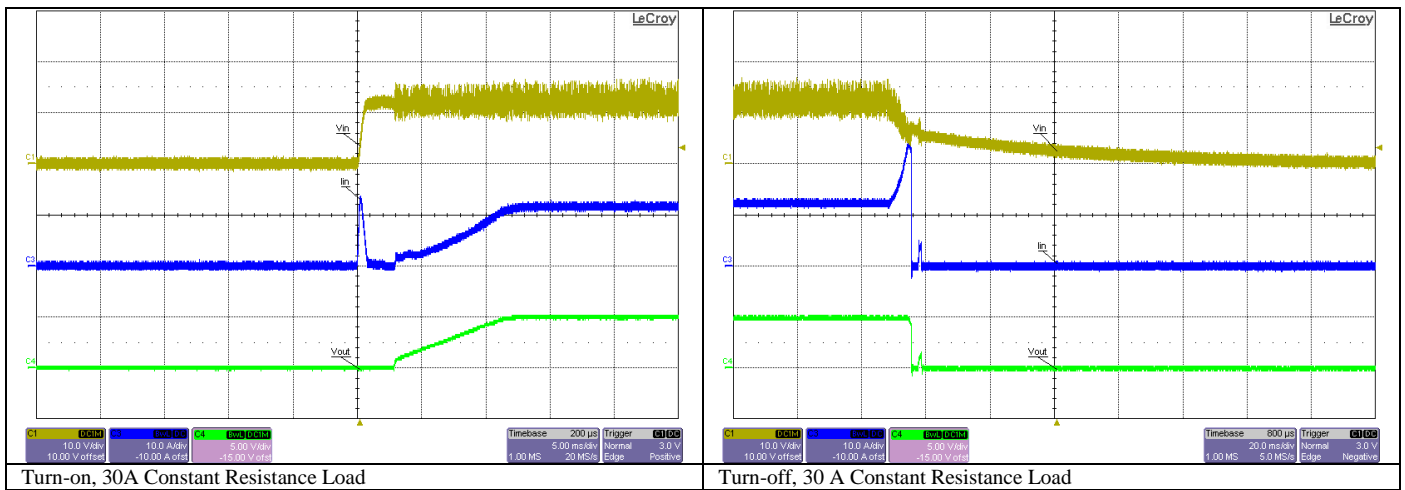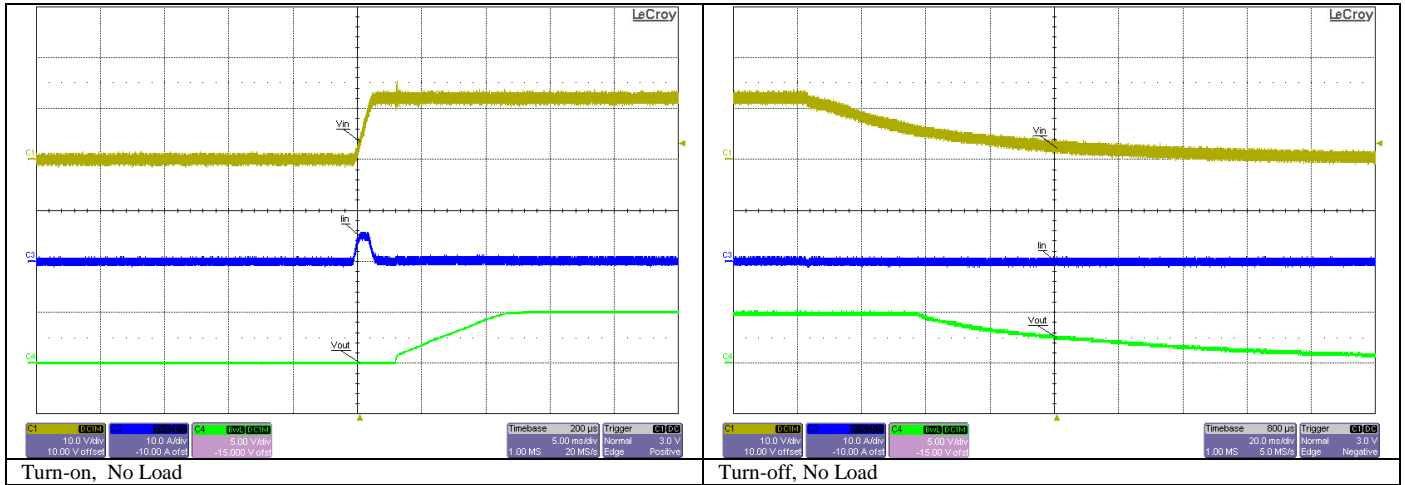
### 5.1 Turn-on and Turn-off from Vin

The output voltage is well controlled at turn-on, showing no evidence of over-shoot.







# PMP8000 Test Results
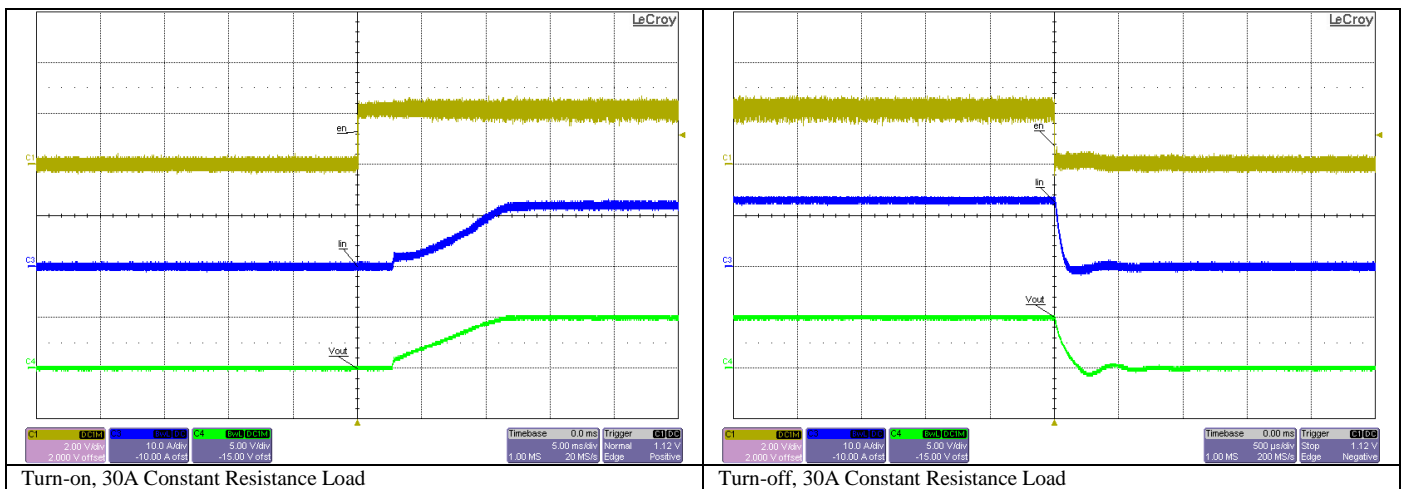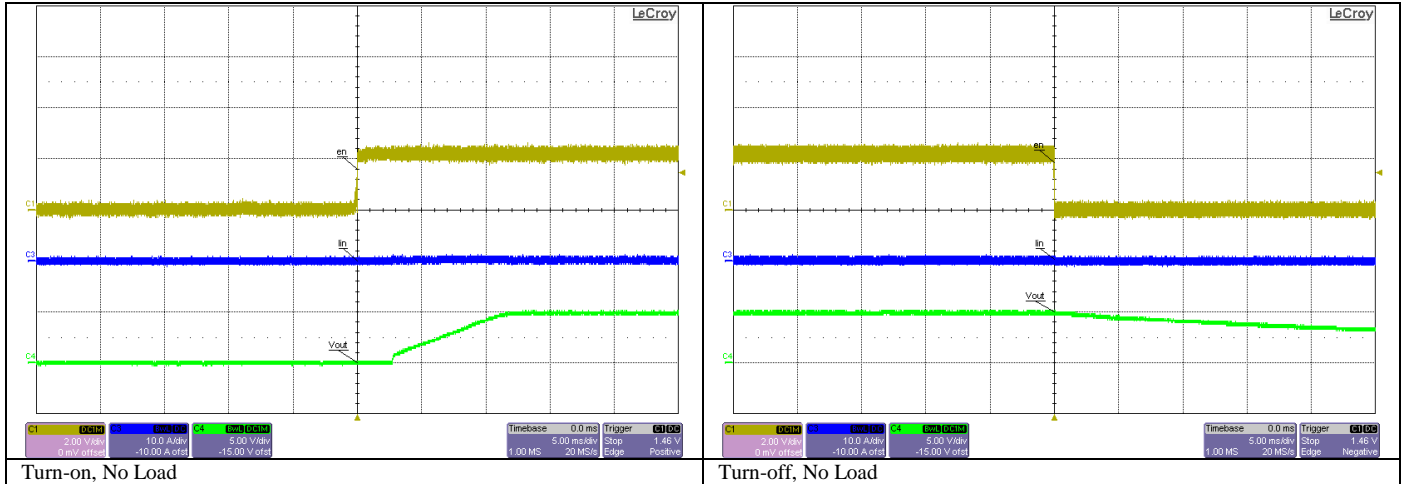
## 5.2 Turn-on and Turn-off from EN


The output voltage is well controlled at turn-on, showing no evidence of over-shoot. Some ringing occurs at turn-off with load due to the output filter resonance.



## 6 Switching and Ripple
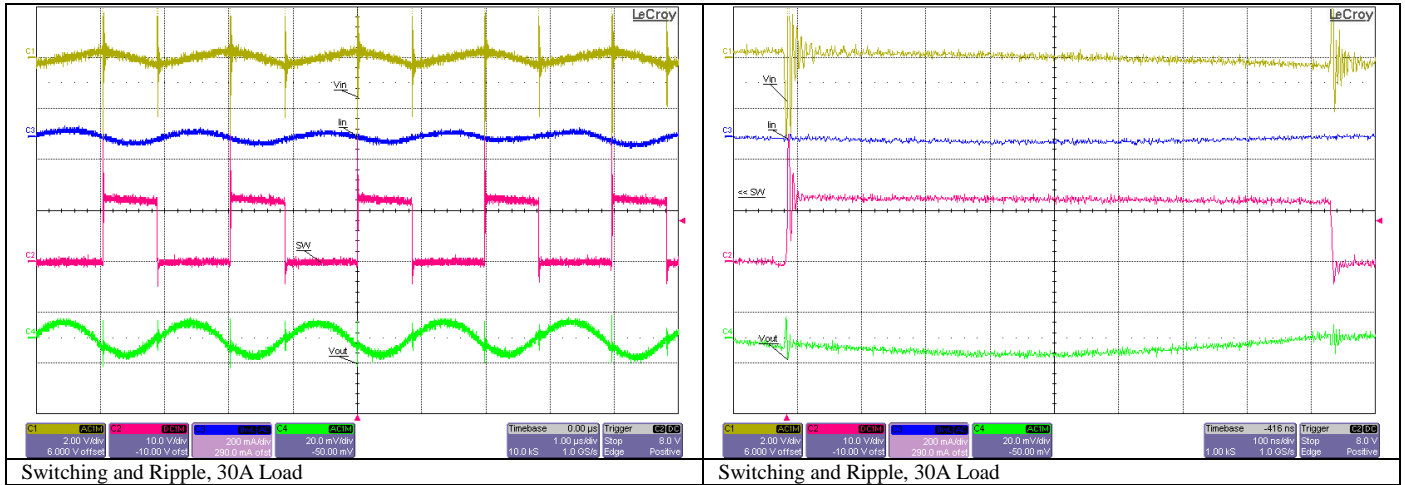
### 6.1 Switching and Ripple

Switching and ripple tests were made with a 470 $\mu$ F, 25V aluminum electrolytic input capacitor for input filter damping.





# PMP8000 Test Results

## 7 Load Transient Response

Load transient response for each condition was taken at two points to represent the minimum and maximum deviation. This difference occurs when the transient step coincides with either the converter off-time or on-time interval.
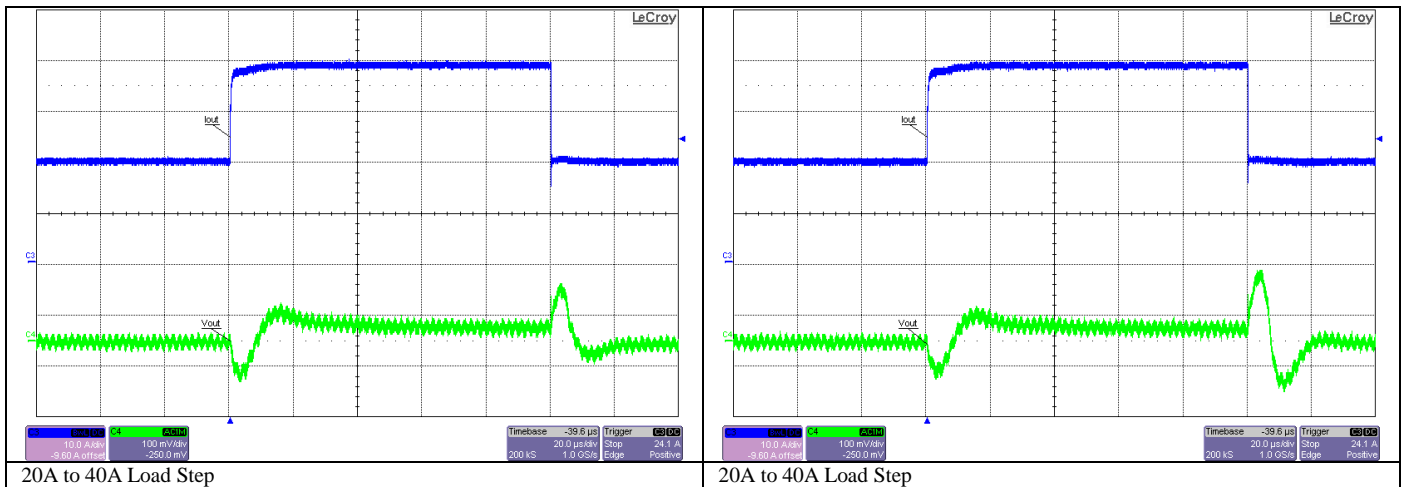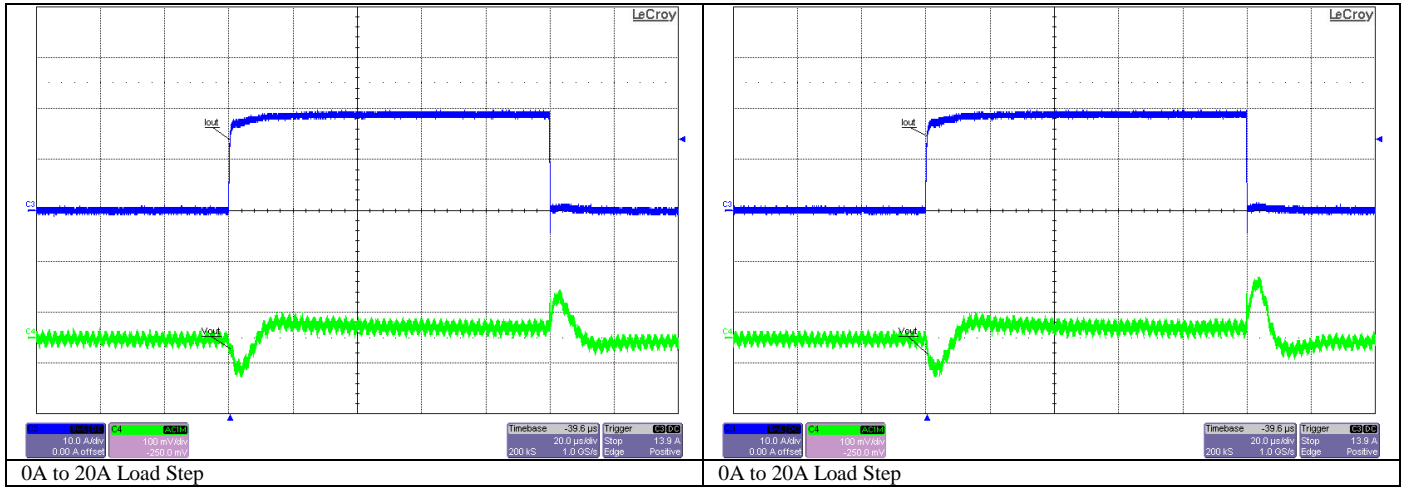
### 7.1 Load Transient Response

The output voltage transient is within 100mV for a 20A load step.



## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.