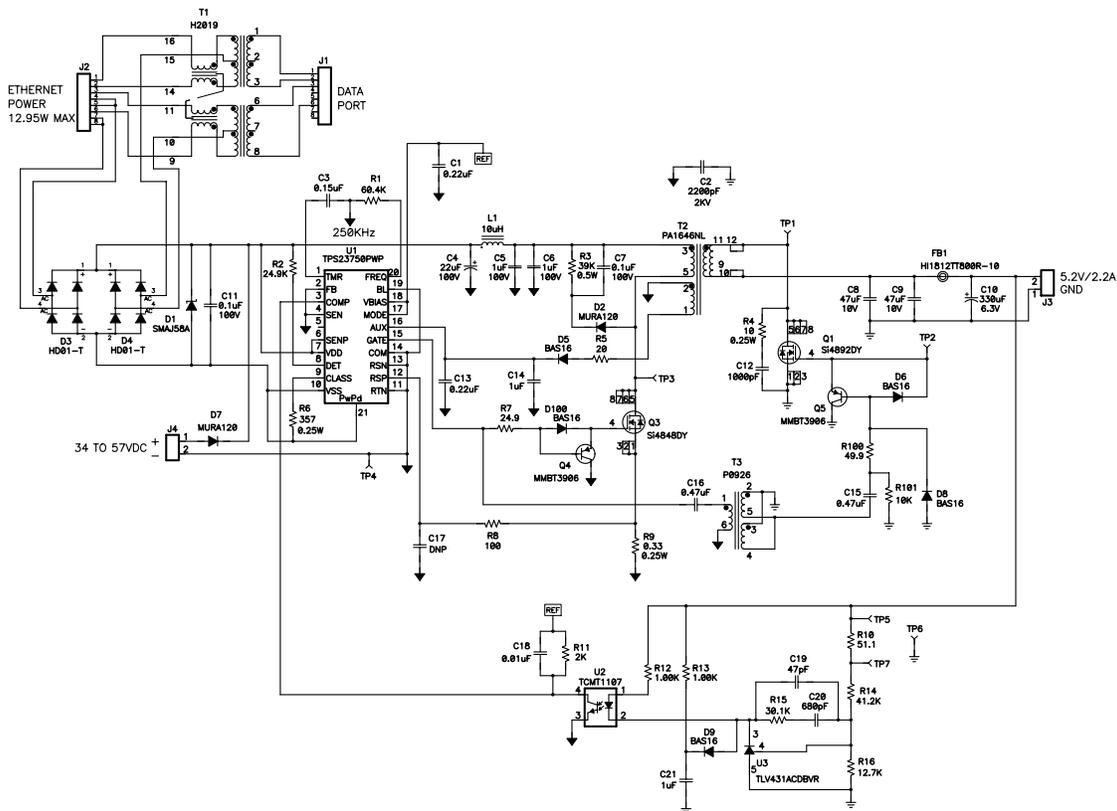


TPS23750 High Efficiency 5V at 2.2A PoE PD

PMP1564 is a high-efficiency, isolated, synchronous flyback Power-over-Ethernet PD power-supply reference design that eases implementation of PoE in devices such as IP phones, WLAN APs and security cameras. The reference design uses a TPS23750 PoE Powered Device Controller with integrated current-mode DC/DC controller. The TPS23750 implements all necessary detection, classification, inrush-current limiting and UVLO functions necessary to comply with the IEEE802.3af Power-over-Ethernet standard. The 48-V PoE input is converted to 5 V at 2.2 A. The design is optimized for 90% efficiency in the smallest board area possible.



1 Efficiency

The efficiency with a 48-V input is given below for the flyback converter (V_{IN} measured on cathode of D7 and for the total system power (J2). V_{OUT} is measured at TP5/TP6.


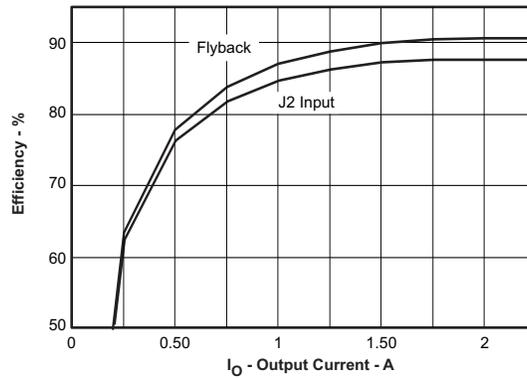


Figure 1.

2 Output Ripple and Noise

12-Oct-05
12:42:51


 1 μ s
 20.0mV

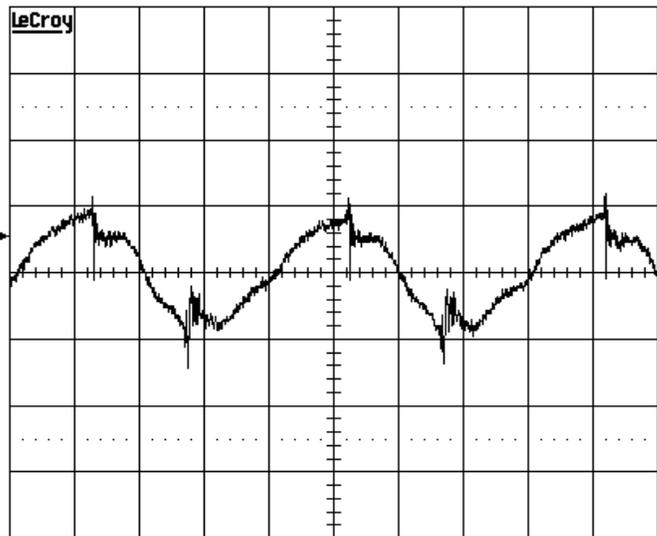

1 μ s BWL
 1 2 V DC \times
 2 .5 V DC \times
 3 2 mV AC \times
 4 50 mV DC \times

3 DC 11.2mV

1 GS/s

□ STOPPED

Figure 2. Output Voltage Ripple With 48V Input and 5.2V/2A Load

3 Input Ripple and Noise

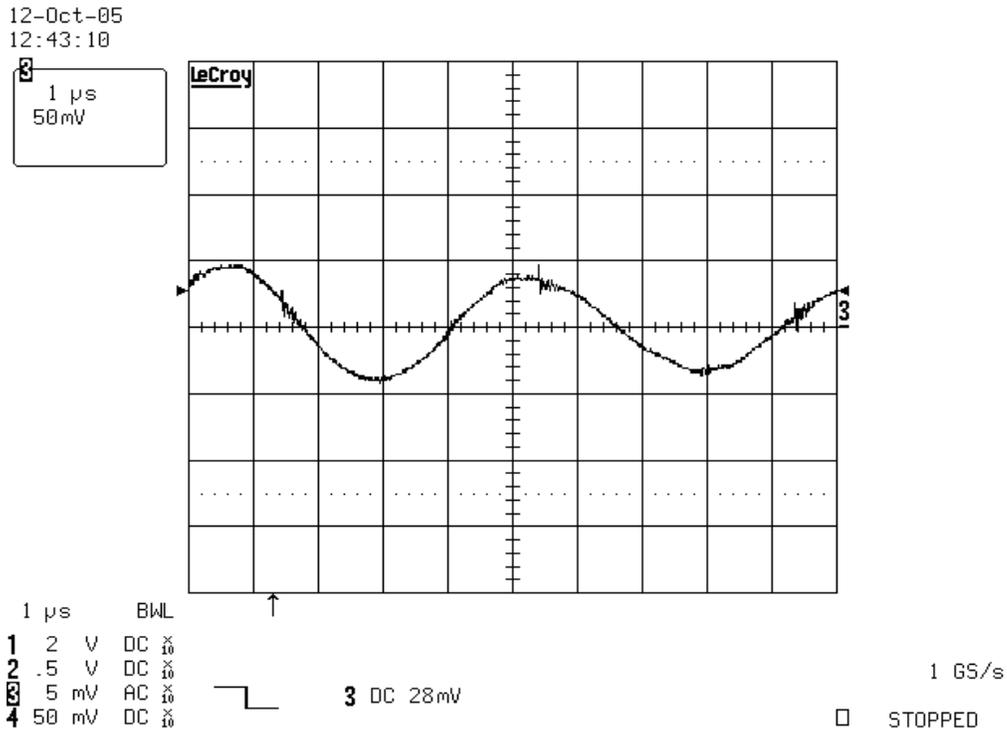


Figure 3. Input Voltage Ripple and Noise Measured at J4 With 48V Input and Max Load on Output

4 Dynamic Loading

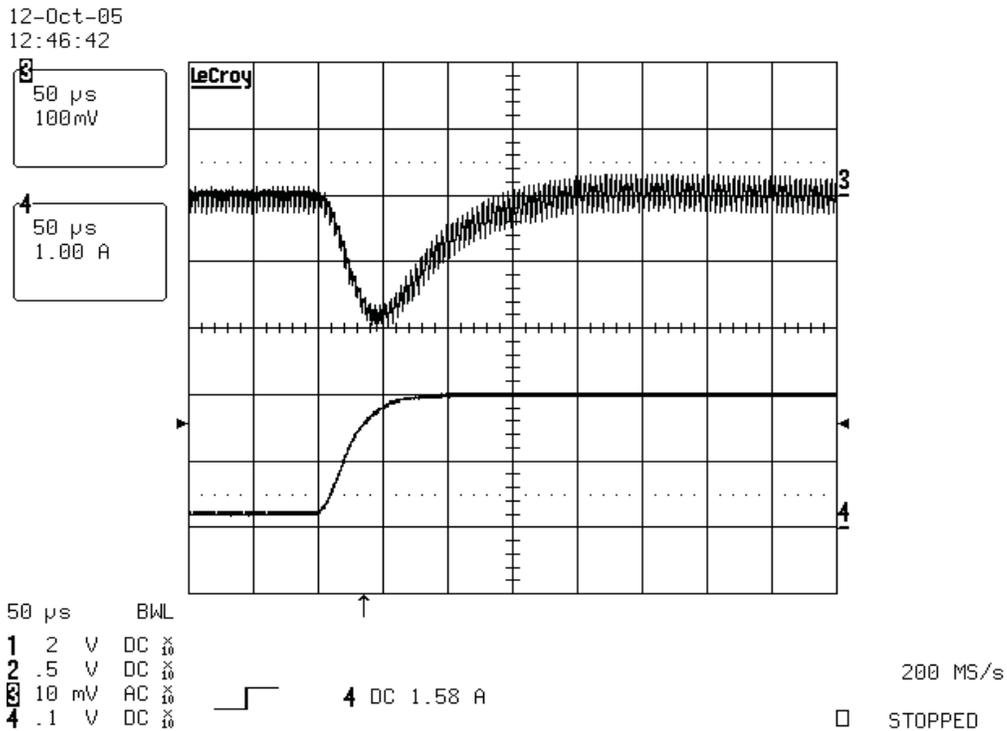


Figure 4. The Output Voltage Transient Response With a Load Step From 10% to 90%

Dynamic Loading

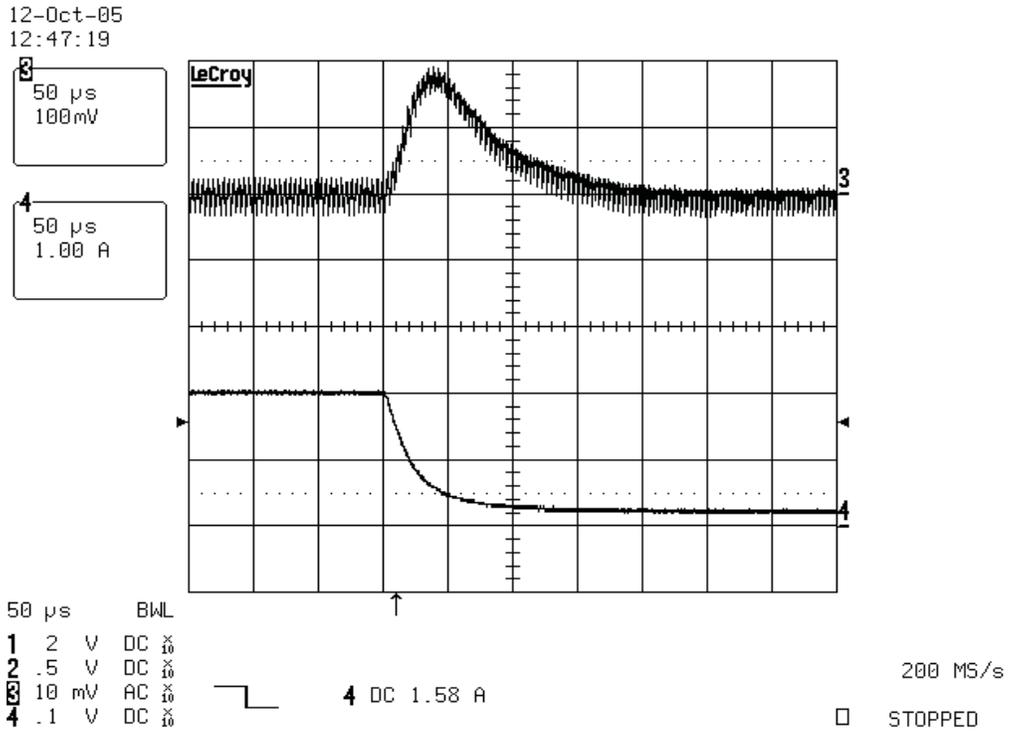


Figure 5. The Output Voltage Transient Response With a Load Step From 90% to 10%

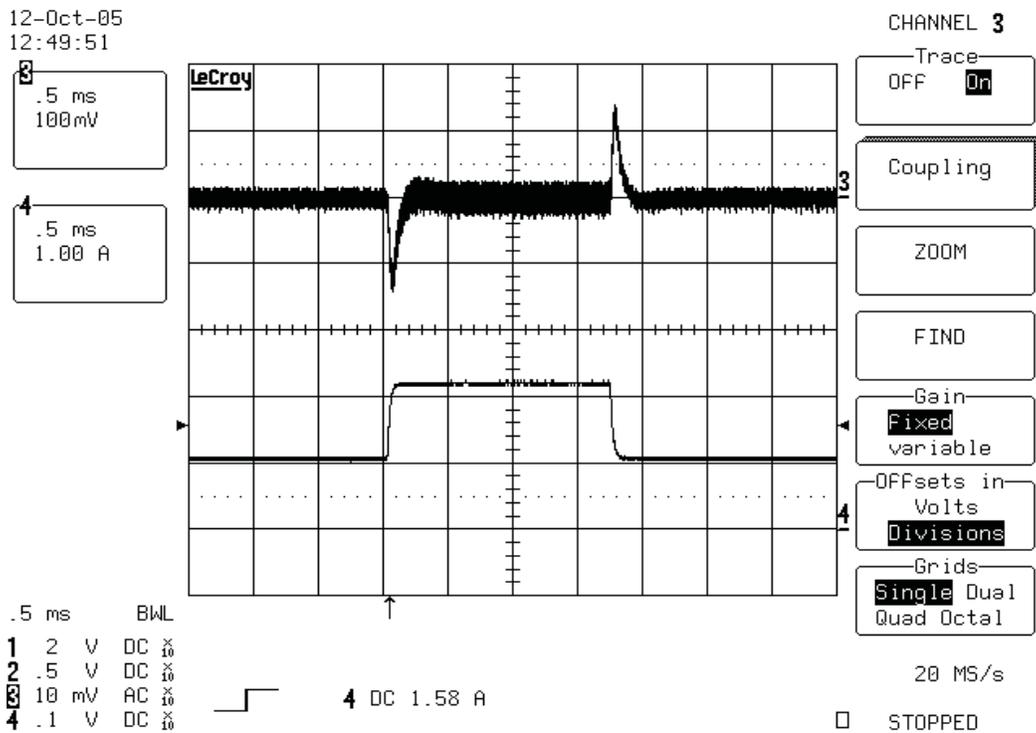


Figure 6. The Output Voltage Transient Response With a Load Step From 50% to 100%

5 Turn On Response

12-Oct-05
12:55:33

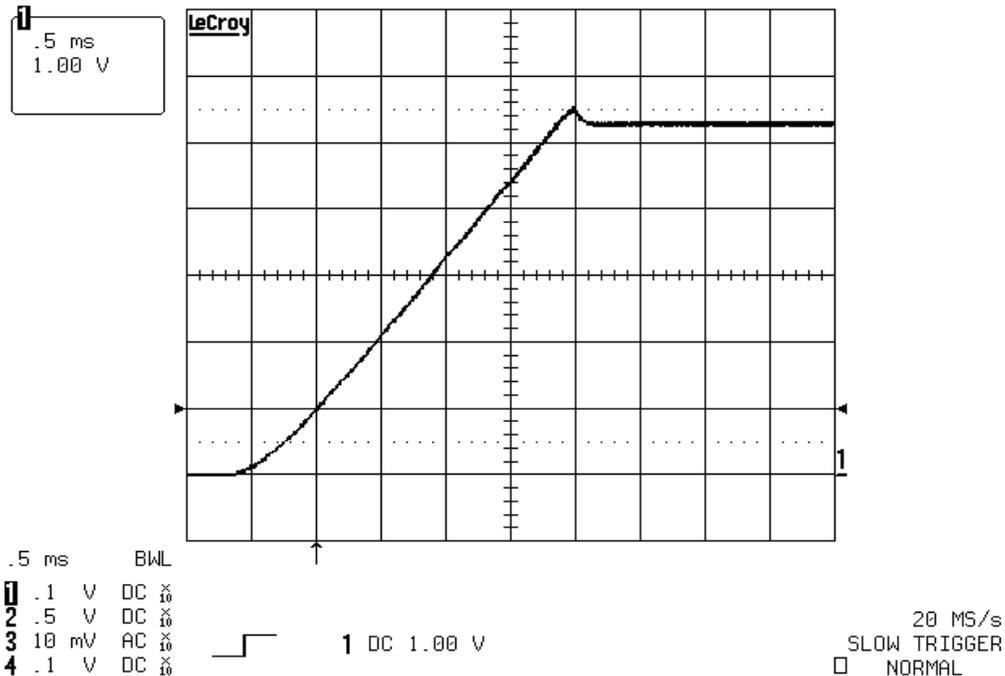


Figure 7. The Output Voltage Turn-On Response With a 48V Input and a 2A Load

12-Oct-05
12:56:08

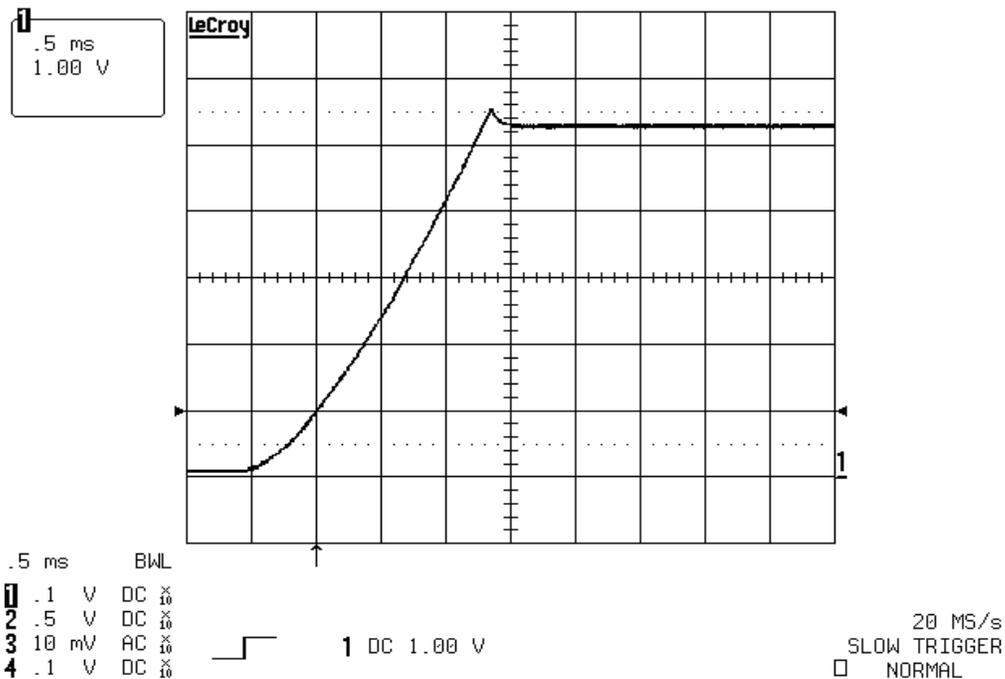


Figure 8. The Output Voltage Turn-On Response With a 48V Input and a 0A Load

6 Stability Analysis (Loop Gain)

The figure below is the flyback-converter loop gain with a 48-V input and a 2-A load. The bandwidth is 3 kHz, the phase margin is 65°, and the gain margin is 18dB.

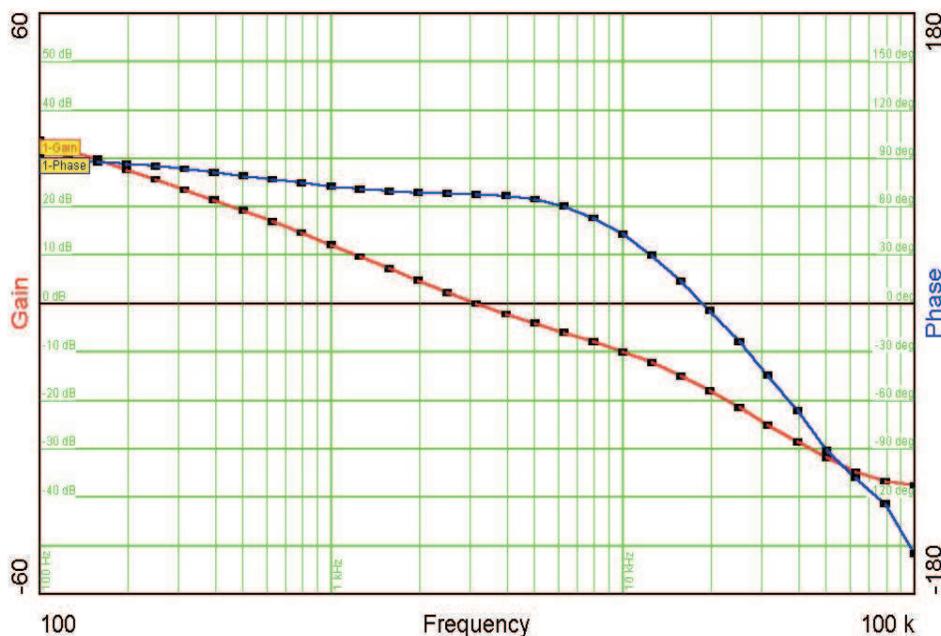


Figure 9. Loop Gain of the Flyback Converter With 48-V Input and 2-A Load

The TPS23750 characteristics makes it an attractive choice for delivering maximum power to the load.

Table 1. TPS23750 Competitive Advantages

Parameter	IEEE 802.3af	TI ⁽¹⁾	Competitor 1 ⁽¹⁾	Competitor 2 ⁽¹⁾	Units
PSE Output Voltage Minimum voltage	44	44	44	44	V
Current Limit min	0.35 ⁽²⁾	0.405	0.325	0.300	A
Available PD Power at input connector	12.9	14.5	12.1	11.4	W
Loss Before PD		14.2	11.9	11.1	W
Minus PD Loss Current ⁽³⁾ Rdson		13.8	11.2	10.5	W
89% Converter Efficiency Power to Load		12.2	10.1	9.4	W

(1) at min current limit and max Rdson

(2) PSE Output Current Maximum current

(3) Adding min current limit + max Rdson + max converter efficiency gives TI and edge over competition

See also: Estimating available application power for Power-over-Ethernet applications

<http://focus.ti.com/lit/an/slyt085/slyt085.pdf> Adding min current limit + max Rdson + max converter efficiency gives TI and edge over competition.

Table 2. PMP1564_Rev A Bill of Materials

Count	RefDes	Value	Description	Size	Part No.	MFR
1	C19	47 pF	Capacitor, Ceramic, 50V, C0G, 5%	603	Std	Std
1	C20	680 pF	Capacitor, Ceramic, 50V, X7R, 10%	603	Std	Std
1	C12	1000 pF	Capacitor, Ceramic, 50V, C0G, 5%	603	Std	Std
1	C18	0.01 μ F	Capacitor, Ceramic, 0.01 μ F, 50V, X7R, 10%	603	Std	Std
1	C3	0.15 μ F	Capacitor, Ceramic, 16V, X7R, 10%	603	Std	Std
2	C1, C13	0.22 μ F	Capacitor, Ceramic, 16V, X7R, 10%	603	Std	Std
2	C15, C16	0.47 μ F	Capacitor, Ceramic, 16V, X7R, 10%	603	Std	Std
0	C17		DNP	603		
2	C7, C11	0.1 μ F	Capacitor, Ceramic, 100V, X7R, 10%	805	C2012X7R2A104K	TDK
2	C14, C21	1 μ F	Capacitor, Ceramic, 16V, X7R, 10%	805	Std	Std
2	C5, C6	1 μ F	Capacitor, Ceramic, 1 μ F, 100V, X7R, 10%	1210	C3225X7R2A105K	TDK
2	C8, C9	47 μ F	Capacitor, Ceramic, 10V, X5R, 20%	1210	C3225X5R1A476M	TDK
1	C2	2200 pF	Capacitor, Ceramic, 2KV, X7R, 10%	1812	C4532X7R3D222K	TDK
1	C10	330 μ F	Capacitor, Aluminum, 6.3V, 20%	8 x 6,2 mm	EEVFK0J331P	Panasonic
1	C4	22 μ F	Capacitor, Aluminum, 100V, 20%	8 x 10,2 mm	EEVFK2A220P	Panasonic
1	D1		Diode, TVS, 58-V, 1W	SMA	SMAJ58A	Diodes Inc.
2	D2, D7		Diode, Rectifier, 1A, 200V	SMA	MURA120	On Semi
2	D3, D4		Bridge Rectifier, 100V, 0.8A	MINI DIP4	HD01-T	Diodes, Inc
5	D5, D6 D8, D9, D100		Diode, Switching, 200mA, 75V, 225 mW	SOT-23	BAS16LT1	On Semi
2	J1, J2		Connector, Jack, Modular, 8 POS	0.705 x 0.820	520252	AMP
2	J3, J4		Terminal Block, 2-pin, 6-A, 3,5 mm	0.27 x 0.25		ED1514
1	L1	10 μ H	Inductor, SMT, 1.1A, 130 m Ω	4,45 x 6,6 mm	P0770.103	Pulse
1	FB1		Ferrite Bead, 6A	1812	HI1812T800R	Steward
1	Q1		MOSFET, N-ch, 30V, 12.4A, 12 m Ω	SO8	Si4892DY	Vishay
2	Q2, Q4		Bipolar, PNP, 40V, 200mA, 225 mW	SOT23	MMBT3906LT1	On Semi
1	Q3		MOSFET, N-ch, 150V, 3.7A, 85 m Ω	SO-8	Si4848DY	Vishay
1	R5	20	Resistor, Chip, 1/16W, 5%	603	Std	Std
1	R7	24.9	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R100	49.9	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R10	51.1	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R8	100	Resistor, Chip, 1/16W, 1%	603	Std	Std
2	R12, R13	1.00K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R11	2K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R101	10K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R16	12.7K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R2	24.9K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R15	30.1K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R14	41.2K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R1	60.4K	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R9	0.33	Resistor, Chip, 1/4W, 5%	1206	Std	Std
1	R4	10	Resistor, Chip, 1/4W, 5%	1206	Std	Std
1	R6	357	Resistor, Chip, 1/4W, 1%	1206	Std	Std
1	R3	39K	Resistor, Chip, 1/2W, 5%	2010	Std	Std
1	T1		Xfmr, Center-tapped, Voice Over IP	0.500 x 0.370	H2019	Pulse
1	T2		XFMR, Flyback EFD15-SMD	0.875 x 0.675	PA1646NL	Pulse

Table 2. PMP1564_Rev A Bill of Materials (continued)

Count	RefDes	Value	Description	Size	Part No.	MFR
1	T3		Transformer, Driver, 330uH, 1500V isolation	0.210 × 0.210	P0926	Pulse
5	TP1–TP3, TP5, TP7		Test Point, Red, Thru Hole Color Keyed	0.100 × 0.100	5000	Keystone
2	TP4, TP6		Test Point, Black, Thru Hole Color Keyed	0.100 × 0.100	5001	Keystone
1	U2		IC, Photocoupler, 3750VRMS, 80-160% CTR	MF4	TCMT1107	Vishay
1	U3		IC, Shunt Regulator, 6V, 10mA, 1%	SOT23-5	TLV431ACDBVR	TI
1	U1		IC, IEEE 802.3af Integrated Primary Side Controller	PWP20	TPS23750PWP	TI

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
Low Power Wireless	www.ti.com/lpw

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265