
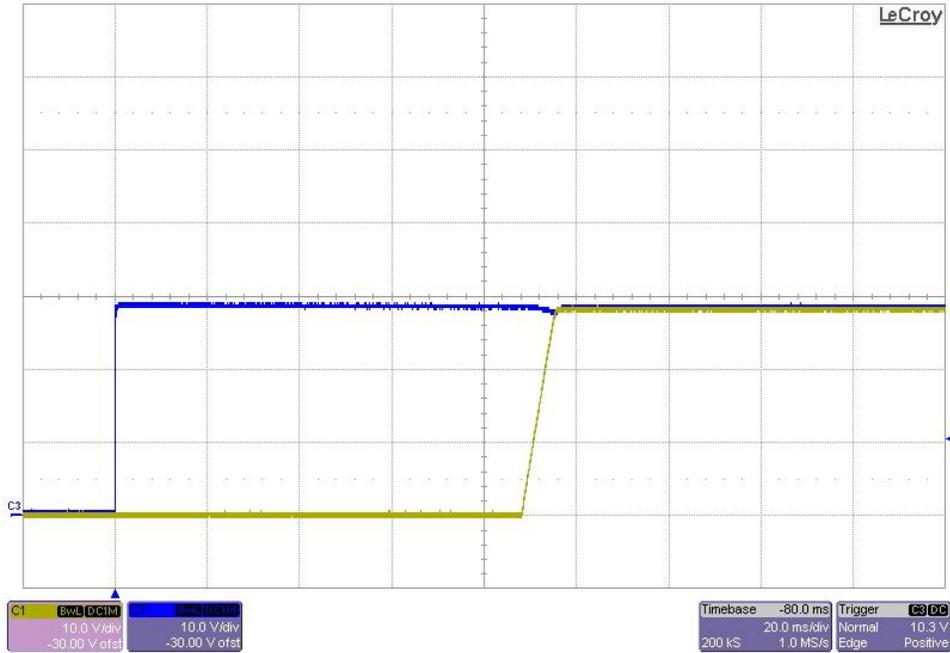


1 Startup

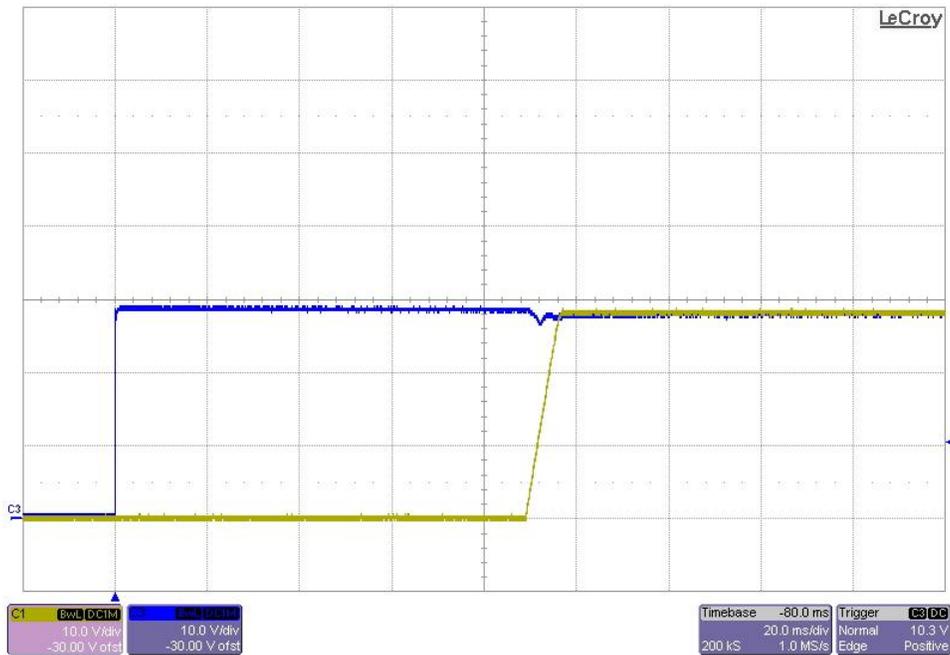The photo below shows the output voltage startup waveform after the application of 28V in. The 28.3V output was loaded to 0A. (10V/DIV, 20mS/DIV)




The photo below shows the output voltage startup waveform after the application of 28V in. The 28.3V output was loaded to 4.5A. (10V/DIV, 20mS/DIV)




2 Efficiency

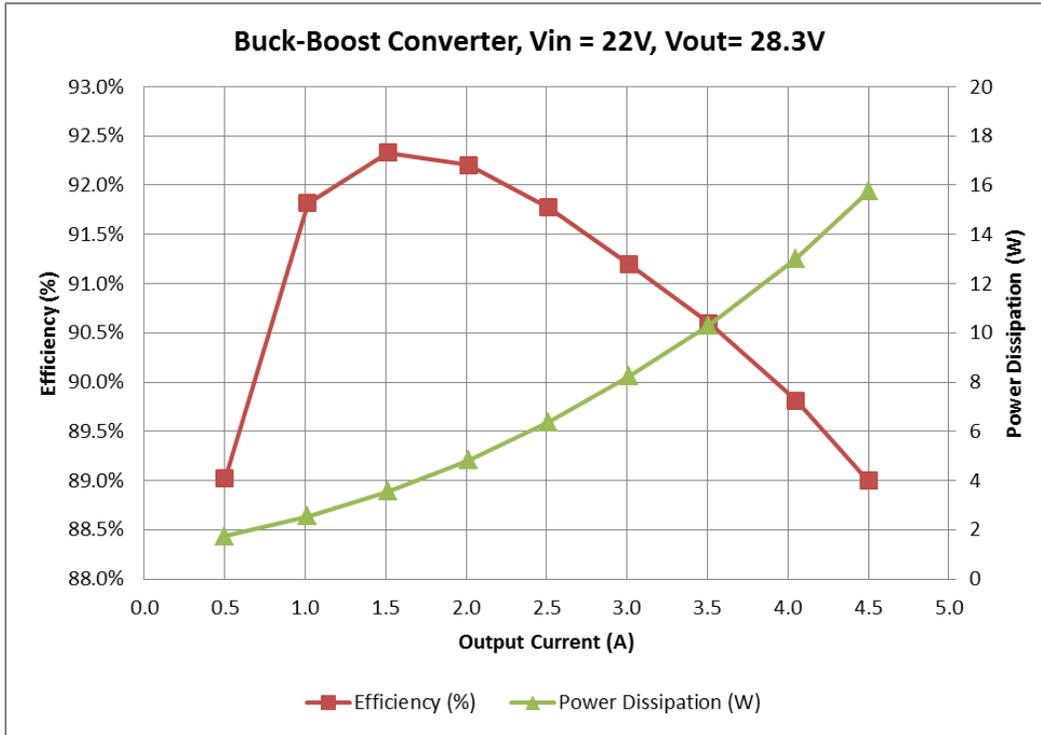
The buck-boost converter efficiency is shown below for $V_{in} = 22V$ and $V_{out} = 28.3V$ ($V_{trim} = 1.25V$).



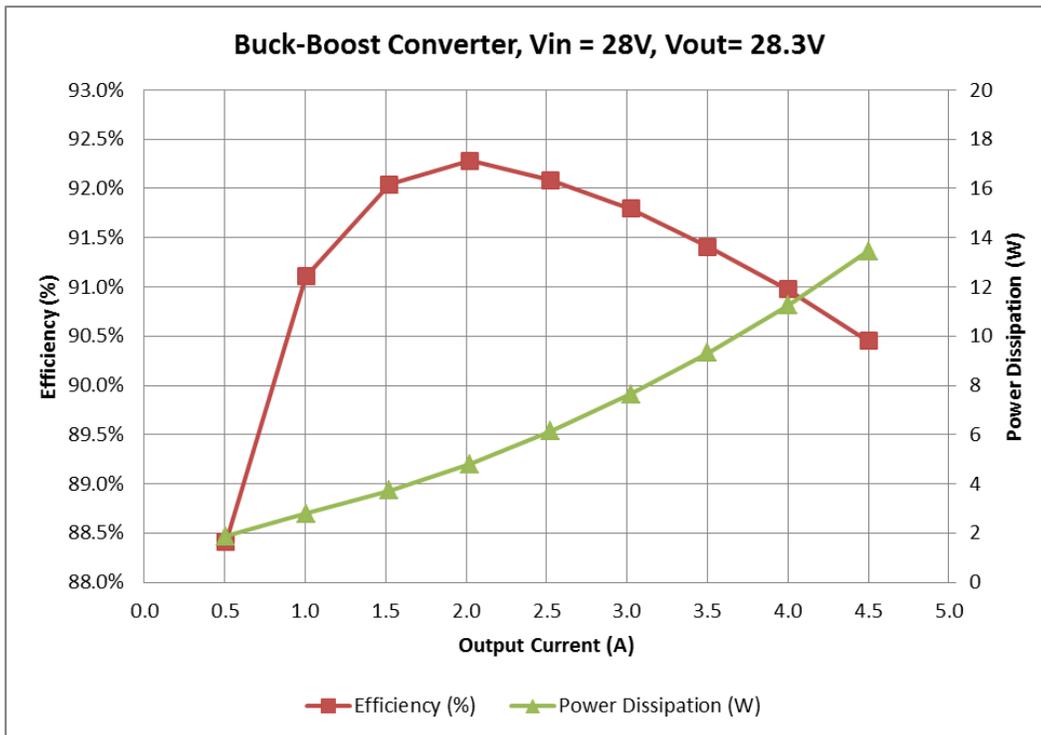The buck-boost converter efficiency is shown below for $V_{in} = 28V$ and $V_{out} = 28.3V$ ($V_{trim} = 1.25V$).




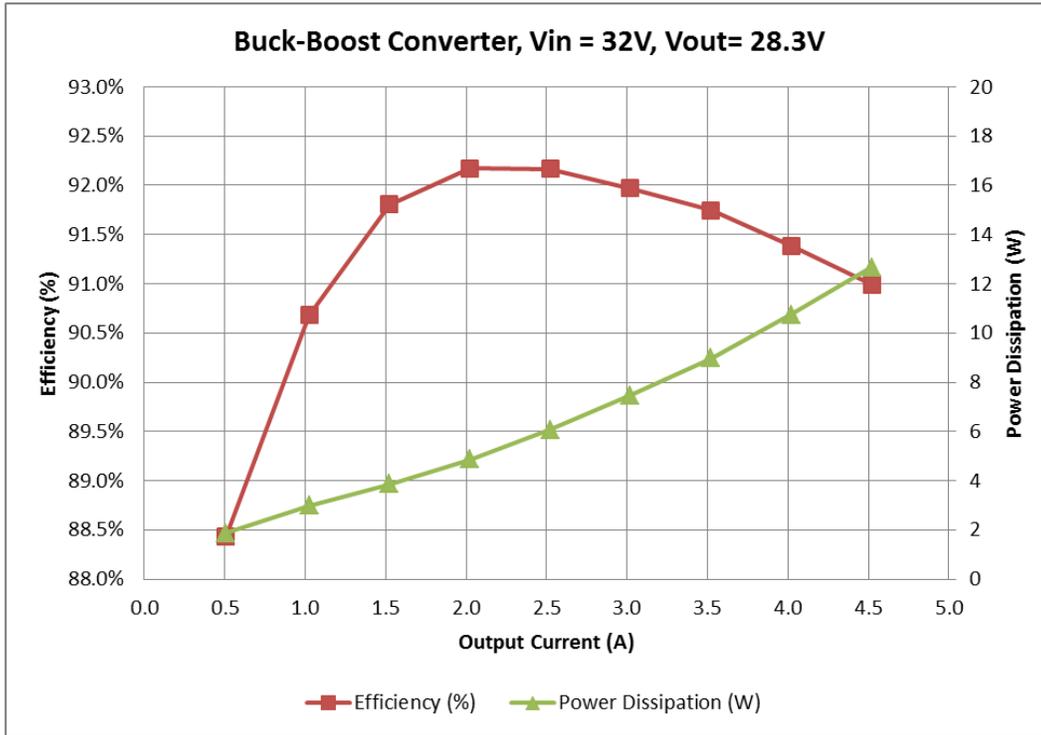The buck-boost converter efficiency is shown below for $V_{in} = 32V$ and $V_{out} = 28.3V$ ($V_{trim} = 1.25V$).




3 Output Ripple Voltage

The 28.3V output ripple voltage (AC coupled) is shown in the figure below. The image was taken with the output loaded to 4.5A. The input voltage is set to 22V. (100mV/DIV, 2uS/DIV)

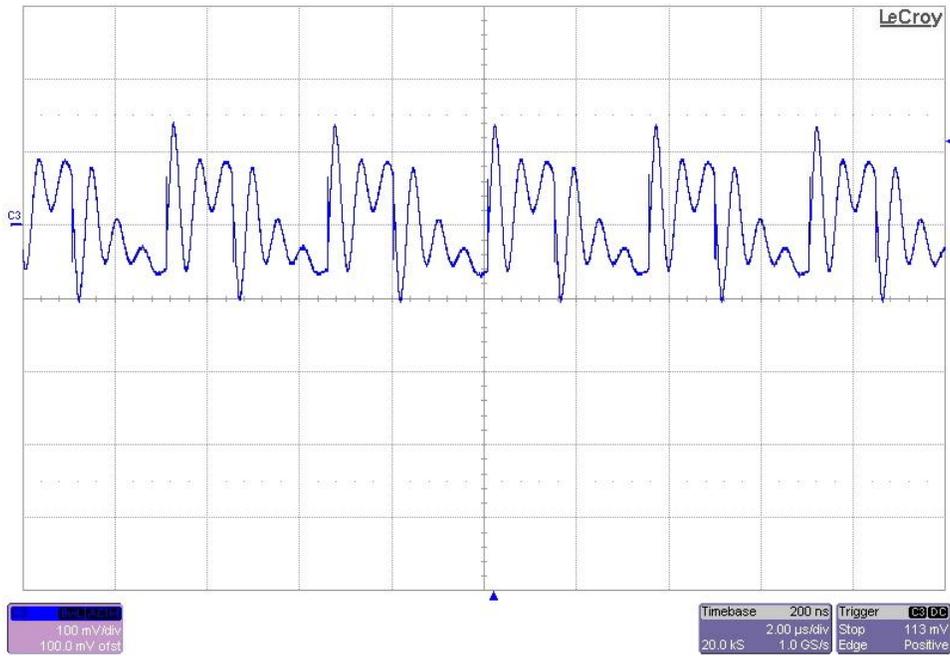


The 28.3V output ripple voltage (AC coupled) is shown in the figure below. The image was taken with the output loaded to 4.5A. The input voltage is set to 28V. (100mV/DIV, 2uS/DIV)

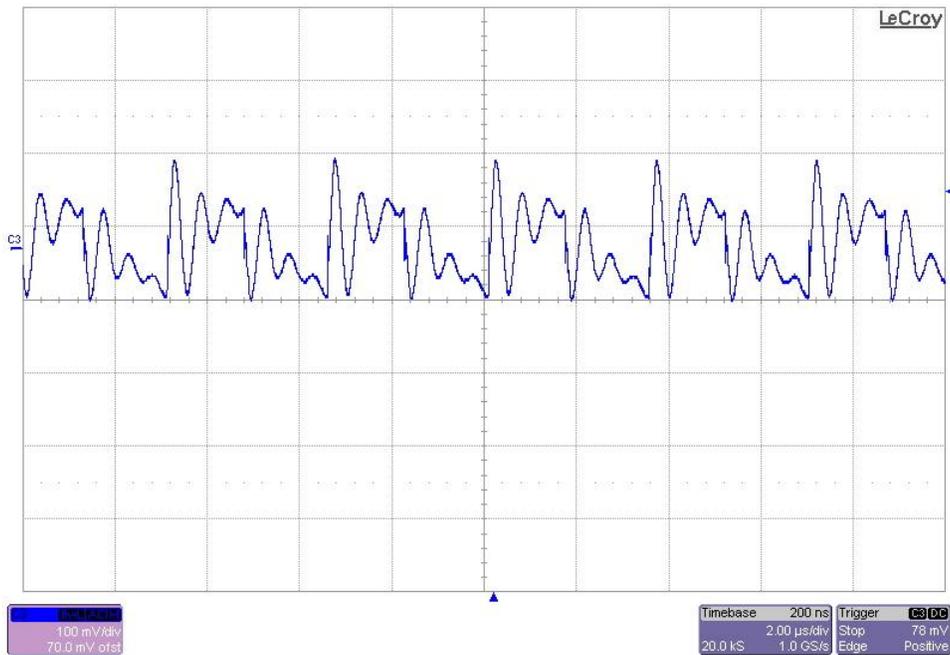


The 28.3V output ripple voltage (AC coupled) is shown in the figure below. The image was taken with the output loaded to 4.5A. The input voltage is set to 32V. (100mV/DIV, 2uS/DIV)



The 28.3V output ripple voltage (AC coupled) is shown in the figure below. The image was taken with the output loaded to 3A. The input voltage is set to 28V. (100mV/DIV, 2uS/DIV)

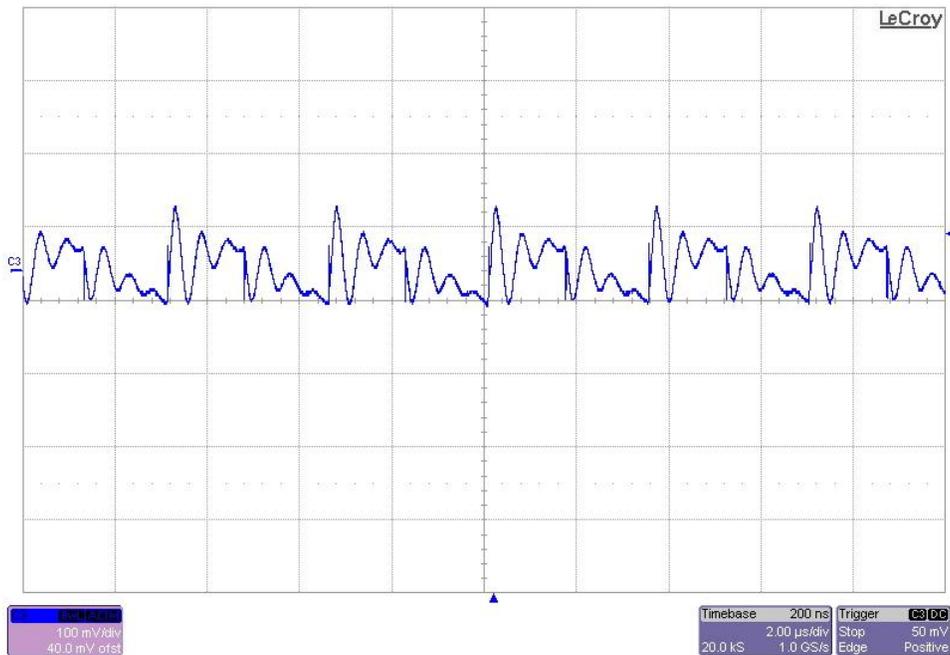


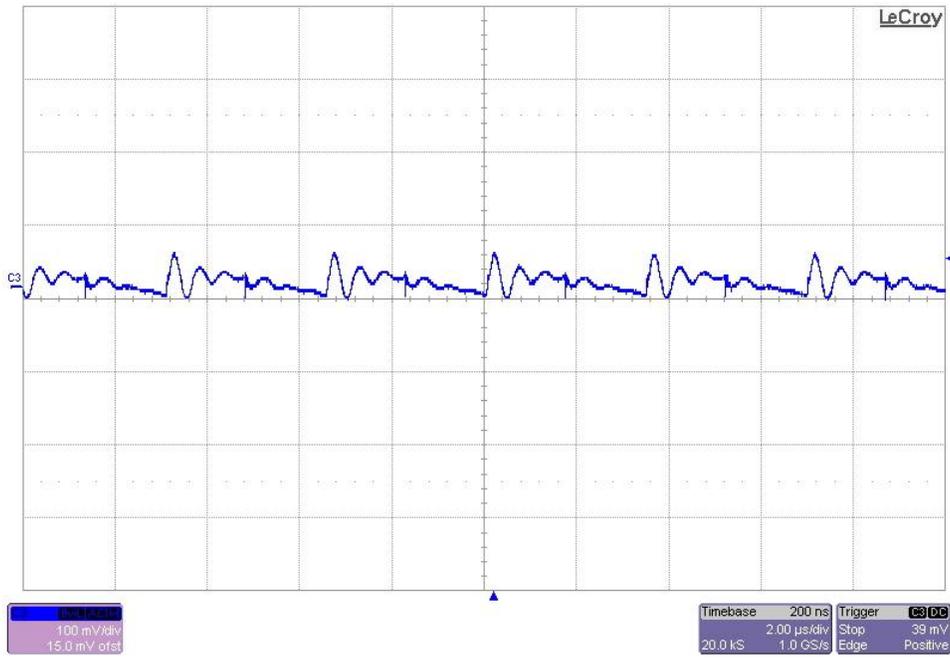The 28.3V output ripple voltage (AC coupled) is shown in the figure below. The image was taken with the output loaded to 1A. The input voltage is set to 28V. (100mV/DIV, 2uS/DIV)




4 Load Transients

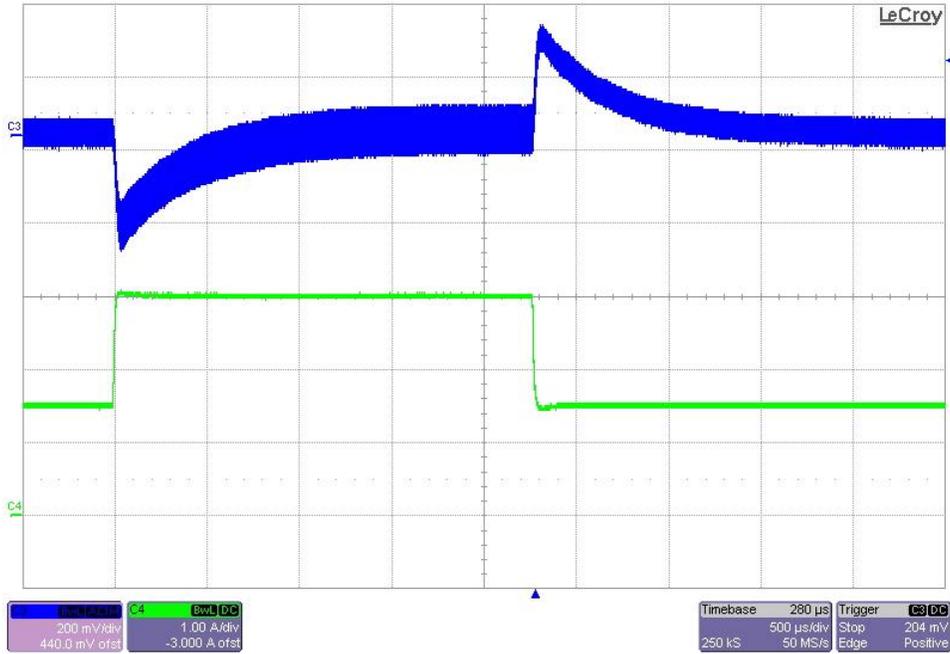
The photo below shows the 28.3V output voltage (ac coupled) when the load current is stepped between 1.5A and 3A. $V_{in} = 28V$. (200mV/DIV, 1A/DIV, 500uS/DIV)



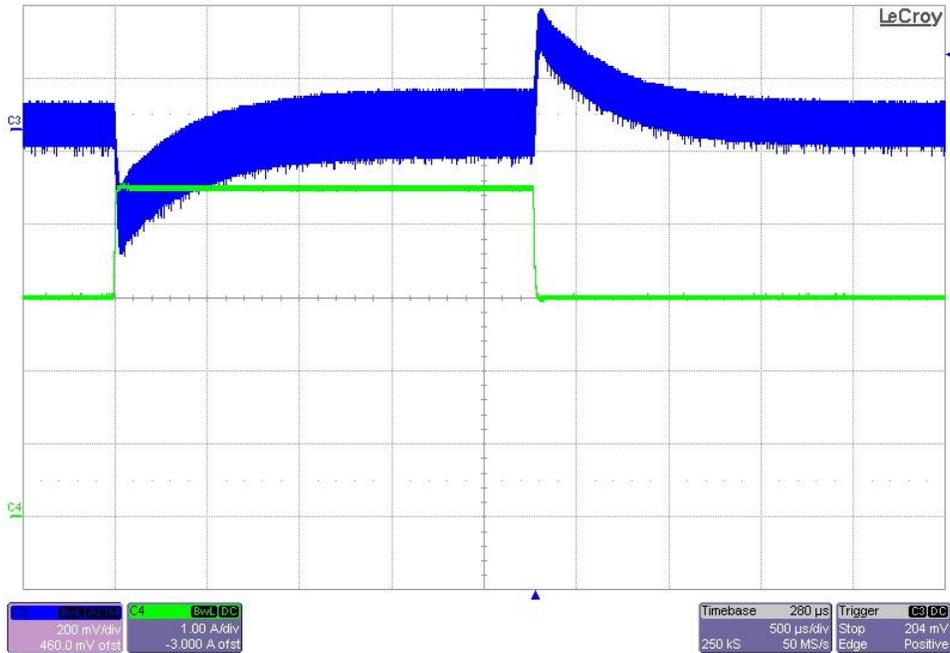The photo below shows the 28.3V output voltage (ac coupled) when the load current is stepped between 3A and 4.5A. $V_{in} = 28V$. (200mV/DIV, 1A/DIV, 500uS/DIV)




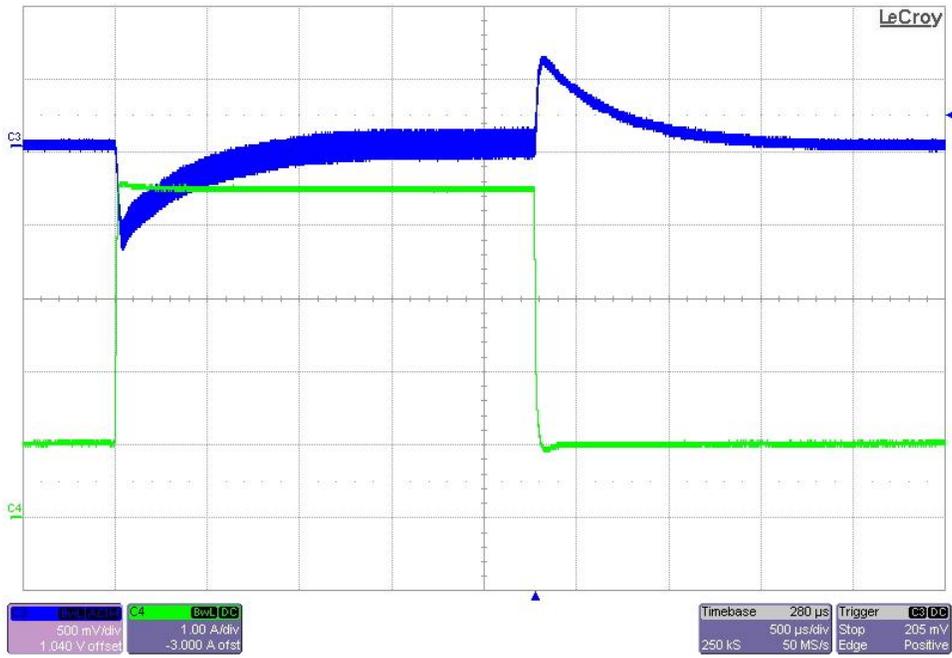The photo below shows the 28.3V output voltage (ac coupled) when the load current is stepped between 1A and 4.5A. $V_{in} = 28V$.
(500mV/DIV, 1A/DIV, 500uS/DIV)




5 Switch Node Waveforms

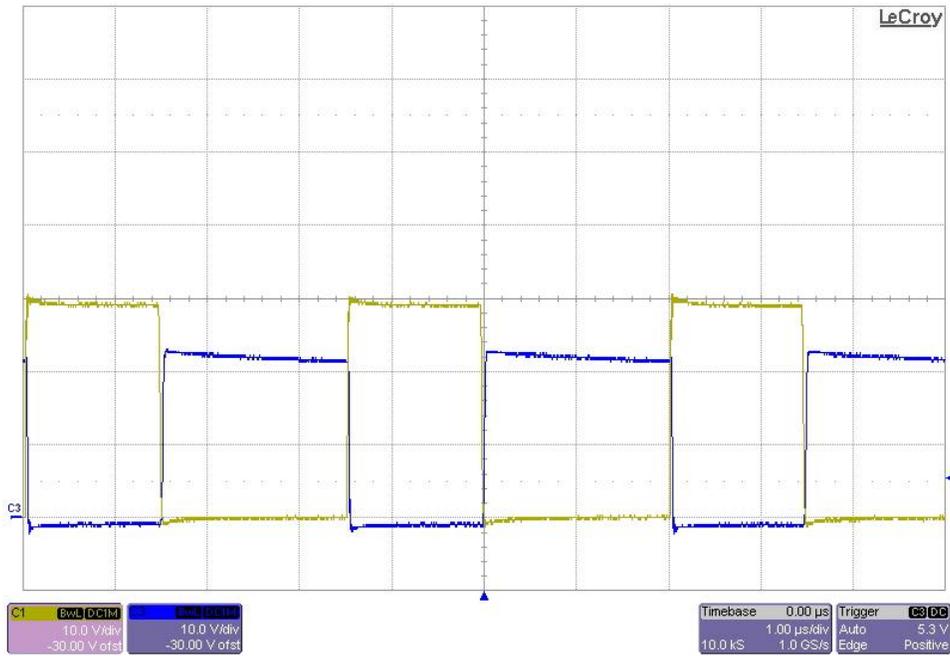
The photo below shows the Q1 FET switching voltage (TP3, blue) and the Q2 FET switching node (TP4, yellow). The input voltage is 22V and the output is loaded to 4.5A. (10V/DIV, 1uS/DIV)



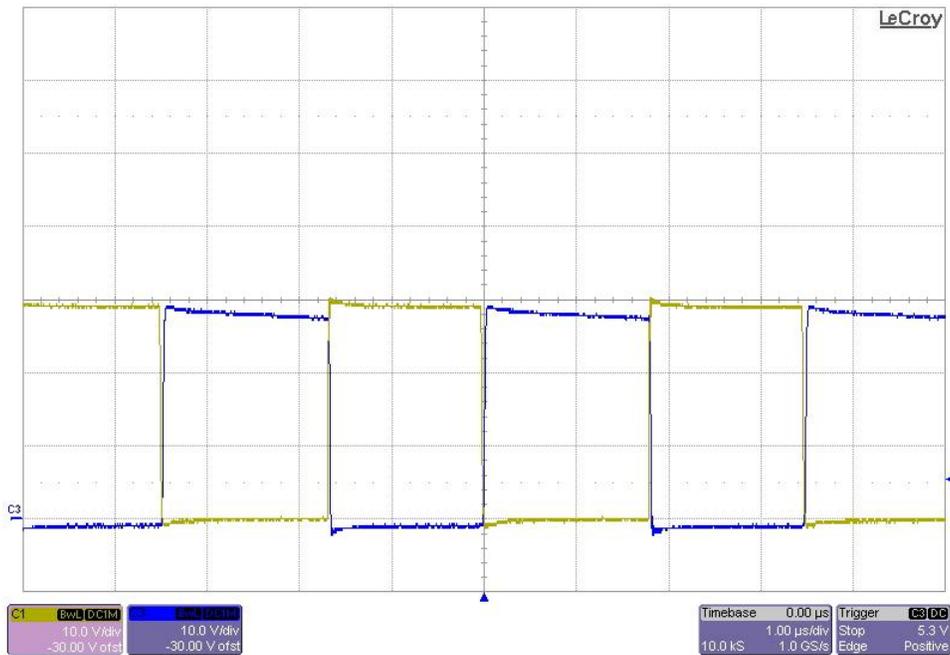The photo below shows the Q1 FET switching voltage (TP3, blue) and the Q2 FET switching node (TP4, yellow). The input voltage is 28V and the output is loaded to 4.5A. (10V/DIV, 1uS/DIV)



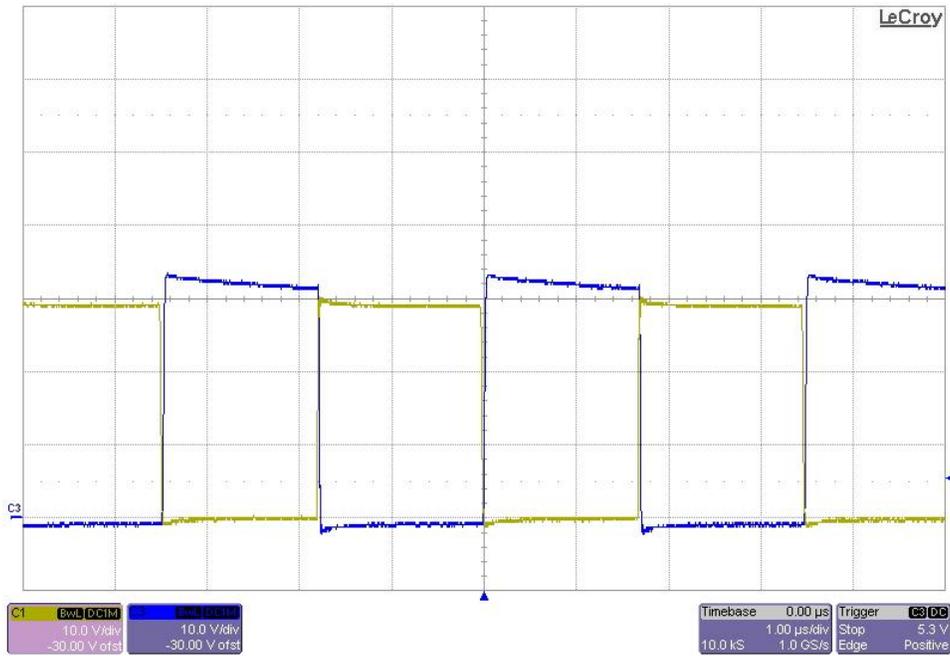The photo below shows the Q1 FET switching voltage (TP3, blue) and the Q2 FET switching node (TP4, yellow). The input voltage is 32V and the output is loaded to 4.5A. (10V/DIV, 1uS/DIV)



6 Loop Gain

The plot below shows the loop gain with the input voltage set to 22V and 32V. The output voltage was set to 23V @ 4.5A ($V_{trim} = 1.57V$).

Loop Gain ($V_{in} = 32V$)


BW: 15.5KHz

PM: 66 degrees

Loop Gain ($V_{in} = 22V$)

BW: 8.16KHz

PM: 50 degrees

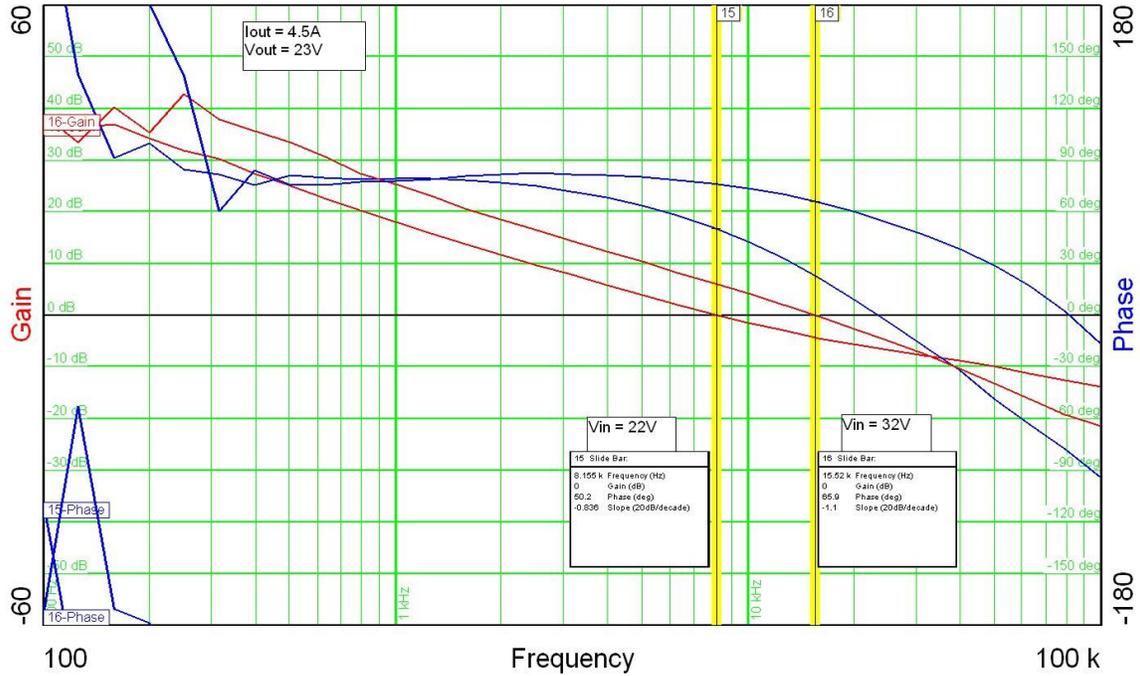


The plot below shows the loop gain with the input voltage set to 22V and 32V. The output voltage was set to 33.6V @ 4.5A ($V_{trim} = 0.93V$).

Loop Gain ($V_{in} = 32V$)
 Loop Gain ($V_{in} = 22V$)

BW: 7.78KHz
 BW: 6.13KHz

PM: 59 degrees
 PM: 54 degrees

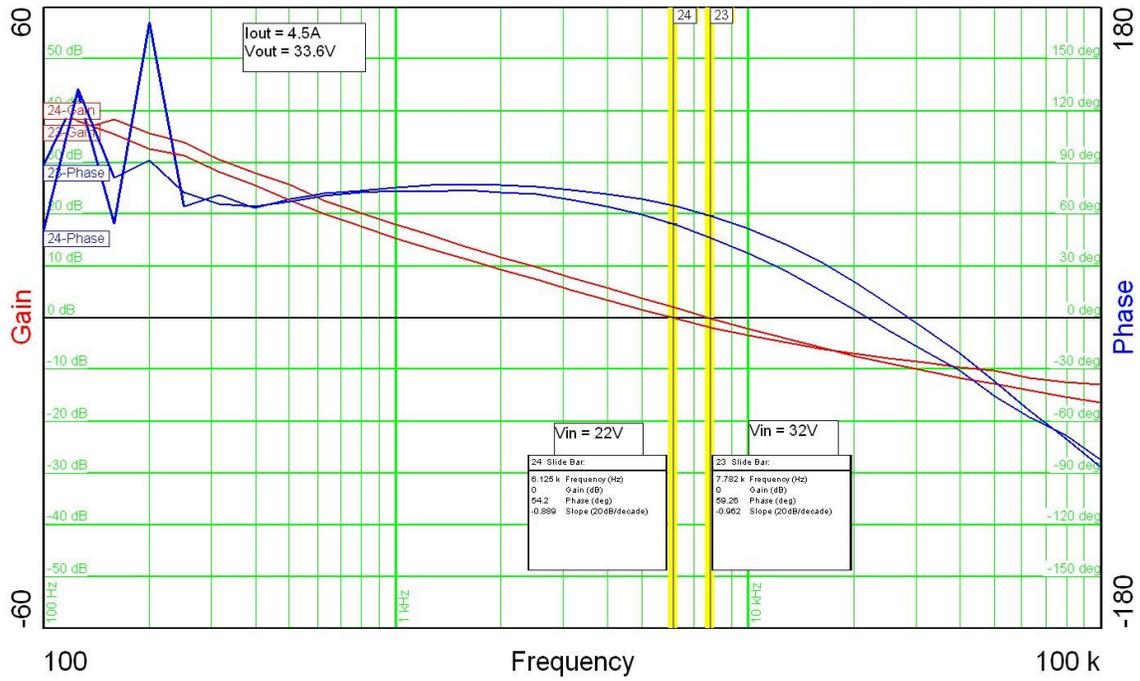


The plot below shows the loop gain with the input voltage set to 28V. The output voltage was set to 28.3V @ 1A, 3A, and 4.5A ($V_{trim} = 1.25V$).

Loop Gain (1A)
 Loop Gain (3A)
 Loop Gain (4.5A)


BW: 7.95KHz
 BW: 7.95KHz
 BW: 7.95KHz

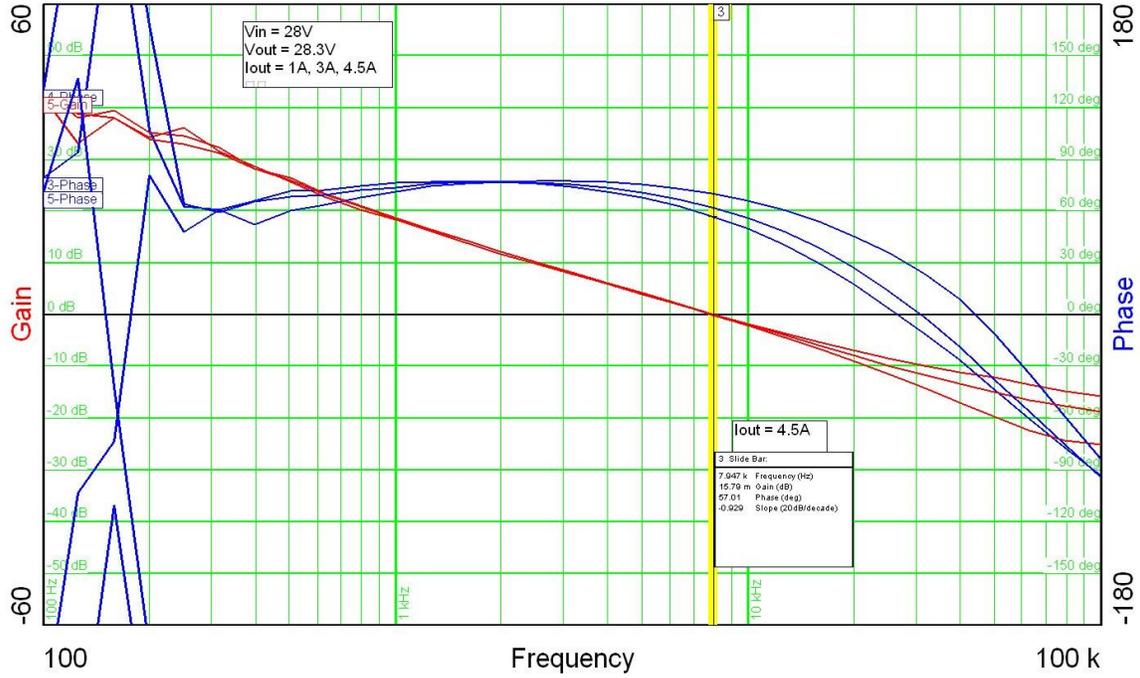PM: 70 degrees
 PM: 61 degrees
 PM: 57 degrees



7 Photo

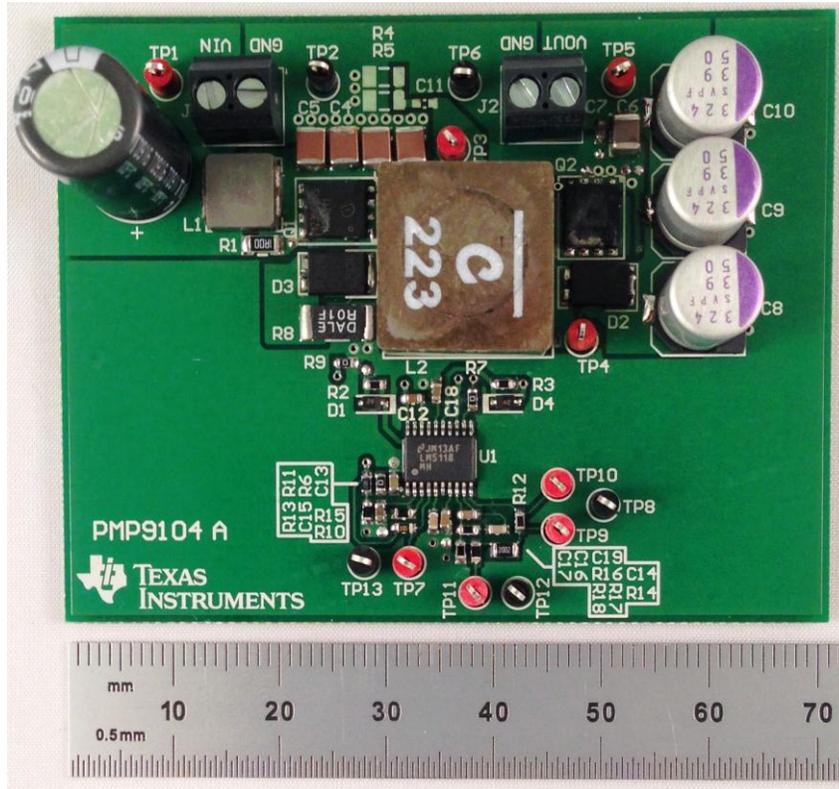The photo below shows the PMP9104 REVB assy.



8 Thermal Image

A thermal image is shown below operating at 28V input and 28.3V@3A output (room temp, no airflow).



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated