


Test Report: PMP21557

Compact low-loss isolated four-output flybuck reference design



Description

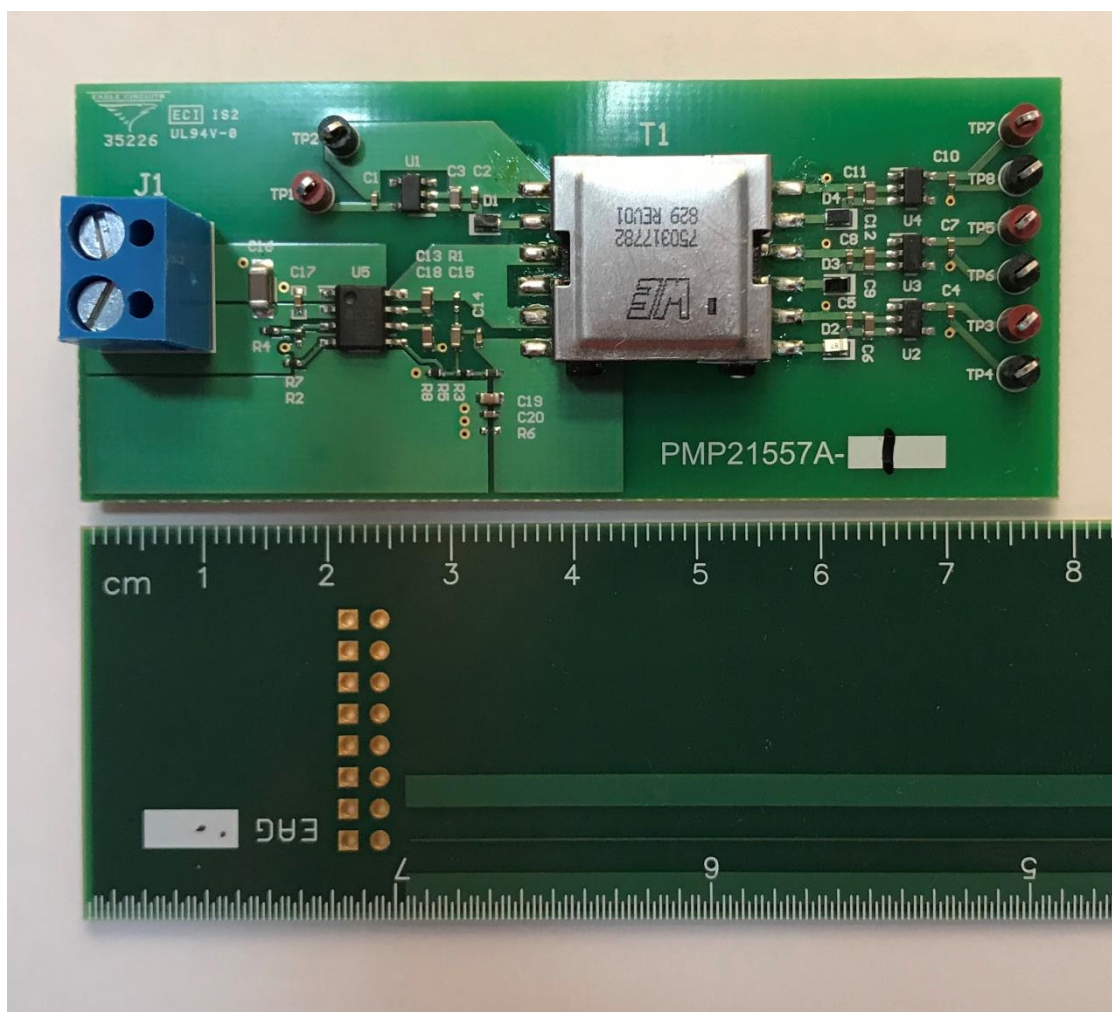PMP21557 is a four-output flybuck that uses the LM25017 converter. The four 3.3V outputs are isolated for 1250 VAC. Each output stage has a TLV75533 Linear Regulator to create a more accurate output voltage.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage Range	19V-29V, 24V nominal
Output Voltage	3.3V +/- 1%
Output Current Per Rail	25mA nominal, 80mA max
Switching Frequency	500kHz

2 Testing and Results

2.1 Efficiency Data

The table below shows the efficiency data for PMP21557. The top row was tested with all outputs on full load. The other two rows were tested with two outputs full load and the other two with no load. In those rows the *Italicized* numbers denote the non-loaded outputs.

Input			Output 1			Output 2		
Vin [V]	Iin [A]	Pin [W]	Vout [V]	Iout[A]	Pout [W]	Vout [V]	Iout[A]	Pout [W]
23.686	0.0574	1.360	3.289	0.079	0.261	3.295	0.080	0.262
23.832	0.030867	0.736	3.296	<i>5.00E-06</i>	<i>0.000</i>	3.302	<i>5.00E-06</i>	<i>0.000</i>
23.834	0.03056	0.728	3.289	0.079	0.260575	3.295	0.080	0.262253

Output 3			Output 4			Total	Calculations	
Vout [V]	Iout[A]	Pout [W]	Vout [V]	Iout[A]	Pout [W]	Pout [W]	EFF [%]	LOSS [W]
3.296	0.080	0.262	3.291	0.079	0.261	1.047	77.00%	0.313
3.296	0.080	2.62E-01	3.291	0.079	2.61E-01	0.524	71.23%	0.212
3.303	<i>5.00E-06</i>	<i>0.000</i>	3.297	<i>5.00E-06</i>	<i>0.000</i>	0.523	71.79%	0.206

2.2 Dimensions

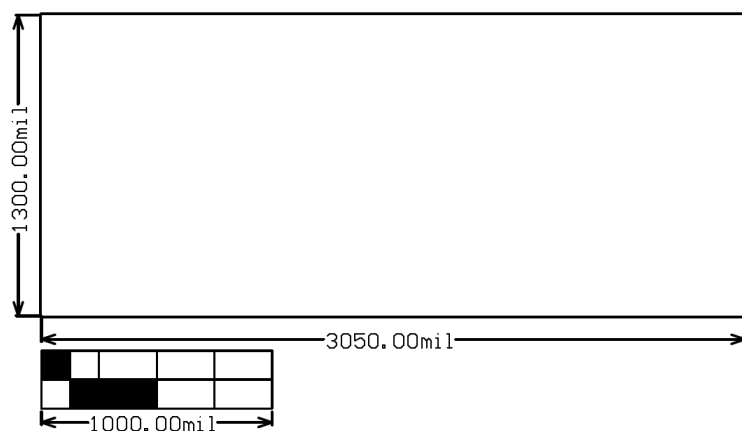


Figure 1. Board dimensions of PMP21557.

3 Waveforms

3.1 Switching

The switch node was measured with 24V input Voltage and all outputs at full load. Measured switching frequency = 434.8kHz, global maxima = 26.9V, global minima = -2.6V

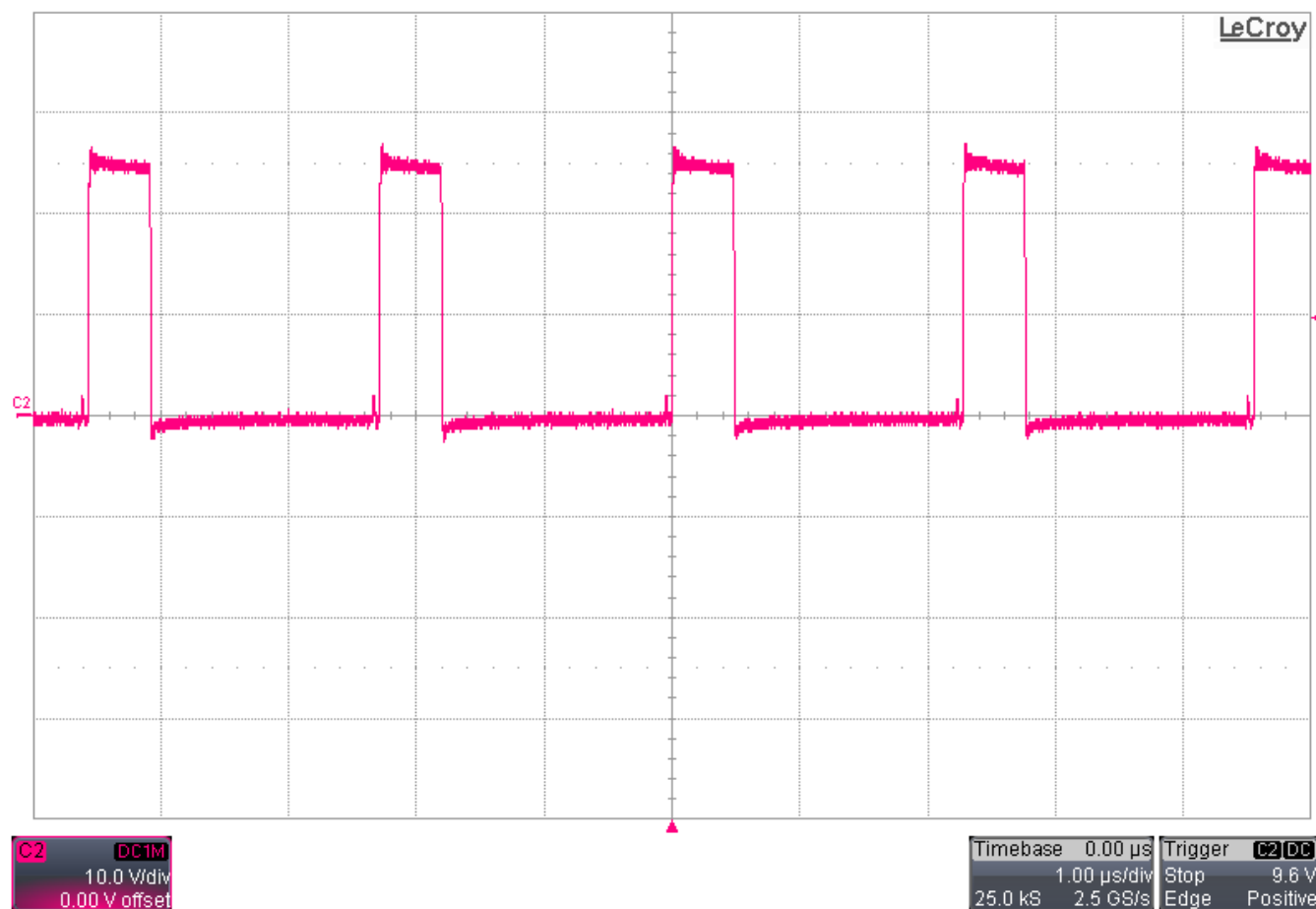


Figure 2. Primary Switching Node Waveform

3.2 Output Voltage Ripple

Measurements were taken using the tip and barrel method across the output caps of the rail.

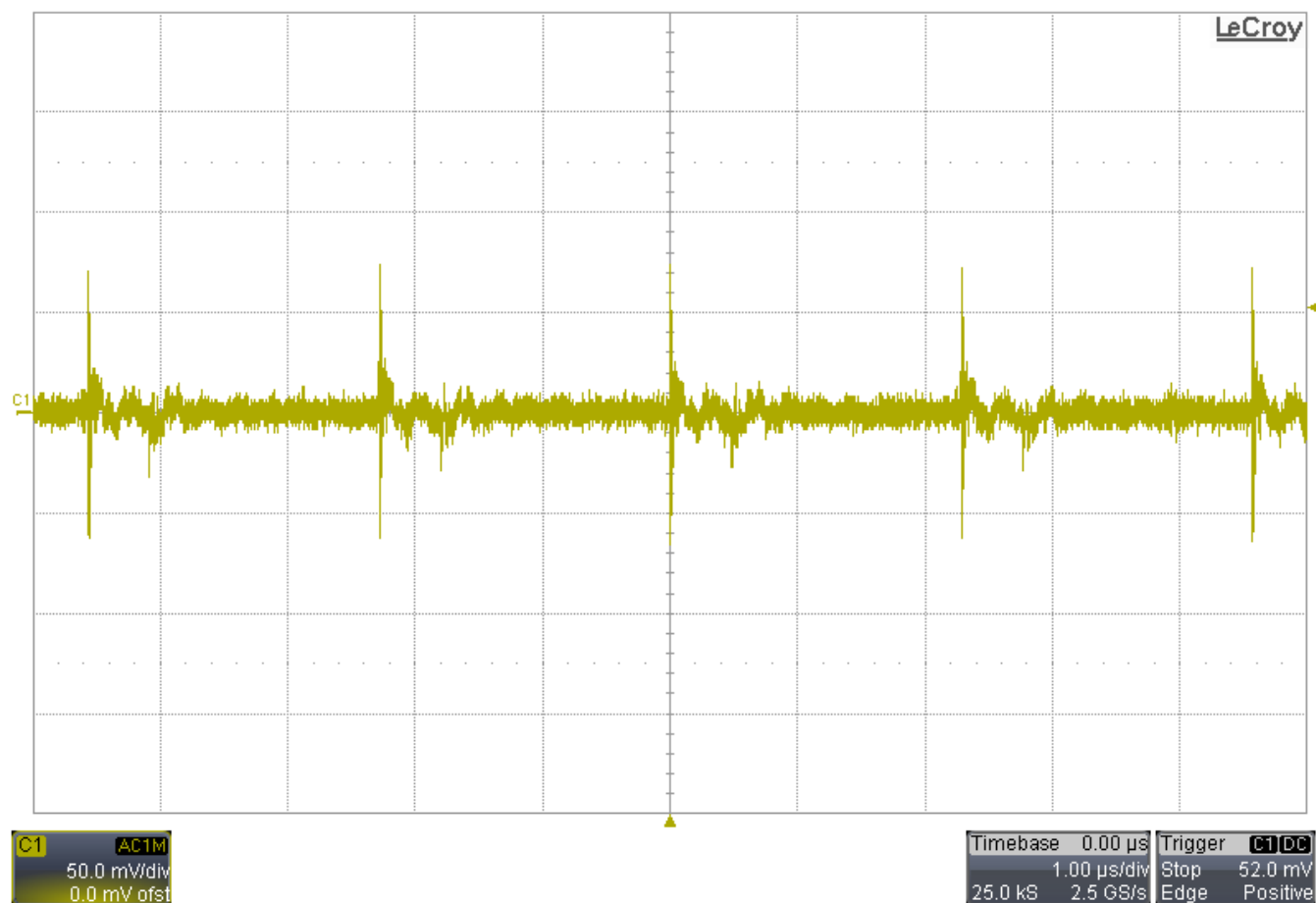


Figure 3. Output 1 Voltage Ripple (C1)

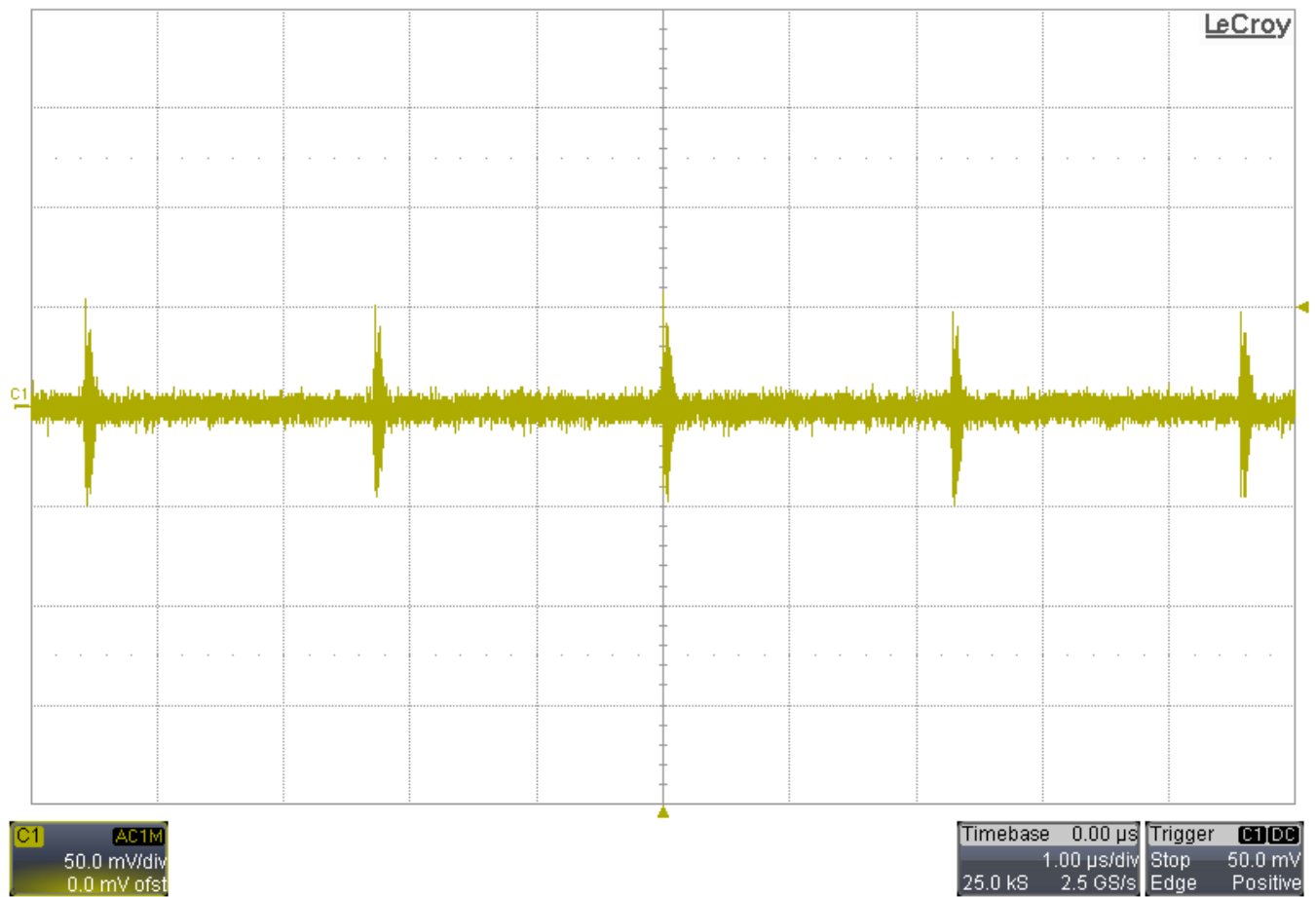


Figure 4. Output 2 Voltage Ripple (C4)

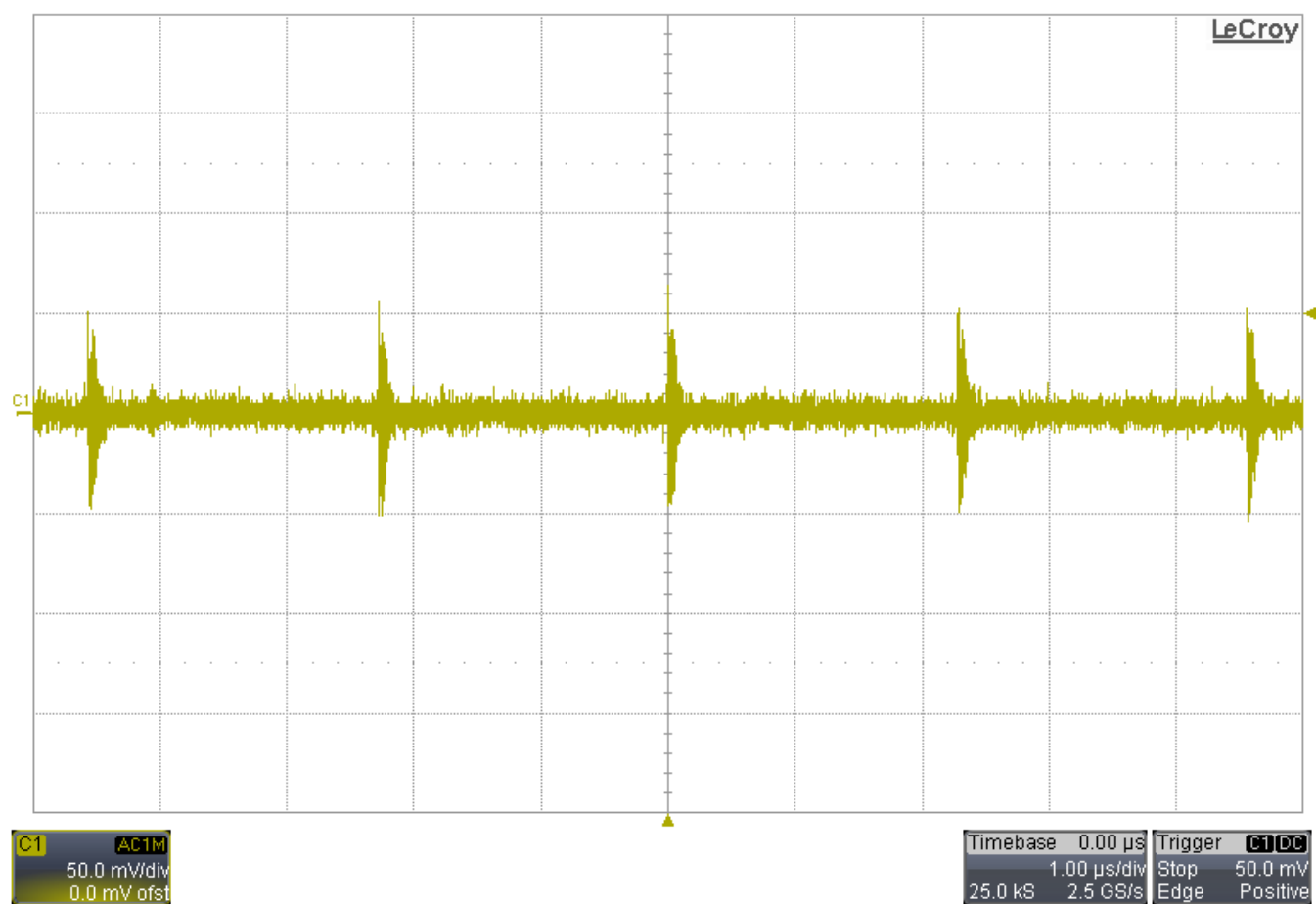


Figure 5. Output 3 Voltage Ripple (C7)

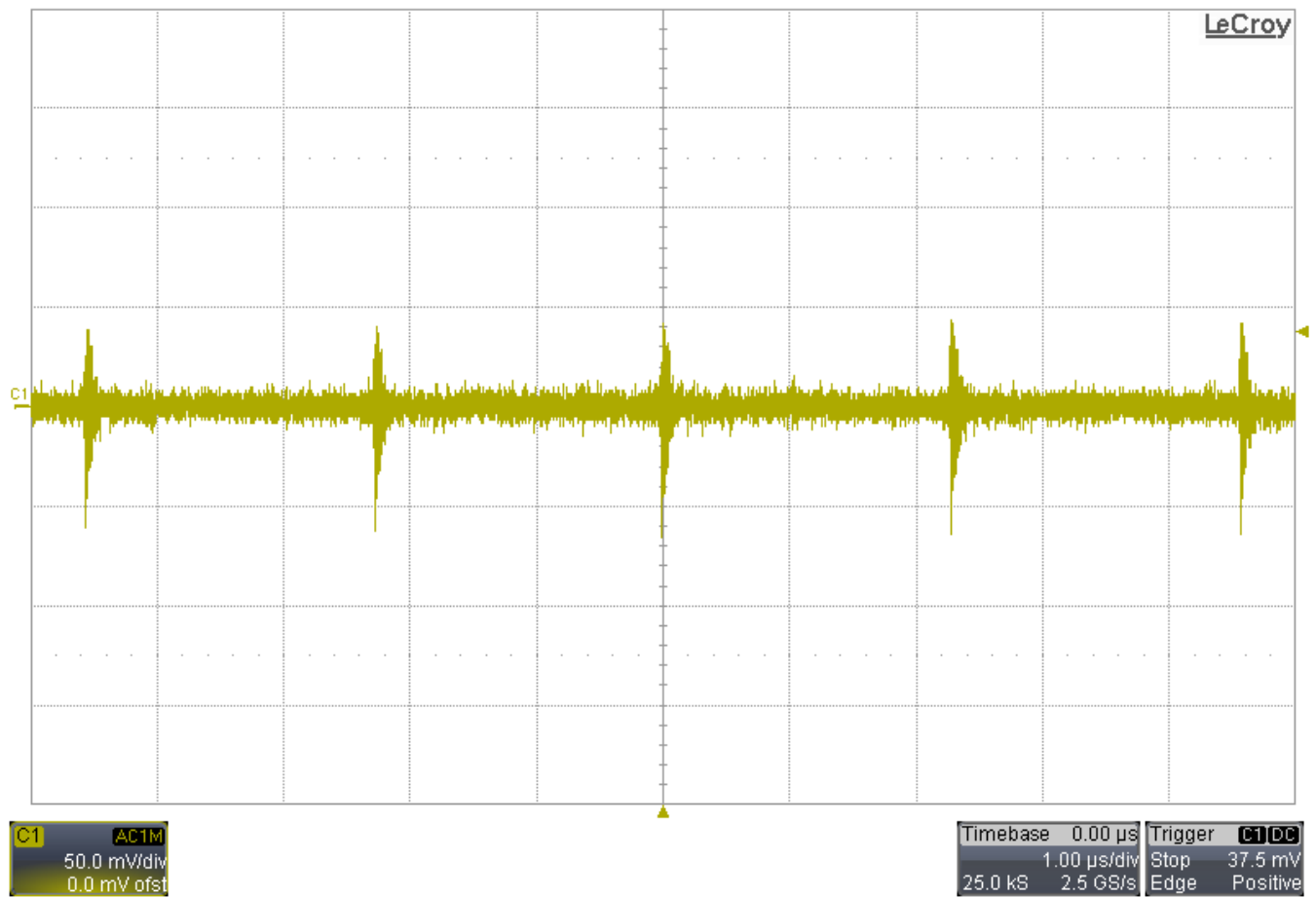


Figure 6. Output 4 Voltage Ripple (C10)

3.3 Load Transients

For the transient testing, V1 and V3 were full loaded. V2 and V4 were loaded with a load step between 10mA for 10ms and 80mA for 20ms. Slew rate was set to 80mA/μs. The output voltage measurements were taken at the output test points. The plots show the high accuracy of the linear regulators during transients.

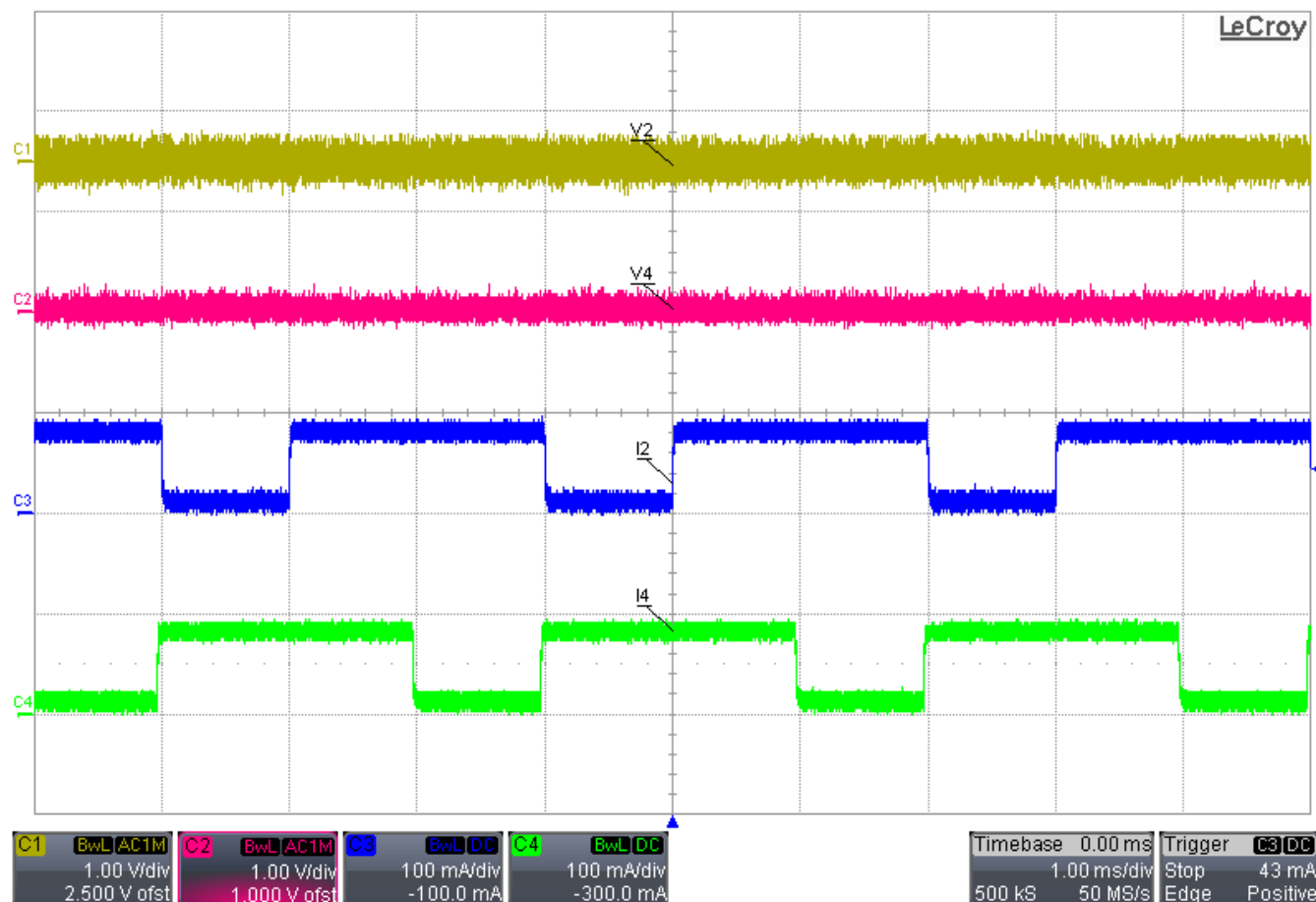


Figure 7. Load Transient on Outputs 2 and 4. Output Voltages 2 and 4 are shown.

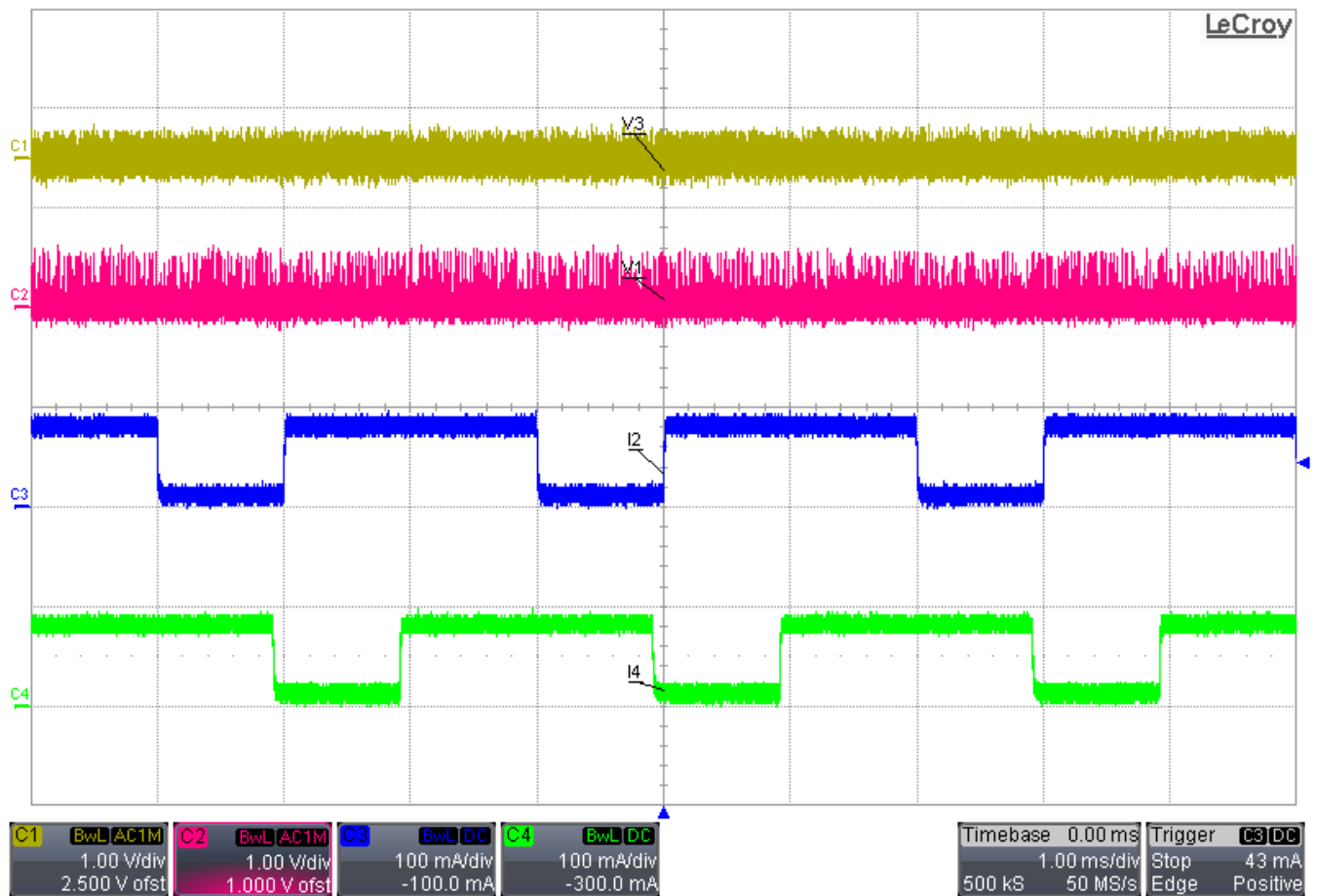


Figure 8. Load Transient on Outputs 2 and 4. Output Voltages 1 and 3 are shown.

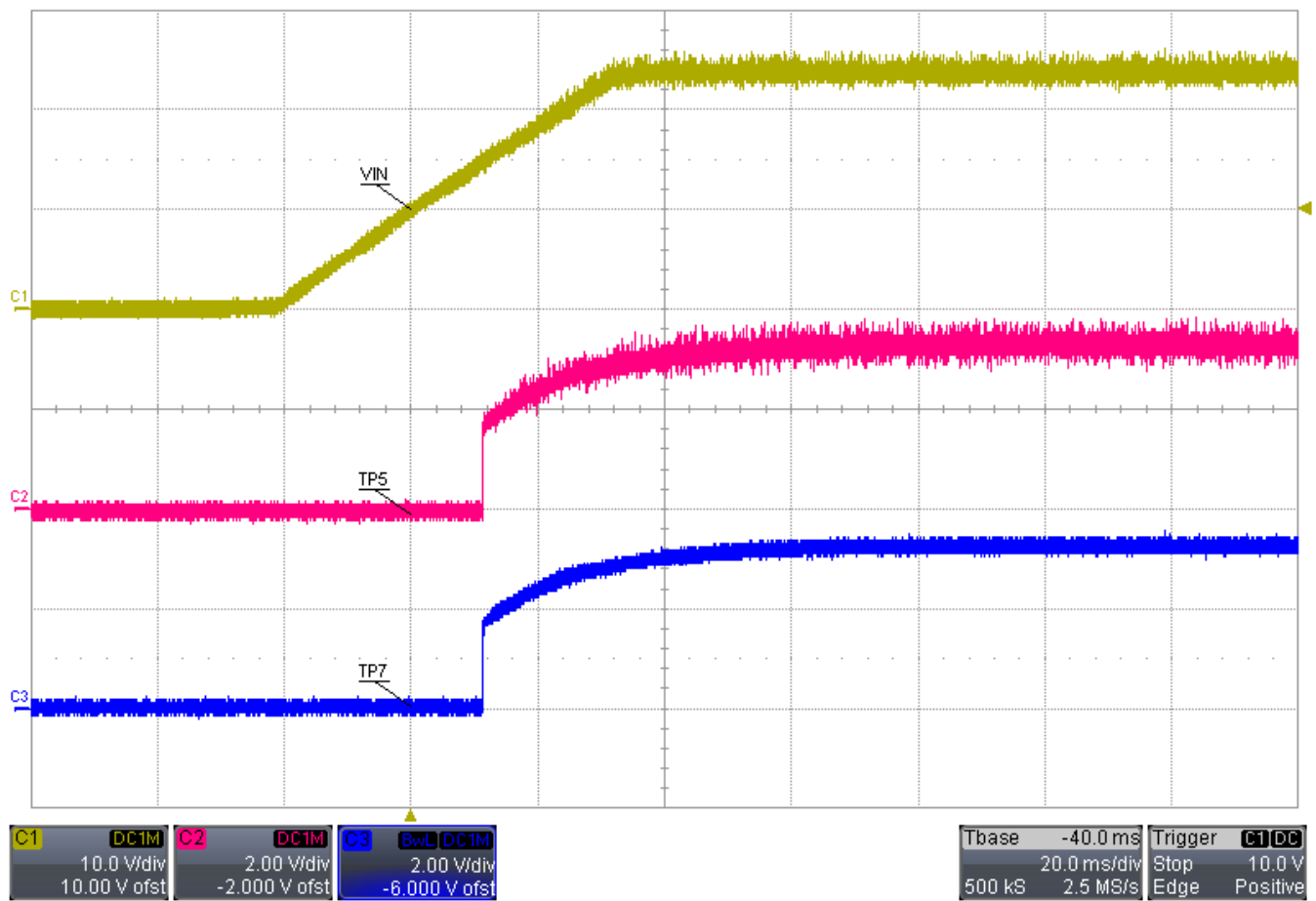


Figure 10. Start up voltages of the input and outputs 3 and 4.

3.5 Power Down Sequence

Power down sequencing was measured by removing a 24VDC source from the input. All of the outputs were set to max load (80mA).

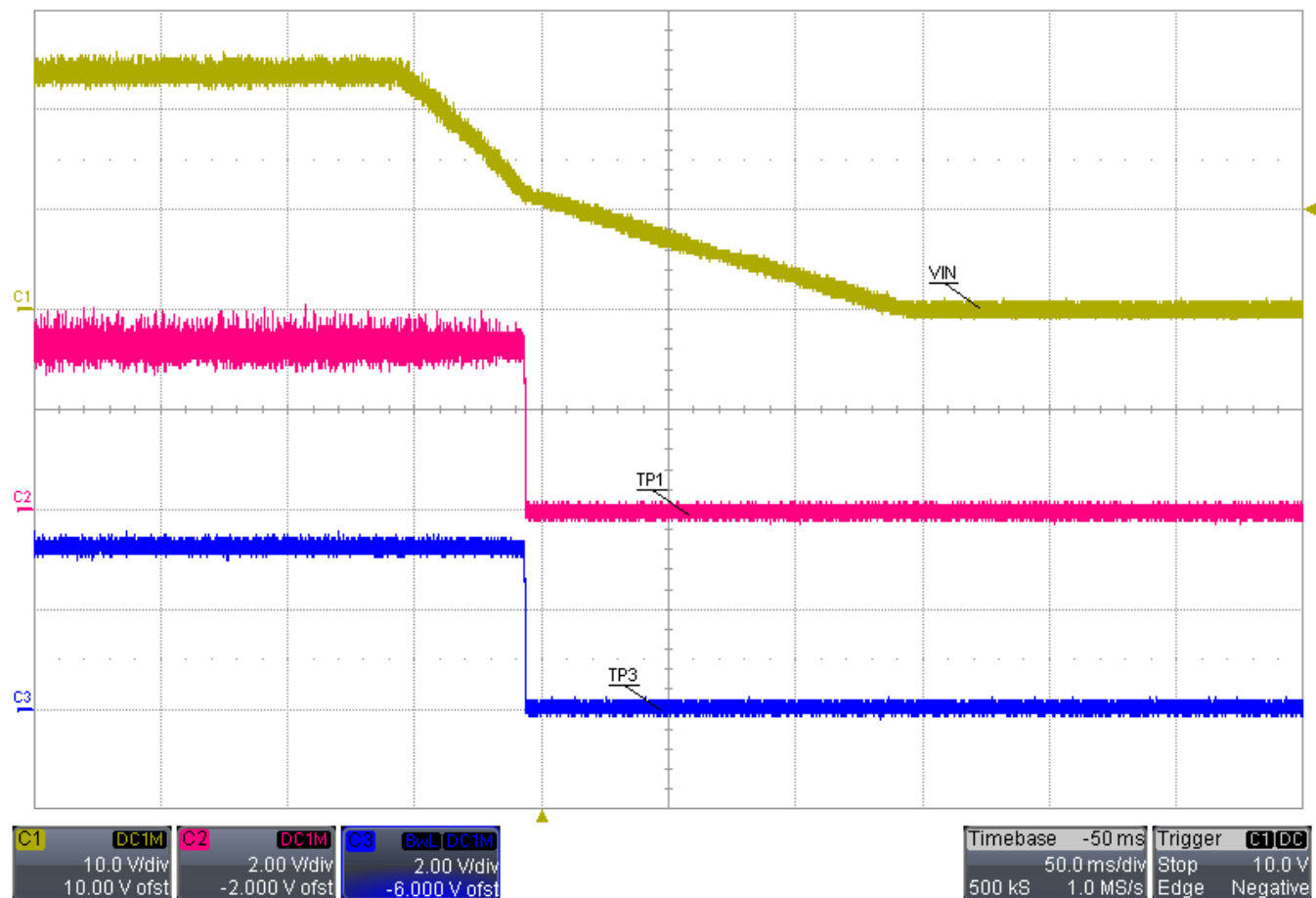


Figure 11. Power down voltages of the input and outputs 1 and 2.

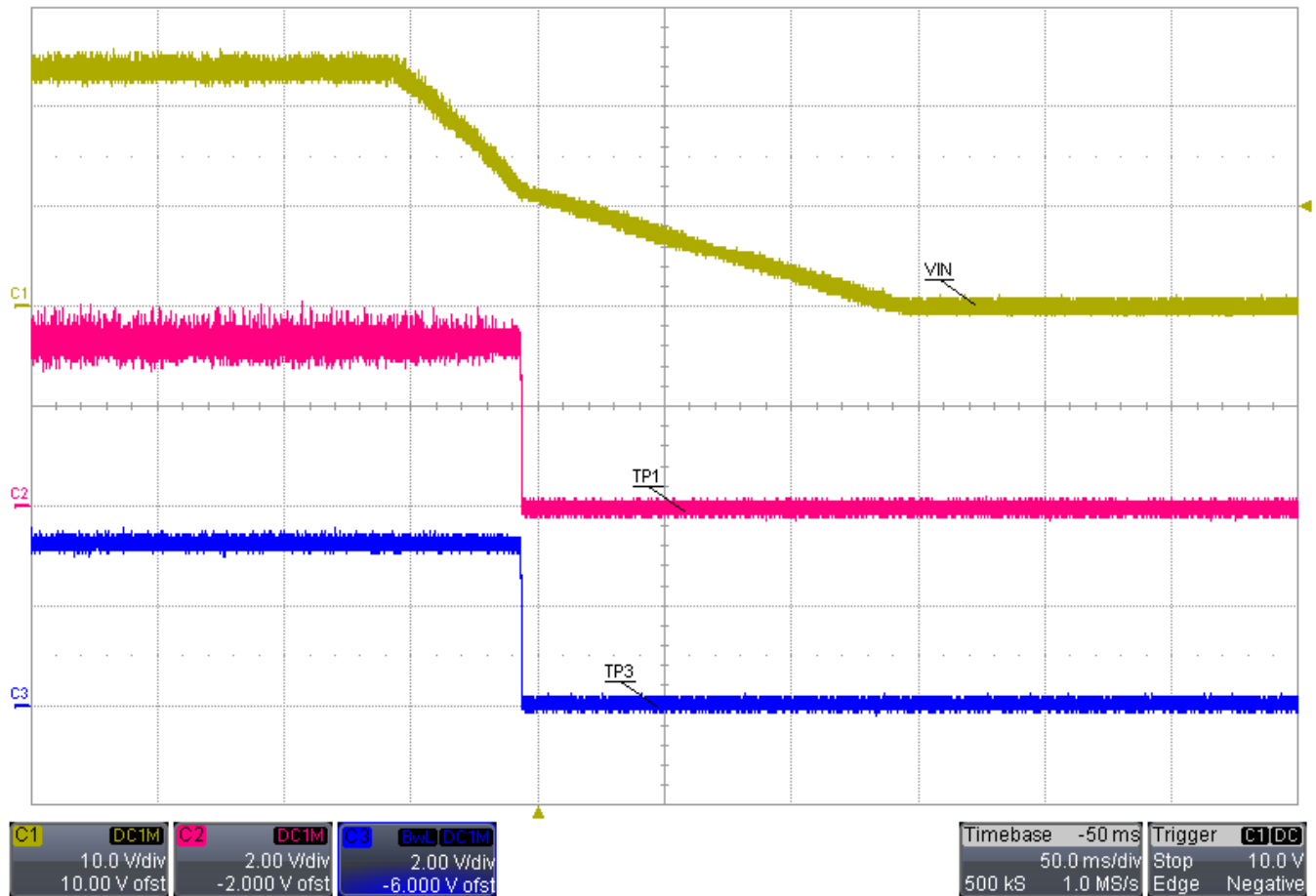


Figure 12. Power down voltages of the input and outputs 3 and 4.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated