

Test Report: PMP30781


Tiny Automotive 2-W Bias Power Supply Reference Design



Description

This reference design provides a tiny auxiliary +12 V supply for general purpose. In this case, SEPIC topology supports wide input range from 6 V to 60 V. Even at input as low as 3.5 V, this solution is able to provide half of the output power. Another benefit of SEPIC is low reflected ripple, resulting in less conducted emissions. The small magnetizing inductance sets Right Half Plane Zero fairly high, so loop bandwidth can be increased, and allows a small output capacitance by keeping good transient response.

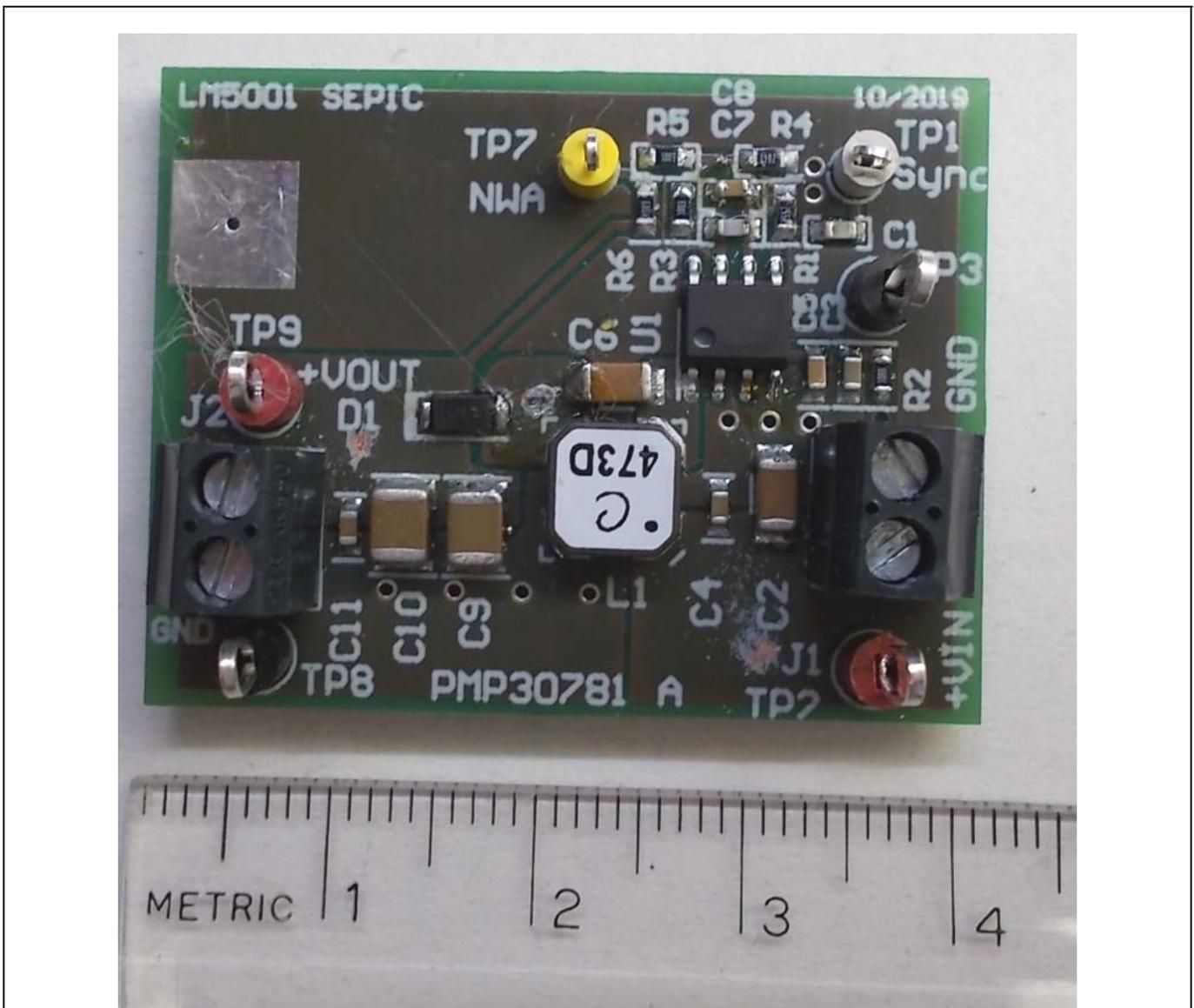This design is the complementary solution to PMP30373, inverting SEPIC (=Cuk) to provide negative output voltage.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage	6 V to 60 V
Output Voltage	12 V
Maximum Output Current	0.2 A
Switching Frequency	500 kHz
Topology	SEPIC

Measured switching frequency at prototype 480kHz;

Provides 200mA full power as low as 5V input voltage;

Provides 150mA as low as 4V input voltage;

Provides 100mA+ as low as 3.5V input voltage.

1.2 Considerations

The switching frequency is around 480 kHz.

Unless otherwise indicated the measurements were done with 0.2 A output current adjusted by a resistor.

2 Testing and Results

2.1 Efficiency Graphs

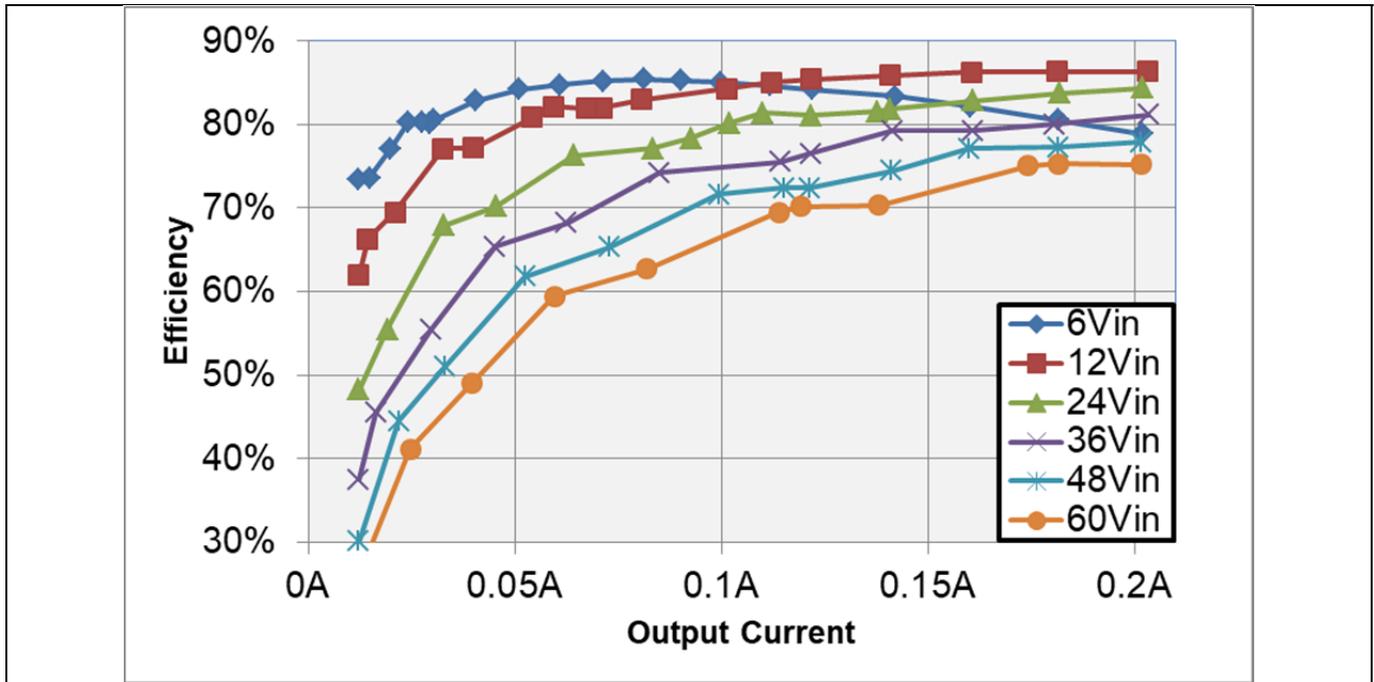


Figure 1 Efficiency vs Output Current

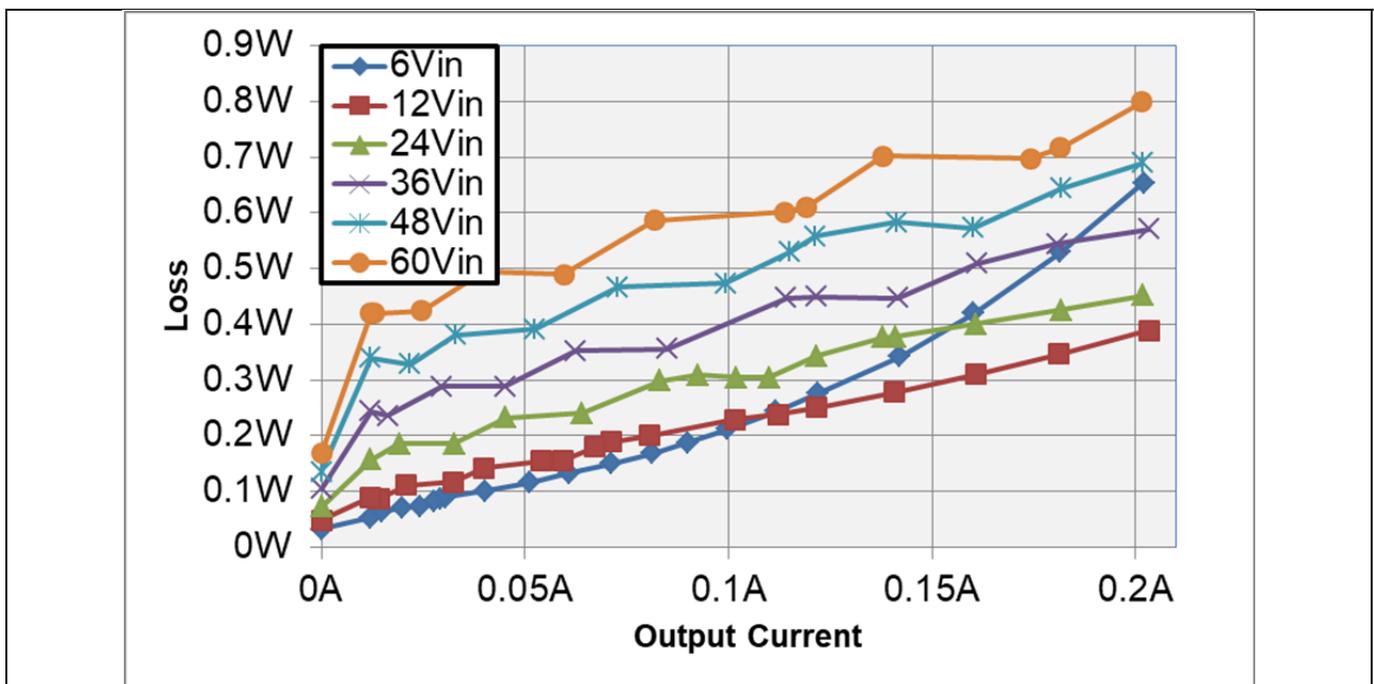


Figure 2 Loss vs Output Current

2.2 Line Regulation

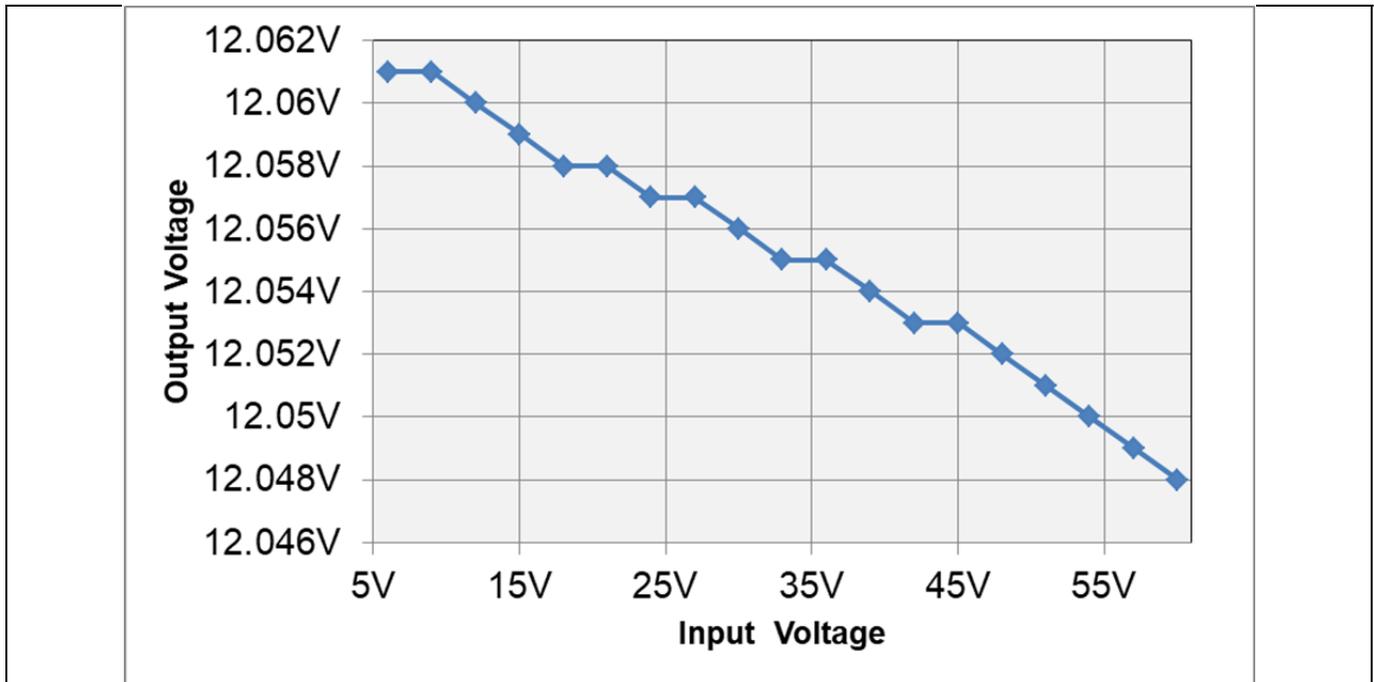


Figure 3 Output Voltage vs Input Voltage

With the same measurement setup efficiency and loss were calculated.

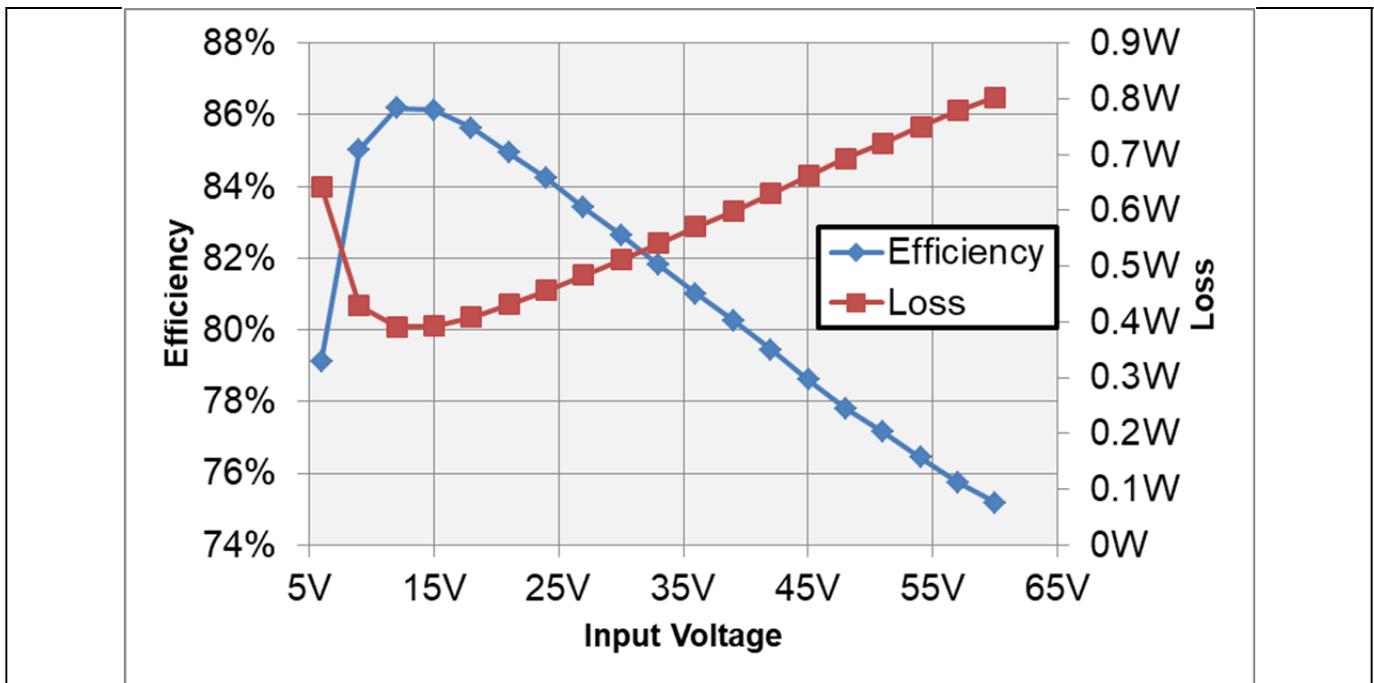


Figure 4 Efficiency and Loss vs Input Voltage

2.3 Load Regulation

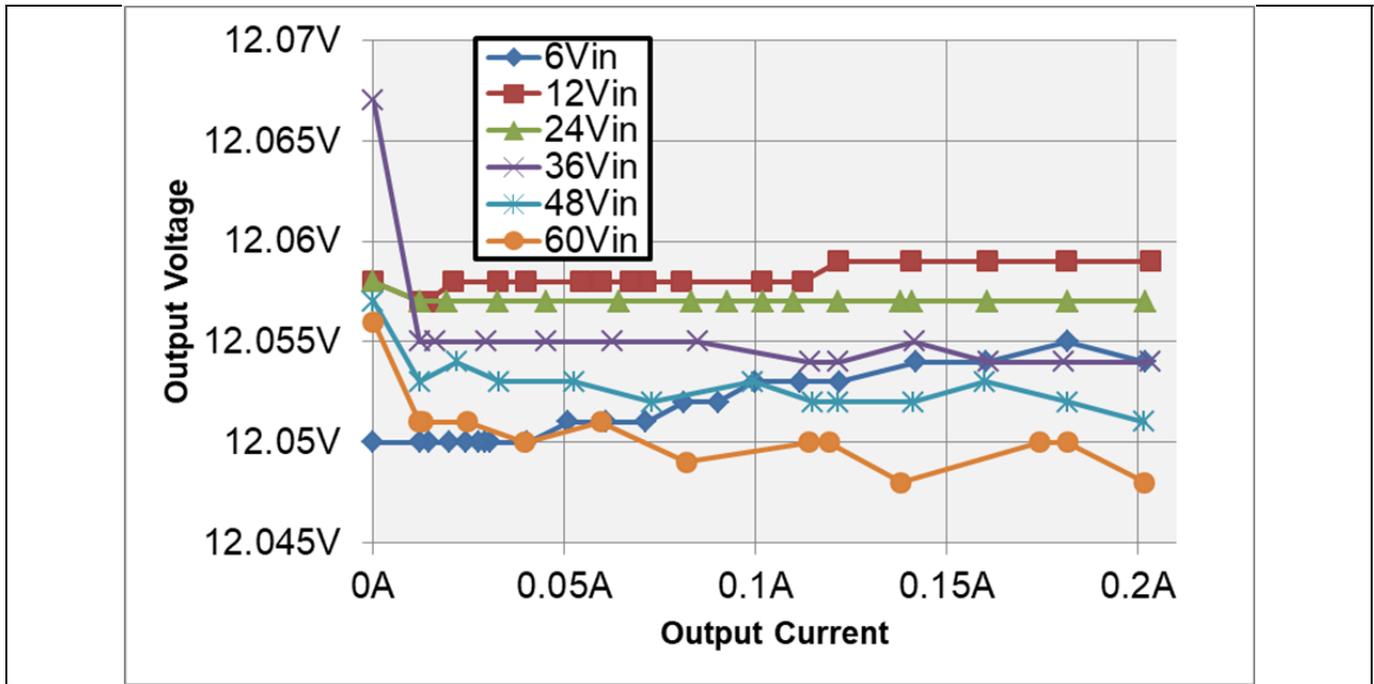


Figure 5 Output Voltage vs Output Current

2.4 Thermal Images

2.4.1 6 V Input Voltage

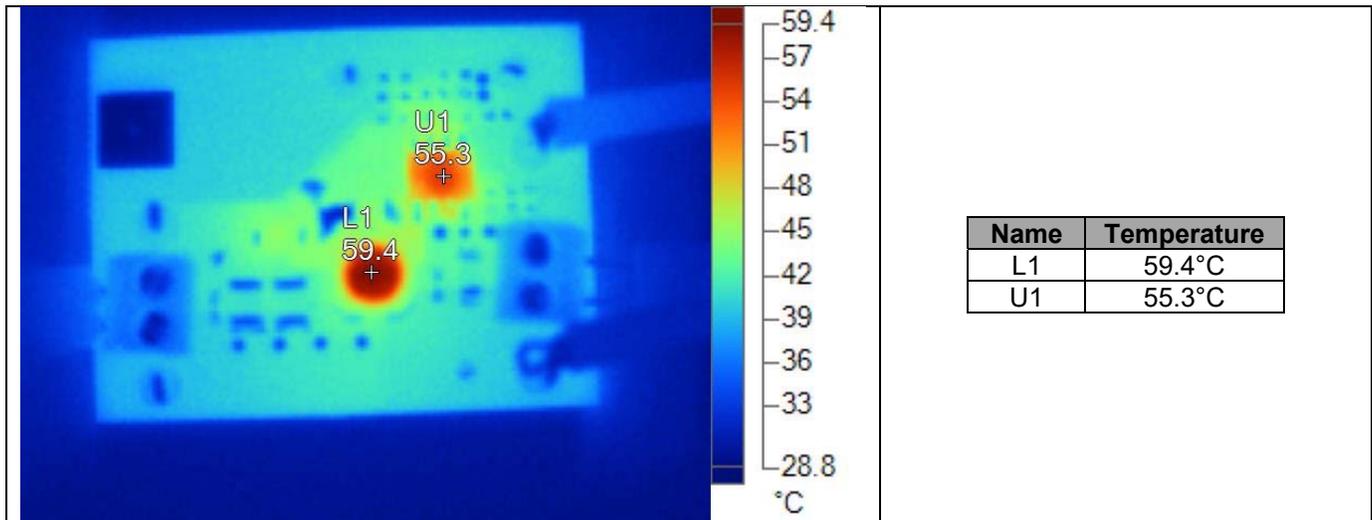


Figure 6 Thermal Image at 6 V Input Voltage

2.4.2 36 V Input Voltage

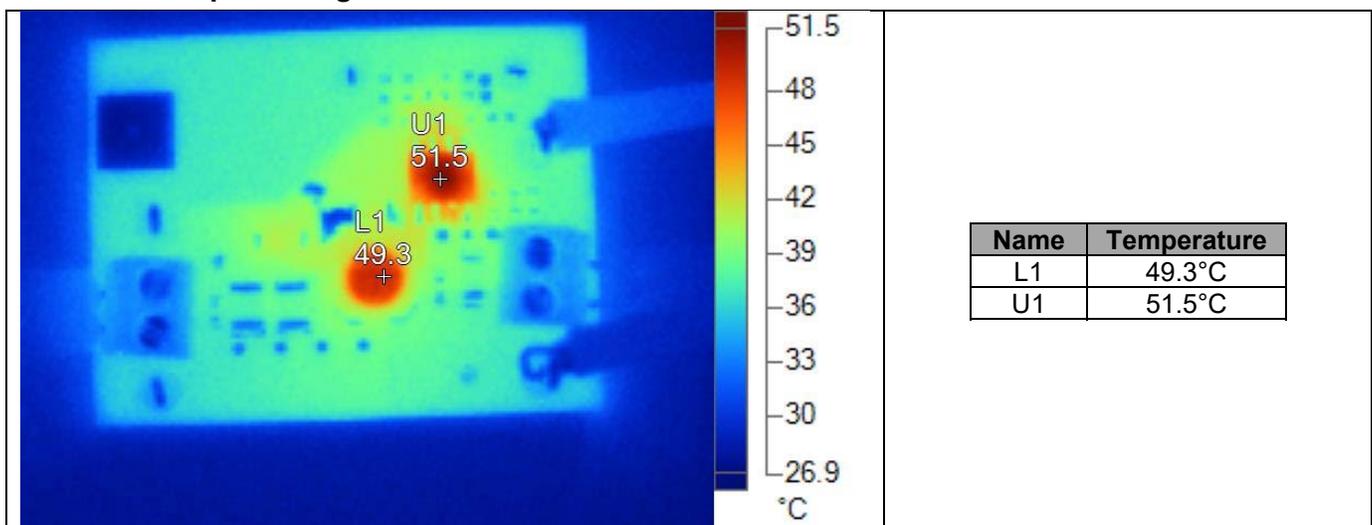


Figure 7 Thermal Image at 36 V Input Voltage

2.4.3 60 V Input Voltage

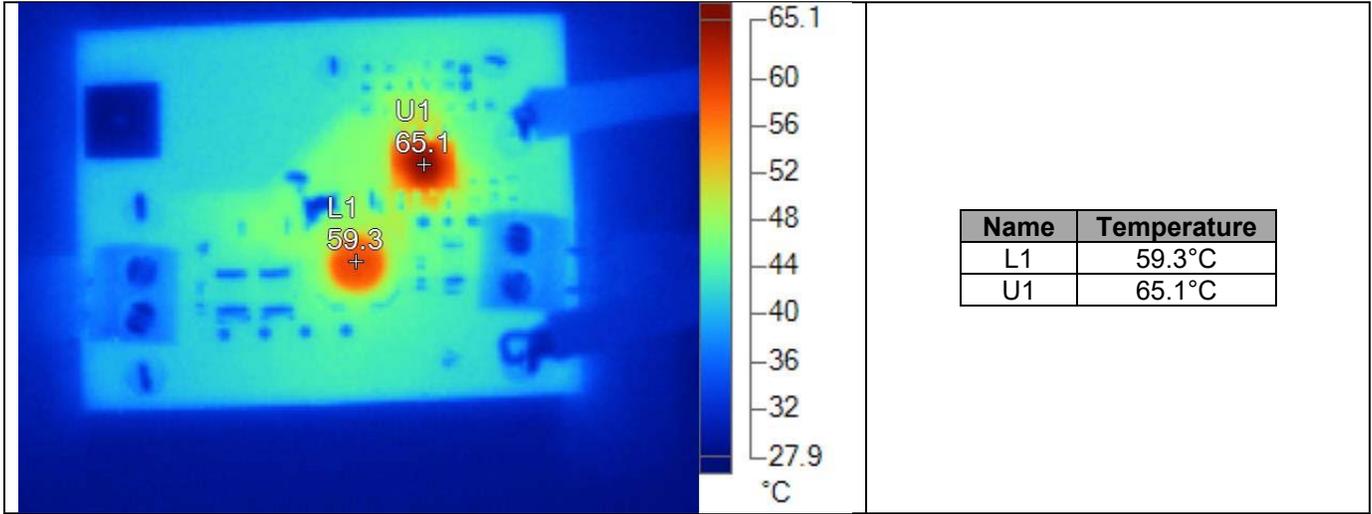


Figure 8 Thermal Image at 60 V Input Voltage

2.5 Dimensions

The size of the boards is 39.4mm x 30.5mm

3 Waveforms

3.1 Switching

3.1.1 SW to GND

3.1.1.1 6 V Input Voltage

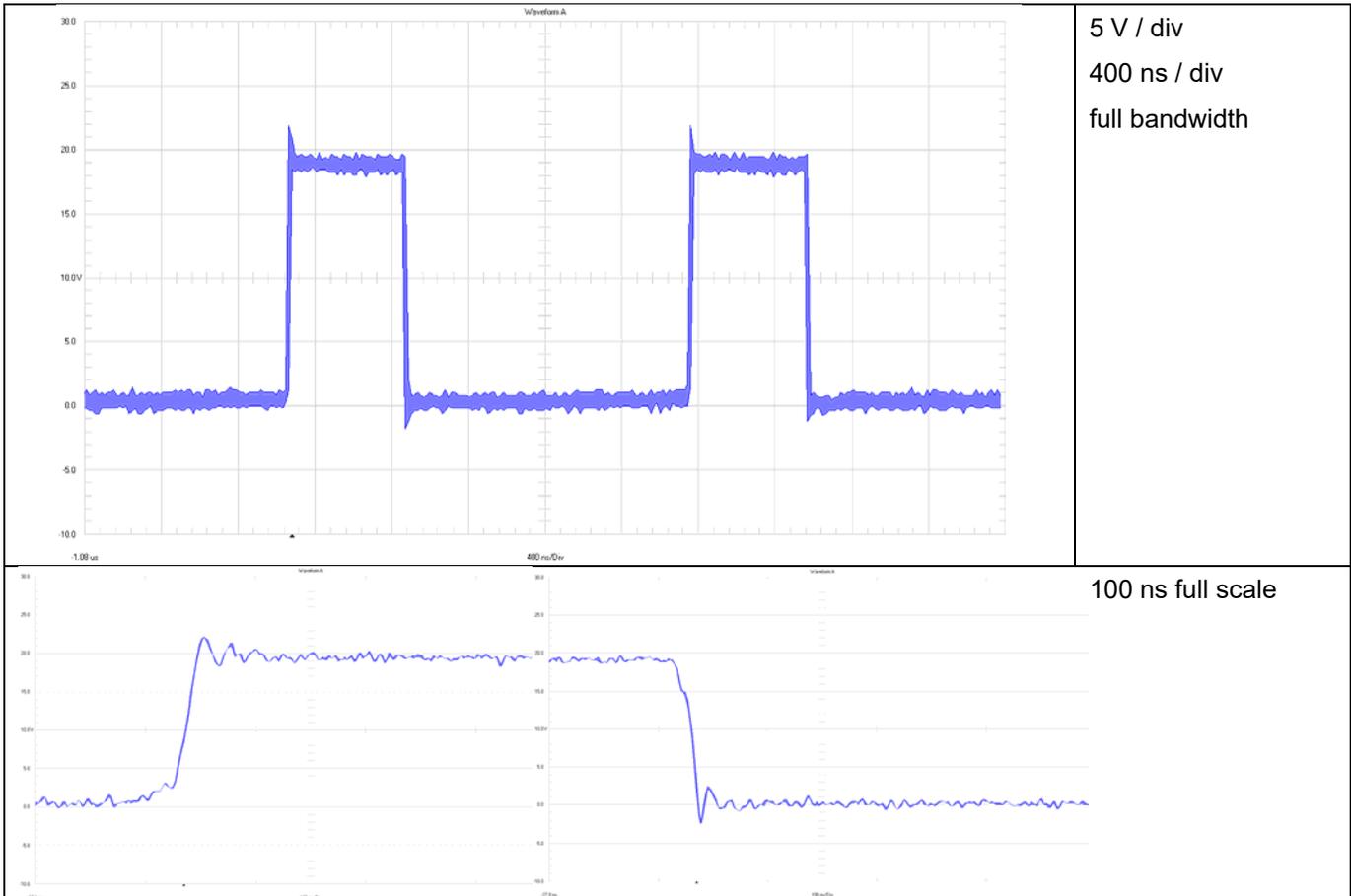


Figure 9 SW-to GND @ 6 V Input Voltage

3.1.1.2 36 V Input Voltage

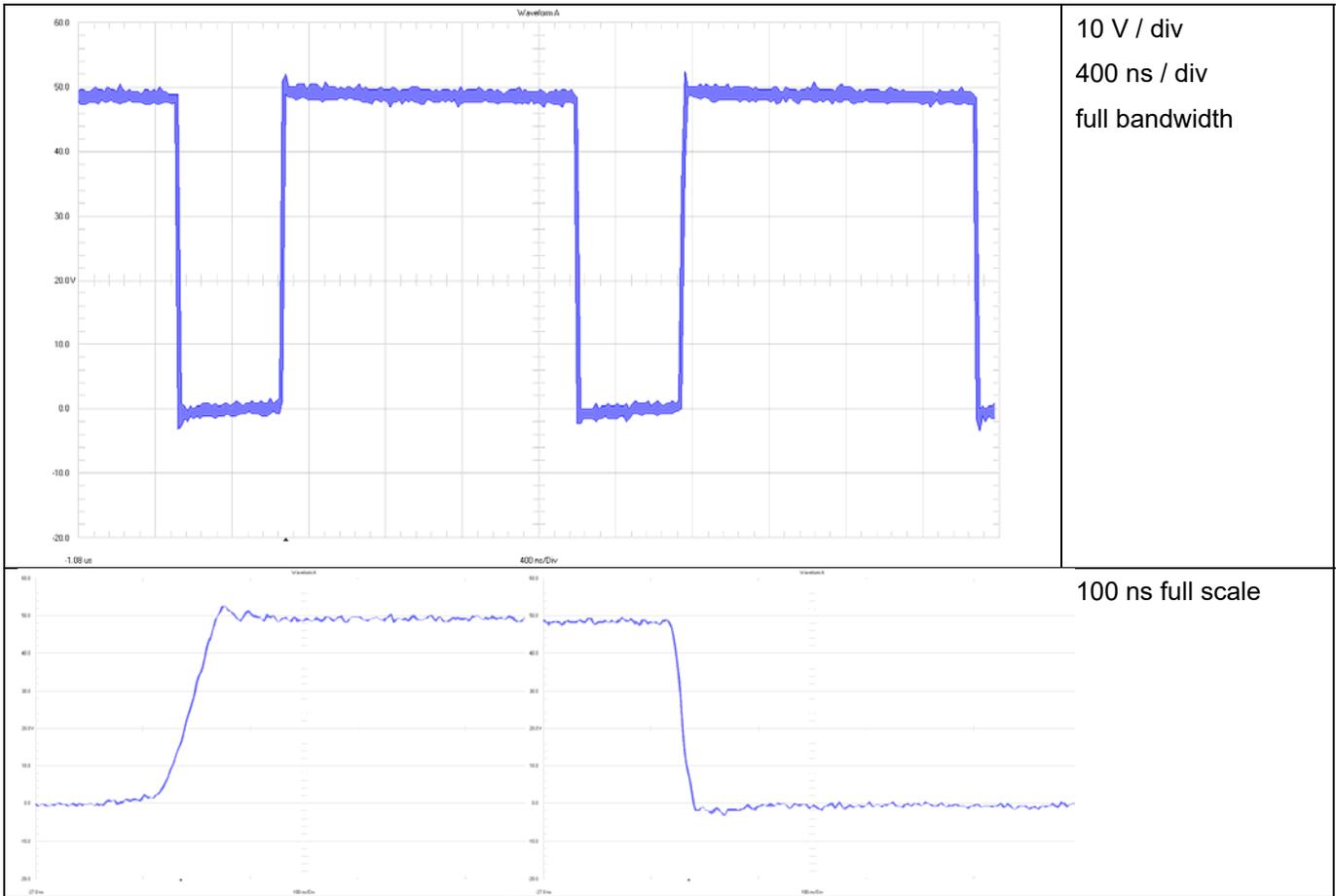


Figure 10 SW-to GND @ 36 V Input Voltage

3.1.1.3 60 V Input Voltage

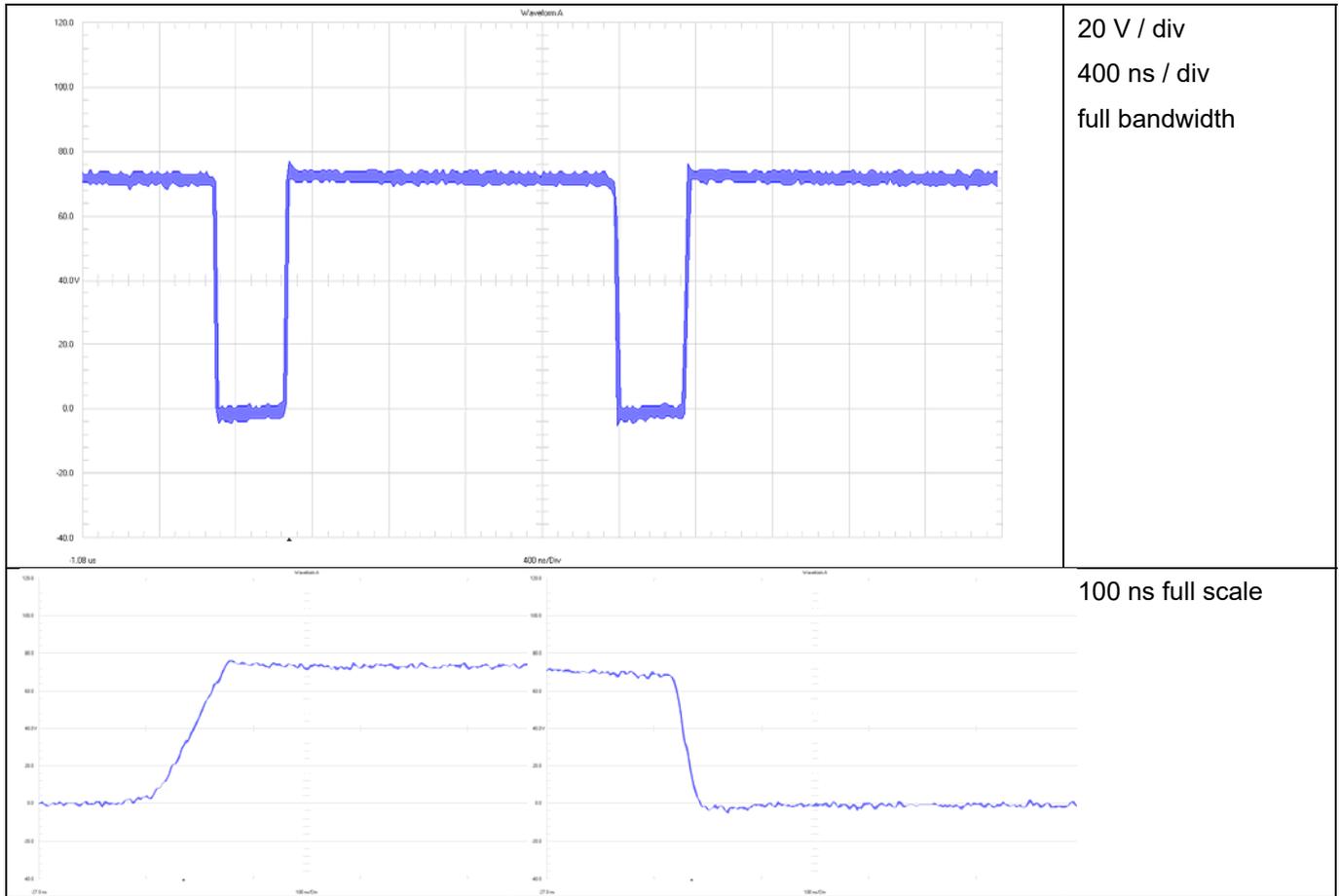


Figure 11 SW-to GND @ 60 V Input Voltage

3.1.2 Diode D1 (referenced to VOUT)

3.1.2.1 6 V Input Voltage

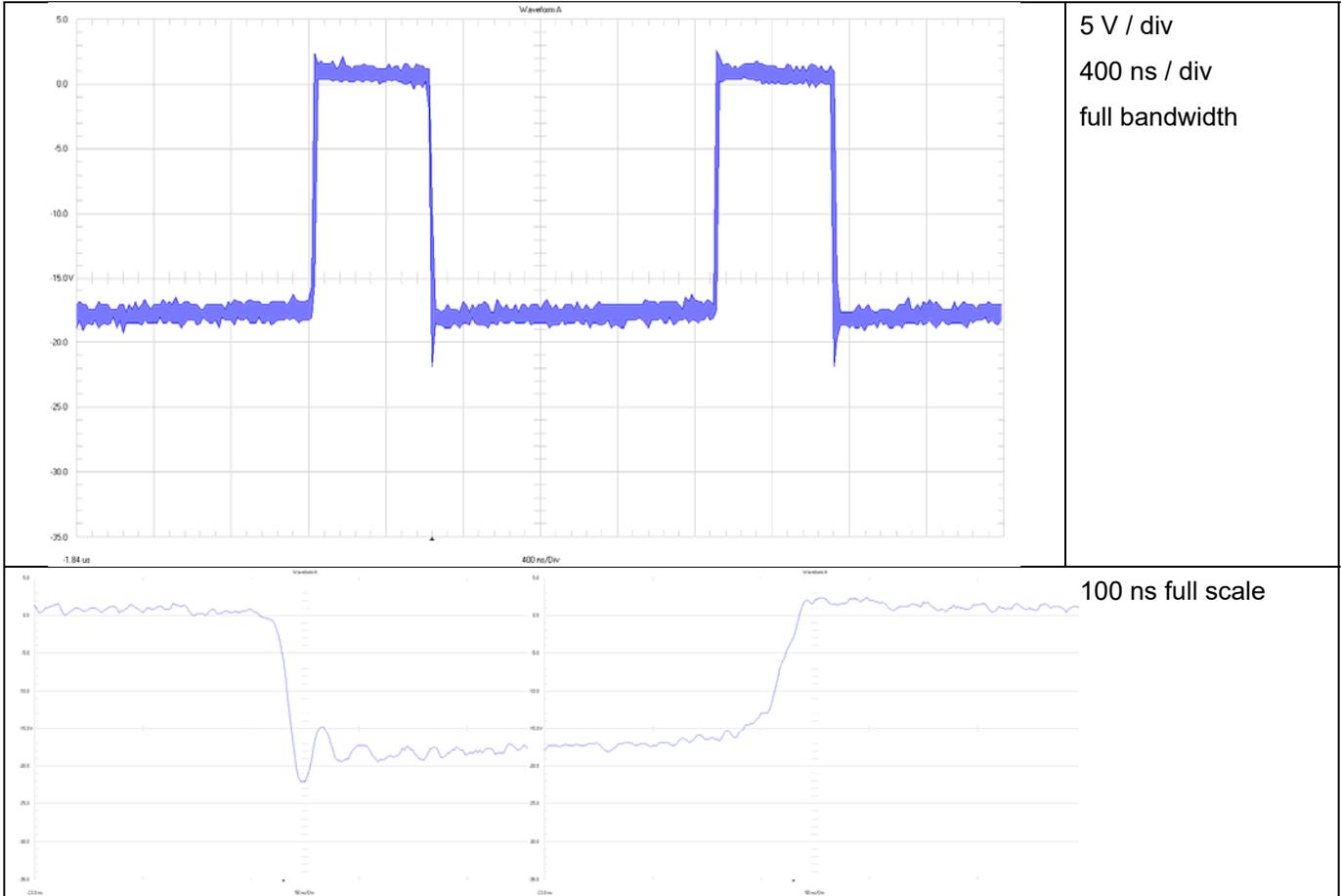


Figure 12 D1 @ 6 V Input Voltage

3.1.2.2 36 V Input Voltage

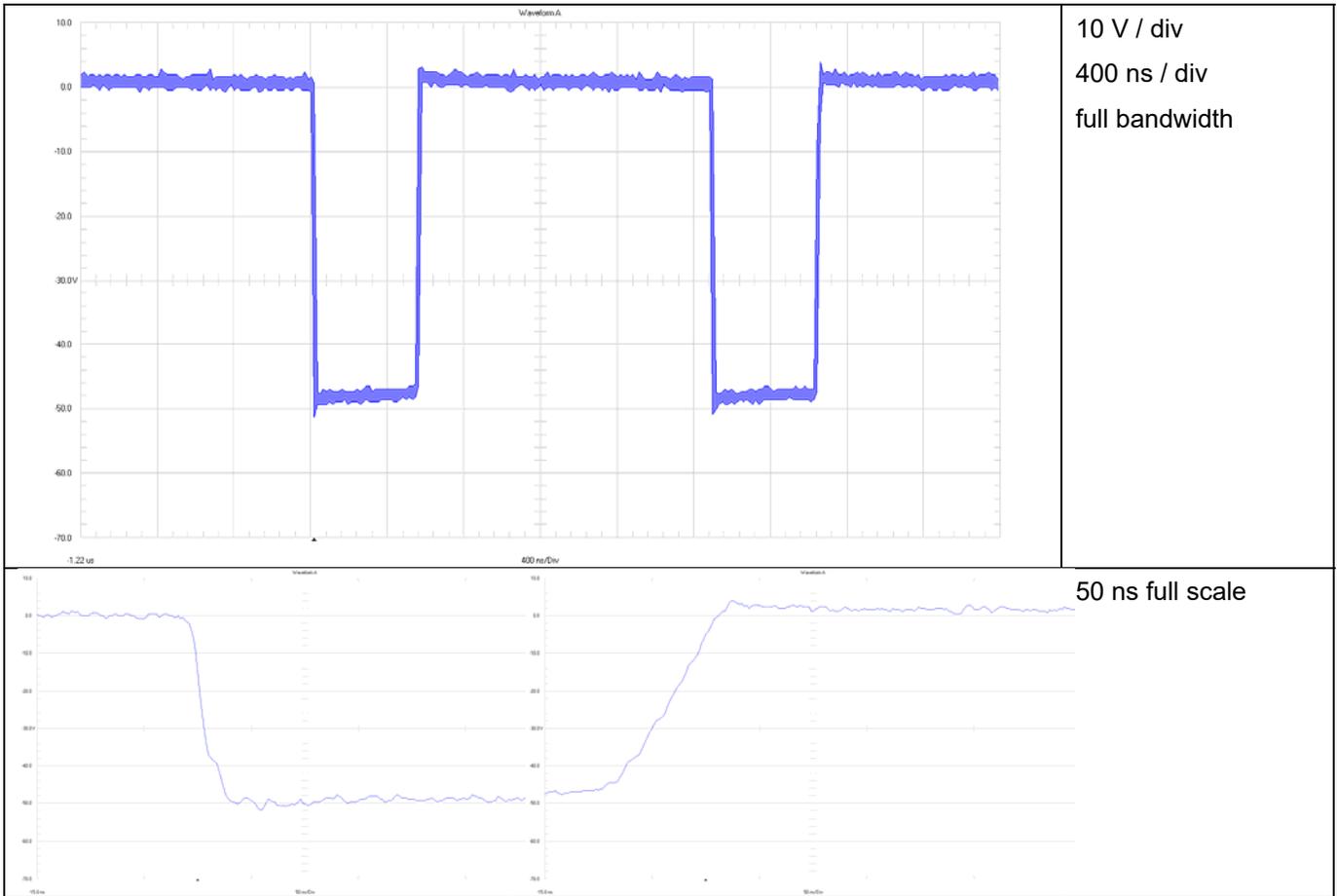


Figure 13 D1 @ 36 V Input Voltage

3.1.2.3 60 V Input Voltage

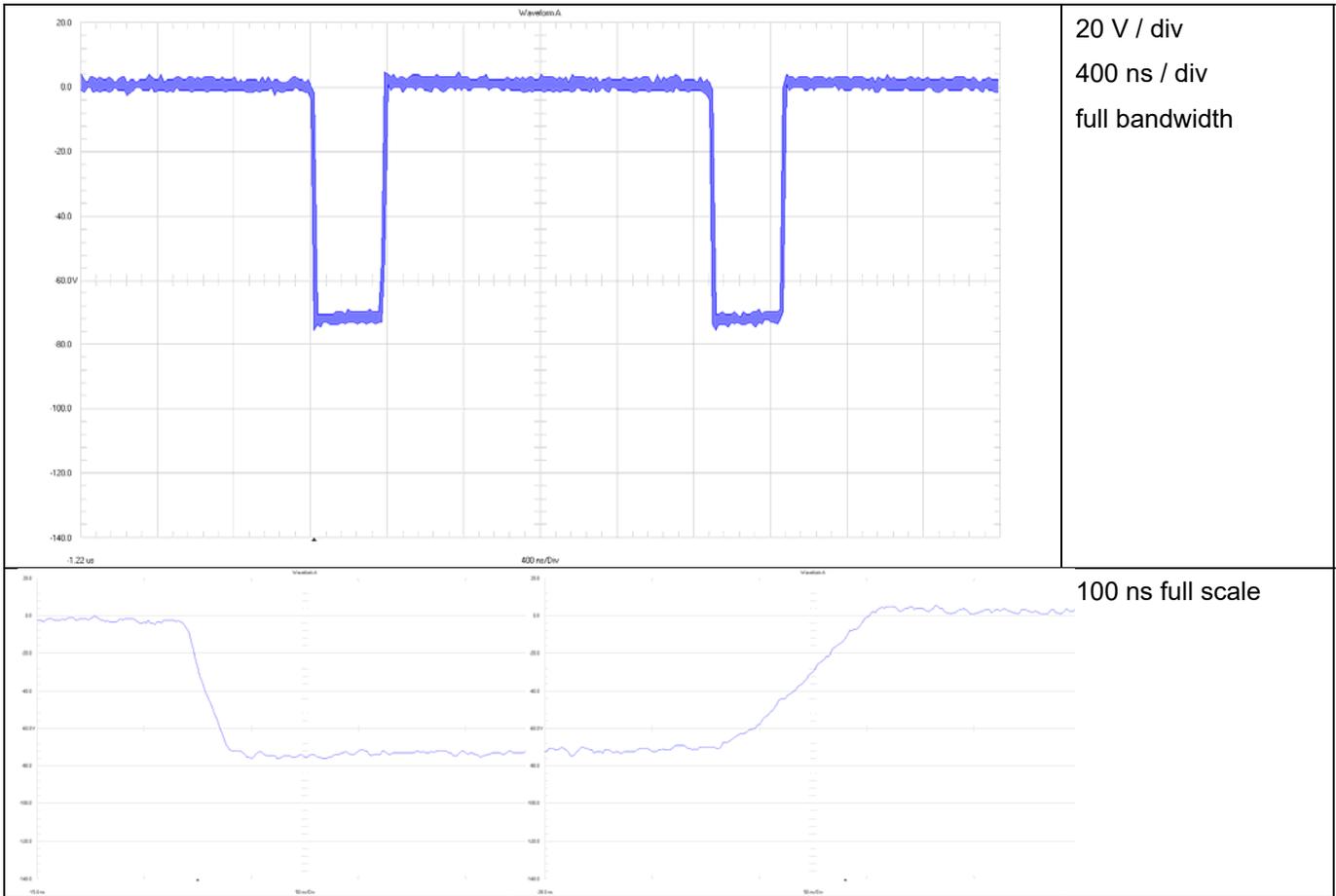


Figure 14 D1 @ 60 V Input Voltage

No ringing, no overshoot reduces RF content to ensure low radiated emissions.

3.2 Output Voltage Ripple

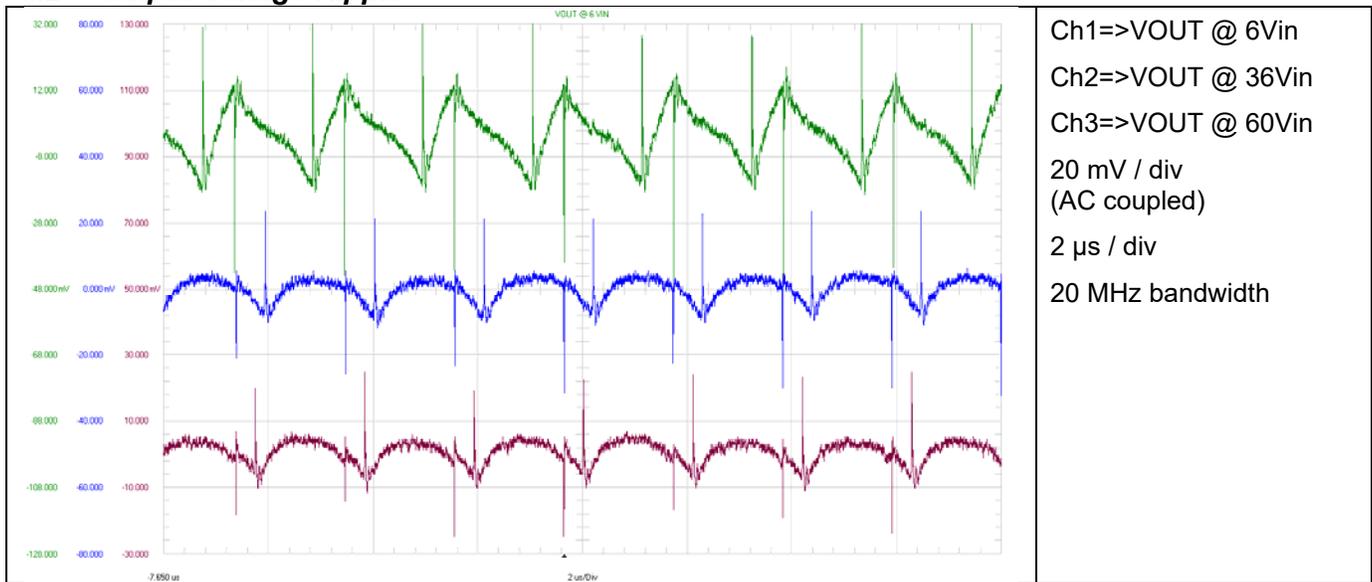


Figure 15 VOUT @ 6 V Input Voltage

All waveforms were captured separately – output voltage ripple is below 0.5% of DC output voltage.

3.3 Input Voltage Ripple

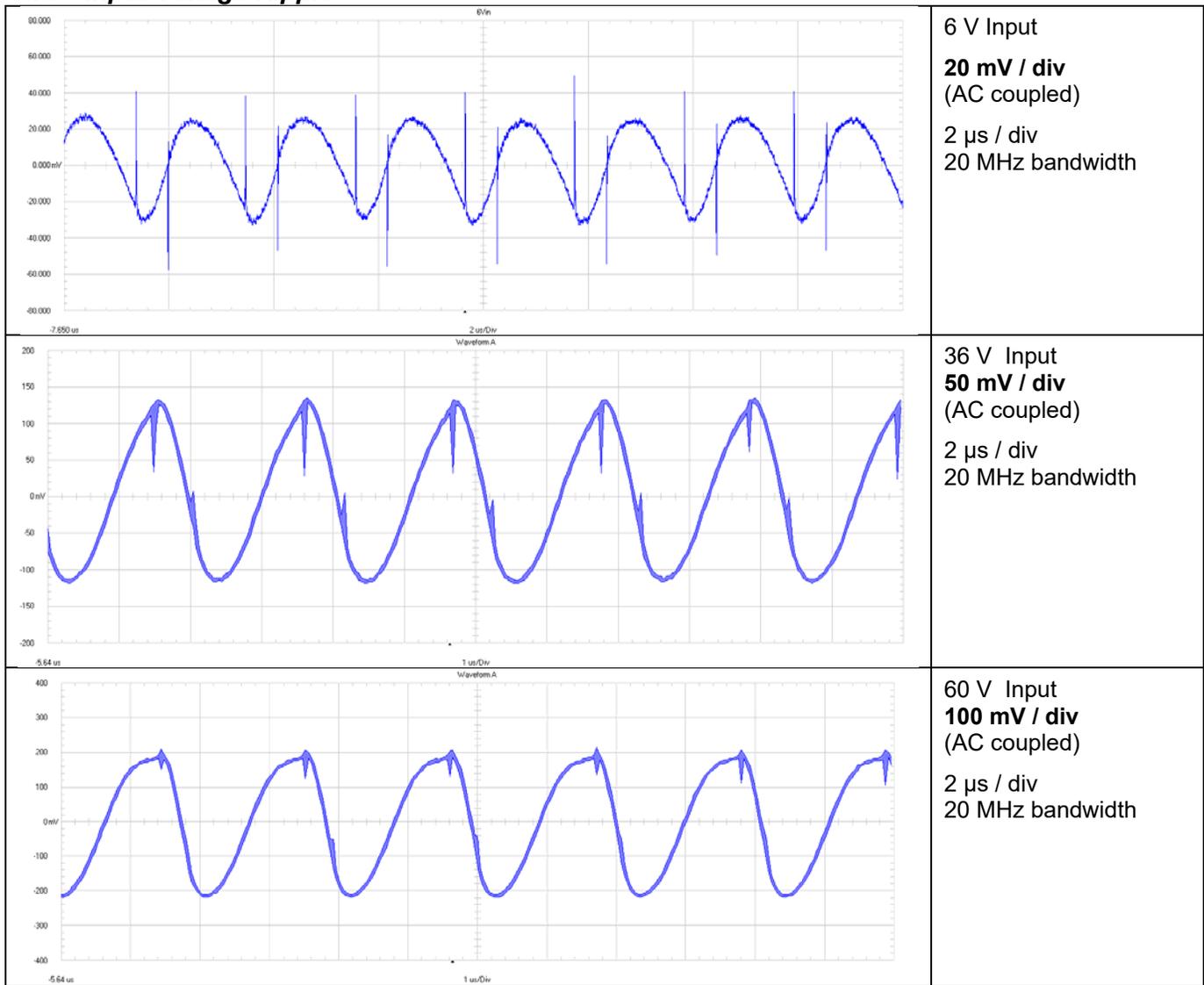


Figure 16 Input Voltage Ripple for 6 V, 36 V and 60 V Input Voltage

Sinusoidal input ripple by SEPIC topology, less harmonic content.

3.4 Bode Plot

	6 Vin	36 Vin	60 Vin
Bandwidth (kHz)	3.97	10.2	8.6
Phasemargin	75°	78°	80°
slope (20dB/decade)	-0.99	-1.0	-1.0
gain margin (dB)	-15.1	-21.2	-23.55
slope (20dB/decade)	-0.5	-1.49	-1.4
freq (kHz)	33.9	81.9	85.2

Table 1 Summary of the Bode Plots

3.4.1 6 V Input Voltage

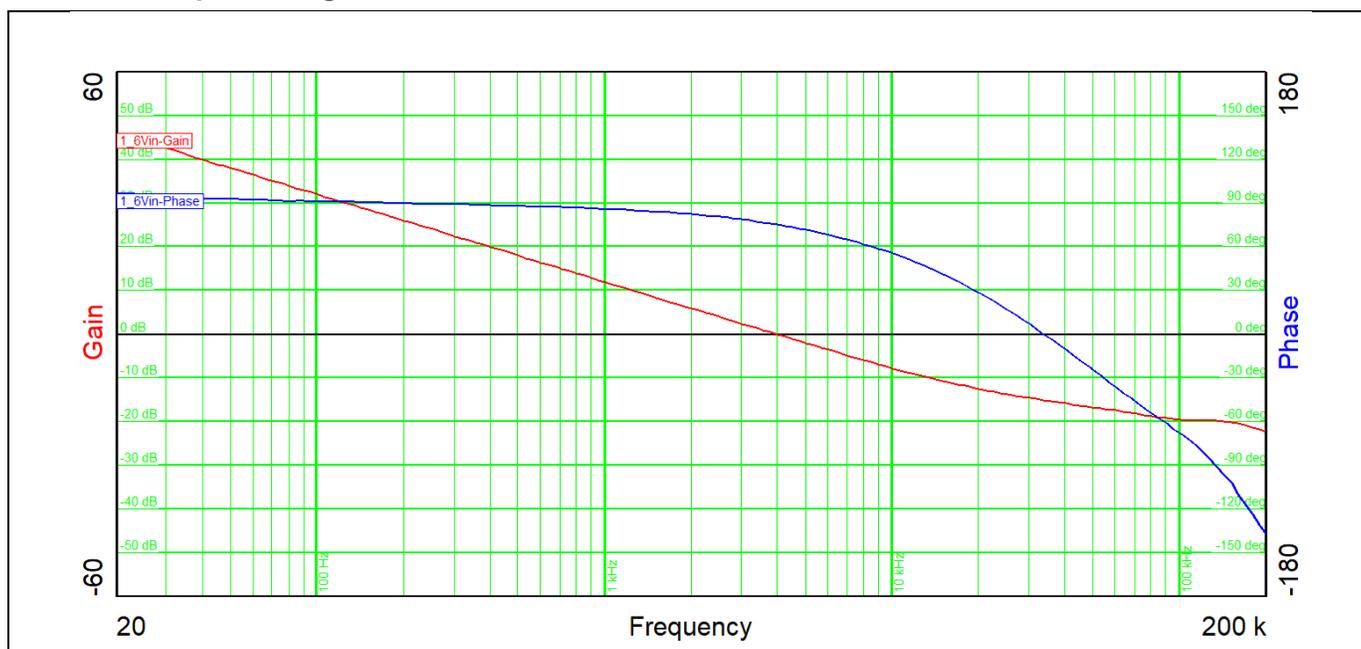


Figure 17 Frequency Response for 6 V Input Voltage

RHPZ at 45kHz limits loop bandwidth to 4kHz by keeping gain margin of -15dB.

3.4.2 36 V Input Voltage

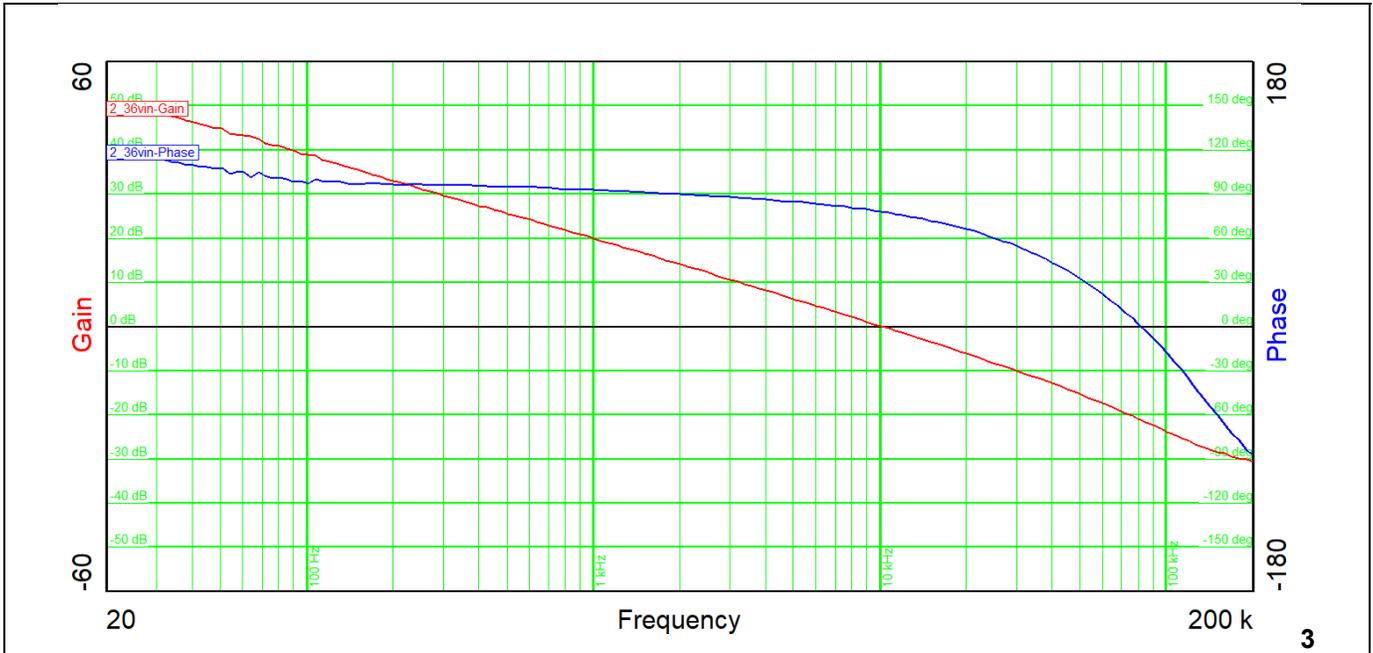


Figure 18 Frequency Response for 36 V Input Voltage

3.4.3 60 V Input Voltage

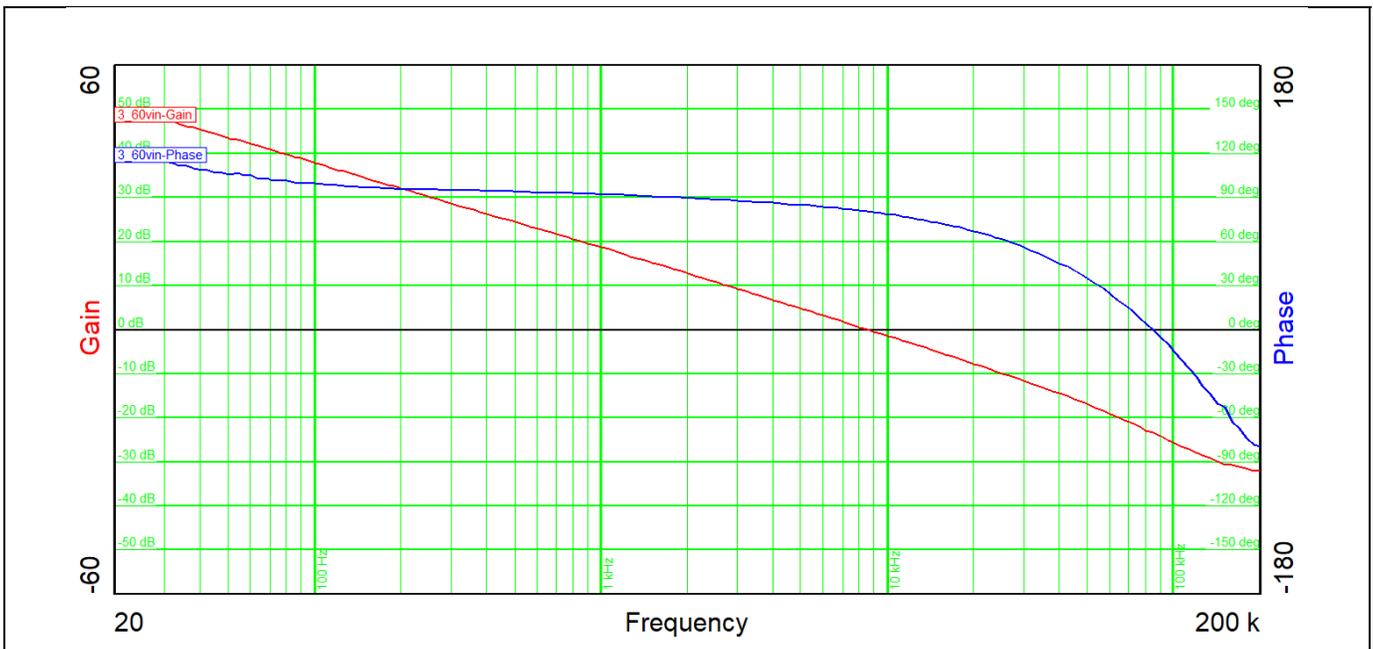


Figure 19 Frequency Response for 60 V Input Voltage

3.5 Load Transients

The electronic load switched between 0.1 A and 0.2 A with a frequency of 100 Hz.

3.5.1 6 V Input Voltage

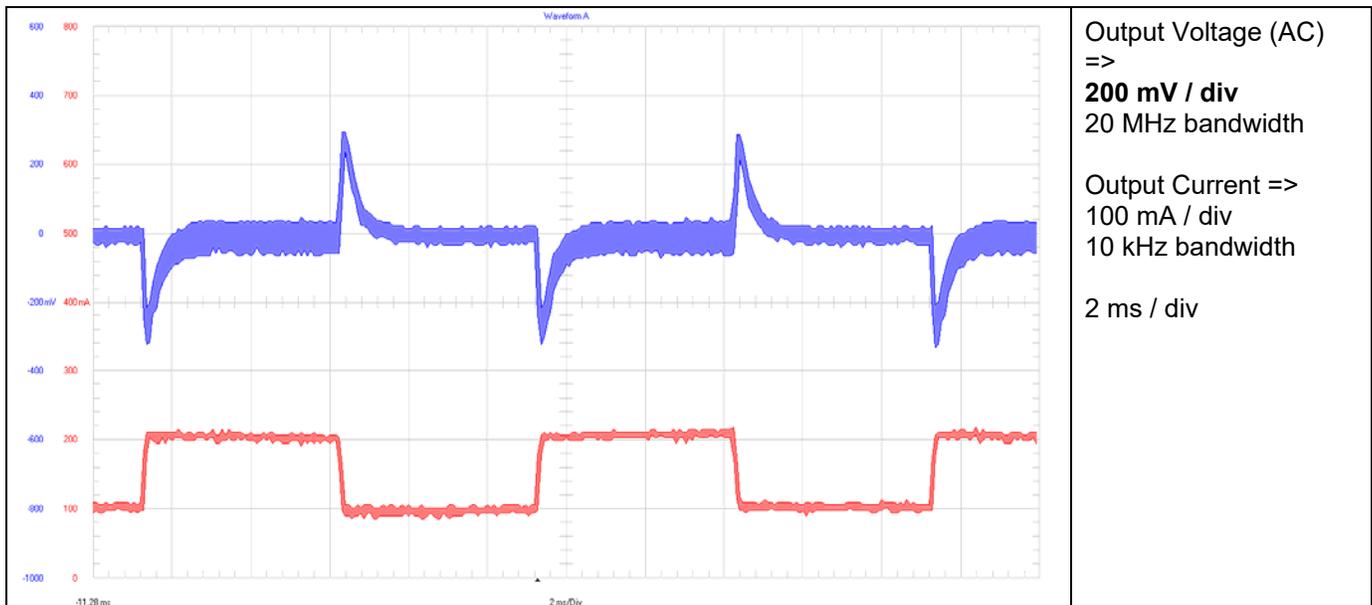


Figure 20 Load Transient for 6 V Input Voltage

3.5.2 36 V Input Voltage

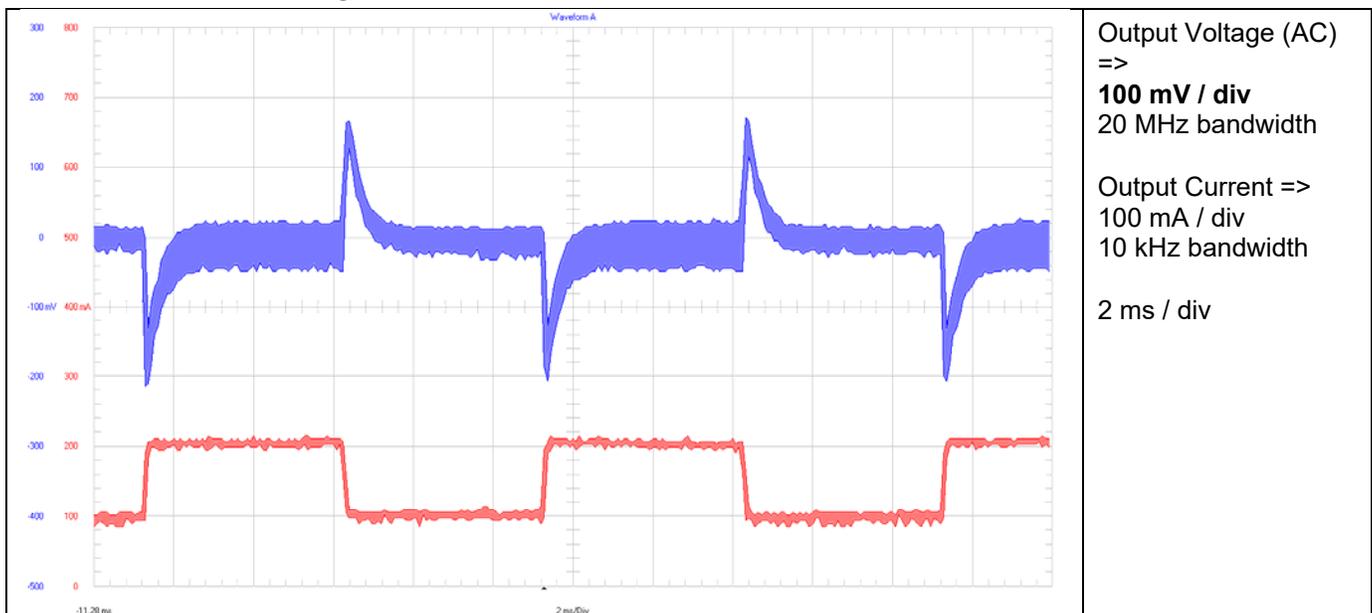


Figure 21 Load Transient for 36 V Input Voltage

3.5.3 60 V Input Voltage

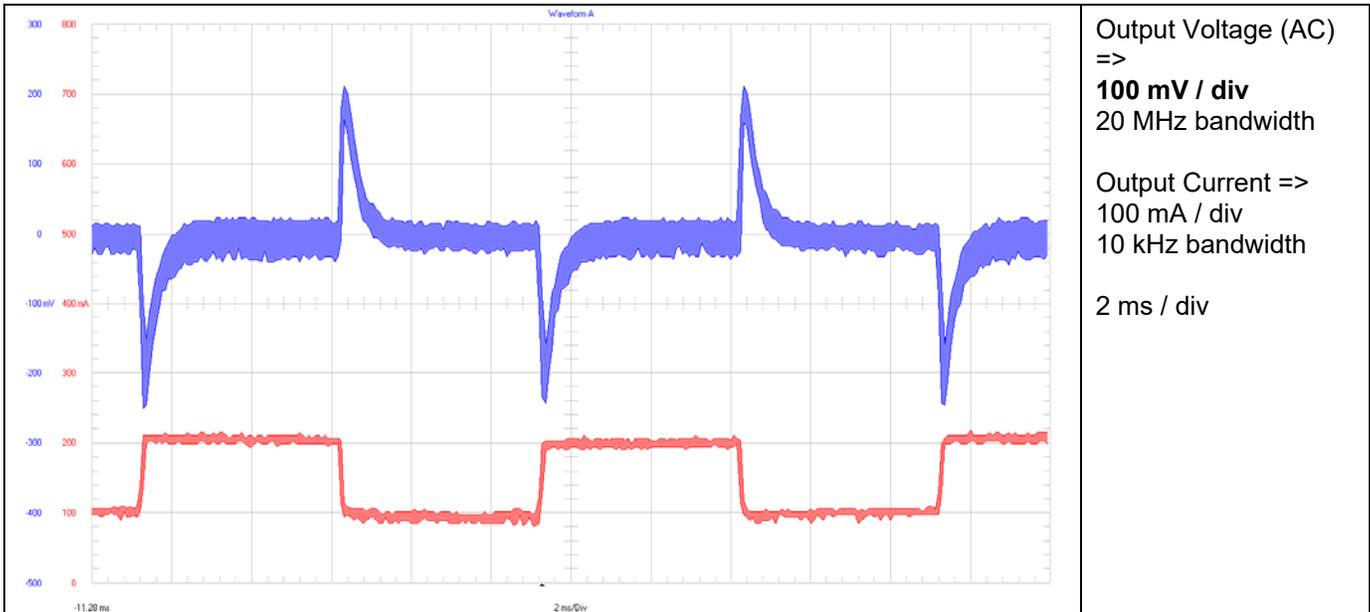


Figure 22 Load Transient for 60 V Input Voltage

Despite small output capacitance transient response is 2.5% of Vout worst case (input voltage 6V)

3.6 Start-up Sequence

3.6.1 6 V Input Voltage

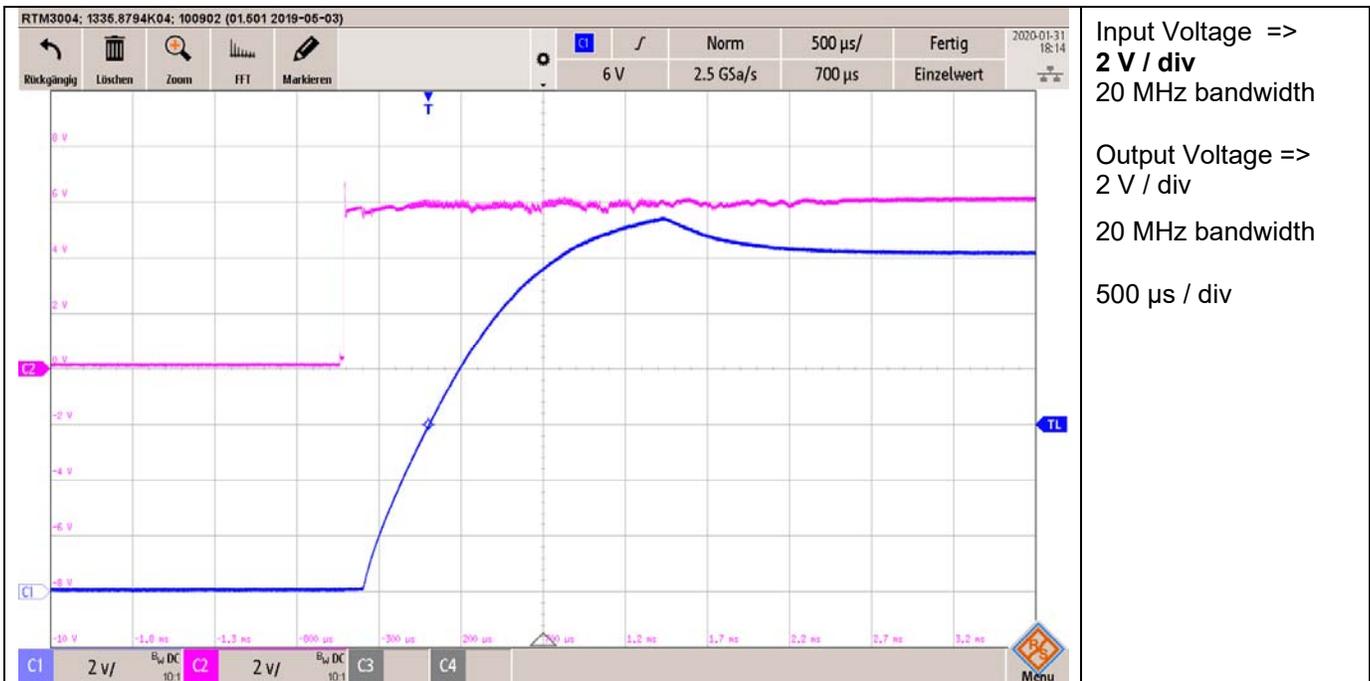


Figure 23 Start-up @ 6 V Input Voltage

3.6.2 36 V Input Voltage

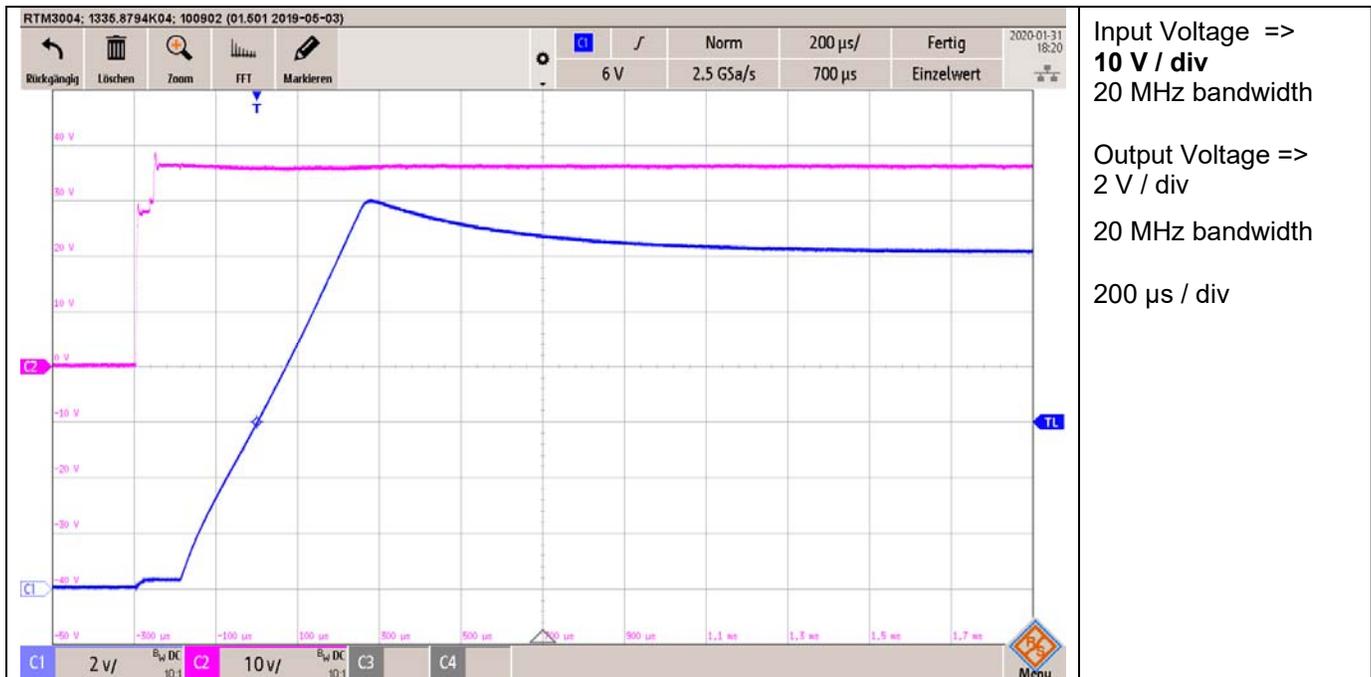


Figure 24 Start-up @ 36 V Input Voltage

3.6.3 60 V Input Voltage

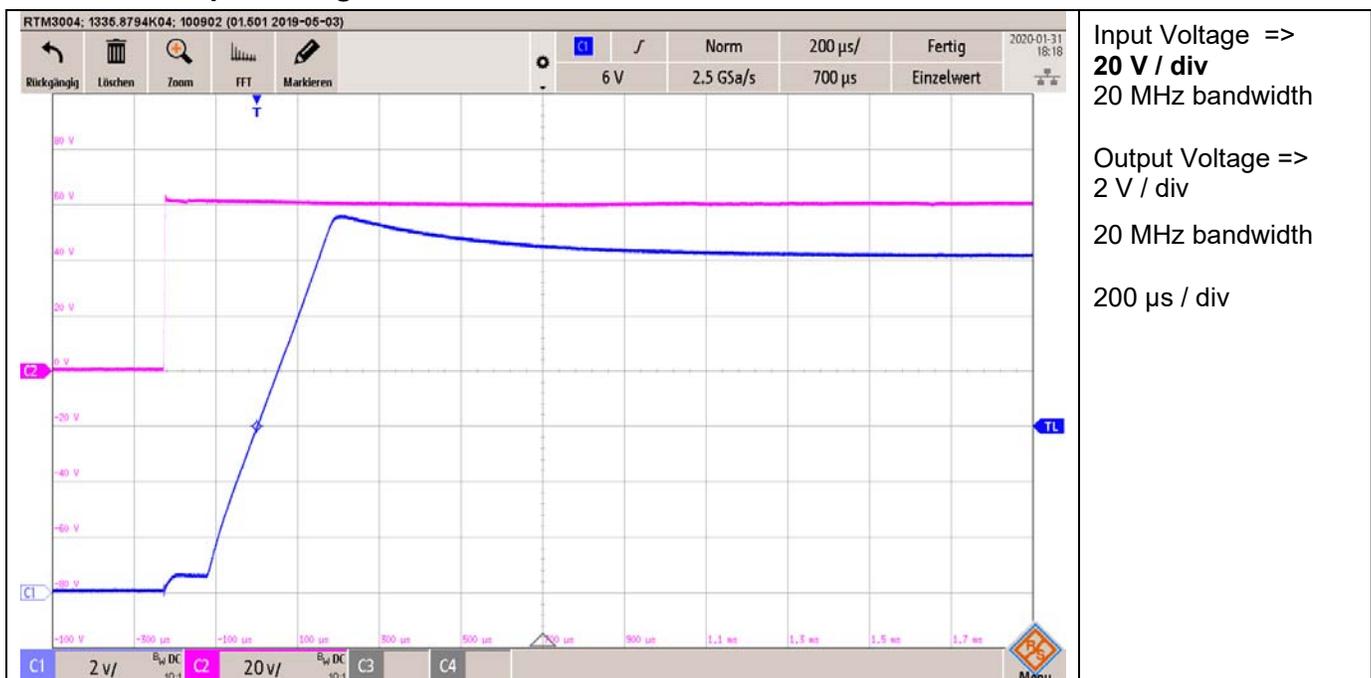


Figure 25 Start-up @ 60 V Input Voltage

3.7 Shut-down Sequence

3.7.1 6 V Input Voltage

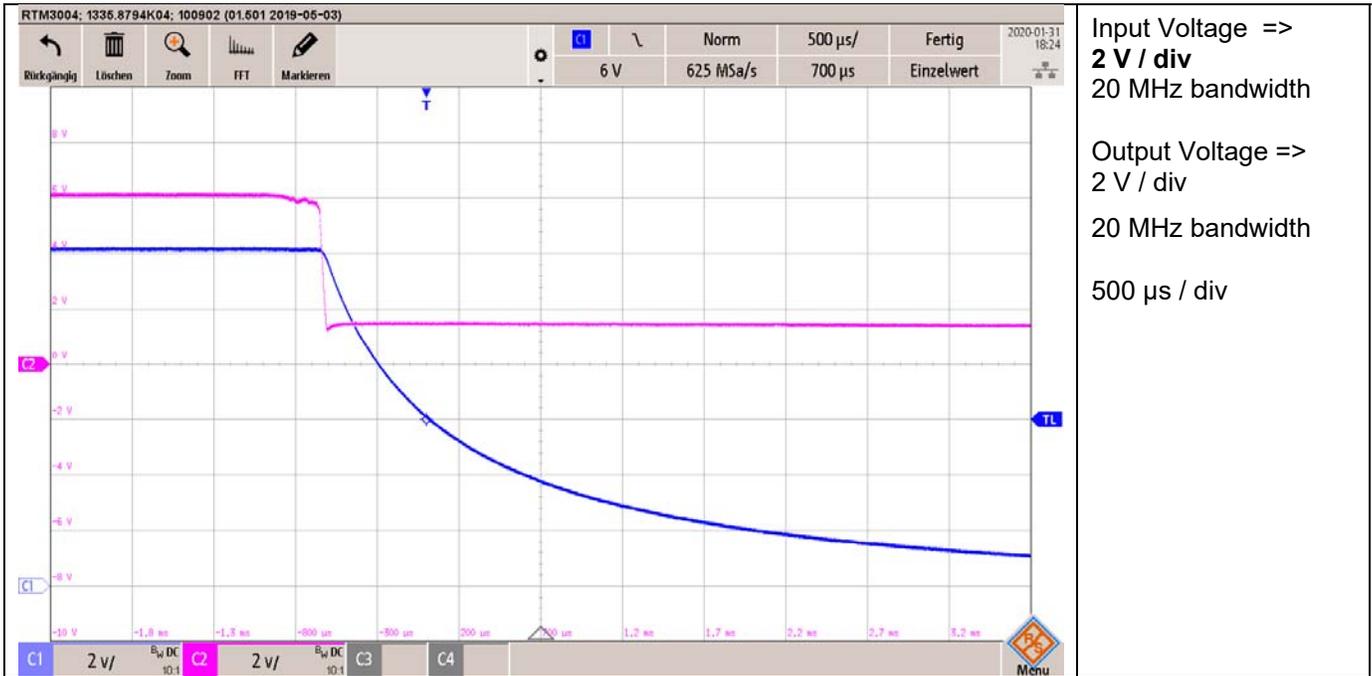


Figure 26 Shut-down @ 6 V Input Voltage

3.7.2 36 V Input Voltage


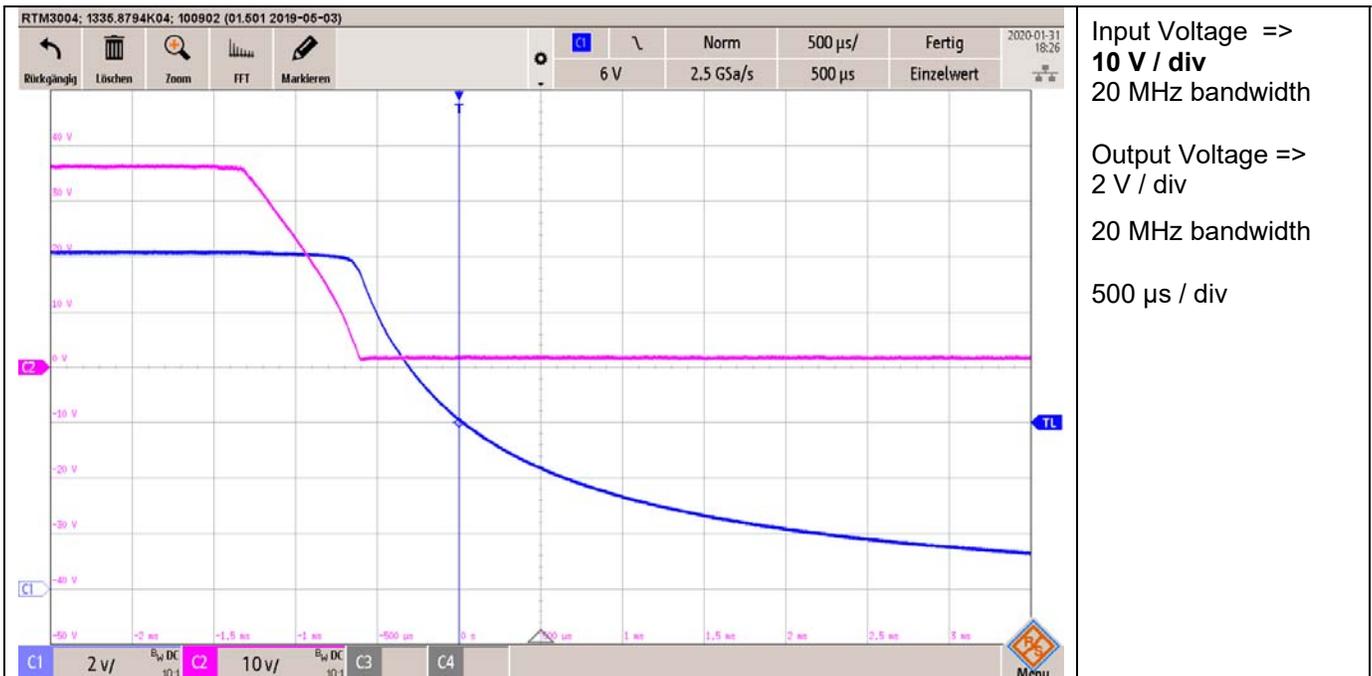


Figure 27 Shut-down @ 36 V Input Voltage

3.7.3 60 V Input Voltage

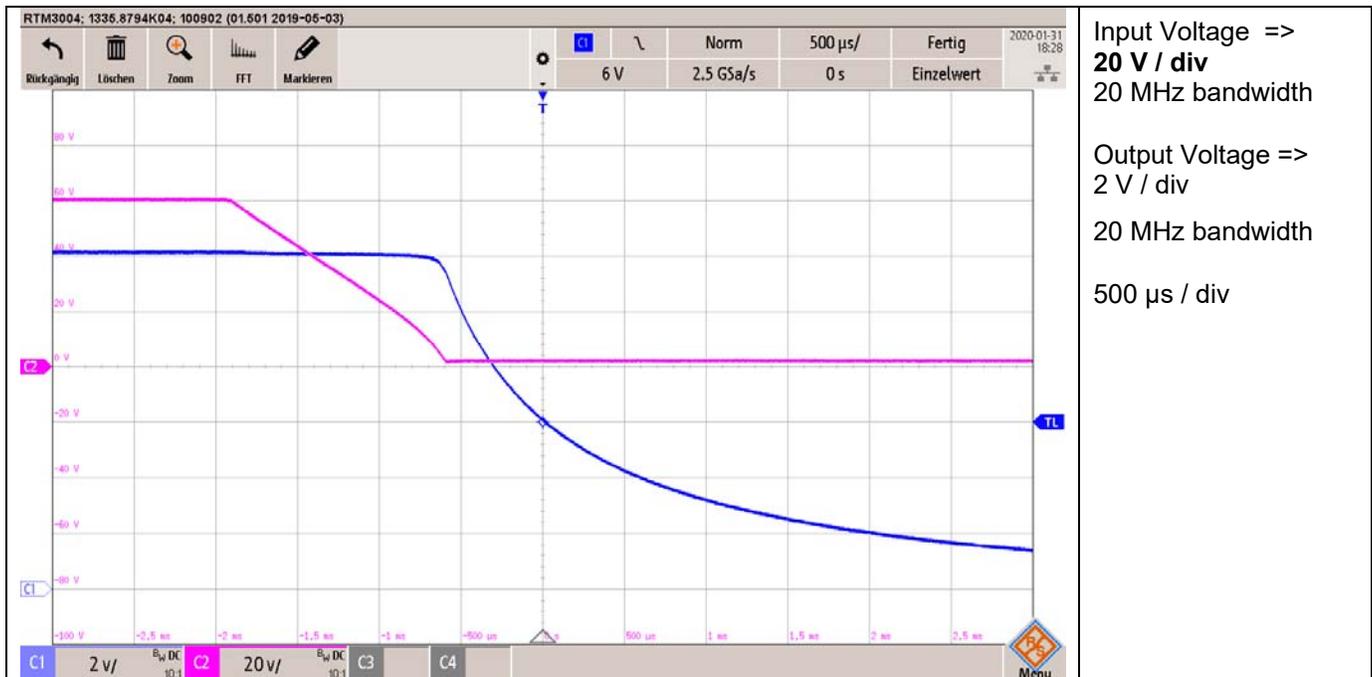

Input Voltage =>
20 V / div
 20 MHz bandwidth

Output Voltage =>
 2 V / div
 20 MHz bandwidth

500 µs / div

Figure 28 Shut-down @ 60 V Input Voltage

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated