

# PMP10051RevB Test Results

---

1	Startup .....	2
2	Shutdown .....	2
3	Efficiency .....	3
4	Output Ripple Voltage .....	4
5	Input Ripple Voltage .....	4
6	Control Loop Frequency Response.....	5
7	Output Voltages at different load conditions.....	7
8	Miscellaneous Waveforms .....	8

Topology: SEPIC  
Device: TPS61175

Unless otherwise mentioned all measurements were done with 6.3V at the input and full load at each output applied.

**Static measurements:**


Switching frequency Fsw 360kHz;

Load resistors:

- R1 = 68.20 Ohms
- R2 = 13.99 kOhm
- R3 = 68.17 Ohm
- R4 = 12.08 kOhm

 
## 1 Startup

The startup waveform is shown in the Figure 1.


 
## 2 Shutdown

The shutdown waveform is shown in the Figure 2. The input voltage was set at 3V, with 1.2A load on the output. The power supply was disconnected.



# PMP10051RevB Test Results

---

## 3 Efficiency

The efficiencies are shown in the Table 1 below.


VIN	IIN	VOUT1	VOUT2	VOUT3	VOUT4	Eff
3.01	0.4996	6.6702	13.509	6.5771	12.75	0.87
6.302	0.2354	6.6758	13.511	6.6263	12.72	<b>0.89</b>
13.21	0.1181	6.6772	13.503	6.6485	12.75	0.85

Table 1

*results in converter power losses of 163mW at nominal input voltage 6.3V*

 
## 4 Output Ripple Voltage

The output ripple voltage is shown in Figure 3, <1%


 
## 5 Input Ripple Voltage

The input ripple voltage is shown in Figure 4.



## 6 Control Loop Frequency Response

Figure 5 shows the loop response. Full-load applied. The input voltage was set to 3V.

 


Figure 5

Figure 6 shows the loop response. Full-load applied. The input voltage was set to 6.3V.


 


Figure 6

Figure 7 shows the loop response. Full-load applied. The input voltage was set to 13.2V.

 

**Figure 7**

Table 1 summarizes the results from Figure 5 Figure 6 and Figure 7.

Vin	3V	6.3V	13.2V
<b>Bandwidth (kHz)</b>	4.158	7.96	9.93
<b>Phase margin</b>	60.1°	58.1°	63°
<b>slope (20dB/decade)</b>	-1.1	-1.23	-1.16
<b>gain margin (dB)</b>	-16.5	-17.5	-18.1
<b>slope (20dB/decade)</b>	-1.43	-1.75	-1.77
<b>freq (kHz)</b>	18.6	31.6	43.5

**Table 1**

# PMP10051RevB Test Results

## 7 Output Voltages at different load conditions

The table below shows the voltage measurements at different load conditions. The fields which are filled with blue means full load is applied.

This is a **WORST CASE** analysis full load (jumper set = 1) / zero load (jumper off = 0):

Jmp11	Jmp21	Jmp31	Jmp41	U11	U21	-U31	-U41
0	0	0	0	6.673	13.486	6.739	12.81
0	0	0	1	6.6867	13.615	6.7985	6.023
0	0	1	0	6.6867	13.575	2.3	12.64
0	0	1	1	6.67	14.424	2.4	7.032
0	1	0	0	6.68	6.78	6.809	12.89
0	1	0	1	6.71	6.1	6.837	5.444
0	1	1	0	6.674	9.7	4.63	12.52
0	1	1	1	6.674	9.24	4.28	8.334
1	0	0	0	6.676	16.017	8.861	16.77
1	0	0	1	6.675	15.233	8.232	12.85
1	0	1	0	6.676	16.76	6.627	16.79
1	0	1	1	6.675	16.225	6.626	12.73
1	1	0	0	6.674	13.513	8.855	16.04
1	1	0	1	6.674	13.509	8.855	12.84
1	1	1	0	6.674	13.508	6.625	16.16
1	1	1	1	6.674	13.503	6.625	12.72

Due to the peak detection of the flyback rectifier this multi output sepic will NOT work properly if an output is NOT loaded. The deviation itself depends on coupling of the transformer and load scenario. **See the load scenario approx. 33mA / 67mA / 100mA at V1 and -V3;** V2 and V4 loaded w/ 1mA; to avoid zero load condition each output could be preloaded w/ a small bias resistor:

Load 11	Load 31	V11 (+6V7)	V21 (+14V)	V31 (-6V7)	V41 (-12V)	Vin (V)	lin (mA)	Effcy (%)
1/3	1/3	6.675	13.414	-6.648	-12.565	6.296	84.3	86.6%
1/3	2/3	6.677	13.417	-6.608	-12.567	6.305	123.9	86.0%
1/3	3/3	6.676	13.415	-6.573	-12.556	6.310	159.1	87.4%
2/3	1/3	6.676	13.479	-6.687	-12.660	6.313	125.0	86.2%
2/3	2/3	6.676	13.484	-6.644	-12.650	6.311	161.7	87.6%
2/3	3/3	6.676	13.478	-6.606	-12.618	6.304	197.5	88.5%
3/3	1/3	6.676	13.525	-6.709	-12.717	6.310	162.4	87.8%
3/3	2/3	6.676	13.502	-6.659	-12.680	6.300	198.6	89.1%
3/3	3/3	6.676	13.513	-6.625	-12.651	6.298	235.0	89.4%

The load variation 33mA / 67mA / 100mA resulted in:

V21, +14V = 13.414V ... 13.525V, **du = 111mV**  
V31, -6.7V = -6.573V .. -6.709V, **du = 136mV**, referred to V11 +6.676V: **-103mV / +33mV**  
V41, -12V = -12.556V .. -12.717V, **du = 161mV**

An improved transformer w/ multifilar windings will improve cross regulation further. V31 range could be balanced slightly by Schottky w/ bigger Vf at output V11.

## Miscellaneous Waveforms

The waveform of the voltage on switchnode (drain to gnd) is shown in Figure 8.

 


Figure 8

The waveform of the voltage on switchnode (anode D1 to gnd) is shown in Figure 9.

 


Figure 9

The waveform of the voltage on diode D2 (referenced to VOUT2) is shown in Figure 10.

 


Figure 10

The waveform of the voltage on switchnode (cathode D3 to GND) is shown in Figure 11.

 


Figure 11

The waveform of the voltage on switchnode (cathode D41 to GND) is shown in Figure 12.


 


Figure 12

## 8 Thermal Image

 

Load resistors at output 1 and 3 (right handed) are radiating to the power stage;  
The rectifiers and the controller are below 50c at 23c ambient temperature.  
The losses at output 2 and output 4 are minor, total converter losses are 163mW.

Name	Temperature
D3	43.9°C
D1	44.4°C
U1	41.5°C

# PMP10051RevB Test Results

---

**For Feasibility Evaluation Only, in Laboratory/Development Environments.** The reference design is not a complete product. It is intended solely for use for preliminary feasibility evaluation in laboratory / development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical / mechanical components, systems and subsystems. It should not be used as all or part of a production unit.

**Your Sole Responsibility and Risk.** You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the reference design for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the reference design. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the reference design and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. Since the REFERENCE DESIGN is not a completed product, it may not meet all applicable regulatory and safety compliance standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the reference design will not result in any property damage, injury or death, even if the REFERENCE DESIGN should fail to perform as described or expected.

**Certain Instructions.** Exceeding the specified reference design ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the reference design and/or interface electronics. Please consult the reference design User's Guide prior to connecting any load to the reference design output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output ranges are maintained at nominal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the reference design schematic. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch.

**Agreement to Defend, Indemnify and Hold Harmless.** You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the reference design that is not in accordance with the terms of this agreement. This obligation shall apply whether Claims arise under the law of tort or contract or any other legal theory, and even if the reference design fails to perform as described or expected.

**Safety-Critical or Life-Critical Applications.** If you intend to evaluate TI components for possible use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated