

# TI Designs

## Tiny I<sup>2</sup>C-Controlled Single-Cell Charger Reference Design for Wearable Applications



### Description

The TIDA-03042 TI Design is a single-cell charger reference design for wearable applications which have a very limited design space. TIDA-03042 works with a host controller through I<sup>2</sup>C control, supports 5-V, 9-V, or 12-V input adaptors and can charge up to 1.5 A. The actual charger design only requires a space of 1.7 cm<sup>2</sup>, allowing for high charging efficiency while minimizing the total count of components and board size.

### Resources

[TIDA-03042](#)  
[BQ25898](#)

Design Folder  
Product Folder




[ASK Our E2E Experts](#)

### Features


- Up to 1.5-A Single-Cell Charger
- Charge Efficiency of 92% at 0.5 A and 1.5 A
- Low-Power PFM Mode for Light Load Operations
- High-Input Voltage Operation Range From 3.9 V to 14 V
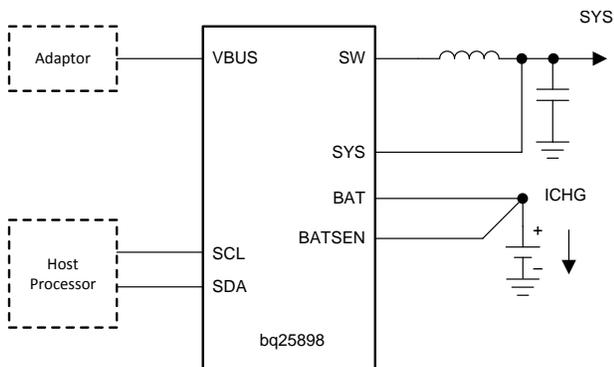
### Applications

- Smart Watch
- Activity Tracker
- Headset



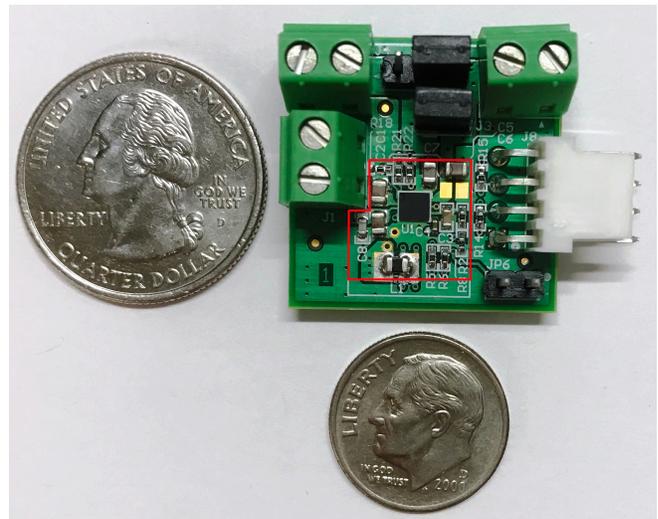Copyright © 2017, Texas Instruments Incorporated



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

# 1 System Overview

## 1.1 System Description

This system is designed as a reference for smart watch and all other wearable applications that require up to 1.5-A charge current for a single-cell Li-Ion battery. This TIDA-03042 design requires a host controller to set the target pre-charge current, fast charge current, charge termination current, charge voltage limit, and the applicable charging profile parameters for the specific single-cell Li-Ion battery in use through I<sup>2</sup>C control. The TIDA-03042 design can be used as a standard charger module for various single-cell Li-Ion battery designs.


## 1.2 Key System Specifications

**Table 1. Key System Specifications**

PARAMETER	DESCRIPTION	MIN	TYP	MAX	UNIT
VBUS	Input voltage from AC adaptor	3.9	—	14	V
VBAT	Voltage applied to BAT pin	0	—	4.5	V
ICHG	Fast charge current	0	—	2	A
IINDPM	Input current limit	0	—	1.5	A

## 1.3 Block Diagram

Figure 1 shows the block diagram of the TIDA-03042.

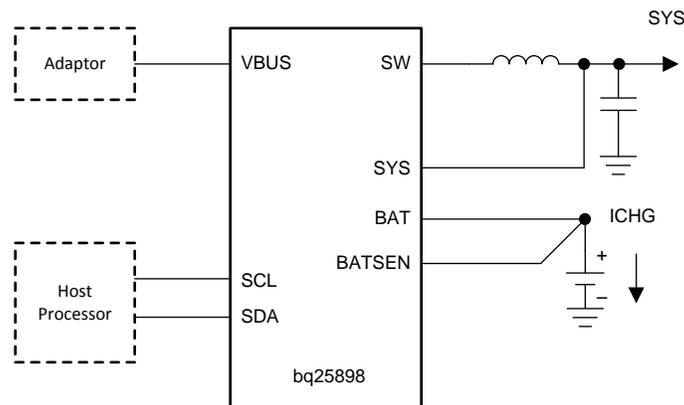

Copyright © 2017, Texas Instruments Incorporated

**Figure 1. TIDA-03042 Block Diagram**

## 1.4 Highlighted Products

### 1.4.1 BQ25898

The BQ25898 is a highly-integrated switch-mode battery charge management and system power path management device for a single-cell Li-Ion and Li-polymer battery for power banks, tablets, and other portable device applications. Its low-impedance power path optimizes switch-mode operation efficiency, reduces battery charging time, and extends battery life during discharging phase. The I<sup>2</sup>C serial interface with charging and system settings makes the device a truly flexible solution. The device has the following key features:

- High-efficiency, 1.5-MHz switch mode buck charge
  - Pulse-frequency modulation (PFM) at light load to boost low-power efficiency
- Single input to support USB input and adjustable high-voltage adapters
  - Supports 3.9-V to 14-V input voltage range
  - Input current limit (100 mA to 3.25 A with 50-mA resolution) to support USB2.0, USB3.0 standard, and high-voltage adapters
- Narrow VDC (NVDC) power-path management
  - Instant-on works with no battery or deeply-discharged battery
  - Ideal diode operation in battery supplement mode
- BATFET control to support ship mode, wakeup, and full-system reset
- Remote battery sensing
- High regulation accuracy
  - $\pm 0.5\%$  charge voltage regulation
  - $\pm 5\%$  charge current regulation
  - $\pm 7.5\%$  input current regulation

## 2 System Design Theory

### 2.1 Charger With Remote Battery Sensing

The bq25898 charger integrated circuit (IC) is used in this TI Design with remote battery sensing to improve the charge voltage accuracy and reduce the charge time.

### 2.2 Default Power-On Reset Setting

All registers reset to the default values when the device has been powered up on reset. [Table 2](#) lists the device default charging parameters.

**Table 2. bq25898 Charging Parameter Default Setting**

DEFAULT MODE	bq25898
Charging voltage	4.208 V
Charging current	2.048 A
Pre-charge current	128 mA
Termination current	256 mA
Temperature profile	JEITA
Safety timer	12 hours

### 2.3 Host Control

The host can access all the registers after power-on reset (POR) and control the charging operations and optimize the charging parameters by writing to the corresponding registers through I<sup>2</sup>C.

The input current limit set by the ILIM pin is 1.5 A. The actual input current limit is the lower limit set by the ILIM pin (when the EN\_ILIM bit REG00[6] is high) or IINLIM register bits (REG00[5:0]).

## 3 Getting Started Hardware and Software

### 3.1 Hardware

#### 3.1.1 Power Supplies

For testing purposes, this reference design requires a power supply capable of supplying at least 2 A.

#### 3.1.2 Battery Simulator

For testing purposes, a battery simulator capable of sinking and sourcing current with constant voltage mode is required to test the charging function of the reference design.

#### 3.1.3 EV2300/EV2400 I<sup>2</sup>C Adapter for PC Connection

The EV2300/EV2400 is a USB-based interface board for the PC that can be used to evaluate battery charger circuits designed with ICs from Texas Instruments. The EV2300/EV2400 board has connections on it for a USB cable and also accepts inputs from the communication port of a battery charger circuit. The EV2300/EV2400 interface board allows the user to evaluate the battery charger circuit by running the appropriate PC software for the corresponding charger IC.

---

**NOTE:** The driver on this page is for the 32-bit version of the Windows® operating system. See the post for the 64-bit driver on the E2E™ online community for the 64-bit Microsoft Windows® 7 driver information.

---

### 3.2 bqStudio Software

Battery Management Studio (bqStudio) offers a full suite of robust tools to assist with the process of evaluating, designing with, configuring, testing, or otherwise using TI battery-management products. This software includes the following features:

- Full access to registers and data memory including support for real-time watching, graphing, and logging an easy interface to send commands, direct low-level communication, and I/O
- Automated and guided support for configuration, calibration, performing a learning cycle, and generating useful files for taking the device to production

---

**NOTE:** Older products such as bq2419x and bq2429x are not supported in bqStudio. Download the specific evaluation software from the appropriate product page.

---

To download the bqStudio software, see the file "Battery Management Studio (bqStudio) Software Suite" at <http://www.ti.com/tool/bqstudio>.

## 4 Testing and Results

### 4.1 Test Equipment

The following subsections describe the test equipment and their purpose when testing this TI Design.

#### 4.1.1 Laptop PC

A laptop PC with a Windows 7 operating system is used to run the bqStuido software with an EV2300/EV2400 adapter.

#### 4.1.2 EV2300/EV2400 Adapter

The EV2300/EV2400 adapter is used between the PC and the reference design board for I<sup>2</sup>C communication to control the test.

#### 4.1.3 Agilent Multimeters

Multimeters are used to measure the currents and voltages during the related tests.

#### 4.1.4 Kepco Bipolar Operational Power Supply

A Kepco power supply is used to simulate a battery that can be charged and discharged.

#### 4.1.5 Hewlett Packard System DC Power Supply

A power supply is used to supply the VBUS power to charge during the charger test.

#### 4.1.6 TIDA-03042 Board

The TIDA-03042 board is a printed-circuit board (PCB) with all the devices in this design.

## 4.2 Test Bench Setup

Figure 2 shows the test bench setup.

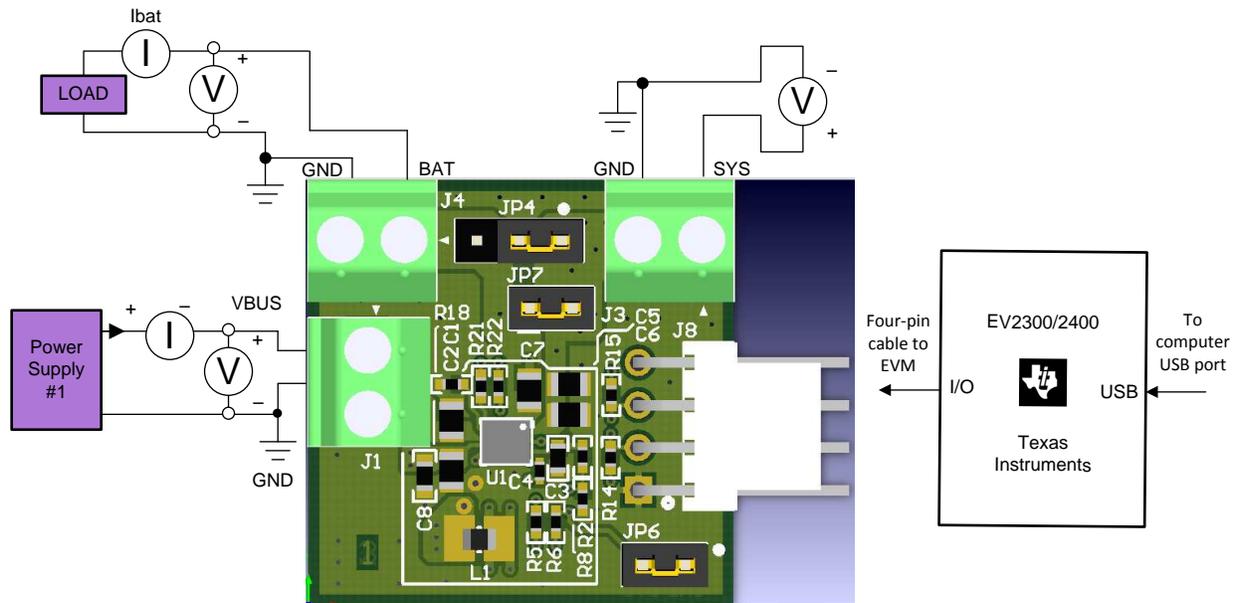


Figure 2. Test Setup

## 4.3 Test Results

### 4.3.1 Major Outputs Test

Table 3. Major Outputs Test Results

PARAMETER	TEST CONDITION	TYP	UNIT
SYS voltage	VBUS = 5 V, ICHG = 0 mA (charge disabled), MIN SYS SETTING = 3.5 V	3.74	V
Precharge current	VBUS = 5 V, VBAT = 2.8 V, IPRECHG SETTING = 128 mA	149	mA
Fast charge current	VBUS = 5 V, VBAT = 3.8 V, ICHG SETTING = 2 A	1.937	A
Charge voltage limit	VBUS = 5 V, VBAT SETTING = 4.208 V	4.208	V
OTG output voltage	VBAT = 4 V, IOTG = 0 A, VOTG SETTING = 4.998 V	5.028	V

### 4.3.2 Charging Efficiency at VBUS = 5 V

Figure 3 shows the efficiency values for common charge-current thresholds using the TIDA-03042 with a bq25898 device. In this example, users can see that the efficiency peaks around ICHG = 0.7 A @ about 92.5% efficiency.

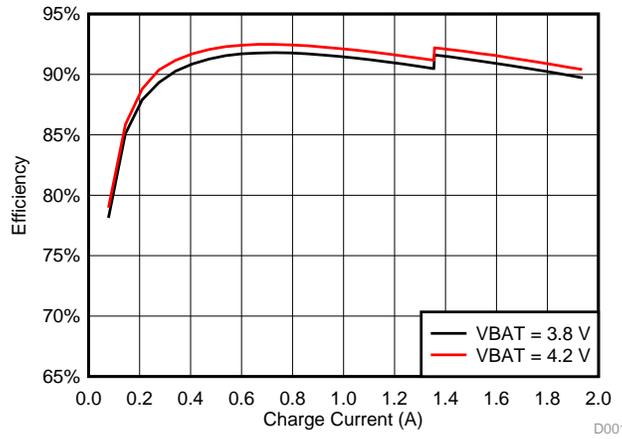


Figure 3. Charging Efficiency at VBUS = 5 V

### 4.3.3 Thermal Performance at VBUS = 5 V and ICHG = 0.5 A

Figure 4, Figure 5, and Figure 6 show the thermal performances of the TIDA-03042 design. The IC temperature only rises to approximately 37°C when ICHG = 0.5 A on such a tiny board.

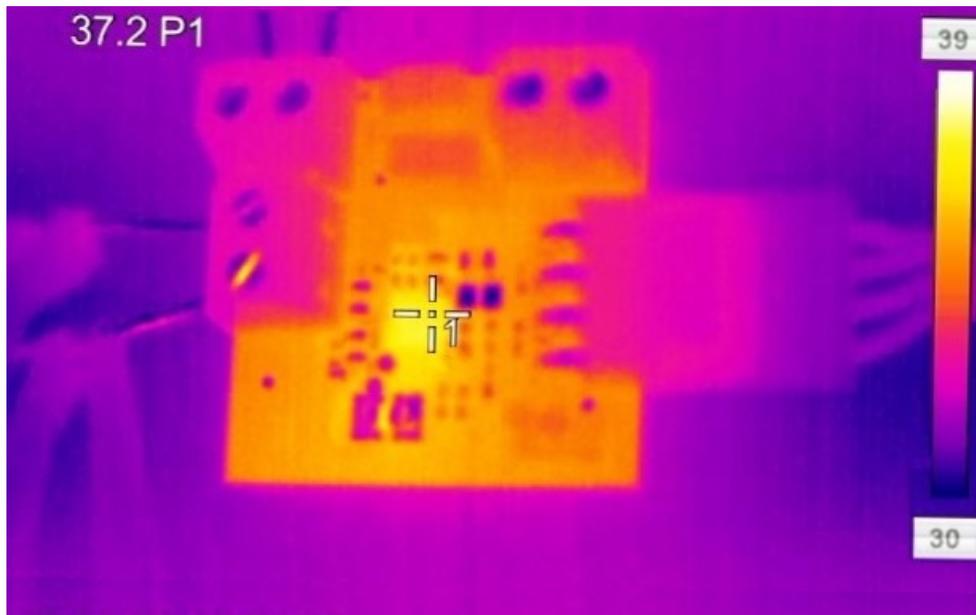


Figure 4. Thermal Performance at VBUS = 5 V and ICHG = 0.5 A

#### 4.3.4 Thermal Performance at VBUS = 5 V and ICHG = 1.0 A

Figure 5 shows the IC temperature rises to approximately 42°C when ICHG = 1 A.



Figure 5. Thermal Performance at VBUS = 5 V and ICHG = 1 A

#### 4.3.5 Thermal Performance at VBUS = 5 V and ICHG = 1.5 A

Figure 6 shows the IC temperature rises to approximately 50°C when ICHG = 1.5 A.

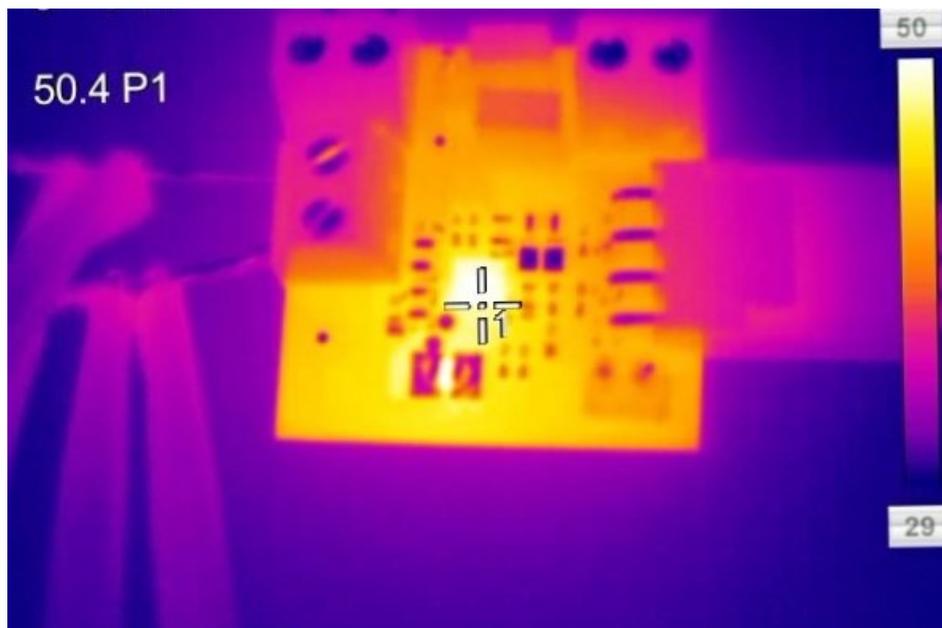


Figure 6. Thermal Performance at VBUS = 5 V and ICHG = 1.5 A

## 5 Design Files

### 5.1 Schematics

To download the schematics, see the design files at [TIDA-03042](#).

### 5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-03042](#).

### 5.3 Altium Project

To download the Altium project files, see the design files at [TIDA-03042](#).

### 5.4 Gerber Files

To download the Gerber files, see the design files at [TIDA-03042](#).

### 5.5 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-03042](#).

### 5.6 Trademarks

E2E is a trademark of Texas Instruments.

Windows is a registered trademark of Microsoft Corporation.

All other trademarks are the property of their respective owners.

## 6 About the Author

**NING TANG** is an applications engineer at Texas Instruments supporting switching converter solutions in battery charging applications. She is responsible for providing technical support and developing EVMs and design notes for single-cell chargers. Ning brings to this role her more than 10 years of extensive experiences in the switching power supply design field.

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated