

Powering Multiple Image Sensors with the Same Power Management IC

David Arciniega, Gerard Copeland

1 Introduction

Image sensors in automotive applications have become the mainstream. As more and more sensors are being integrated into automobiles, the need for automotive camera modules has increased significantly. Thermals, size, and performance are all critical in the design of the automotive camera modules and are equally important. Therefore, the camera module designer must take all three items into account. With multiple sensor vendors and each sensor vendor offering multiple sensor options, designing the camera module can be simplified if the same power scheme can be used on all designs.

2 Device Overview

Powering all the various image sensors out in the market today can be simplified by using a fully programmable Power Management IC such as the TPS650330-Q1 Power Management IC. The TPS650330-Q1 Power Management IC has been designed to accept an input voltage range from 4 V to 18.3 V since camera modules are being used in a wide range of applications, such as surround view cameras, smart rear view cameras, remote front cameras, driver monitoring, and cabin monitoring. With each voltage rail having its own independent input and output pins, designing over a wide range of applications is simplified.

3 Device Description

For applications which require functional safety, such as 360° view L5 autonomous driving, blind spot detection, and eMirrors, the TPS650330-Q1 is part of a pin compatible drop in replacement family which integrates functional safety features. Contact Texas Instruments™ for additional information on these devices.

With the TPS650330-Q1 Power Management IC, the required voltages to power any Image Sensor are fully programmable. If power sequencing is needed, the TPS650330-Q1 can be programmed to meet the power sequencing requirements. All this is done internal to the device eliminating the need to use external resistors for voltage settings or connections to meet the power sequencing requirements. By integrating these features, the overall solution size is reduced.

The examples shown in [Figure 1](#), [Figure 2](#), and [Figure 3](#) highlight how one Power Management IC can be used to power multiple sensors from different sensor vendors in a Power over Coax (PoC) application. At least one of the output voltage settings is different in each example, and the same device is being used since the TPS650330-Q1 is fully programmable.

(1) Texas Instruments is a trademark of Texas Instruments.
(2) AR02333 is a trademark of Aptina Imaging Corporation.
(3) Aptina is a registered trademark of Aptina Imaging Corporation.
(4) OV2775 is a trademark of OmniVision Technologies Inc.
(5) Omnivision is a registered trademark of OmniVision Technologies Inc.
(6) IMX390 is a trademark of Sony Corporation.
(7) Sony is a registered trademark of Sony Corporation.
(8) All other trademarks are the property of their respective owners.

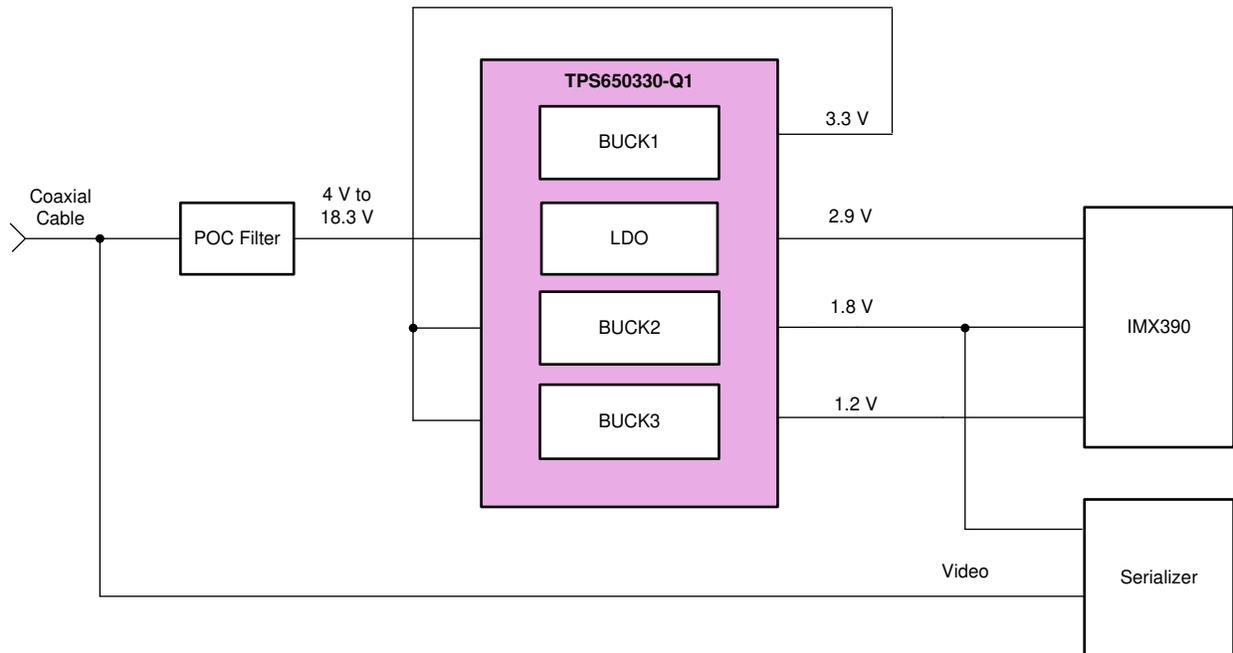


Figure 1. Sony® IMX390™ Powered by the TPS650330-Q1 Power Management IC (Texas Instruments Reference Design [TIDA-020003](#))

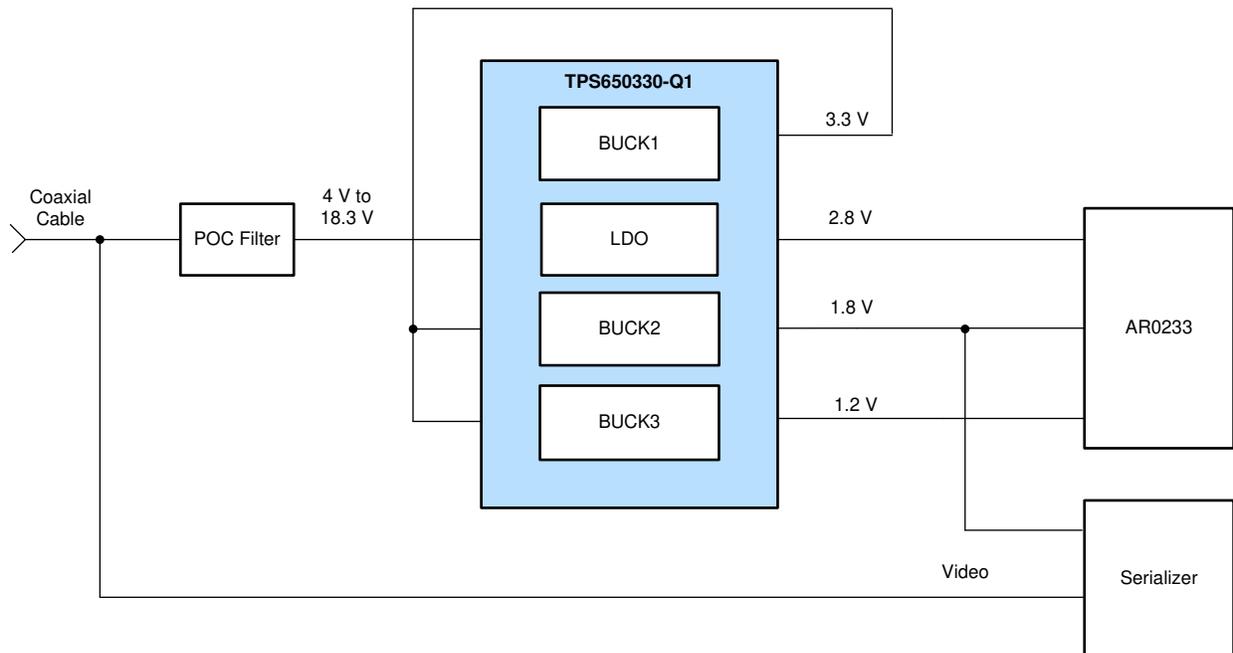


Figure 2. Aptina® AR0233™ Powered by the TPS650330-Q1 Power Management IC (Texas Instruments Reference Design [TIDA-050035](#))

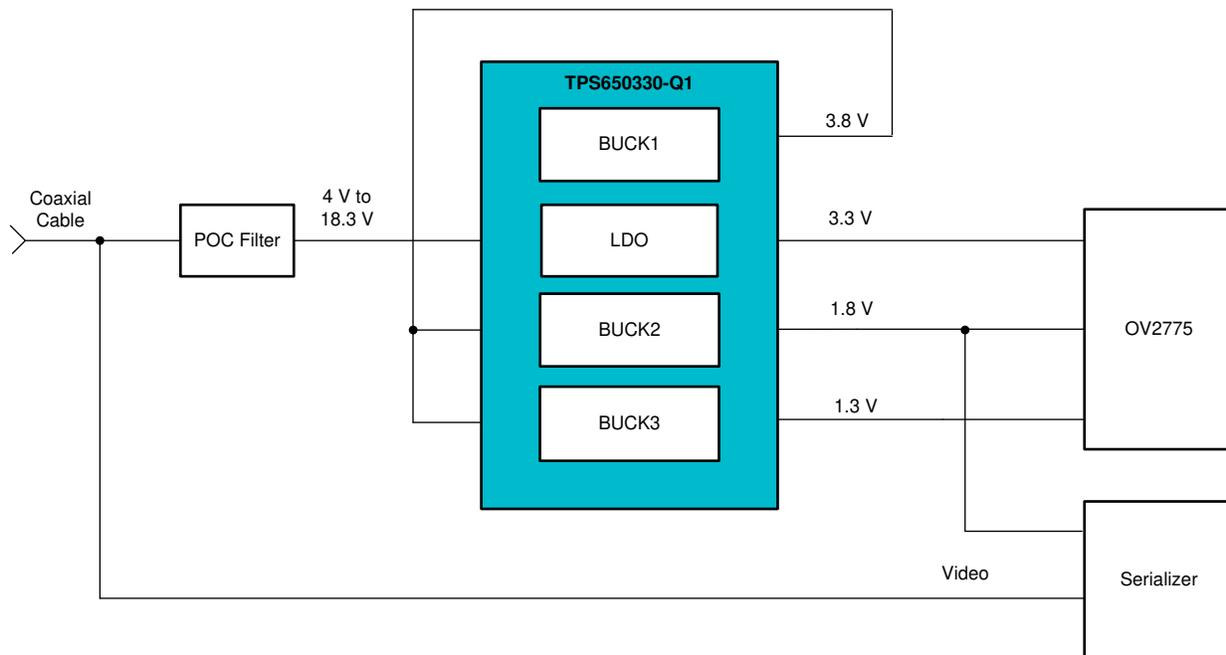


Figure 3. Omnivision® OV2775™ Powered by the TPS650330-Q1 Power Management IC

The TPS650330-Q1 device integrates highly efficient regulators to meet the strict system-level thermal requirements. The configuration of the TPS650330-Q1 device also plays a key role in making sure the overall system-level efficiency minimizes the power dissipation. The following graph compares three different configurations for a power over coaxial application.

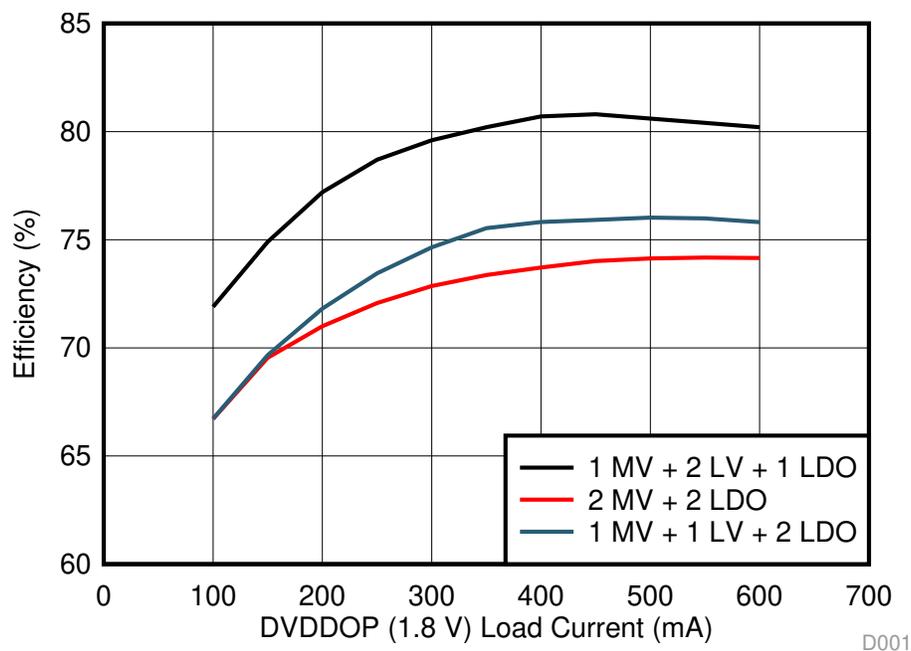


Figure 4. Overall System Level Efficiency Comparison Graph ⁽⁹⁾

⁽⁹⁾ Legend:
 • MV—Refers to a Mid Voltage Buck
 • LV—Refers to a Low Voltage Buck
 • LDO—Refers to a Low Dropout Regulator

The 1 MV + 2 LV + 1 LDO configuration is for the TPS650330-Q1. Comparing [Figure 5](#) and [Figure 6](#) shows the impact the 2 MV + 2 LDO and 1 MV + 1 LV + 2 LDO configurations have on the overall system level efficiency.

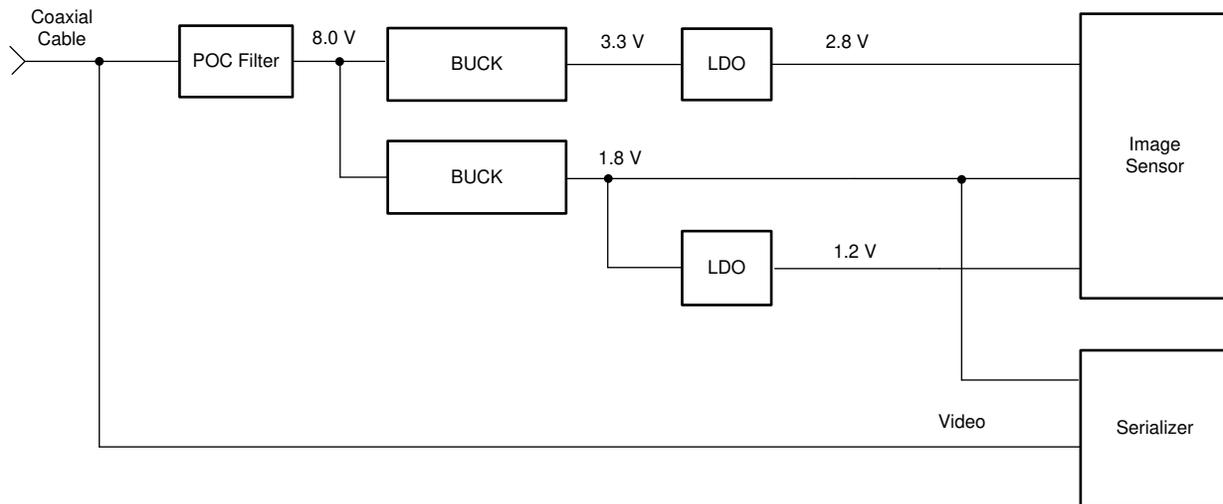


Figure 5. 2 MV + 2 LDO Configuration

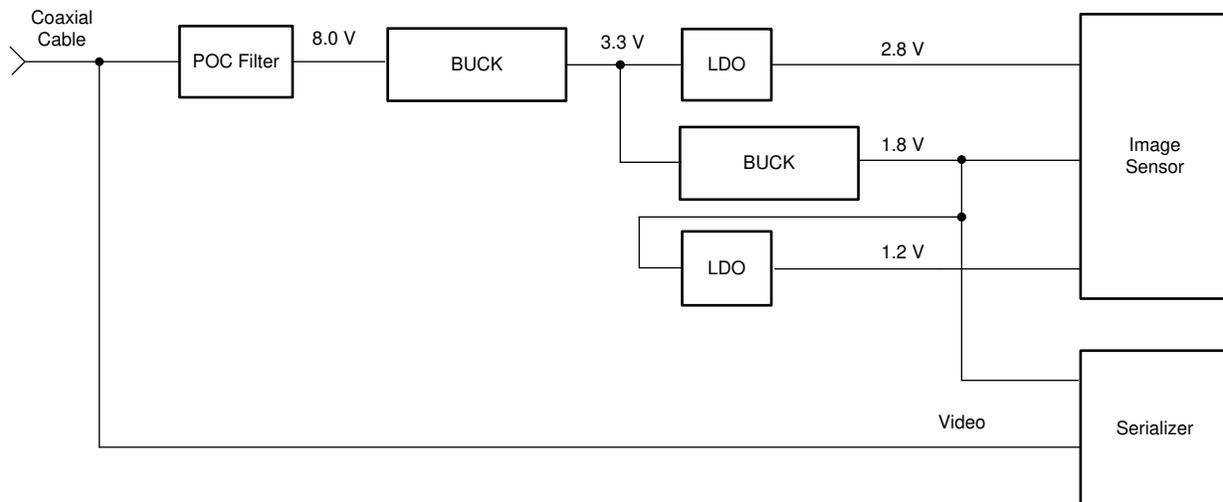


Figure 6. 1 MV + 1 LV + 2 LDO Configuration

The overall solution size challenge is accomplished with the design of the internal regulators. The regulators have been designed to take advantage of the smallest external components available in the market today which meet the overall system load requirements.

[Figure 7](#) and [Figure 8](#) provide examples of small, single board solution sizes that can be achieved. The layouts include the TPS650330-Q1 PMIC, the DS90UB953-Q1 serializer, and their required passive components including the Power Over Coax (POC) filter. A typical image sensor is shown on the opposite side for size reference.

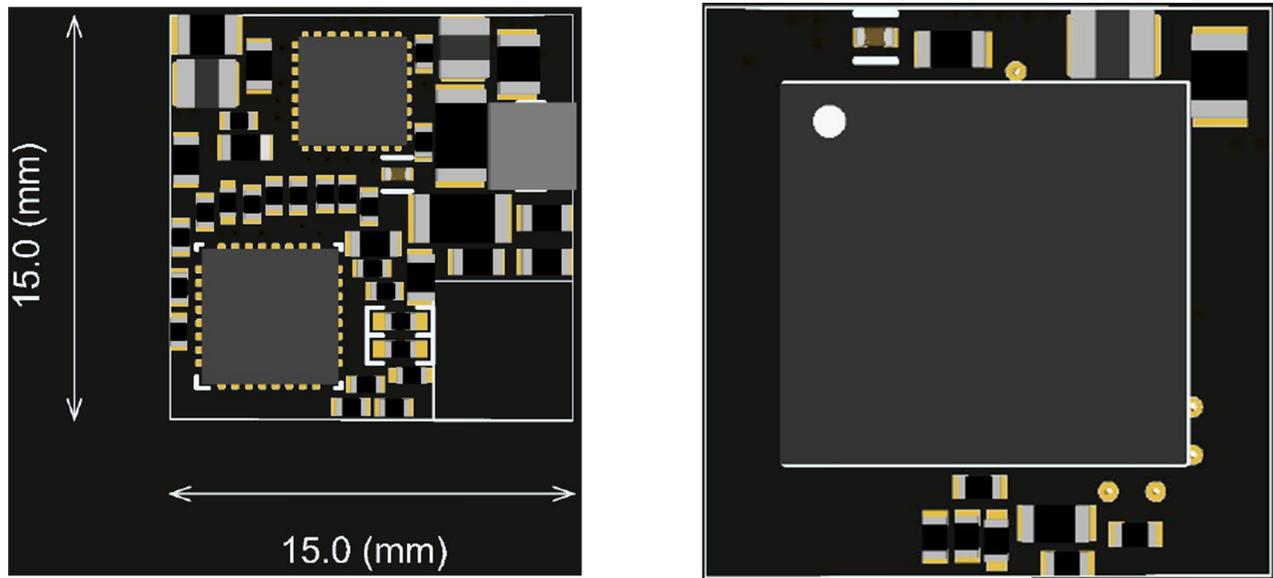


Figure 7. Layout Example – Double Sided

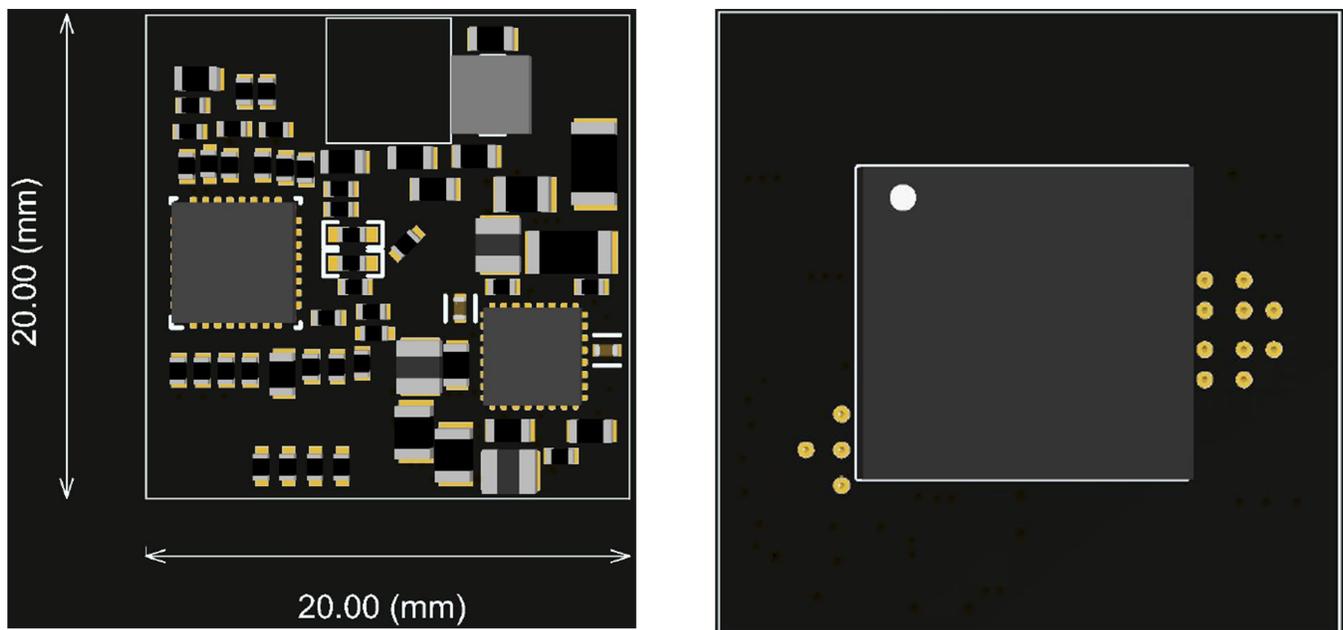


Figure 8. Layout Example – Single Sided

From a performance point of view, noise and EMI are two items which impact the system-level performance. The TPS650330-Q1 device integrates a low noise LDO that can be used to power sensitive analog rails of the Image Sensors. EMI reduction techniques have been implemented in the integrated DCDC converters of the TPS650330-Q1. One such technique is the implementation of an Adaptive Randomized Spread Spectrum (ARSS), which is a technique patented by Texas Instruments. See the [Passing CISPR-25 Radiated and Conduction Emissions Using the TPS65033x-Q1](#) application report for more information regarding TPS650330-Q1 EMI performance. Collectively, these items help the camera module designer meet some of the performance challenges being dealt with today.

Camera Module designers may conclude that a high current load on the LDO output will result in a higher power loss and that using a DCDC converter may make sense even though the integrated LDO can support a sizeable current load. In this case, see [Figure 9](#) for an example of how one of the integrated DCDC converters can be used to power the analog rail in order to minimize the power loss.

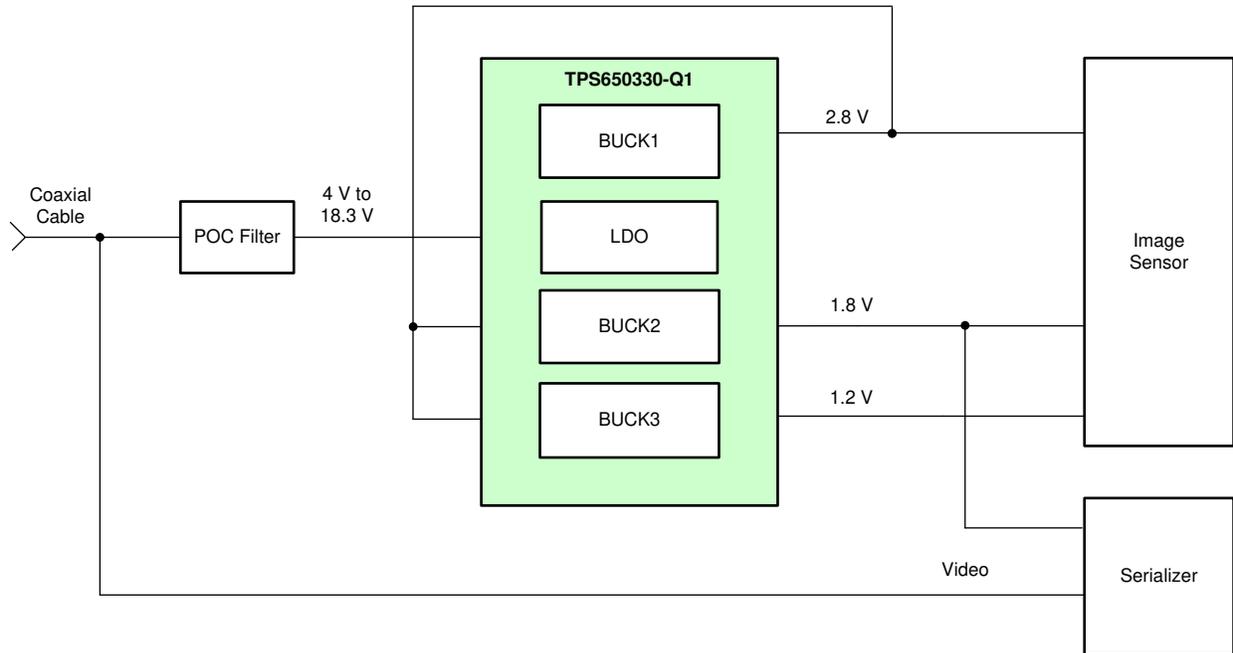


Figure 9. Using a DCDC Converter to Power the Analog Rail.

4 Summary

The flexibility of the TPS650330-Q1 device makes it the ideal power solution for any camera module design. Using the TPS650330-Q1 Power Management IC reduces time to market and adds the peace of mind that a proven power solution on one camera module design will easily port over to any camera module design. By minimizing external components and integrating functional safety features into pin compatible PMICs, layout and component changes become a thing of the past with the TPS650330-Q1.

5 References

1. Automotive 2-MP Camera Module Reference Design with MIPI CSI-2 Interface, PMIC, FPD-Link III and POC ([TIDA-020003](#)).
2. Scalable Automotive 2-MP Camera Module Reference Design with Camera PMIC ([TIDA-050035](#)).
3. Passing CISPR-25 Radiated and Conduction Emissions Using the TPS65033x-Q1 ([SLVAEN0](#)).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated