

# Loop Response Considerations for Peak Current Mode Buck LED Driver Application

Sean Zhou

## ABSTRACT

A popular LED driver is the internal loop compensated Peak Current Mode (PCM) buck. The loop response is good for proper inductor and output capacitor design, but improper inductor and output capacitor values can lead to instability or bad transient performance. This application report details the PCM buck LED driver, analyzes the stability constraint, and provides a simple equation to calculate bandwidth and phase margin of the converter.

The model proposed in this application report is introduced in [Section 1](#). [Section 2](#) provides peak current mode loop modeling. The inside current loop is simplified as a single pole. The overall loop response transfer function is obtained. The inductor and output capacitor design limits are derived considering loop response. At the end of this section, the equation to calculate bandwidth and phase margin is provided. In [Section 3](#), the inductor and output capacitor is designed step-by-step considering loop response. The theory is verified by simulation and bench measurement results.

## Contents

1	Introduction .....	2
2	Peak Current Mode Loop Modeling .....	2
3	Inductor and Output Capacitor Design .....	8
4	Summary .....	12
5	References .....	12

## List of Figures

1	Simplified Schematic for PCM Buck LED Driver .....	2
2	V-I Characteristic of LED(SFH4715A) .....	3
3	R <sub>LED</sub> Test .....	3
4	Update Simplified Schematic for PCM Buck LED Driver .....	4
5	Overall Control Implementation .....	5
6	Bode Plot Model for PCM Buck LED Driver.....	7
7	TPS92200D1 Design With 2 IRLED, 1.0-A Output .....	10
8	Schematic of a Simplified SIMPLIS Model.....	10
9	Bode Plot Simulation Result at V <sub>IN</sub> = 12 V, I <sub>O</sub> = 1 A .....	11
10	Bode Plot Test Result at V <sub>IN</sub> = 12 V, I <sub>O</sub> = 1 A.....	11

## List of Tables

1	Design Example Specification .....	8
2	Calculation, Simulation, and Bench Measurement Results Comparison .....	12

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction

This application report uses the TPS92200D1 and TPS92200D2[1] (hereafter referred to as TPS92200D1/D2) as the example to analyze the control loop. The TPS92200D1/D2 regulator is an easy-to-use synchronous step-down LED driver operating from 4-V to 30-V supply voltage. It is capable of delivering up to 1.5-A DC load current in a very small solution size with very flexible dimming method. The device is suitable for a wide range of applications from consumer to industrial for power conditioning from an unregulated source. The TPS92200D1/D2 employs peak-current mode control with internal loop compensation, which reduces design time, and requires few external components.

A lot of PCM loop models are available for system design. The most popular model is provided in *A New Small-Signal Model for Current-Mode Control* [2]. The model predicted the sample and hold effects in the current loop, while using a three-terminal switch model to calculate the power stage small-signal model. Using this method, a simplified loop model is provided in the *TPS65270 Loop Compensation Design Consideration Application Report*[3], and an equivalent circuit is obtained to simulate the loop response. However, all of the models require simulation tools to draw the bode plot, then find a crossover frequency and phase margin based on the bode plot. Besides, the transfer function of inner current loop is quite complex, making it hard to understand how it impacts the whole loop response. In this document, a simple equation is provided to calculate bandwidth. The phase margin is obtained by simplifying the inside current loop as a single pole. The inner current loop stability criteria can be obtained based on the model. Each zero and pole in the model has a clear physical meaning, making it easy to analyze the impact of each component value on the loop response. The inductor and output capacitor design procedure of the internally compensated PCM buck LED driver is given using the model. The model accuracy is verified by both simulation and bench measurement results.

## 2 Peak Current Mode Loop Modeling

### 2.1 Overall Control Block Diagram and Transfer Function Derivation

Figure 1 shows the simplified schematic for the PCM buck LED driver.


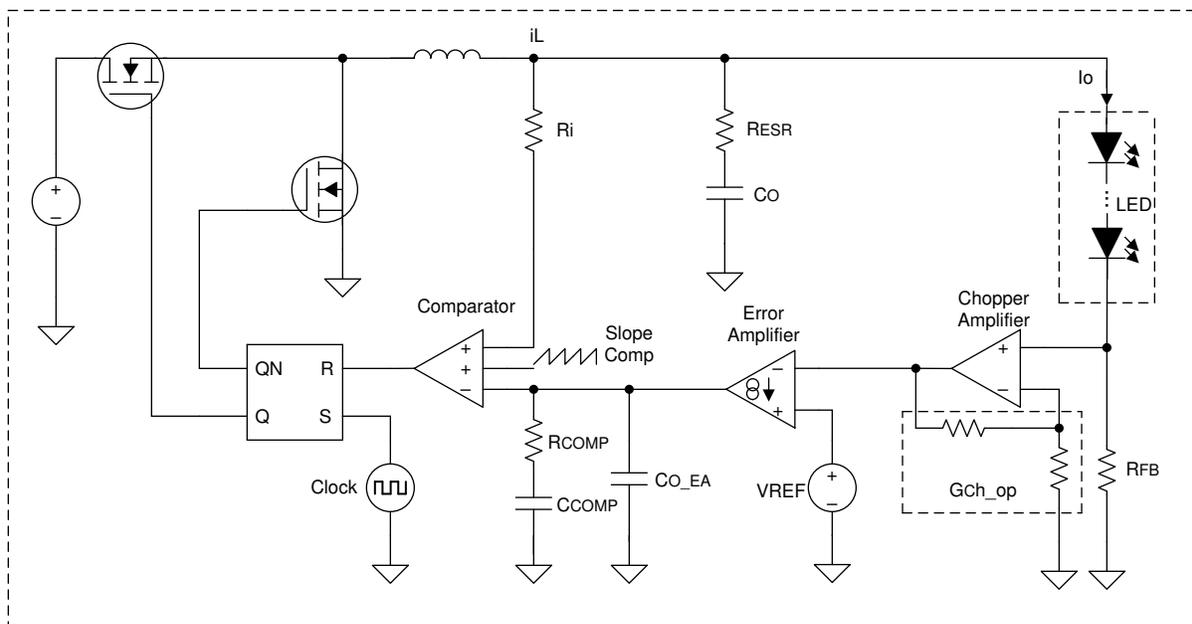


Figure 1. Simplified Schematic for PCM Buck LED Driver

Since this is for an LED driver, the load is a little different comparing with traditional resistor load when considering the loop. The LED has the non-linear V-I characteristic, **Figure 2** shows a typical V-I characteristics of the Osram Infrared (IR) LED: SFH4715A.


It is clear that the LED needs a threshold bias voltage, it only conducts some leakage current below the minimum forward threshold bias voltage. And it is also non-linear above threshold bias voltage. When considering the loop response of the LED load, it needs to linearize near the working point. For example, when it works under 1.5 A, the forward voltage is about 1.44 V, it can get the linearized resistance  $R_{LED}$  as shown in **Figure 2**.

It models the LED load with a DC bias power supply  $V_{th}$  with a serial resistance  $R_{LED}$  as **Figure 2** shows.

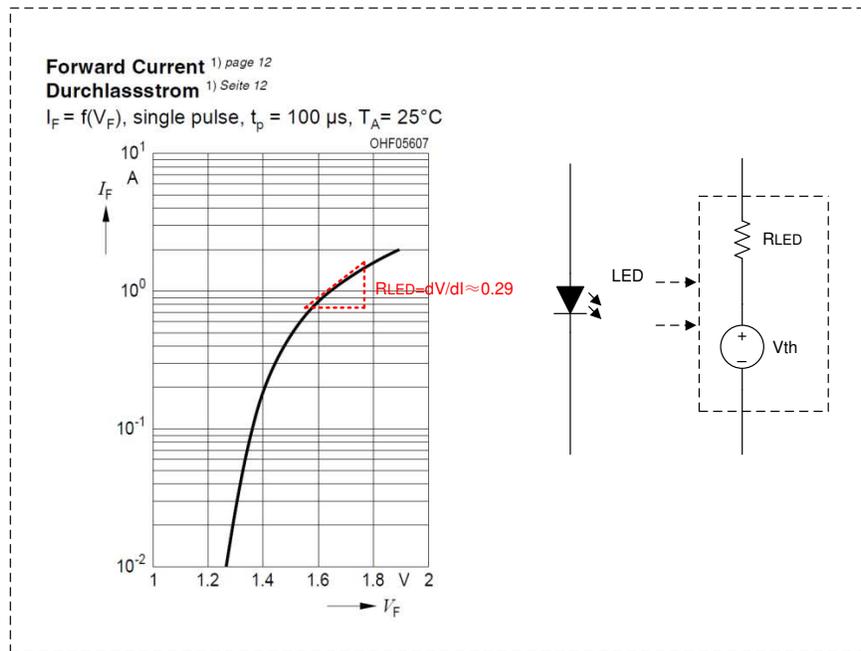


**Figure 2. V-I Characteristic of LED(SFH4715A)**

**Figure 3** shows the tested  $R_{LED}$  of IR LED (SFH4715A) and White LED (XMLAWT0T5051).

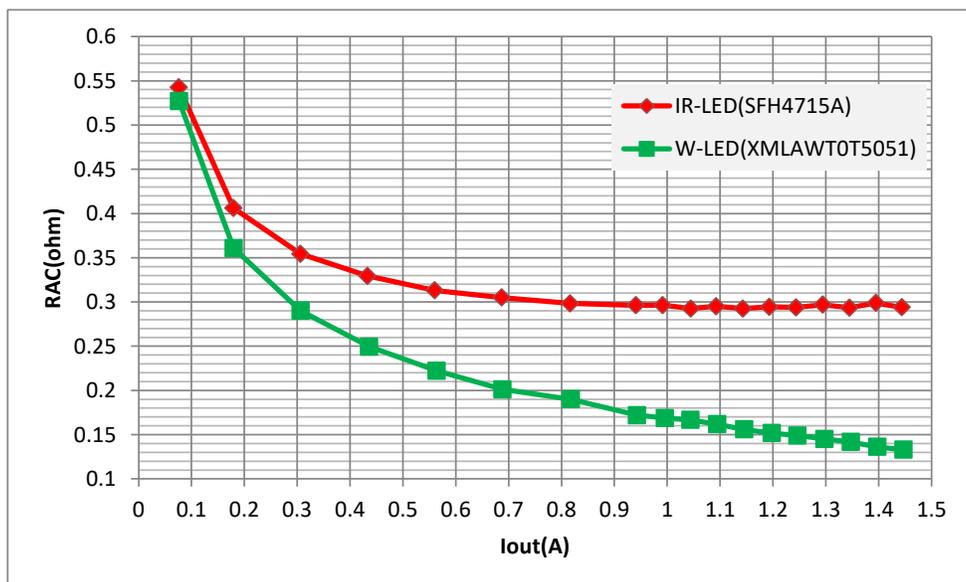

**Figure 3.  $R_{LED}$  Test**


When the LED model is connected to the circuit in [Figure 1](#), you get a simplified schematic for the PCM buck LED driver as [Figure 4](#) shows.

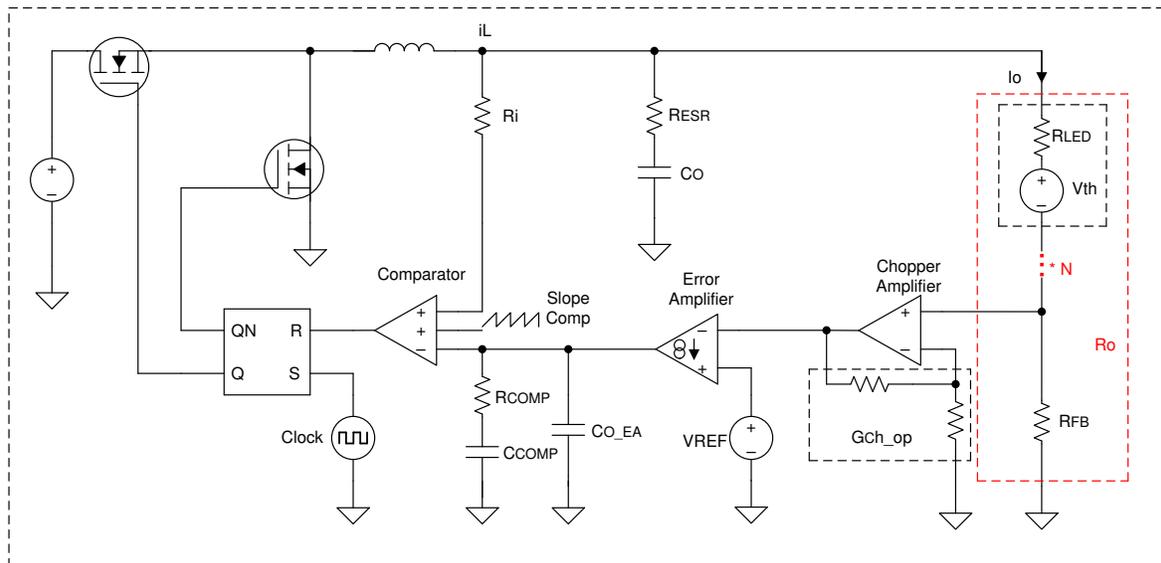

**Figure 4. Update Simplified Schematic for PCM Buck LED Driver**

$R_{FB}$  is used to set the maximum current, Since  $R_{FB}$  is serially connected with the LED load, so the total output resistance load is obtained as [Figure 5](#) illustrates.

$$R_o = N * R_{LED} + R_{FB} \quad (1)$$

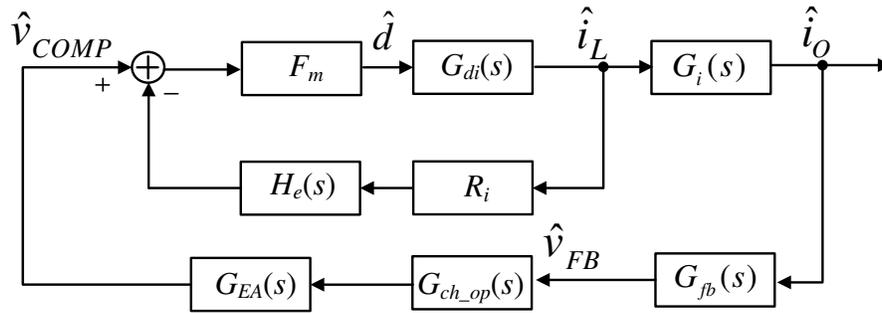

**Figure 5. Overall Control Implementation**

Figure 5 shows the overall control block model where:

- $G_{di}(s)$  is the duty cycle to  $i_L$  transfer function
- $G_i(s)$  is the  $i_L$  to  $i_o$  transfer function
- $G_{fb}(s)$  is the  $i_o$  to  $V_{FB}$  transfer function
- $G_{ch\_op}(s)$  is the gain of the chopper amplifier
- $G_{EA}(s)$  is the transfer function of the error amplifier with certain compensation
- $F_m$  is the gain of PCM PWM comparator
- $R_i$  is the current sensing resistor
- $H_e(s)$  is the transfer function model of inductor current sampling-hold effect

Equation 2 shows the transfer function from the inductor current to the output current.

$$G_i(s) = \frac{\hat{i}_O(s)}{\hat{i}_L(s)} = \frac{1 + sR_{ESR}C_O}{1 + s(R_{ESR} + R_O)C_O} \quad (2)$$

$G_{di}(s)$  is the duty cycle to the  $i_L$  transfer function.

$$G_{di}(s) = \frac{\hat{i}_L(s)}{\hat{d}(s)} = \frac{V_{IN}(1 + sC_O R_O)}{R_O + sL + s^2 LC_O R_O} \quad (3)$$

The internal loop compensation is designed so that the crossover frequency is much higher than the corner frequency,  $1/(2\pi\sqrt{LC_O})$ . For crossover frequency and higher frequency, Equation 3 can be simplified as Equation 4.

$$G_{di}(s) = \frac{\hat{i}_L(s)}{\hat{d}(s)} \approx \frac{V_{IN}}{sL} \quad (4)$$

The sensed inductor current, external ramp, and the output of error amplifier  $V_{COMP}$  are compared, which determines when to turn off the high-side MOSFET, hence the duty cycle is determined.  $F_m$  is the comparator gain.  $f_{SW}$  is the switching frequency.  $S_n$  is the on-time slope of the sensed-current waveform and  $S_e$  is the external ramp slope.

$$F_m = \frac{f_{SW}}{S_n + S_e}$$

where

- $S_n = R_i \frac{V_{IN} - V_O}{L}$
- $S_e = V_{Se} \times f_{SW}$

(5)

$H_e(s)$  is the transfer function model of inductor current sampling-hold effect. [2]:

$$H_e(s) = \frac{s/f_{SW}}{e^{s/f_{SW}} - 1} \approx 1 - \frac{s}{2f_{SW}} + \frac{s^2}{(\pi f_{SW})^2} \quad (6)$$

Equation 7 shows the transfer function from  $i_L$  to  $i_o$ .

$$G_{fb}(s) = \frac{\hat{v}_{FB}(s)}{\hat{i}_O(s)} = R_{FB} \quad (7)$$

Equation 8 shows the transfer function of the error amplifier with certain compensation.

$$G_{EA}(s) = \frac{\hat{v}_{COMP}(s)}{\hat{v}_{FB}(s)} = -G_m \frac{1 + sR_{COMP}C_{COMP}}{s(C_{COMP} + C_{O\_EA}) * \left(1 + sR_{COMP} \frac{C_{COMP}C_{O\_EA}}{C_{COMP} + C_{O\_EA}}\right)} \quad (8)$$

## 2.2 Inside Current Loop Model

Based on Equation 4 to Equation 6 and Figure 5, the transfer function from control to inductor current is  $G_{ci}(s)$ :

$$G_{ci}(s) = \frac{\hat{i}_L(s)}{\hat{v}_{COMP}(s)} = \frac{1}{R_i} \frac{1}{1 + s \times \left[ \frac{V_{Se} f_{SW} L + (0.5V_{IN} - V_O)R_i}{V_{IN} R_i f_{SW}} \right] + s^2 \times \frac{1}{(\pi f_{SW})^2}} \quad (9)$$

For the PCM buck converter, the crossover frequency is much smaller than half of the switching frequency, so around the crossover frequency, Equation 9 can be simplified as Equation 10. The inside current loop is simplified as a single pole, which is very helpful for the loop response analysis of the PCM buck converter.

$$G_{ci}(s) = \frac{\hat{i}_L(s)}{\hat{v}_{COMP}(s)} = \frac{1}{R_i} \frac{1}{1 + s \times \left[ \frac{V_{Se} f_{SW} L + (0.5V_{IN} - V_O)R_i}{V_{IN} R_i f_{SW}} \right]} \quad (10)$$

If the inside current loop  $G_{ci}(s)$  is not stable, subharmonic oscillation occurs. A system is stable as long as each of the poles of the closed loop transfer function lies in the left half plane. The minimum inductor value is calculated to prevent subharmonic oscillation:

$$L > \frac{R_i(V_O - 0.5V_{IN})}{V_{Se} f_{SW}} \quad (11)$$

### 2.3 Overall Loop Model

$f_{Z\_EA}$  and  $f_{P\_EA}$  are zeros and poles introduced by the error amplifier with certain compensation.  $f_{Z\_OUT}$  and  $f_{P\_OUT}$  are zeros and poles introduced by the output capacitor and load.  $f_{P\_ci}$  is the pole introduced by the inside current loop. Based on Equation 2, Equation 7, Equation 8, and Equation 10, the open loop transfer function  $L(s)$  around crossover frequency is obtained:

$$L(s) = G_i(s) \times G_{fb}(s) \times G_{EA}(s) \times G_{ci}(s) = -K \frac{\left(1 + \frac{s}{2\pi f_{Z\_EA}}\right) \times \left(1 + \frac{s}{2\pi f_{Z\_OUT}}\right)}{s \times \left(1 + \frac{s}{2\pi f_{P\_EA}}\right) \times \left(1 + \frac{s}{2\pi f_{P\_ci}}\right) \times \left(1 + \frac{s}{2\pi f_{P\_OUT}}\right)}$$

where

- $K = \frac{G_{ch\_op} * G_m * R_{FB}}{R_i(C_{COMP} + C_{O\_EA})}$
- $f_{Z\_EA} = \frac{1}{2\pi R_{COMP} C_{COMP}}$
- $f_{P\_EA} = \frac{1}{2\pi R_{COMP} \frac{C_{COMP} C_{O\_EA}}{C_{COMP} + C_{O\_EA}}}$
- $f_{P\_ci} = \frac{V_{IN} R_i f_{SW}}{2\pi [V_{Se} f_{SW} L + (0.5V_{IN} - V_O) R_i]}$
- $f_{Z\_OUT} = \frac{1}{2\pi R_{ESR} C_O}$
- $f_{P\_OUT} = \frac{1}{2\pi (R_{ESR} + R_O) C_O}$

(12)

### 2.4 Inductor and Output Capacitor Design Limits

Figure 6 shows the Bode plot with proper inductor and output capacitor design.

$f_c > f_{P\_OUT}$ ,  $f_c > f_{Z\_EA}$ ,  $f_c \ll f_{P\_EA}$ ,  $f_c \ll f_{P\_ci}$ ,  $f_c \ll f_{Z\_OUT}$

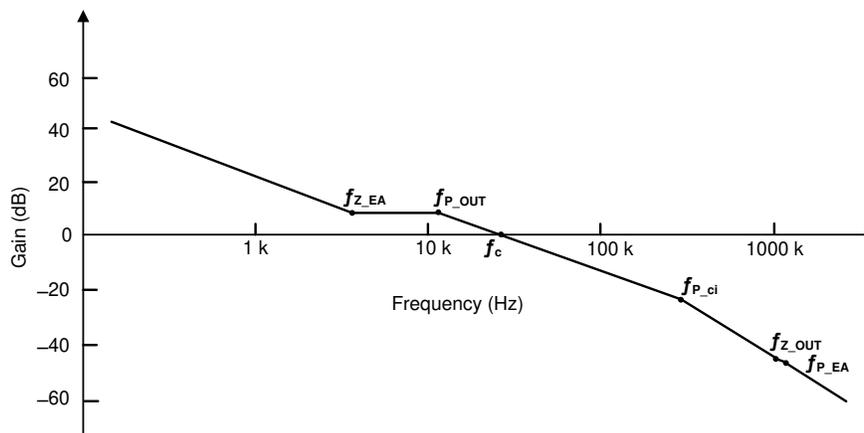


Figure 6. Bode Plot Model for PCM Buck LED Driver

The gain curve must go across 0 dB with a  $-20$  dB/dec slew rate, so that the phase margin is enough. The zero introduced by the compensation network  $f_{z\_EA}$  cancels the pole of output impedance  $f_{p\_OUT}$ , and they are placed before crossover frequency:  $f_{p\_OUT} < f_c$ ,  $f_{z\_EA} < f_c$ . The parasitic capacitor of error amplifier  $C_{O\_EA}$  is quite small, so  $f_{p\_EA} \gg f_c$ .

If  $L$  is too large, the pole introduced by the current loop  $f_{p\_ci}$  is smaller than the crossover frequency  $f_c$ . The gain curve goes across 0 dB with a  $-40$  dB/dec slew rate, and the phase margin is not enough. Additionally, the loop response is influenced by  $V_{IN}$  since  $f_{p\_ci}$  is influenced by  $V_{IN}$ . To prevent that from happening,  $L$  must be properly designed to ensure  $f_{p\_ci} \gg f_c$ . Equation 13 calculates the maximum inductor value.

$$L \ll \frac{V_{IN}R_i}{2\pi f_c V_{Se}} + \frac{(V_O - 0.5V_{IN})R_i}{V_{Se}f_{SW}} \quad (13)$$

If the Equivalent Series Resistance (ESR) of the output capacitor is too large, the zero introduced by the output capacitor  $f_{z\_OUT}$  is smaller than the crossover frequency  $f_c$ . The gain curve has a 0 dB/dec slew rate after  $f_{z\_OUT}$ , which makes the crossover frequency too large. Some high-frequency poles introduced by the parasitic parameters in the IC influence the phase margin, and the phase margin is not enough. To prevent that, the ESR of the output capacitor must be properly designed to ensure  $f_{z\_OUT} \gg f_c$ . Equation 14 calculates the maximum ESR.

$$R_{ESR} \ll \frac{1}{2\pi f_c C_O} \quad (14)$$

## 2.5 The Equation to Calculate Bandwidth and Phase Margin

From Equation 12 and considering  $f_c \gg f_{p\_OUT}$ ,  $f_c \gg f_{z\_EA}$ ,  $f_c \ll f_{p\_EA}$ ,  $f_c \ll f_{p\_ci}$ , and  $f_c \ll f_{z\_OUT}$ , the magnitude of the open loop transfer function at crossover frequency  $f_c$  is shown in Equation 15.

$$|L(j2\pi f_c)| = K \frac{\left|1 + j\frac{f_c}{f_{z\_EA}}\right| \times \left|1 + j\frac{f_c}{f_{z\_OUT}}\right|}{2\pi f_c \times \left|1 + j\frac{f_c}{f_{p\_EA}}\right| \times \left|1 + j\frac{f_c}{f_{p\_ci}}\right| \times \left|1 + j\frac{f_c}{f_{p\_OUT}}\right|} \approx K \frac{\left|1 + j\frac{f_c}{f_{z\_EA}}\right|}{2\pi f_c \times \left|1 + j\frac{f_c}{f_{p\_OUT}}\right|} = 1 \quad (15)$$

Considering  $R_{ESR} \ll R_O$ , the crossover frequency  $f_c$  is obtained in Equation 16.

$$f_c = \frac{(KR_{COMP}C_{COMP} - 1) + \sqrt{(1 - KR_{COMP}C_{COMP})^2 + 4KR_O C_O}}{4\pi R_O C_O} \quad (16)$$

Phase margin is the phase of the open loop transfer function at  $f_c$  minus  $-180^\circ$ : Equation 17

$$\begin{aligned} \text{PhaseMargin} = & 90^\circ - \arctan(2\pi f_c R_O C_O) \times \frac{180^\circ}{\pi} + \arctan(2\pi f_c R_{COMP} C_{COMP}) \times \frac{180^\circ}{\pi} - \arctan(2\pi f_c R_{COMP} C_{O\_EA}) \times \frac{180^\circ}{\pi} \\ & - \arctan\left(\frac{2\pi f_c [V_{Se}f_{SW}L + (0.5V_{IN} - V_O)R_i]}{V_{IN}R_i f_{SW}}\right) \times \frac{180^\circ}{\pi} + \arctan(2\pi f_c R_{ESR} C_O) \times \frac{180^\circ}{\pi} \end{aligned} \quad (17)$$

## 3 Inductor and Output Capacitor Design

In this section, the inductor and output capacitor is designed in a practical application using TPS92200D1/D2. The loop response is considered during the process. Table 1 lists the design specifications.

**Table 1. Design Example Specification**

$V_{IN}$ (V)	$V_O$ (V)	$I_O$ (A)	$I_{O\_min}$ (A)	$f_{SW}$ (kHz)	OUTPUT RIPPLE (mV)	$V_{REF}$ (V)
8 V to 16 V, typical 12 V	3.6 (2 IR-LED)	1.0	0.1	1000	< 30	1.2

### 3.1 Inductor Design

Equation 18 calculates the value of the output conductor.  $K_{IND}$  is a coefficient that represents the amount of inductor ripple current relative to the maximum output current of the device (For TPS92200D1/D2, the maximum output current  $I_{O\_max}$  is 1.5 A). A reasonable value of  $K_{IND}$  is 0.2 – 0.4. Since the ripple current increases with the input voltage, the maximum input voltage is used to calculate the minimum inductance  $L_{MIN}$ , while  $K_{IND} = 0.2$  is selected. The maximum inductor value is calculated to be 4.65  $\mu$ H. Choose the nearest standard inductor:  $L = 4.7 \mu$ H.

$$L_{max} = \frac{V_{IN\_max} - V_O}{I_{O\_max} \times K_{IND}} \times \frac{V_O}{V_{IN\_max} \times f_{SW}} \quad (18)$$

From Equation 13, the maximum inductor value is calculated to get enough phase margin. Three times margin is suggested and the limit is calculate in Equation 19 with the TPS92200D1/D2 internal parameter. If you assume the target crossing over frequency  $f_c$  is about 20 kHz, then the result is  $L < 60 \mu$ H at the minimum  $V_{IN}$ . The selected 4.7- $\mu$ H inductor meets the requirement.

$$L < \frac{1}{3} \left[ \frac{V_{IN}}{2\pi f_c \times 0.441} + \frac{(V_O - 0.5V_{IN})}{f_{SW} \times 0.441} \right] \quad (19)$$

The TPS92200D1/D2 is protected from overcurrent conditions with the cycle-by-cycle current limit. To prevent inductor saturation in case of short circuit conditions, the inductor saturation current must be greater than the device maximum peak current limit, which is 3.3 A (typical) for the TPS92200D1/D2.

### 3.2 Output Capacitor Design

The output capacitor is designed based on output ripple and loop response. The output voltage ripple is composed of two parts. One is caused by the inductor current ripple going through the ESR of the output capacitor, see Equation 20. The other is caused by the inductor current ripple charging and discharging the output capacitor, see Equation 21. The target output ripple is 30 mV, so  $\Delta V_{O\_ESR} < 30$  mV and  $\Delta V_{O\_C} < 30$  mV, then  $R_{ESR} < 125$  m $\Omega$  and  $C_O > 0.91 \mu$ F.

$$\Delta V_{O\_ESR} = I_O \times K_{IND} \times R_{ESR} \quad (20)$$

$$\Delta V_{O\_C} = \frac{I_O \times K_{IND}}{8 \times f_{SW} \times C_O} \quad (21)$$

From Equation 14, the maximum ESR value is calculated to get a reasonable crossover frequency and enough phase margin. If you assume the target crossing over frequency  $f_c$  is about 20 kHz, then the result is  $R_{ESR} \ll 796$  m $\Omega$ . Three times the margin is suggested and the result is  $R_{ESR} < 265$  m $\Omega$ .

Output capacitor value determines loop response in internally compensated PCM buck converters, as Equation 16 and Equation 17. With TPS92200D1/D2 internal parameter, the calculation equation is as in Equation 22 and Equation 23. The target  $f_c$  is about 20 kHz, so  $C_O$  is about 12.4  $\mu$ F. One 10- $\mu$ F, 16-V ceramic capacitor with 2-m $\Omega$  ESR is used:  $C_O = 10 \mu$ F,  $R_{ESR} = 2$  m $\Omega$ . The crossover frequency is  $f_c = 20.8$  kHz and the phase margin is calculated as 114.6 $^\circ$  at  $V_{IN} = 12$  V,  $I_O = 1.0$  A.

$$f_c = \frac{(13.638R_{FB} - 1) + \sqrt{(1 - 13.638R_{FB})^2 + 2727272R_{FB}R_O C_O}}{4\pi R_O C_O} \quad (22)$$

$$\begin{aligned} \text{PhaseMargin} = & 90^\circ - \arctan(2\pi f_c R_O C_O) \times \frac{180^\circ}{\pi} + \arctan(2\pi f_c \times 20\mu) \times \frac{180^\circ}{\pi} - \arctan(2\pi f_c \times 0.01115\mu) \\ & \times \frac{180^\circ}{\pi} - \arctan\left(\frac{2\pi f_c (f_{SW} L \times 0.441 + 0.5V_{IN} - V_O)}{V_{IN} f_{SW}}\right) \times \frac{180^\circ}{\pi} + \arctan(2\pi f_c R_{ESR} C_O) \times \frac{180^\circ}{\pi} \end{aligned} \quad (23)$$

### 3.3 Simulation and Bench Verification

Figure 7 shows the schematic for bench verification. SIMPLIS is used to simulate the loop response as shown in Figure 8. Figure 9 and Figure 10 are the loop responses from the SIMPLIS simulation and bench test under  $V_{IN} = 12$  V,  $V_O = 3.6$  V,  $I_O = 1.5$  A, and  $f_{SW} = 1.0$  MHz. Table 2 compares the calculation results, simulation results, and bench measurement at different  $V_{IN}$ . It can be seen that the proposed model in this application report is accurate.

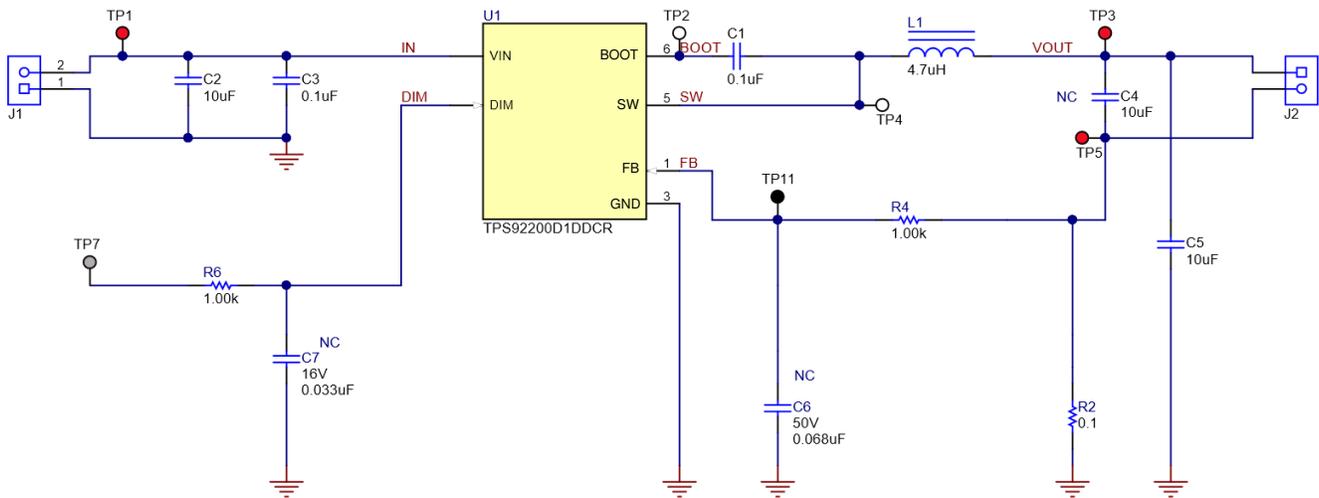


Figure 7. TPS92200D1 Design With 2 IRLED, 1.0-A Output

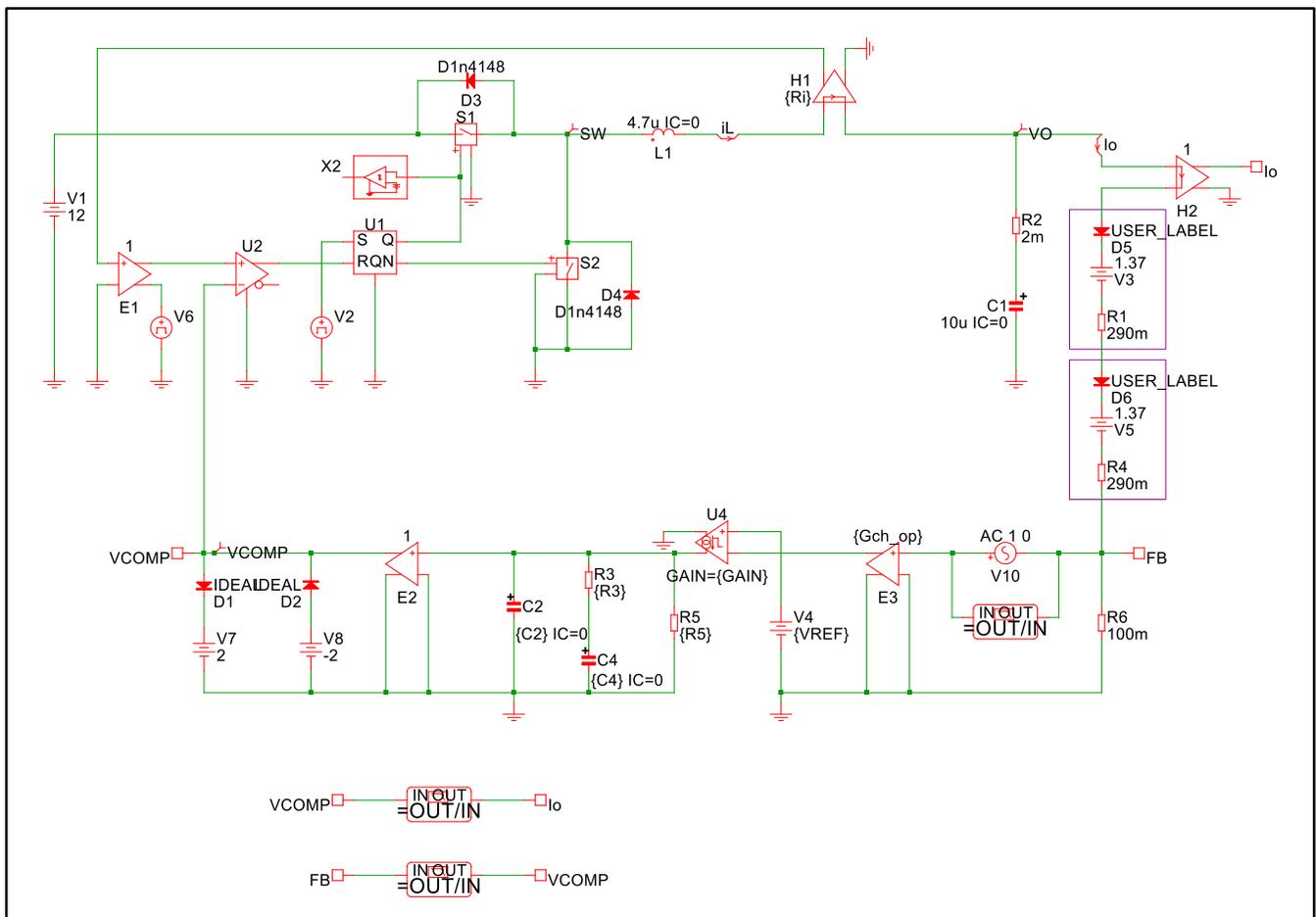


Figure 8. Schematic of a Simplified SIMPLIS Model

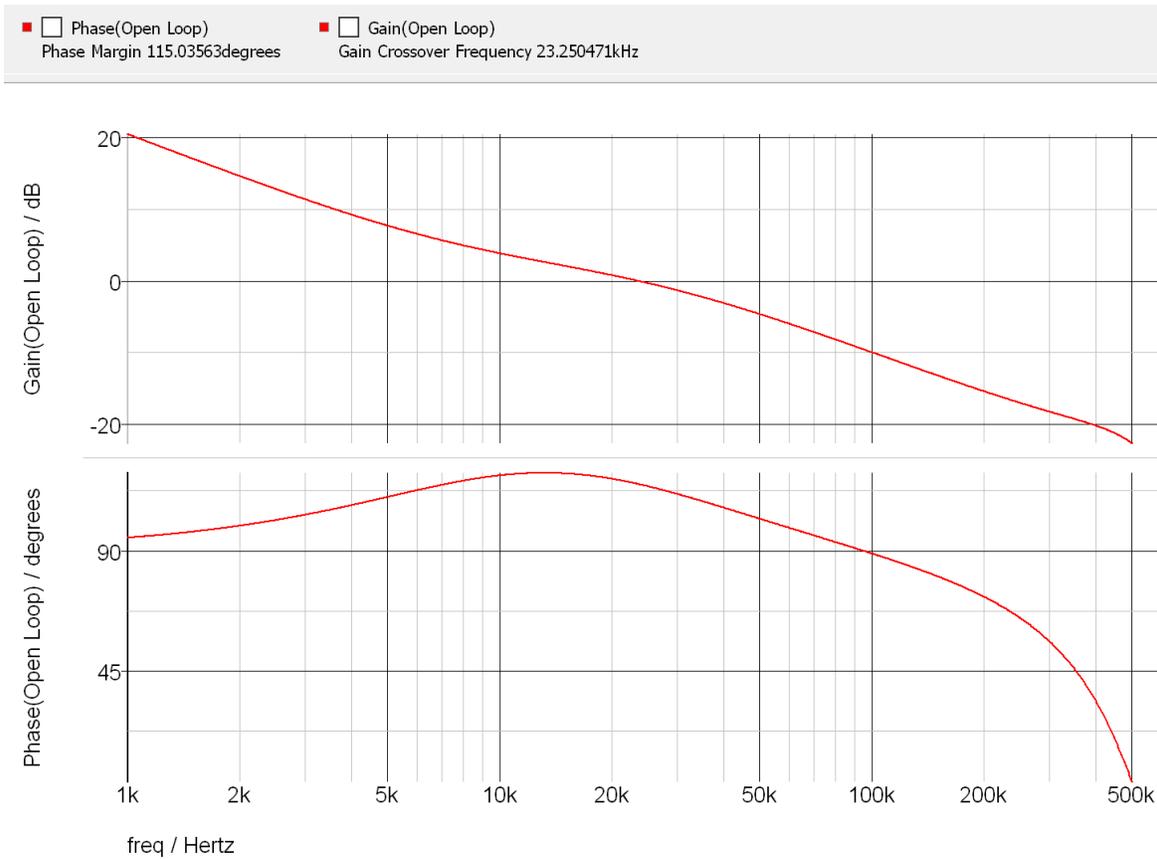


Figure 9. Bode Plot Simulation Result at  $V_{IN} = 12\text{ V}$ ,  $I_O = 1\text{ A}$

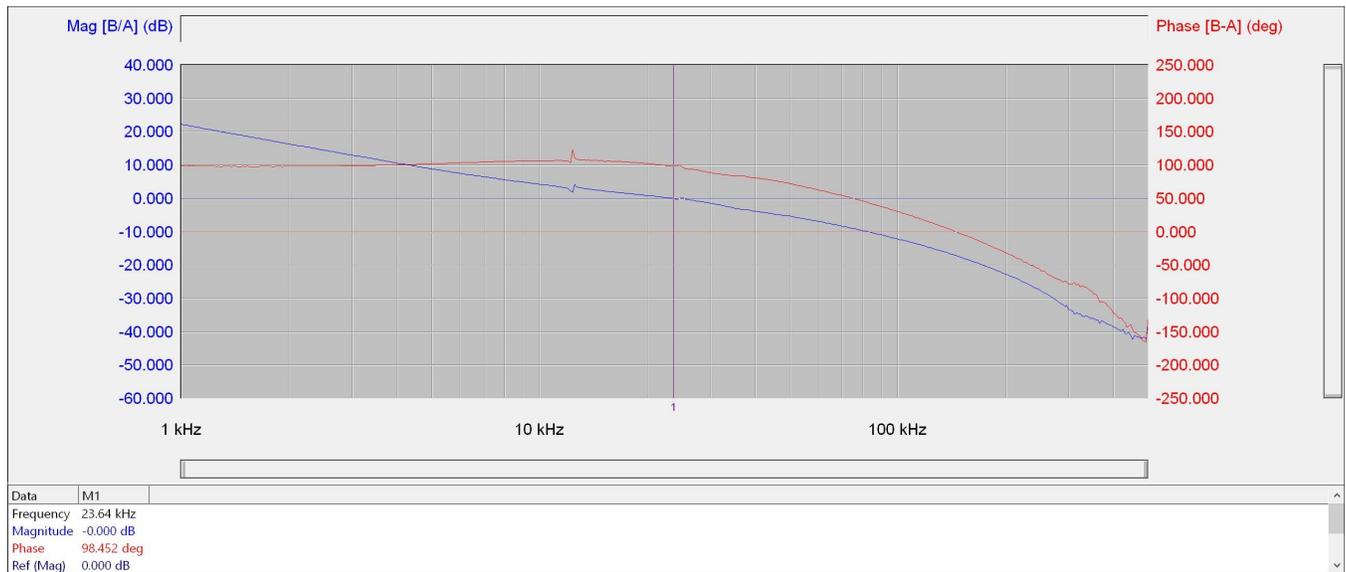


Figure 10. Bode Plot Test Result at  $V_{IN} = 12\text{ V}$ ,  $I_O = 1\text{ A}$

**Table 2. Calculation, Simulation, and Bench Measurement Results Comparison**

$V_{IN}$ (V)	$I_o$ (A)	LED Load	CALCULATION RESULTS		SIMULATION RESULTS		BENCH MEASUREMENT	
			$f_c$ (kHz)	PHASE MARGIN (°)	$f_c$ (kHz)	PHASE MARGIN (°)	$f_c$ (kHz)	PHASE MARGIN (°)
12	1	2 IR LED	20.8	114.6	23.25	115.0	23.64	98.5
12	1	4 IR LED	14.2	100.5	15.25	101.46	12.69	101.4
24	1	6 IR LED	11.8	93	12.55	97.2	12.0	90.1
24	1	4 White LED	20.91	117.2	21.39	113.1	23.26	100.7
24	1	6 White LED	13.6	101.24	16.94	104.7	17.45	94.7

## 4 Summary

For an internally-compensated, Peak Current Mode buck LED driver, the loop response is very different to the traditional buck converter due to the different load connection and character [4][5]. It should pay more attention to choose the inductor and output capacitor. This application report analyzes the whole loop of the PCM buck LED driver, simplifies the inside current loop as a single pole, provides the constraint to ensure loop stability, and gives out an equation to calculate bandwidth and phase margin. The inductor and output capacitor is designed step-by-step considering loop response. The theory is verified by simulation and bench measurement results.

## 5 References

1. Texas Instruments, [TPS92200 4-V to 30-V, 1.5A Synchronous Buck LED Driver With Flexible Dimming Options Data Sheet](#)
2. R.B. Ridley, A New Small-Signal Model for Current-Mode Control, PhD Dissertation, Virginia Polytechnic Institute and State University, November, 1990.
3. Texas Instruments, [TPS65270 Loop Compensation Design Consideration Application Report](#)
4. Texas Instruments, [How to Evaluate the Maximum Inductor in an Internal Compensation PCM Buck Converter Application Report](#)
5. Texas Instruments, [Loop Response Consideration in Peak Current Mode Buck Converter Design Application Report](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated