

# Application Report

## Passing CISPR-25 Radiated and Conduction Emissions Using the TPS65033x-Q1



Gerard Copeland

Power Products

### ABSTRACT

This application report provides a summary of the CISPR-25 Conducted and Radiated Emissions test results using the TPS650330-Q1 Power Management Integrated Circuit (PMIC) for automotive camera applications. This device is capable of passing CISPR-25 and other automotive electromagnetic-compatibility (EMC) test specifications. Similar results can be achieved using other devices in the TPS65033x-Q1 family. Due to an advanced spread spectrum clocking (SSC) feature, these devices can pass EMC tests without needing a fully-optimized layout, allowing for more flexible component placement and routing as required by the camera application.

### Table of Contents

1 Introduction.....	2
2 Spread Spectrum.....	2
3 Schematics and Printed Circuit Board (PCB) Description.....	3
4 Design Considerations.....	6
5 Summary.....	8
6 Conducted and Radiated Emission Average and Peak Plots.....	9
7 References.....	13
8 Revision History.....	14

### List of Figures

Figure 2-1. Spread Bands of Harmonics in Modulated Square Signals 2 .....	2
Figure 2-2. TPS650330-Q1 SSC Conducted Emission Comparison.....	3
Figure 3-1. CISPR-25 EMC Test Setup.....	3
Figure 3-2. DUT Schematics.....	4
Figure 3-3. Printed Circuit Board Top Layer.....	6
Figure 3-4. Printed Circuit Board Layer 2 (Ground Plane).....	6
Figure 3-5. Printed Circuit Board Layer 3.....	6
Figure 3-6. Printed Circuit Board Layer 4.....	6
Figure 3-7. Printed Circuit Board Layer 5 (Ground Plane).....	6
Figure 3-8. Printed Circuit Board Layer 6.....	6
Figure 3-9. Printed Circuit Board Layer 7 (Ground Plane).....	6
Figure 3-10. Printed Circuit Board Bottom Layer.....	6
Figure 4-1. Bottom Layer (PMIC Layer)- Zoom.....	7
Figure 4-2. Top Layer - Zoom.....	8
Figure 6-1. Conducted Emissions 0.15 MHz to 108 MHz.....	9
Figure 6-2. Radiated Emissions - Rod Antenna 0.15 MHz to 30 MHz.....	10
Figure 6-3. Radiated Emissions - Bicon Horizontal Antenna 30 MHz to 200 MHz.....	10
Figure 6-4. Radiated Emissions - Bicon Vertical Antenna 30 MHz to 200 MHz.....	11
Figure 6-5. Radiated Emissions - Logarithmic Horizontal Antenna 200 MHz to 1000 MHz.....	11
Figure 6-6. Radiated Emissions - Logarithmic Vertical Antenna 200 MHz to 1000 MHz.....	12

### List of Tables

Table 3-1. Bill of Materials.....	4
-----------------------------------	---

Table 5-1. Emissions Test Operating Conditions..... 8

## Trademarks

All other trademarks are the property of their respective owners.


## 1 Introduction

This application report illustrates the EMI/EMC performance of the TPS650330-Q1 and relevant circuits in automotive applications using example schematics and layout design. With this example, the TPS650330-Q1 and associated components pass the CISPR-25<sup>1</sup> conducted emission in the 0.15 MHz to 108 MHz frequency range, and radiated emission in the 0.15 MHz to 1000 MHz frequency range.

## 2 Spread Spectrum

The TPS650330-Q1, TPS650331-Q1, TPS650332-Q1, and TPS650333-Q1 are a family of PMICs for camera applications. Each device includes three step-down (buck) converters and one low dropout (LDO) regulator. The three buck converters are capable of spread spectrum clocking (SSC), a feature that modulates the switching frequency of each converter to spread the power that can cause EMI. This internal modulation spreads the operating frequency from 2.0 MHz to 2.5 MHz with a center frequency of 2.25 MHz and can be enabled or disabled with a single register write through I2C communication.

The goal of spread spectrum architecture is to spread out emitted RF energy over a larger frequency range. Spreading the operating frequency of the buck converters results in a more continuous power spectra that is lower in peak amplitude, as shown in Figure 2-1. This peak reduction is possible because the time integral of the curve (the EMI energy emitted by the circuit) remains constant whether spread spectrum is enabled or disabled.

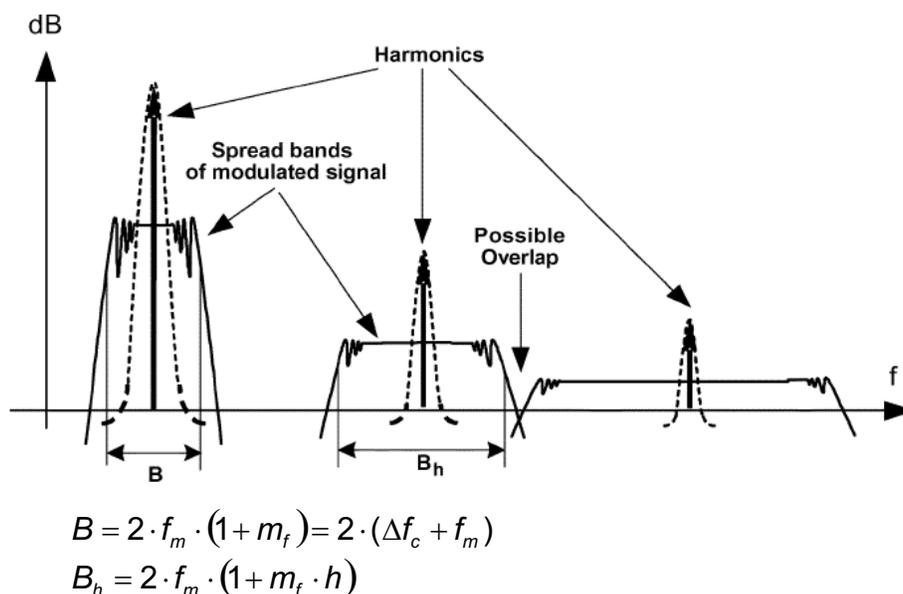

**Figure 2-1. Spread Bands of Harmonics in Modulated Square Signals<sup>2</sup>**

Figure 2-2 compares the conducted emission performance with SSC enabled and disabled using the TPS650330-Q1 and the example layout discussed in this application report.

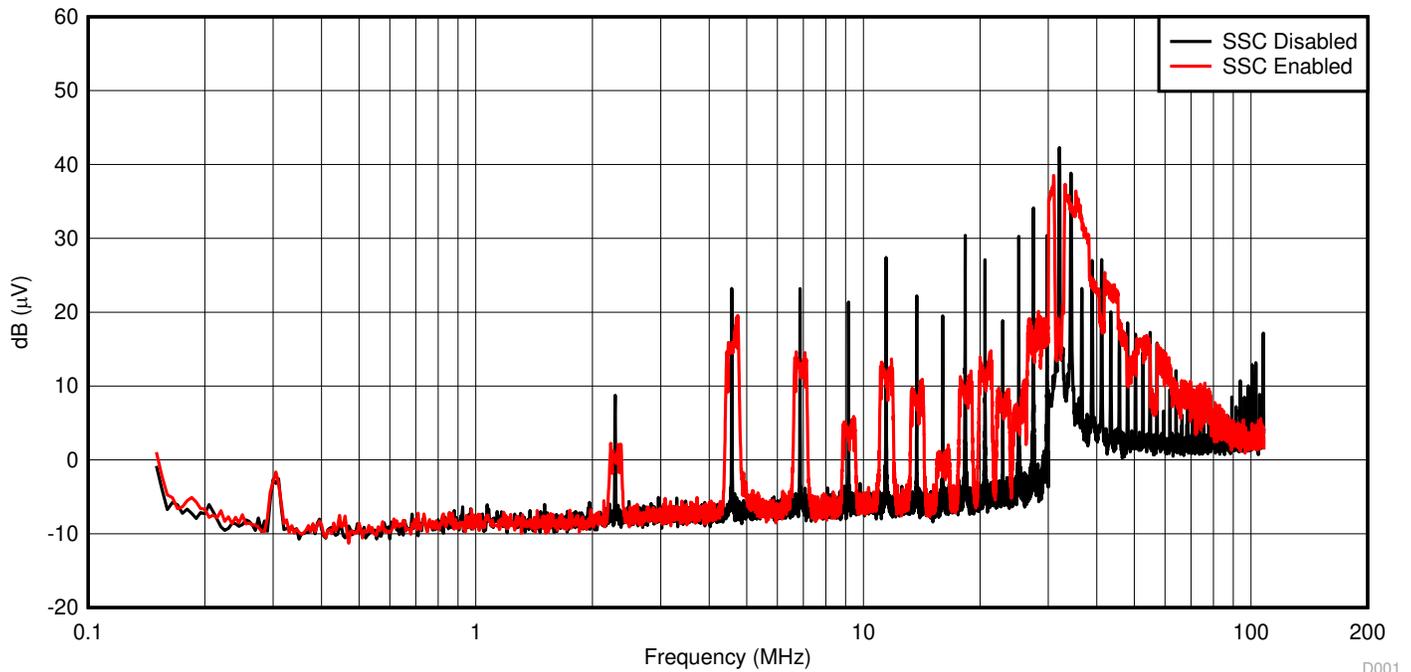


Figure 2-2. TPS650330-Q1 SSC Conducted Emission Comparison

### 3 Schematics and Printed Circuit Board (PCB) Description

This layout is derived from a compact camera module reference design. All non-power components have been removed from the original design, and the remaining power solution was tested according to the CISPR-25 automotive specification. A power over coax (POC) filter is included on both ends of the harness (FPD-Link coax cable) to replicate the expected EMI in a typical automotive camera application. The schematic and layout for the POC filter on the receiver side are taken from the [Automotive Camera PMIC Power Supply Reference Design with Power Over Coax Filter](#) reference design. The schematic and layout for the POC filter on the DUT-side is shown in Figure 3-2. As intended for a camera module reference design, the layout balances the tradeoffs between PCB area and EMI performance. For example, some components for the low-voltage buck converters are located on the layer opposite of the PMIC to minimize the total area occupied by the power solution. These are less critical for EMI performance compared to the mid-voltage buck converter.

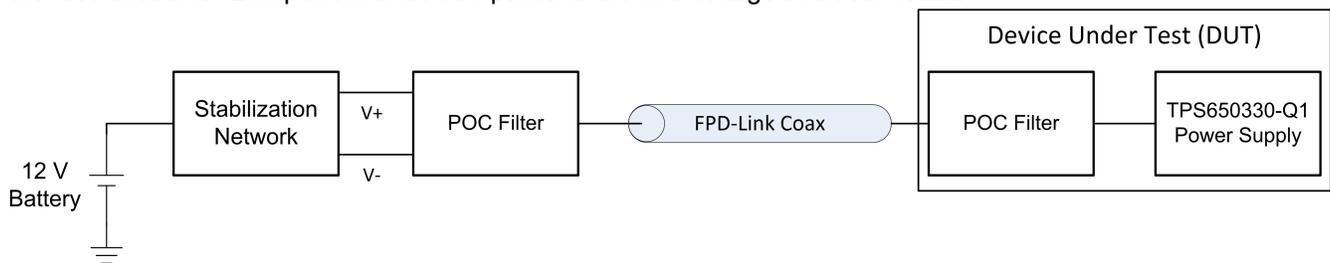


Figure 3-1. CISPR-25 EMC Test Setup

### 3.1 Schematics

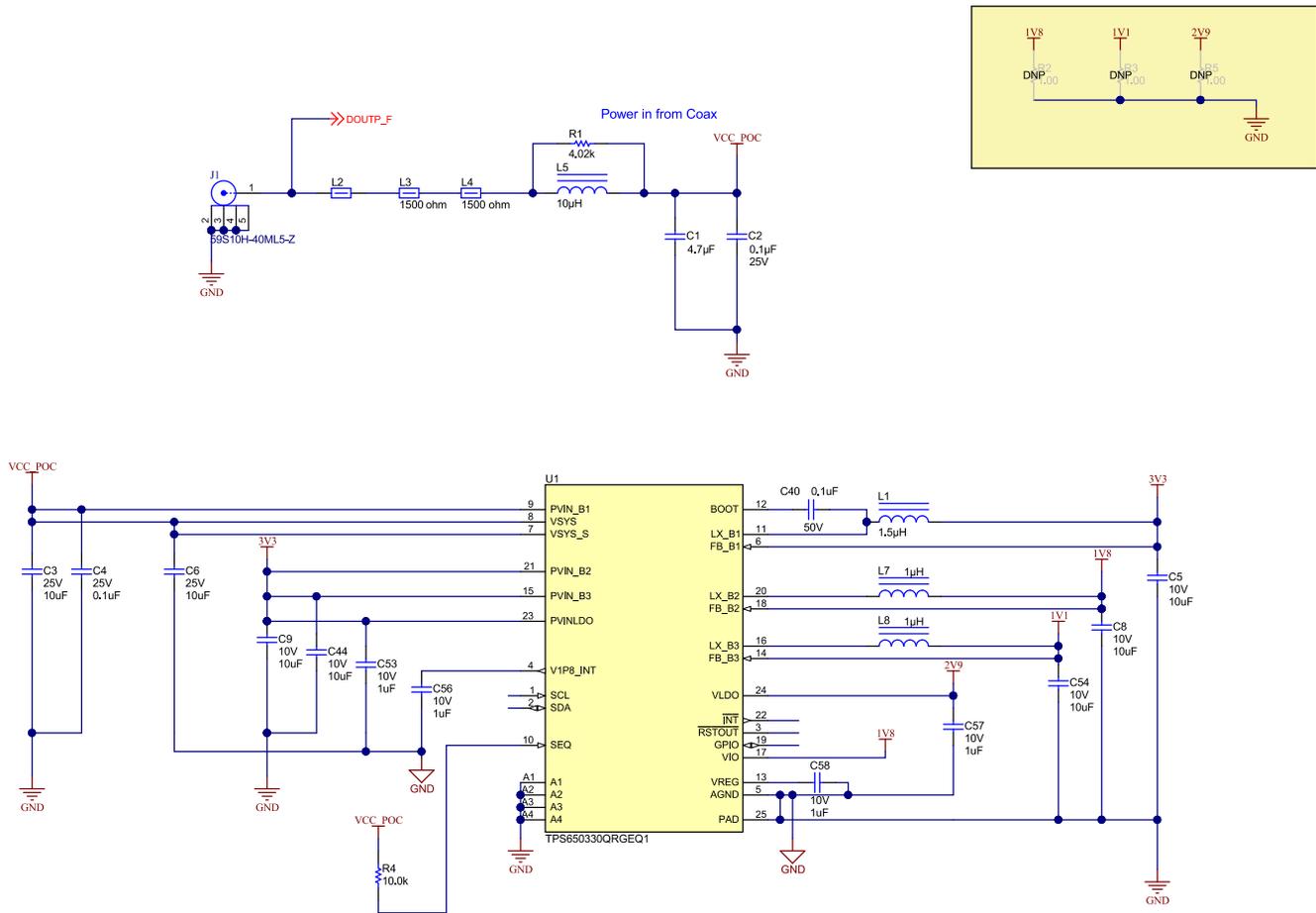


Figure 3-2. DUT Schematics


Table 3-1. Bill of Materials

ITEM	DESIGNATOR	QUANTITY	PART NUMBER	MANUFACTURER	DESCRIPTION
1	!PCB1	1	TIDA-020006	Any	Printed Circuit Board
2	C1	1	CGA4J1X7R1E475M125AC	TDK Corporation	CAP, CERM, 4.7 $\mu$ F, 25 V, $\pm$ 20%, X7R, 0805
3	C2	1	C1005X7R1E104K050BB	TDK Corporation	CAP, CERM, 0.1 $\mu$ F, 25 V, $\pm$ 10%, X7R, 0402
4	C3, C6	2	GRM21BZ71E106KE15L	MuRata	CAP, CERM, 10 $\mu$ F, 25 V, $\pm$ 10%, X7R, 0805
5	C4	1	GRM155R71E104KE14D	MuRata	CAP, CERM, 0.1 $\mu$ F, 25 V, $\pm$ 10%, X7R, 0402
6	C5, C8, C9, C44, C54	5	GRM188Z71A106MA73D	MuRata	CAP, CERM, 10 $\mu$ F, 10 V, $\pm$ 20%, X7R, 0603
7	C40	1	CGA2B3X7R1H104M050BB	TDK	CAP, CERM, 0.1 $\mu$ F, 50 V, $\pm$ 20%, X7R, AEC-Q200 Grade 1, 0402


**Table 3-1. Bill of Materials (continued)**

ITEM	DESIGNATOR	QUANTITY	PART NUMBER	MANUFACTURER	DESCRIPTION
8	C53, C56, C57, C58	4	885012206026	Wurth Elektronik	CAP, CERM, 1 $\mu$ F, 10 V, $\pm$ 10%, X7R, 0603
9	H1	1	CMT821	Sunex	Lens holder, M12x0.5, 11.2, centered
10	J1	1	59S10H-40ML5-Z	Rosenberger	Connector, HF, 50 $\Omega$ , TH
11	L1	1	TFM201610ALMA1R5MTAA	TDK	Inductor, Shielded, Metal Composite, 1.5 $\mu$ H, 2.3 A, 0.11 $\Omega$ , AEC-Q200 Grade 0, SMD
12	L2, L3, L4	3	BLM18HE152SN1D	MuRata	Ferrite Bead, 1500 $\Omega$ at 100 MHz, 0.5 A, 0603
13	L5	1	LQH3NPZ100MJRL	MuRata	Inductor, Wirewound, Ferrite, 10 $\mu$ H, 0.81 A, 0.288 $\Omega$ , AEC-Q200 Grade 1, SMD
14	L7, L8	2	TFM201610ALMA1R0MTAA	TDK	Inductor, Shielded, Metal Composite, 1 $\mu$ H, 3.1 A, 0.06 $\Omega$ , AEC-Q200 Grade 0, SMD
15	R1	1	CRCW06034K02FKEA	Vishay-Dale	RES, 4.02 k, 1%, 0.1 W, 0603
16	R4	1	RC0603FR-0710KL	Yageo	RES, 10.0 k, 1%, 0.1 W, 0603
17	U1	1	TPS650330QRGEQ1	Texas Instruments	Automotive Camera PMIC, RGE0024K (VQFN-24)
18	FID1, FID2, FID3, FID4	0	N/A	N/A	Fiducial mark. There is nothing to buy or mount.
19	R2, R3, R5	0	CRM2512-FX-1R00ELF	Bourns	RES, 1.00, 1%, 2 W, 6.3x3.1 mm


### 3.2 Board Layout

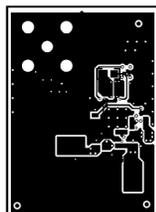


**Figure 3-3. Printed Circuit Board Top Layer**

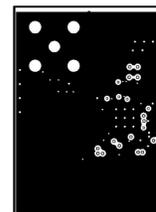


**Figure 3-4. Printed Circuit Board Layer 2 (Ground Plane)**

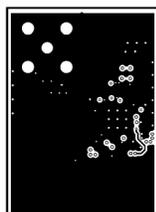


**Figure 3-5. Printed Circuit Board Layer 3**

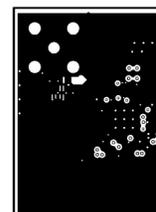


**Figure 3-6. Printed Circuit Board Layer 4**

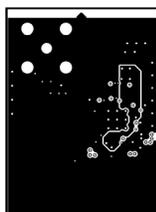


**Figure 3-7. Printed Circuit Board Layer 5 (Ground Plane)**

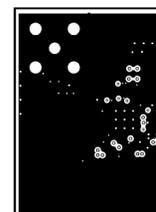

**Figure 3-8. Printed Circuit Board Layer 6**

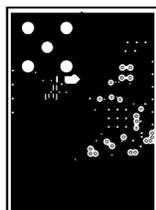

**Figure 3-9. Printed Circuit Board Layer 7 (Ground Plane)**

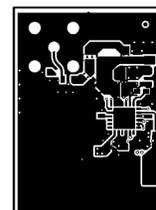

**Figure 3-10. Printed Circuit Board Bottom Layer**

### 4 Design Considerations

Automotive camera modules are typically as small as possible to support placement in remote regions of the vehicle. A designer may need to sacrifice some layout best practices in terms of conducted and radiated emissions in order to meet stringent size constraints. The SSC feature of the TPS650330-Q1 allows for a sub-optimal layout while still passing CISPR-25 emissions testing specifications.

Design considerations for this layout to reduce emissions include:

1. Minimize the loop area between the buck converter input capacitors and the thermal pad of the PMIC. Smaller decoupling capacitors are placed closer to the device pins.
2. Minimize the loop area between the input capacitor, output inductor, and output capacitor of each buck converter.

3. The mid-voltage buck converter (Buck 1) has the highest priority for external component placement on the PCB.
4. The input capacitors for the low-voltage buck converters (Buck 2 and Buck 3) have the next highest placement priority.
5. External components for the less EMI critical converter can be placed on the opposite side. In this case the less critical converter is Buck 2 because it has a higher output voltage (1.8 V).
6. Incorporate multiple solid ground planes with low impedance connections to the ground pours on the external component layers.

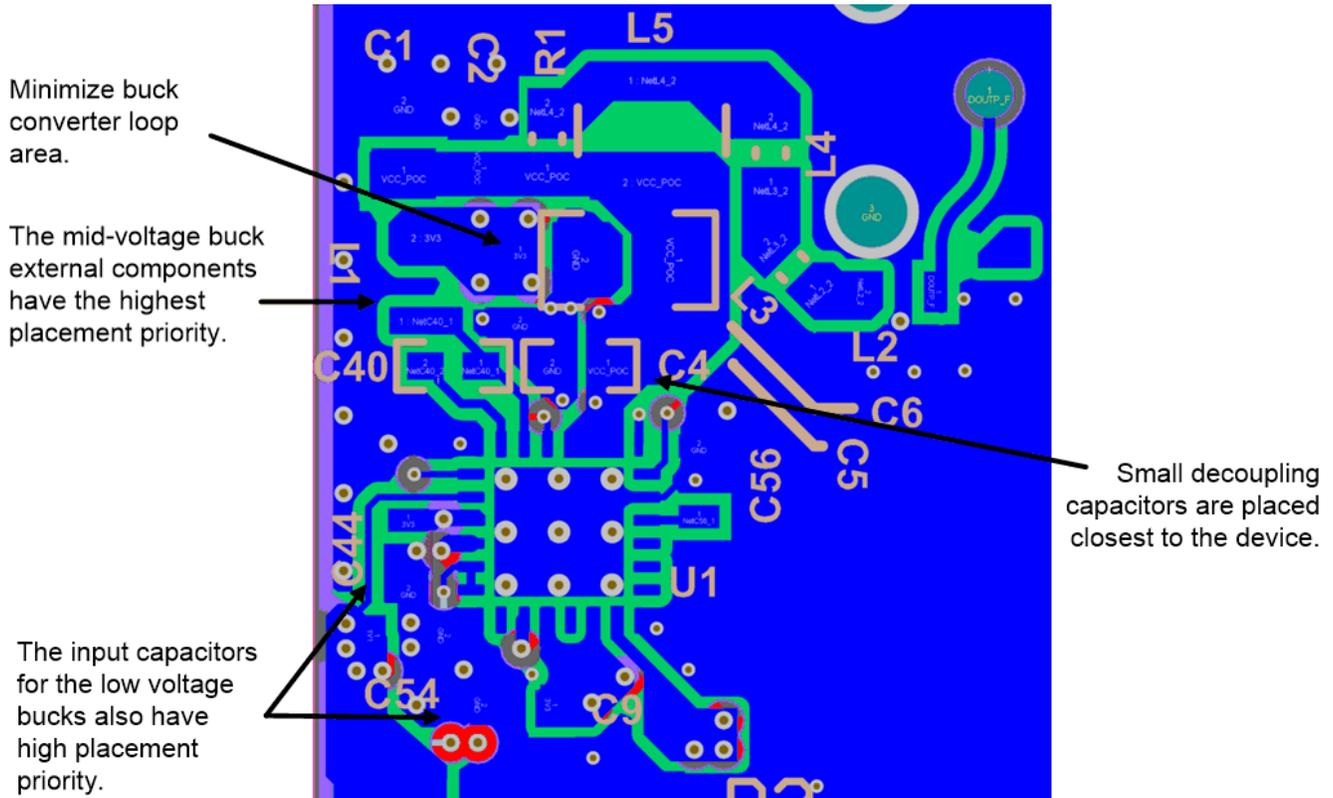


Figure 4-1. Bottom Layer (PMIC Layer)- Zoom

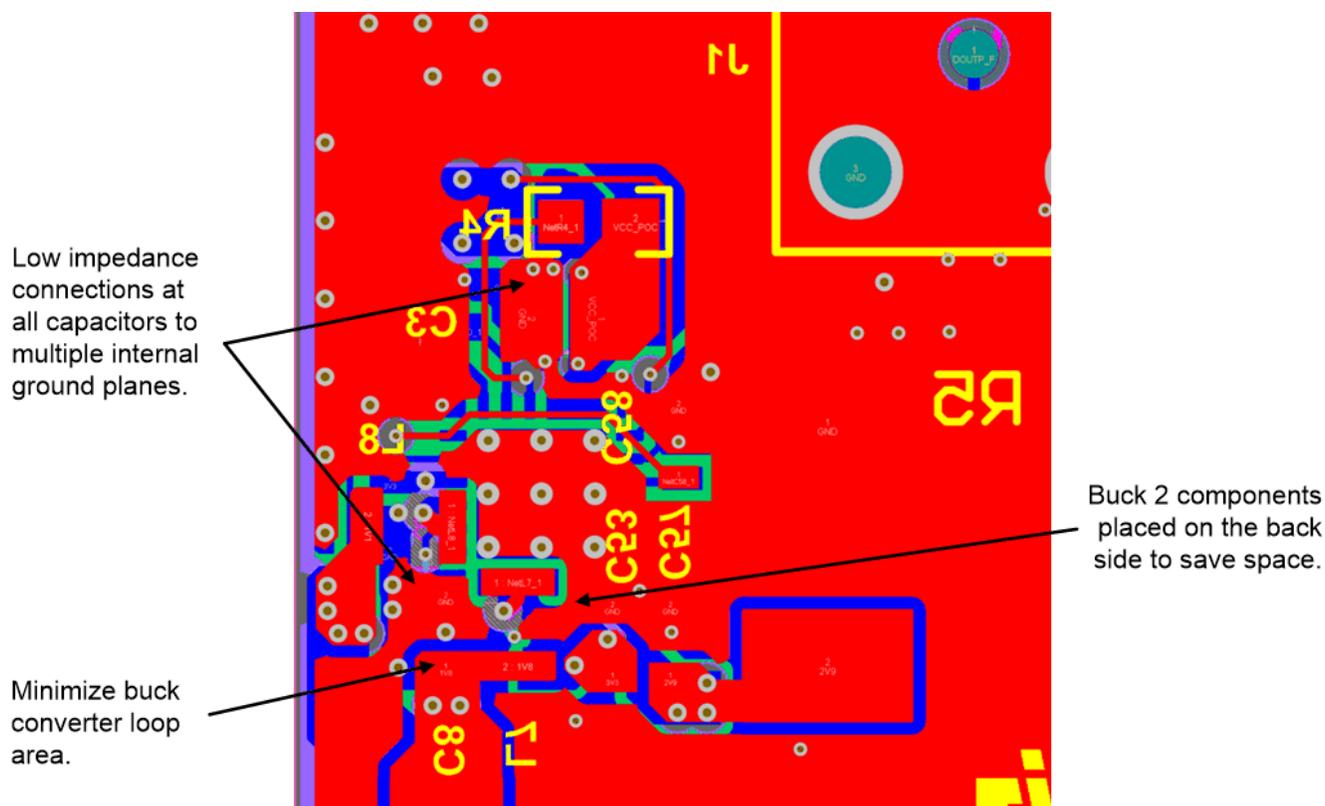


Figure 4-2. Top Layer - Zoom

## 5 Summary

The TPS65033x-Q1 device family passes the CISPR25 Class-5 Conducted and Radiated Emissions required for automotive applications. Passing results can be achieved using the integrated SSC feature combined with the design and layout considerations described in [Section 3](#) and [Section 4](#). The operating conditions are given in [Table 5-1](#).

Table 5-1. Emissions Test Operating Conditions


REGULATOR	OUTPUT VOLTAGE (V)	OUTPUT CURRENT (mA)
Buck 1	3.3	770 <sup>(1)</sup>
Buck 2	1.8	600
Buck 3	1.1	600
LDO	2.9	150

(1) The output current for Buck 1 is comprised of the input currents for Buck 2, Buck 3, and the LDO. There is no additional loading on the 3.3 V rail.

## 6 Conducted and Radiated Emission Average and Peak Plots

Red Trace - PK

Blue Trace - AVG

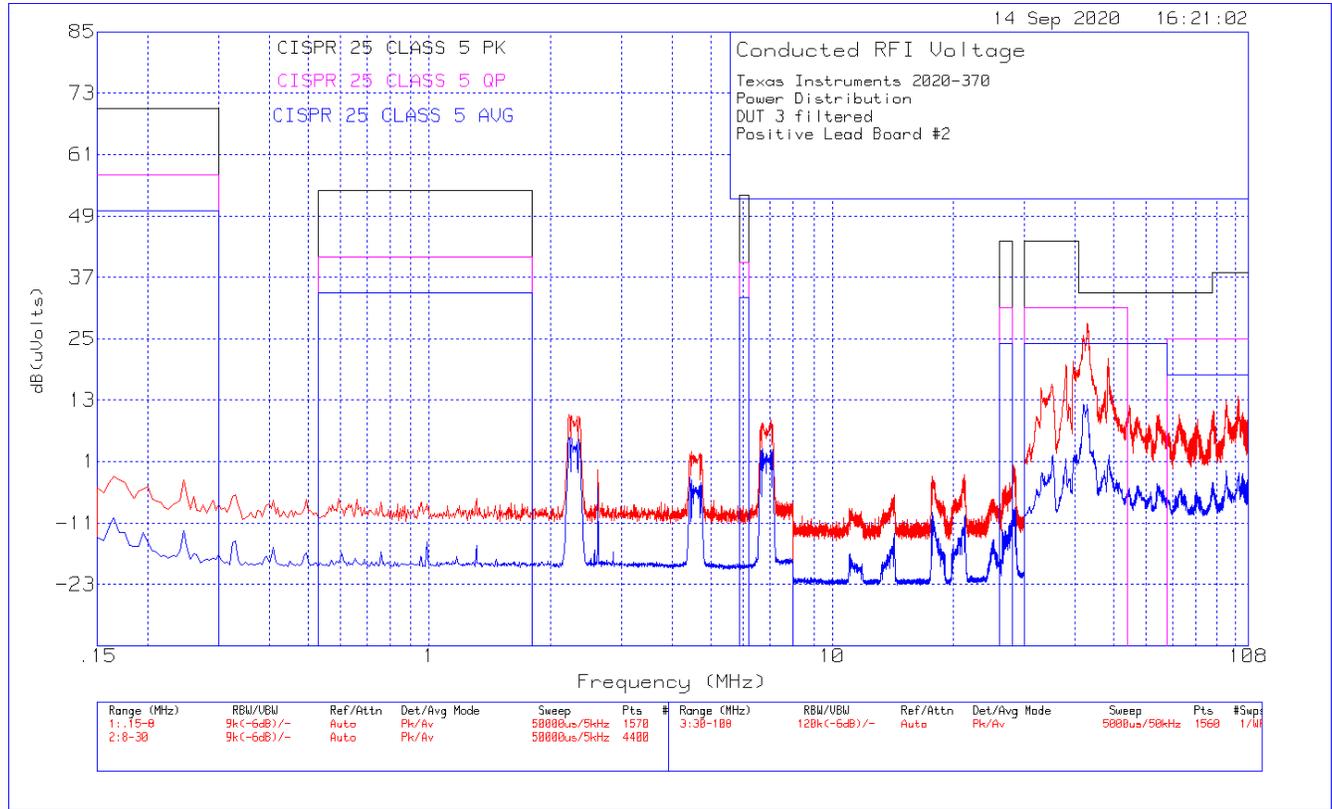

**Figure 6-1. Conducted Emissions 0.15 MHz to 108 MHz**

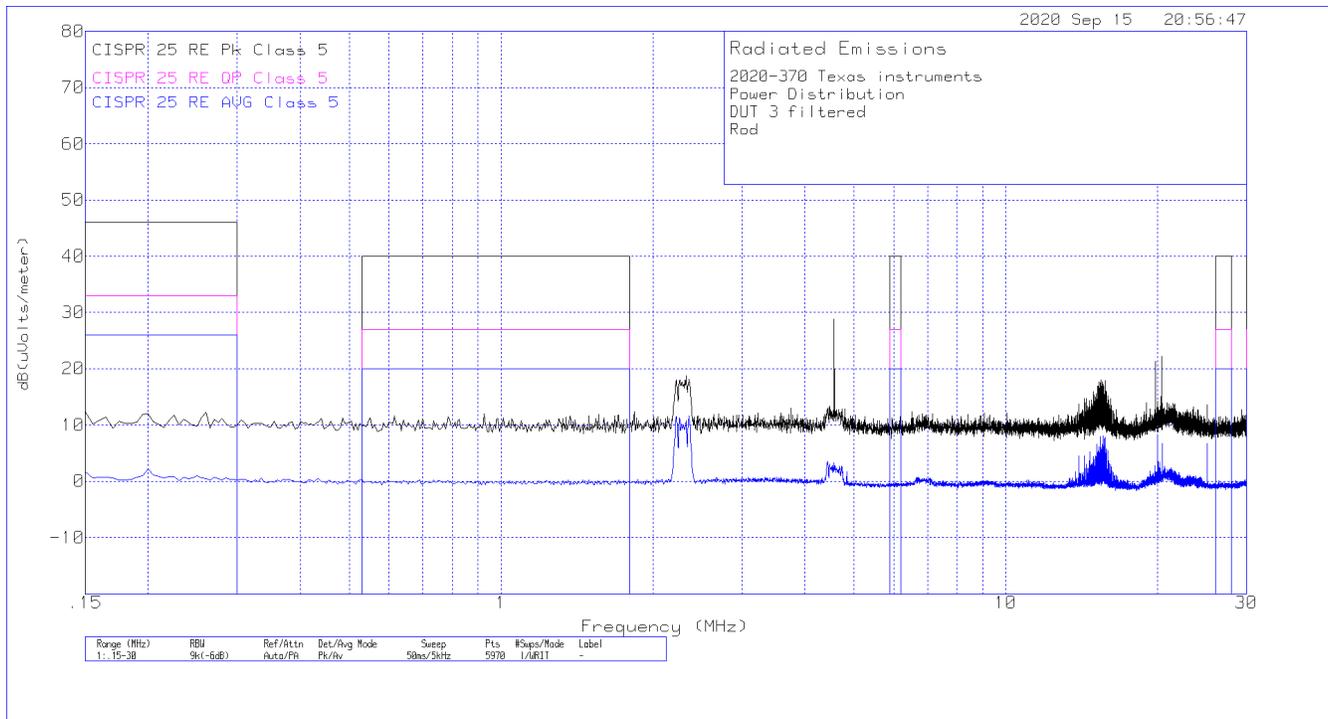


Figure 6-2. Radiated Emissions - Rod Antenna 0.15 MHz to 30 MHz



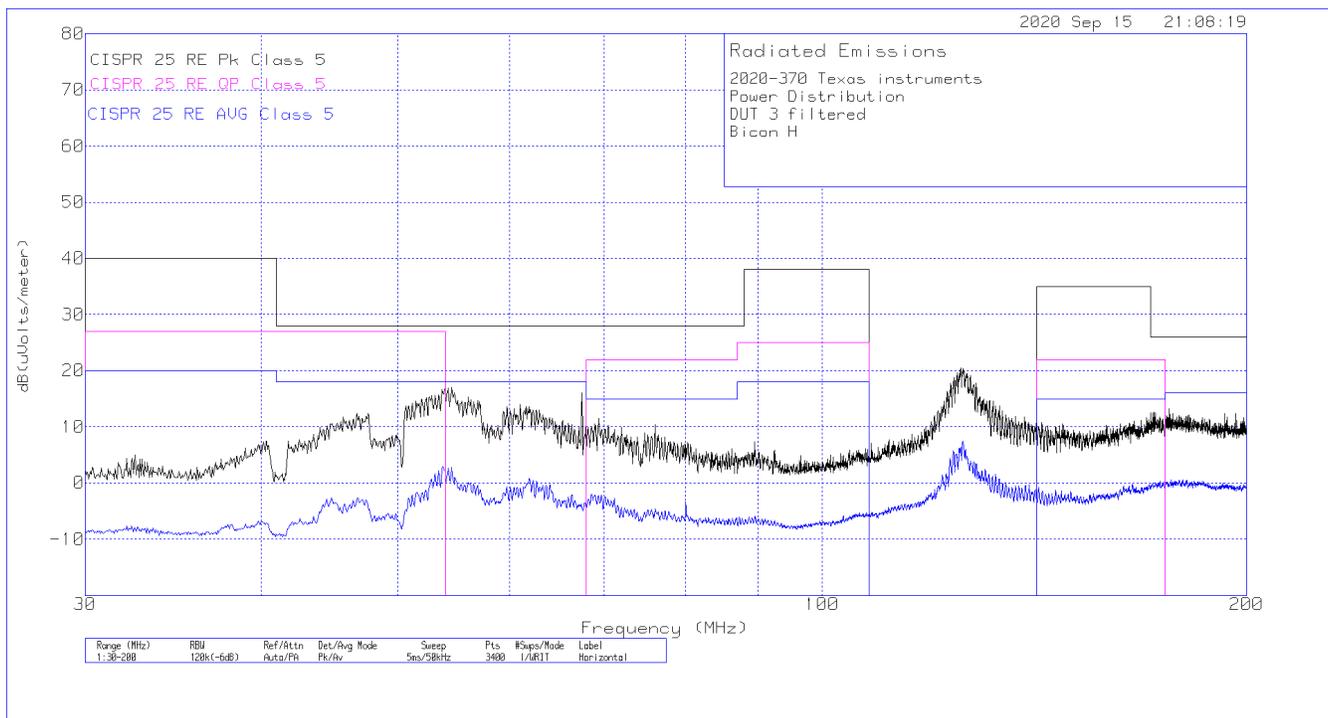



Figure 6-3. Radiated Emissions - Bicon Horizontal Antenna 30 MHz to 200 MHz

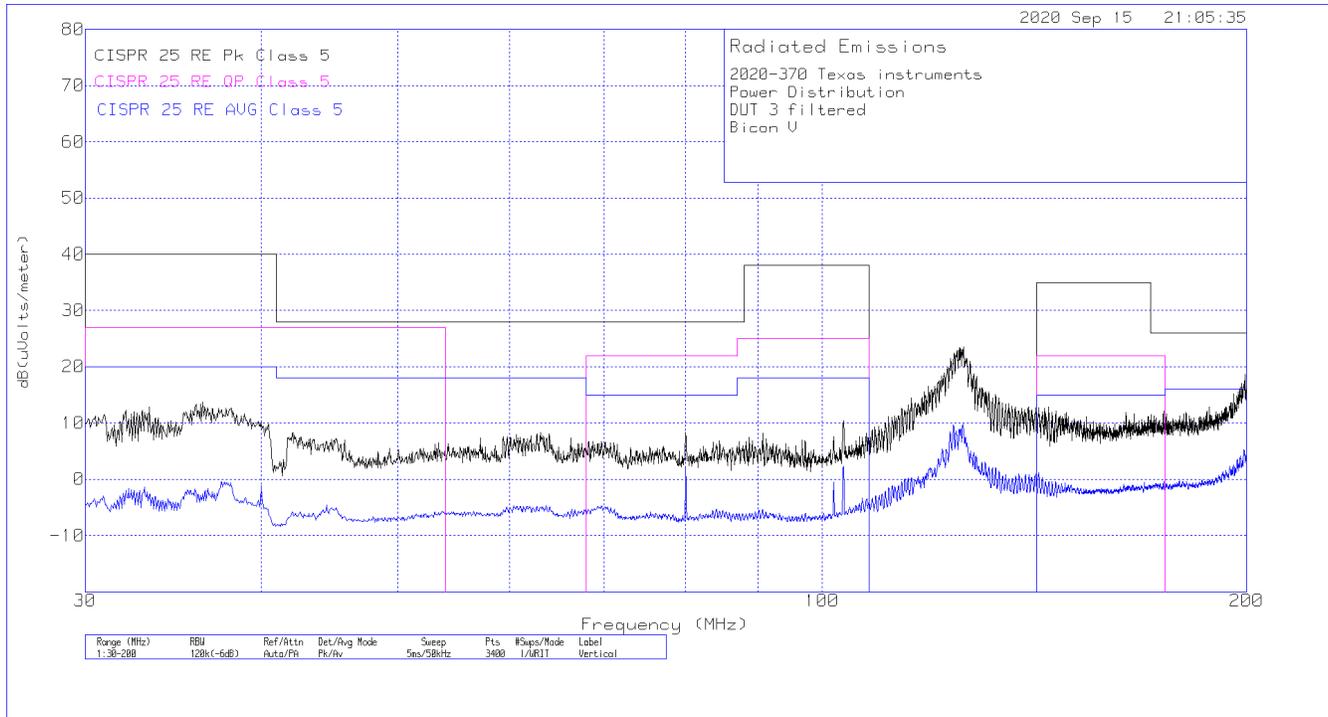

**Figure 6-4. Radiated Emissions - Bicon Vertical Antenna 30 MHz to 200 MHz**

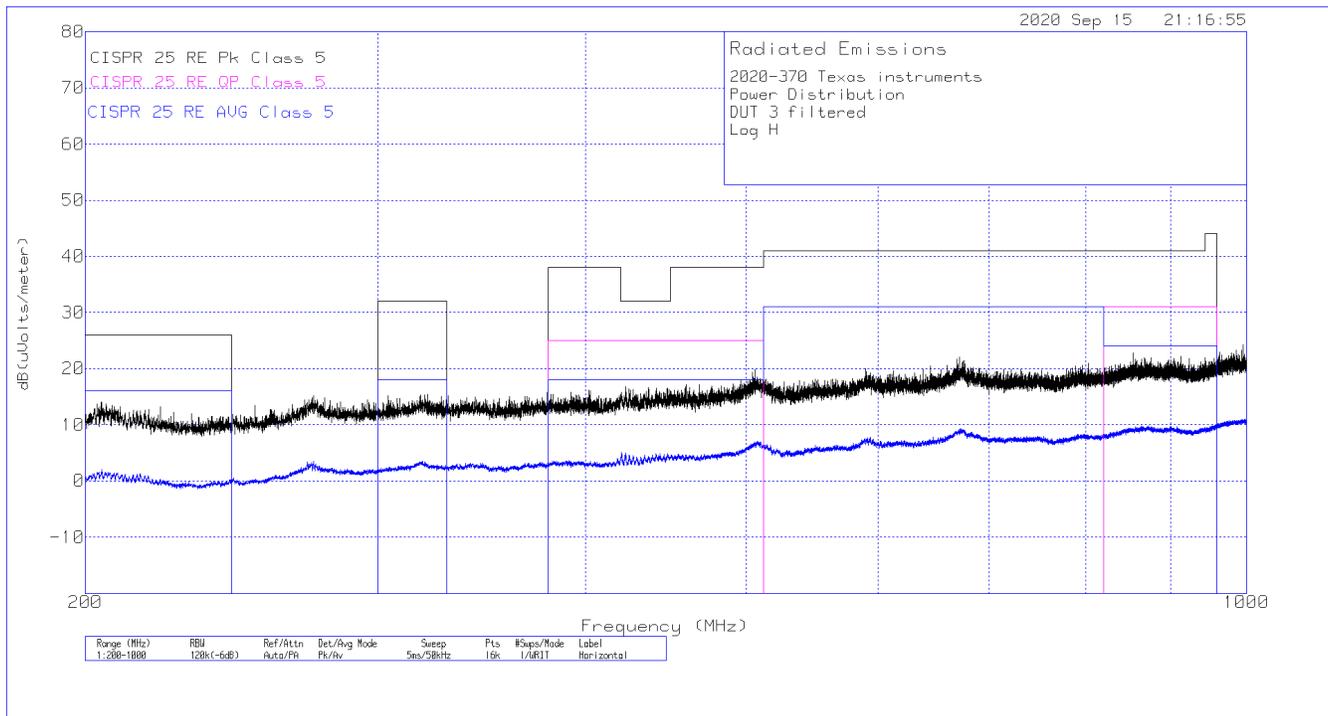

**Figure 6-5. Radiated Emissions - Logarithmic Horizontal Antenna 200 MHz to 1000 MHz**

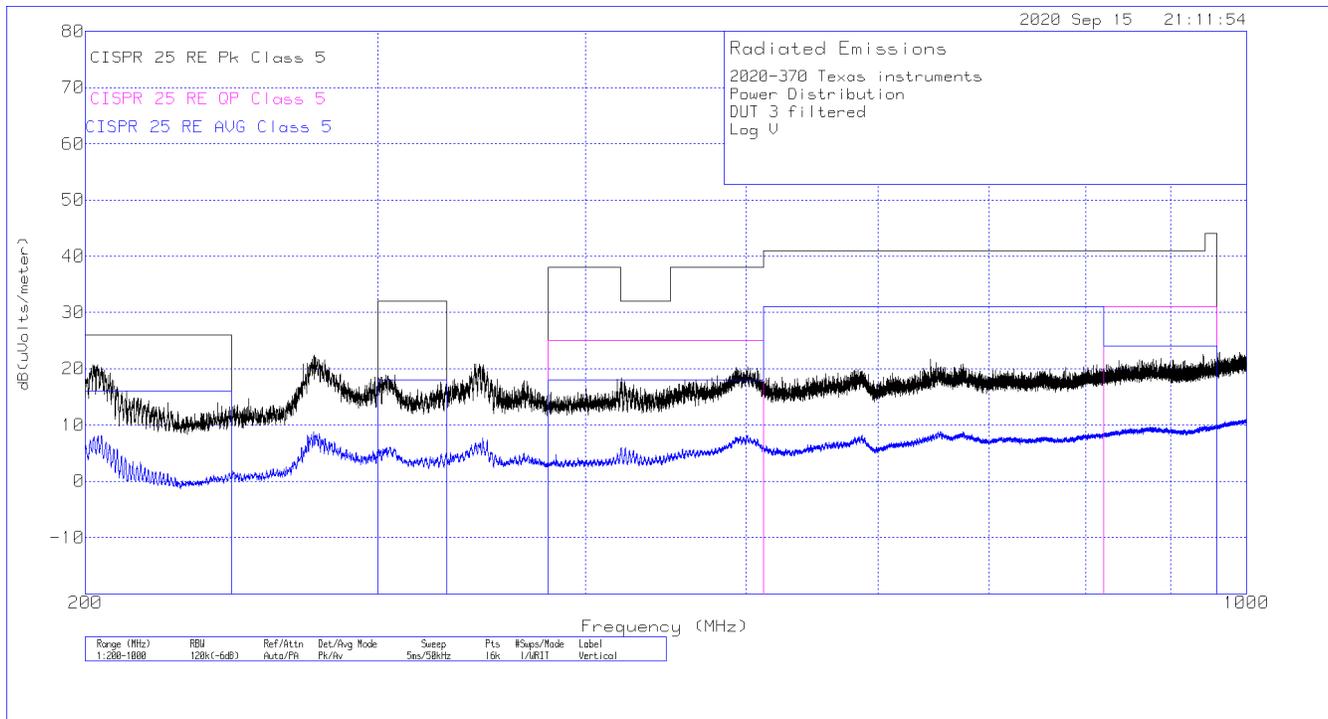

**Figure 6-6. Radiated Emissions - Logarithmic Vertical Antenna 200 MHz to 1000 MHz**

## 7 References

1. CISPR, CISPR 25:2016, fourth edition (or EN 55025:2017), "Vehicles, boats and internal combustion engines – Radio disturbance characteristics – Limits and methods of measurement for the protection of on-board receivers," October 27, 2016.
2. "EMI Reduction in Switched Power Converters Using Frequency Modulation Techniques," in IEEE TRANSACTIONS ON ELECTROMAGNETIC COMPATIBILITY, VOL. 4, NO. 3, AUGUST 2005, pp 569-576 by Josep Balcells, Alfonso Santolaria, Antonio Orlandi, David González, Javier Gago.

## 8 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Revision * (April 2020) to Revision A (October 2020)</b>	<b>Page</b>
• Updated the numbering format for tables, figures, and cross-references throughout the document.....	<a href="#">2</a>
• Updated <i>Schematics and Printed Circuit Board (PCB) Description</i> section.....	<a href="#">3</a>
• Updated the <i>Conducted and Radiated Emission Average and Peak Plots</i> section.....	<a href="#">9</a>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated