



# HIGH VOLTAGE SEMINAR

**MIKE O'LOUGHLIN**



HIGH VOLTAGE CONTROLLERS

ACHIEVING HIGH POWER DENSITY AND ULTRA LOW  
STANDBY POWER IN FLYBACK CONVERTERS

# Agenda

- Basic PSR flyback operation/problems and issues
- Wake-up monitoring (UCC24650) with PSR sampling initiation (UCC28730)
  - Speeds up transient response
  - Greatly reduces output capacitance ( $\approx C_{OUT}/7$ )
  - Can meet zero power ( < 5 mw)
- Device feature set
- Design tips and tricks
- Questions

# Typical Primary Side Regulation (PSR)

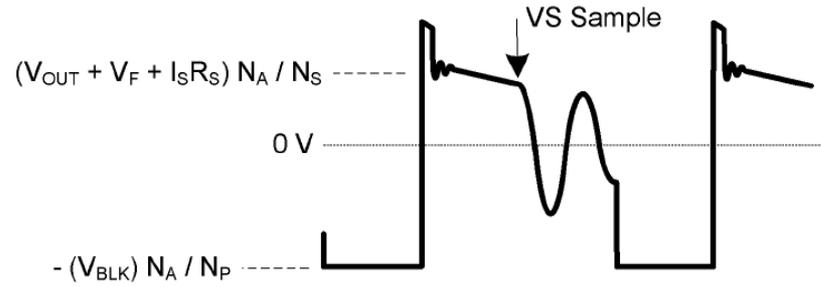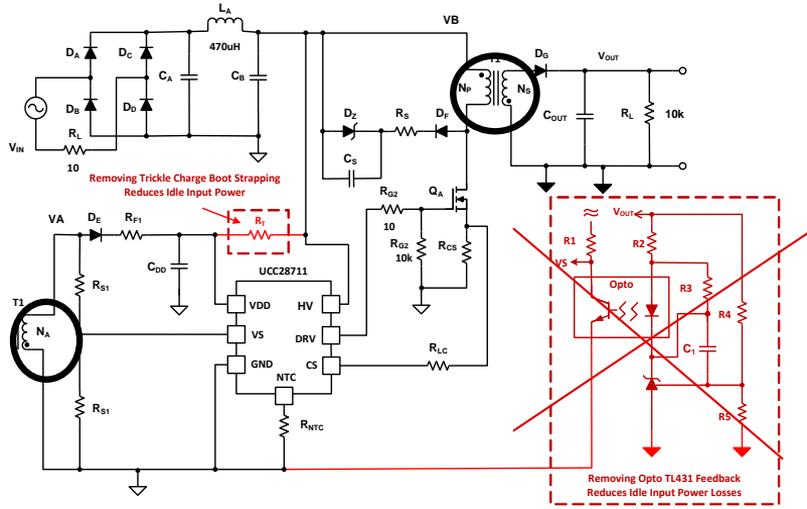


- Uses  $N_A/N_S$  Turns ratio to sample  $V_{OUT}$ 
  - ✓ Control Reflected Output Voltage ( $V_{OUT}$ )
    - Sampled during rectifier diode conduction @ Knee
    - Removes the need of TL431 feedback
      - Saves \$\$\$\$ and reduces standby power





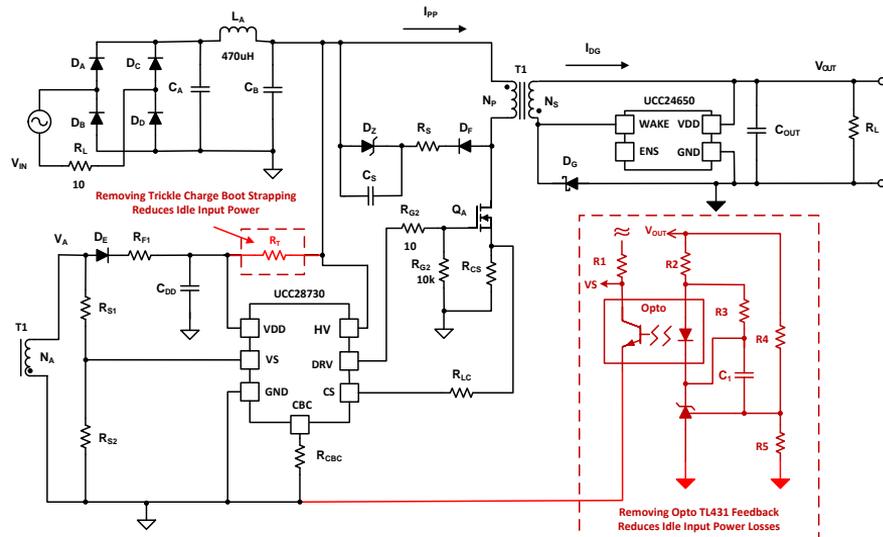
# Improving the load transient response with the UCC28730

- Wake-up monitoring (UCC24650) with PSR sampling initiation (UCC28730) for fast transient response.
  - UCC28730 PSR with output sampling initiation
    - Has all the features of traditional PSR controller
    - Can operate down to 32 Hz to meet < 5 mW Standby power
  - UCC24650 Secondary side wake-up monitoring
    - Monitors  $V_{OUT}$  and will activate PSR sampling if  $V_{OUT}$  drops out of regulation.


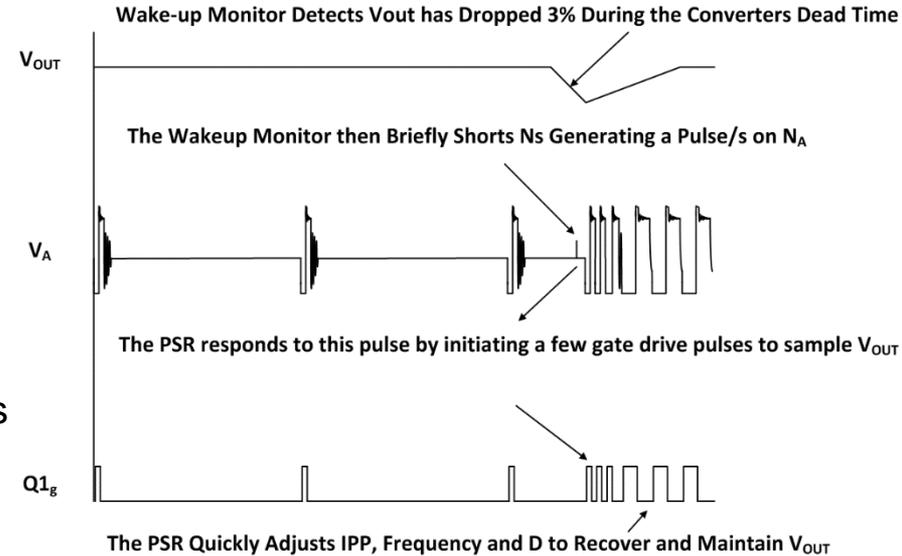
# UCC24650 performance advantage

- UCC24650 Monitors  $V_{OUT}$ 
  - If  $V_{OUT} < 0.97 \times V_{OUT1}$ 
    - The secondary winding is shorted
      - 1us every 30 us with a current-limited switch
- UCC28730
  - Monitors the auxiliary winding ( $V_A$ ) during the deadtime
    - If a + pulse is observed
      - It Triggers PSR Sampling
        - » Gate drive initiates a few sample pulses
          - »  $V_{OUT}$  is sampled
          - » The controller quickly responds
            - » Adjusts  $I_{PP}$ , frequency and Duty cycle
            - » Recovers and Maintains  $V_{OUT}$



# Faster transient response with wake-up

- Reduces the amount of  $C_{OUT}$
- $C_{OUT}$  needs to be sized for
  - Output transients (dV) and the V loop for stability

$$C_{OUT\_No\_Wakeup} \geq \frac{100 \times I_{MAX}}{V_{OUT} \times f_{max}}$$

$$C_{OUT} \geq \frac{I_{MAX}}{dV \times \frac{f_{max}}{10}}$$

# How much is $C_{OUT}$ reduced with wake-up?

- Typical design
  - $f_{min} = 1$  kHz
  - $f_{max} = 80$  kHz
- Using a design with Wake-up
  - $C_{OUT}$  is reduced by a factor of 6.5
  - Output C with Wake-up ( $C_{OUT2}$ )
  - Output C without Wake-up ( $C_{OUT1}$ )

$$C_{OUT1} \geq \frac{I_{MAX}}{dV \times f_{min}}$$

$$C_{OUT2} \geq \frac{I_{MAX}}{dV \times \frac{f_{max}}{10}}$$

$$C_{OUT2} = 10 \times \frac{C_{OUT1} f_{min}}{f_{max}} = \frac{C_{OUT1}}{6.5}$$



# Reducing $C_{OUT}$

- Increases design's power density
- Reduces the cost of the design



$$\bullet C_{OUT1} \geq \frac{I_{MAX}}{dV \times f_{min}}$$

$$\bullet C_{OUT2} \geq \frac{I_{MAX}}{dV \times \frac{f_{max}}{10}}$$

$$\bullet C_{OUT2} = 10 \times \frac{C_{OUT1} f_{min}}{f_{max}} = \frac{C_{OUT1}}{6.5}$$
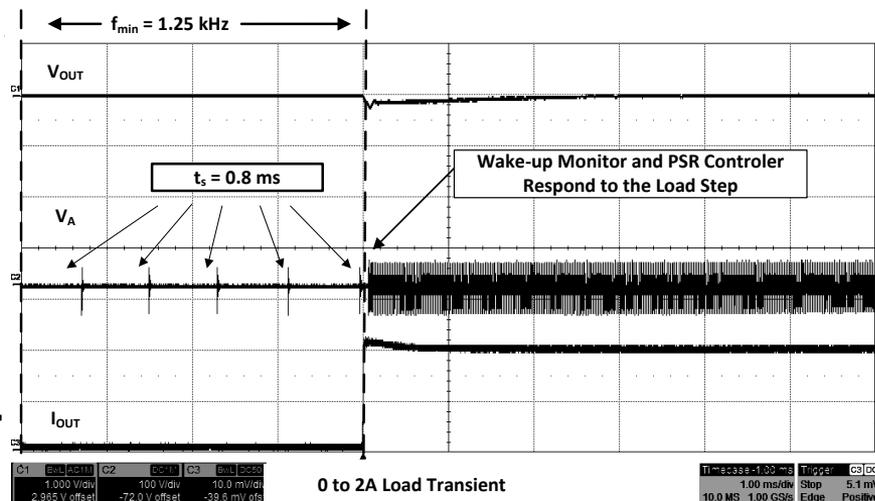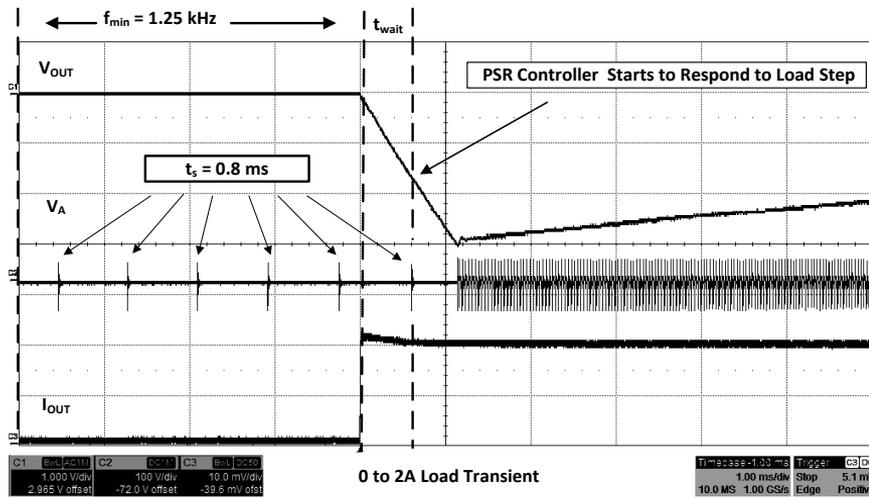
# Transient response with and without wake-up

- 5 V/10 W Design was evaluated,  $f = 1.25 \text{ kHz}$  to  $80 \text{ kHz}$
- The design was tested with a full load transient step (0 to 2A)
- Without wake-up, controller could not sample ( $t_{\text{wait}}$ )  $V_{\text{OUT}}$  for 600us,  $V_{\text{OUT}}$  drooped 3V ☹
  - $t_{\text{wait}}$  could have been as long 800 us
- With wake-up, controller responded quickly no waiting,  $V_{\text{OUT}}$  only drooped 0.4v ☺



# UCC24650 200-V wake-up monitor for fast transient PSR

## 1 Features


- Enables Excellent Load Transient Performance and Zero Standby Power
- Enables Smallest Output Capacitor for Tight  $\Delta V_{OUT}$
- No External Components Required
- <50  $\mu A$  Device Current Consumption (Typical)
- 5-V to 28-V Output Monitoring Capability
- 3% Voltage Droop Detection (Patent Pending)
- 200-V Wake-Up Switch
- Enables and Disables SR Controller, Relay Control, or Other Secondary Circuits
- SOT-23 5-Pin Package

## 2 Applications

- <5-mW *Zero-Power* Standby Applications
- Adapters and Chargers for Consumer Electronics
  - Smart Phones, Tablets, Set-Top Box
- TV and Monitor Power Supplies
- Home Appliance SMPS
  - Refrigerator, Washing Machine, Air Conditioners
- Industrial Power Supplies for Lighting and Home Automation

Note: No opto feedback required

Simplified Application Schematic

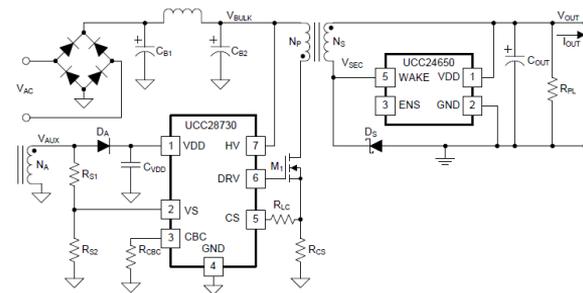





# UCC28730 Protection/fault activation

- Over Voltage Protection (OVP)
  - $(N_S/N_A) * (4.62V/R_{S2}) * (R_{S1} + R_{S2}) - V_D$
- Over Current Protection ( $I_{OCP}$ )  $V_{RCS} = 1.5V$ 
  - $I_{OCP} = 1.5V/R_{CS}$ 
    - Nominal Peak  $V_{RCS} = 0.74V$
- Input Under Voltage Protection (UVLO)
  - $V_{IN} > (N_P/N_A) * (225\mu A * R_{S1})$  to startup
  - $V_{IN} < (N_P/N_A) * (80\mu A * R_{S1})$  to shutdown
- Thermal Shut Down (TSD = 165 C)
- All faults stop switching and reactivate soft start

# Startup/fault



Simplified Application Schematic

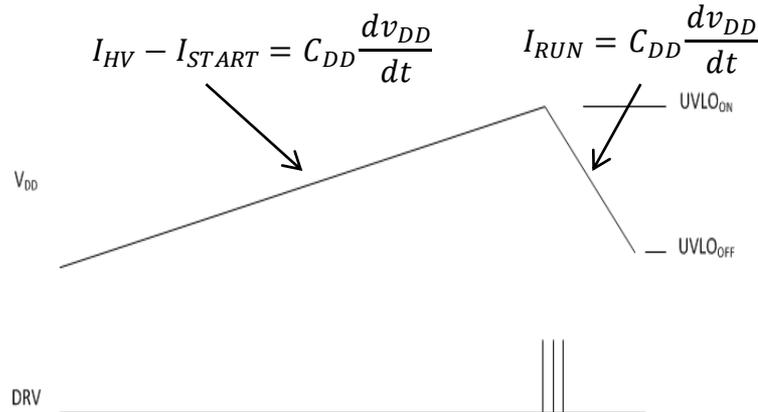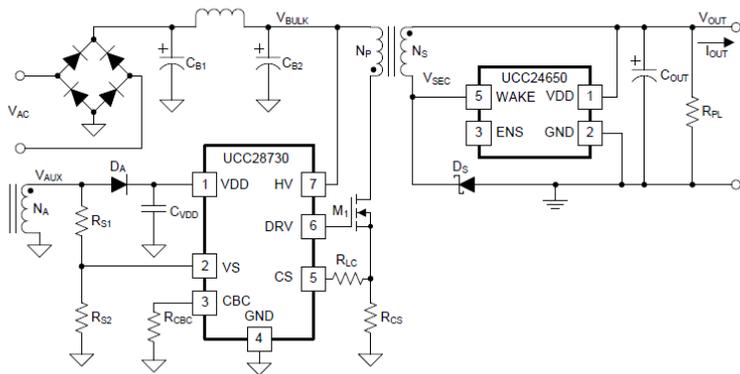

## ➤ VDD charged through HV Input:



- 3 small gate driver pulses are initiated @ UVLO<sub>ON</sub>
- $I_{PP}$  controlled to 1/3 max at startup
- If fault is detected UVLO/soft start initiated
- Will retry at UVLO<sub>ON</sub>

# Startup with input under voltage fault

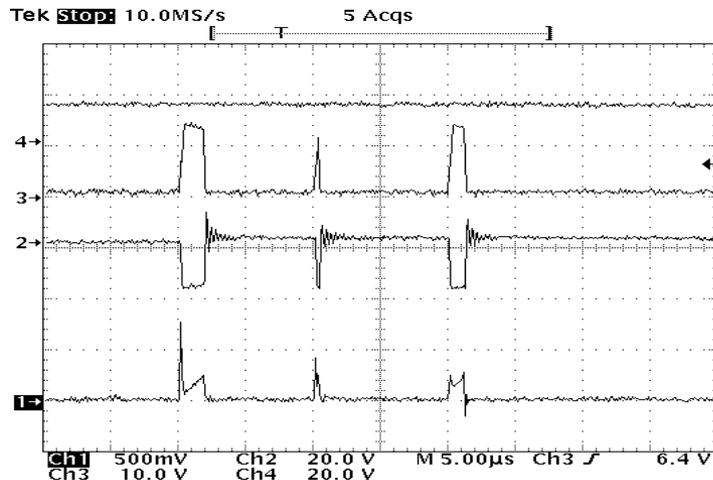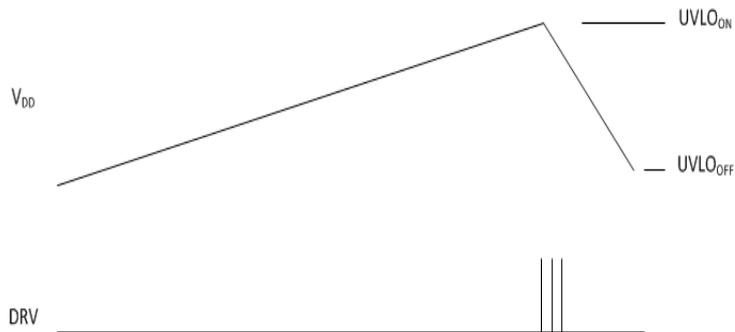

- At UVLO<sub>ON</sub> three gate drive pulse are initiated:
  - CS peak is controlled to 1/3 max (245 mV)
  - Input UVLO detected UVLO restart is initiated

# Startup with no faults

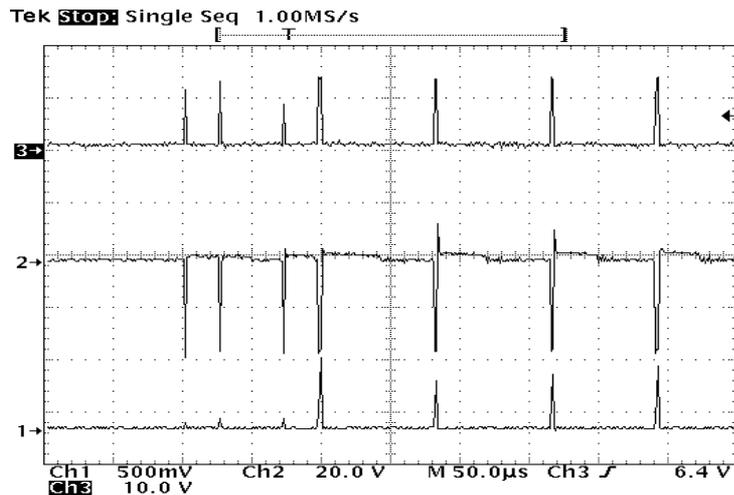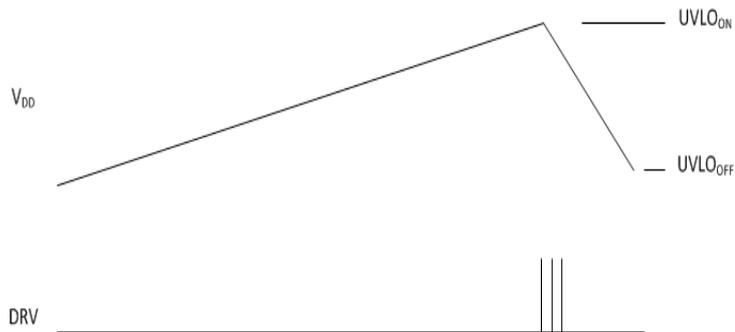


➤ At UVLO<sub>ON</sub> three gate drive pulse are initiated:



- CS peak is controlled to 1/3 max (245 mV)
- No Faults have been detected so supply starts switching
- After 3<sup>rd</sup> initiated pulse I<sub>PP</sub> is controlled to maximum threshold
  - (CS Controlled to 740mV)
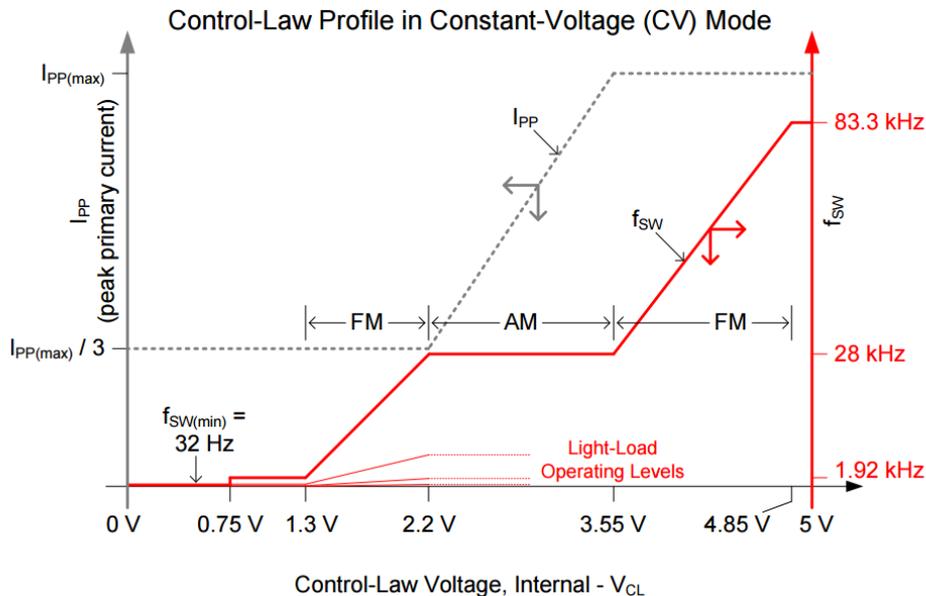
# UCC28730 zero power: reducing $f_{sw}$

- Control Law
  - Reduces  $f_{sw}$  @ Standby (32 Hz minimum)
  - Enables
    - Low bias current (50uA)
    - $P_{IN} < 5mW$  at Standby



# Device timing/control

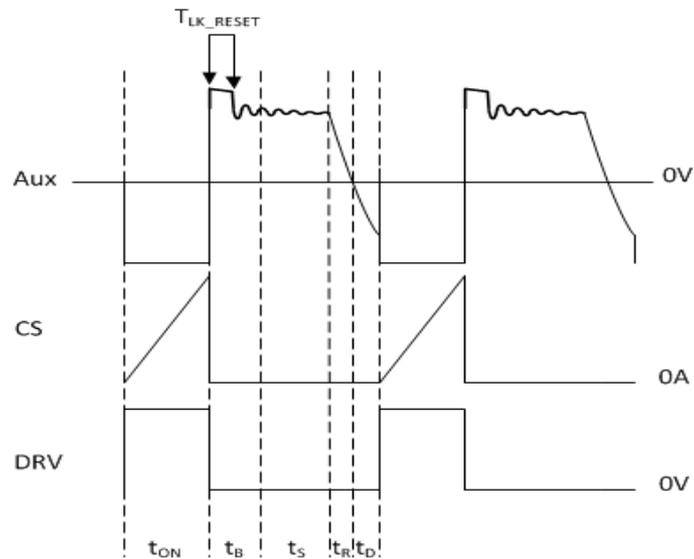
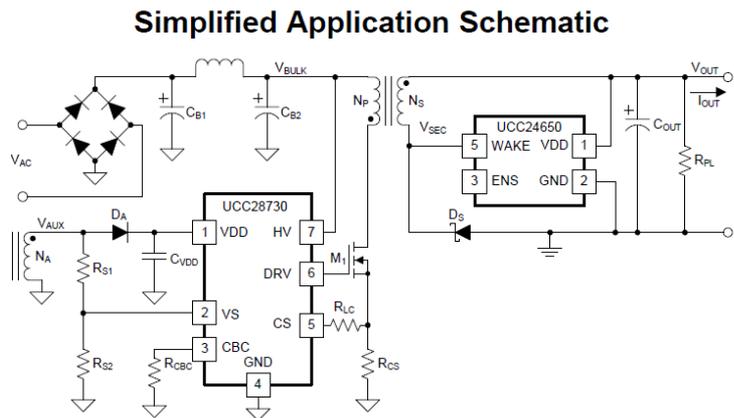


- At max frequency converter is close to critical conduction
- When DRV turns off OFF, VS looks for + transition and activates a VS blanking delay ( $t_B$ )
  - Prevents false OVP from leakage spike ( $T_{LK\_RESET}$ )
  - $t_B$  adjusts with loading
    - $V_{CS} = 0.74V$ ,  $t_B = 2.25 \mu S$ ;  $V_{CS} = 0.245V$ ,  $t_B = 750 \text{ nS}$






# Device timing/control (FM)

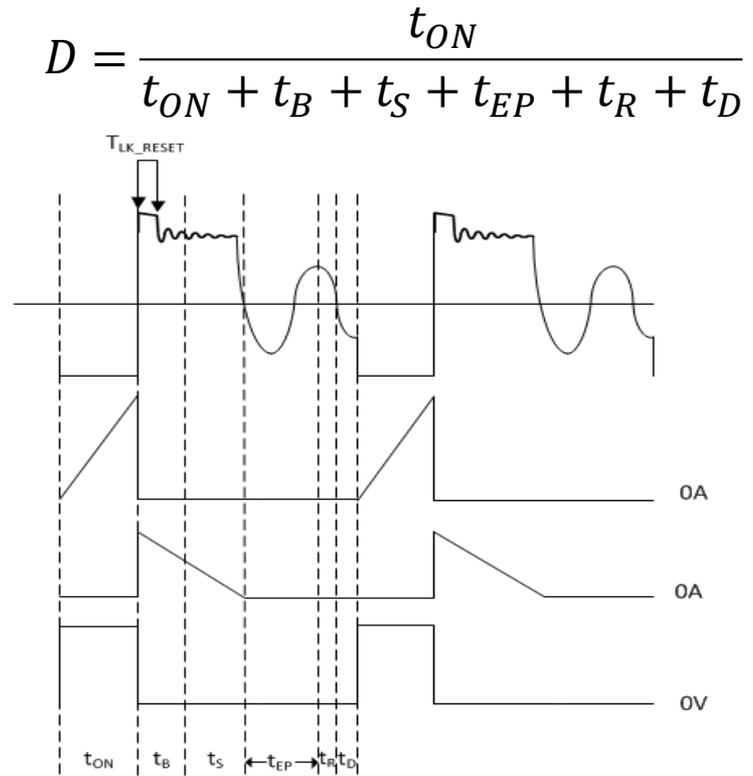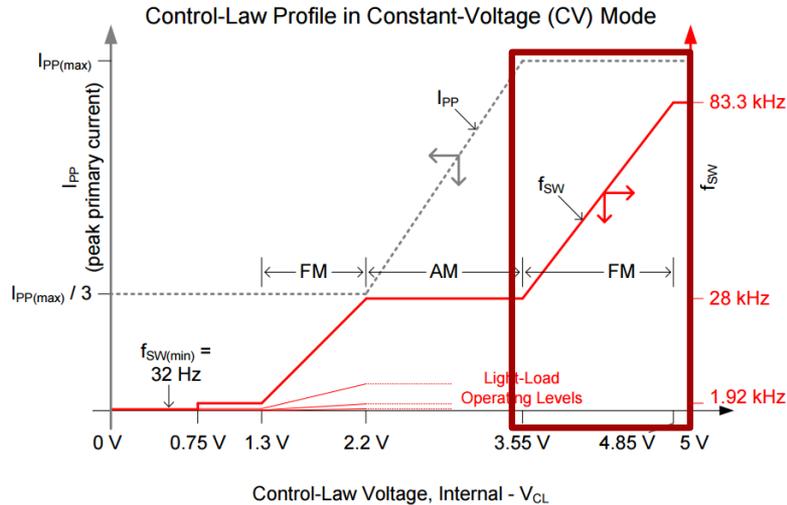


➤  $V_{E/A}$  3.55V to 5V,  $V_{CS} = 0.74V$

- Fixed  $I_{PP}$  set at Max
- A delay is added/adjusted ( $t_{EP}$ ) to adjust  $D$ /frequency (28 kHz < 83 kHz)
- Controller will not turn on M1 until VS zero is detected and  $t_D$  has timed out (150ns)
  - This achieves valley switching deep into DCM

# Device timing/control (AM)

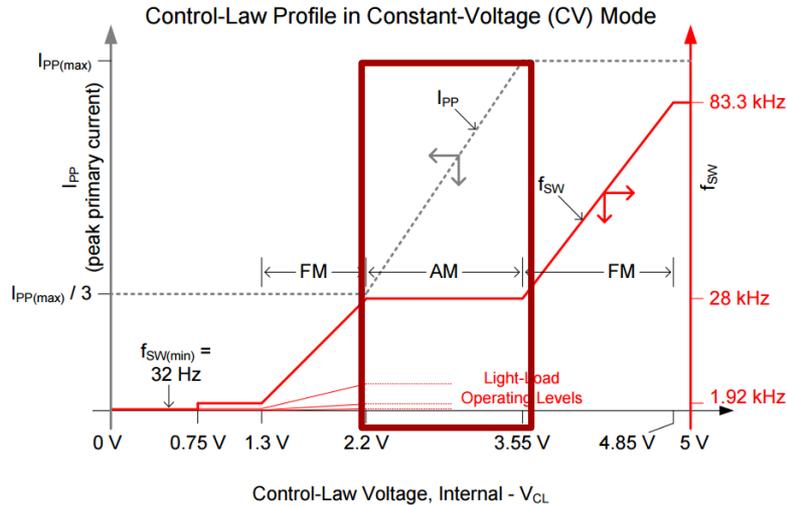

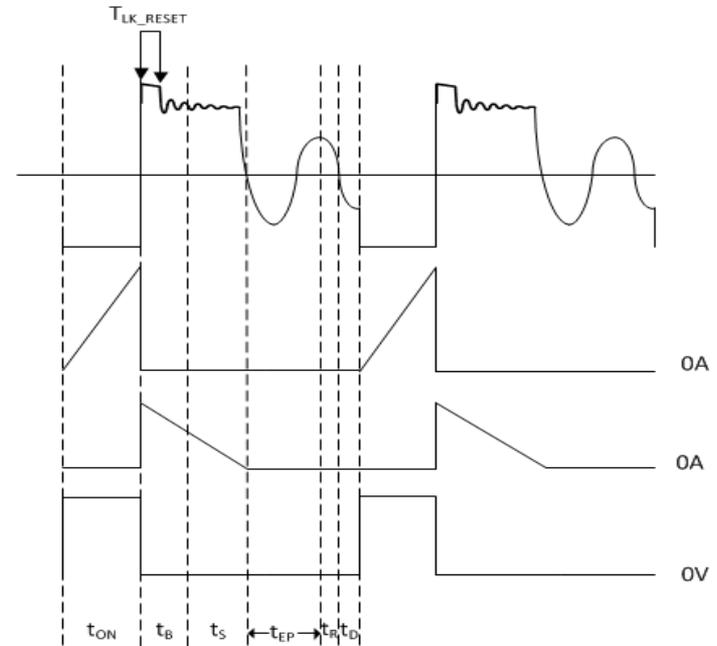
$$D = \frac{t_{ON}}{t_{ON} + t_B + t_S + t_{EP} + t_R + t_D}$$




➤  $V_{E/A}$  2.2V to 3.35V,  $V_{CS} = 0.74V$  to 0.245V

- Converter is operating deeper into DCM
- Frequency is Fixed 28 kHz (Excluding Dither)
- Duty Cycle is Controlled by Adjusting CS amplitude (AM) from  $I_{PP}$  to  $1/3 I_{PP}$ 
  - Was done to remove audible noise as load and  $f$  decrease

# Device timing/sensing (FM)

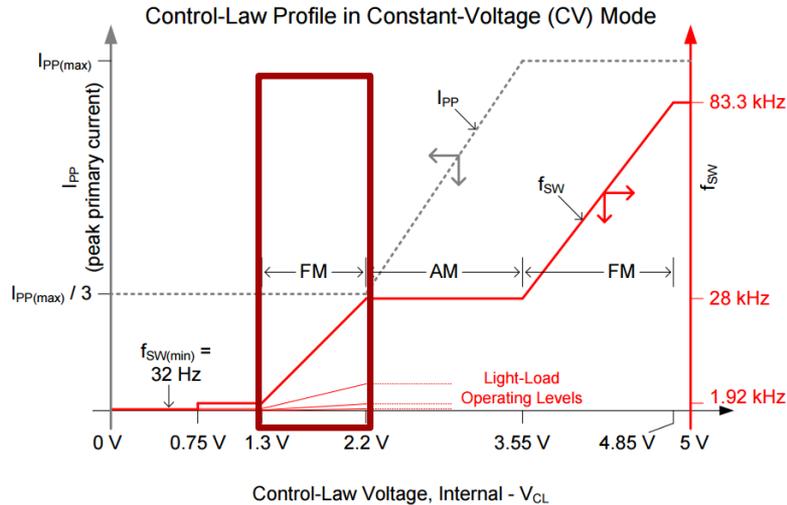

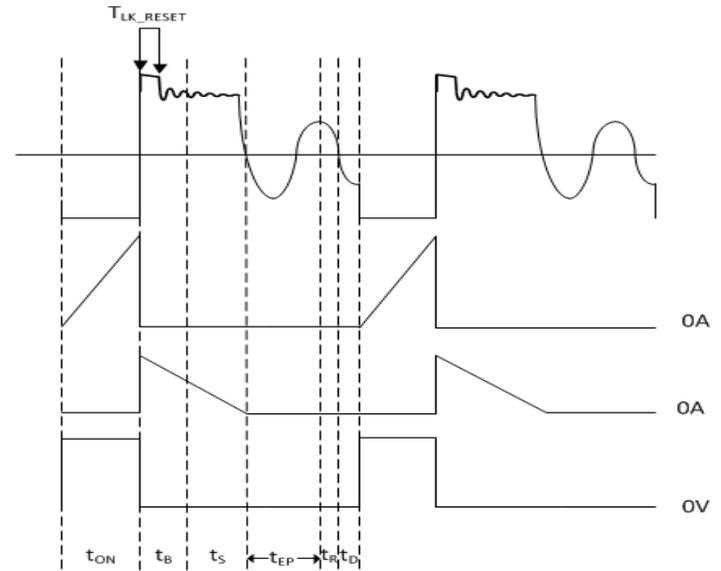
$$D = \frac{t_{ON}}{t_{ON} + t_B + t_S + t_{EP} + t_R + t_D}$$




➤  $V_{E/A}$  1.3V to 2.2V,  $V_{CS} = 0.245$  V

- Duty cycle is controlled by adjusting  $t_{EP}$  (VCO/fixed peak current again)
- Frequency is adjusted from 28 kHz down to 1.92 kHz depending on E/A out
- $I_{PP}$  is fixed to  $1/3 I_{PP MAX}$

# Device timing/sensing (FM)

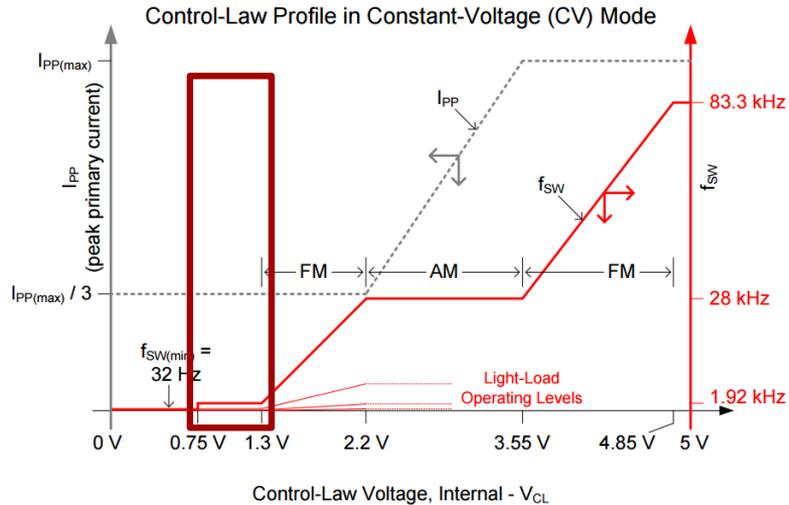

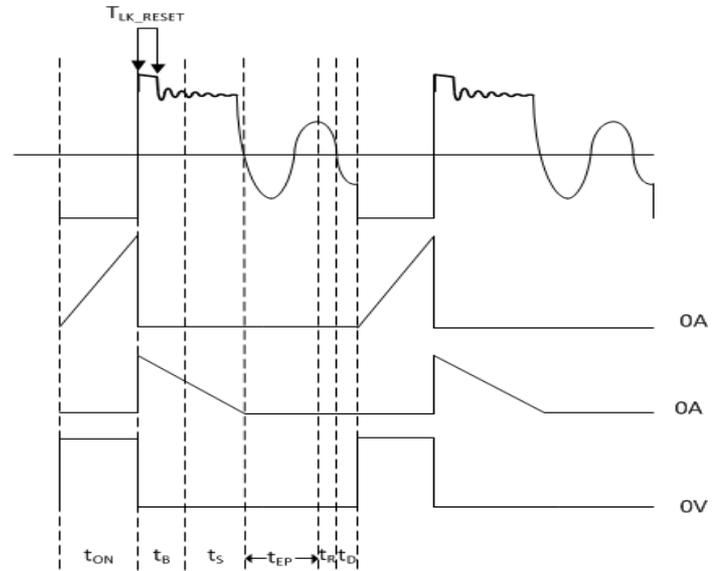
$$D = \frac{t_{ON}}{t_{ON} + t_B + t_S + t_{EP} + t_R + t_D}$$




➤ VE/A 0.75 V to 1.3 V,  $V_{RCS} = 0.245 \text{ V}$

- Frequency shifts to lower operating level as load gets lighter

# Device timing/sensing (FM)

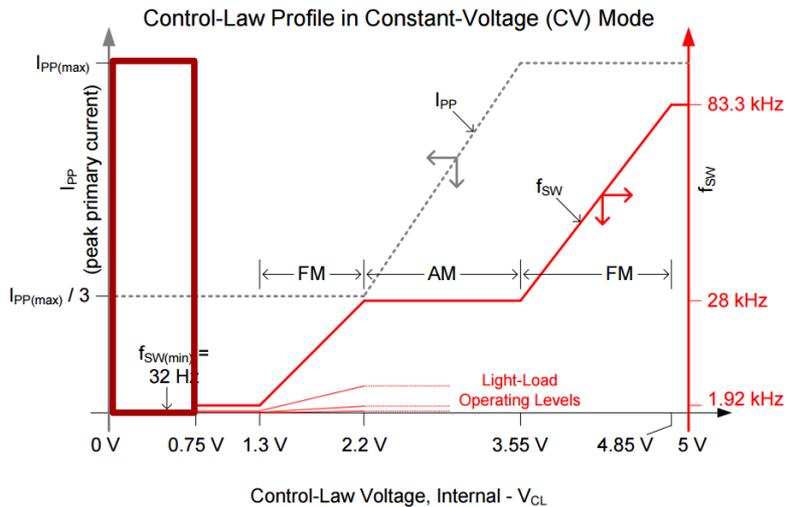


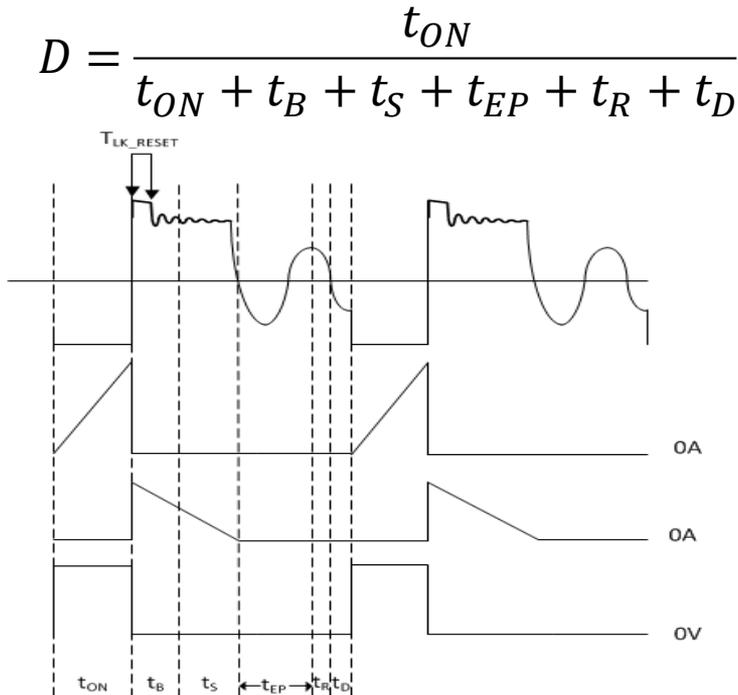- VE/A 0 V to 0.75 V,  $V_{RCS} = 0.245$  V
  - Frequency bottoms out at 32 Hz



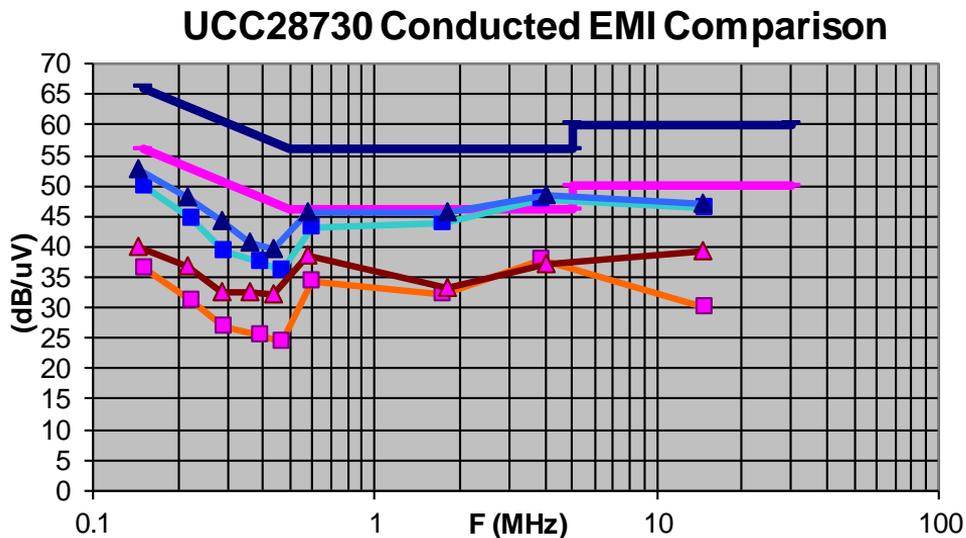
# System EMI reduction evaluation

- EMI comparison with and without dithering
  - ✓ Charger at 5V/1A: Vout return connected to earth
  - ✓ 2-5 dB reduction with EMI jittering scheme


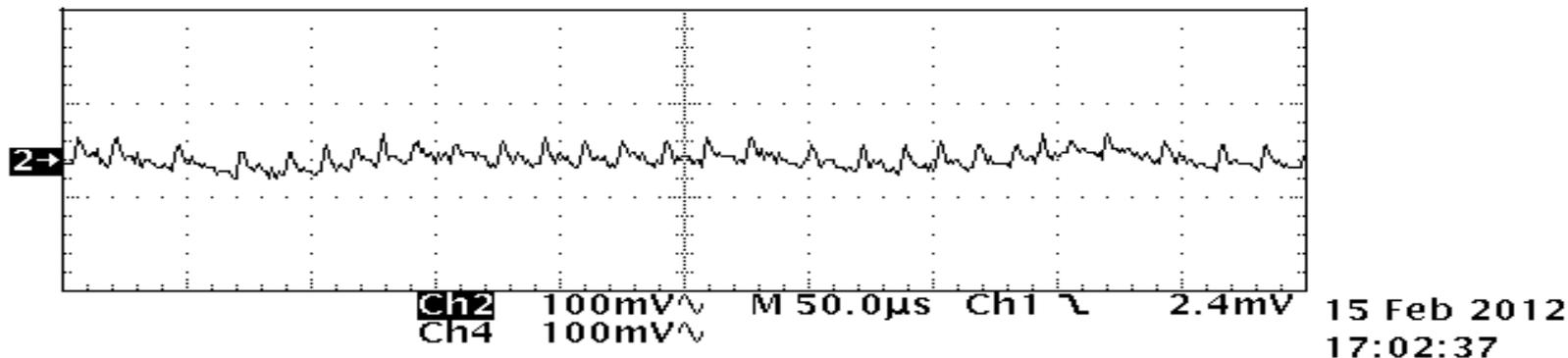
# Frequency dithering affects output ripple





- Frequency jitter does cause a small amount of low frequency output ripple
  - Still meets USB specifications
  - CH2 =  $V_{OUT}$

# $R_{LC}$ offset CS adjustment

$$R_{LC} = \frac{K_{LC} \times R_{S1} \times R_{CS} \times t_d \times N_{PA}}{L_p}$$


➤ Adds offset to the CS signal

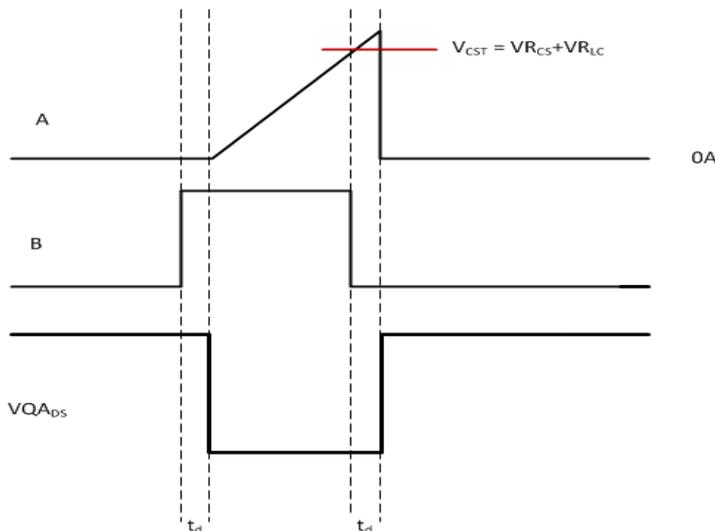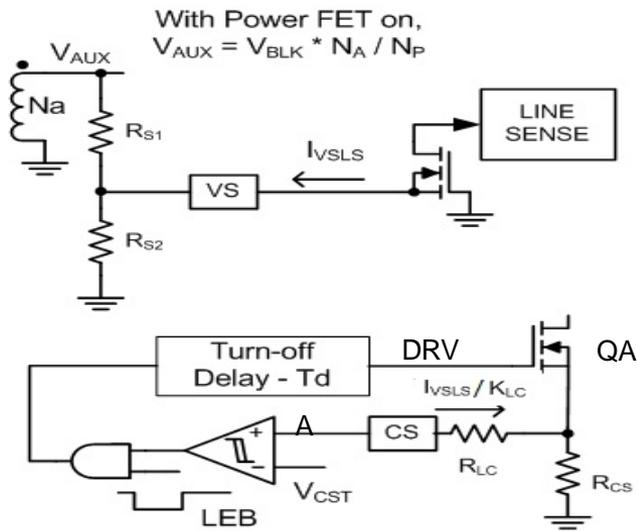- Provides Some VFF
- Provides an adjustment to reduce  $I_{pp}$  over shoot
  - Caused by FET turnoff delays



# Design tips and recommendations

## Simplified Application Schematic

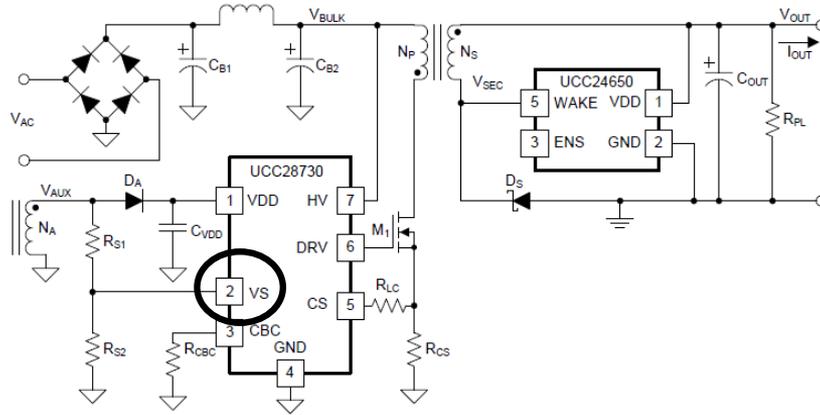


## ➤ VS Pin Recommendations

- No filtering/high impedance pin/noise sensitive
- Don't probe the VS pin directly with a scope probe
  - Can estimate behavior at this pin from  $D_E$




# Design tips and recommendations

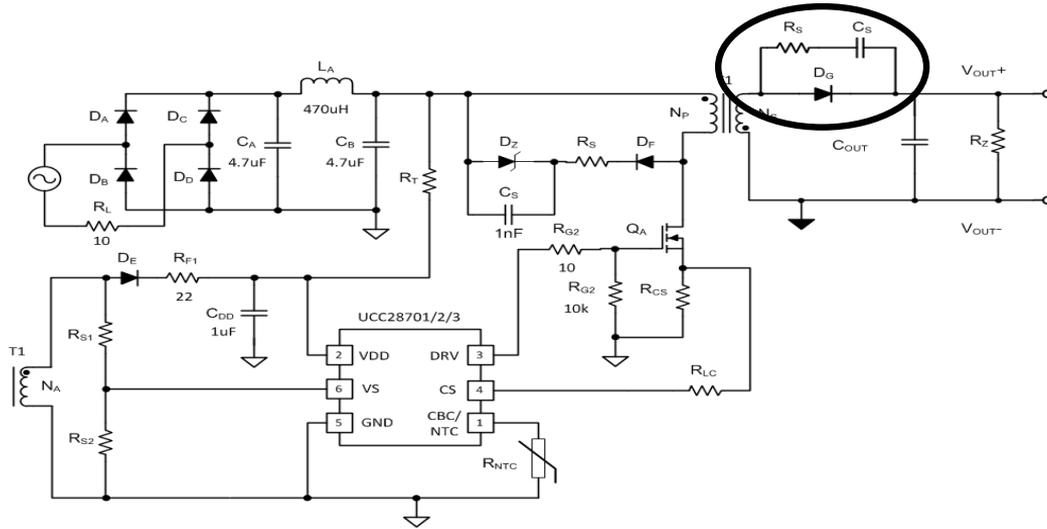

- Leave place for a snubber on the output
  - You may or may not need it
  - Excessive ringing on VS pin could cause misbehavior

# Transformer calculations

Simplified Application Schematic

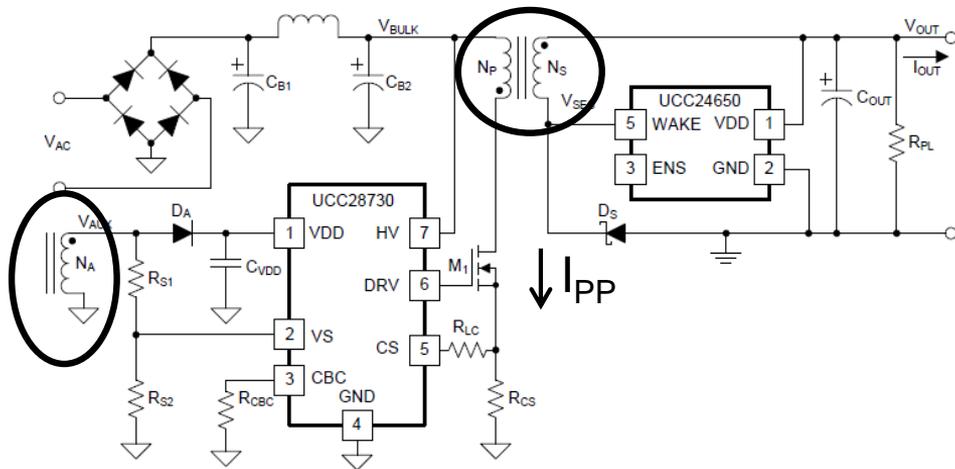

$$\frac{N_P}{N_S} = \sqrt{\frac{L_{PM}}{L_{SM}}}$$


$I_{PP}$  = Peak T1 Primary  $I_P$

$$L_{PM} = \frac{\frac{2 \times P_{OUT}}{\eta}}{I_{PP}^2 \times f_{max}}$$

- T1 primary inductance ( $L_{PM}$ ) set by  $f_{max}$ 
  - $f_{max}$  target 38 kHz to 76 kHz

# Transformer turns ratio ( $N_P/N_S$ )


$$D_{MAX} = \frac{t_{ON}}{T_{SW}}$$

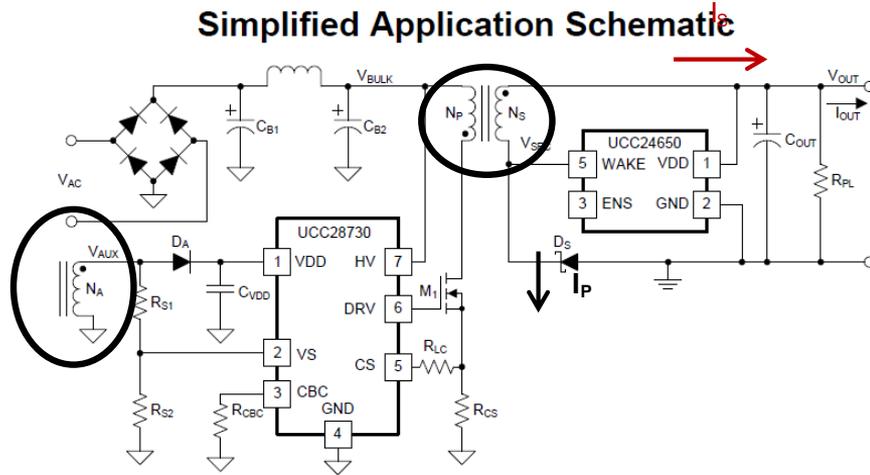

$$D_{MAG} = \frac{t_{DM}}{T_{SW}} \quad D_{MAG} = 0.432$$

$$D_{MAX} = 1 - D_{MAG} - \frac{t_r \times f_{MAX}}{2}$$
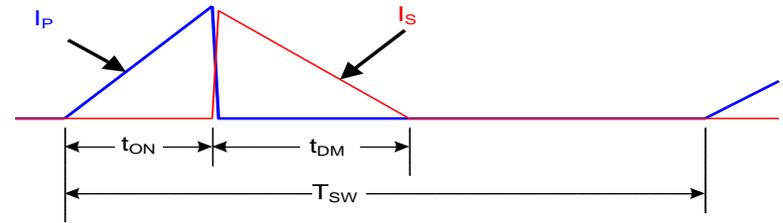
$$\frac{N_P}{N_S} = \frac{D_{MAX}(V_1 - I_{PP}(R_{dson}(QA) + R_{CS}))}{D_{MAG}(V_{OUT} + V_{DG} + V_{CBC})}$$



➤  $L_{PM}$  selected based on  $f_{max}$

- UCC28730 requires  $D_{MAG}$  of 0.432 by design
- Calculate  $D_{MAX}$  based on  $D_{MAG}$  and  $\frac{1}{2}$  of LC tank ( $t_r$ )
- Use volt second balance to calculate  $N_P/N_S$



# Device features: UCC28730

## Low Standby Power Integrated 700-V Start-up Primary Side Regulated Flyback Controller

### Features

- **Less than 5mW standby power**
- AM-FM modulation scheme, operates at low frequency at light loads (no burst mode)
- Internal 700-V startup switch with X-Cap Discharge
- DCM operation with FET valley switching
- Frequency jitter scheme to reduce generated EMI/EMC
- Protection Functions: Over Voltage, Low Line & Over Current


### Applications

- Adapters and chargers for consumer electronics
- Home appliances
- Industrial automation
- Standby and auxiliary power supplies


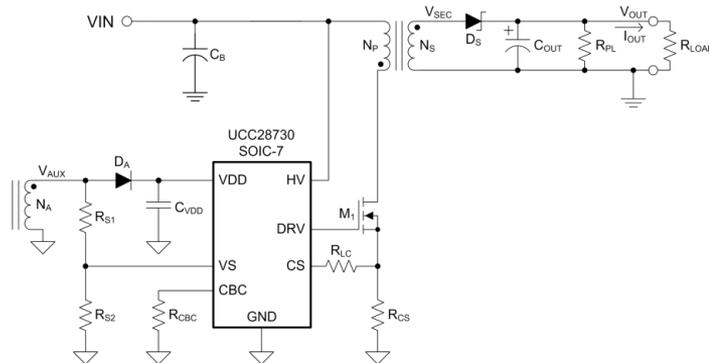
### Benefits

- **Exceeds energy star, coc tier 2, DOE level VI standards**
- Maintains regulation across load range with minimal audible noise
- Simplified fast start, lower standby power, and no leakage for bleed resistors
- Minimized switching losses to improve efficiency
- Minimal external filtering to pass EMI
- Intelligent protection with minimal external components





# Summary: UCC28730 and UCC24650

- Fast transient response ( $C_{OUT}/7$ )
  - High power density
  - Save \$\$
- Industry's first PSR controller that help enables zero-standby (< 5 mW )
- Please use design tips to simplify your design process



**©2021 Texas Instruments Incorporated. All rights reserved.**

The material is provided strictly "as-is" for informational purposes only and without any warranty.  
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated