Selecting the Correct Texas Instruments Signal Switch



ABSTRACT

Texas Instruments offers a wide variety of switches and multiplexers supporting a variety of configuration, voltage, bandwidth, and package needs. This application note summarizes the key features and performance characteristics of our analog signal switches and application considerations for choosing the appropriate TI signal switch.

Table of Contents

1 Introduction	
1.1 Ideal Versus Non-Ideal Switch	
2 Basic Signal Switch Structure	6
2.1 NFET Switch	
2.2 Transmission Gate Switch	6
2.3 NFET With Charge Pump	
3 Analog Versus Digital Signal Switches	9
3.1 Bidirectional Switches	
3.2 Configuration and Channels	
4 Signal Switch Specifications and Features	
5 Texas Instruments Analog Signal Switches and Multiplexers Portfolio	17
5.1 Precision Switches and Multiplexers	
5.2 Protection Switches and Multiplexers	17
5.3 General Purpose Switches and Multiplexers	
5.4 Automotive Switches and Multiplexers	<mark>2</mark> 3
6 Switches and Multiplexers Performance in Digital Signal Applications	24
7 Applications	25
7.1 SPI Multiplexing	25
7.2 Multiplexing Signals to External ADC	26
7.3 Multiplexing Signals to External ADC in Fault Sensitive Conditions	<mark>2</mark> 7
7.4 Switchable Op Amp Gain Setting	<mark>2</mark> 7
7.5 Multiplexing Body Control Module (BCM) Inputs	28
7.6 High Current Range Selection Using External Resistor	<mark>2</mark> 9
7.7 Fault Protection in Factory Automation Control Systems	
7.8 Sample and Hold Circuitry	30
8 Summary	3 [^]
9 Revision History	3 [^]
A Appendix A	32
A.1 Analog Performance – CD, HC, CBT, LVC, and LV	32
A.2 SN74CBT Characteristics	34
A.3 CD74HCT Characteristics	35
A.4 CD74HC Characteristics	36
A.5 SN74HC Characteristics	39
A.6 CD4066B Characteristics	42
A.7 LV-A Characteristics	46
A.8 LVC Characteristics	50
A.9 CBTLV Characteristics	54
List of Figures	
Figure 1-1. Ideal Switch	
Figure 1-2. Behavioral Model of CMOS (FET) Switch	
Figure 2-1. N-channel FET Switch	
Figure 2-2. On-State Resistance vs Lowest I/O Voltage for an N-channel FET Switch With V_{CC} = 5 V	6

Table of Contents www.ti.com

Figure 2-3. Parallel N-/P-Channel FET (Transmission Gate) Switch	7
Figure 2-4. On-State Resistance vs Input Voltage for a Parallel n-/p-Channel FET Switch	
Figure 2-5. Basic Structure of an NMOS Series Switch With the Charge Pump	
Figure 3-1. Bidirectional Signal Path	
Figure 4-1. Logic Thresholds	10
Figure 4-2. On-Resistance	
Figure 4-3. Source and Drain Off Capacitance	11
Figure 4-4. Source and Drain On Capacitance	12
Figure 4-5. Bandwidth	
Figure 4-6. Channel-to-Channel Crosstalk	
Figure 4-7. Charge Injection	
Figure 4-8. Off-Isolation	
Figure 4-9. ON Leakage Current	
Figure 4-10. OFF Leakage Current	
Figure 4-11. Break-Before-Make Time (t _{BBM})	
Figure 4-12. Turn-ON (t _{ON}) and Turn-OFF (t _{OFF}) Time	
Figure 4-13. Fail-Safe Logic	
Figure 5-1. Powered-off Protection	
Figure 5-2. Overvoltage Protection Threshold	
Figure 5-3. TMUX1072 Overvoltage Protection Waveform	19
Figure 5-4. Undervoltage Protection Threshold	20
Figure 7-1. Multiplexing Flash Memory	25
Figure 7-2. Isolation of JTAG, SPI, and GPIO Signals	
Figure 7-3. Multiplexing Signals to External ADC	
Figure 7-4. Multiplexing Signals to External ADC in Fault Sensitive Conditions	
Figure 7-5. Switchable Op Amp Gain Setting	
Figure 7-6. Multiplexing BCM Inputs	
Figure 7-7. High Current Range Selection Using External Resistor	
Figure 7-8. Fault Protection in Factory Automation Control Systems	
Figure 7-9. A Sample and Hold Circuit Realized Using the TMUX611x Analog Switch	
Figure A-1. Log r _{on} vs V _I , V _{CC} = 5 V (SN74CBT3125)	
Figure A-2. r _{on} vs V _I , V _{CC} = 5 V (SN74CBT3125)	24
Figure A-3. V _I vs V _O , V _{CC} = 5 V (SN74CBT3125)	30
Figure A-4. V ₁ vs V ₀ , V _{CC} = 5 V (CD74HCT4066)	35
Figure A-5. r _{on} vs V _I , V _{CC} = 5 V (CD74HCT4066)	36
Figure A-6. V _I vs V _O , V _{CC} = 4.5 V (CD74HC4066)	36
Figure A-7. r _{on} vs V _I , V _{CC} = 4.5 V (CD74HC4066)	
Figure A-8. V _O vs V _I , V _{CC} = 6 V (CD74HC4066)	37
Figure A-9. r _{on} vs V _I , V _{CC} = 6 V (CD74HC4066)	38
Figure A-10. V _O vs V _I , V _{CC} = 9 V (CD74HC4066)	38
Figure A-11. r _{on} vs V _I , V _{CC} = 9 V (CD74HC4066)	39
Figure A-12. V _O vs V _I , V _{CC} = 2 V (SN74HC4066)	39
Figure A-13. r _{on} vs V _I , V _{CC} = 2 V (SN74HC4066)	40
Figure A-14. V _O vs V _I , V _{CC} = 4.5 V (SN74HC4066)	40
Figure A-15. r _{on} vs V _I , V _{CC} = 4.5 V (SN74HC4066)	
Figure A-16. V _O vs V _I , V _{CC} = 6 V (SN74HC4066)	
Figure A-17. r _{on} vs V _I , V _{CC} = 6 V (SN74HC4066)	
Figure A-18. V _O vs V _I , V _{CC} = 5 V (CD4066B)	
Figure A-19. r _{on} vs V _I , V _{CC} = 5 V (CD4066B)	
Figure A-20. V _O vs V _I , V _{CC} = 10 V (CD4066B)	
Figure A-21. r _{on} vs V _I , V _{CC} = 10 V (CD4066B)	
Figure A-22. V _O vs V _I , V _{CC} = 15 V (CD4066B)	
Figure A-23. r _{on} vs V _I , V _{CC} = 15 V (CD4066B)	
Figure A-24. V _O vs V _I , V _{CC} = 2 V (SN74LV4066A)	
Figure A 26 V, yo V, V = 2.5 V (SN74LV4066A)	
Figure A-26. V _O vs V _I , V _{CC} = 2.5 V (SN74LV4066A)	
Figure A-27. r _{on} vs V _I , V _{CC} = 2.5 V (SN74LV4066A)	4/
Figure A-28. V _O vs V _I , V _{CC} = 3.3 V (SN74LV4066A)	48
Figure A-29. r _{on} vs V _I , V _{CC} = 3.3 V (SN74LV4066A)	
Figure A-30. V _O vs V _I , V _{CC} = 5 V (SN74LV4066A)	
Figure A-31. r _{on} vs V _I , V _{CC} = 5 V (SN74LV4066A)	
Figure A-32. V _O vs V _I , V _{CC} = 1.8 V (SN74LVC1G66)	
Figure A-33. r _{on} vs V _I , V _{CC} = 1.8 V (SN74LVC1G66)	50

Trademarks Figure A-34. V_O vs V_I, V_{CC} = 2.5 V (SN74LVC1G66)......51 Figure A-38. V_O vs V_I, V_{CC} = 5 V (SN74LVC1G66).......53 Figure A-39. r_{on} vs V_I, V_{CC} = 5 V (SN74LVC1G66).......53 Figure A-41. r_{on} vs V_I, V_{CC} = 2.5 V (SN74 CBTLV3125)......54 **List of Tables** Table 3-1. Configurations and Channels.....9 Table 5-2. Analog Protection Switches and Multiplexers......21 Table 5-3. General-Purpose Switches and Multiplexers......22 Table 6-1. Summary of Digital Performance24 Table A-7. CD74HC4066 Analog Parameter Measurement Data......39 Table A-10. SN74LV4066A Analog Parameter Measurement Data49 Table A-11. SN74LVC1G66 Analog Parameter Measurement Data......53

Table A-12. SN74CBTLV3125 Analog Parameter Measurement Data......55

Trademarks

All trademarks are the property of their respective owners.

Introduction Www.ti.com

1 Introduction

Analog switches are designed to pass (or isolate) analog signals (both voltage and current) and support analog applications such as audio and video data transmission. Texas Instruments offers a wide variety of switches and multiplexers to improve system design with better accuracy, system reliability and platform scalability.

Selecting the right one can be a formidable task. This application report discusses some of the key characteristics and features of TI's switches and multiplexer families to make the selection process simpler and more efficient.

1.1 Ideal Versus Non-Ideal Switch

When first considering switches, a schematic of the ideal switch (similar to Figure 1-1) might come to mind.

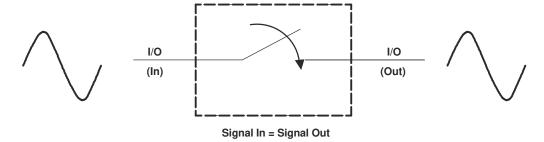


Figure 1-1. Ideal Switch

An input signal applied to the left I/O pin (or port) in Figure 1-1 results in an identical output signal at the right I/O pin, and vice versa. However, in the real world, switches are not ideal and there always is some loss. In the case of clean, properly working mechanical switches, the loss is so minuscule that it hardly bears noting.

Like mechanical switches, solid-state switches are not ideal either. In fact, losses associated with solid-state switches can be significant. Why use a switch like this if it is so far from ideal? The answer is convenience. Solid-state switches are small, fast, easy to use, easy to control, and consume relatively little power compared to traditional electrically controlled switches, such as relays. The switches referred to in this application report are complementary metal-oxide semiconductor (CMOS) field-effect transistor (FET) switches. As mentioned previously, they are not ideal, so we need a way to examine and compare the performance characteristics of the different CMOS families. Figure 1-2 shows a simplified-circuit model of a CMOS switch.

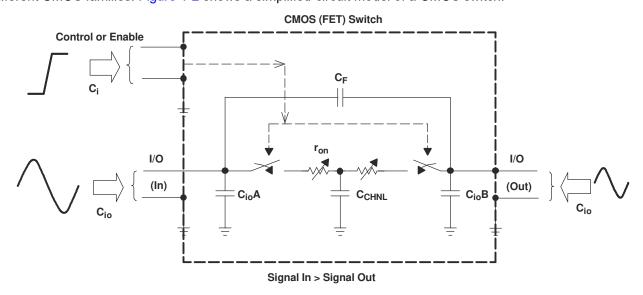


Figure 1-2. Behavioral Model of CMOS (FET) Switch

The output signal (right side, Figure 1-2) is altered due to parasitic effects of the switch. Results may include decreased amplitude, signal distortion, phase shift, the introduction of noise, and frequency attenuation.

www.ti.com Introduction

Parameters contributing to the nonideal characteristics include:

- C_i Control (enable) pin input capacitance
- C_{io} Capacitance measured from either the input or output of the switch
- C_{CHNL} NMOS (PMOS) channel capacitance
- R_{ON} The resistance inserted into the signal path as a result of the switch path being turned on
- C_F Feed-through capacitance; negligible at lower frequencies or when switch is closed.

2 Basic Signal Switch Structure

Texas Instruments signal switches share the common switch architectures NFET switch, Transmission gate switch and NFET with charge pump.

2.1 NFET Switch

Figure 2-1 shows a simplified FET switch, which consists of an N-channel transistor and gate bias and enable circuitry. The switch is bidirectional; the source and drain are interchangeable (while operating, the side with the lowest $V_{I/O}$ is the source). TI CBT bus switches are this type.

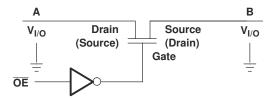


Figure 2-1. N-channel FET Switch

For an N-channel FET to operate properly, the gate should be biased more positive than the magnitude of the signals to be passed. This is because the on-state resistance, R_{ON} (or $R_{DS(ON)}$ as it also is called), increases as the gate, minus source voltage, V_{GS} , decreases. If the lowest $V_{I/O}$ signal approaches the magnitude of V_{CC} , V_{GS} decreases and R_{ON} increases (see Figure 2-2). The ability to maintain a low R_{ON} in a FET switch depends on maintaining V_{GS} as large as possible. In many applications, this characteristic is not a problem, but the designer should be aware of the nonlinearity of this type of device.

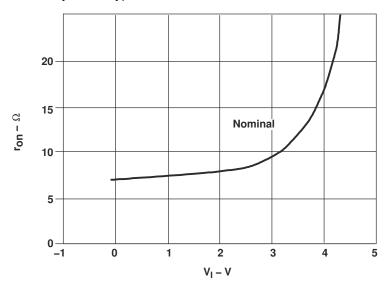


Figure 2-2. On-State Resistance vs Lowest I/O Voltage for an N-channel FET Switch With V_{CC} = 5 V

An N-channel FET can be used to implement a level translator. This switch can pass a signal from 0 V to V_{CC} – V_T , where V_T is the threshold voltage of the NMOS. This characteristic can be used for down translation. For voltage-translation applications, the switch is required to translate efficiently over a wide frequency range and is required to maintain the proper signal level. For example, when translating from a 5-V TTL to a 3.3-V LVTTL signal, the switch is required to maintain the required V_{OH} (output high voltage) and V_{OL} (output low voltage) of 3.3-V LVTTL signal. One important consideration is that the switch can be used only for down translation, for example, high to low level. For low- to high-level translation, additional components (for example, pullup resistors) are required.

2.2 Transmission Gate Switch

Analog (or bilateral, as they also are called) switches consist of a single N-channel transistor in parallel with a single P-channel transistor (see Figure 2-3). These are also known as the Transmission gate switch.

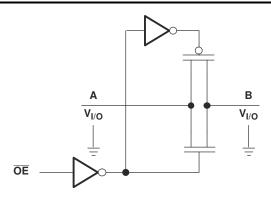


Figure 2-3. Parallel N-/P-Channel FET (Transmission Gate) Switch

As before, when $V_{I/O}$ approaches V_{CC} , the N-channel conductance decreases (R_{ON} increases) while the P-channel gate-source voltage is maximum and its R_{ON} is minimal. The resulting parallel resistance combination is much flatter than individual channel resistances (see Figure 2-4). Examples of switches and multiplexers with parallel n and p channel include TMUX11xx, TMUX61xx, TMUX12xx, TMUX13xx, TMUX6xxx, TMUX7xxx, TMUX8xxx, TS5Axxxx, TS3Axxxx, HCT, HC, CD4000, TMUX40xx, LV-A, LVC, and CBTLV families.

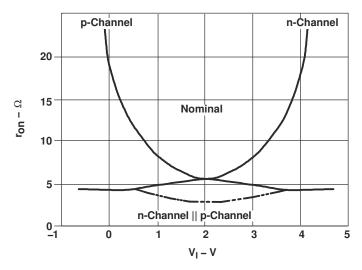



Figure 2-4. On-State Resistance vs Input Voltage for a Parallel n-/p-Channel FET Switch

A flat R_{ON} is especially important if $V_{I/O}$ signals must swing from rail to rail. However, the tradeoff is increased switch capacitance due to the additional P-channel transistor and associated bias circuitry.

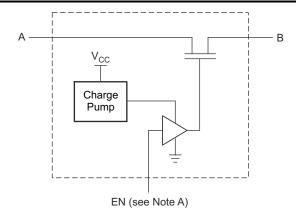2.3 NFET With Charge Pump

Some manufacturers offer N-channel signal switches with charge-pump-enabled pass transistors. A design of this type as shown in Figure 2-5 allows the gate voltage to be higher than V_{CC} . This increases V_{GS} above what is possible in noncharge-pump devices and allows signals at or above V_{CC} to be passed. A switch of this type has the advantage of low, relatively flat R_{ON} (over the signal range), without the addition of a P channel and while maintaining C_{io} values comparable to pure N-channel FET switches. This performance comes at the expense of increased I_{CC} (from a few μA to several mA in some cases). Examples include TMUX1072, TMUX136, TMUX15xx, and the CB3Q family.





Note A: EN is the internal enable signal applied to the switch.

Figure 2-5. Basic Structure of an NMOS Series Switch With the Charge Pump

See *Switches and muxes: What are common switch architectures?* more details on the basics of analog signal switches offered by Texas Instruments.



3 Analog Versus Digital Signal Switches

TI offers a wide variety of signal switches, and sometimes the nomenclature can be confusing to the point of implying limited functionality for a device or family. See details below on digital vs analog and bi-directional functionality of switches.

- Digital switch. Accepts digital inputs and will drive the output depending on the input logic.
- Analog switch. Designed to conduct (or isolate) both analog and digital signals. These will not drive a new signal but will provide bi-directionality to the signal applied to the inputs/outputs.

More details can be found in Switches and muxes: What are switches and multiplexers?.

3.1 Bidirectional Switches

There are two meanings:

The switch conducts equally well from source (S) to drain (D) or from drain (D) to source (S). Each channel has very similar characteristics in both directions and supports both analog and digital signals. TI analog switches and multiplexers are typically bidirectional (Figure 3-1).

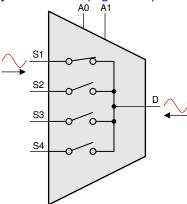


Figure 3-1. Bidirectional Signal Path

Switch can be used in analog or digital applications.

See Switches and muxes: Are switches and multiplexers bidirectional? for more details.

3.2 Configuration and Channels

Switch Configuration defines the number of signals that can be selected and Channel defines the number of configurations (circuits) in a single device. Texas Instruments offers switches and multiplexers in different configurations and channel count. Table 3-1 shows the 1- and 2- channel configurations, but the number of channels may exceed.

Table 3-1. Configurations and Channels 1-Channel 2-Channel 1:1 Configuration D₁ 2:1 D2

4 Signal Switch Specifications and Features

It should be apparent that the most important switch characteristic depends on how it is used. For example, what V_{CC} levels are present, what amplitude signals are required to be passed, what is the maximum signal distortion limit for the system and so forth. These specifications and features are covered in more detail below:

- Supply Voltage: Single power supply Device with only positive power supply pins with reference
 to ground. For noncharge-pump switches, V_{CC} determines the amplitude of the analog signals that can
 be passed without clipping. The voltage applied is labeled as V_{DD}, V_{CC}, V₊ and so forth. Switches like
 TMUX1072, SN3257-Q1, TMUX136, and the TMUX15xx, CB3Q family with integrated charge pumps can
 elevate the gate voltage above V_{CC} (at the expense of larger I_{CC}) and, thus, pass signals of a magnitude
 greater than V_{CC}.
- Supply Voltage: Dual power supply Device with positive and negative supply pins with reference to ground. Voltage applied at the positive pin is labeled as V_{DD}, V_{CC}, V₊, and so forth, and at the negative pin is labeled as V_{SS}, V_{EE}, V-, and so forth. For noncharge-pump switches, V_{CC} determines the amplitude of the analog signals that can be passed without clipping. One or more of the gates of the pass transistors must be biased relative to the minimum and maximum values of the expected input voltage range. Switches, such as the TMUX11xx, TMUX61xx, TMUX62xx, TMUX74xxF, TMUX72xx, TMUX81xx, TMUX82xx, MUX36Sxx, MUX36Dxx, CD4000, and TMUX40xx series allow for biasing from two supplies, making it easy to pass both positive and negative signals.
- Switch Control Signal Levels (V_{IH}/V_{IL}): V_{IH} is the minimum voltage for the input control signal to achieve a *Logic 1* value and V_{IL} is the maximum voltage for the input control signal to remain a *Logic 0* value. Why are these important analog switch considerations? In most applications, the signal switch is controlled by the output of a digital source, therefore, the control signal levels, V_{IH} and V_{IL} , must be compatible with that source to ensure proper operation of the switch. To prevent digital logic control issues, the system must ensure that the output high (V_{OH}) logic output is higher than the input high (V_{IH}) logic input it is controlling. In addition, the output low (V_{OL}) of the logic output must be lower than the input low (V_{IL}) of the logic input it is controlling. See Figure 4-1 for this logic standard. Some components may not meet the standard, but having $V_{IH} < V_{OH}$ and $V_{II} > V_{OL}$ ensures proper system operation. Furthermore, operating the control logic between the VIH and VIL levels will leave the device in an undetermined state where the outputs cannot be known for certain. See Implications of Slow or Floating CMOS Inputs for more information.

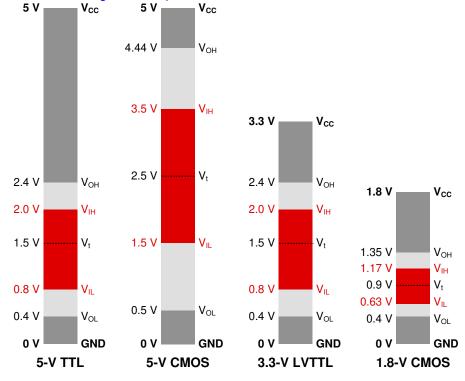


Figure 4-1. Logic Thresholds

- Integrated Pulldown on Logic Pins: The logic inputs of TI muxes are CMOS inputs. Leaving the logic
 inputs of TI muxes floating is never recommended (See Implications of Slow or Floating CMOS Inputs)
 except when using a device that has integrated pulldown resistors on the logic pins. These resistors will
 hold the logic pin to a known state when not being driven high or low. This removes the need for additional
 external components, saving money and space.
- ON Resistance (R_{ON}): The resistance inserted into the signal path as a result of the switch path being turned on. Because it contributes to signal loss and degradation, low R_{ON} tradeoffs must be considered. Noncharge-pump switches achieve low R_{ON} with large pass transistors. These larger transistors lead to larger die sizes and increased C_{io}. This additional channel capacitance can be very significant as it limits the frequency response of the switch. As stated in Section 2.3, switches utilizing charge-pump technology can achieve low R_{ON} and C_{io}, but require significantly higher I_{CC}.

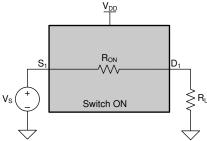


Figure 4-2. On-Resistance

- Switch Output Level: The maximum signal level a switch without a charge pump can pass is typically limited to the switch V_{CC}. Is there sufficient noise margin on the device downstream of the switch such that signal attenuation in the switch will not cause data errors? For instance, the N-channel transistor of a CBT device clamps the switch output at a little more than 1 V below the operating V_{CC}, making it unsuitable for 5-V CMOS high-level (V_{IH} = 3.5 V) signal transmission unless operated from at least 4.5-V V_{CC}. This clamping won't be seen in devices with transmission gate architecture.
- ON/OFF Capacitance (C_{ON}/C_{OFF}): The ON capacitive loading when a switch path is in the low impedance state. The OFF capacitive loading when a switch path is in the high impedance state. Total switch and load capacitance must be considered because it can affect response time, settling time and fanout limits. See more details in the application note: Improve Stability Issues with Low CON Multiplexers. C_{io} is the capacitance of an input/output (I/O) terminal of the device with the input conditions applied that, according to the product specification, establishes the high-impedance state at the output. This parameter is the internal capacitance encountered at an input/output (I/O) of the device. These values are established by the design, process, and package of the device.

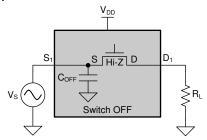


Figure 4-3. Source and Drain Off Capacitance

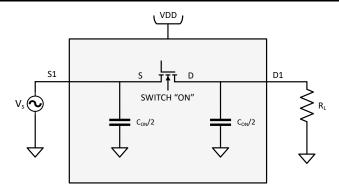


Figure 4-4. Source and Drain On Capacitance

Frequency Response: All CMOS switches have an upper limit to the frequency that can be passed.
 No matter how low R_{ON} and C_{io} can be maintained in the chip manufacturing process, they still form an undesired low-pass filter that attenuates the switch output signal. Bandwidth (BW) of a switch is the frequency range of signals that can pass through the switch with no more than 3 dB of attenuation.

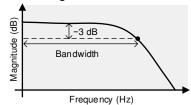


Figure 4-5. Bandwidth

- Latchup-Immunity: This feature prevents the device's power rails from shorting together (latching up)
 due to electrical overstress, injected currents, or electrically fast transients. See Using Latch-Up Immune
 Multiplexers to Help Improve System Reliability for information on TI multiplexers Latch-Up Immunity.
- Sine-Wave Distortion or Total Harmonic Distortion: These are measurements of the linearity of the
 device. Nonlinearity can be introduced a number of ways (design, device physics, and so forth) but, typically,
 the largest contributor is R_{ON}. As shown in Figure 2-2 and Figure 2-4, R_{ON} varies with V_{I/O} for all types
 of CMOS switches. Having a low R_{ON} is important, but a flat R_{ON} over the signal range is almost equally
 important.
- Crosstalk: There are two types of crosstalk to consider:
 - Channel-to-channel crosstalk (X_{TALK}): A measurement of unwanted signal coupling from an ON channel to an OFF channel. This is measured in a specific frequency and in specified in dB. The level of crosstalk is a measure of how well decoupled the switch control signal is from the switch output. Due to the parasitic capacitance of CMOS processes, changing the state on the control signal causes noise to appear on the output. In audio applications, this can be a source of the annoying pop that is sometimes heard when switching the unit on or off. Devices such as the TS5A22364 have built in shunt resistors that will discharge any built up capacitance on the unselected signal path to reduce this popping sound.

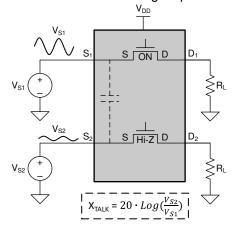


Figure 4-6. Channel-to-Channel Crosstalk



- Crosstalk between switches. The level of crosstalk also is a measure of adjacent-channel rejection. As
 with control-to-output crosstalk, parasitic capacitance can couple the signal on one switch with that on
 another switch.
- Charge Injection (Q_C): Charge injection is a measurement of unwanted signal coupling from the control (IN) input to the analog output. This is measured in coulomb (C) and measured by the total charge induced due to switching of the control input. TI specifies enable-to-output crosstalk and some competitors use this parameter. As with enable-to-output crosstalk, changing the state on the control pin causes a charge to be coupled to the channel of the transistor introducing signal noise. It is presented in this report for a relative comparison with the competition. TI muxes such as the TMUX1308, TMUX1309 and SN74HC4851 have built in injection current control circuity to shunt any injected current to ground, stabilizing the output signal. See more details in *Prevent crosstalk with injection current control*.

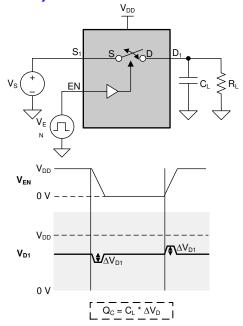


Figure 4-7. Charge Injection

• Off Isolation: A measurement OFF-state switch impedance. This is measured in dB at a specific frequency, with the corresponding channel in the OFF state.

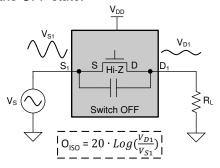


Figure 4-8. Off-Isolation

• ON Leakage Current: Leakage current measured at the input port in the ON state, with the corresponding output port in the ON state and the output being open (See Figure 4-9). Leakage current during the high-impedance state should be very small. Leakage current, if high, may load an isolated bus and corrupt the data.



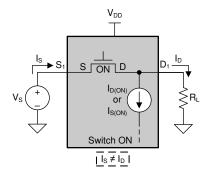


Figure 4-9. ON Leakage Current

• **OFF Leakage Current**: Leakage current measured at the input port, with the corresponding channel output in the OFF state under worst-case input and output conditions (See Figure 4-10). Leakage current is an important parameter, as it contributes to DC errors both when the switch is ON and when it is OFF.

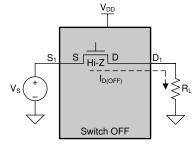


Figure 4-10. OFF Leakage Current

Break-Before-Make Time (t_{BBM}): Ensures that in a multiplexer, two multiplexer paths are never electrically connected when the signal path is changed by the select input. Break before make delay is a safety feature that prevents two inputs from connecting when the device is switching. The output first breaks from the ON-state switch before making the connection with the next on-state switch. It guarantees that two multiplexer paths are never electrically connected when the signal path is changed by the select input. See Figure 4-11 for more details.

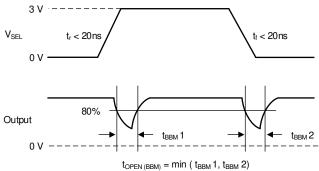


Figure 4-11. Break-Before-Make Time (t_{BBM})

Turn ON (t_{ON}) / Turn OFF (t_{OFF}) Time: The time required for a switch path to be internally changed to an ON or OFF state. These parameters determine how quickly the switch can respond to a desired ON or OFF state (See Figure 4-12). In general, switch enable and disable times are not symmetrical. This is not usually an issue, as few applications require high control (enable) signal frequencies. See more details on switch timing characteristics in Switches and muxes: What are timing characteristics?

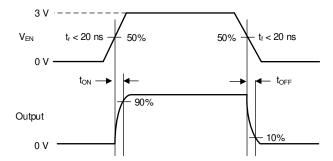


Figure 4-12. Turn-ON (t_{ON}) and Turn-OFF (t_{OFF}) Time

- **Propagation Delay** (t_{pd}): This is the time required for the signal to pass through the switch from the input to the output. This parameter is negligible for all but the most critical timing budgets. When the switch is ON, the propagation delay through one or more of the pass transistors is minimal. The load seen on the output of the switch and the driving strength at the input will typically have far greater contributions and limitations on the propagation delay and timing than the switch itself. The On-resistance and On-capacitance and load of the device can be used for a method to approximate the propagation delay.
- 1.8 V Control Logic: Switches with this feature have a built-in voltage translator to prevent voltage mismatch between the supply rail and the control logic. V_{IH} and V_{IL} levels are compatible with the 1.8-V logic levels at any voltage supply. See the Simplifying Design With 1.8 V logic MUXes and Switches Tech Note for more information. Most of the new TMUX devices (for example: TMUX1108, TMUX1511, TS3A27518E, TS5A26542) come with the 1.8 V control logic feature. The built-in voltage translator prevents voltage mismatch between the supply rail of the TMUX device and the control logic of the processor. This feature enables the mux to be controlled directly by the processor through standard 1.8 V GPIO pins. This eliminates the need for an external voltage translator, saving space in the system.
- 1.2V Control Logic: Similar to the 1.8V control logic, this feature allows for muxes, such as the TMUX1575, to be logic compatible with 1.2V logic levels reducing the need for an external voltage translator, saving space in the system.
- Support Negative Voltage: This is defined as a multiplexer that allows negative voltages to be pass without the need for a dual supply. The TMUX4157N is an example of this with a single negative voltage supply, while TS5A22362 and TS5A22364 are both examples of devices that support negative analog signal pass through with only a positive single sided supply.
- Fail-safe Logic: Ensures the switch stays off and the logic pin does not back-power VDD when the voltage on the signal pin is greater than VDD. TI switches, such as TMUX1574, TMUX1575, TMUX72xx, TMUX73xx and TMUX4157N, with Fail-safe Logic will protect downstream components when a logic signal is present on the select pins while the switch is unpowered. This feature allows voltages on the control pins to be applied before the supply pin, protecting the device from potential damage. The switch maintains in a high-impedance state on the SEL logic pins preventing power from going through VDD during power sequencing. For example, the Fail-Safe Logic feature allows the select pins of the TMUX1574 to be ramped to 5.5 V while supply V_{DD} = 0 V. Additionally, the feature enables operation of the multiplexer with V_{DD} below the voltage on the select pins.
 - Protects mux and downstream ICs from damage.
 - Eliminates need for power sequencing solutions.
 - Reduces BOM count and cost Simplifies system design.
 - Improves system reliability.

See more details in What is fail-safe logic?.

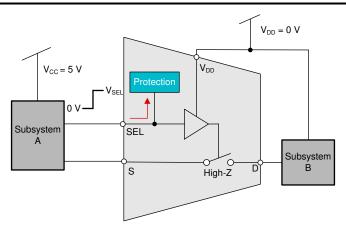


Figure 4-13. Fail-Safe Logic



5 Texas Instruments Analog Signal Switches and Multiplexers Portfolio

Texas Instruments offers a comprehensive portfolio of precision, protection, and general-purpose switches and multiplexers to support end-to-end signal chain needs.

This TI analog signal switch and multiplexer portfolio is intended to give a top level view of the characteristics and parameters that the device in that category have. The categories are not always mutually exclusive for example especially when referring to the protection category. Many of the devices in the protection category have some of the same low leakage / low R_{ON} parameters of the precision family yet add additional protection features.

The following sections highlight key features and applications of the precision, protection, and general-purpose switches and multiplexers.

5.1 Precision Switches and Multiplexers

TI offers a broad range of precision multiplexers and switches in different configurations to improve performance and minimize offset errors and signal distortion in high-accuracy measurement systems. The key differentiating features of these precision switches are:

- Low ON Leakage (I_{ON})
- Low ON Resistance (R_{ON})
- Low ON Capacitance (C_{ON})
- Low Charge Injection (Q_C)

In addition to the above features, the TI analog precision switches also support 1.8 V control logic, fail safe logic, break-before-make switching and are available in ultra small packages.

Table 5-1 below shows performance specifications of analog precision switches:

Table 5-1. Analog Precision Switches and Multiplexers									
V _{SIGNAL}	Part Number	Configuration	R _{ON} (Typ) (Ω)	C _{ON} (pF)	Q _C (pC)	Ι _{ΟΝ} (μ Α)	Package/Pin		
	TMUX1101/02	1:1, 1 channel	2	18	-1.5	0.002	SC70 5, SOT-23 5		
	TMUX1121/22/23	1:1, 2 channel	1.9	17	-1.5	0.002	VSSOP 8		
	TMUX1111/12/13	1:1, 4 channel	2	19	-1.5	0.002	TSSOP 16, UQFN 16		
	TMUX1119	2:1, 1 channel	2.5	21	-6	0.004	SC70 6, SOT-23 6		
Low Voltage (V _{SIGNAL} =<	TMUX1136	2:1, 2 channel	1.8	20	-6	0.002	USON 10, VSSOP 10		
24V)	TMUX1133	2:1, 3 channel	2	20	-1	0.002	TSSOP 16		
	TMUX1134	2:1, 4 channel	2	20	-1	0.002	TSSOP 20		
	TMUX1104	4:1, 1 channel	2.5	40	1.5	0.0035	USON 10, VSSOP 10		
	TMUX1109	4:1, 2 channel	2.5	35	1	0.003	TSSOP 16, UQFN 16		
	TMUX1108	8:1, 1-channel	2.5	65	1	0.004	TSSOP 16, UQFN 16		
	TMUX7234	2:1, 4 channel	3.5	76	3	0.0002	TSSOP 20, WQFN 20		
	TMUX6121/22/23	1:1, 2 channel	120	4.2	0.15	0.0004	VSSOP 10		
	TMUX6111/12/13	1:1, 4 channel	120	4.2	0.6	0.0005	TSSOP 16, WQFN 16		
	TMUX6119	2:1, 1 channel	120	4.3	0.19	0.0004	SOT-23 8		
	TMUX6136	2:1, 2 channel	120	5.5	-0.4	0.0004	TSSOP 16		
Mid Voltage (25V =< V _{SIGNAL} =< 99V)	TMUX6104	4:1, 1 channel	125	5	0.35	0.001	TSSOP 14		
SIGNAL ,	MUX36S04	4:1, 2 channel	125	6.7	0.3	0.0033	TSSOP 16, WQFN 16		
	MUX36S08	8:1, 1 channel	125	9.4	0.3	0.0033	TSSOP 16, WQFN 16		
	MUX36D08	8:1, 2 channel	125	8.7	0.31	0.0053	QFN 32, SOIC 28, TSSOP 28, WQFN 32		
	MUX36S16	16:1, 1 channel	125	13.5	0.31	0.0053	QFN 32, SOIC 28, TSSOP 28, WQFN 32		

Table 5-1 Analog Precision Switches and Multiplexers

5.2 Protection Switches and Multiplexers

TI offers a broad range of protection multiplexers and switches in different configurations to protect upstream and downstream components from and during fault conditions while maximizing signal integrity. The key differentiating features of these protection switches are:



- Powered Off Protection: Protects switch and isolates signal path when signals are present at the I/O pins and VDD = 0 V. See the Eliminate Power Sequencing With Powered-off Protection Signal Switched Tech Note and Simplify power sequencing with powered-off protection for more information. TI switches with powered-off protection will protect downstream components when input signals are present in the I/O pins while the switch is not powered. The switch maintains a high-impedance state on the I/O pins which prevents back-powering V_{DD} and the Select (SEL) pin with the following features.
 - Provides electrical isolation between subsystems.
 - Prevents data from being transmitted unintentionally.
 - Eliminates need for power sequencing solutions.
 - Reduces BOM count and cost Simplifies system design.
 - Improves system reliability.

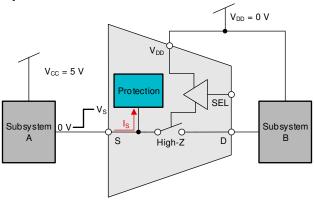


Figure 5-1. Powered-off Protection

Over Voltage Protection / Fault Detection: Fault-protect multiplexers have built in fault-protected features such as overvoltage detection and protection. These can easily be identified with an 'F' appended to the multiplexer name, such as TMUX7412F, TMUX7308F and TMUX7462F. These devices detect overvoltage inputs by comparing the voltage on a source pin with the supplies. A signal is considered overvoltage if it exceeds the supply voltage by the threshold voltage (V_T or V_{TH}), listed in the data sheet. Upon detection of an overvoltage event, the switch enters a high impedance state, isolates the signal path and protects downstream components.

Depending on the device the overvoltage threshold can be determined 1 of 3 ways; A fixed threshold, a threshold that is equal to the VDD supply, or a configurable threshold via an extra supply provided through the IC.

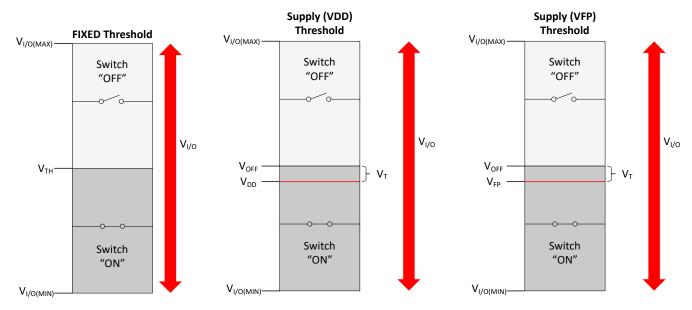


Figure 5-2. Overvoltage Protection Threshold



The TMUX1072 is a unique low voltage device that supports overvoltage detection as well. This devices has a fixed threshold for fault events. When the voltage at the COM pin exceeds the overvoltage threshold, VOVP_TH, the open drain output FLT pin pulls the pin low to indicate an overvoltage event has been detected and the I/O path goes HI-Z. The open drain output will release the FLT pin when the voltage on the COM pin returns below the VOVP_TH.

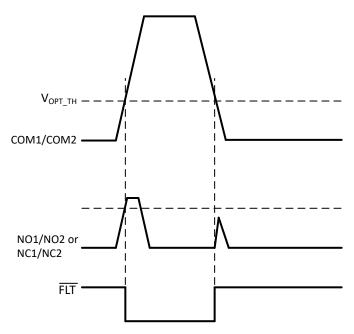


Figure 5-3. TMUX1072 Overvoltage Protection Waveform

Undervoltage Protection - Devices with undervotlage protection detect undervoltage inputs on the I/O's
by comparing the voltage on a source pin with the supplies. A signal is considered undervoltage if it
falls below the supply voltage by the threshold voltage (V_{TH}), listed in the data sheet. Upon detection of
an undervoltage event, the switch enters a high impedance state, isolates the signal path and protects
downstream components.

Depending on the device, the overvoltage threshold can be determined 1 of 2 ways; A threshold that is equal to the VSS supply, or a configurable threshold via an extra supply provided through the IC.



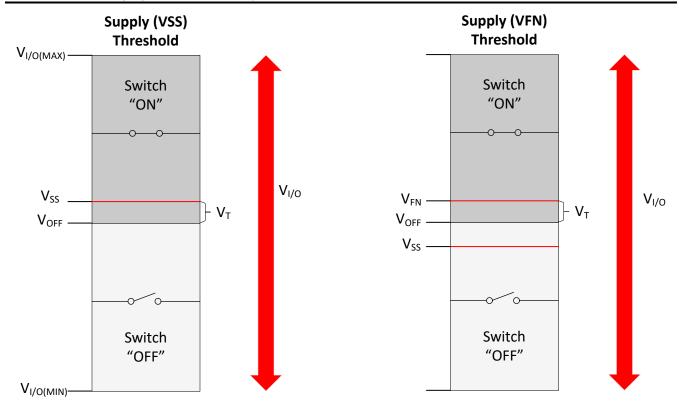


Figure 5-4. Undervoltage Protection Threshold

- Input voltage tolerance: This is defined as a specific protection referencing the maximum voltage that can be applied to any source pin. The voltage can be referenced from source pin to supply or between the source pins and one or more drain pins. Below is an example of a device with a maximum voltage that can be applied to any source input pin of +60 V or -60 V. It shall be cautioned that the device is rated to handle maximum stress of 85 V across different pins as well. The device has different maximum stress ratings across different pin combinations and are defined as the following:
- 1. Between the source pins and supply rails

For example, if the device is powered by VDD supply of 20 V, the maximum negative signal level on any source pin is –60 V to maintain the 60 V maximum rating on any source pin. If the device is powered by VDD supply of 40 V, the maximum negative signal level on any source pin is reduced to –45 V to maintain the 85 V maximum rating across the source pin and the supply.

2. Between the source pins and one or more drain pins

For example, if channel S1 is ON and the voltage on S1(A) pin is 40 V. In this case, the drain voltage is also 40 V. The maximum negative voltage on any of the other source pins is –45 V to maintain the 85 V maximum rating across the source pin and the drain pin.

Table 5-2 shows performance specification of analog protection switches:



Table 5-2. Analog Protection Switches and Multiplexers

lable 5-2. Analog Protection Switches and Multiplexers								
V _{cc}	Part Number	Configuration	R _{ON} (Typ) (Ω)	Package/Pin	Features			
	TMUX1511	1:1, 4 channel	2	TSSOP 14, UQFN 16	1.8-V compatible control inputs, Fail- safe logic, Supports JTAG signals, Supports SPI signals, Supports input voltage beyond supply			
	TMUX154E	2:1, 2 channel	6	UQFN 10, VSSOP 10	1.8-V compatible control inputs, Powered-off protection, Supports I ² C signals, Supports input voltage beyond supply			
	TMUX1574	2:1, 4 channel	2	SOT-23-THN 16, TSSOP 16, UQFN 16	1.8-V compatible control inputs, Fail- safe logic, Supports JTAG signals, Supports SPI signals, Supports input voltage beyond supply			
	TMUX1575	2:1, 4 channel	1.7	DSBGA 16	1.2-V compatible control inputs, 1.8-V compatible control inputs, Powered-off protection, Supports SPI signals, Supports input voltage beyond supply			
	TMUX136	2:1, 2 channel	4.6	UQFN 10	1.8-V compatible control inputs, Supports I ² C signals			
	TMUX1072	2:1, 2 channel	6	UQFN 12, VSSOP 10	1.8-V compatible control inputs, Supports I ² C signals, Supports input voltage beyond supply			
Low Voltage (V _{SIGNAL} =< 24V)	TS5A3159A	2:1, 2 channel	0.7	DSBGA 6, SC70 6, SOT-23 6	Powered-off protection, Break-before- make			
- Company (Colonal Colonal Col	SN74CBTLV3257	2:1, 4 channel	5	SOIC 16, SSOP 16, TSSOP 16, TVSOP 16, UQFN 16, VQFN 16	Powered-off protection, Supports JTAG signals, Supports SPI signals			
	TS5A3359	3:1, 1channel	0.7	DSBGA 8, VSSOP 8	Powered-off protection, Break-before- make			
	SN74CBT3305C ⁽¹⁾	1:1, 2 channel	3	SOIC 8, TSSOP 8	Supports I ² C signals, Undershoot protection			
	SN74CBTD3306C	1:1, 2 channel	3	SOIC 8, TSSOP 8	Signal path translation, Undershoot protection			
	SN74CB3Q3257	2:1, 4 channel	4	SSOP 16, TSSOP 16, TVSOP 16, VQFN 16	Powered-off protection, Supports JTAG signals, Supports SPI signals, Supports input voltage beyond supply			
	SN74CBTLV1G125 (1)	1:1, 1 channel	5	SOT-23 5, SC-70 5	Powered-off protection			
	SN74CB3T1G125 ⁽¹⁾	1:1, 1 channel	5	SC70 5, SOT-23 5	Powered-off protection, Signal path translation			
	SN74CBTLV3126	1:1, 4 channel	5	SOIC 14, SSOP 16, TSSOP 14, TVSOP 14, VQFN 14	Powered-off protection, Supports JTAG signals, Supports SPI signals			
	TS3A27518E	2:1, 6 channel	4.4	TSSOP 24, WQFN 24	Powered-off protection, Break-before- make, Supports SPI signals, Supports JTAG signals, 1.8-V compatible control inputs			
	TMUX8212	4:1 ,1 channel	5	TSSOP 16				
	TMUX8108	8:1, 1 channel	37	TSSOP 16	1.8-V compatible control inputs, Break- before-make, Fail-safe logic, Powered- off protection			
	TMUX8109	4:1, 2 channel	37	TSSOP 16	on protostion			
	TMUX7412F	1:1, 1 channel	9.5	WQFN 16	1.8-V compatible control inputs, Break-before-make, Fail-safe logic,			
Mid Voltage (25 V =<	TMUX7462F	1:1, 4 channel	9.5	WQFN 16	Overvoltage protection			
V _{SIGNAL} = < 99V)	TMUX7308F	8:1, 1 channel	250	TSSOP 16, WQFN 16	1.8-V compatible control inputs, Break-before-make, Fail-safe logic, Overvoltage protection, Powered-off protection			
	MPC509	4:1, 2 channel	1300	SOIC 16, PDIP 16				
	MPC508	8:1, 1 channel	1300	SOIC 16, PDIP 16	Dual supply, Break-before-make, Overvoltage protection, Powered-off			
	MPC507	8:1, 2 channel	1300	SOIC 28	protection			
	MPC506	16:1, 1 channel	1300	SOIC 28				

⁽¹⁾ See Appendix A for analog performance of CBT and CBTLV family.



5.3 General Purpose Switches and Multiplexers

TI offers a broad portfolio of bidirectional general-purpose switches and multiplexers across a wide voltage range, channel count and configuration that are typically used in low-frequency or digital (ON or OFF) applications where size and BOM optimization or both are most important.

Table 5-3 below shows performance specifications of general purpose multiplexer family of devices:

Table 5-3. General-Purpose Switches and Multiplexers

Table 5-3. General-Purpose Switches and Multiplexers									
V _{SIGNAL}	Part Number	Configuration	R _{ON} (Typical) (Ω)	Package Pin	Features				
Low Voltage (V _{SIGNAL} =< 24 V)	TMUX1309	4:1, 2 channel	59	SOT-23-THIN 16, TSSOP 16, WQFN 16	1.8-V compatible control inputs, Break-before-make, Injection current				
	TMUX1308	8:1, 1 channel	59	SOT-23-THIN 16, TSSOP 16, WQFN 16	control				
	TMUX1247	2:1, 1 channel	3	SC70 6					
	TMUX1219	2:1, 1 channel	3	SC70 6, SOT-23 6					
	TMUX1204	4:1, 1 channel	9	USON 10, VSSOP 10	1.8-V compatible control inputs, Break-before-make, Fail-safe logic				
	TMUX1209	4:1, 2 channel	5	TSSOP 16, UQFN 16	, ,				
	TMUX1208	8:1, 1 channel	5	TSSOP 16, UQFN 16					
	SN74LVC2G66	1:1, 2 channel	6	DSBGA 8, SM8 8, VSSOP 8	Supports I ² C signals				
	TS5A3157	2:1, 1 channel	5.5	DSBGA 6, SC70 6, SOT-23 6	Break-before-make				
	TS5A23157	2:1, 2 channel	10	UQFN 10, VSSOP 10	Break-before-make, Supports I ² C signals				
	CD74HC4053 ⁽¹⁾	2:1, 3 channel	45	PDIP 16, SOIC 16, SO 16, TSSOP 16	Break-before-make				
	SN74LV4053A ⁽¹⁾	2:1, 3 channel	23	PDIP 16, QFN 16, SOIC 16, SOP 16, TSSOP 16, CDIP 16	Support mixed-mode voltage operation on all ports				
	SN74LVC1G3157 ⁽¹⁾	2:1, 1 channel	6	SC70 6, SOT-23 6, SON 6, DSBGA 6, X2SON 6	Break-before-make				
	CD4051B ⁽¹⁾	8:1, 1 channel	125	PDIP 16, SOIC 16, SO 16, TSSOP 16	Break-before-make				
	TMUX4051	8:1, 1 channel	125	SOT-23 THIN 16, TSSOP 16, WQFN 16	±12-V signal range, 1.8-V compatible logic				
	TMUX4052	4:1, 2 channel	125	SOT-23 THIN 16, TSSOP 16, WQFN 16	±12-V signal range, 1.8-V compatible logic				
	TMUX4053	2:1, 3 channel	125	SOT-23 THIN 16, TSSOP 16, WQFN 16	±12-V signal range, 1.8-V compatible logic				
	TS12A4514	1:1, 1 channel	6.5	PDIP 8, SOIC 8, SOT-23 5	Break-before-make				
	TMUX8212	1:1, 4 channel	5	TSSOP 16					
	TMUX8108	8:1, 1 channel	37	TSSOP 16	1.8-V compatible control inputs, Break-before-make, Fail-safe logic,				
	TMUX8109	4:1, 2 channel	37	TSSOP 16	Powered-off protection				
Mid Voltage (25 V =< V _{SIGNAL} = < 99V)	TMUX6219	2:1, 1 channel	2	VSSOP 8					
	MUX509	4:1, 2 channel	125	SOIC 16, TSSOP 16					
	MUX508	8:1, 1 channel	125	SOIC 16, TSSOP 16	Break-before-make				
	MUX507	8:1, 2 channel	125	SOIC 28, TSSOP 28	Dieak-Deloie-Illake				
	MUX506	16:1, 1channel	125	SOIC 28, TSSOP 28					

⁽¹⁾ See Appendix A for analog performance of HC, LV, LVC and CD400 family.



5.4 Automotive Switches and Multiplexers

Table 5-4 below shows performance specification of automotive (AECQ100) switches:

Table 5-4. Automotive Switches and Multiplexers - AECQ100

Configu		Part Number	Package/Pin	Features
		TS5A3166-Q1	SC70 5	Low R _{ON} (<10 Ω), Powered-off protection
	1:1, 1 channel	SN74LVC1G66-Q1	SC70 5, SOT-23 5	Low R _{ON} (<10 Ω)
		SN74CBTLV1G125-Q1	SOT-23 5	Low R _{ON} (<10 Ω), Powered-off protection
	1:1, 2 channel	SN74LVC2G66-Q1	VSSOP 8	Low R _{ON} (<10 Ω), Supports I ² C signals
	1:1, 4 channel	CD4066B-Q1	SOIC 14	Low C _{ON} (<10 pF)
		CD74HCT4066-Q1	SOIC 14, TSSOP 14 52 mm2: 6 x 8.65 (SOIC 14),	Low C _{ON} (<10 pF)
	2:1, 1 channel	TS5A3159-Q1	SOT-23 6	Break-before-make, Low R _{ON} (<10 Ω)
		SN74LVC1G3157-Q1	SC70 6, SOT-23 6	Low R _{ON} (<10 Ω)
	2:1, 2 channel	TS5A22364-Q1	VSSOP 10	Low R _{ON} (<10 Ω), Break-before-make, Supports negative voltages
	2:1, 2 channel	TS5A3357-Q1	VSSOP 10	Low R _{ON} (<10 Ω), Break-before-make, Supports I ² C signals
	2:1, 3 channel	TMUX4053	SOT-23 THIN 16, TSSOP 16, WQFN 16	R _{ON} (<125 Ω), ±12-V signal range, 1.8-V compatible logic
	2:1, 4 channel	SN3257-Q1	SOT-23-THN 16, TSSOP 16	Low R _{ON} (<10 Ω), 1.8-V compatible control inputs, Break-before-make, Fail-safe logic, Integrated pulldown resistor on logic pin, Powered-off protection, Supports SPI signals, Supports input voltage beyond supply
Low Voltage (V _{SIGNAL} =< 24 V)	2:1, 6 channel	TS3A27518E-Q1	TSSOP 24, WQFN 24	Low R _{ON} (<10 Ω), Powered-off protection, Break-before- make, Supports SPI signals, Supports JTAG signals, 1.8- V compatible control inputs
	3:1, 1 channel	TS5A3357-Q1	VSSOP 8	Break-before-make
		TMUX1309-Q1	SOT-23-THIN 16, TSSOP 16, WQFN 16	1.8-V compatible control inputs, Break-before-make, Fail-safe logic, Injection current control
	4:1, 2 channel	TMUX4052	SOT-23 THIN 16, TSSOP 16, WQFN 16	R _{ON} (<125 Ω), ±12-V signal range, 1.8-V compatible logic
		TS3A5017-Q1	VQFN 16	Powered-off protection, Supports SPI signals
		SN74LV4052A-Q1	SOIC 16, TSSOP 16	Low C _{ON} (<10 pF)
		TMUX1308-Q1	SOT-23-THN 16, TSSOP 16	1.8-V compatible control inputs, Break-before-make, Current injection control
		TMUX1208-Q1	UQFN 16	1.8-V compatible control inputs, Break-before-make, Fail- safe logic
	8:1, 1 channel	TMUX4051	SOT-23 THIN 16, TSSOP 16, WQFN 16	R _{ON} (<125 Ω), ±12-V signal range, 1.8-V compatible logic
		SN74HC4851-Q1	SOIC 16, TSSOP 16	Current Injection Control
		SN74LV4051A-Q1	SOIC 16, SOIC 16, TSSOP 16	Low R _{ON} (<10 Ω), Break-before-make
		CD74HCT4051-Q1	SOIC 16	Low C _{ON} (<10 pF), Break-before-make
	16:1, 1 channel	CD74HCT4067-Q1	SOIC 24	Low C _{ON} (<10 pF), Break-before-make
	1:1, 4 channel	TMUX7212-Q1	TSSOP 16	
Mid Voltage (25 V =< V _{SIGNAL} = < 99V)	2:1 1 channel	TMUX6219-Q1	VSSOP 8	Low R _{ON} (<10 Ω), 1.8V compatible logic inputs, Break- before-make
S.OHAL	2:1, 1 channel	TMUX7219-Q1	VSSOP 8	



6 Switches and Multiplexers Performance in Digital Signal Applications

For switches and multiplexers in use in digital signal applications, in addition to the signal switch specifications highlighted in Section 4, the following features also need to be considered:

- Number of bits required to be switched. With TI's wide variety of signal switches, it is possible to switch
 between 1 to 32 bits at the same time with a single device. For instance, the LVC1G66 or CBT1G125 can be
 used to switch a single bit, while the CBTLV16211 is capable of switching 24 bits total in banks of 12. Or, by
 tying the adjacent enable pins together, it is possible to control 24 bits with one enable signal.
- Special features. TI offers bus switches with special features, such as an integrated diode for single-component level shifting (CBTD), active clamps for undershoot protection (CBTK), Schottky-diode clamps for undershoot protection (CBTS), a bus-hold option (CBTH) for holding floating or unused I/O pins at valid logic levels, and an integrated-series-resistor option (CBTR) to reduce signal-reflection noise.

Table 6-1 summarizes the digital performance characteristics of TI signal switches from which generalities can be derived regarding switch-family performance. For exact parameters, refer to the respective data sheets.

Table 6-1. Summary of Digital Performance

Part Number ⁽¹⁾	V _{cc}	R _{ON}	t _{pd} ⁽²⁾	t _{ON} (3)	t _{OFF} ⁽⁴⁾	V _{IH} (control inputs)	V _{IL} (control inputs)	C _i (control)	C _{io} (on)	C _{io} (off)
TMUX1209	1.08-5.5 V	5-9 Ω	_	60 ns	45 ns	1.8-V CMOS	1.8-V CMOS	1 pF	42 pF	38 pF
TMUX1511	1.5-5.5 V	2 Ω	67 ps	20 µs	4 μs	1.8-V CMOS	1.8-V CMOS	3 pF	3.3-6 pF	2.4-4 pF
CD4066	3-18 V	200-1300 Ω	7-40 ns	15-70 ns	15-70 ns	approximately. 0.7 × V _{CC}	approximately . 0.2 × V _{CC}	5-7.5 pF	-	8 pF
CD74HC4066	2-10 V	15-142 Ω	4-90 ns	8-150 ns	12-225 ns	5-V CMOS	5-V CMOS	10 pF	-	5 pF
CD74HCT4066	4.5-5.5 V	25-142 Ω	4-18 ns	4-18 ns	9-36 ns	5-V TTL	5-V TTL	10 pF	_	5 pF
SN74HC4066	2-6 V	30-150 Ω	3-75 ns	18-225 ns	22-250 ns	5-V CMOS	5-V CMOS	3-10 pF	_	9 pF
LVC1G66	1.65-5.5V	3-30 Ω	0.6-2 ns	1.5-10 ns	1.4-10 ns	5-V CMOS	5-V CMOS	2 pF	13 pF	6 pF
LV4066A	2-5.5 V	21-225 Ω	0.3-18 ns	1.6-32 ns	3.2-32 ns	5-V CMOS	5-V CMOS	1.5 pF	_	5.5 pF
CBT3125	4-5.5 V	5-22 Ω	0.25-0.35 ns	1.8-5.6 ns	1-4.6 ns	5-V TTL/LVTTL	5-V TTL/ LVTTL	3 pF	-	4 pF
CBTLV3125	2.3-3.6 V	5-40 Ω	0.15-0.25 ns	2-4.6 ns	1-4.2 ns	LVTTL/2.5-V CMOS	LVTTL/ 2.5-V CMOS	2.5 pF	_	7 pF

⁽¹⁾ Data are based on data-sheet parameters for the parts tested for this application report. Refer to the respective data sheets for specific parameters and load conditions.

- (3) t_{ON} is the same as t_{PZL}/t_{PZH}.
- (4) t_{OFF} is the same as t_{PLZ}/t_{PHZ} .

⁽²⁾ t_{pd} is the same as t_{PLH}/t_{PHL}. The switch contributes no significant propagation delay other than the RC delay of the typical on-state resistance of the switch and the load capacitance when driven by an ideal voltage source (zero output impedance).

www.ti.com Applications

7 Applications

The examples below show some common applications of signal switches and multiplexers:

7.1 SPI Multiplexing

Common applications that require the features of the multiplexer like the TMUX1574 and SN3257-Q1 include multiplexing various protocols from a possessor or MCU such as SPI, eMMC, I2S, or standard GPIO signals. These devices provides superior isolation performance when the device is powered. The added benefit of powered-off protection allows a system to minimize complexity by eliminating the need for power sequencing in hot-swap and live insertion applications. The example shown in Figure 7-1 illustrates the use of the SN3257-Q1 to multiplex an SPI bus to multiple flash memory devices.

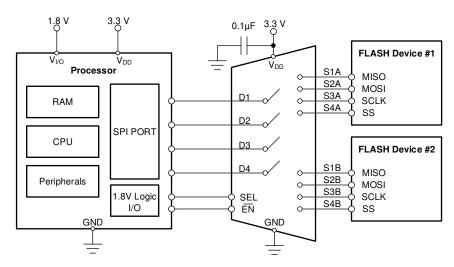


Figure 7-1. Multiplexing Flash Memory

One useful application of multiplexers is isolating various protocols from a possessor or MCU such as JTAG, SPI, or standard GPIO signals. Switch like the TMUX1511 provides excellent isolation performance when the device is powered. The added benefit of powered-off protection allows a system to minimize complexity by eliminating the need for power sequencing in hot-swap and live insertion applications

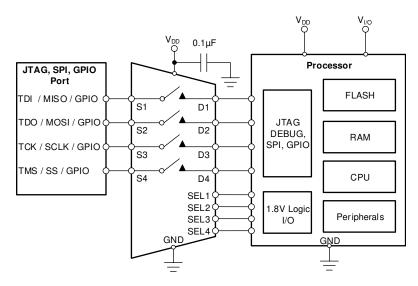


Figure 7-2. Isolation of JTAG, SPI, and GPIO Signals

Applications INSTRUMENTS

www.ti.com

7.2 Multiplexing Signals to External ADC

Figure 7-3 shows a 16-bit, 4 input, multiplexed, data-acquisition system. This example is typical in industrial applications that require low distortion for precision measurements. The circuit uses the ADS8864, a 16-bit, 400- kSPS successive-approximation-resistor (SAR) analog-to-digital converter (ADC), along with a precision amplifier, and a 4 input multiplexer (TMUX1104).

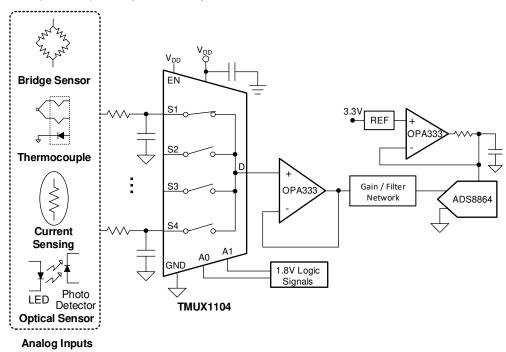


Figure 7-3. Multiplexing Signals to External ADC

www.ti.com Applications

7.3 Multiplexing Signals to External ADC in Fault Sensitive Conditions

In analog input programmable logic controllers (PLC) a multiplexer is often used to switch multiple sensors to a single ADC. By using a multiplexer, the number of components in the system can be reduced to save system cost and size. In a PLC module a ±10 V input signal range is common for interfacing with external field transmitters and sensors; however, there are a number of fault cases that may occur that can be damaging to many of the integrated circuits. Such fault conditions may include, but are not limited to, human error from wiring connections incorrectly, component failure or wire shorts, electromagnetic interference (EMI) or transient disturbances, and so forth.TMUX7308F is an appropriate multiplexer for protected downstream devices from such fault conditions.

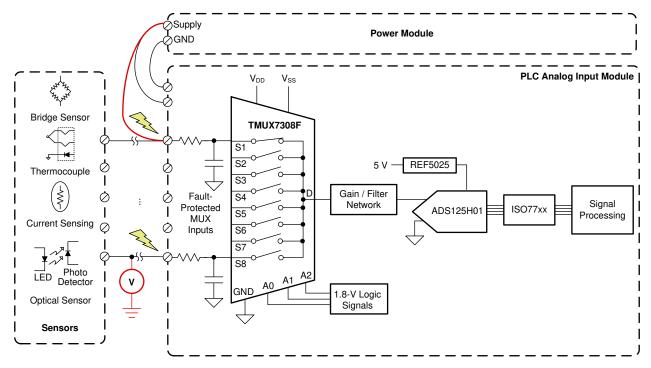


Figure 7-4. Multiplexing Signals to External ADC in Fault Sensitive Conditions

7.4 Switchable Op Amp Gain Setting

One example application of the multiplexer is to change an Op Amp from unity gain setting to an inverting amplifier configuration. Utilizing a switch like the TMUX1219 allows a system to have a configurable gain and allows the same architecture to be utilized across the board for various inputs to the system.

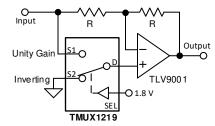


Figure 7-5. Switchable Op Amp Gain Setting

Applications INSTRUMENTS

www.ti.com

7.5 Multiplexing Body Control Module (BCM) Inputs

Automotive BCMs are complex systems designed to manage numerous functions such as lighting, door locks, windows, wipers, turn signals and many more inputs. The BCM monitors these physical switches and controls power to various loads within the vehicle. A CMOS multiplexer can be used to multiplex the inputs and minimize the number of GPIO or ADC inputs needed by an onboard MCU. The TMUX1308-Q1 features multiplexing various physical switches in a body control module (BCM) or electronic control unit (ECU). Figure 7-1 shows a typical BCM system using the TMUX1308-Q1 to multiplex system inputs.

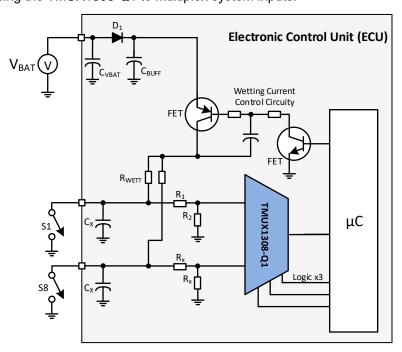


Figure 7-6. Multiplexing BCM Inputs

www.ti.com Applications

7.6 High Current Range Selection Using External Resistor

One example to take advantage of the precision performance of devices such as the TMUX721x which provide higher current support is the implementation of parametric measurement unit (PMU) in the semiconductor automatic test equipment (ATE) application.

In Automated Test Equipment (ATE) systems, the Parametric Measurement Unit (PMU) is tasked to measure device (DUT) parametric information in terms of voltage and current. When measuring voltage, current is applied at the DUT pin, and current range adjustment can be done through changing the value of the internal sense resistor. There is sometimes a need, depending on the DUT, to use even higher testing current than natively supported by the system. A 4 channel SPST switch, together with external higher current amplifier and resistor, can be used to achieve the flexibility. The PMU operating voltage is typically in mid voltage (up to 20 V). An appropriate switch like the TMUX721x with low leakage current (0.05 nA typical) works well in these applications to ensure measurement accuracy and low RON and flat RON_FLATNESS allows the current range to be controlled more precisely. Below shows a simplified diagram of such implementations in memory and semiconductor test equipment.

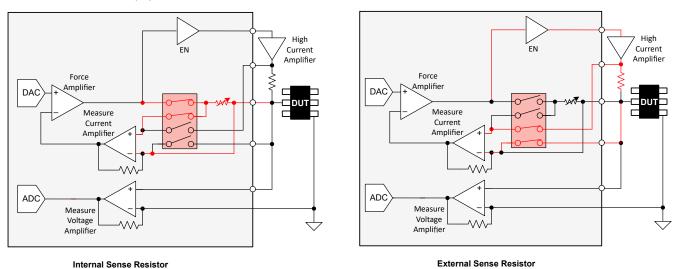


Figure 7-7. High Current Range Selection Using External Resistor

7.7 Fault Protection in Factory Automation Control Systems

The need to monitor remote sensors is common among factory automation control systems. For example, an analog input module or mixed module (AI, AO, DI, and DO) of a programmable logic controller (PLC) will interface to a field transmitter to monitor various process sensors at remote locations around the factory. A switch or multiplexer, such as the TMUX7462F, is often used to connect multiple inputs from the system and reduce the number of downstream channels.

There are a number of fault cases that may occur that can be damaging to many of the integrated circuits. Such fault conditions may include, but are not limited to, human error due to miswiring, component failure, wire shorts, electromagnetic interference (EMI), transient disturbances, and more.



Applications www.ti.com

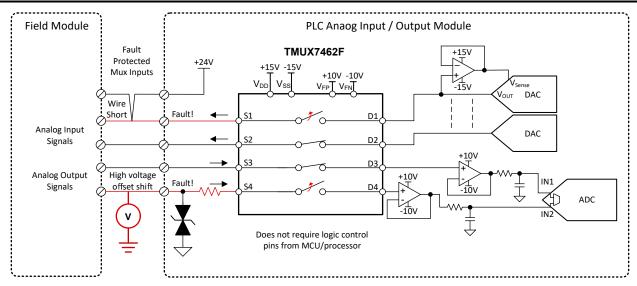


Figure 7-8. Fault Protection in Factory Automation Control Systems

7.8 Sample and Hold Circuitry

One useful application to take advantage precision performance in devices such as the TMUX6121, TMUX6122, and TMUX6123 is the sample and hold circuit. A sample and hold circuit can be useful for an analog to digital converter (ADC) to sample a varying input voltage with improved reliability and stability. It can also be used to store the output samples from a single digital-to-analog converter (DAC) in a multi-output application. A simple sample and hold circuit can be realized using an analog switch like one of the TMUX6121, TMUX6122, and TMUX6123 analog switches.

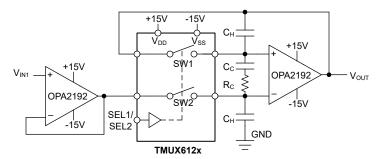


Figure 7-9. A Sample and Hold Circuit Realized Using the TMUX611x Analog Switch

www.ti.com Summary

8 Summary

Factors that go into selecting a signal switch can be numerous (low r_{on} , low leakage, channel count, switch configuration, powered- off protection, and so forth). This application report has presented the various TI signal-switch architecture, highlighted the key features and examples of protection, precision and general-purpose switches and multiplexers to support end-to-end signal chain needs and provided example applications of switches to aid the designer in selecting the right TI signal switch.

9 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

C	hanges from Revision D (December 2021) to Revision E (June 2022)	Page
•	Updated <i>Application Note</i> with new TMUX40xx (TMUX4051, TMUX4052, TMUX4053) signal switches multiplexers	
_ С	hanges from Revision C (August 2021) to Revision D (December 2021)	Page
•	Updated Behavioral Model of CMOS (FET) Switch title	
	Added CF description	
	Updated Digital and Analog switch definitions	
	Deleted Bus Switch definition	
•	Updated topic title	
•	Updated with newer devices throughout publication	
•	Added Integrated Pulldown on Logic Pins topic	
•	Updated with newer devices throughout publication	
•	Updated Source and Drain on Capacitance image	
•	Added Latch-up Immunity	
•	Updated Propagation Delay definition	
•	Updated Fail-safe logic with example devices	
•	Updated Analog Precision Switches and Multiplexers table	
•	Updated Protection Switches and Multiplexers topic adding new protection devices	
•	Updated Analog Protection Switches and Multiplexers table	
•	Updated General-Purpose Switches and Multiplexers table	<mark>22</mark>
•	Updated Automotive Switches and Multiplexers – AECQ100 table	23
•	Updated Switches and Multiplexers Performance in Digital Signal Applications title	
•	Added Multiplexing Signals to External ADC topic	26
•	Added Multiplexing Signals to External ADC in Fault Sensitive Conditions topic	
•	Added High Current Range Selection Using External Resistor topic	<mark>2</mark> 9
•	Added Fault Protection in Factory Automation Control Systems topic	<mark>2</mark> 9
•	Added Sample and Hold Circuitry topic	30
С	hanges from Revision B (April 2020) to Revision C (August 2021)	Page
•	Updated the numbering format for tables, figures, and cross-references throughout the publication	4
С	hanges from Revision A (March 2020) to Revision B (April 2020)	Page
•	Updated Figure 27: Switchable Op Amp Gain Setting	27
С	hanges from Revision * (October 2001) to Revision A (March 2020)	Page
•	Updated Application Note with new TMUX signal switches and multiplexers	1

Appendix A www.ti.com

A Appendix A

A.1 Analog Performance - CD, HC, CBT, LVC, and LV

Table A-1. V_{CC} Above 5.5 V

Parameter (1)	Better Performance		
R _{ON}	CD74HC4066	CD74HC4066 ⁽²⁾	CD4066
(typical to maximum)	15-126 Ω	30 Ω	200-550 Ω
R _{ON} (peak)	SN74HC4066 ⁽²⁾	CD74HC4066	CD4066
(typical to maximum)	50 Ω (typical)	not specified	not specified
Frequency response	CD74HC4066 ⁽³⁾	CD4066	SN74HC4066 ⁽³⁾
	200 MHz	40 MHz	30 MHz
THD/Sine-wave distortion	CD74HC4066	SN74HC4066 ⁽³⁾	CD4066
	0.008%	0.05%	0.4%
Crosstalk	SN74HC4066	CD4066	CD74HC4066
(enable to output)	20 mV	50 mV	550 mV
Crosstalk	CD4066	CD74HC4066 ⁽³⁾	SN74HC4066 ⁽³⁾
(between switches)	-50 dB at 8 MHz	-72 dB at 1 MHz	-45 dB at 1 MHz
Feedthrough attenuation	CD74HC4066 ⁽³⁾	CD4066	SN74HC4066 ⁽³⁾
	-72 dB at 1 MHz	-50 dB at 1 MHz	-42 dB at 1 MHz

- (1) Data are based on data-sheet parameters for the parts tested for this application report. Refer to the respective data sheets for specific parameters and load conditions.
- (2) Specification at V_{CC} = 6 V.
- (3) Specification at $V_{CC} = 4.5 \text{ V}$.

Table A-2. $V_{CC} = 4.5 \text{ V}$

Table A-2. V _{CC} = 4.5 V								
Parameter (1)	Better Performance							
R _{ON} (typical to maximum)	LVC1G66 3-10 Ω	CBT3125 ⁽²⁾ 5-15 Ω	LV4066A 21-100 Ω	CD74HC/ HCT4066 25-142 Ω	SN74HC4066 50-106 Ω	CBT3125 ⁽³⁾ 5-1000 Ω		
R _{ON} (peak) (typical to maximum)	CBT3125 ^{(2) (3)} 10 Ω	LVC1G66 6-15 Ω	LV4066A 31-125 Ω	CD74HC/ HCT4066 ⁽³⁾ 50-70 Ω	SN74HC4066 70-215 Ω	CBT3125 ⁽³⁾ 1000 Ω		
Frequency response	CBT3125 ⁽²⁾ (3) >200 MHz	LVC1G66 195 MHz	CD74HC/ HCT4066 ⁽⁴⁾ 200 MHz	LV4066A 50 MHz	SN74HC4066 30 MHz			
THD/Sine-wave distortion	LVC1G66 0.01%	CD74HC/ HCT4066 0.023%	CBT3125 ^{(2) (3)} 0.035%	SN74HC4066 0.05%	LV4066A 0.1%			
Crosstalk (enable to output)	SN74HC4066 15 mV	LV4066A 50 mV	LVC1G66 100 mV	CBT3125 ⁽³⁾ 120 mV	CD74HCT4066 130 mV	CD74HC4066 200 mV		
Crosstalk (between switches)	CD74HC/HCT4066 -72 dB	LVC2G66 -58 dB	CBT3125 ⁽²⁾ (3) -53 dB	SN74HC4066 -45 dB	LV4066A -45 dB			
Feedthrough attenuation	CD74HC/HCT4066 -72 dB	LVC1G66 -58 dB	SN74HC4066 -42 dB	LV4066A -40 dB	CBT3125 ⁽³⁾ -36 dB			

- (1) Data are based on data-sheet parameters for the parts tested for this application report. Refer to the respective data sheets for specific parameters and load conditions.
- (2) CBT3125, $0 \le V_{I/O} \le (V_{CC} 2 V)$.
- (3) Value from application report measurement. Not specified in data sheet.
- (4) Ranked here due to load variation from other devices in this report.

Table A-3. $V_{CC} = 3 V$

Parameter (1)	Better Performance				
R _{ON} (typical to maximum)	LVC1G666-15 Ω	CBTLV31255-15 Ω	LV4066A29-190 Ω	CD74HC4066 ⁽²⁾ Not specified	SN74HC4066 ⁽²⁾ Not specified
R _{ON} (peak)(typical to maximum)	CBTLV3125 ⁽³⁾ 15-20 Ω	LVC1G6612-20 Ω	LV4066A57-225 Ω	CD74HC4066 ⁽²⁾ Not specified	SN74HC4066 ⁽²⁾ Not specified
Frequency response	CBTLV3125 ⁽³⁾ >200 MHz	LVC1G66175 MHz	CD74HC4066 ⁽²⁾ Not specified	LV4066A35MHz	SN74HC4066 ⁽¹⁾ Not specified

www.ti.com Appendix A

Table A-3. $V_{CC} = 3 V$ (continued)

Parameter (1)	Better Performance				
THD/Sine-wave distortion	LVC1G660.015%	CD74HC4066 ⁽²⁾ Not specified	SN74HC4066 ⁽²⁾ Not specified	CBTLV3125 ⁽³⁾ 0.09%	LV4066A0.1%
Crosstalk(enable to output)	SN74HC4066 ⁽²⁾ Not specified	LV4066A20 mV	LVC1G6670 mV	CBTLV3125 ⁽³⁾ 70 mV	CD74HC4066 ⁽²⁾ Not specified
Crosstalk(between switches)	CD74HC4066 ⁽²⁾ Not specified	LVC2G66-58 dB	CBTLV3125 ⁽³⁾ -49 dB	SN74HC4066 ⁽²⁾ Not specified	LV4066A-45 dB
Feedthrough attenuation	CD74HC4066 ⁽²⁾ Not specified	LVC1G66-58 dB	CBTLV3125-52 dB	SN74HC4066 ⁽²⁾ Not specified	LV4066A-40 dB

- (1) Data are based on data-sheet parameters for the parts tested for this application report. Refer to the respective data sheets for specific parameters and load conditions.
- (2) Position in table based on estimated performance. Information not specified in data sheet.
- (3) Value from application report measurement. Not specified in data sheet.

Table A-4. $V_{CC} = 2.5 V$

Parameter (1)	Better Performance				
R _{ON} (typical to maximum)	LVC1G66	CBTLV3125	LV4066A	CD74HC4066 ⁽²⁾	SN74HC4066 ⁽³⁾
	9-20 Ω	5-40 Ω	38-225 Ω	Not specified	150 Ω
R _{ON} (peak)(typical to maximum)	CBTLV3125 ⁽⁴⁾	LVC1G66	LV4066A	CD74HC4066 ⁽²⁾	SN74HC4066 ⁽³⁾
	15-45 Ω	20-30 Ω	143-600 Ω	Not specified	320 Ω
Frequency response	CBTLV3125 ⁽⁴⁾	LVC1G66	CD74HC4066 ⁽²⁾	LV4066A	SN74HC4066 ⁽²⁾
	>200 MHz	120 MHz	Not specified	30 MHz	Not specified
THD/Sine-wave distortion	LVC1G66	CD74HC4066 ⁽²⁾	SN74HC4066 ⁽²⁾	LV4066A	CBTLV3125 ⁽⁴⁾
	0.025%	Not specified	Not specified	0.1%	0.11%
Crosstalk(enable to output)	SN74HC4066 ⁽²⁾	LV4066A	CBTLV3125 ⁽²⁾	LVC1G66	CD74HC4066 ⁽²⁾
	Not specified	15 mV	30 mV	50 mV	Not specified
Crosstalk(between switches)	CD74HC4066 ⁽²⁾	LVC2G66	CBTLV3125	SN74HC4066 ⁽²⁾	LV4066A
	Not specified	-58 dB	-45 dB	Not specified	-45 dB
Feedthrough attenuation	CD74HC4066 ⁽²⁾	LVC1G66	CBTLV3125	SN74HC4066 ⁽²⁾	LV4066A
	Not specified	-58 dB	-52 dB	Not specified	-40 dB

⁽¹⁾ Data are based on data-sheet parameters for the parts tested for this application report. Refer to the respective data sheets for specific parameters and load conditions.

- Position in table based on estimated performance. Information not specified in data sheet.
- (3) Data at $V_{CC} = 2 \text{ V}$.
- (4) Value from application report measurement. Not specified in data sheet.

Appendix A www.ti.com

A.2 SN74CBT Characteristics

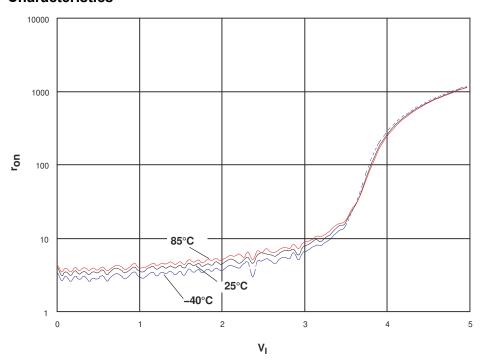


Figure A-1. Log r_{on} vs V_{I} , V_{CC} = 5 V (SN74CBT3125)

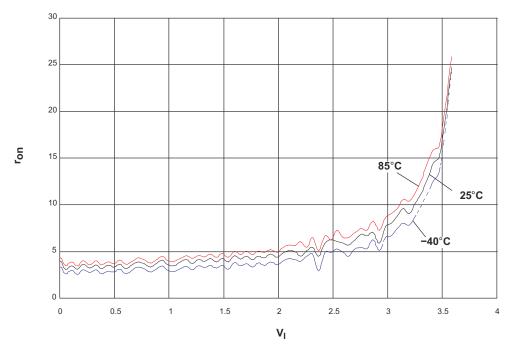


Figure A-2. r_{on} vs V_I, V_{CC} = 5 V (SN74CBT3125)

www.ti.com Appendix A

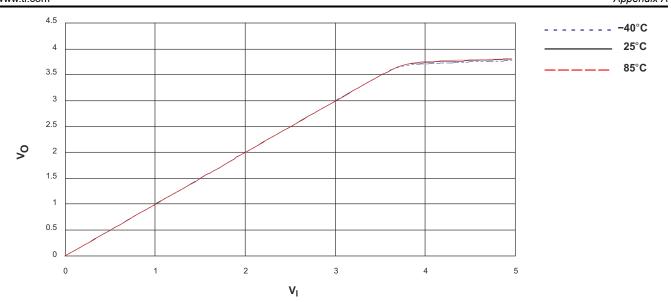


Figure A-3. $V_I vs V_O$, $V_{CC} = 5 V (SN74CBT3125)$

Table A-5. SN74CBT3125 Analog Parameter Measurement Data

V _{CC} (1)	Frequency Response	Sine-Wave Distortion	Total Harmonic Distortion	Crosstalk		Charge Injection	Feedthrough
		1	kHz	Between Switches	Enable to Output	injection	
5 V	>200 MHz	0.035%	0.15%	-53 dB	120 mV	7.2 pC	-36 dB

(1) Postcharacterization measurement for SN74CBT3125

A.3 CD74HCT Characteristics

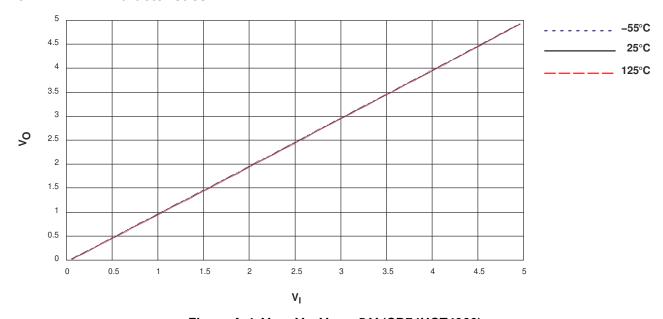


Figure A-4. V_I vs V_O , V_{CC} = 5 V (CD74HCT4066)

Appendix A www.ti.com

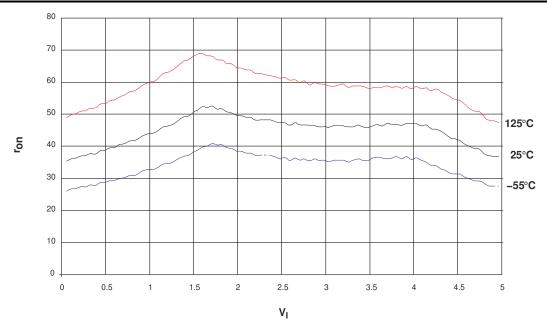


Figure A-5. r_{on} vs V_{I} , V_{CC} = 5 V (CD74HCT4066)

Table A-6. CD74HCT4066 Analog Parameter Measurement Data

V _{CC} (1)	Frequency Response	Total Harmonic Distortion	Crosstalk		Charge Injection ⁽²⁾	Feedthrough	
	Response	1 kHz	Between Switches	Enable to Output			
4.5 V	200 MHz	0.023%	-72 dB	130 mV	8.1 pC	-72 dB	

- (1) Data-sheet values for CD74HCT4066, except as noted.
- (2) Post-characterization measurement for CD74HCT4066.

A.4 CD74HC Characteristics

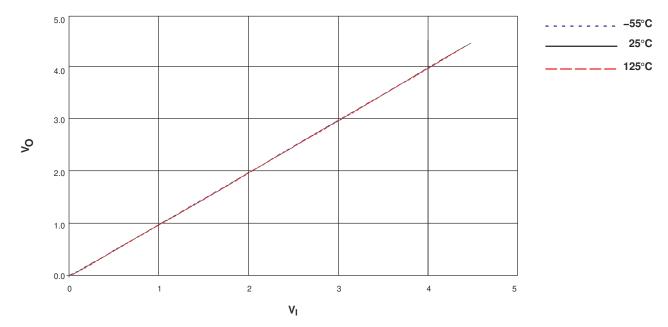


Figure A-6. V_I vs V_O , V_{CC} = 4.5 V (CD74HC4066)

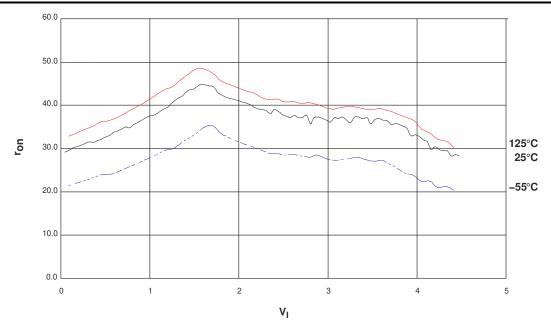


Figure A-7. r_{on} vs V_{I} , V_{CC} = 4.5 V (CD74HC4066)

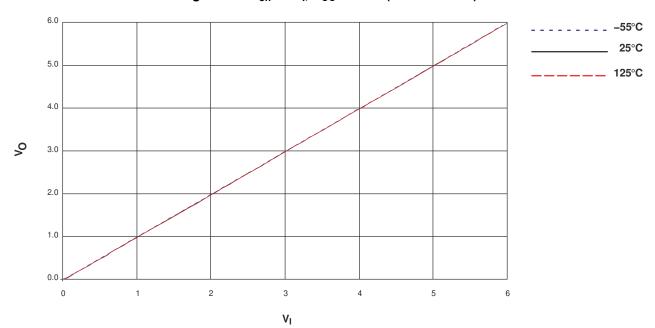


Figure A-8. V_O vs V_I , V_{CC} = 6 V (CD74HC4066)

Appendix A

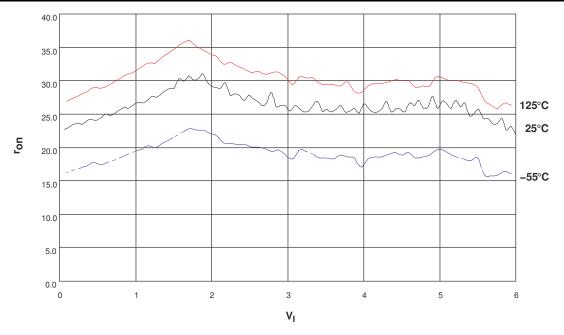


Figure A-9. r_{on} vs V_{I} , V_{CC} = 6 V (CD74HC4066)

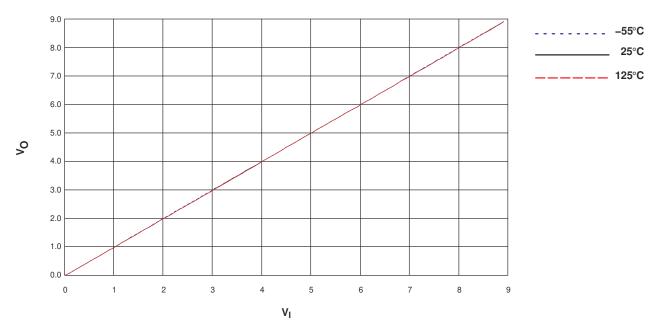


Figure A-10. V_O vs V_I , V_{CC} = 9 V (CD74HC4066)

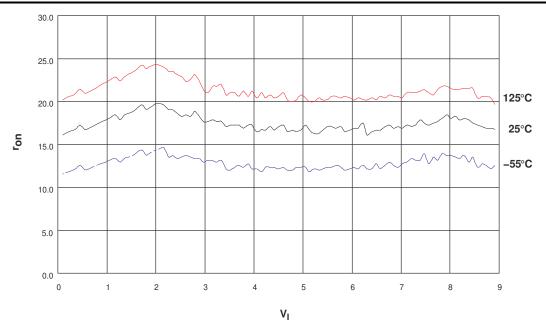


Figure A-11. r_{on} vs V_{I} , V_{CC} = 9 V (CD74HC4066)

Table A-7. CD74HC4066 Analog Parameter Measurement Data

V (1)	Frequency Response	Total Harmonic Distortion	Crosstalk		Charge Injection ⁽²⁾	Feedthrough	
V _{CC} (1)		1 kHz	Between Switches	Enable to Output	Charge injection —	reedinough	
4.5 V	200 MHz	0.022%	-72 dB	200 mV	6.2 pC	-72 dB	
9 V	200 MHz	0.008%	N/A	550 mV	9.0 pC	N/A	

- (1) Data-sheet values for CD74HC4066, except as noted.
- (2) Post characterization measurement for CD74HC4066.

A.5 SN74HC Characteristics

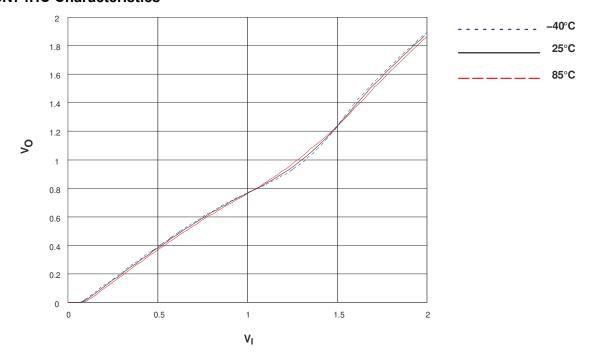


Figure A-12. V_O vs V_I , V_{CC} = 2 V (SN74HC4066)

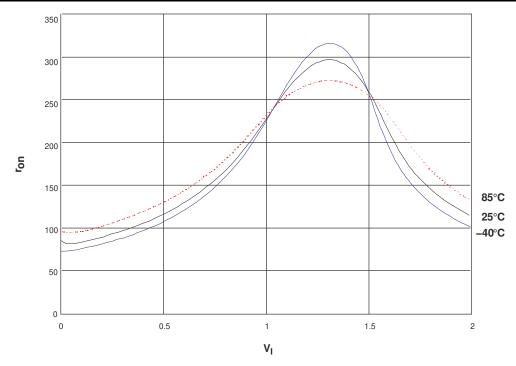


Figure A-13. r_{on} vs V_{I} , V_{CC} = 2 V (SN74HC4066)

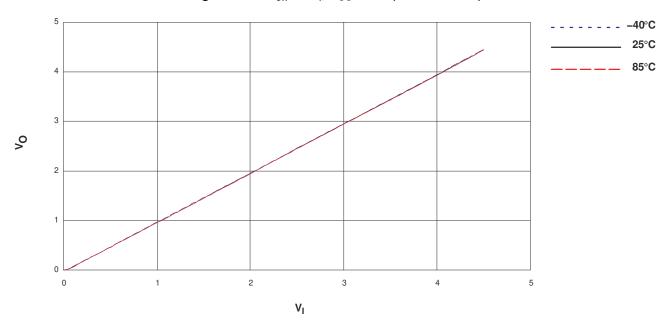


Figure A-14. V_O vs V_I , V_{CC} = 4.5 V (SN74HC4066)

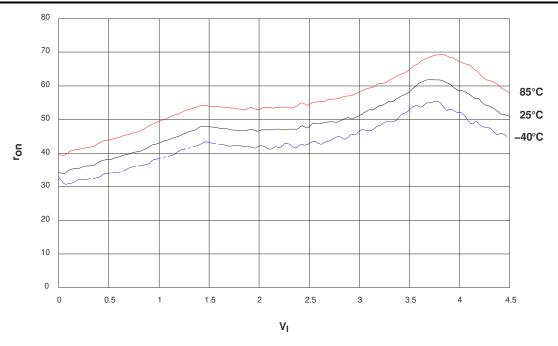


Figure A-15. r_{on} vs V_I, V_{CC} = 4.5 V (SN74HC4066)

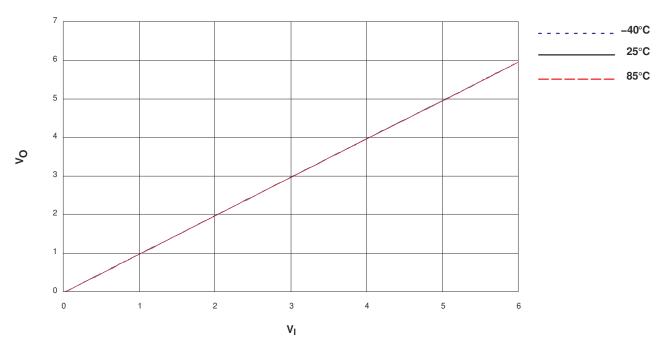


Figure A-16. V_O vs V_I , V_{CC} = 6 V (SN74HC4066)

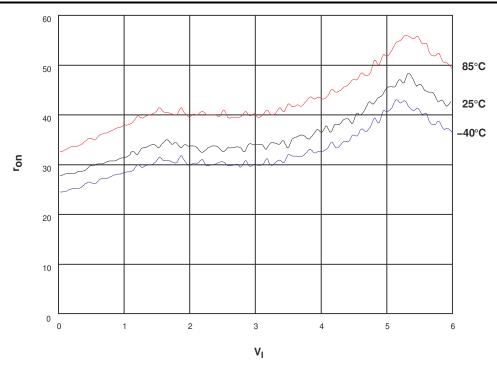


Figure A-17. r_{on} vs V_{I} , V_{CC} = 6 V (SN74HC4066)

Table A-8. SN74HC4066 Analog Parameter Measurement Data

V _{CC} (1)	Frequency	Sine-Wave Distortion	on Crosstalk		Charge Injection ⁽²⁾	Feedthrough	
	CC \ /	Response	1 kHz	Between Switches	Enable to Output		reculiiougii
	2 V	N/A	N/A	N/A	N/A	3.8 pC	N/A
4	1.5 V	30 MHz	0.05%	-45 dB	15 mV	5.9 pC	-42 dB
	6 V	N/A	N/A	N/A	20 mV	7.9 pC	N/A

- (1) Data-sheet values for SN74HC4066, except as noted.
- (2) Post characterization measurement for SN74HC4066.

A.6 CD4066B Characteristics

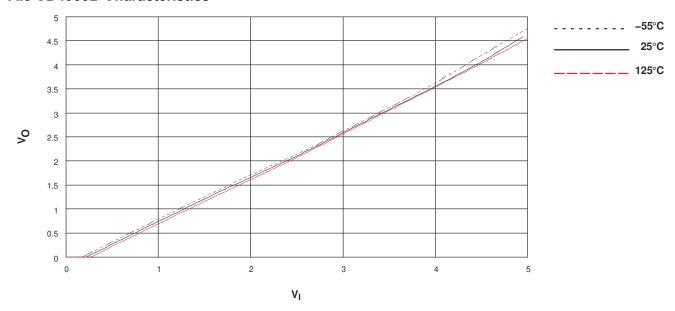


Figure A-18. V_O vs V_I , $V_{CC} = 5 V$ (CD4066B)

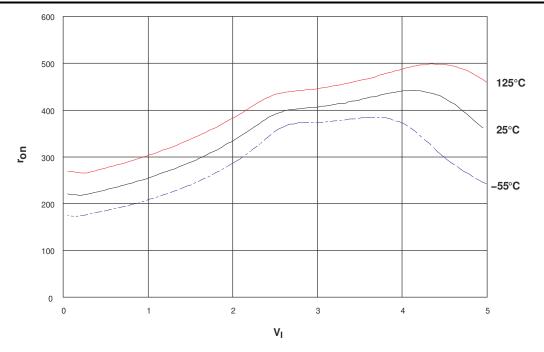


Figure A-19. r_{on} vs V_{I} , V_{CC} = 5 V (CD4066B)

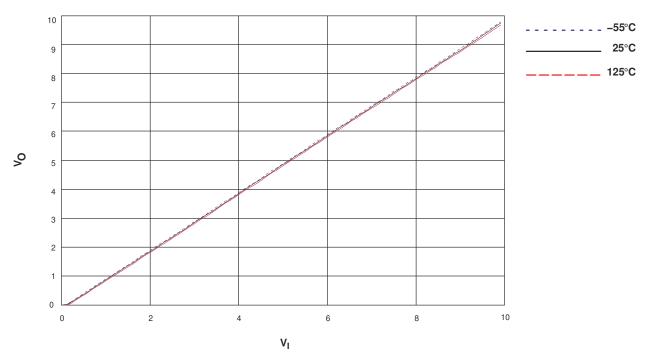


Figure A-20. V_O vs V_I , V_{CC} = 10 V (CD4066B)

Appendix A INSTRUMENTS

www.ti.com

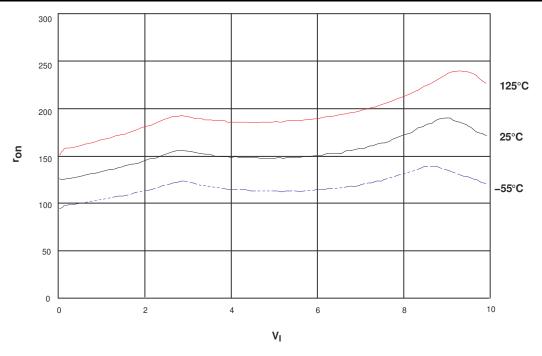


Figure A-21. r_{on} vs V_{I} , V_{CC} = 10 V (CD4066B)

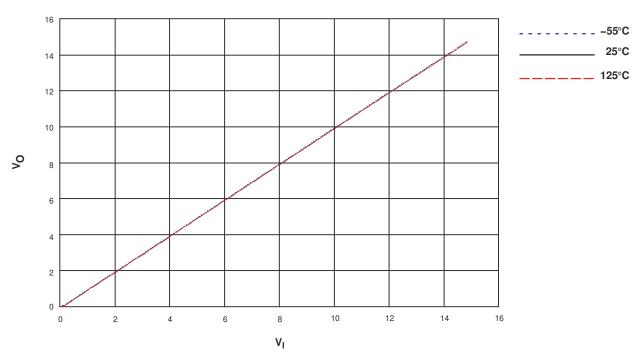


Figure A-22. V_O vs V_I , V_{CC} = 15 V (CD4066B)

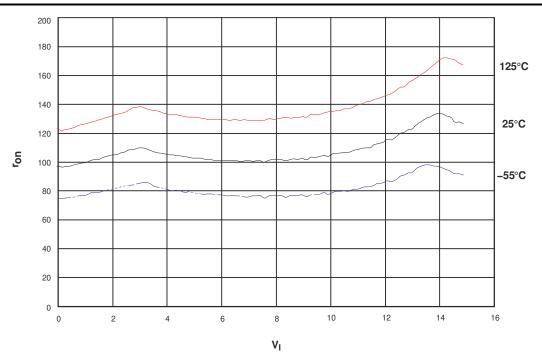


Figure A-23. r_{on} vs V_{I} , V_{CC} = 15 V (CD4066B)

Table A-9. CD4066B Analog Parameter Measurement Data

V N (1)	Frequency Response	Total Harmonic Distortion	Crosstalk		Charge	Feedthrough
V _{CC} /V _{SS} ⁽¹⁾		1 kHz	Between Switches	Enable to Output	Injection ⁽²⁾	i eediiii dugii
5 V/-5 V	40 MHz	0.04%	-50 dB at 8 MHz	50 mV		-50 dB at 1 MHz
10 V/0 V	141 MHz ⁽²⁾	0.032%(2)	-75 dB ⁽²⁾	35 mV ⁽²⁾	18.8 pC	-65 dB ⁽²⁾

⁽¹⁾ Data-sheet values for CD4066B, except as noted.

⁽²⁾ Post characterization measurement for CD4066B. Frequency response, THD, crosstalk, and feedthrough measured using load conditions specified in Appendix A, in order to make a more valid comparison with other devices in this report.

Appendix A

A.7 LV-A Characteristics

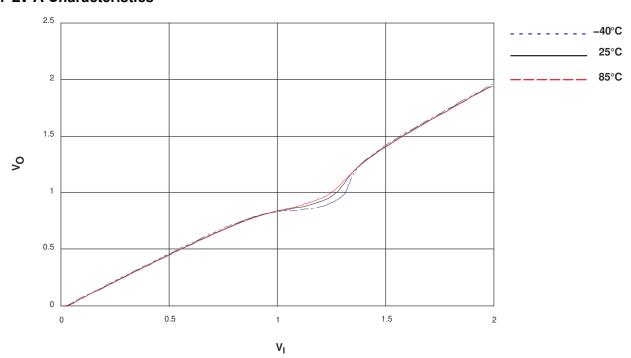


Figure A-24. V_O vs V_I , V_{CC} = 2 V (SN74LV4066A)

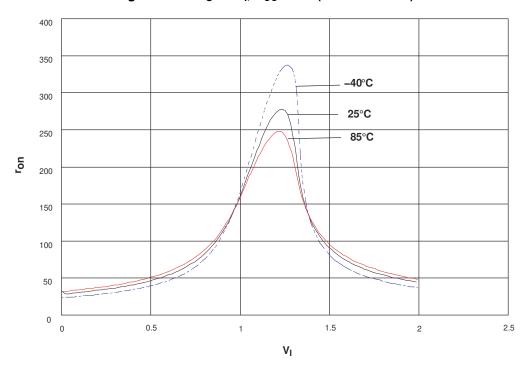


Figure A-25. r_{on} vs V_{I} , V_{CC} = 2 V (SN74LV4066A)

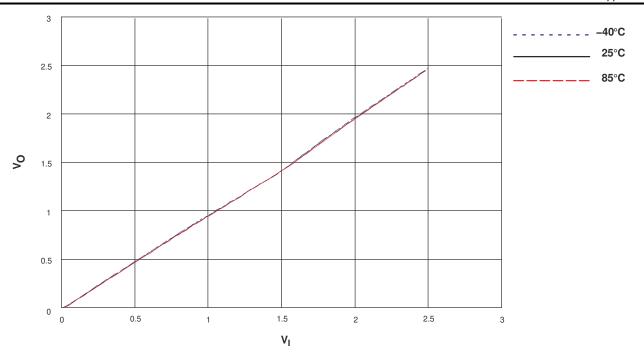


Figure A-26. V_O vs V_I , V_{CC} = 2.5 V (SN74LV4066A)

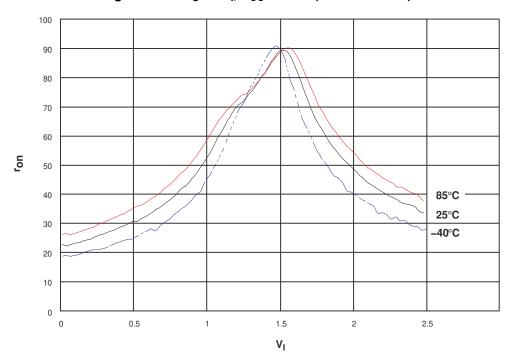


Figure A-27. r_{on} vs V_{I} , V_{CC} = 2.5 V (SN74LV4066A)

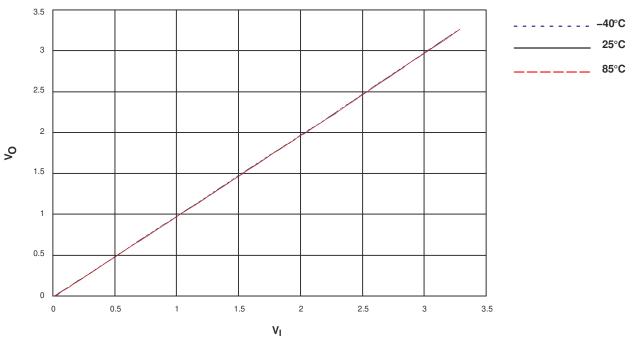


Figure A-28. V_O vs V_I , V_{CC} = 3.3 V (SN74LV4066A)

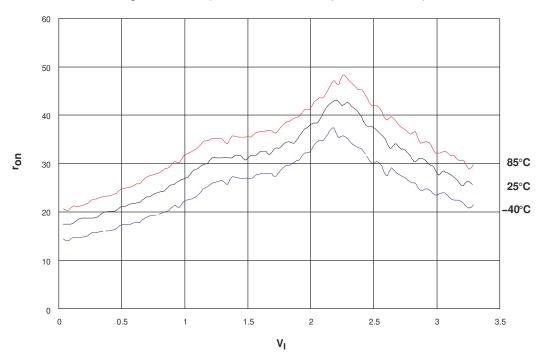


Figure A-29. r_{on} vs V_I, V_{CC} = 3.3 V (SN74LV4066A)

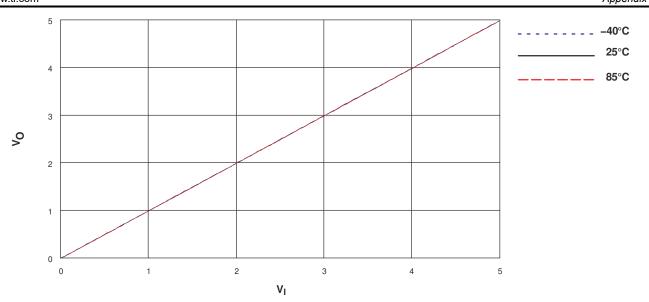


Figure A-30. V_O vs V_I , V_{CC} = 5 V (SN74LV4066A)

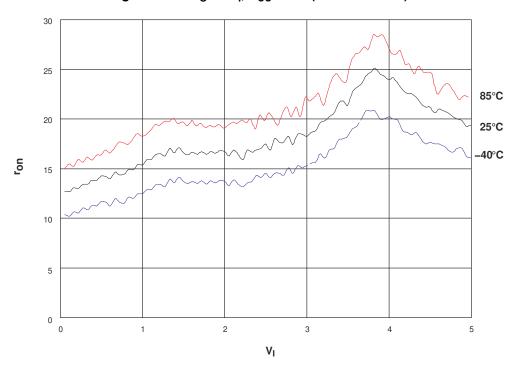


Figure A-31. r_{on} vs V_{I} , V_{CC} = 5 V (SN74LV4066A)

Table A-10. SN74LV4066A Analog Parameter Measurement Data

V _{CC} (1) Frequency		Sine-Wave Distortion	tion Crosstalk		ve Distortion Crosstalk		Charge	Feedthrough
V CC \	Response 1 kHz		Between Switches	Enable to Output	Injection ⁽²⁾	i ecutillough		
2.3 V	30 MHz	0.1%	-45 dB	15 mV	2.1 pC	-40 dB		
3 V	35 MHz	0.1%	-45 dB	20 mV	2.7 pC	-40 dB		
4.5 V	50 MHz	0.1%	-45 dB	50 mV	3.0 pC	-40 dB		

- (1) Data-sheet values for SN74LV4066A, except as noted.
- (2) Post characterization measurement for SN74LV4066A.

A.8 LVC Characteristics

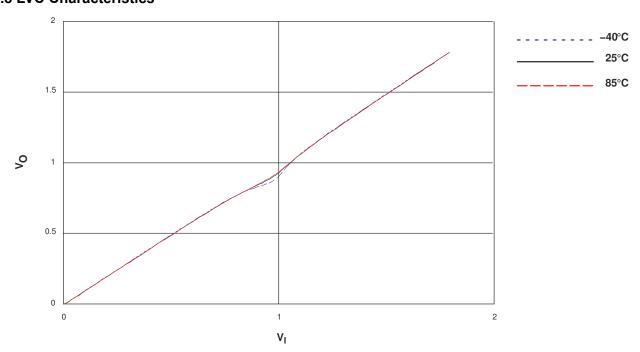


Figure A-32. V_O vs V_I , V_{CC} = 1.8 V (SN74LVC1G66)

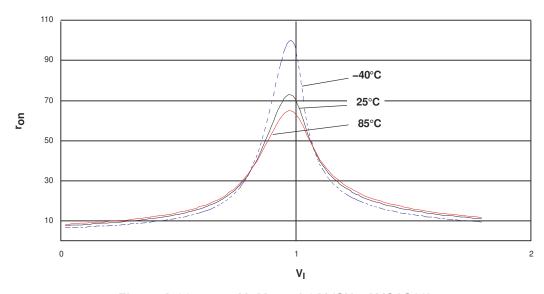


Figure A-33. r_{on} vs V_{I} , V_{CC} = 1.8 V (SN74LVC1G66)

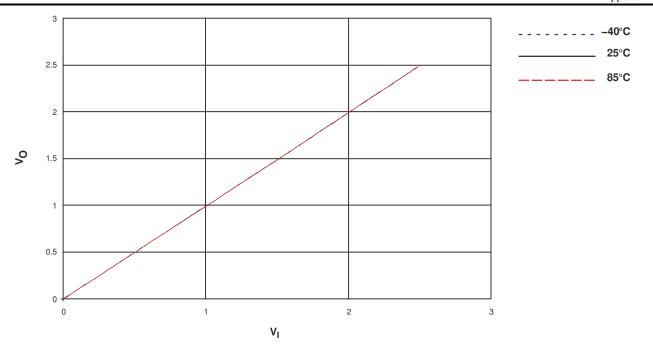


Figure A-34. V_O vs V_I , V_{CC} = 2.5 V (SN74LVC1G66)

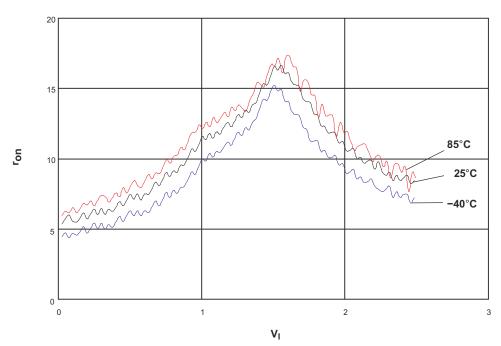


Figure A-35. r_{on} vs V_{I} , V_{CC} = 2.5 V (SN74LVC1G66)

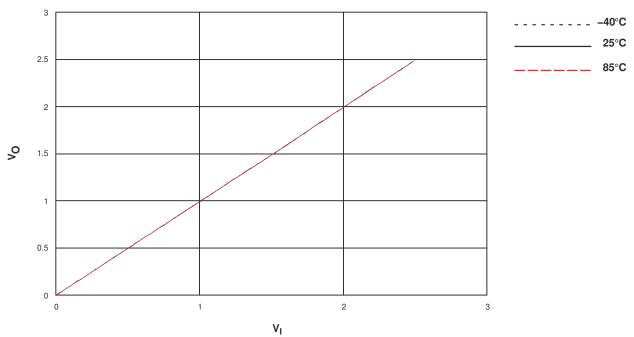


Figure A-36. V_O vs V_I , V_{CC} = 3.3 V (SN74LVC1G66)

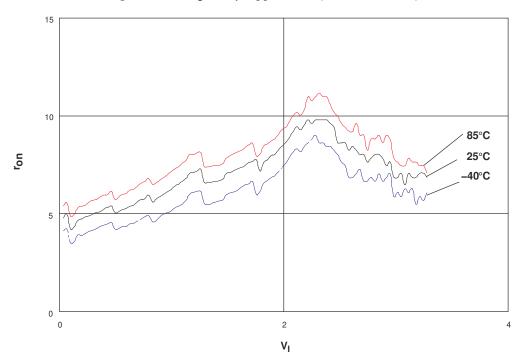


Figure A-37. r_{on} vs V_{I} , V_{CC} = 3.3 V (SN74LVC1G66)

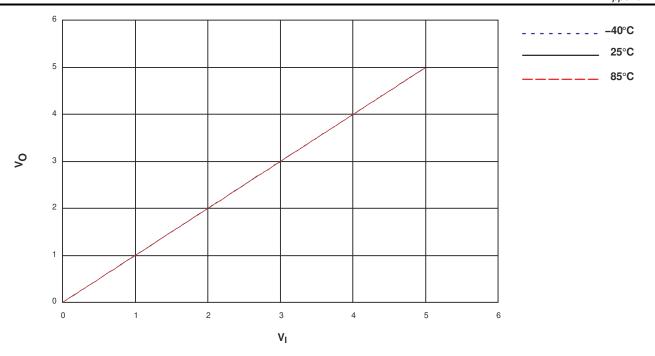


Figure A-38. V_O vs V_I , V_{CC} = 5 V (SN74LVC1G66)

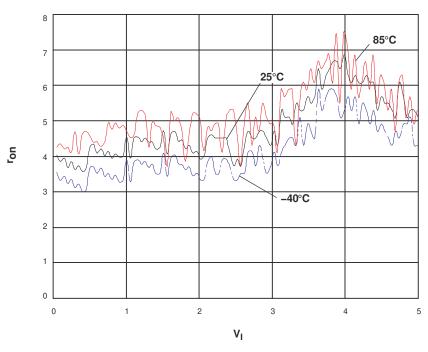


Figure A-39. r_{on} vs V_{I} , V_{CC} = 5 V (SN74LVC1G66)

Table A-11. SN74LVC1G66 Analog Parameter Measurement Data

V _{CC} (1)	Frequency Response	Sine-Wave Distortion		CrosstalkEnable to	Charge	Feedthrough
V CC \ /		1 kHz	10 kHz	Output	Injection ⁽²⁾	recumougn
1.8 V	V 35 MHz 0.1% 0.15%		0.15%	35 mV	2.5 pC	-42 dB
2.5 V	120 MHz	0.025%	0.025%	50 mV	3.0 pC	-42 dB
3 V	175 MHz	0.015%	0.015%	70 mV	3.3 pC	-42 dB
4.5 V	195 MHz	0.01%	0.01%	100 mV	3.5 pC	-42 dB

⁽¹⁾ Data-sheet values for SN74LVC1G66, except as noted.

⁽²⁾ Post characterization measurement for SN74LVC1G66.



A.9 CBTLV Characteristics

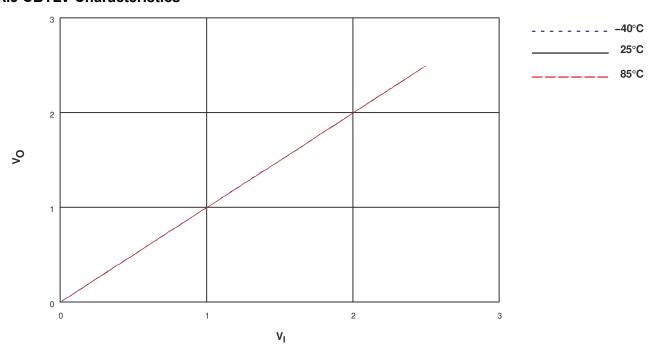


Figure A-40. V_O vs V_I , V_{CC} = 2.5 V (SN74CBTLV3125)

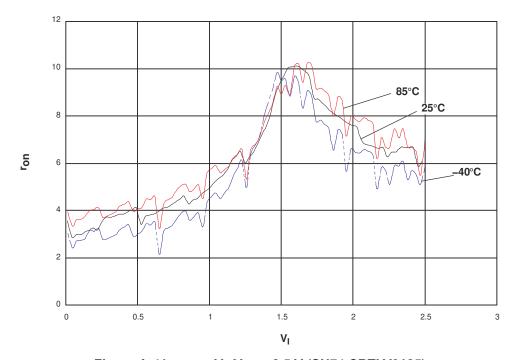


Figure A-41. r_{on} vs V_{I} , V_{CC} = 2.5 V (SN74 CBTLV3125)

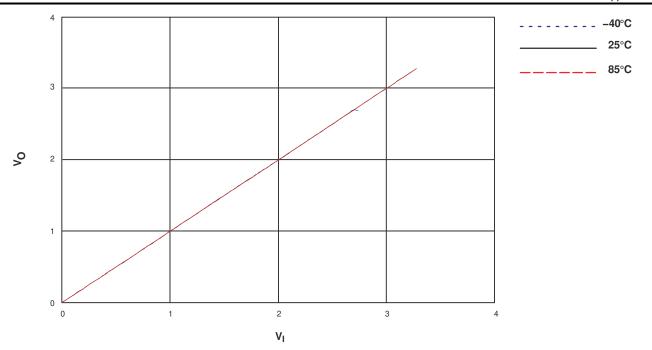


Figure A-42. V_O vs V_I , V_{CC} = 3.3 V (SN74CBTLV3125)

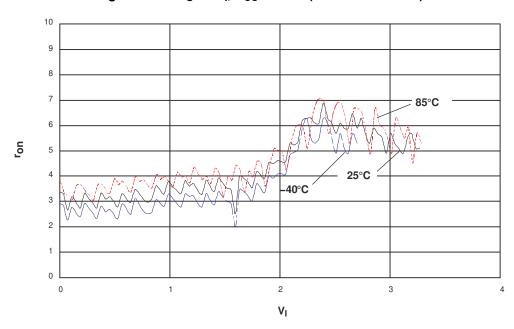


Figure A-43. r_{on} vs V_{I} , V_{CC} = 3.3 V (SN74CBTLV3125)

Table A-12. SN74CBTLV3125 Analog Parameter Measurement Data

	V _{CC} (1)	Frequency Response	Sine-Wave Distortion	Total Harmonic Distortion	Cross	stalk	Charge Injection	Feedthrough	
		Response	1 kHz	1 kHz	Between Switches Enable to Output		injection		
	2.5 V	>200 MHz	0.089%	0.11%	-45 dB	30 mV	12.1 pC	-52 dB	
	3.3 V	>200 MHz	0.033%	0.09%	-49 dB	70 mV	15.5 pC	-52 dB	

(1) Post characterization measurement for CBTLV3125.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2022, Texas Instruments Incorporated