

Application Examples for the CDCUx877x PLL Family

*Christian Schmoeller**CDC - Clock Distribution Circuits*

ABSTRACT

This application report provides examples of how to use the PLLs of the CDCUx877x family.

The CDCUx877x PLLs are designed for use on the DDR2 Registered Dual Inline Memory Modules (RDIMM). A differential input clock is required. The PLLs distributes 10 differential clock outputs to DDR2 DRAMs or Registers.

This report provides information on the use of the PLL as zero delay buffer, as a simple 1:10 buffer, and on how to handle the differential output signal if only a single-ended clock signal is needed.

Contents

1	Application as Zero-Delay-Buffer	2
2	Application as 1:10 Clock Buffer.....	3
3	Switching Into Bypass Mode	3
4	Using Differential Outputs for Single Ended Inputs	4
5	References	4

List of Figures

1	Principle Use of the CDCUx877x PLL on RDIMM Modules	2
2	The CDCUx877x Used as 1:10 Clock Buffer	3
3	Example Circuit for Switching PLL Into Bypass Mode.....	3
4	Example Termination for Differential Signal That Drives a Single-Ended Input Stage	4

1 Application as Zero-Delay-Buffer

The CDCUx877x PLL family is used as a zero-delay-clock buffer on RDIMM modules.

It receives a differential clock from a Memory Controller, and distributes 10 differential clock outputs to 9, 18, or 32 DRAMs and 1, 2, or 4 Registers. In custom designs, any other combination is possible. This principle use is shown in Figure 1.

To get a Zero delay buffer, the delay of all the differential clock outputs (to DRAMs and Registers) and the delay of the Feedback path must be matched. If this is the case, there is ZERO DELAY between Point 1), 2), 3) and 4) in Figure 1. Then, the clock signals at these points have the same phase.


To avoid violating the setup and hold timings at the register inputs, the delay of the differential input clock (A in Figure 1) and the pre register Address/Command signals (F in Figure 1) must also be matched.

Note: Align the delay of different signals by aligning the trace length or/and using tuning capacitors.

CAUTION

When using the PLL as zero delay buffer, the user must take care that the delays of the following Signals from Figure 1 are matched:

B = C (= D) and A = F

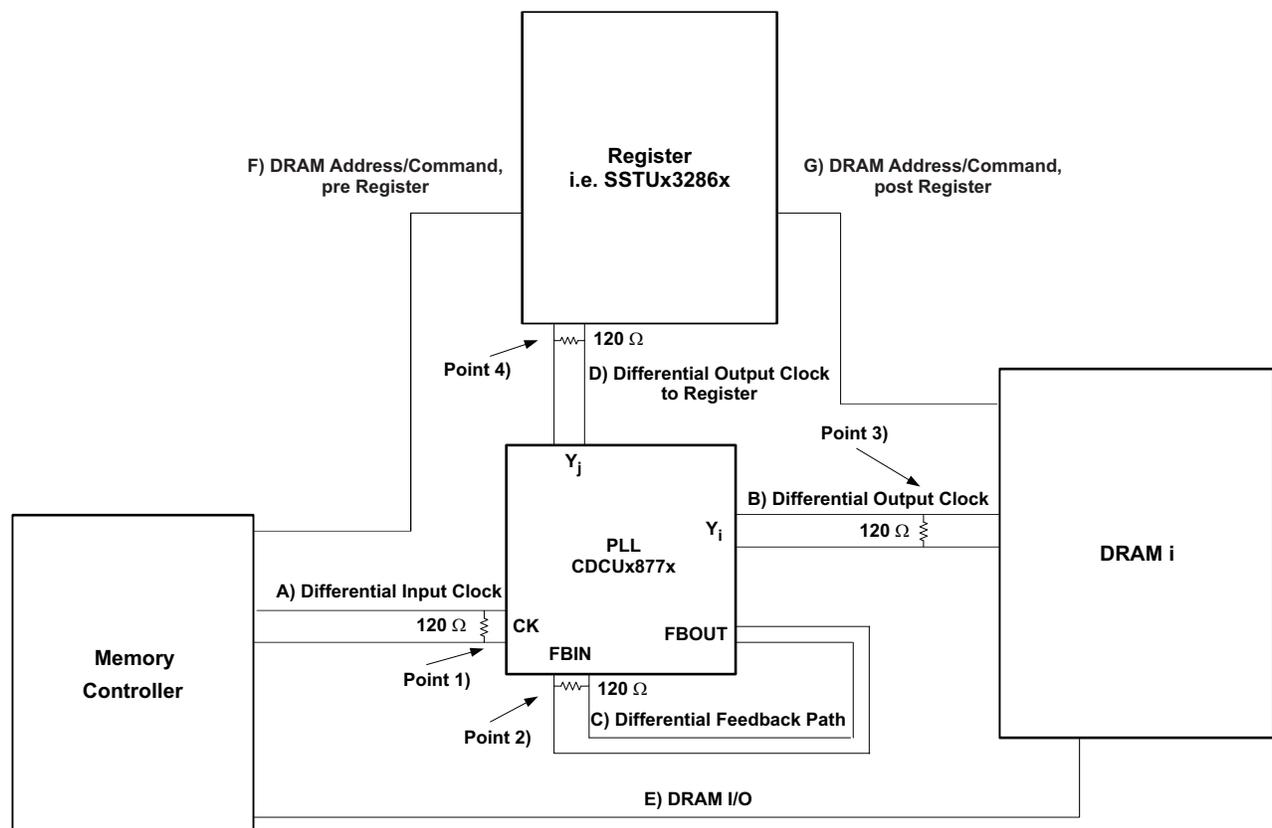

Note: Clock at Points 1), 2), 3) and 4) have the same phase.

Figure 1. Principle Use of the CDCUx877x PLL on RDIMM Modules

2 Application as 1:10 Clock Buffer

When AVDD is tied to GND, the PLL is in bypass mode. Now, it behaves like a differential 1:10 clock Buffer (see [Figure 2](#)).

CAUTION

When using the CDCUx877x as a 1:10 Buffer, the parameters specified in the data sheet are no longer valid. In this mode, the PLL is turned off, so the user has no jitter cleaning or lock functionality.

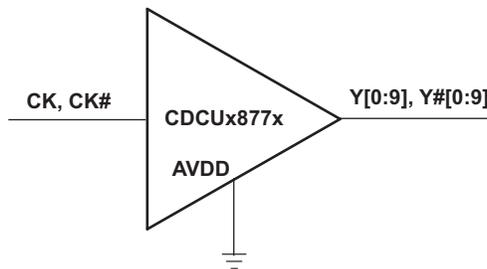


Figure 2. The CDCUx877x Used as 1:10 Clock Buffer

3 Switching Into Bypass Mode

To switch into bypass mode during operation, a circuit like the one shown in [Figure 3](#) is recommended. For this example an analog SPDT switch [TS5A6542](#) is used.


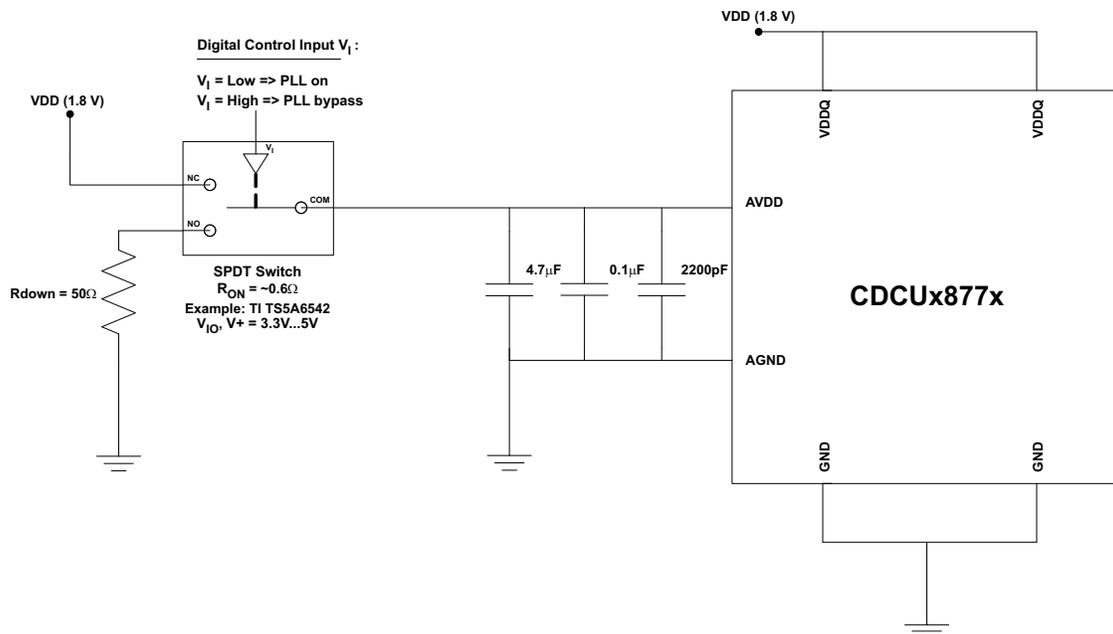


Figure 3. Example Circuit for Switching PLL Into Bypass Mode

4 Using Differential Outputs for Single Ended Inputs

The output stages of the CDCUx877x PLLs are designed for differential use. However, to drive a single-ended clock input, use of a load as shown in Figure 4 is recommended. Terminate the differential signal with $120\ \Omega$ (if the trace impedance is $60\ \Omega$), and connect one side of the termination to the single-ended input. Connect the other end of the termination to a dummy load. This should be a R/C load that equals the load of the input stage. If the R value of the input stage load is not known, use only a capacitor for the dummy load.

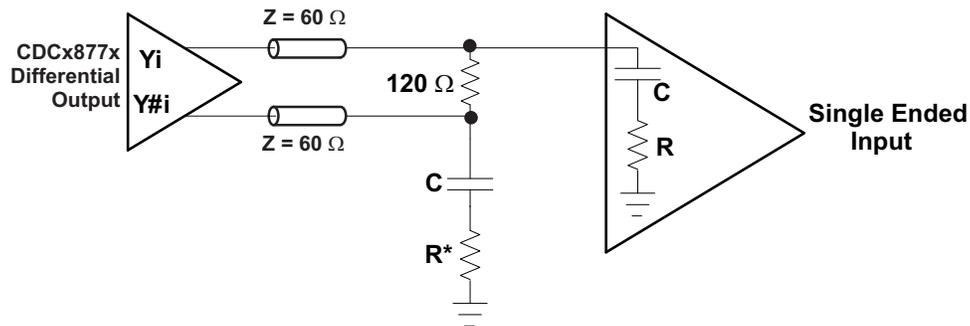

* If value of R is unknown use $0\ \Omega$.

Figure 4. Example Termination for Differential Signal That Drives a Single-Ended Input Stage

5 References

1. CDCU877/A 1.8V Phase-Lock Loop Clock Driver for DDR2 SDRAM Applications, Data sheet ([SCAS688](#))
2. CDCU877B 1.8V Phase-Lock Loop Clock Driver for DDR2 SDRAM Applications, Data sheet ([SCAS801](#))
3. CDCUA877 1.8V Phase-Lock Loop Clock Driver for DDR2 SDRAM Applications, Data sheet ([SCAS769](#))
4. CDCU2A877 1.8V Phase-Lock Loop Clock Driver for DDR2 SDRAM Applications, Data sheet ([SCAS827](#))
5. JEDEC Solid State Technology Association, Registered DIMM Design Specification (JESD21)
6. TS5A6542 SPDT Analog Switch With Input Logic Translation, Data sheet ([SCDS211](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated