


# How to Isolate Two-Wire Loop-Powered Field Transmitters



Tony Calabria, Systems Manager, Isolation, Interface Group

Improving process, quality, and consistency starts with automation in today's expanding industrial world. Growth in system monitoring equipment, such as field transmitters, has made manufacturing in factories more efficient and reliable. Loop-powered field transmitters are a sensor variant which use the two-wire 4 mA to 20 mA bus for both communication and power for the equipment. This removes the need for additional wiring and components to separately power the system, saving the factory cost on both materials and installation.

A field transmitter consists of a sensor, a transmitter, and, in certain circumstances, an isolator. Isolation is needed when the sensor has the ability to be electrically connected to a voltage potential that is different than the loop supply. Since the entire system is powered from 4 mA–20 mA, the zero scale value sets the maximum budget for the system, which can be on the order of 3.3 mA. Power savings from any of the components, including the isolator, can be distributed among the system allowing for more end product differentiation. Figure 1 shows a typical block diagram including the current flow used for the communication bus and power for the system.

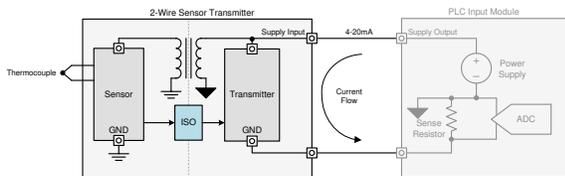


**Figure 1. Loop-Powered Field Transmitter with a PLC Input Module**

Implementing isolation within 4 mA to 20 mA loop-powered field transmitters can be challenging for process automation end equipment designers. Since these systems operate off a strict power budget, decisions are made to trade off performance with features. Designers may fear that integrating isolation uses board space they may not have, while taking significant power away from the other critical blocks in the system, potentially limiting equipment capability. However, advancements in digital isolation technology have brought power consumption down an order of


magnitude and increased isolator channel density, giving designers more design flexibility in sensor design systems.

Historically, the only available low power isolation options were either pulse transformers or opto-couplers. These isolation solutions can consume anywhere from 500  $\mu$ A up to 1 mA per channel, forcing designers to minimize the number of communication lines brought across the isolation barrier or slowing data transfer speeds. Additional components, such as a second micro controller (MCU), could be used to decrease the communication lines across the isolation barrier, further consuming more of the constrained power budget. In these solutions, communication speed and, in some cases, data transfer rate can be limited to just a single direction with so few isolation lines. A typical implementation, shown in Figure 2, uses a pulse transformer as a unidirectional solution for implementing isolation in a field transmitter and an additional MCU to convert the isolated data interface to a single line.

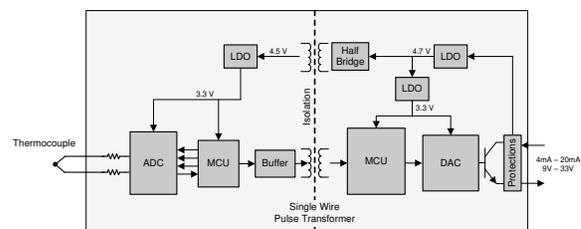

**Figure 2. Field Transmitter - Single Channel Pulse Transformer for Data Isolation**


Texas Instruments' [ISO70xx](#) digital isolator family integrates two to four ultra-low-power digital isolator channels in a small 8-pin D and 16-pin DBQ package. This device offers up to 3.0 kVrms isolation rating per UL1577 and 400 Vrms of isolation working voltage per VDE. In loop-powered field transmitters, the [ISO70xx](#) family can be used to replace opto-couplers or a pulse transformer at a fraction of the power and footprint size. Figure 3 shows an example of the four channel [ISO7041](#) used in a field transmitter.

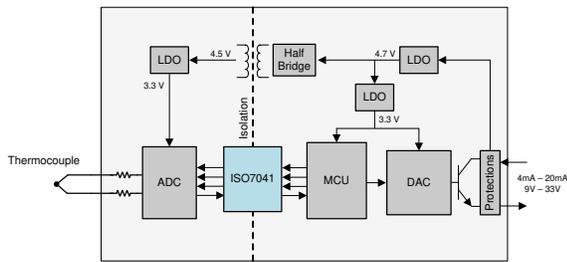

**Figure 3. Field Transmitter - ISO7041 for Multi-channel and Bi-directional Data Isolation**

Benefits using digital isolators in field transmitters:

- Power scalability: The **ISO7041** power scales with the data transfer rate as shown in [Figure 4](#). At 10 kbps, all four channels consume under 20  $\mu$ A combined. The power savings can be distributed to the sensor to improve accuracy or precision of the system.

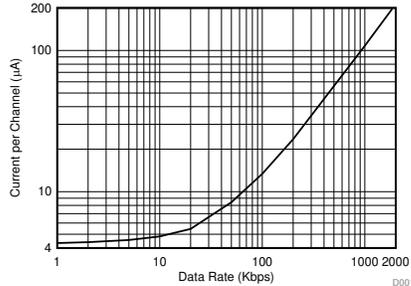

**Figure 4. ISO7041 Individual Channel Power Versus Data Rate**

- Increased data throughput: Four digital isolator channels can operate at up to 2 Mbps while consuming very low power for easy two way communication. This flexibility allows designers to rethink and re-architect how they transfer data between the sensor and transmitter.
- Extended temperature range: The **ISO7021** and **ISO7041** are rated from  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  while most opto-couplers are rated up to a maximum of  $85^{\circ}\text{C}$ . There are some opto-couplers available in the market rated for  $105^{\circ}\text{C}$  that come at a higher cost.
- Smaller solution size: A single channel pulse transformer for data isolation can require a circuit board surface area as large as  $50\text{ mm}^2$  with an additional height requirement of 5 mm. Opto-coupler designs can occupy similar board area or more depending on the amount of data lines. The **ISO7041** in the 16-pin DBQ package offers four channels of data isolation across  $17.5\text{ mm}^2$  of area with a height requirement of 2.5 mm. Overall, a digital isolator solution is a more compact design, including lower package height.

- Stability and reliability: **ISO70xx** uses TI's capacitive isolation technology where the high voltage capacitors made from  $\text{SiO}_2$  dielectric provide high level of isolation. The high voltage capacitors are constructed in a well controlled semiconductor process and offer very low part-to-part variation. Also, the isolation barrier lifetime is well defined by the time dependent dielectric breakdown (TDDb) technique. Opto-couplers have a lot of manufacturing variability and no defined technique in the standard to calculate lifetime of the device.

For years, a single pulse transformer was the only power efficient way to isolate data between the sensor and transmitter in a 4 mA–20 mA loop-powered field transmitter. Later, low speed opto-coupler solutions were able to replace pulse transformers at adequate power budgets. Now, ultra-low-power digital isolators are available to provide data isolation between the sensor and transmitter at extremely low power levels. The **ISO70xx** is the latest release in low power technologies for galvanic isolation. For a deeper explanation of TI's isolation technology, refer to the [Enabling High Voltage Signal Isolation Quality and Reliability White Paper](#). The size, scalability, technology robustness, and ultra-low-power consumption of the **ISO70xx** digital isolators make them an optimal choice for power constrained designs.

**Table 1. Related Technical Documents**

Literature Number	Document Title
TIDU813B	<a href="#">Uniquely Efficient Isolated DC/DC Converter for Ultra-Low Power and Low Power Apps Reference Design</a>
SLAA426	<a href="#">Considerations for Selecting Digital Isolators</a>
SLLY063	<a href="#">High-voltage reinforced isolation: Definitions and test methodologies</a>
SLLA284A	<a href="#">Digital Isolator Design Guide</a>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated