

## ***The PWM and Analog Dimming Solution to Implement 0.05% to 100% Dimming Range Based on UCC28810/11 Constant Current Buck***

Richard Yang Lv Jian

China Power FAE

### **ABSTRACT**

In this paper, the combined dimming solution (PWM and 1- to 10-V analog) based on the UCC28810/11 device is provided to meet today's wider dimming range specification for the LED ceiling lamp application. This solution is different from the traditional 10% to 100% PWM dimming, and it divides the dimming range into two parts: for the first part, 5% to 100% LED current dimming will be implemented by 1- to 10-V analog dimming signal; for the second part, 0.05% to 5% LED current dimming will be implemented by 1% to 100% PWM dimming signal.

### Content

<b>1</b>	<b>Introduction .....</b>	<b>2</b>
<b>2</b>	<b>Principle Analysis Based on UCC28810/11 Buck Constant Current Solution.....</b>	<b>3</b>
	2.1 The Origin of UCC28810/11 Constant Current Buck.....	3
	2.2 Ideal Operation Analysis of UCC28810/11 Device Constant Current Buck .....	4
<b>3</b>	<b>Practical UCC28810/11 Device Constant Current Principle Analysis .....</b>	<b>5</b>
	3.1 Constant Current Analysis for the Traditional Operation .....	5
	3.2 The Improved UCC28811 Constant Output Current Solution.....	7
<b>4</b>	<b>The PWM and Analog Dimming Design Analysis.....</b>	<b>8</b>
	4.1 The 5% to 100% Analog Dimming Solution.....	8
	4.2 The Improved 0.05% to 5% PWM Dimming Solution .....	9
<b>5</b>	<b>The Practical Design Example.....</b>	<b>10</b>
<b>6</b>	<b>5% to 100% Analog Dimming and 0.05% to 5% PWM Dimming Design Result.....</b>	<b>16</b>
	6.1 5% to 100% Analog Dimming Design Result .....	16
	6.2 0.05% to 5% PWM Dimming Design Measurement Result .....	20
	6.3 5% to 100% Analog Dimming Design Measurement Result for the Output Current.....	22
<b>7</b>	<b>Conclusions.....</b>	<b>23</b>
<b>8</b>	<b>References.....</b>	<b>23</b>

### Figures

Figure 1.	Internal Block Diagram of the UCC28810/11 Device and Its Multiplier Function.....	3
Figure 2.	Internal 1.7-V Creating Function for the UCC28810/11 Device .....	3
Figure 3.	Basic Buck Constant Current Solution with the Internal 1.7-V Reference.....	4
Figure 4.	Waveform Analysis for the Steady Operation.....	6
Figure 5.	Solution for the Tight Output Current Control When Output Voltage Varies.....	7
Figure 6.	UCC28810/11 Analog Dimming Solution.....	8
Figure 7.	Improved Solution for the UCC28810/11 PWM Dimming .....	10

<b>Figure 8.</b>	<b>Curve of Frequency versus L.....</b>	<b>12</b>
<b>Figure 9.</b>	<b>Calculated Output Current When Analog Dimming.....</b>	<b>13</b>
<b>Figure 10.</b>	<b>Calculated Frequency Curve When <math>V_{\text{analog}}</math> Out Voltage Varies .....</b>	<b>13</b>
<b>Figure 11.</b>	<b>ISNS Pin Voltage Comparison Between With Improved Circuit and Without Improved Circuit .....</b>	<b>14</b>
<b>Figure 12.</b>	<b>Circuit to Improve Analog Dimming Performance.....</b>	<b>15</b>
<b>Figure 13.</b>	<b>Spice Simulation Result to Meet the 180-ns Delay Specification .....</b>	<b>15</b>
<b>Figure 14.</b>	<b>Measured Waveforms for the 5% to 100% Analog Dimming Control .....</b>	<b>18</b>
<b>Figure 15.</b>	<b>Operation Frequency Curve—Comparison Between Measurement and Calculation.....</b>	<b>19</b>
<b>Figure 16.</b>	<b>Curve of Output Current—Comparison Between Measurement and Calculation When Analog Dimming is Conducted .....</b>	<b>19</b>
<b>Figure 17.</b>	<b>Measured Waveforms When PWM Dimming is Conducted .....</b>	<b>22</b>
<b>Figure 18.</b>	<b>Measured Output Current Waveforms When Analog Dimming is Conducted.....</b>	<b>23</b>

## 1 Introduction

With the increasing stringent dimming control tendency for the ceiling lamp, the single traditional analog dimming or PWM dimming cannot meet the current market requirement. Instead, the combined mode of PWM and analog dimming is a good choice. However, deeper and wider dimming remains the challenge due to the influences of parasitic effect on the junction capacitor for the MOS and output diode. An additional challenge is meeting the good linearity specification between the LED output current and dimming signal.

In this paper, the combined analog dimming and PWM dimming solution based on the UCC28810/11 device is provided to meet this specification. Due to a contribution of power-factor correction (PFC) output or Flyback output in the front of AC input, in this paper the UCC28810/11 device will be provided by the DC input voltage. For a better understanding of this solution, this paper provides the detail theoretical analysis and practical design with extensive experiment data. This paper proves that the design calculation matches with the experiment very well.

## 2 Principle Analysis Based on UCC28810/11 Buck Constant Current Solution

### 2.1 The Origin of UCC28810/11 Constant Current Buck

To implement constant current, the logic circuit inside the UCC28810/11 device must be changed due to the influence of the internal multiplier (see Figure 1). Because the output-clamped voltage of this multiplier is 1.7 V, we can create a simple external circuit to let the multiplier stabilize at 1.7 V; that is, the internal reference voltage of 1.7 V can be created in this way.

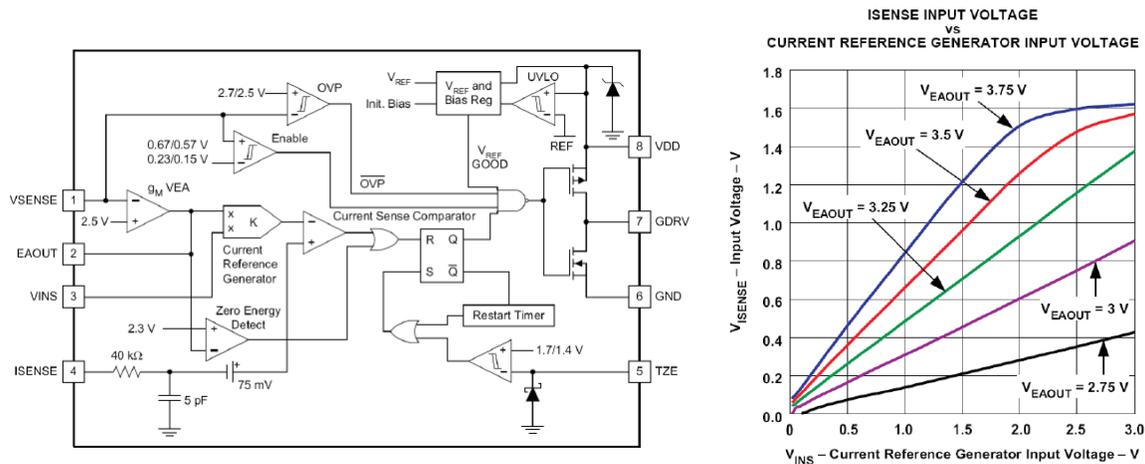


Figure 1. Internal Block Diagram of the UCC28810/11 Device and Its Multiplier Function

The internal reference voltage of 1.7 V can be created as shown in Figure 2.


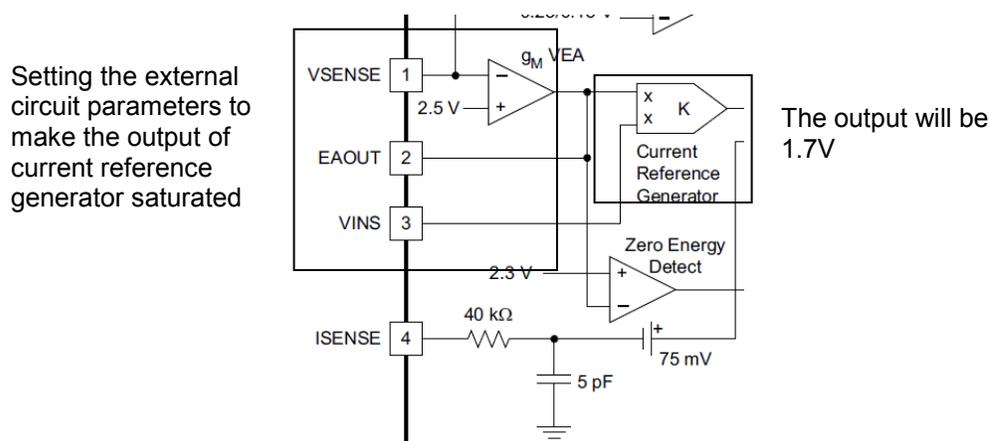


Figure 2. Internal 1.7-V Creating Function for the UCC28810/11 Device

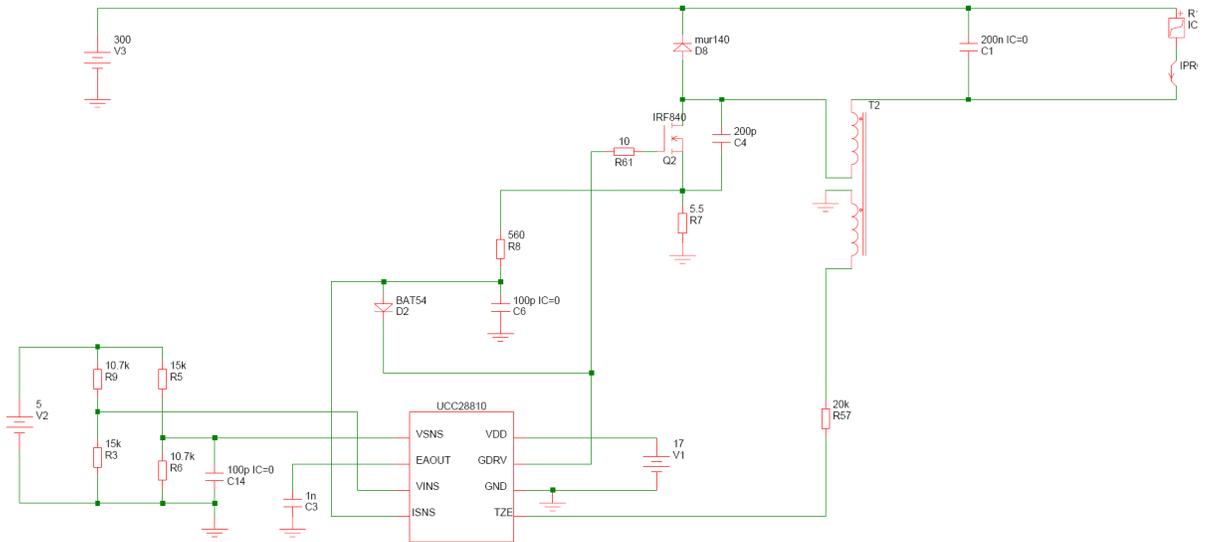

**Figure 3. Basic Buck Constant Current Solution with the Internal 1.7-V Reference**

## 2.2 Ideal Operation Analysis of UCC28810/11 Device Constant Current Buck

The LED output current will be 0.5 times the peak current going through the BUCK MOS due to the critical operation mode for the UCC28810/11. As mentioned in Section 2.1, the internal reference voltage will be 1.7 V, and then the current through MOS will be:

$$I_{PP} = \frac{1.7}{R_S} \quad (1)$$

Then the output current will be:

$$I_o = \frac{0.85}{R_S} \quad (2)$$

The turn-on time and turn-off time will be

$$T_{on} = \frac{2 \cdot I_o \cdot L}{V_{in} - V_o} \quad T_{off} = \frac{2 \cdot I_o \cdot L}{V_o} \quad (3)$$

The switching frequency will be:

$$F_{sw} = \frac{(V_{in} - V_o) \cdot V_o}{2 I_o \cdot L \cdot V_{in}} \quad (4)$$

### 3 Practical UCC28810/11 Device Constant Current Principle Analysis

#### 3.1 Constant Current Analysis for the Traditional Operation

In practical operation, the resonance between the junction capacitor of the MOS and Diode and the inductance of the BUCK inductor occurred when the current of BUCK inductor decreased to zero. During this process, the  $V_{DS}$  of MOS decreases gradually. However, this voltage may come to zero at some certain input condition showing that the ZVS condition is realized completely. However, it must be pointed out that the negative current of inductor current will be discovered due to this resonance mechanism. This causes the total average current through the BUCK inductor to vary slightly from the ideal operation BUCK current. This variance means the practical LED current formula must be recalculated based on this resonance consideration.

Due to the complicated formula of junction capacitance of the MOS and Diode, it can be defined as  $C_{oss}$  for simplification but not affecting our analysis result. So the inductance of the BUCK inductor can be defined as  $L$ . We can obtain Equation 5, as referenced in Figure 4:


During the stage of  $T_{d\_off}$ :

The junction capacitor of the MOS and Diode will be discharged gradually, which makes the current through inductor go reverse when the BUCK inductor current decreases to zero. The voltage of MOS will be:

$$V_{DS\_MOS} = V_{in} - V_o + V_o \cdot \cos(\omega \cdot t) \quad \omega = \frac{1}{\sqrt{L \cdot C_{oss}}} \quad (5)$$

The  $T_{d\_off}$  stage will come to the end when the voltage of MOS decreases to  $V_{in} - V_o$ , (see Figure 4), then we have:

$$T_{d\_off} = \frac{\pi}{2\omega} \quad (6)$$

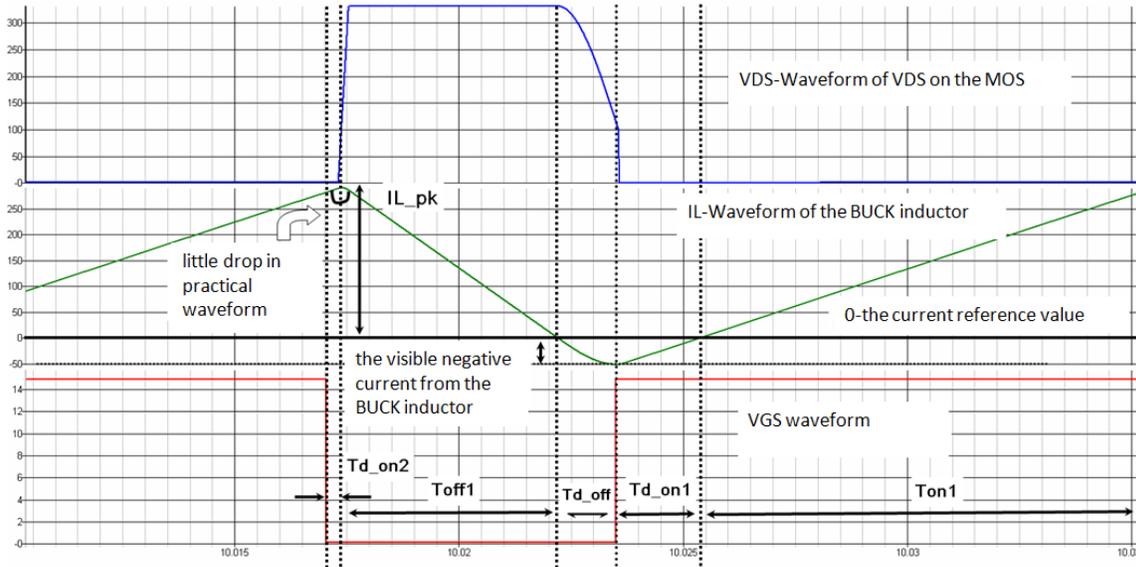

**Figure 4. Waveform Analysis for the Steady Operation**

According to the similar analysis, the following formulae can be obtained as:

$$T_{d\_on1} = \frac{V_o}{(V_{in} - V_o) \cdot \omega} \tag{7}$$

$$T_{on1} = \frac{1.7}{R_s} \cdot \frac{L}{V_{in} - V_o} \tag{8}$$

$$T_{off1} = \frac{1.7}{R_s} \cdot \frac{L}{V_o} \tag{9}$$

So the entire periodic can be obtained as:

$$T_s = T_{d\_on1} + T_{d\_off} + T_{d\_on2} + T_{d\_off1} \tag{10}$$

The switching frequency can be obtained as:

$$F_{sw} = \frac{1}{\frac{\pi}{2\omega} + \frac{V_o}{(V_{in} - V_o) \cdot \omega} + \frac{1.7}{R_s} \cdot \frac{L}{V_{in} - V_o} + \frac{1.7}{R_s} \cdot \frac{L}{V_o}} \tag{11}$$

The ultimate LED output current can be obtained as:


$$I_o = \frac{0.85}{R_s} - 0.5 \cdot \left( \frac{1.7}{R_s} + V_o \cdot \omega \cdot C_{oss} \right) \cdot \frac{\frac{\pi}{2} + \frac{V_o}{V_{in} - V_o}}{\left( \frac{\pi}{2\omega} + \frac{V_o}{(V_{in} - V_o) \cdot \omega} + \frac{1.7}{R_s} \cdot \frac{L}{V_{in} - V_o} + \frac{1.7}{R_s} \cdot \frac{L}{V_o} \right) \cdot \omega} \tag{12}$$

From Equation 12, it can be seen that LED current is not dependent on the single parameter; instead, it is influenced by several parameters such as  $R_s$ ,  $V_{in}$ ,  $V_o$ ,  $L$ , and  $C_{oss}$ . In practical design, we can know the parameters of  $R_s$ ,  $L$ , and  $C_{oss}$ , but  $V_{in}$  and  $V_o$  must be evaluated.

From Equation 12, we can see LED output current is minimally affected with some certain input voltage variation. However, the LED current will be affected when output voltage is varied. So, the compensation circuit must be determined to tightly stabilize the output current when the LED voltage changed.

### 3.2 The Improved UCC28811 Constant Output Current Solution

Because a variation in output voltage affects LED current, the simple compensation solution is proposed by connecting a large-value resistor,  $R_L$ , from the ISNS pin of the UCC28811 device to the negative terminal of the LED.

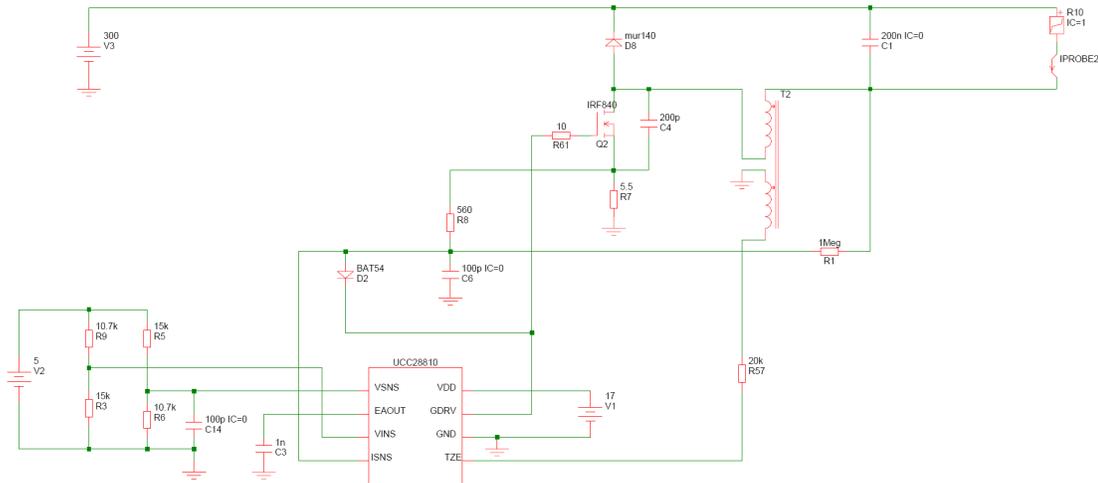

**Figure 5. Solution for the Tight Output Current Control When Output Voltage Varies**

Shown as Figure 5, the total output current can be calculated by Equations 13 and 14:

The voltage of the ISNS pin of the UCC28810/11 device will be:

$$V_{isns} = I_{pp} \cdot R_s + \frac{(V_{in} - V_o) \cdot R_m}{R_m + R_L} \tag{13}$$

Then the LED output current can be obtained as:



Referring to Figure 6, if we designate resistor R8 as  $R_L$ , resistor R2 as  $R_{dim}$ , resistor R7 as  $R_s$ , and the external 5-V supply as  $V_{anog}$ , we can have the following formulae:

The LED output current when conducting analog dimming can be obtained as:

$$I_o(V_{anog}) = 0.5 \cdot I_{pp}(V_{anog}) - 0.5 \cdot (I_{pp}(anog) + V_o \cdot \omega \cdot C_{oss}) \cdot \frac{\frac{\pi}{2} + \frac{V_o}{V_{in} - V_o}}{\left( \frac{\pi}{2\omega} + \frac{V_o}{(V_{in} - V_o) \cdot \omega} + I_{pp}(V_{anog}) \cdot \frac{L \cdot V_{in}}{(V_{in} - V_o) \cdot V_o} \right) \cdot \omega}$$

$$I_{pp}(V_{anog}) = \frac{1.7 - \frac{(V_{anog} - V_f - 1.7) \cdot R_L}{R_{dim}}}{R_s} \quad (V_{anog} \geq 1.7 + V_f) \quad (16)$$

The switching frequency can be obtained as follows:


$$F_s(V_{anog}) = \frac{\omega}{\frac{\pi}{2} + \frac{V_o}{(V_{in} - V_o)} + I_{pp}(V_{anog}) \cdot \frac{L \cdot V_{in} \cdot \omega}{(V_{in} - V_o) \cdot V_o}} \quad (17)$$

In practical application, the external  $V_{anog}$  will be provided by the microchip, which will produce the output voltage varied from  $1.7 + V_f$  to 5 V. During this range, the output current will be line with  $V_{anog}$ , and the line ratio is mainly dependent on  $R_L$  and  $R_{dim}$ . We can achieve the optimized line ratio according to the design specification.

The experiment verified that the 5% to 100% analog dimming can be easy to implement when the external  $V_{anog}$  varied from 5 V to  $1.7 + V_f$ . Actually, concern about the influence of  $V_f$  is not necessary, because very little voltage variation occurs during the actual 0°C-to-75°C temperature variation if a low forward diode, such as BAT54, is chosen.

## 4.2 The Improved 0.05% to 5% PWM Dimming Solution

First of all, note that the original PWM dimming solution shown in Figure 7 (Q4, R14, and R15) will not work well due to a flickering issue. This issue is primarily caused because the deep PWM dimming range is extremely wide, therefore the UCC28810/11 device cannot easily detect the ISNS signal due to the influence of the junction capacitor of MOS. The junction capacitor will not let the UCC28810/11 device have the stable control if the peak voltage of ISNS dominates the entire period of sense voltage recognized by the controller. Figure 7 shows the improved solution.

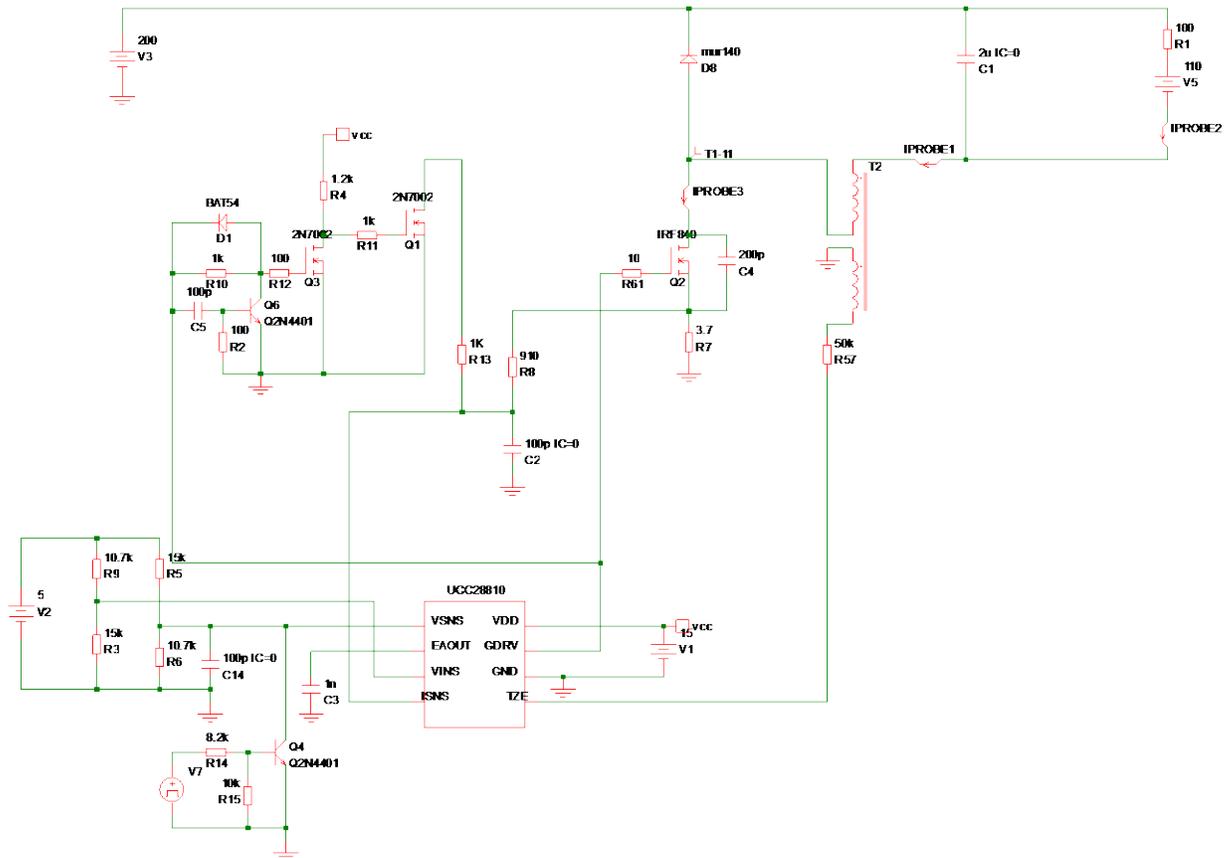

**Figure 7. Improved Solution for the UCC28810/11 PWM Dimming**

In Figure 7, the circuit of Q1, Q3, R13, and Q6 is added to move out the peak voltage of ISNS at the beginning of its rising stage.

Extensive experimentation proves that this circuit works well to provide good dimming performance from 0.05% to 100% dimming range even across a wide temperature range.

## 5 The Practical Design Example

To verify the previous solution, see the following table of design specifications. For the practical application of this solution:

- The input is always 90 VAC to 130 VAC.
- Nonisolated solution is chosen.
- PFC is used.
- PFC outputs approximately 200 VDC.

The design parameters are shown as the following table:

Table of Design Specification

Design specification	Parameters	Requirement
<b>Input and output</b>		
BUCK input voltage	$V_{in}$	150VDC-220VDC
BUCK output current	$I_o$	200mA
BUCK output voltage range	$V_o$	60-130V
effi	$\eta$	>0.94
<b>Dimming spec</b>		
Analog dimming	0-10V	10mA-200mA
PWM dimming	1%-100%	100uA-10mA

Dimming design specification: PWM dimming and analog dimming are provided by the external signals. However, 0 to 10 V will be converted to the 2- to 5-V analog signal through the microchip, and 1% to 100% PWM dimming signal could have the direct control of the UCC28810/11 device.


According to the design requirement, the analog dimming is as described in Section 4.1, and PWM dimming is as described in Section 4.2. The detail design procedure is presented as follows.

**Step 1:** Choose the inductance of the BUCK inductor according to the efficiency specification.

To achieve the 94% efficiency, the minimum operation frequency of 30K is chosen. Given the total MOS and Diode junction capacitance of 200 pF,  $V_{in}$  is with 200 VDC,  $V_o$  is with 130 V,  $R_s$  is first chosen with  $3.7R$ . The formula and curve of frequency versus L can be obtained as follows:

$$F_s(L) = \frac{1/\sqrt{L \cdot C_c}}{\frac{\pi}{2} + \frac{V_o}{(V_{in} - V_o)} + \frac{1.7}{R_s} \cdot \frac{L \cdot V_{in}}{(V_{in} - V_o) \cdot V_o \cdot \sqrt{L \cdot C_c}}} \quad (18)$$

The curve of frequency versus L is shown from Figure 7.

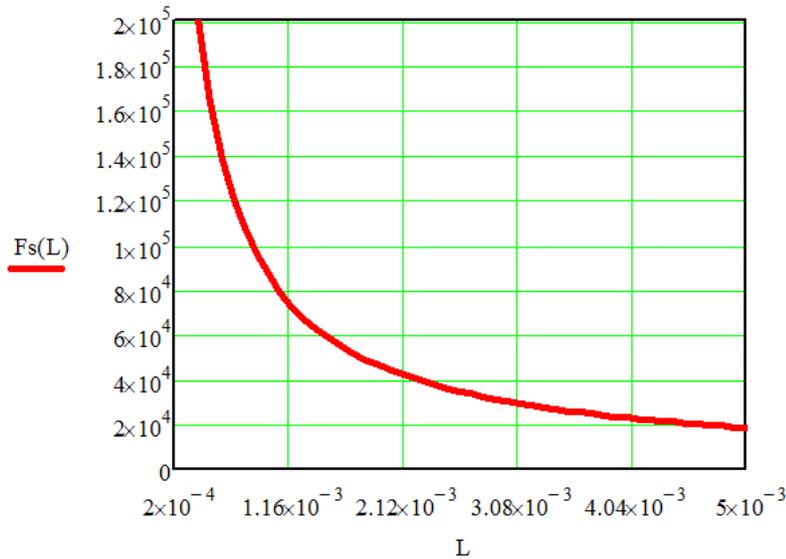

**Figure 8. Curve of Frequency versus L**

It can be seen that the value of inductance of the BUCK inductor must be chosen as 3.0 mH.

So in Step 1, we obtain:

$$R_s = 3.7R \quad L = 3.0 \text{ mH}$$


**Step 2:** Choose the analog dimming resistor  $R_{\text{dim}}$  and the ISNS buffer resistor  $R_L$ .

According to the analog dimming design objective, a 2-V to 5-V analog signal will make the output current vary from 20 to 10 mA. If we first choose  $R_L$  as 910  $\Omega$ , then  $R_{\text{dim}}$  can be solved from Equation 19:

$$10\text{mA} = 0.5 \cdot I_{pp} - 0.5 \cdot (I_{pp} + V_o \cdot \omega \cdot C_{oss}) \cdot \frac{\frac{\pi}{2} + \frac{V_o}{V_{in} - V_o}}{\left( \frac{\pi}{2\omega} + \frac{V_o}{(V_{in} - V_o) \cdot \omega} + I_{pp} \cdot \frac{L \cdot V_{in}}{(V_{in} - V_o) \cdot V_o} \right) \cdot \omega}$$

$$I_{pp} = \frac{1.7 - \frac{(5-2) \cdot R_L}{R_{\text{dim}}}}{R_s} \quad (19)$$

The value of  $R_{\text{dim}}$  can be solved as 1.9 K if the forward voltage of dimming diode is 0.3 V. As a result, the analog dimming curve can be plotted as shown in Figure 9.

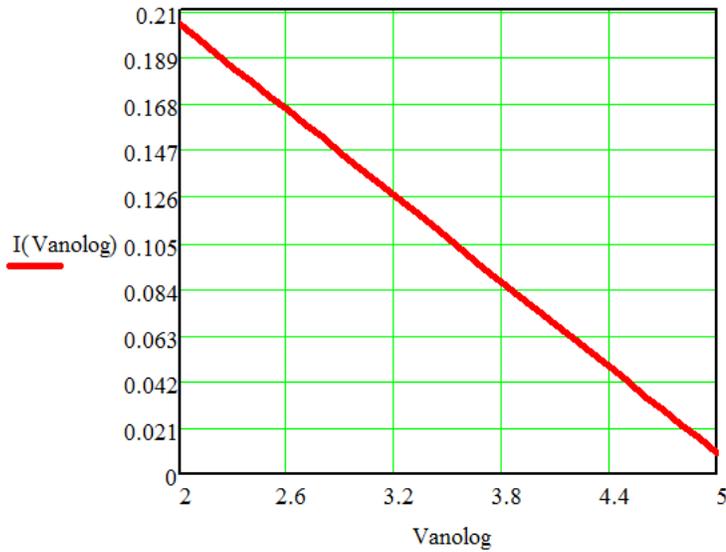


**Figure 9. Calculated Output Current When Analog Dimming**

Check the operation frequency during analog dimming according to Equation 20:

$$F_s(V_{anog}) = \frac{\frac{\pi}{2} + \frac{V_o}{V_{in} - V_o}}{\left( \frac{\pi}{2\omega} + \frac{V_o}{(V_{in} - V_o) \cdot \omega} + I_{pp}(V_{anog}) \cdot \frac{L \cdot V_{in}}{(V_{in} - V_o) \cdot V_o} \right) \cdot \omega} \quad (20)$$

$$I_{pp}(V_{anog}) = \frac{1.7 - \frac{(V_{anog} - V_f - 1.7) \cdot R_L}{R_{dim}}}{R_s}$$

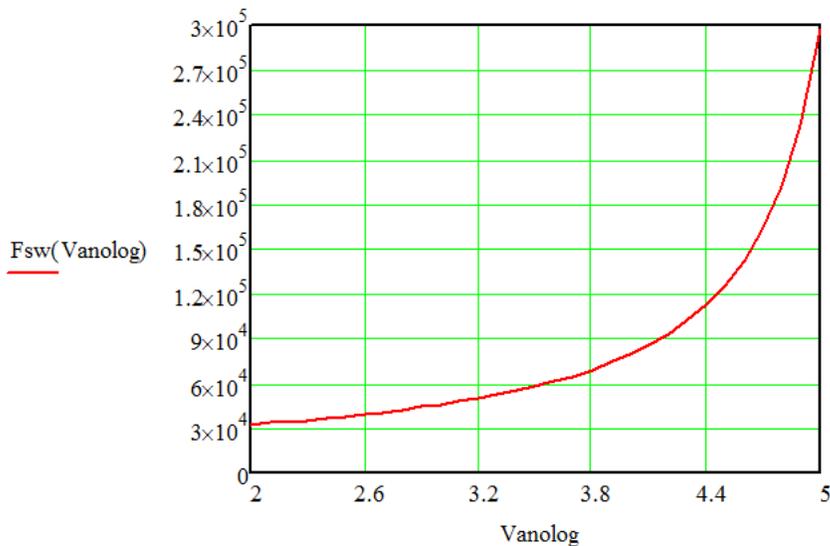

**Figure 10. Calculated Frequency Curve When V<sub>analog</sub> Out Voltage Varies**


The frequency can go up to 300K when coming to 5% dimming, which means it will be good for PWM dimming, especially 1% PWM dimming. But efficiency may be lower.

So in step 2, we obtain the following:

$$R_L = 910 \text{ } \Omega \quad R_{\text{dim}} = 1.9 \text{ K}$$


**Step 3:** Choose the parameters for the PWM dimming improvement circuit

Due to the influence of the junction capacitor of the MOS and Diode, the UCC28810/11 device may detect the wrong information on the ISNS pin when coming to 5% dimming (see Figure 10).

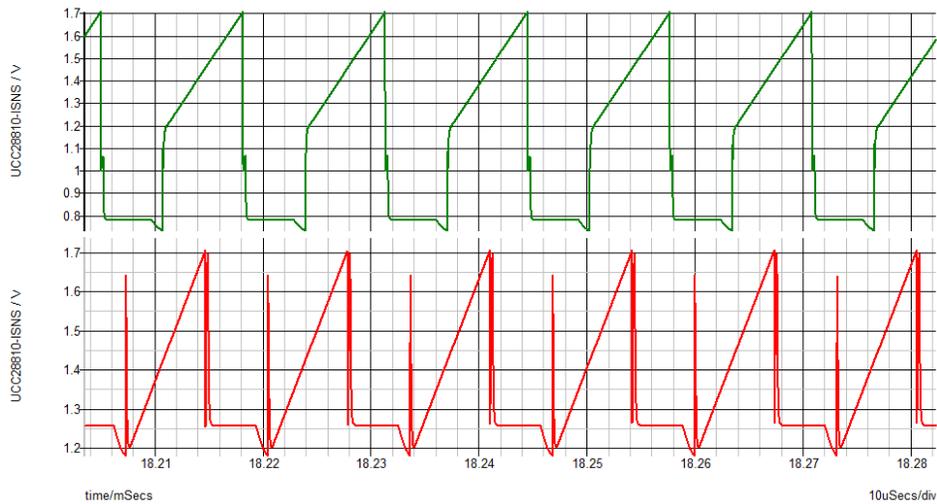


**Figure 11. ISNS Pin Voltage Comparison Between With Improved Circuit and Without Improved Circuit**

In practical design, we measure the waveform of ISNS to determine how much delay must be produced by the improved circuit (refer to Figure 11). So, it is recommended to make a simple spice simulation regarding the setup of the C13, R51, and R46 circuit.

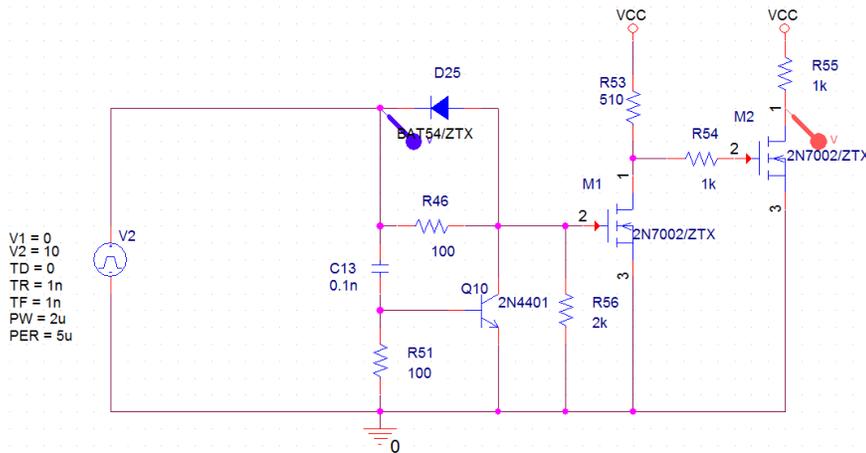

**Figure 12. Circuit to Improve Analog Dimming Performance**

For example, if we need to produce a 180-ns delay for the above-mentioned circuit, the preceding parameters can meet the requirement; Figure 12 shows its waveform.

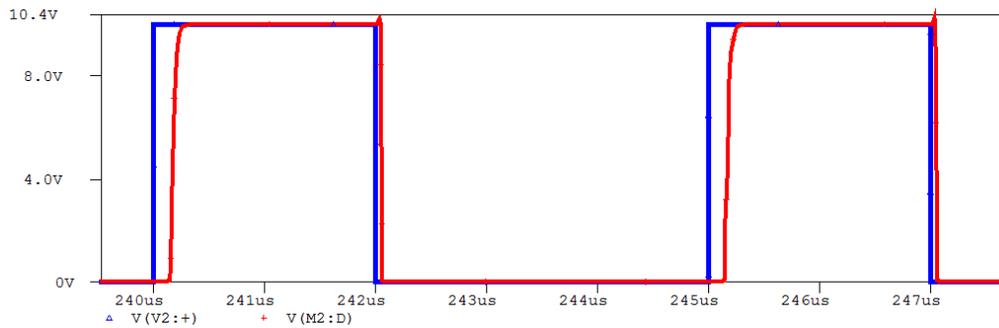

**Figure 13. Spice Simulation Result to Meet the 180-ns Delay Specification**

**Step 4:** Design PWM dimming circuit.

PWM dimming is very easy to implement because the UCC28810/11 device provides the drive turn-off function when Vsense is latched down to 0.57 V. Shown as Q4 in Figure 7, PWM dimming control can be done with a simple external transistor connected to the Vsense pin of the UCC28810/11 device.

However, the external duty cycle D of the PWM signal will produce the dimming performance with a duty cycle of 1-D for this solution


## 6 5% to 100% Analog Dimming and 0.05% to 5% PWM Dimming Design Result


### 6.1 5% to 100% Analog Dimming Design Result


Analog dimming is critically important because the output current must be very stable and not have any flickering issue. For a better understanding of this design, the waveforms of ISNS pin voltage of the UCC28810/11 device and the current of the BUCK inductor are investigated. These waveforms must be stable during the entire dimming process.

Waveforms of channel 2—ISNS pin voltage of the UCC28810/11 device

Waveforms of channel 4—Current of the BUCK inductor

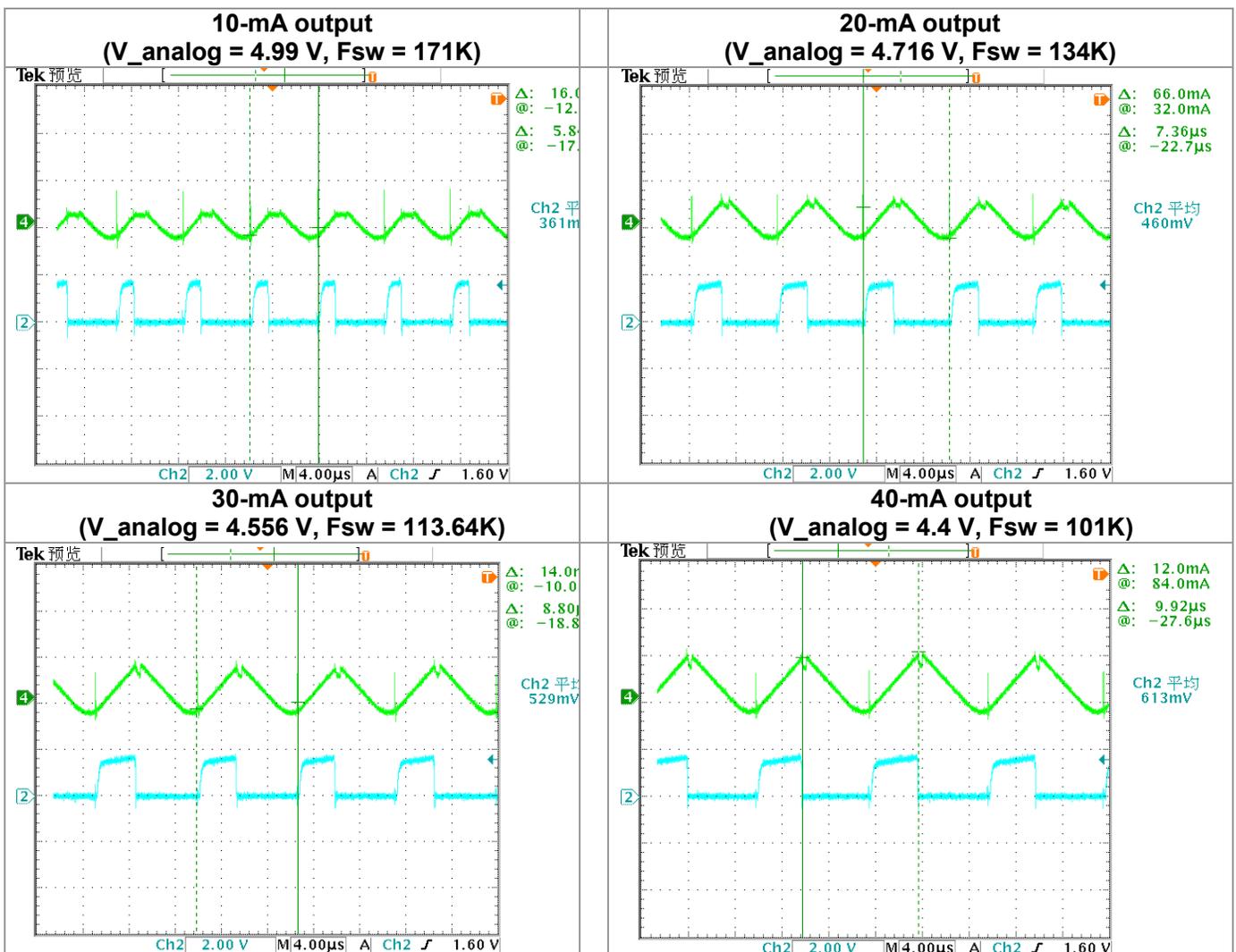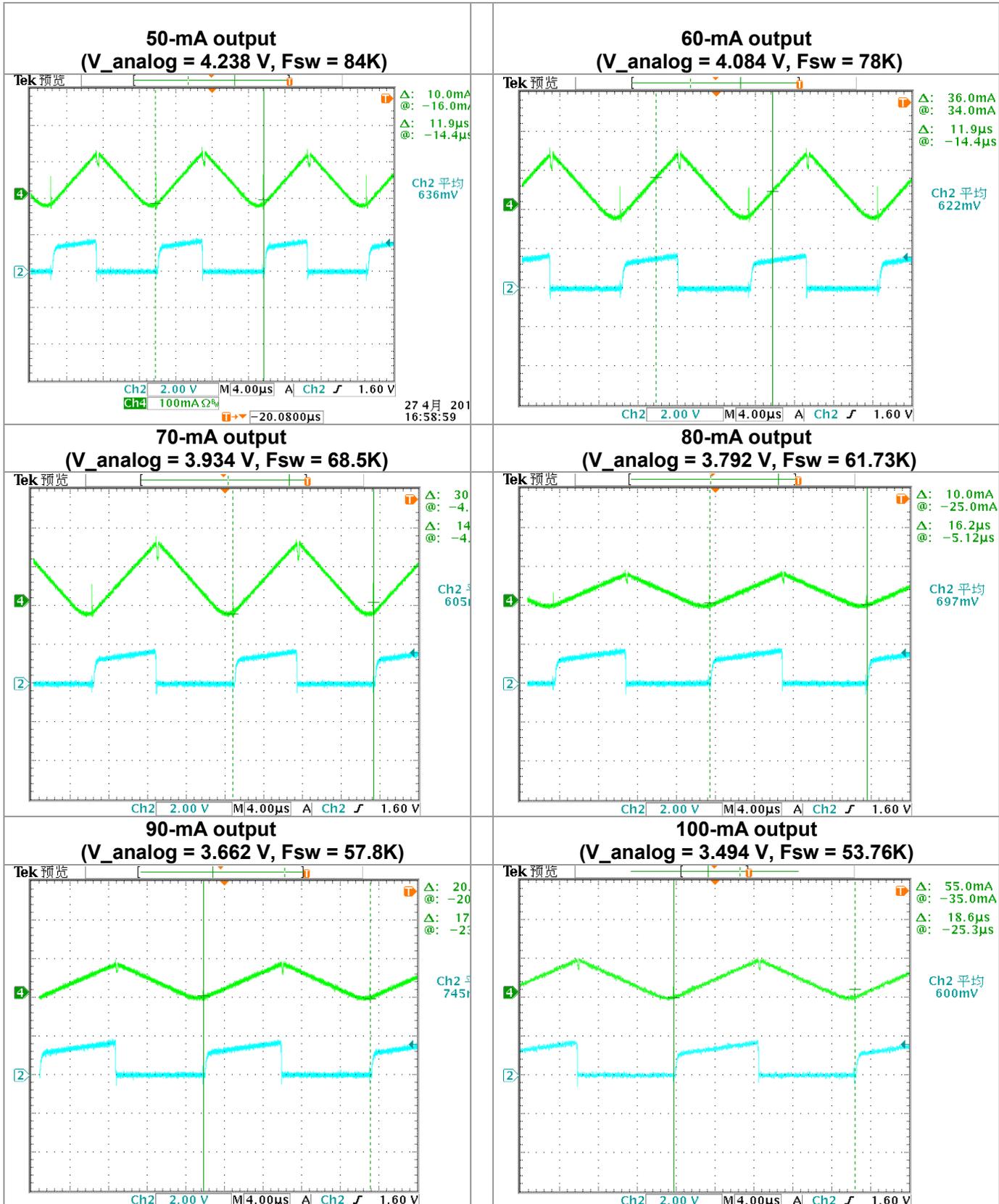




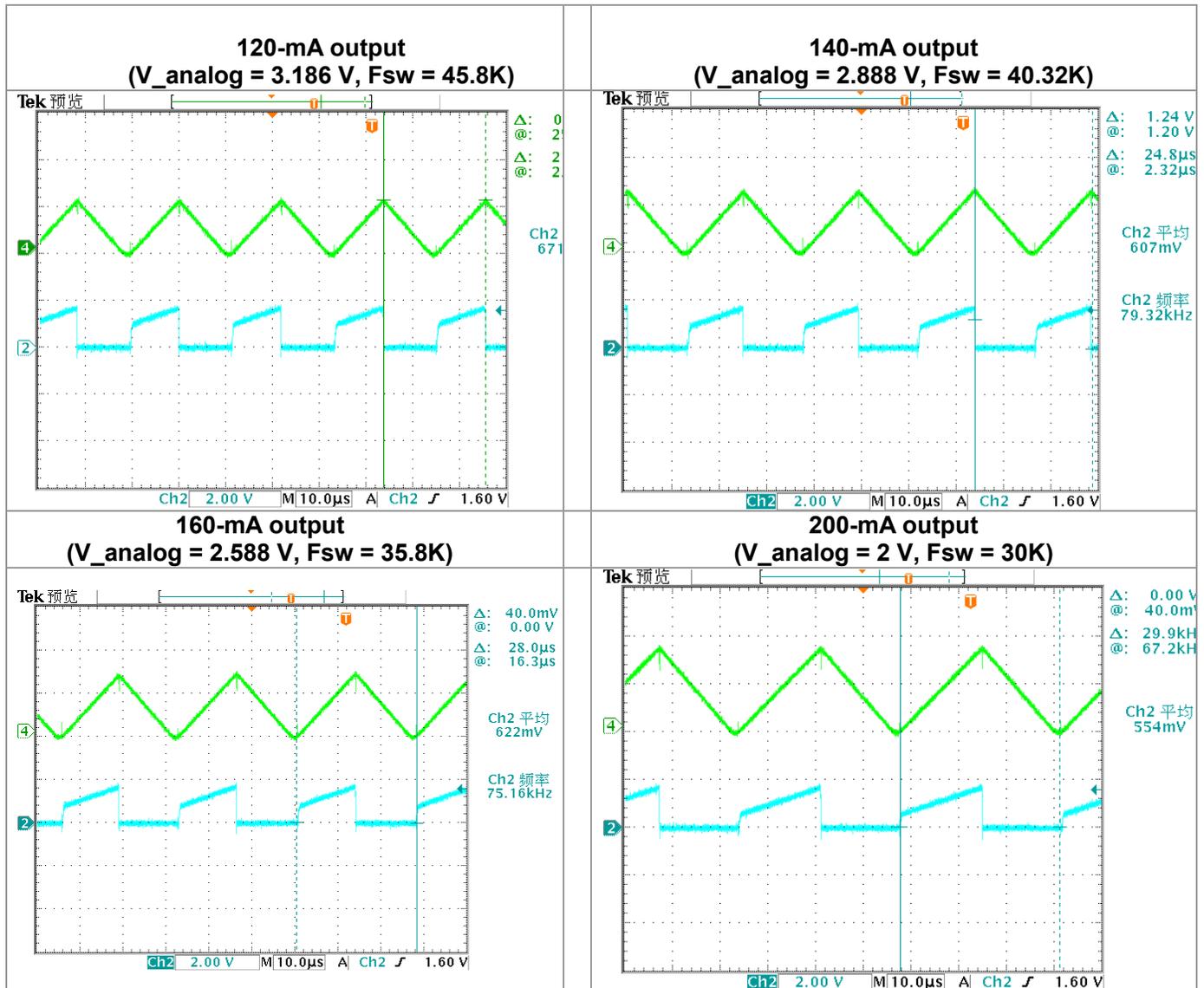

**Figure 14. Measured Waveforms for the 5% to 100% Analog Dimming Control**


From the measured waveforms in Figure 14, we can see the improvement on the voltage of the ISNS pin of the UCC28811 device. The original peak voltage on this pin disappears, which keeps the loop stable during the following PWM dimming.

Additionally, we must verify the design calculation formula regarding the operation frequency. In Figure 15,  $F_{\text{sw}}(V_{\text{analog}})$  represents the calculation result, and  $F_{\text{sw\_measure}}(V_{\text{analog}})$  represents the measurement result. It can be seen that the calculation matches very well with the measurement.

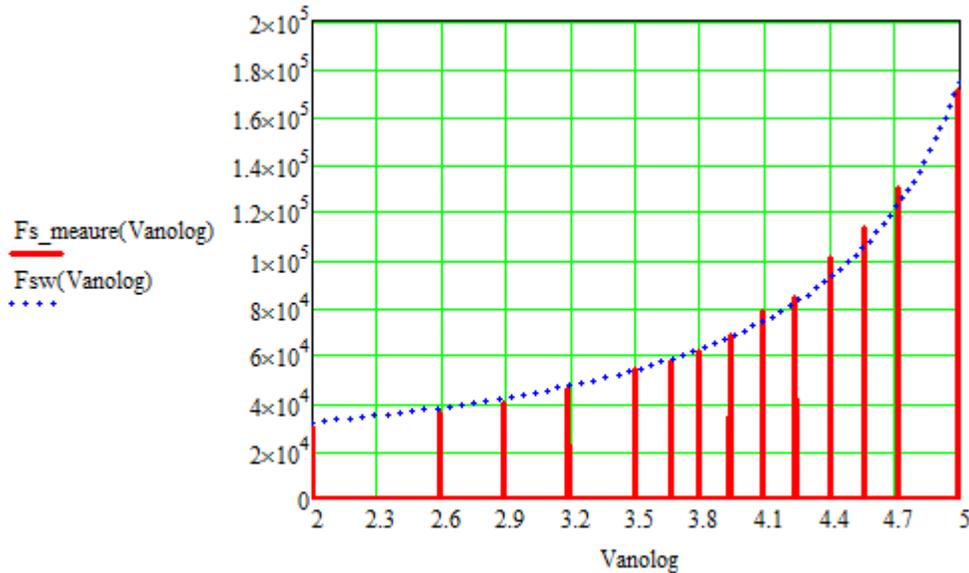

**Figure 15. Operation Frequency Curve—Comparison Between Measurement and Calculation**

Because analog dimming is critical, the dimming curve must be linear with the signal of Vanalog. Figure 16 shows the comparison between the practical measurement and calculation result. In Figure 16,  $I(V_{analog})$  represents the calculation result based on Equation 16.  $I_{o\_meure}(V_{analog})$  represents the measurement result above.

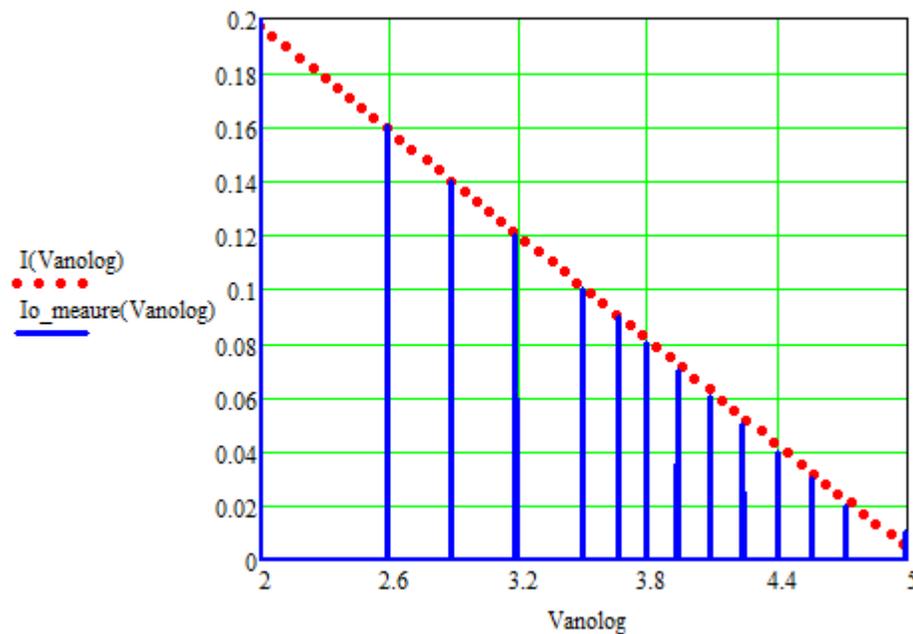

**Figure 16. Curve of Output Current—Comparison Between Measurement and Calculation When Analog Dimming is Conducted**

It can be seen that the calculation matches very well with the measurement.

### 6.2 0.05% to 5% PWM Dimming Design Measurement Result


The 0.05% to 5% PWM dimming starts after the analog dimming comes to 5% dimming level for this solution. The following measured waveforms present the PWM dimming performance.


Waveforms of channel 1—Output current when PWM dimming


Waveforms of channel 2—ISNS pin voltage of the UCC28811 device

Waveforms of channel 3—UCC28811 device input PWM dimming signal

Waveforms of channel 4—Current of the BUCK inductor

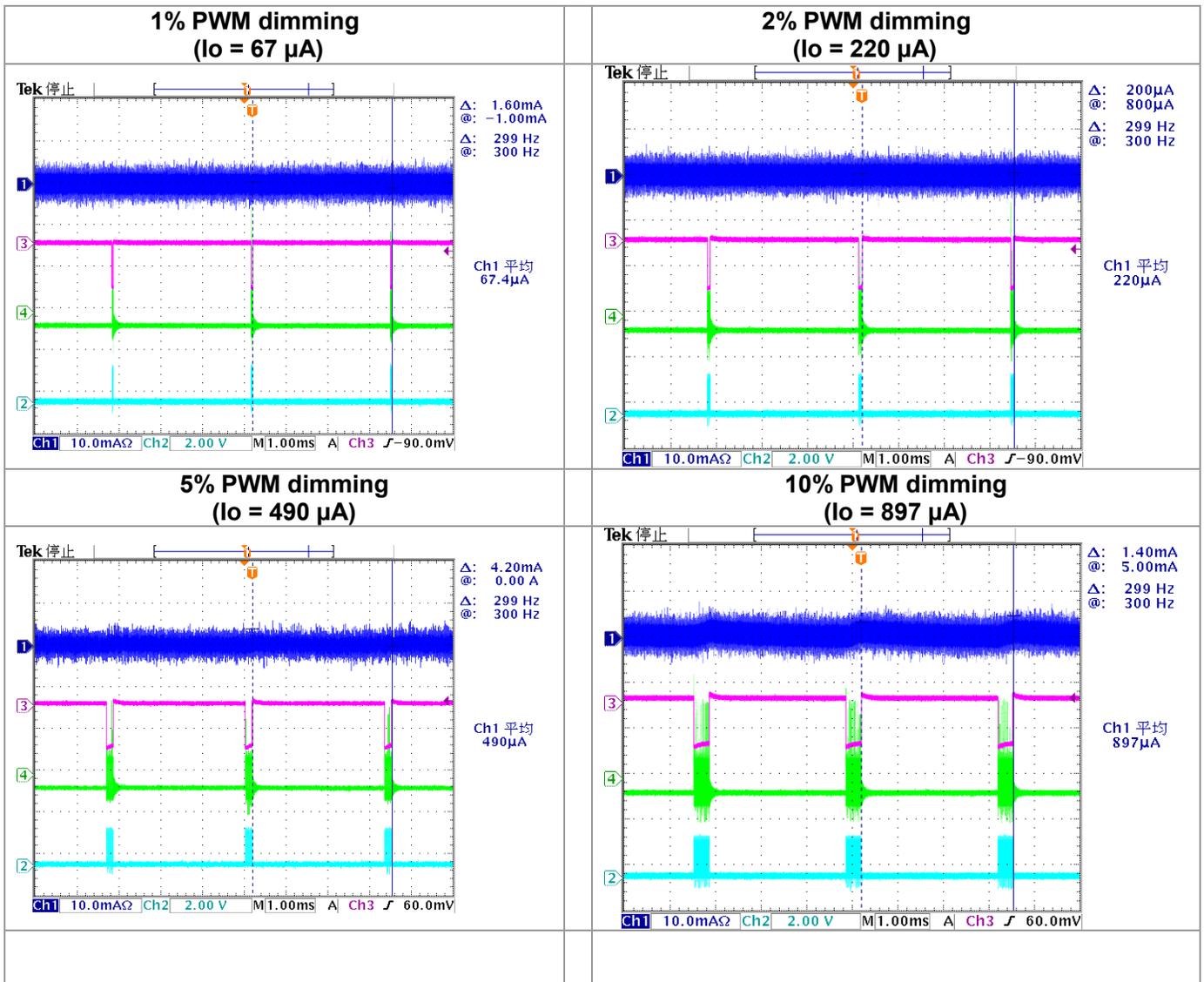

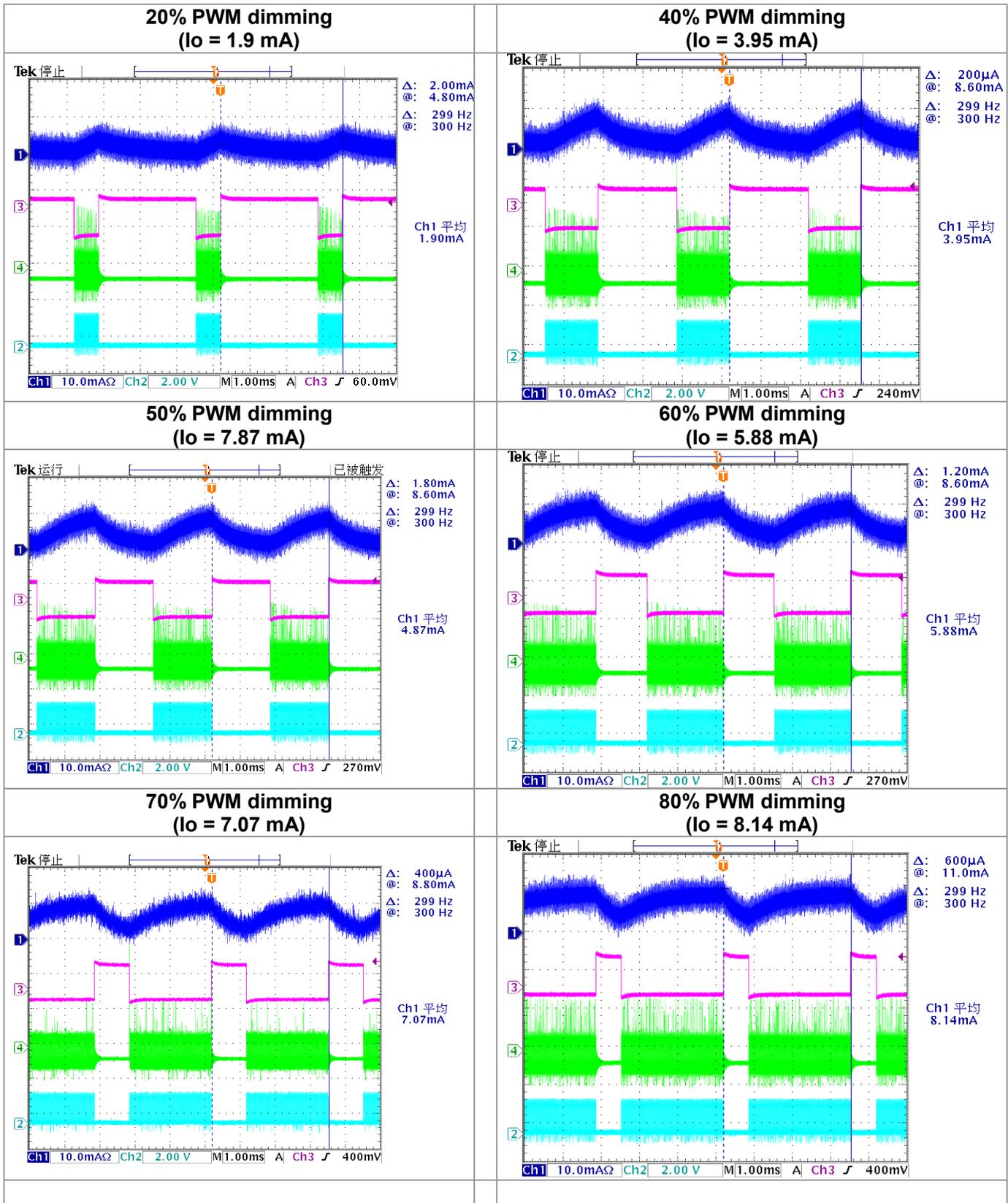

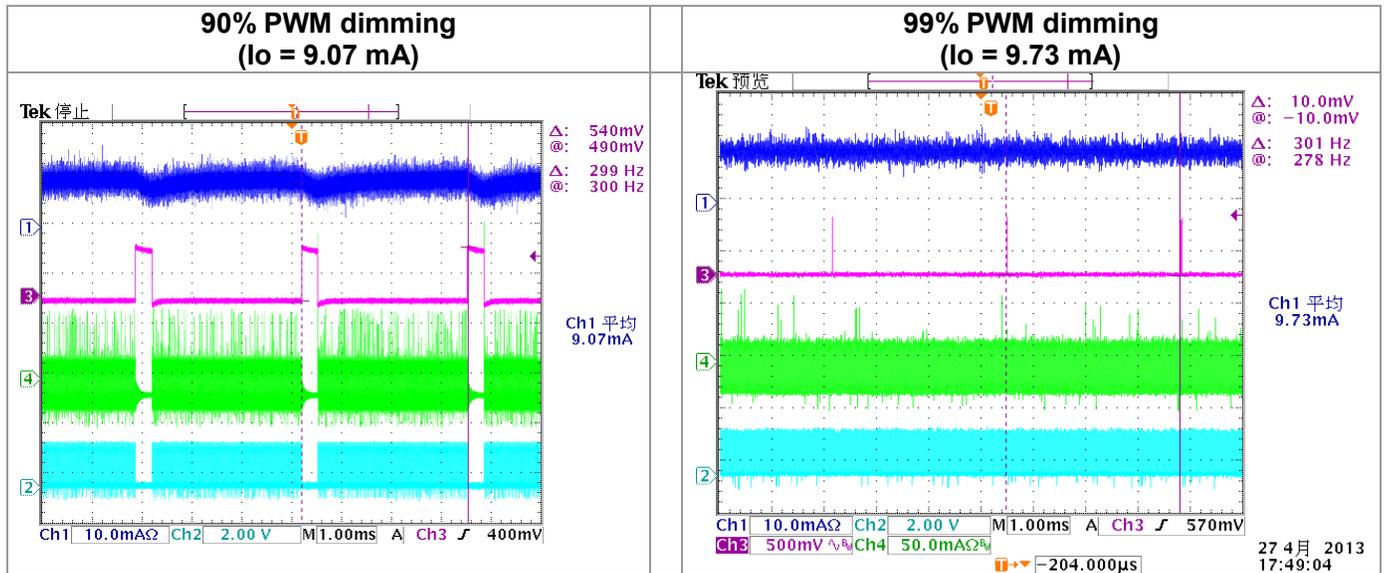

**Figure 17. Measured Waveforms When PWM Dimming is Conducted**

It can be seen that the dimming performance is very good due to the contribution of improved circuit for the analog dimming.

### 6.3 5% to 100% Analog Dimming Design Measurement Result for the Output Current

The output current must be measured during the analog dimming process. During this process, the dimming performance is very good due to the contribution of improved circuit for the analog dimming.

Waveforms of channel 1—Output current when analog dimming

Waveforms of channel 2—Current of the BUCK inductor

Waveforms of channel 3—ISNS pin voltage of the UCC28810/11 device

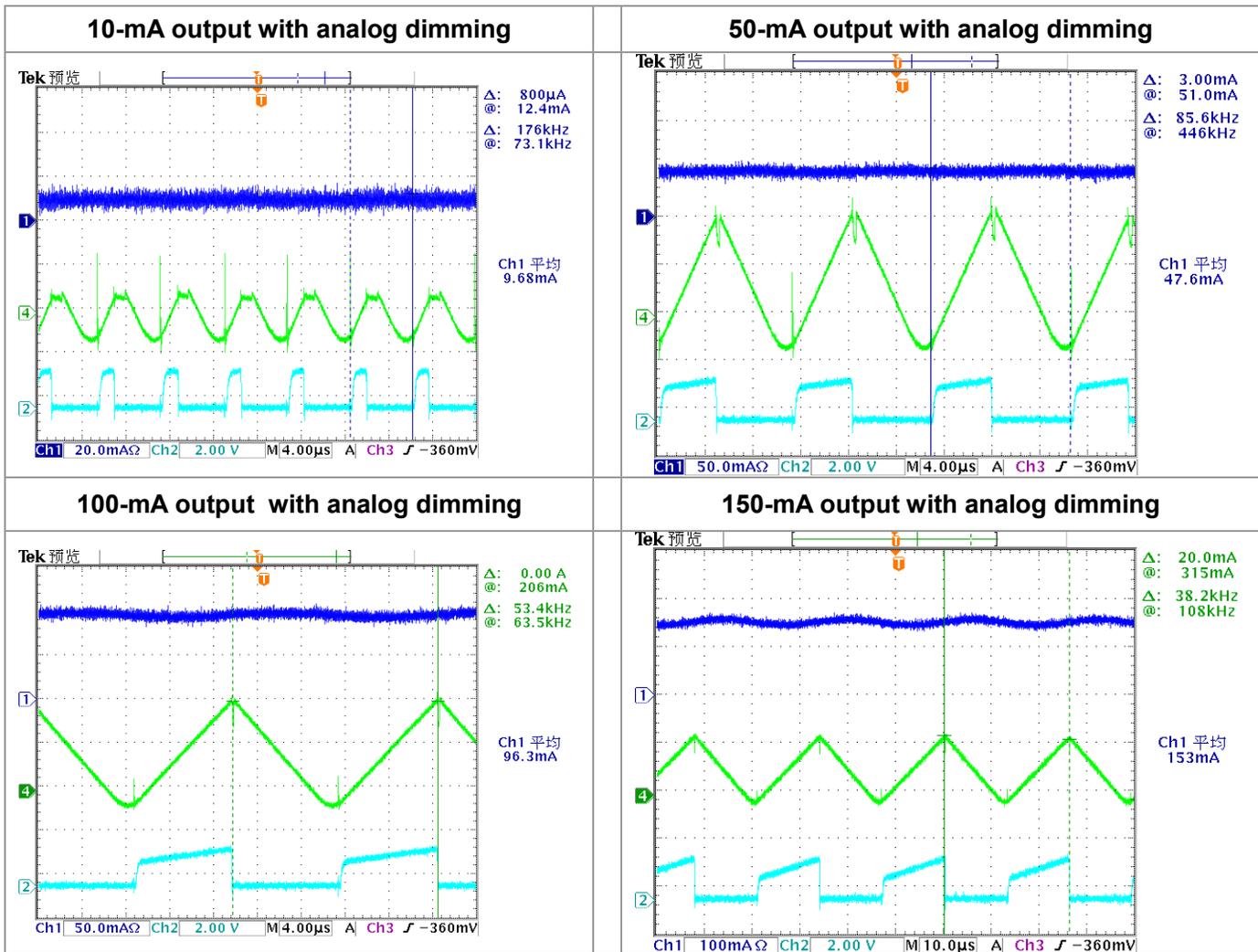


Figure 18. Measured Output Current Waveforms When Analog Dimming is Conducted

## 7 Conclusions

This paper provides the entire analysis, design, and experiment data regarding the combine dimming mode design. The result proves that the design idea is feasible for practical application.

## 8 References

- [1] UCC28811 LED Lighting Power Controller
- [2] Using the UCC28810 EVM-003 User's Guide
- [3] Using the UCC28810 EVM-002 A 0.9 A Constant Current Supply with PFC for 100-W LED

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)