

Using Voltage Supervisor for Input Over-Voltage Protection in LED Drivers

Atul Singh

ABSTRACT

Lighting electronics meant for AC-DC applications tend to get subjected to input line variations leading to sustained over-voltage on the driving circuitry. Metal oxide varistors (MOV's) meant for suppressing the transients fail at such sustained over-voltage leading to system failure and hence the need for incorporation of separate circuitry for the Input Over-Voltage Protection. The TLV809 family of supervisory circuits that provide circuit initialization and timing supervision, primarily for DSPs and processor-based systems can be used for the Over-Voltage Protection in LED drivers and other AC-DC power supply applications.

Contents


1	Introduction	1
2	Functional Block and Timing Diagram	2
3	Input Over-Voltage Protection in LED Drivers	3
4	Conventional Approach	4
5	Proposed Approach	5
6	References	6

List of Figures

1	Typical Application	2
2	Functional Block Diagram	2
3	Timing Diagram	3
4	Input Over-Voltage Protection With Conventional Approach.....	4
5	Input Over-Voltage Protection With Voltage Supervisor.....	5
6	Voltage Transient Measurement	5

1 Introduction

The TLV809K33 is a family of ultra-low current supply voltage supervisors (SVS) that monitor a single voltage rail. Because this device is a fixed-voltage monitor, it is typically configured as shown in [Figure 1](#). During power-on, $\overline{\text{RESET}}$ is asserted when the supply voltage (V_{DD}) becomes higher than 1.1 V. Thereafter, the supervisory circuit monitors V_{DD} and keeps $\overline{\text{RESET}}$ active as long as V_{DD} remains below the threshold voltage V_{IT} . An internal timer delays the return of the output to the inactive state (high) to ensure proper system reset. The delay time (t_d (typ) = 200 ms) starts after V_{DD} has risen above the threshold voltage, V_{IT} . When the supply voltage drops below the V_{IT} threshold voltage, the output becomes active (low) again. No external components are required. All the devices in this family have a fixed sense-threshold voltage (V_{IT}) set by an internal voltage divider.

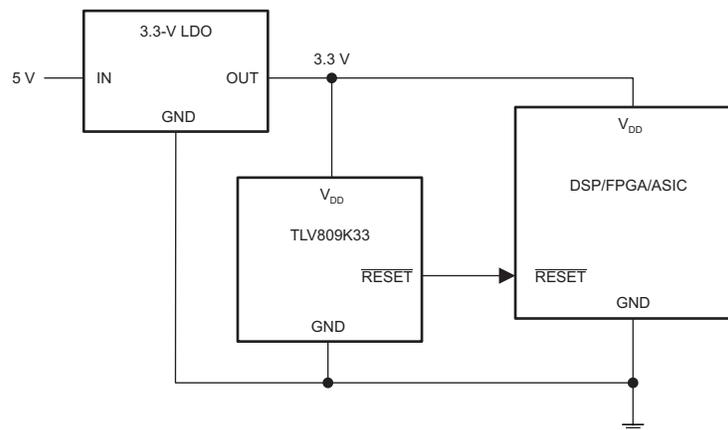
Figure 1. Typical Application

2 Functional Block and Timing Diagram

The TLV809 family of voltage supervisors has an internal Schmitt trigger that provides hysteresis of 30 mV (min) to 60 mV (max) to avoid false trigger due to V_{DD} voltage fluctuations. The V_{DD} voltage fluctuations become more pronounced and more susceptible to false trigger when it is derived from the input AC. Therefore, an internal hysteresis makes the device suitable for the shutdown in case of Input Over-Voltage in the AC-DC LED drivers. [Figure 2](#) shows the functional block diagram of TLV809.

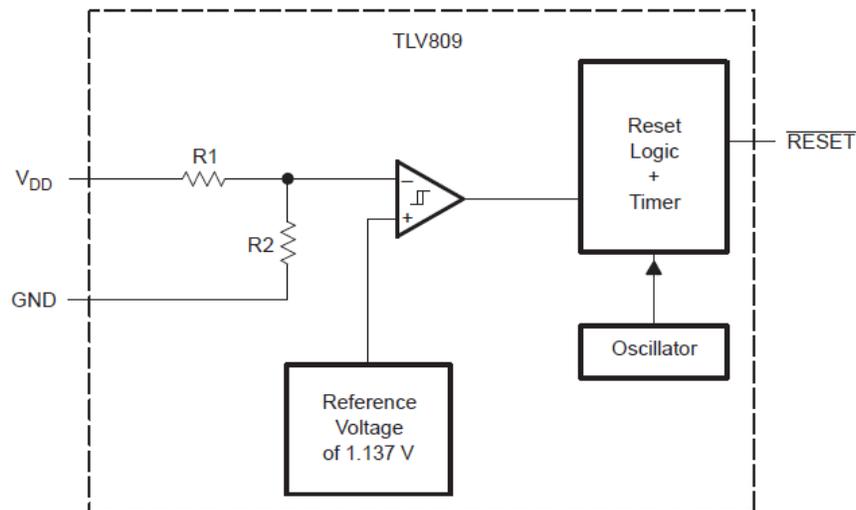

Figure 2. Functional Block Diagram

Figure 3 shows that state change of the $\overline{\text{RESET}}$ incorporates an internal delay of 200 ms and the undefined behavior of the Reset output for $V_{\text{DD}} < 1.1 \text{ V}$.

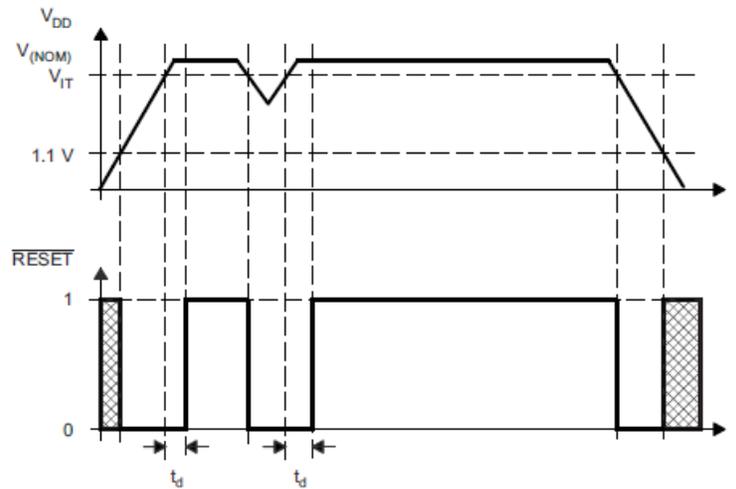


Figure 3. Timing Diagram

3 Input Over-Voltage Protection in LED Drivers

TPS92210-based LED drivers can be prevented against Input Over-Voltage by an external shutdown/retry by pulling VCG pin to ground. Voltage on the VCG is internally clamped; the clamp level varies with the operating conditions. In normal use, VCG is current fed with the voltage internally clamped. The gate of the HV Mosfet is held at a constant DC voltage using the VCG pin. It is shunt regulated to 14 V during normal operation and regulation is increased to 16 V during fault, UVLO and start-up conditions. When pulled low (below 9 V), the VCG pin pulls down the gate of the external HV Mosfet disabling the PWM action.

4 Conventional Approach

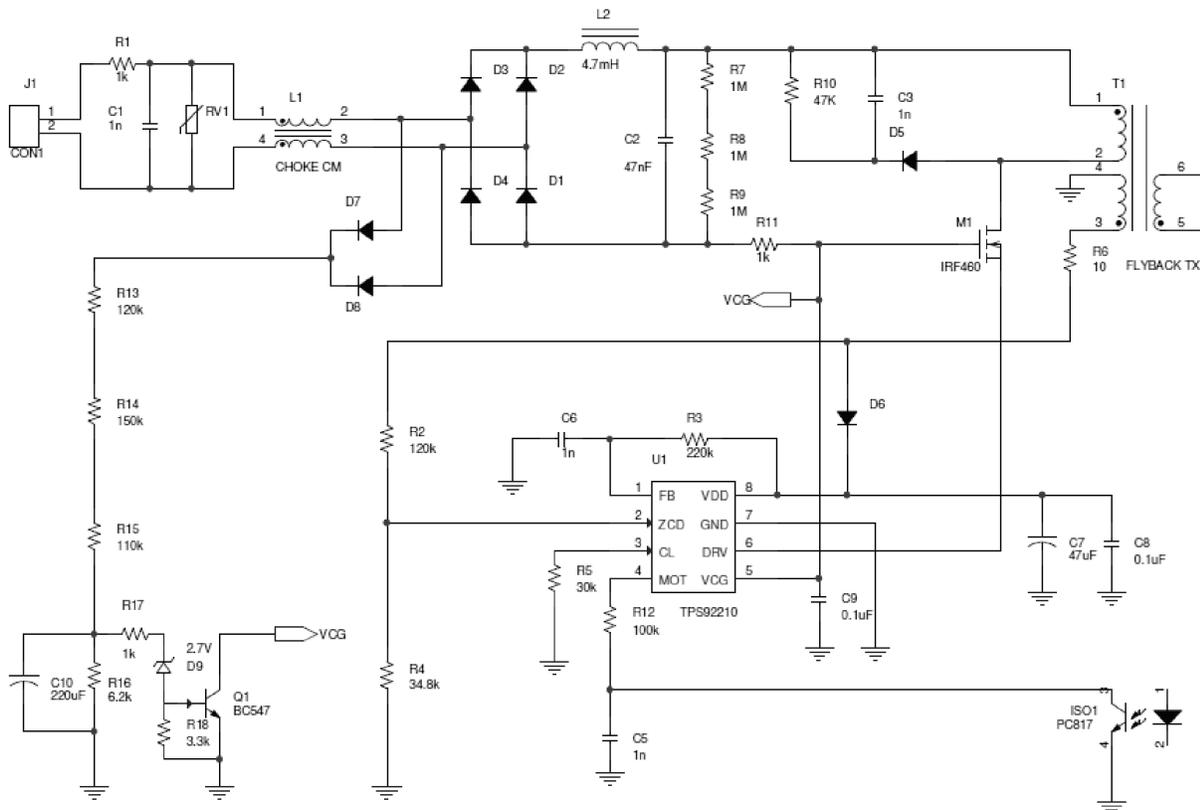


Figure 4. Input Over-Voltage Protection With Conventional Approach

The VCG pin can be pulled low by turning ON an NPN transistor with Zener diode at the base. Once the rectified AC line voltage exceeds the set point, the Zener diode conducts and turns ON the transistor that pulls down the VCG pin.

Disadvantages with the approach:

- Need of a higher capacitance C10 (220 μ F) to make the Zener diode to conduct and turn ON Q1.
- The set point for the input over the voltage cut off can not be precisely fixed as it depends on the breakdown voltage of the Zener diode. The Zener diodes have a tolerance of 5% (min) to 10% (max), which translates to shifting the AC line cutoff voltage set point.
- The AC line voltage hysteresis attainable with the above approach is more than 30 V, which is on a higher side as C10 (220 μ F) in parallel to R16 (6.2k) takes more time to discharge.

5 Proposed Approach

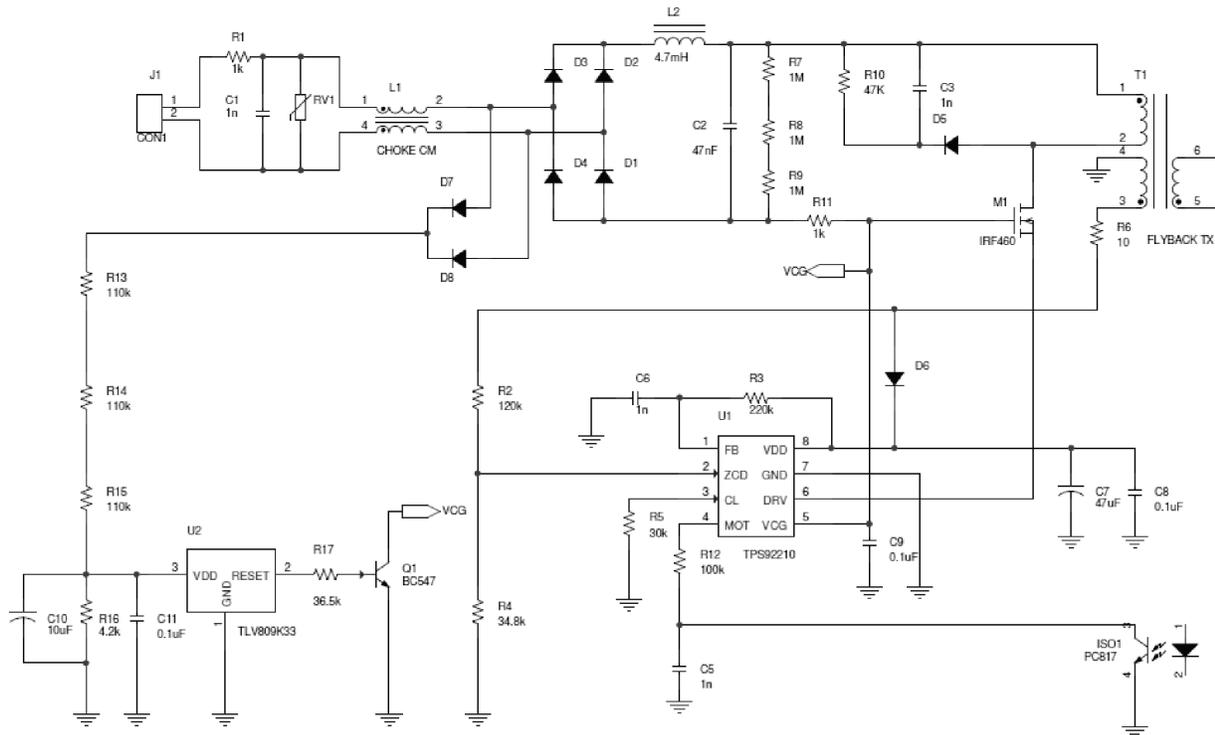


Figure 5. Input Over-Voltage Protection With Voltage Supervisor

The disadvantages with the conventional approach mentioned in Section 4 can be easily overcome using the voltage supervisor TLV809K33. The use of the TLV809K33 allows the use of smaller capacitor C10 (10 μ F) as it requires only the voltage reference for the RESET output state change from low to high. The TLV809XX has built-in rejection of fast transients on the V_{DD} pin. Transient rejection depends on both the duration and amplitude of the transient. Transient amplitude is measured from the bottom of the transient to the negative threshold voltage (V_{IT-}) of the device, as shown in Figure 6.

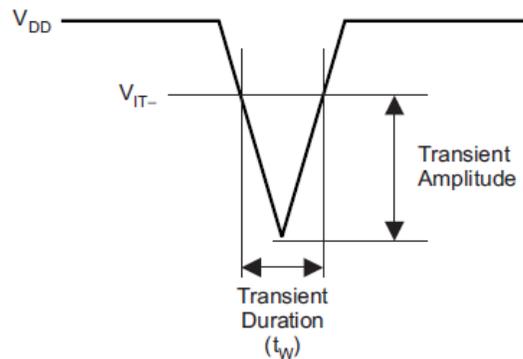


Figure 6. Voltage Transient Measurement

The TLV809XX uses a unique sampling scheme to maintain an extremely low average quiescent current of 150 nA. The TLV809XX typically consumes only about 100 nA of dc current. However, this current rises to approximately 15 μ A for around 200 μ s while the TLV809XX samples the input voltage. If the source impedance back to the supply voltage is high, then the additional current during sampling may trigger a false reset as a result of the apparent voltage drop at V_{DD} . For high V_{DD} source or trace impedance applications, it is recommended to add a small 0.1- μ F bypass capacitor near the TLV809XX V_{DD} pin. This bypass capacitor effectively keeps the average current at 150 nA and reduces the effects of a high-impedance voltage source. The voltage supervisor pulls the RESET output high once the V_{DD} voltage crosses the specified threshold (2.93 V for TLV809K33) after a delay of 200 ms, which ensures precise AC cutoff set point. The inbuilt hysteresis of 40 mV avoids false trigger and provides AC line Hysteresis of around 10 V, which is good enough for lighting applications.

The transistor Q1 (BC547) in [Figure 5](#) can be replaced by Signal Mosfet 2N7002 and used for pulling down the VCG pin. The use of signal Mosfet reduces the dependency on the input gate capacitance (C_{iss}) of the external HV Mosfet (M1).

The input over voltage shutdown used for the TPS92210-based LED driver can also be implemented for other AC-DC power supply applications requiring cutoff at higher AC line voltages.

6 References

- *TLV809J25, TLV809L30, TLV809K33, TLV809I50 3-Pin Supply Voltage Supervisors Data Sheet* ([SLVSA03](#))
- *TPS92210 Natural PFC LED Lighting Driver Controller Data Sheet* ([SLUS989](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com