

Solve Point-of-Load Power Design Challenges in Single Board Computer Applications

Richard Nowakowski, Uwe Fuhrmann, Thomas Mauer

ABSTRACT

Single-board computers (SBCs) and computer-on-module (CoM) systems embed all of the functions of a computer onto a single circuit board, and are commonly used in industrial applications in a rackmount format for factory automation and process control.

The heart of the SBC is the core processor, and newer processors have special power requirements. More recent processors include the AM57xx series Sitara™ processor family from Texas Instruments (TI), which are single or multicore Arm® Cortex®-A15 processors with an integrated digital signal processor (DSP) and industrial communication subsystem (ICSS).

SBCs are embedded in other devices to provide interfacing and control in a wide range of applications, from slot machines to factory automation programmable logic controllers (PLCs) requiring a high level of flexibility, since the environment where the SBC is placed can vary. In some end applications, airflow is not available, and a high thermally efficient solution is necessary.

SBCs come in various sizes and have a dedicated form factor requiring a high level of integration. This requirement drives reduced external components for a smaller, lighter and more reliable product in the power-supply section. Discrete step-down converters with integrated field-effect transistors (FETs) offer a high level of design flexibility and thermal performance.

Contents

1	Point-of-load Architecture Considerations	2
2	Operating Voltage Accuracy.....	2
3	Sequencing	3
4	Thermal Performance	5
5	Power Modules.....	7
6	Complete Solution	7
7	Conclusion	8
8	Additional Resources	9
9	References	9

List of Figures

1	TPS568215 Transient Response	3
2	Output Voltage Waveform for Sequential Start-up: Channel 1: 3.3 V; Channel 2: Vcore; Channel 3: PG; Channel 4: Input Voltage	4
3	TPS62135 with track, PG and EN pins for Sequencing	5
4	TPS543B20 Safe Operating Area	6
5	TPS543B20 Efficiency Plot	7

List of Tables

1	Feedback Voltage Regulation as Shown in the TPS54424 Data Sheet.....	2
2	Suggested Step-Down Converters and Controllers for SBC and CoM Systems	8

Trademarks

Sitara, D-CAP3, MicroSiP are trademarks of Texas Instruments.
 Arm, Cortex are registered trademarks of Arm Limited.
 All other trademarks are the property of their respective owners.

1 Point-of-load Architecture Considerations

SBCs benefit from a DC/DC point-of-load power solution that supports the needs of advanced processors, offers high efficiency with good thermal performance, and reduces the overall component count and total cost. SBCs are usually provided 5 V or 12 V from an external power source, but some applications have only 24 V available to provide. Since newer processors have much lower core voltages, duty-cycle limitations make it difficult to regulate a sub-1-V core rail with a 24-V input while switching at a higher frequency (such as 1 MHz or above) in order to maintain a small form factor.

As shown in [Equation 1](#), for example, to regulate 1 V from a 24-V input (with a 4.2% duty cycle), the minimum controllable on-time must be lower than 40 ns when switching at 1 MHz to avoid pulse skipping. Implementing an intermediate bus voltage which converts 24 V to either 5 V or 12 V solves the pulse skipping problem and is more suitable for powering low voltage processors.

$$\text{Minimum Controllable On - Time} = \frac{\text{Duty Cycle}}{\text{Switching Frequency}} \quad (1)$$

2 Operating Voltage Accuracy

As the process technology advances, the processors require tighter voltage accuracy and lower operating voltages. The processor data sheet may specify the voltage tolerance as a percentage or value in millivolts, which includes DC, AC, and ripple variations over the entire operating temperature range. Any voltage outside this range is not recommended, and the processor can behave unexpectedly.

You must also consider the tolerance of the resistor divider used by the DC/DC converter, the routing and trace losses of the circuit board, and the variations of the application, like input voltage variations, temperature swings and fast changes in the load. All of these factors contribute to DC/DC converter accuracy. Many designers will want headroom or margin to make sure that the solution is always within the tolerance expectation of the processor.

It is important to check the feedback voltage accuracy of the DC/DC converter in the data sheet rather than the front page. [Table 1](#) shows the regulated feedback voltage specification of the TPS54424, which is a 4.5-V to 17-V, 4-A converter with a reference accuracy that is ± 50 mV or $\pm 0.83\%$ over input voltage and temperature variations. Choosing tighter tolerance resistors improves the total output voltage accuracy. If you need more headroom, you can choose 0.1% or 0.5% resistors⁽²⁾, even though they may cost a little bit more. The additional headroom allows user to meet the total $\pm 3\%$ or $\pm 5\%$ output voltage variation with less bulk and bypass capacitance.

Table 1. Feedback Voltage Regulation as Shown in the TPS54424 Data Sheet

Parameter	Test Condition	Minimum	Typical	Maximum	Unit
Regulated feedback voltage	T _J = -40°C to 150°C, V _{IN} = 4.5V to 17V	595	600	605	mV
	T _J = 25°C, V _{IN} = 4.5V to 17V	596	600	604	mV

It is always wise to place the DC/DC converter as close to the load as possible, although layout constraints, connectors and board density requirements can interfere. A DC/DC converter's remote sense feature compensates for any voltage drops from long trace lines. This feature is especially useful when routing higher currents when the voltage drop can be a large portion of the overall DC error.

Because the load profile can change dramatically in SBC applications, it is important to consider AC transient performance. Choosing a DC/DC converter with a nonlinear control mode, such as constant on-time control, TI's D-CAP3™ control mode or DCS-control, allows a fast transient response time with reduced output capacitance. A nonlinear control mode improves AC transient performance compared to a linear control mode.⁽²⁾

It is possible to tune DC/DC converters with externally compensated current-mode control for a fast transient response as well, and synchronize them to an external clock. [Figure 1](#) shows the TPS568215 8-A step-down converter achieving a $\pm 30\text{-mV}$ total voltage deviation from a 12-V input to 1.2-V output at 1.2 MHz, with less than 200 μF of ceramic output capacitance using D-CAP3 control mode.


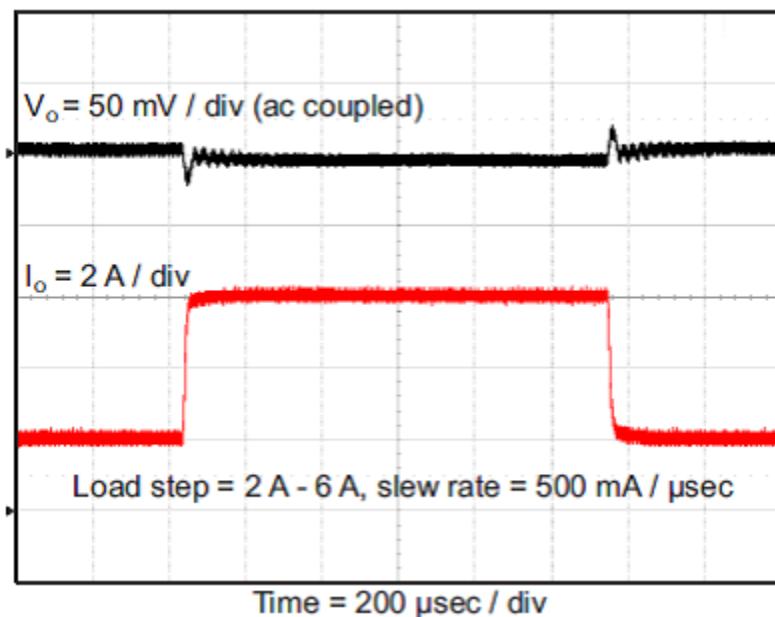


Figure 1. TPS568215 Transient Response

3 Sequencing

The processor manufacturer may recommend power sequencing to eliminate bus contention issues between the various blocks of the processor and other processors on the board, to reduce power-up/power-down stresses on the processor's internal isolation structures, or to stagger supplies to avoid start-up in-rush currents. There are several methods to power up and down a number of supplies, but the most popular method is sequential sequencing.

Sequential sequencing connects the power good (PG) pin of one voltage regulator to the enable (EN) pin of another voltage regulator. [Figure 2](#) shows the power-up configuration for two converters, and you can add more rails onto the series, which enables you to stagger the voltage rails and avoid high in-rush currents during start-up.

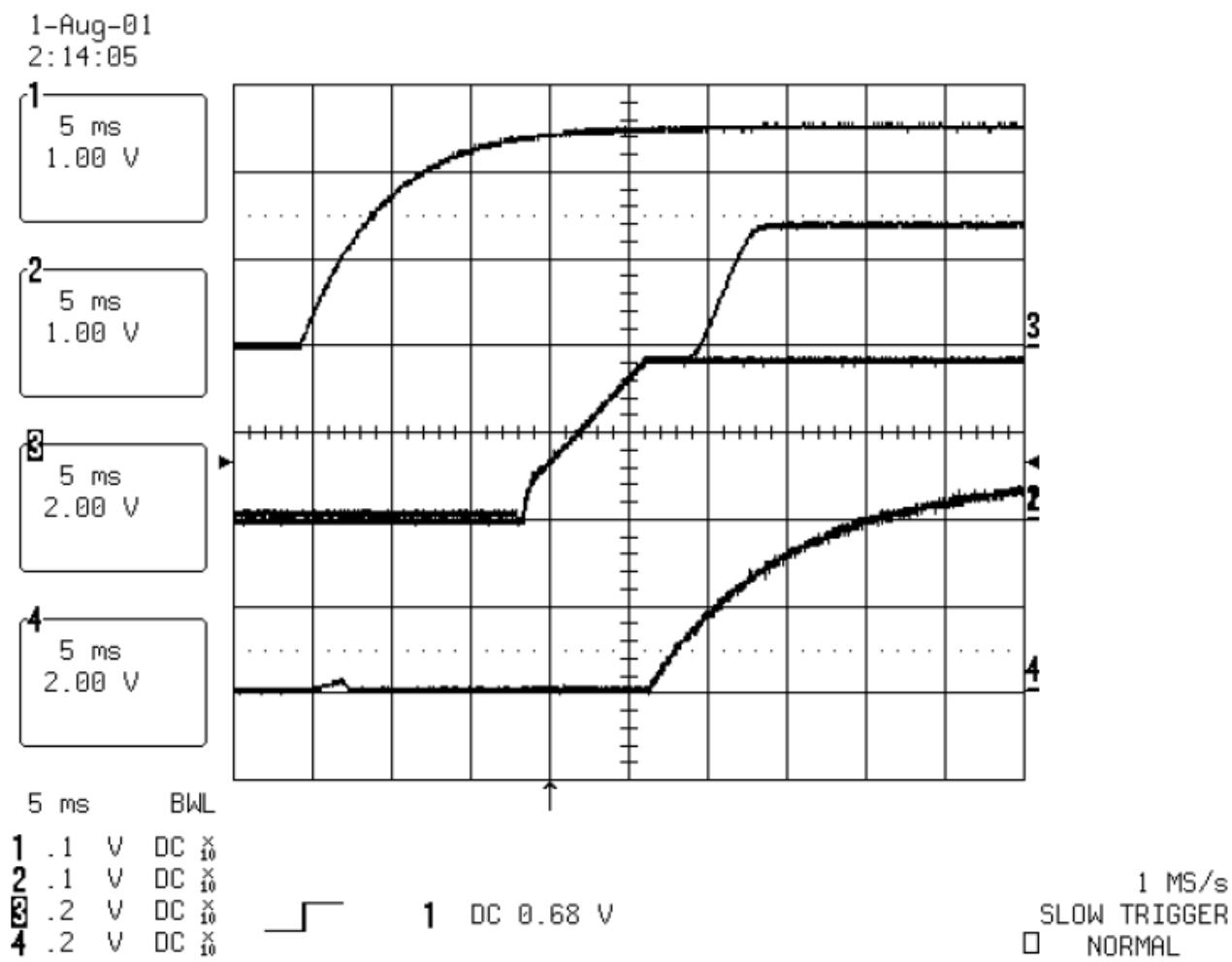

**Figure 2. Output Voltage Waveform for Sequential Start-up:
Channel 1: 3.3 V; Channel 2: Vcore; Channel 3: PG; Channel 4: Input Voltage**

A DC/DC converter with a tracking pin, such as the TPS62135 (4-A output current) shown in [Figure 3](#) or TPS62148 (2-A output current), helps with power-supply sequencing and performs a more reliable power-down function than with the PG and EN pins. Power-supply sequencers are also available that very reliably control multiple rails, but consume more board space.⁽³⁾

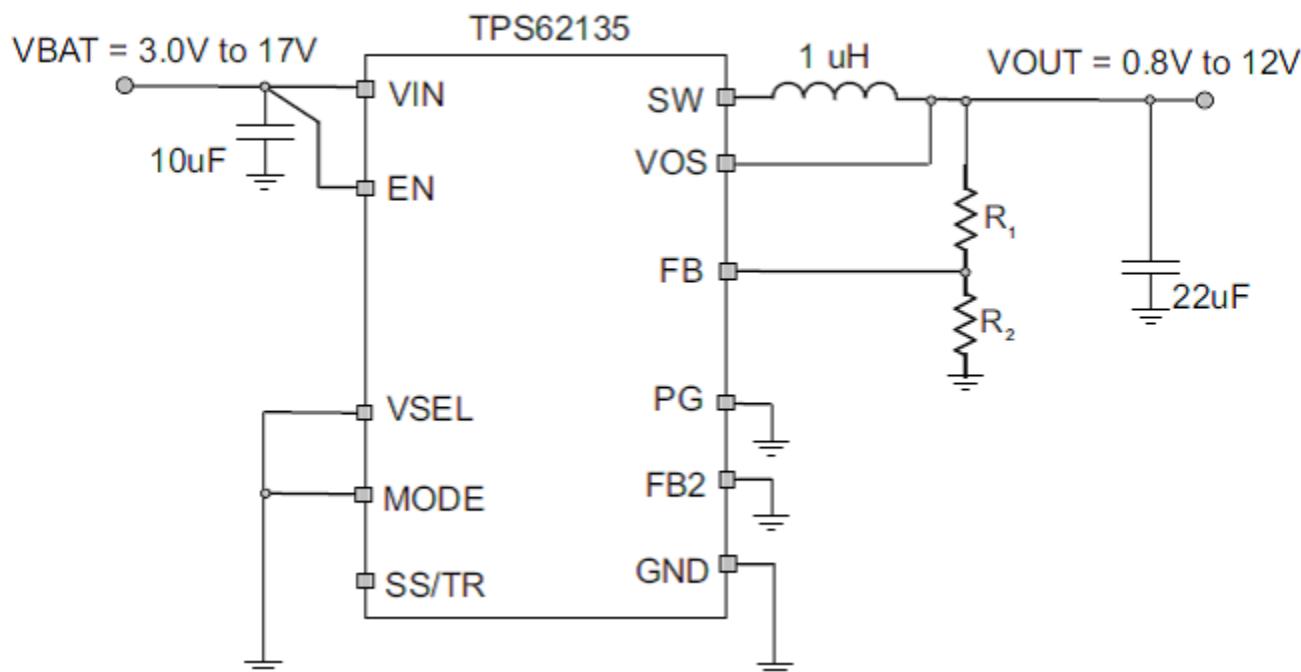


Figure 3. TPS62135 with track, PG and EN pins for Sequencing

4 Thermal Performance

SBCs are typically built on a circuit board with four, eight, or even 16 layers, depending on the form-factor constraints. Because the SBC is designed for use in a wide variety of applications, you must pay special attention to DC/DC converter selection to ensure that the SBC operates in thermally challenging environments with or without available airflow. Higher circuit board temperatures translate to lower reliability, and higher current DC/DC converters contribute significantly to the overall thermal budget.

As shown in the safe operating curve of [Figure 4](#) and the efficiency plot in [Figure 5](#), the high-efficiency TPS543B20 25-A DC/DC converter delivers 25 A and 1 V with an ambient temperature of 90°C, without airflow. At 10 A and 1 V, the entire solution will dissipate only 1 W.

Derating the DC/DC converter is good design practice when optimizing for efficiency and size. In some cases, DC/DC converters are available in pin-compatible output current options or offered with a programmable current limit to provide flexibility.

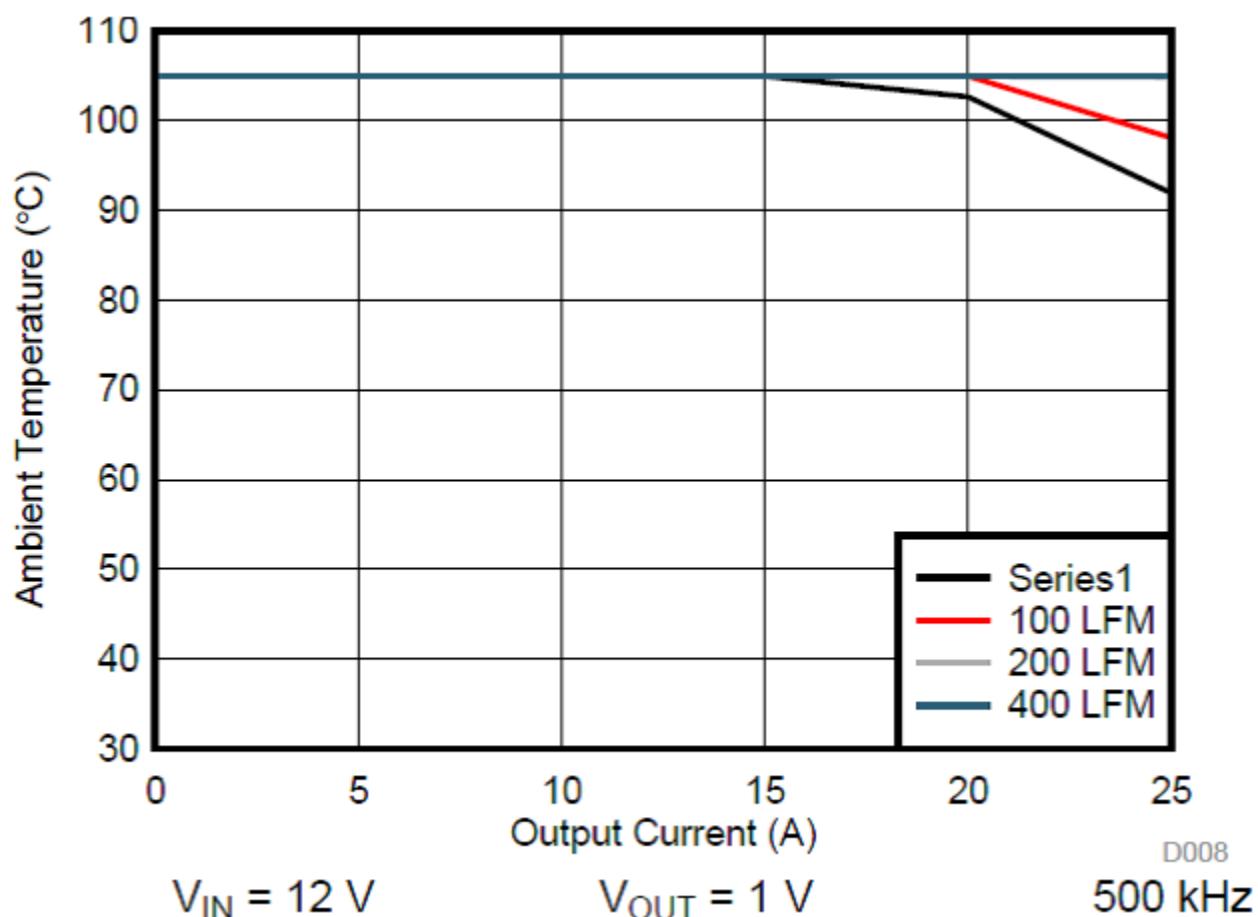


Figure 4. TPS543B20 Safe Operating Area

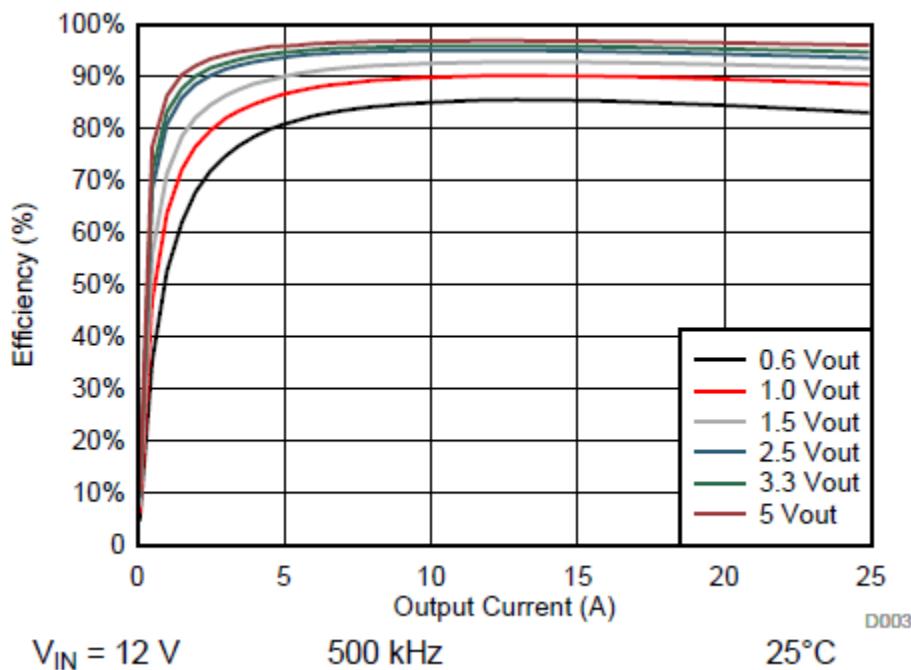


Figure 5. TPS543B20 Efficiency Plot

5 Power Modules

Power modules are quickly gaining in popularity because of their high integration, which enables faster design time, ease of use and a smaller printed circuit board (PCB). These characteristics are important in SBC and CoM systems due to the increasing number of power-supply rails, while available board space is very limited.

A common challenge with power modules or any other device that must provide the same functionality in a smaller space is thermal performance. TI's TPS82130 is a MicroSiP™ power module that accepts up to a 17-V input voltage and delivers up to 3 A of output current in a tiny 2.8mm-by-3mm package that is only 1.5 mm tall. It has an exposed thermal pad on its bottom side to improve thermal performance. Because this thermal pad connects to ground potential, using vias to internal ground layers in the PCB removes heat and decreases the power-module temperature.⁽⁴⁾

6 Complete Solution

The DC/DC converters in [Table 2](#) are ideal for powering SBCs and CoM applications. These converters feature fast transient response, tight VFB accuracy, PG and EN pins, good thermal performance and either a programmable current limit or scalability. Devices with the same package are pin-compatible for design flexibility, unless noted with a different feature in the comment column of [Table 2](#).

TI also has a wide variety of products and reference designs to solve design challenges for SBC and CoM applications.⁽⁵⁾ Reference designs such as a discrete power solution for the AM437x Sitara family show possible ways of integrating TI devices into subsystems addressing voltage regulation, transient response, thermal and sequencing challenges.⁽⁶⁾

Table 2. Suggested Step-Down Converters and Controllers for SBC and CoM Systems

Device	I _{OUT} Maximum	Input voltage	Package Size	Comment
5-V/12-V Input Rail				
TPS543C20	40 A	4.5 V to 16 V	5mm by 7mm	Remote sense, stackable
TPS543B20	25 A	4.5 V to 18 V	5mm by 7mm	Remote sense
TPS53318	14 A	4.5 V to 22 V	3.5mm by 4.5mm	Fast transient, 1.5-V power stage
TPS56C215	12 A	3.8 V to 17 V	3.5mm by 3.5mm	Fast transient
TPS568215	8 A	4.5 V to 17 V	3.5mm by 3.5mm	Fast transient
TPS53319	8 A	4.5 V to 22 V	3.5mm by 4.5mm	Fast transient, 1.5-V power stage
TPS54824	8 A	4.5 V to 17 V	3.5mm by 3.5mm	Frequency synchronization
TPS54424	4 A	4.5 V to 17 V	3.5mm by 3.5mm	Frequency synchronization
TPS62135	4 A	3 V to 17 V	2mm by 3mm	Tracking
TPS62148	2 A	3 V to 17 V	2mm by 3mm	Tracking
TPS82130	3 A	3 V to 17 V	2.8mm by 3.0mm	Power module
TPS82140	2 A	3 V to 17 V	2.8mm by 3.0mm	Power module
TPS82150	1 A	3 V to 17 V	2.8mm by 3.0mm	Power module
3.3-V/5-V Input Rail				
TPS54618	6 A	2.95 V to 6 V	3mm by 3mm	Frequency synchronization
TPS54418	4 A	2.95 V to 6 V	3mm by 3mm	Frequency synchronization
TPS62823	3 A	2.4 V to 5.5 V	1.5mm by 2mm	Small solution with 47 OnH
TPS62826	3 A	2.4 V to 5.5 V	1.5mm by 1.5mm	Highest power density
TPS62822	2 A	2.4 V to 5.5 V	1.5mm by 2mm	Small solution with 470 nH
TPS62825	2 A	2.4 V to 5.5 V	1.5mm by 1.5mm	Highest power density
TPS62821	1 A	2.4 V to 5.5 V	1.5mm by 2mm	Small solution with 470 nH

7 Conclusion

Products using SBCs and CoMs benefit from a high performance and high efficient point-of-load power solution. DC/DC converters designed to power advanced processors will solve the voltage accuracy, load transient, and power sequencing challenges. Because SBC and CoM may use in space-constrained environments with little or no airflow, small and efficient DC/DC converters are required to solve difficult thermal challenges.

8 Additional Resources

- Watch the video, "[How to meet FPGA's DC voltage accuracy and AC load transient specification](#)"
- Check out the webinar, "[DC/DC Buck Converters: What do all of these features mean?](#)"
- Learn more about [power management](#) for FPGAs and processors.
- Download the [Small Efficient Flexible Power Supply Reference Design for NXP iMX7 Series Application Processors](#).
- Read the blog post, "[Look at the details when designing an industrial PC – 1% is not always 1%](#)."

9 References

- (1) Kollman, Robert. "[Power Tip #18: Your regulator's output-voltage accuracy may not be as bad as you think](#)," EETimes, August 4, 2010.
- (2) Texas Instruments Control Mode Quick Reference Guide, SLYT710, 2018.
- (3) [TI power sequencers](#).
- (4) Horton, Sandra, and Chris Glaser, "[Improving the thermal performance of a MicroSiP power module](#)," Analog Applications Journal SLYT724, 3Q 2017.
- (5) TI [single board computers](#).
- (6) TI [AM437x Discrete Power Reference Design](#).

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), evaluation modules, and samples (<http://www.ti.com/sc/docs/samptersms.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated