

Using Input Current Limiting to Extend Battery Life



Despite constant advances in battery technology, producing a battery still involves multiple tradeoffs between different design goals such as size, self-discharge, or capacity to name a few. In applications such as wireless sensors, a battery-powered device is intended to operate for years in the field. In that case, high-energy-density, low-discharge coin cell batteries such as the ones based on Li-SOCl₂ or Li-MnO₂ chemistry are often the designer's choice. The main drawback of such batteries is their high internal resistance (ESR) and limited current capability. High ESR can prevent proper startup of the system. Moreover, if a pulsed load, typical for wireless sensors, overdrives the battery, its capacity and the lifetime can be significantly reduced. Adding a buffer capacitor to the battery can help to some extent, as explained in the [Coin Cells and Peak Current Draw White Paper](#). However, a relatively large capacitor is required to buffer the current peaks, adding to the system cost and size.

To accommodate variable battery voltage and to maximize efficiency, a DC/DC converter is often used to generate a fixed-voltage supply. [Figure 1](#) shows an example of a typical power tree of a wireless sensor. A supercapacitor can be used if there is a heavy load that requires significantly larger current than the battery can provide. Such a system might operate only once a day for less than a second, for example only to measure the temperature and transmit the data. The rest of the time the system is in standby. Therefore, the load that the battery sees has a very small duty cycle, with short but high-current pulses.

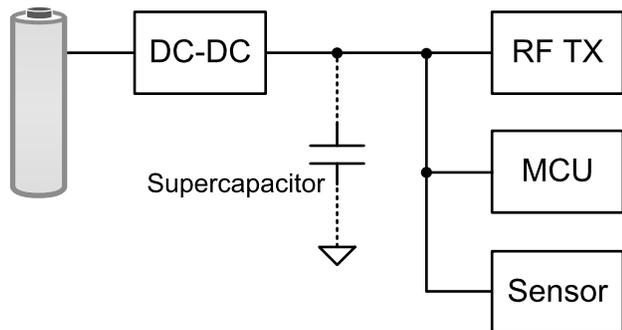


Figure 1. Power Tree of a Battery-Powered Wireless Sensor

One of the drawbacks of switch-mode converters is the inrush current generated every time the converter is turned on. If the battery ESR is not sufficiently low, the inrush current might trigger the UVLO and prevent the device from a reliable startup. This is explained in more detail in the [Achieving a Clean Startup by Using a DC/DC Converter with a Precise Enable-pin](#)

Threshold Technical Brief. This becomes more pronounced as the battery ages and its ESR increases. Even if the start is successful, the inrush current spikes can still have detrimental effects on the battery capacity and lifetime. Having to charge a supercapacitor can further increase and prolong the inrush current pulse.

For these reasons, matching a heavy pulsed load to a weak battery requires some sort of current limiting on the converter side. With its features, the TPS63900 device is tailored for such battery-powered applications. With the output current of up to 1 A, this device supports commonly-used RF standards such as BLE, LoRa and NB-IoT. [Table 1](#) lists the main features of the device, and [Figure 2](#) shows the typical application circuit. Owing to the small component count, the TPS63900 is suitable for cost-sensitive battery-powered applications.

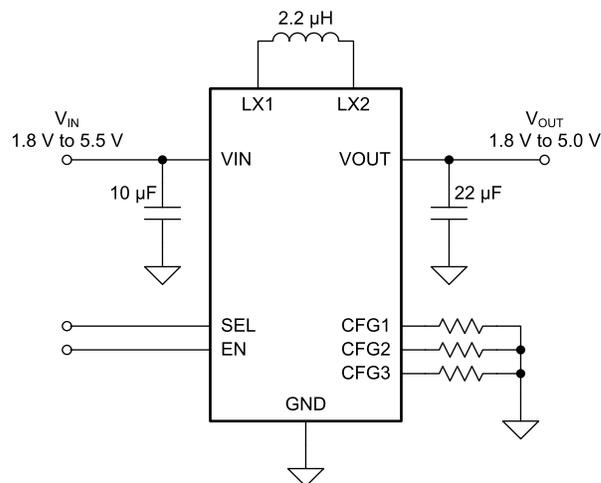


Figure 2. TPS63900 Typical Application

Table 1. TPS63900 Main Features

| | |
|-------------------------|--|
| Input voltage | 1.8 V – 5.5 V |
| Output voltage | 1.8 V – 5 V in 100-mV steps |
| Output current | up to 1 A |
| I _q | 200 nA |
| Input current limit | 1 mA, 2.5 mA, 5 mA, 10 mA, 25 mA, 50 mA, 100 mA, unlimited |
| Dynamic voltage scaling | 2-level |
| Package | DFN, 10-pin, 2.5 mm x 2.5 mm |

One of the main features of the TPS63900 device is the input current limiting. The TPS63900 can limit the current drawn from the input supply to protect the batteries that do not support high peak currents. The input current limit is active during normal operation as well as during startup. This effectively limits the inrush current, and can also be used to reliably charge heavy loads, such as a supercapacitor, from a weak battery. The converter has eight current limit settings going down to 1 mA, as listed in [Table 1](#). As an example, [Figure 3](#) shows the input current limit set at 50 mA which is active during startup.

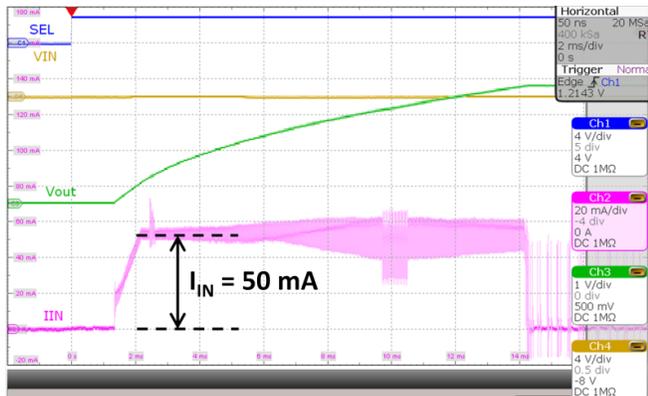


Figure 3. Inrush Current Limited at 50 mA

Besides the input current limiting, the TPS63900 has ultra-low quiescent current of only 200 nA, allowing efficiency to be above 90% even at load current of 10 μ A. The dynamic voltage scaling feature allows for two different user-selectable output voltages to be dynamically changed during operation. How this can further extend the battery life is explained in the [Extending Battery Life with Low Quiescent Current and Dynamic Voltage Scaling Application Report](#).

References

- [TPS63900 1.8-V to 5.5-V, 400-mA, 200-nA Quiescent Current Buck-Boost Converter Data Sheet](#)
- [Coin Cells and Peak Current Draw White Paper](#)
- [Achieving a Clean Startup by Using a DC/DC Converter With a Precise Enable-pin Threshold Technical Brief](#)
- [Extending Battery Life with Low Quiescent Current and Dynamic Voltage Scaling Application Report](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated