
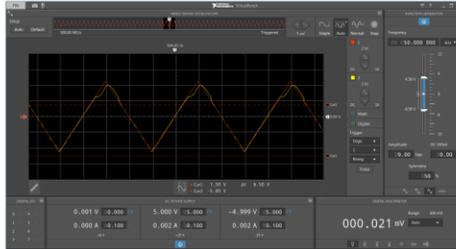



Lab Manual

TI Precision Labs – Op Amps

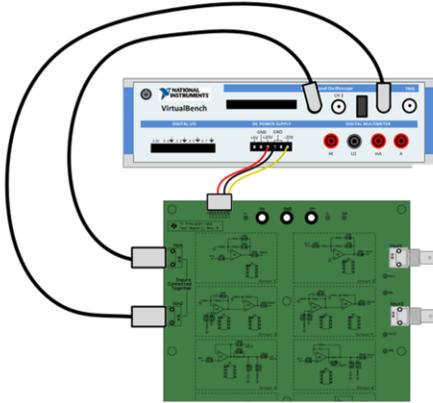

TIDesigns
PRECISION

 TEXAS INSTRUMENTS

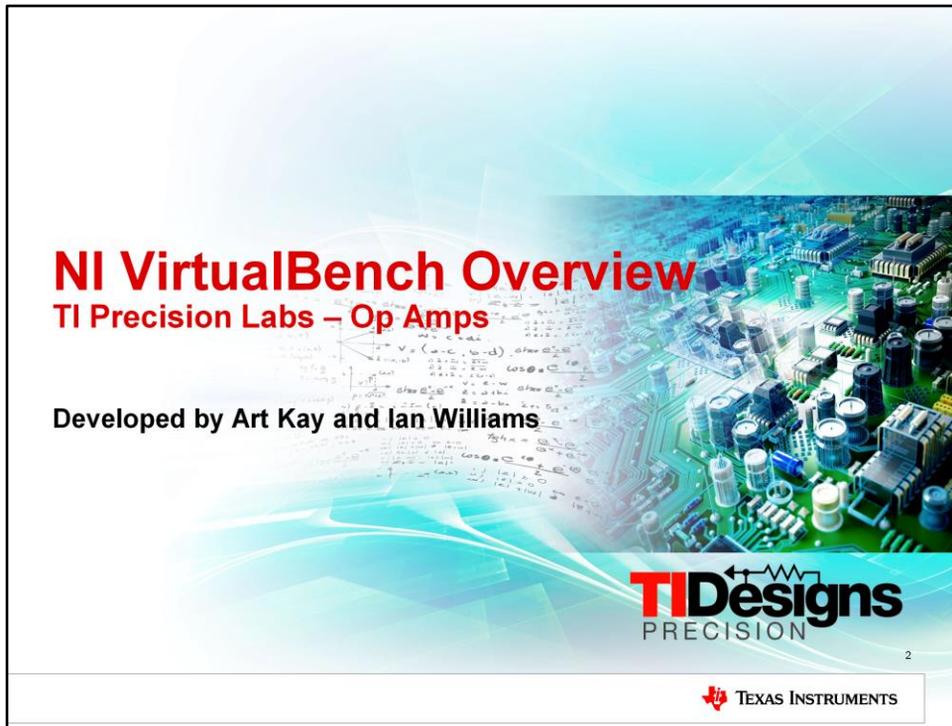

Hello, and welcome to the TI Precision Labs presentation which gives an overview of the National Instruments VirtualBench. The VirtualBench is a very powerful piece of hardware which combines multiple pieces of traditional lab equipment into one compact and easy-to-use device. This presentation will describe the features of the VirtualBench, as well as give a tutorial on how to configure the VirtualBench hardware and software.

VirtualBench Specifications

Mixed-Signal Oscilloscope

Bandwidth	100 MHz
Channels	2 analog, 34 digital
Ranges	10mV/div, 100mV/div, ... 10V/div
Sampling Rate	1 GS/s (single channel), 500 MS/s/ch (dual channel)
Waveform Measurements	cursors, 22 automatic measurements
Waveform Math	add, subtract, multiply, FFT
Record Length	1 million samples

Function Generator

Max Frequency	20 MHz (sine), 5 MHz (square)
Channels	1
Waveform Types	sine, square, ramp, triangle, DC

3



I won't go into detail on all of the specifications, but they are copied here. Some key specs to note are the 100 MHz oscilloscope bandwidth, up to 1 gigasample per second sampling rate, and up to 20MHz sinusoidal function generator.

VirtualBench Specifications

Digital Multimeter

Resolution	5 ½ digits
Measurement Functions	VDC, VAC, IDC, IAC, continuity, resistance, diode
Max Voltage	300 V max input voltage
Max Current	10 A max input current
Basic Accuracy	up to 0.015% VDC

Programmable DC Power Supply


Channels	3
Voltage/Current (Ch1)	0 to +6V / 0 to 1A
Voltage/Current (Ch2)	0 to +25V / 0 to 0.5A
Voltage/Current (Ch3)	0 to -25V / 0 to 0.5A

4



The specs are continued here for the multimeter and power supply. The multimeter has 5 and a half digits of resolution, and the three-channel power supply can support both single supply and split supply devices.


VirtualBench Front Panel

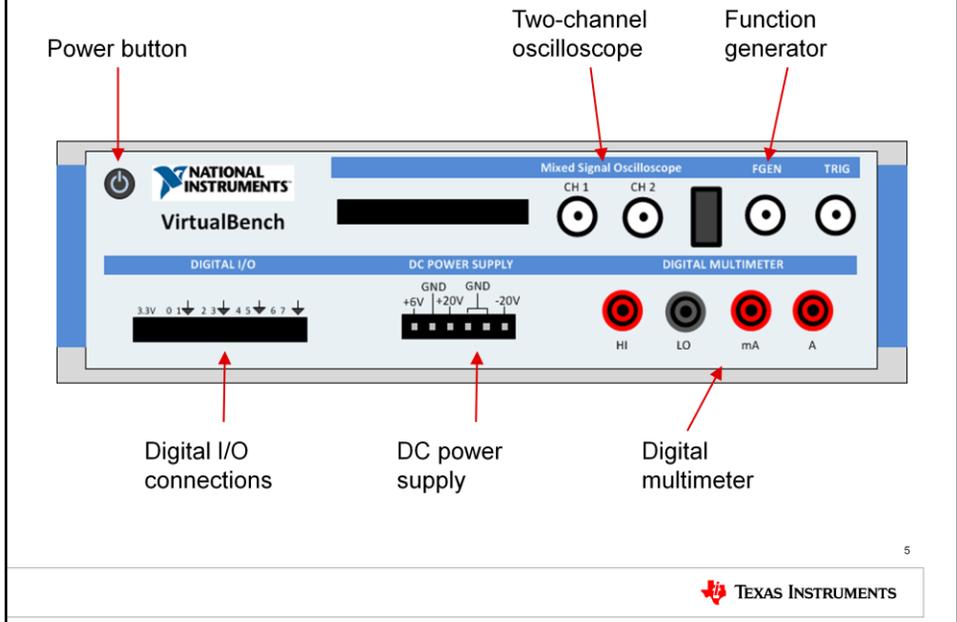

The front panel of the virtual bench is used to make connections to your system under test. You must turn on the VirtualBench by pressing the power button on the top left before using the device. Then, you can connect to the oscilloscope, function generator, digital I/O, DC power supply, and digital multimeter as required in your experiments.

VirtualBench Front Panel

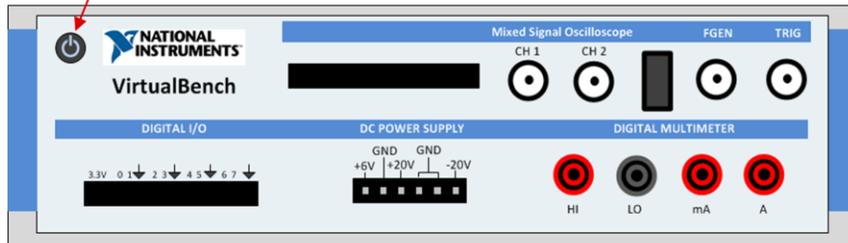Only press the On/Off Power button when instructed. This button will cause the software to auto boot on the laptop. Software booting is slow, please be patient.




6

 TEXAS INSTRUMENTS


Make sure that you only press the power when instructed. Power to the circuit is controlled using the software interface on the laptop. The front panel button is only used when you want to boot the software from initial start up.

Power Supply Voltage & Current Limits

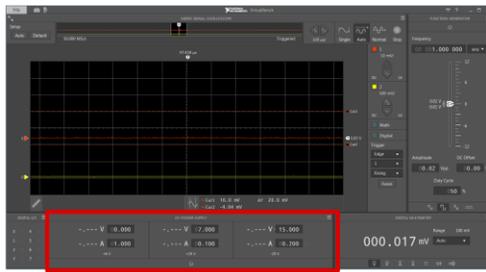

Voltage and current levels displayed here

Click in box and type to set values

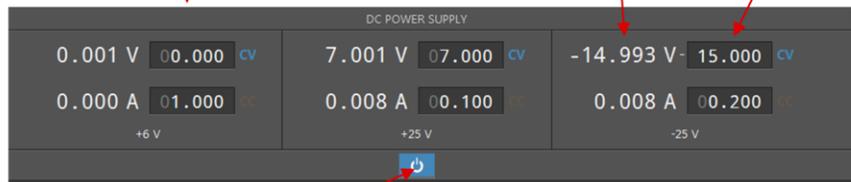


Press the power button to turn on the power supplies

7



This slide shows the location of power supply voltage and current settings. Also, the button in the center turns on and off the supplies.

Configure the Function Generator

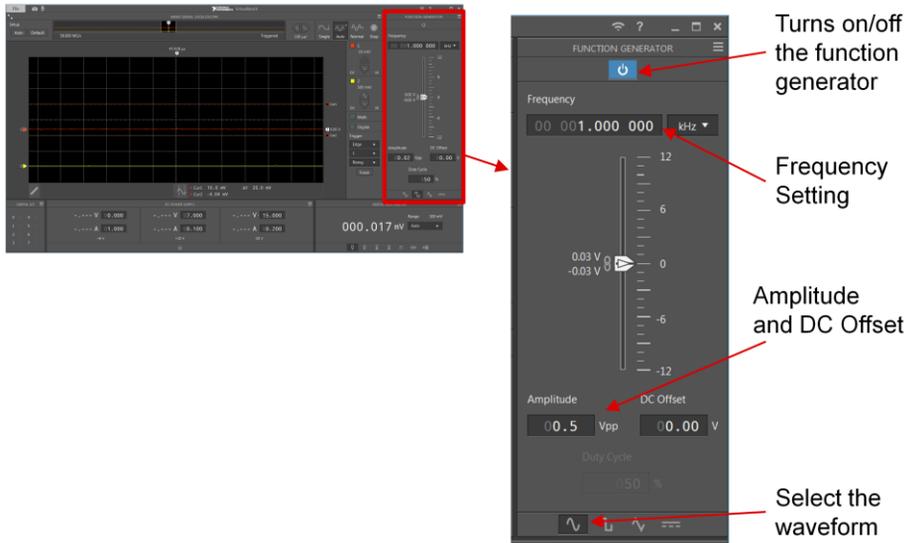


The image shows a screenshot of a function generator interface. On the left, a smaller window displays a waveform on a grid. On the right, a larger window titled 'FUNCTION GENERATOR' shows the configuration settings. Red arrows point from text labels to specific controls in the interface:

- Turns on/off the function generator:** Points to a power button icon at the top of the 'FUNCTION GENERATOR' window.
- Frequency Setting:** Points to the frequency input field, which is set to '00 001.000 000 kHz'.
- Amplitude and DC Offset:** Points to a vertical slider control. Below it, the 'Amplitude' is set to '0.5 Vpp' and the 'DC Offset' is set to '0.00 V'.
- Select the waveform:** Points to a waveform selection icon at the bottom of the 'FUNCTION GENERATOR' window.

8


This slide shows how to set the function generator.

Configure the Oscilloscope

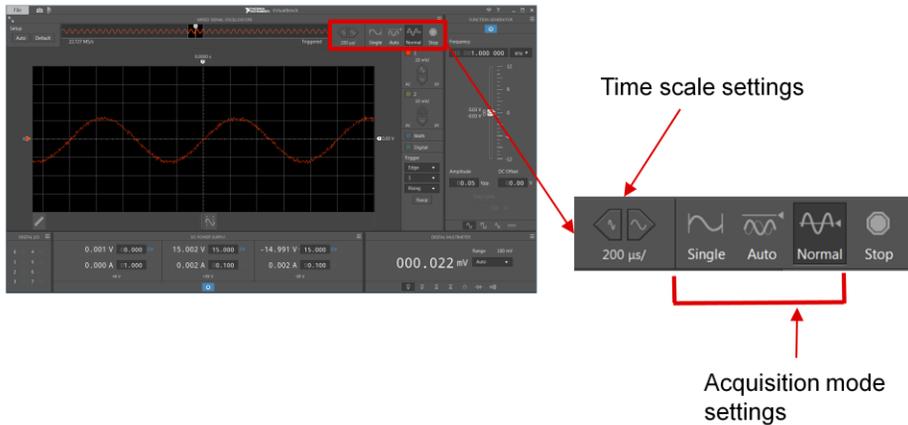

Here we set the horizontal time base on the scope as well as the triggering mode. "Auto" is untriggered roll or automatic triggering. Normal is triggered. For periodic signals it is best to use normal mode.

Configure the Oscilloscope

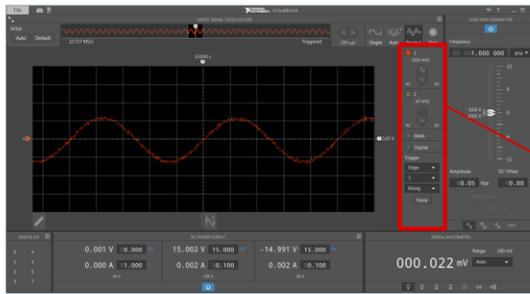

Press to enable channels

Vertical scale

Enable/Disable Math and Digital functions

Trigger settings, channel


The settings menu is a vertical panel with the following elements from top to bottom: a red square icon for channel 1, a '200 mV/' label with a vertical scale knob, an 'AC' filter icon, a '1X' magnification label, a green square icon for channel 2, a '10 mV/' label with a vertical scale knob, another 'AC' filter icon, another '1X' magnification label, a 'Math' button, a 'Digital' button, a 'Trigger' section with a dropdown menu set to 'Edge', a channel selection dropdown set to '1', a 'Rising' trigger type dropdown, and a 'Force' button.

10



Here we can set the vertical scale on the scope

Oscilloscope Settings – Coupling & Probe

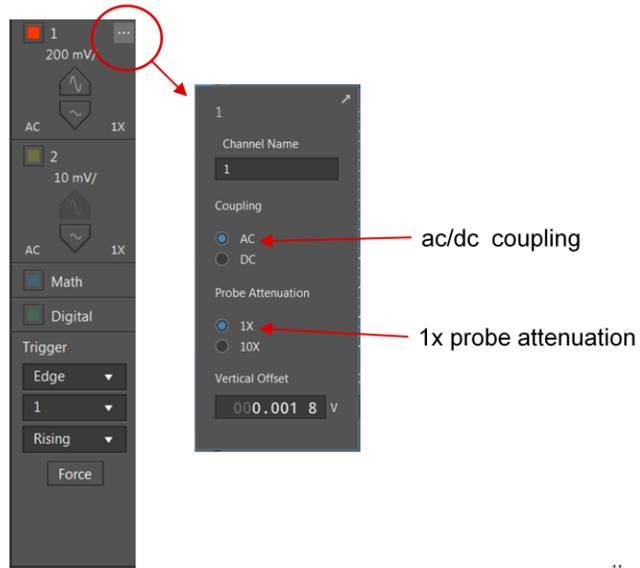


11



The ac/dc coupling is in a hidden button. Hover your mouse above the corner and click for these menus

Oscilloscope Cursors

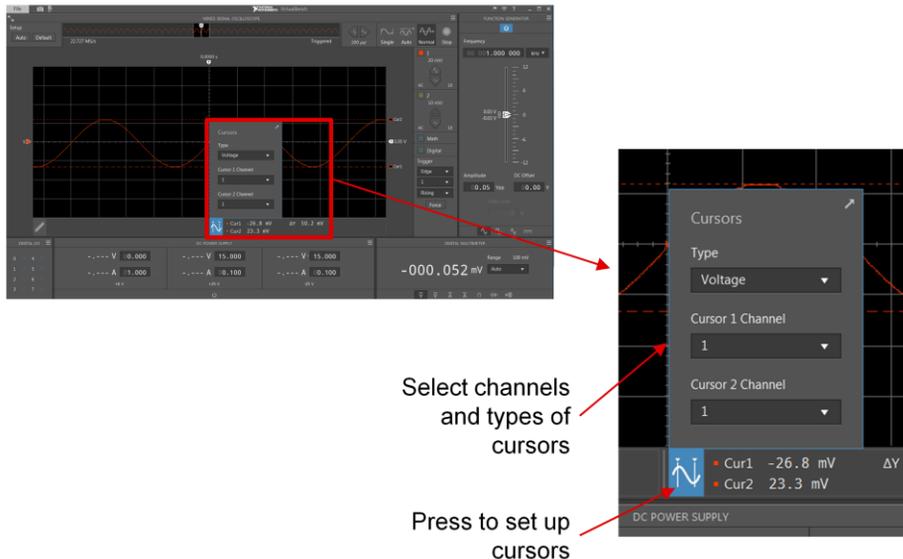


12




Cursors may be used to measured oscilloscope signals. Click the cursor icon, located above the power supply settings, to open the cursor menu. Select voltage type, then select the channel for the cursors.

Oscilloscope Cursors

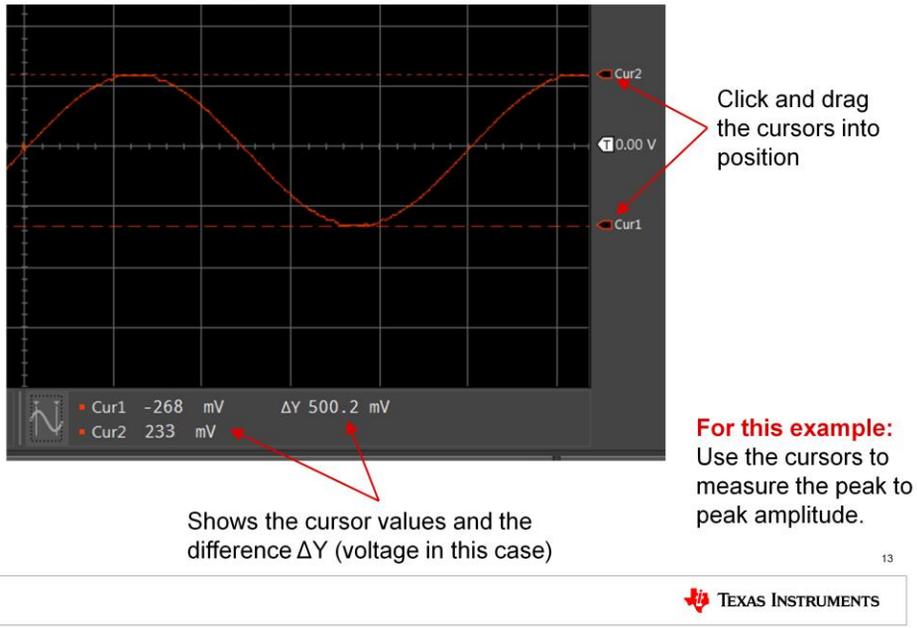

The cursors location may be adjusted to make a measurement. Click and drag the cursor indicators into position at the top and bottom of the sinusoidal waveform. The voltage level at each cursor, as well as the delta Y, in this case voltage difference, will be displayed next to the cursor icon. Use the cursors to measure the signal's peak-to-peak amplitude.

Measurement Options

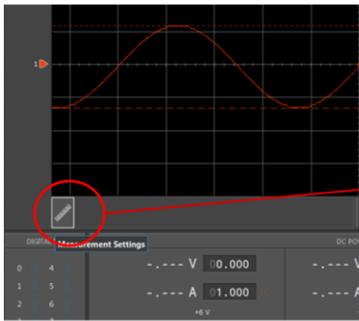

Select channel to measure

The 'Measurements' window is open, showing a list of measurements on the left and a grid of measurement options on the right. A red arrow points to '1' in the 'Oscilloscope' list, and another red arrow points to the 'Peak-to-peak' measurement option in the 'Voltage' section.

Time	Voltage
Frequency: 1.0062 kHz	Amplitude: 50.2 mV
Pos Pulse Width: 499.48 μ s	High: 23.0 mV
Pos Duty Cycle: 50.3 %	Low: -27.2 mV
Period: 993.87 μ s	Peak-to-peak: 50.2 mV
Neg Pulse Width: 494.39 μ s	Maximum: 23.0 mV
Neg Duty Cycle: 49.7 %	Minimum: -27.2 mV
Rise Rate: 137 V/s	Mean: -2.14 mV
Rise Time: 294.09 μ s	RMS: 18.4 mV
Fall Rate: 135 V/s	Overshoot: ---
Fall Time: 297.79 μ s	

For this example:
Channel = 1
Measurement 1 = Frequency
Measurement 2 = Peak-to-peak


Select measurement to display

14



The VirtualBench can also make measurements automatically. Click the ruler icon, above the digital I/O settings, to open the measurement options window. Here you can select what channel to measure, and which measurement rate you want to display.

More on the Measurement Options

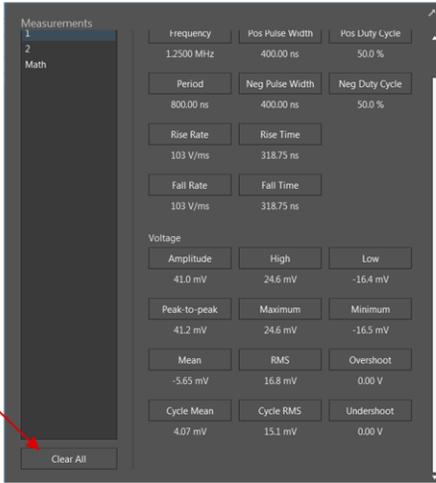

The screenshot shows a measurement options menu with a list of measurements on the left and a grid of options on the right. The list includes '1', '2', and 'Math'. The 'Clear All' button is at the bottom of the list. The right side of the menu is organized into sections: Frequency (1.2500 MHz, 400.00 ns, 50.0 %), Period (800.00 ns, 400.00 ns, 50.0 %), Rise Rate (103 V/ms, 318.75 ns), Fall Rate (103 V/ms, 318.75 ns), Rise Time, and Fall Time. The Voltage section includes Amplitude (High/Low: 41.0 mV, 24.6 mV, -16.4 mV), Peak-to-peak (Maximum/Minimum: 41.2 mV, 24.6 mV, -16.5 mV), Mean (RMS/Overshoot: -5.65 mV, 16.8 mV, 0.00 V), Cycle Mean (Cycle RMS/Undershoot: 4.07 mV, 15.1 mV, 0.00 V).


Use "Clear All" to remove old measurements

Use slider to see all options

TEXAS INSTRUMENTS

“Clear All” and the slider feature can help to use this effectively.

Measurement Results

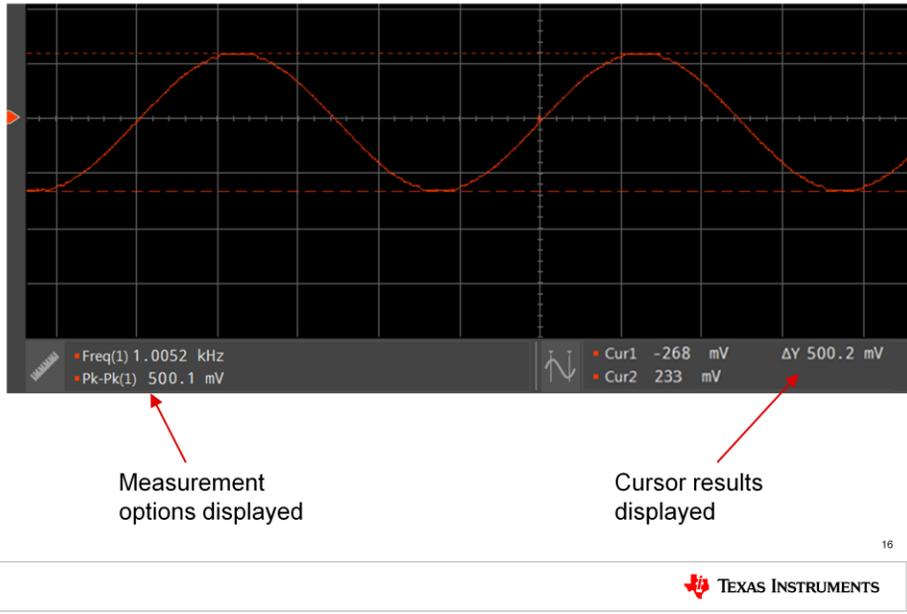

The measurement results are displayed next to the ruler icon. You should read a result of 1kHz, 500mVpp – the same as the function generator. The amplitude should be the same as the delta Y measurement from the cursor.

V_{OS} & I_B – Lab
TI Precision Labs – Op Amps

Developed by Art Kay and Ian Williams

TIDesigns
PRECISION

17

 TEXAS INSTRUMENTS

Hello, and welcome to the presentation for the TI Precision Lab supplement for op amp input offset voltage (V_{OS}) and input bias current (I_B). This lab will walk through detailed calculations, SPICE simulations, and real-world measurements that greatly help to reinforce the concepts established in the op amp V_{OS} and I_B lecture.

Required/Recommended Equipment

- Calculation
 - Pencil and paper
 - **Recommended:** MathCAD, Excel, or similar
- Simulation
 - SPICE simulation software
 - **Recommended:** TINA-TI™
- Measurement
 - TI Precision Labs PCB from Texas Instruments
 - Oscilloscope
 - $\pm 12\text{V}$ power supply
 - **Recommended:** National Instruments VirtualBench™

The detailed calculation portion of this lab can be done by hand, but calculation tools such as MathCAD or Excel can help greatly.

The simulation exercises can be performed in any SPICE simulator, since Texas Instruments provides generic SPICE models of the op amps used in this lab. However, the simulations are most conveniently done in TINA-TI, which is a free SPICE simulator available from the Texas Instruments website. TINA simulation schematics are embedded in the presentation.

Finally, the real-world measurements are made using a printed circuit board, or PCB, provided by Texas Instruments. If you have access to standard lab equipment, you can make the necessary measurements with any oscilloscope and $\pm 12\text{V}$ power supply. However, we highly recommend the VirtualBench from National Instruments. The VirtualBench is an all-in-one test equipment solution which connects to a computer over USB or Wi-Fi and provides power supply rails, analog signal generator and oscilloscope channels, and a 5 ½ digit multimeter for convenient and accurate measurements. This lab is optimized for use with the VirtualBench.

Experiment 1

$R_{IN} = 0\Omega$


19



In experiment 1, we'll determine the effects of VOS and IB in a circuit where the input resistance, R_{IN} , is equal to 0 ohms.

Calculation – $R_{IN} = 0\Omega$

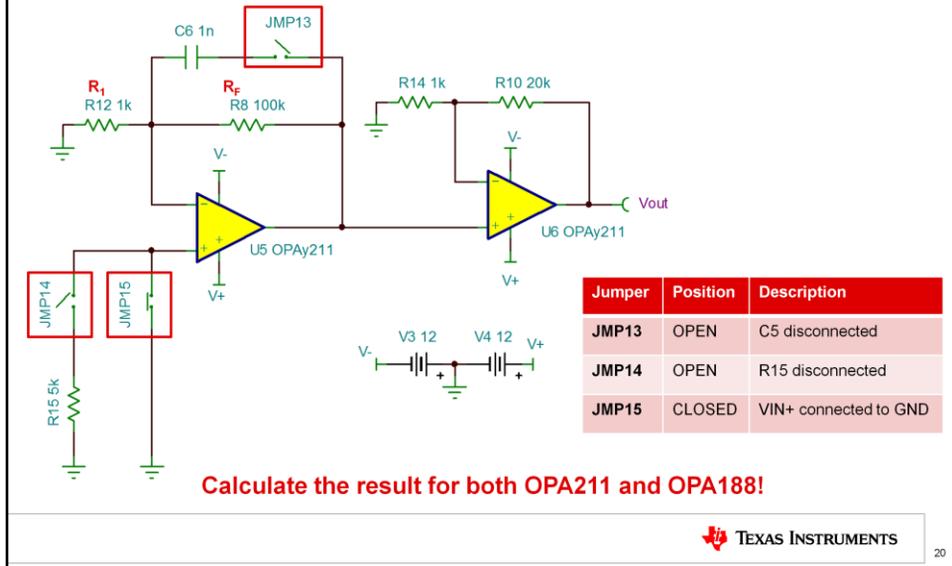Calculate the total output voltage due to V_{OS} and I_B for the circuit shown below. Use the typical and maximum values for V_{OS} and I_B given on the next slide.



First, calculate the expected total output voltage due to V_{OS} and I_B for the circuit shown here, using the techniques and equations given in the V_{OS} and I_B lecture. Take note of the jumper positions in the table. JMP13 and JMP14 are open, and JMP15 is closed. JMP15 shorts the non-inverting input of U5 to ground, causing R_{IN} to be 0 ohms.

Calculate the output voltage twice – first with the OPA211 selected for U5 and U6, then with the OPA188. The different parameters of these op amps will give you different results.

Calculation – $R_{IN} = 0\Omega$

PARAMETER		OPA211			UNIT
		MIN	TYP	MAX	
Input Offset Voltage	V_{OS}		± 30	± 125	μV
Input Bias Current	I_B		± 60	± 175	nA

PARAMETER		OPA188			UNIT
		MIN	TYP	MAX	
Input Offset Voltage	V_{OS}		± 6	± 25	μV
Input Bias Current	I_B		± 160	± 1400	pA

Device	Typical Output	Maximum Output
OPA188	$\pm 13mV$	$\pm 56mV$
OPA211	$\pm 191mV$	$\pm 635mV$

21



In order to perform the calculations, you need to know the typical and maximum values of V_{OS} and I_B for each op amp. Those values are given here.

Enter your answers in the table at the bottom of the slide. The solutions are already provided to allow you to check your work.

Calculation – $R_{IN} = 0\Omega$

OPA211

Calculate typical output error from Vos & Ib

$$i_b = \pm 60\text{nA}$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1\text{k}\Omega$$

$$V_{ib} = i_b R_{eq} = \pm 60\mu\text{V}$$

$$V_{os} = \pm 30\mu\text{V}$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21(\pm 30\mu\text{V} + \pm 60\mu\text{V})$$

$$V_{out_error} = \pm 191\text{mV or } \pm 64\text{mV}$$

$$V_{out_error} = \pm 191\text{mV Choose the largest}$$

Calculate maximum output error from Vos & Ib

$$i_b = \pm 175\text{nA}$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1\text{k}\Omega$$

$$V_{ib} = i_b R_{eq} = \pm 175\mu\text{V}$$


$$V_{os} = \pm 125\mu\text{V}$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21(\pm 125\mu\text{V} + \pm 175\mu\text{V})$$

$$V_{out_error} = \pm 106\text{mV or } \pm 636\text{mV}$$
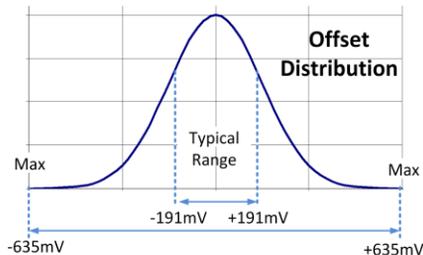
$$V_{out_error} = \pm 635\text{mV Choose the largest}$$



22



One important point to note is that IB and VOS can be positive or negative. This means that there are different possibilities for the output voltage due to VOS and IB which must all be considered.

First, calculate R_{EQ} , the equivalent input resistance, then multiply R_{EQ} by I_B to determine the input voltage due to I_B . Next, use the equation $V_{out} = G_1 G_2 (V_{os} + V_{ib})$, gain of the first stage, times G_2 , gain of the second stage, times the sum of V_{OS} and V_{IB} to calculate the total output. Again, there are four possibilities. Pick the largest value.

Repeat the same steps, using the maximum values instead of the typical values.

Calculation – $R_{IN} = 0\Omega$

OPA188

Calculate typical output error from Vos & Ib

$$i_b = \pm 160\text{pA}$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1\text{k}\Omega$$

$$V_{ib} = i_b R_{eq} = \pm 0.16\mu\text{V}$$

$$V_{os} = \pm 6\mu\text{V}$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21 (\pm 6\mu\text{V} + \pm 0.16\mu\text{V})$$

$$V_{out_error} = \pm 13\text{mV or } \pm 12\text{mV}$$

$$V_{out_error} = \pm 13\text{mV Choose the largest}$$

Calculate maximum output error from Vos & Ib

$$i_b = \pm 1400\text{pA}$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1\text{k}\Omega$$

$$V_{ib} = i_b R_{eq} = \pm 1.4\mu\text{V}$$


$$V_{os} = \pm 25\mu\text{V}$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21 (\pm 25\mu\text{V} + \pm 1.4\mu\text{V})$$

$$V_{out_error} = \pm 56\text{mV or } \pm 50\text{mV}$$
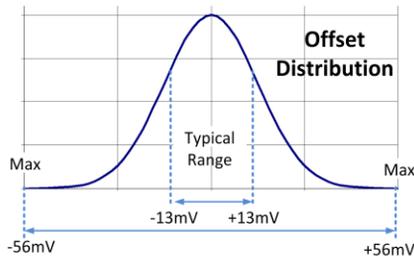
$$V_{out_error} = \pm 56\text{mV Choose the largest}$$



23



Repeat the same procedure for the OPA188. The different specifications of the OPA188 will give a different output voltage result in both the typical and maximum case.

Simulation Setup – $R_{IN} = 0\Omega$


Click **Analysis** → **DC Analysis** → **Calculate nodal voltages** to simulate the total output voltage from V_{OS} and I_B .

The screenshot shows the TI schematic editor interface. The main window displays a circuit diagram with two op-amp stages, U5 and U6, both labeled OPAy211. U5 is configured as a voltage follower with a feedback resistor R8 (100k) and a capacitor C6 (1n). U6 is configured as an inverting amplifier with a feedback resistor R10 (20k) and an input resistor R14 (1k). The circuit also includes resistors R15 (5k) and two diodes V3 and V4. Jumpers JMP13, JMP14, and JMP15 are used to connect different parts of the circuit. A menu is open, showing the path: **Analysis** → **DC Analysis** → **Calculate nodal voltages**. Below the circuit, two icons represent simulation files: '01 - Vos and Ib - OPA188.TSC' and '01 - Vos and Ib - OPA211.TSC'. The Texas Instruments logo is visible at the bottom right.

The next step is to run a SPICE simulation analysis for the total DC output voltage. The necessary TINA-TI simulation schematics are embedded in this slide set – simply double-click the icons to open them. Ensure that the jumpers are set correctly. In the OPA211 circuit, JMP13 and JMP14 are open, and JMP15 is closed. In the OPA188 circuit, JMP9 and JMP10 are open, and JMP11 is closed.

To simulate the output voltage, click **Analysis** → **DC Analysis** → **Calculate nodal voltages**.

Simulation Results – $R_{IN} = 0\Omega$

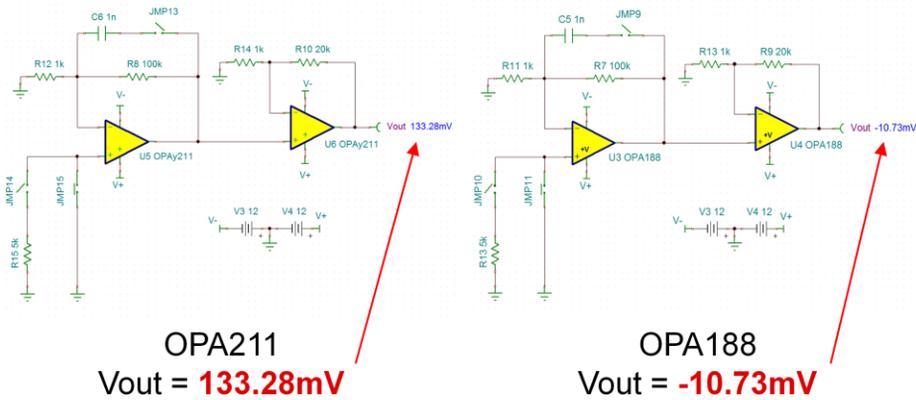


25

 TEXAS INSTRUMENTS

For the OPA211, you should get a result of around 133.28mV. For the OPA188, you should get a result of about -10.73mV.

Disable Function Generator

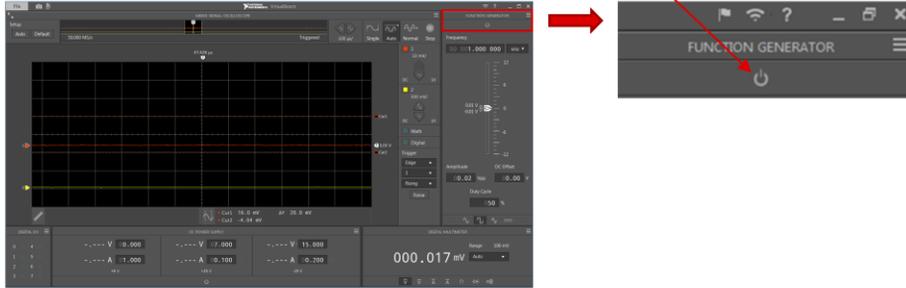Power button GRAY =
Function Generator OFF




26




Also make sure the Function Generator is OFF.

Disable DC Power Supply

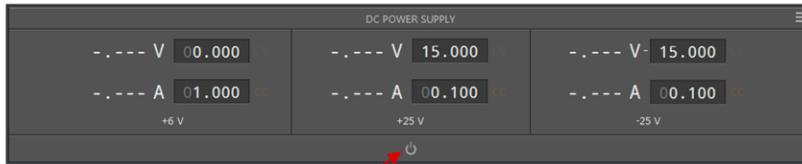

Power button GRAY = DC power supply OFF

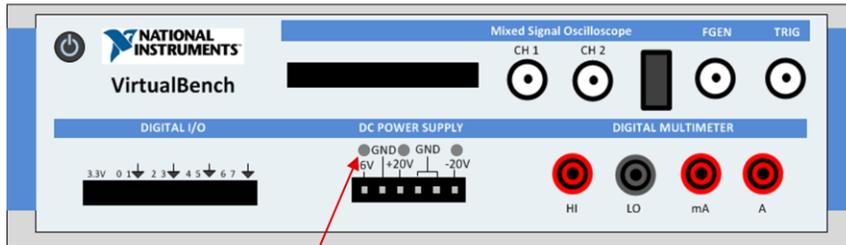


LEDs OFF = DC power supply OFF

27

 TEXAS INSTRUMENTS


Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

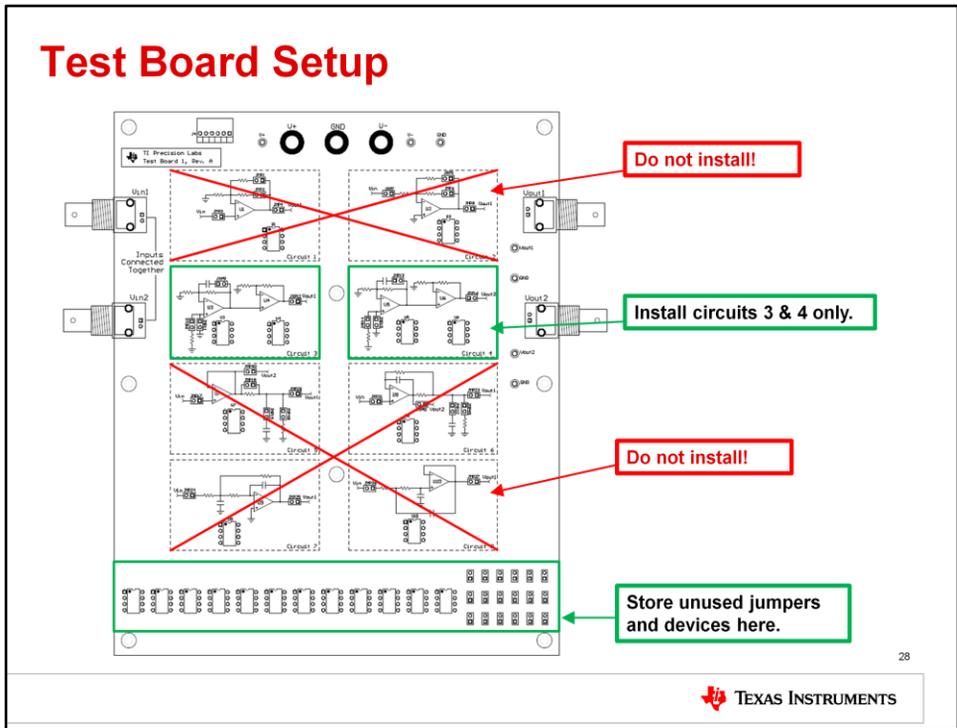

For the test board to function properly, it is important that you only install jumpers and devices in circuits 3 and 4. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup – Jumpers

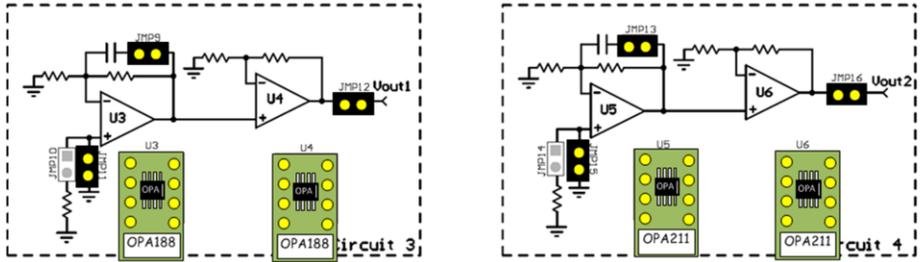

Jumper, Device	Description
JMP9, JMP13	Filter noise with feedback capacitor
JMP11, JMP15	Connect VIN+ to GND
JMP12, JMP16	Connect Circuit 3 to Vout1, connect Circuit 4 to Vout2
U3, U4	Install OPA188
U5, U6	Install OPA211


29

 TEXAS INSTRUMENTS

To prepare the test board for the measurement, install the jumpers and devices on circuit 3 and circuit 4 as shown here.

On circuit 3, install JMP9, JMP11, and JMP12, as well as the OPA188 in sockets U3 and U4. On circuit 4, install JMP13, JMP15, and JMP16, as well as the OPA211 in sockets U5 and U6.

Hardware Setup – Cables

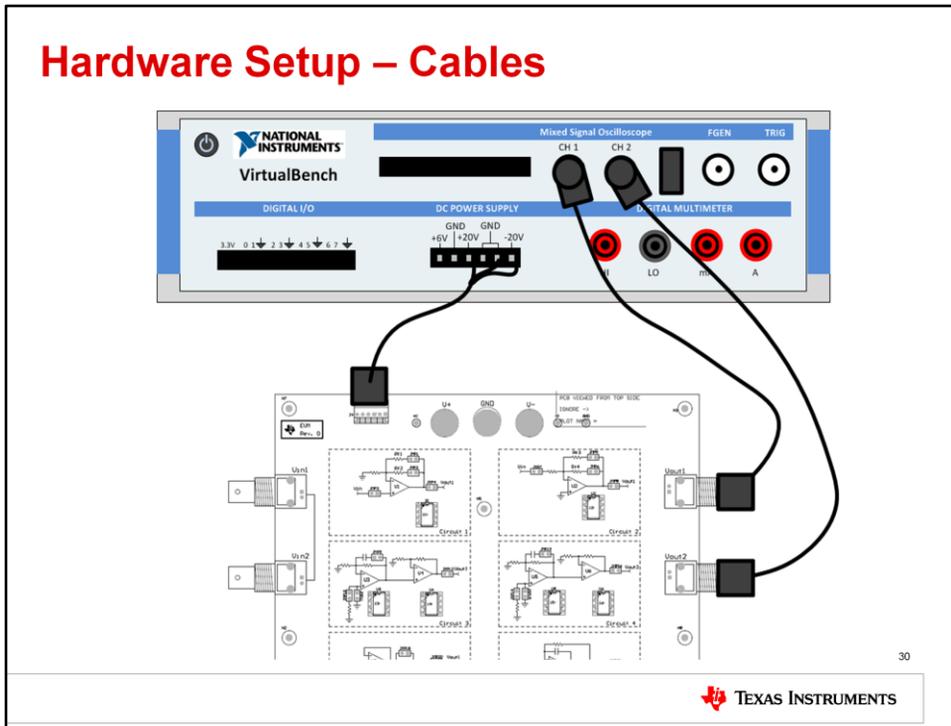

This slide gives the connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board. Connect Vout1 on the test board to VirtualBench oscilloscope channel 1, and Vout2 on the test board to Virtual Bench oscilloscope channel 2, using BNC cables.

VirtualBench™ Instrument Setup



100ms/div, "Auto" acquisition

DC coupled, 1x, adjust range as needed from 10mV/div to 1V/div

Use mean measurement option. This is where you read output voltage.

First:
Power supply enable/disable

±12V, 0.500A power supply

31


 TEXAS INSTRUMENTS

Next apply power to the National Instruments VirtualBench and connect it to your computer with a USB cable. The hardware should be detected as a virtual CD drive, and you can run the VirtualBench software directly from the drive. Once the software opens, configure the software as follows:

Set the time scale to 100ms per division, with the acquisition mode set to "Auto." Enable channels 1 and 2 on the oscilloscope, and set them to 1x, DC-coupled mode. Adjust the vertical scale as needed from 10mV/div to 1V/div. Set the +25V power supply to +12V, 0.500A. Set the -25V power supply to -12V, 0.500A. Press the power button to turn on the power supply rails.

Enable "mean" measurements on both channels in order to read the output voltage of each circuit.

Oscilloscope Settings – Coupling & Probe

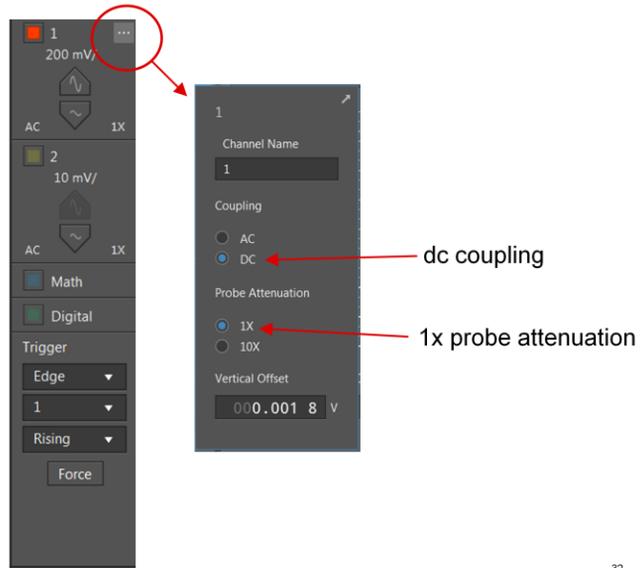


32



The icon at the top right of the oscilloscope opens a new window with more options for each channel. Each channel can be given a custom name. Set the coupling mode to dc. Set probe attenuation to 1x.

Measurement Results – $R_{IN} = 0\Omega$

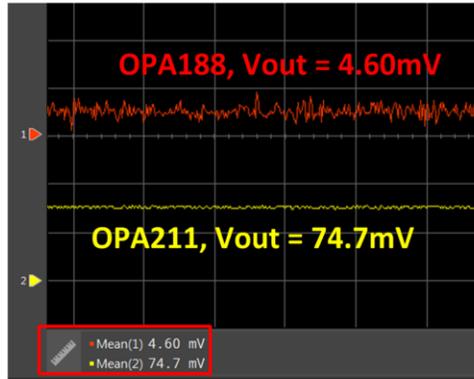

Measured result
should be less than
calculated maximum



Device	Calculated Maximum	Calculated Typical	Simulated Typical	Measured
OPA188	$\pm 56\text{mV}$	$\pm 13\text{mV}$	-10.73mV	4.60mV
OPA211	$\pm 635\text{mV}$	$\pm 191\text{mV}$	$+133.28\text{mV}$	74.7mV

33



The expected output voltage results from the measurement are shown here. The OPA211 has a measured output voltage of 74.7mV , and the OPA188 has a measured output voltage of 4.60mV . You may have different results in your experiment.

How did the measured and simulated results compare to the typical hand calculated results? Take a moment to look over the previous results and draw your own conclusions.

Experiment 2

$R_{IN} = 5k\Omega$


34



For the next part of the lab, we'll repeat the same procedure as experiment 1, but this time with $5k\Omega$ of input resistance. This will emphasize the effects of input bias current, I_B .

Calculation – $R_{IN} = 5k\Omega$

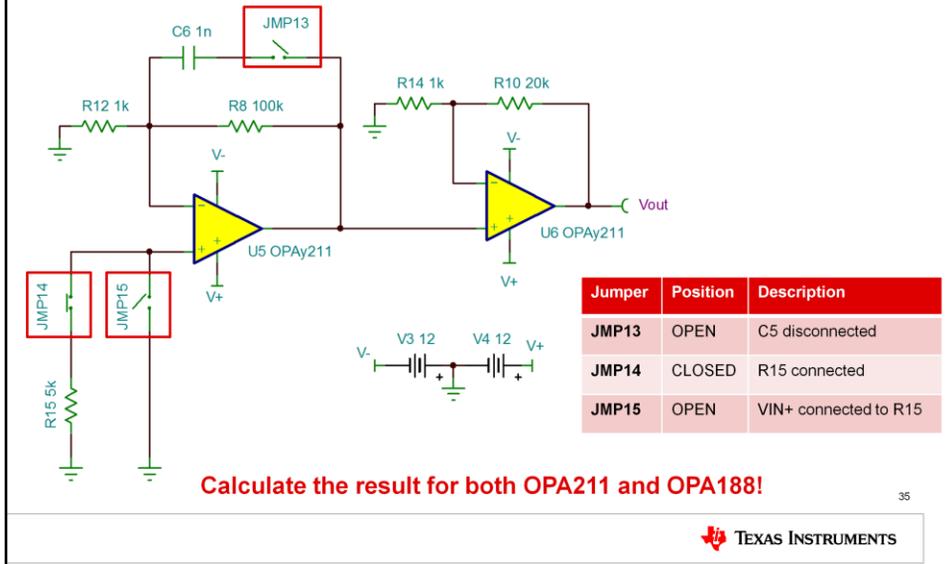Calculate the total output voltage due to V_{OS} and I_B for the circuit shown below. Use the typical and maximum values for V_{OS} and I_B given on the next slide.



As shown in the schematic, jumper JMP15 shorting the positive input of U5 to ground is now removed. Jumper JMP14 is now installed in order to connect the positive input of U5 to a 5kΩ resistor. The I_B of U5 will now flow through this resistor, developing a DC voltage due to Ohm's law and increasing the amount of offset voltage.

As before, calculate the total output voltage due to V_{OS} and I_B for this circuit, using both the OPA211 and OPA188.

Calculation – $R_{IN} = 5k\Omega$

PARAMETER		OPA211			UNIT
		MIN	TYP	MAX	
Input Offset Voltage	V_{OS}		± 30	± 125	μV
Input Bias Current	I_B		± 60	± 175	nA

PARAMETER		OPA188			UNIT
		MIN	TYP	MAX	
Input Offset Voltage	V_{OS}		± 6	± 25	μV
Input Bias Current	I_B		± 160	± 1400	pA

Device	Typical Output	Maximum Output
OPA188	$\pm 15mV$	$\pm 71mV$
OPA211	$\pm 191mV$	$\pm 2492mV$

36



The data sheet parameters for both devices are provided again for reference. Enter your calculated results in the lower table. The answers have been provided so that you can check your work.

Calculation – $R_{IN} = 5k\Omega$

OPA211

Calculate typical output error from Vos & Ib

$$i_b = \pm 60nA$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1k\Omega$$

$$R_{in} = 5k\Omega$$

$$V_{ib} = i_b R_{eq} + i_b R_{in} = \pm 360\mu V$$

$$V_{os} = \pm 30\mu V$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21 (\pm 30\mu V + \pm 360\mu V)$$

$$V_{out_error} = \pm 827mV \text{ or } \pm 700mV$$

$$V_{out_error} = \pm 827mV \text{ Choose the largest}$$

Calculate maximum output error from Vos & Ib

$$i_b = \pm 175nA$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1k\Omega$$

$$R_{in} = 5k\Omega$$

$$V_{ib} = i_b R_{eq} + i_b R_{in} = \pm 1050\mu V$$


$$V_{os} = \pm 125\mu V$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21 (\pm 125\mu V + \pm 1050\mu V)$$

$$V_{out_error} = \pm 2492mV \text{ or } \pm 1962mV$$
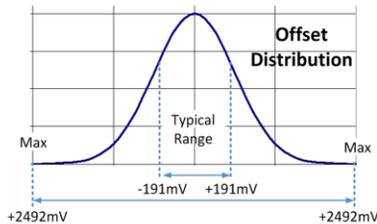
$$V_{out_error} = \pm 2492mV \text{ Choose the largest}$$



37



With $R_{IN} = 5k$, the calculations change slightly since the voltage caused by I_B is now affected by R_{IN} . Use the new equation $V_{IB} = I_B * R_{EQ} + I_B * R_{IN}$. Otherwise, the steps are the same as in experiment 1. Repeat the calculations for the maximum values.

Calculation – $R_{IN} = 5k\Omega$

OPA188

Calculate typical output error from Vos & Ib

$$i_b = \pm 160 \text{pA}$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1 \text{k}\Omega$$

$$R_{in} = 5 \text{k}\Omega$$

$$V_{ib} = i_b R_{eq} + i_b R_{in} = \pm 0.96 \mu\text{V}$$

$$V_{os} = \pm 6 \mu\text{V}$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21 (\pm 6 \mu\text{V} + \pm 0.96 \mu\text{V})$$

$$V_{out_error} = \pm 15 \text{mV or } \pm 11 \text{mV}$$

$$V_{out_error} = \pm 15 \text{mV Choose the largest}$$

Calculate maximum output error from Vos & Ib

$$i_b = \pm 1400 \text{pA}$$

$$R_{eq} = \frac{R_f R_1}{R_f + R_1} \approx 1 \text{k}\Omega$$

$$R_{in} = 5 \text{k}\Omega$$

$$V_{ib} = i_b R_{eq} + i_b R_{in} = \pm 8.4 \mu\text{V}$$


$$V_{os} = \pm 25 \mu\text{V}$$

$$V_{out_error} = G_1 G_2 (V_{os} + V_{ib})$$

$$V_{out_error} = 101 * 21 (\pm 25 \mu\text{V} + \pm 8.4 \mu\text{V})$$

$$V_{out_error} = \pm 71 \text{mV or } \pm 35 \text{mV}$$
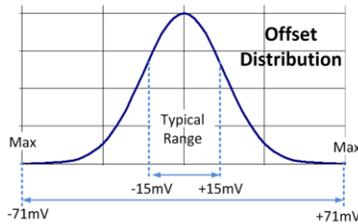
$$V_{out_error} = \pm 71 \text{mV Choose the largest}$$




38

Repeat both sets of calculations for the OPA188, again using typical and maximum values. As before, the different electrical characteristics of the OPA188 will result in different output voltage calculations.

Simulation Results – $R_{IN} = 5k\Omega$

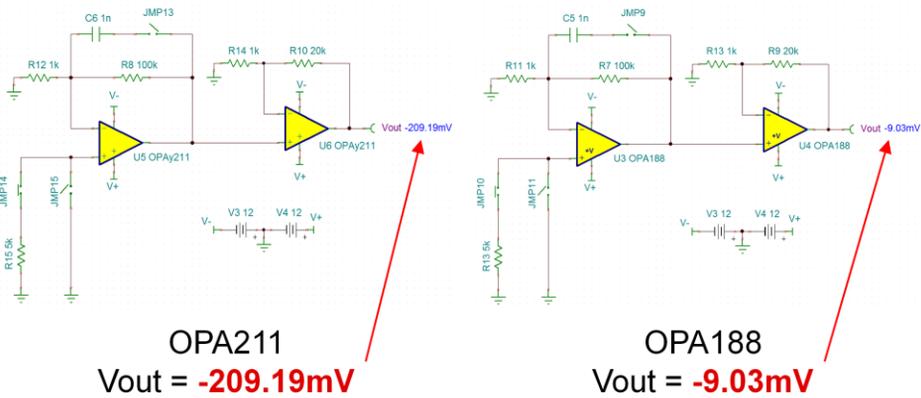Open switches **JMP15** and **JMP11**, and close switches **JMP14** and **JMP10**. Re-run the simulation to determine the new output voltage due to V_{OS} and I_B .



39


 TEXAS INSTRUMENTS

Re-run the simulated DC nodal voltage analysis, making sure to use the proper jumper settings.

In the OPA211 circuit, JMP13 and JMP15 are open, and JMP14 is closed.
In the OPA188 circuit, JMP9 and JMP11 are open, and JMP10 is closed.

Test Board Setup – Jumpers

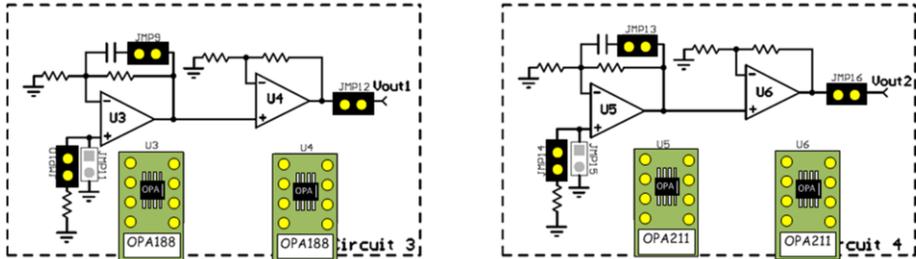Remove jumpers **JMP11** and **JMP15**, and install jumpers **JMP10** and **JMP14**.



The only change →


Jumper, Device	Description
JMP9, JMP13	Filter noise with feedback capacitor
JMP10, JMP14	Connect VIN+ to 5kΩ
JMP12, JMP13	Connect Circuit 3 to Vout1, connect Circuit 4 to Vout2
U3, U4	Install OPA188
U5, U6	Install OPA211

40

 TEXAS INSTRUMENTS

The jumper settings on the test board must be modified before re-running the bench measurement. Remove jumpers **JMP11** and **JMP15**, and install jumpers **JMP10** and **JMP14**. All other jumpers and devices remain the same from the previous experiment.

VirtualBench™ Instrument Setup

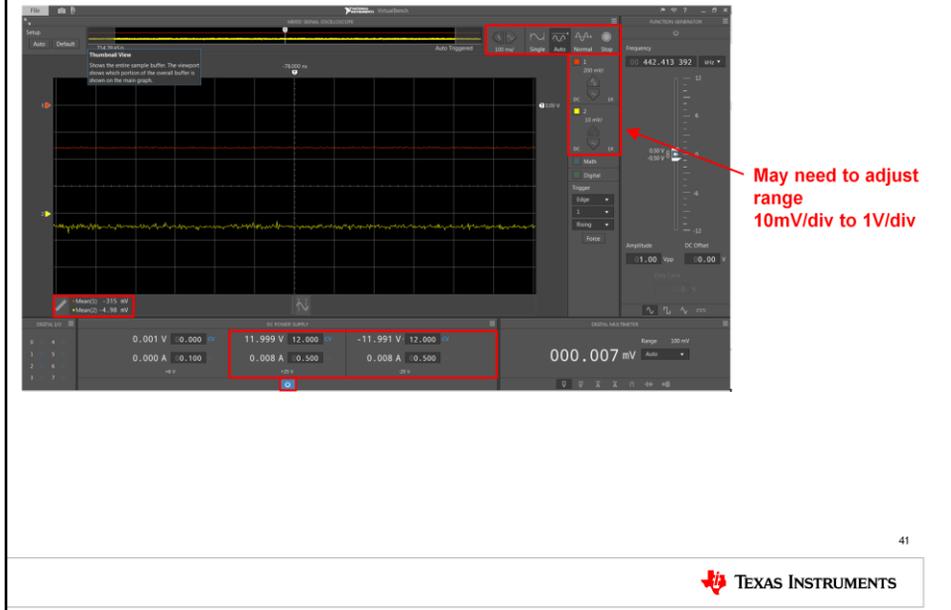


Next apply power to the National Instruments VirtualBench and connect it to your computer with a USB cable. The hardware should be detected as a virtual CD drive, and you can run the VirtualBench software directly from the drive. Once the software opens, configure the software as follows:

Set the time scale to 100ms per division, with the acquisition mode set to “Auto.” Enable channels 1 and 2 on the oscilloscope, and set them to 1x, DC-coupled mode. Adjust the vertical scale as needed from 10mV/div to 1V/div. Set the +25V power supply to +12V, 0.500A. Set the -25V power supply to -12V, 0.500A. Press the power button to turn on the power supply rails.

Enable “mean” measurements on both channels in order to read the output voltage of each circuit.

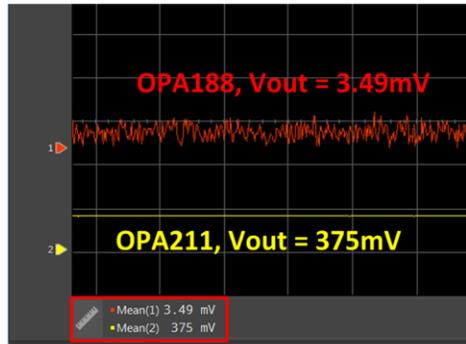Measurement Results – $R_{IN} = 5k\Omega$



Measured result
should be less than
calculated maximum



Device	Calculated Maximum	Calculated Typical	Simulated Typical	Measured
OPA188	$\pm 71\text{mV}$	$\pm 15\text{mV}$	-9.03mV	3.49mV
OPA211	$\pm 2492\text{mV}$	$\pm 827\text{mV}$	-209.19mV	375mV

42



In experiment 2, the OPA188 has a measured output voltage of 3.49mV, and the OPA211 has a measured output voltage of 375mV. You may have different results in your experiment.

How did the measured and simulated results compare to the hand calculated results? In this example, the OPA211 output was greater than the calculated and simulated typical values, but less than the calculated maximum value. The OPA188 output was less than the calculated and simulated typical values.

Final Results

How did the change in input resistance affect the output voltage measurement?

Device Rin = 0Ω	Calculated Maximum	Calculated Typical	Simulated Typical	Measured
OPA188	±56mV	±13mV	-10.73mV	4.60mV
OPA211	±635mV	±191mV	133.28mV	74.7mV

Device Rin = 5kΩ	Calculated Maximum	Calculated Typical	Simulated Typical	Measured With Rin
OPA188	±71mV	±15mV	-9.03mV	3.94mV
OPA211	±2492mV	±827mV	-209.19mV	375mV

Answer: Dramatic increase for the OPA211, small change for OPA188.
This is due to the OPA211 having much larger I_B than the OPA188.

43



Let's now compare the results of both experiments. How did the change in input resistance affect the output voltage measurement?

In the OPA211, increasing the input resistance caused a dramatic increase in output voltage. However, the OPA188 did not see such a large increase. This is because the OPA211 has a much larger input bias current (I_B), than the OPA188.

Input/Output Limitations – Lab

TI Precision Labs – Op Amps

Developed by Art Kay and Ian Williams

TIDesigns
PRECISION

44

 TEXAS INSTRUMENTS

Hello, and welcome to the presentation for the TI Precision Lab supplement for op amp input and output limitations. This lab will walk through detailed calculations, SPICE simulations, and real-world measurements that greatly help to reinforce the concepts established in the op amp input and output limitations lecture.

Required/Recommended Equipment

- Calculation
 - Pencil and paper
 - **Recommended:** MathCAD, Excel, or similar
- Simulation
 - SPICE simulation software
 - **Recommended:** TINA-TI™
- Measurement
 - TI Precision Labs PCB from Texas Instruments
 - Oscilloscope
 - Function generator
 - $\pm 5V$ power supply
 - **Recommended:** National Instruments VirtualBench™

The detailed calculation portion of this lab can be done by hand, but calculation tools such as MathCAD or Excel can help greatly.

The simulation exercises can be performed in any SPICE simulator, since Texas Instruments provides generic SPICE models of the op amps used in this lab. However, the simulations are most conveniently done in TINA-TI, which is a free SPICE simulator available from the Texas Instruments website. TINA simulation schematics are embedded in the presentation.

Finally, the real-world measurements are made using a printed circuit board, or PCB, provided by Texas Instruments. If you have access to standard lab equipment, you can make the necessary measurements with any oscilloscope, function generator, and $\pm 5V$ power supply. However, we highly recommend the VirtualBench from National Instruments. The VirtualBench is an all-in-one test equipment solution which connects to a computer over USB or Wi-Fi and provides power supply rails, analog signal generator and oscilloscope channels, and a 5 ½ digit multimeter for convenient and accurate measurements. This lab is optimized for use with the VirtualBench.

Experiment 1

Voltage Follower


46



In experiment 1, we'll determine the effects of input and output limitations in a basic voltage follower, or unity-gain buffer, circuit.

Calculation – Voltage Follower

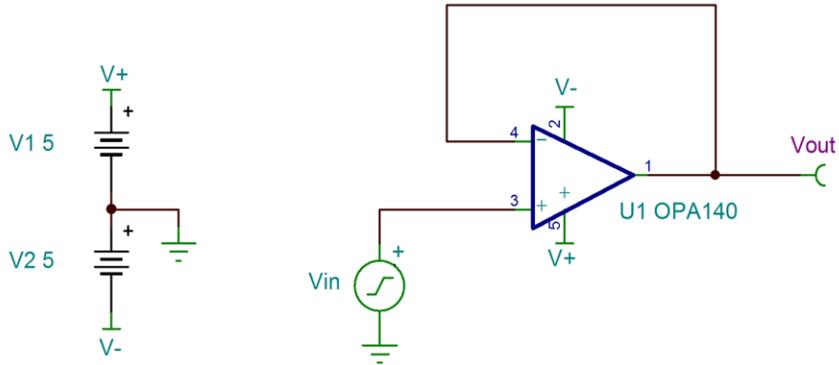Calculate the input common mode voltage range and output voltage swing for the circuit shown below. Use the data sheet parameters given on the next slide.



47


 TEXAS INSTRUMENTS

First, calculate the input common mode voltage range and output voltage swing for the circuit shown here, using the techniques and equations given in the input/output limitations lecture. Use the data sheet parameters given on the next slide.

Calculation – Voltage Follower

PARAMETER		OPA140			UNIT
		MIN	TYP	MAX	
Input Voltage Range	V_{CM}	$(V-) - 0.1$		$(V+) - 3.5$	V
Voltage Output Swing from Rail	V_O	$(V-) + 0.2$		$(V+) - 0.2$	V

Calculated Answers	Min	Max
Common Mode Input Range	-5.1	+1.5V
Output Swing Range	-4.8	4.8V

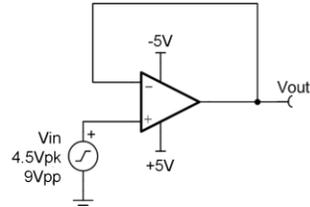

With a 9Vpp (4.5Vpk) input signal, is the circuit limitation caused by input common mode range or output voltage swing?

Answer: The maximum input common mode voltage of +1.5V is the limit, since the peak input signal is +4.5V.

48

 TEXAS INSTRUMENTS


This circuit uses the OPA140. In order to perform the calculations, you need to know the input voltage range and voltage output swing values for that device. Those values are given here.

Enter your answers in the table in the middle of the slide. The solutions are already provided to allow you to check your work.

Also answer the question at the bottom of the slide. Again, the solution is already provided.

Simulation Setup – Voltage Follower

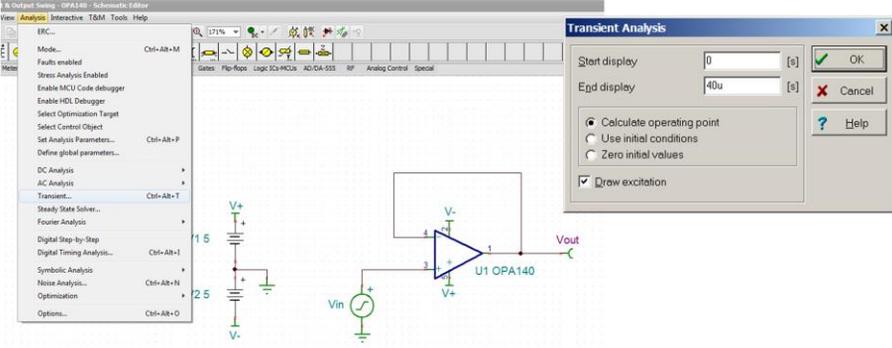Click **Analysis** → **Transient** to show the common mode limitations for the OPA140. Run the analysis from 0μs to 40μs. The input is a 4.5Vpk, 50kHz triangle wave.



02 - Input and Output Swing - OPA140.TSC


49

 TEXAS INSTRUMENTS

The next step is to run a SPICE simulation analysis for the transient output voltage behavior. This will allow us to see the op amp's output voltage response for a specified input signal, which in this case is a 2Vp, 1kHz triangle wave.

The necessary TINA-TI simulation schematic is embedded in this slide set – simply double-click the icon to open it. To simulate the transient output behavior, click **Analysis** → **Transient**. Run the analysis from 0ms to 2ms.


Simulation Results – Voltage Follower

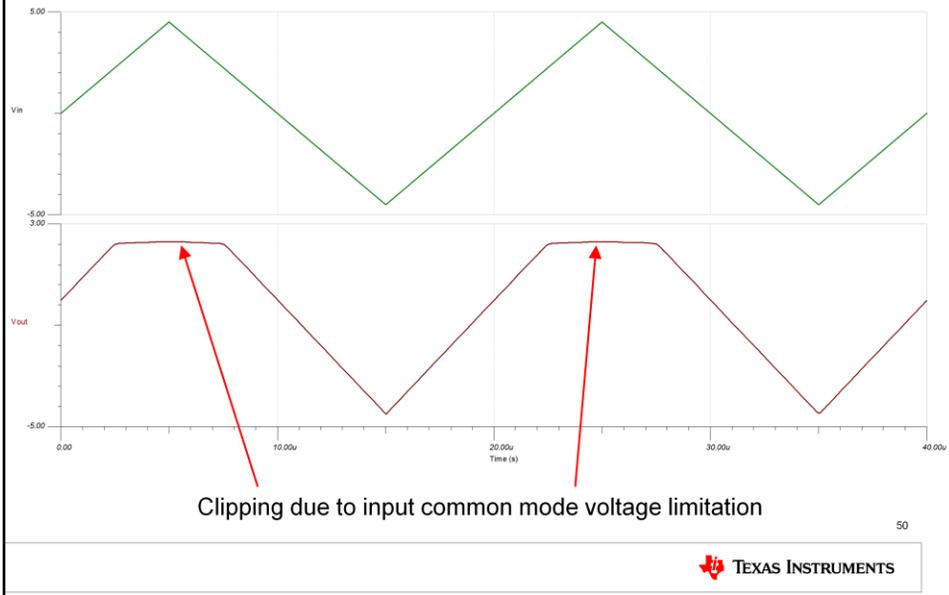

You should see a result similar to this. V_{in} is a triangle wave, as expected, but V_{out} cannot exceed +1V. This is due to the input common mode voltage limitation of the OPA735.

Disable Function Generator

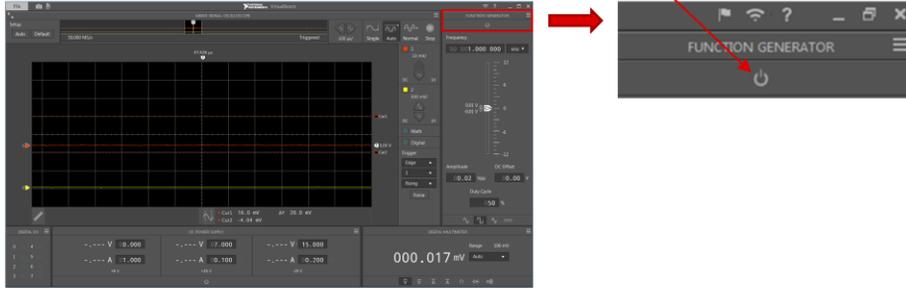Power button GRAY =
Function Generator OFF




51




Also make sure the Function Generator is OFF.

Disable DC Power Supply

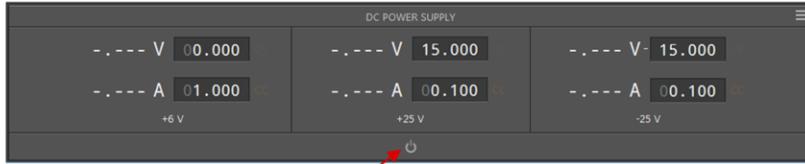

Power button GRAY = DC power supply OFF

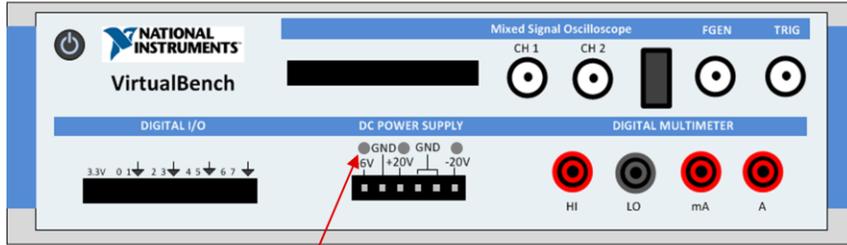


LEDs OFF = DC power supply OFF

52




Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

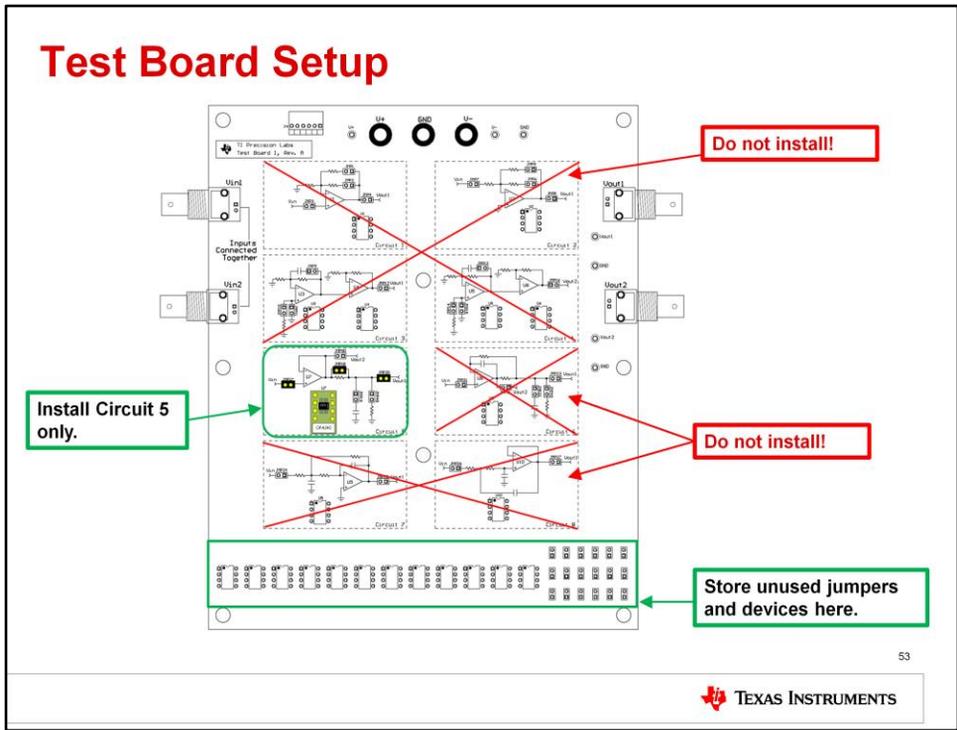

For the test board to function properly, it is important that you only install jumpers and devices in circuit 5. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup – Jumpers

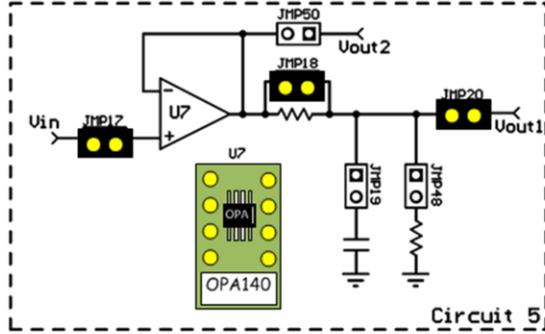


Jumper, Device	Description
JMP17	Connect input to signal source.
JMP18	Short output resistance
JMP20	Connect Circuit 5 output to Vout1
U7	Install OPA140

54

To prepare the test board for the measurement, install the jumpers and devices on circuit 5 as shown here.

Install JMP17, JMP18, and JMP20, as well as the OPA735 in socket U7.

Hardware Setup – Cables

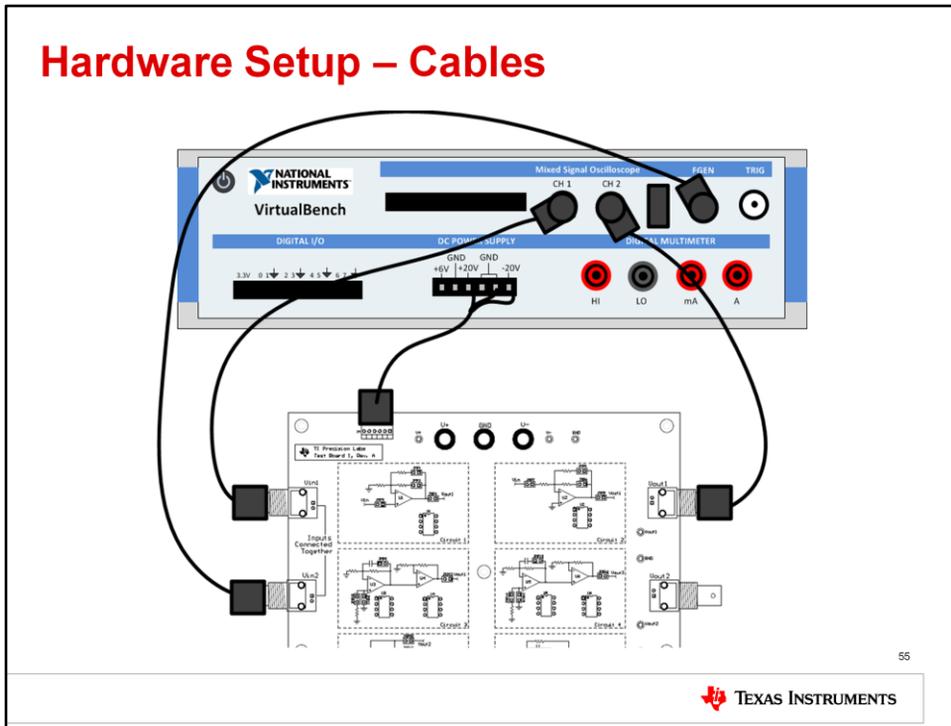

This slide gives the connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board. Connect Vin2 on the test board to VirtualBench channel FGEN, or function generator. Then connect Vin1 on the test board to VirtualBench oscilloscope channel 1, and Vout1 on the test board to VirtualBench oscilloscope channel 2.

VirtualBench™ Instrument Setup

5 μ s/div, "Auto" acquisition

50kHz signal frequency

DC coupled, 1x, 2V/div

9Vpp, 0V offset, 50% symmetry triangle wave

First: Power supply enable/disable

± 5 V, 0.100A power supply

Set cursors to +1.5V and -5.1V to show valid common mode range.

56

TEXAS INSTRUMENTS

Next apply power to the National Instruments VirtualBench and connect it to your computer with a USB cable. The hardware should be detected as a virtual CD drive, and you can run the VirtualBench software directly from the drive. Once the software opens, configure the software as follows:

Set the time scale to 5 μ s per division, with the acquisition mode set to "Auto." Enable channels 1 and 2 on the oscilloscope, and set them to 1x, DC-coupled mode, 2V/div. Enable the function generator and setup the signal as follows:



50kHz frequency, 9Vpp, 0V offset, 50% symmetry triangle wave.

Enable the cursors and set them to +1.5V and -5V to show the valid input common mode range.

Set the +25V power supply to +5V, 0.500A. Set the -25V power supply to -5V, 0.500A. Press the power button to turn on the power supply rails.

Measurement Results – Voltage Follower

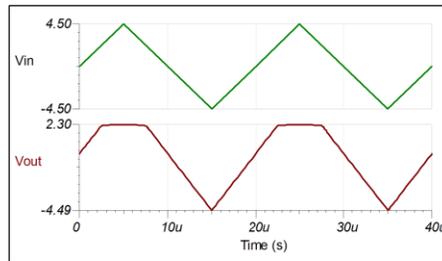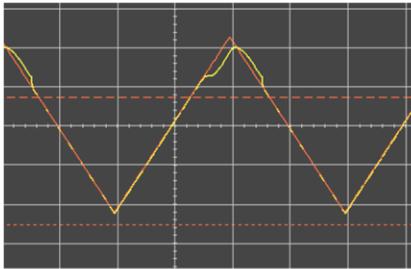1. Compare TINA-TI™ simulation results to measured results.



2. Use the cursors on the VirtualBench and TINA-TI™ tool to measure the voltage where Vout becomes limited (clipped). Compare this to your calculation.

Answer (calculation):	clipped at +1.5V
Answer (simulation):	clipped at +2.3V
Answer (measurement):	visible distortion above +2.5V

57




The expected measurement results are shown here. Compare the oscilloscope display of the VirtualBench to the simulation results from TINA-TI. Also, use the cursors on the VirtualBench and TINA-TI tool to measure the voltage where Vout becomes limited, or clipped. Compare this to your calculation.

The results have already been entered into the table to allow you to check your results. You may have different results in your experiment.

Extra Experiment: 1kHz vs. 50kHz Input

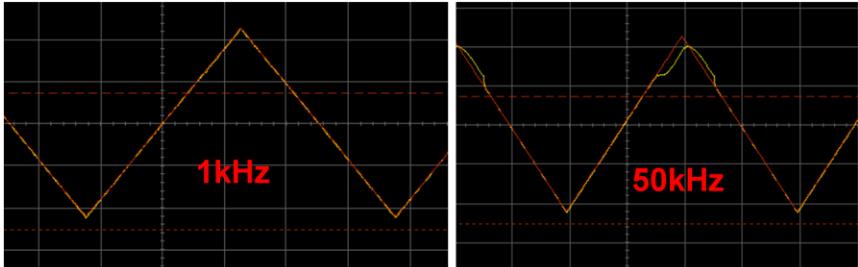3. Change the triangle waveform frequency to 1kHz and compare the common mode range to the 50kHz wave. Change the time scale to 200 μ s/div.



4. What conclusion do you draw from the measurement?

The 1kHz waveform does not show the common mode limitation, but the 50kHz waveform does. This device is actually "rail-to-rail" for low frequencies, but common mode performance $\sim 2V$ from the positive rail degrades at higher frequencies.

58

Experiment 2

Inverting Amplifier


59



In experiment 2, we'll determine the effects of input and output limitations in an inverting amplifier circuit with gain.

Calculation – Inverting Amplifier

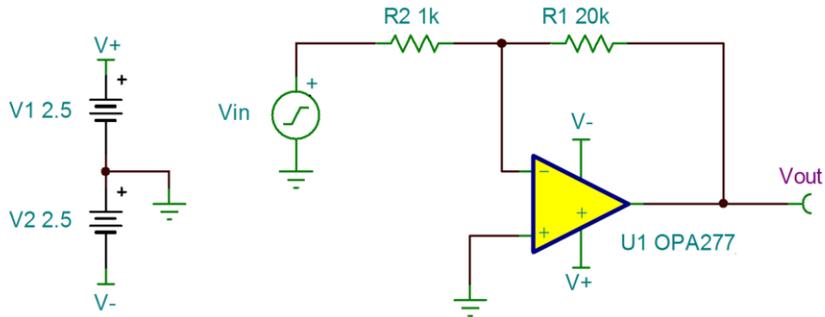Calculate the input common mode voltage range and output voltage swing for the circuit shown below. Use the data sheet parameters given on the next slide.



60


 TEXAS INSTRUMENTS

First, calculate the input common mode voltage range and output voltage swing for this inverting amplifier circuit, using the techniques and equations given in the input/output limitations lecture. Use the data sheet parameters given on the next slide.

Calculation – Inverting Amplifier

PARAMETER (data sheet)		CONDITION	OPA277			UNIT
			MIN	TYP	MAX	
Input Voltage Range	V_{CM}		(V-) +2		(V+) -2	V
Voltage Output	V_o	$R_L = 10k\Omega$	(V-) +0.5		(V-) -1.2	V
Voltage Output		$R_L = 2k\Omega$	(V-) +1.5		(V-) -1.5	

Answers	Min	Max
Common Mode Input Range	-0.5V	0.5V
Output Swing Range	-2.0V	1.3V

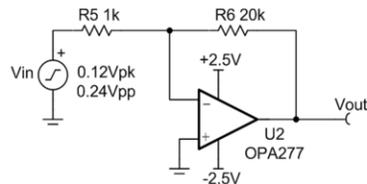

With a 0.24Vpp (0.12Vpk) input signal, is the circuit limitation caused by input common mode range or output voltage swing?

Answer: The output wants to be $\pm 2.4V_{pk}$. This violates both the negative and positive output swing limit. There's no issue with the input common mode range.

61




This circuit uses the OPA277. In order to perform the calculations, you need to know the input voltage range and voltage output swing values for that device. Those values are given here.

Enter your answers in the table in the middle of the slide. The solutions are already provided to allow you to check your work.

Also answer the question at the bottom of the slide. Again, the solution is already provided.

Simulation Setup – Inverting Amplifier

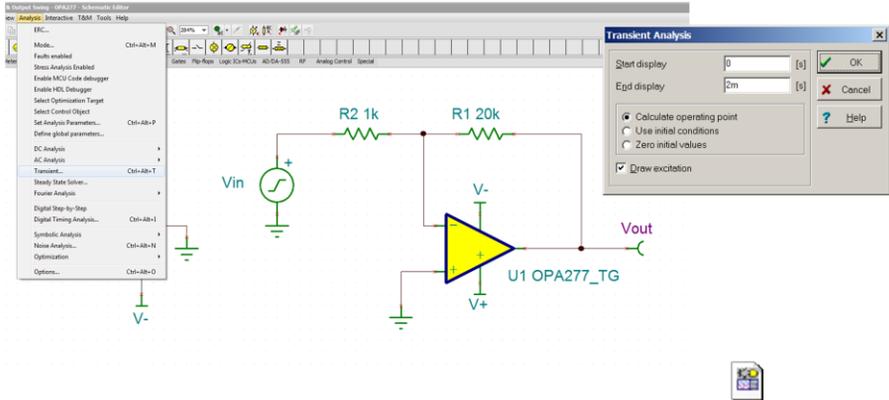Click **Analysis** → **Transient** to show the common mode limitations for the OPA277. Run the analysis from 0ms to 2ms. The input is a 120mVpk, 1kHz triangle wave.



02 - Input and Output Swing - OPA277.TSC


62

 TEXAS INSTRUMENTS

Run a SPICE simulation as before, but now using this inverting amplifier circuit with the OPA277.

The necessary TINA-TI simulation schematics are embedded in this slide set – simply double-click the icon to open them. Click **Analysis** → **Transient** and run the transient from 0ms to 2ms. The input signal to this circuit is a 120mVp, 1kHz triangle wave.


Simulation Results – Inverting Amplifier

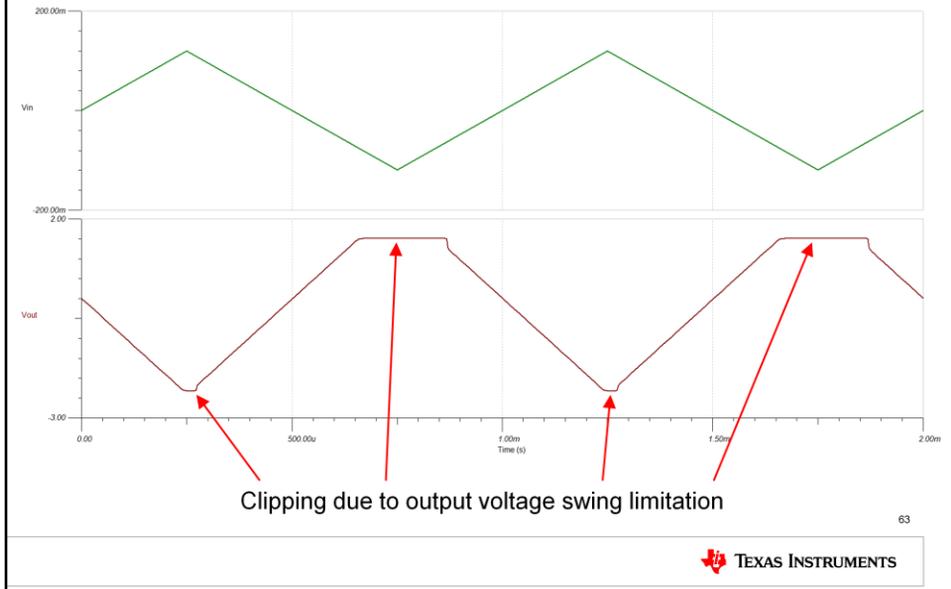

You should see a result similar to this. V_{in} is a triangle wave, as expected, but V_{out} clips at both the positive and negative ends of the triangle wave due to output voltage swing limitations.

Disable Function Generator

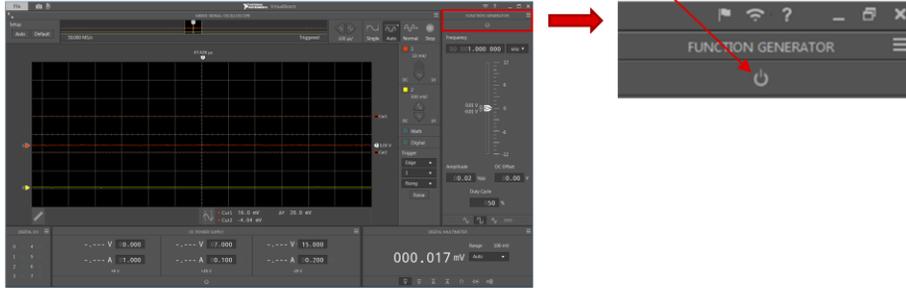
Power button GRAY =
Function Generator OFF




64

Also make sure the Function Generator is OFF.

Disable DC Power Supply

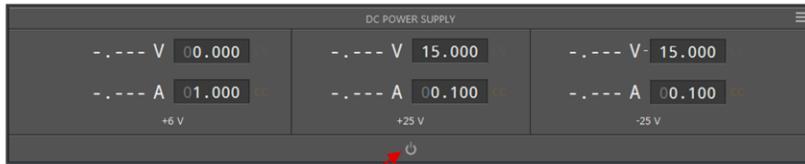

Power button GRAY = DC power supply OFF

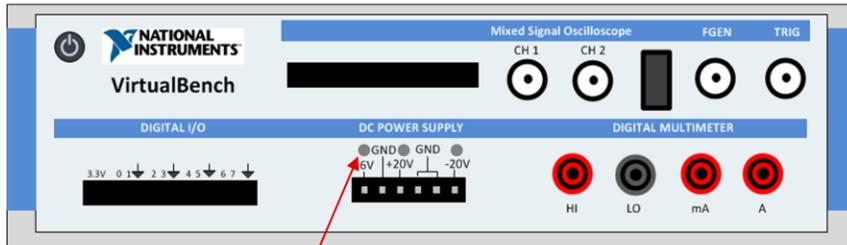


LEDs OFF = DC power supply OFF




Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

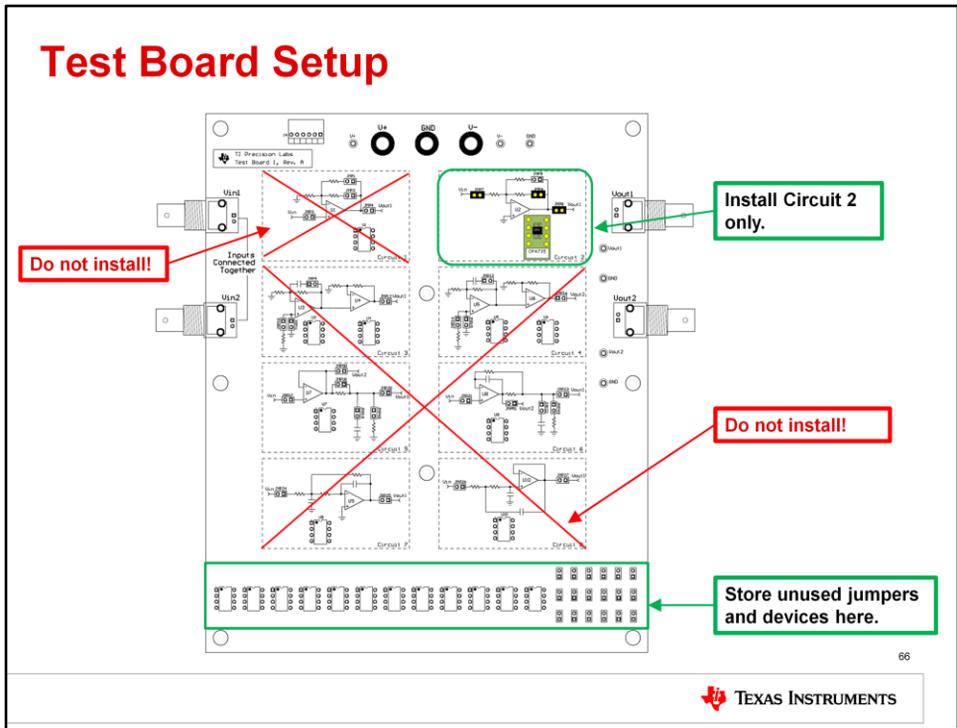

For this measurement, only circuit 2 is used. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup – Jumpers

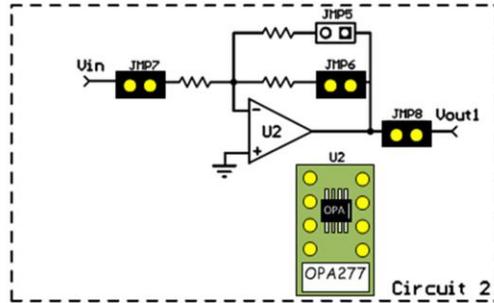

Jumper, Device	Description
JMP6	Connect $R_f = 20k\Omega$ for a gain of 20V/V
JMP7	Connect input to signal source
JMP8	Connect Circuit 2 output to V_{out1}
U2	Install OPA277


67



To prepare the test board for the measurement, install the jumpers and devices on circuit 2 as shown here.

Install JMP6, JMP7, and JMP8, as well as the OPA277 in socket U2.

Hardware Setup – Cables

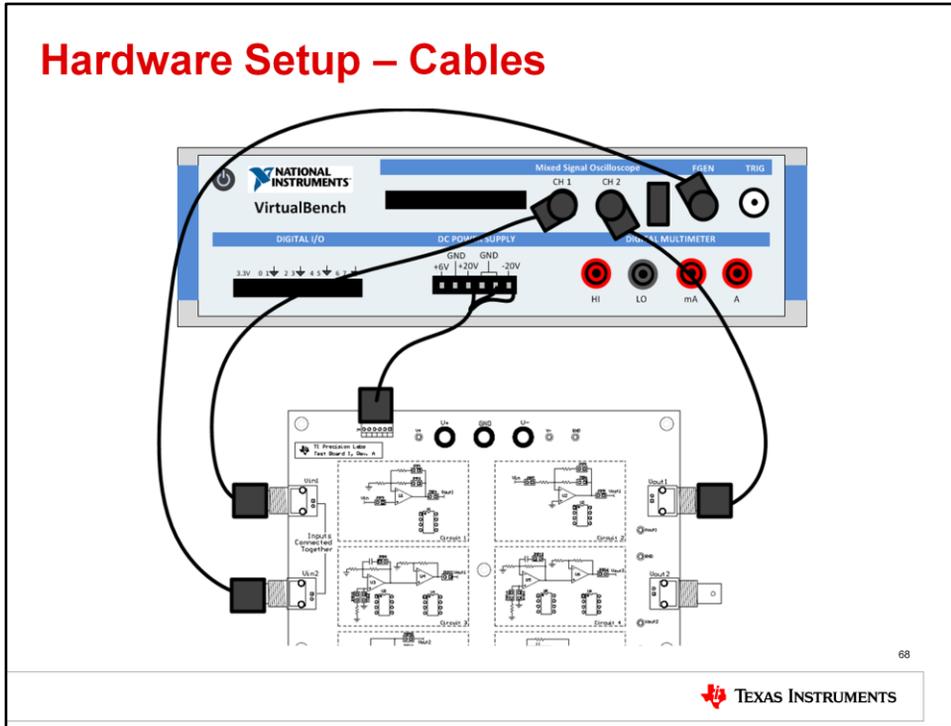

The cable connections to the VirtualBench are exactly the same as in experiment 1. No changes are necessary.

VirtualBench™ Instrument Setup

The screenshot displays the VirtualBench software interface. The main window shows a waveform plot with two channels: a red triangle wave (CH1) and a green square wave (CH2). The plot is set to a 200µs/div time scale and 'Auto' acquisition. The right-hand control panel shows the function generator settings: Frequency is 1 kHz, DC Coupled, 1x vertical scale, and 50% symmetry. The bottom control panel shows the DC Power Supply settings: 2.500 V, 0.500 A, and -2.500 V, 0.500 A. A red box highlights the 'First' button and the power supply settings. Red arrows point from text labels to these specific settings.

200µs/div, "Auto" acquisition

1kHz signal frequency

DC coupled, 1x, CH1=100mV/div, CH2=1V/div

0.22Vpp, 0V offset, 50% symmetry triangle wave

First:
Power supply enable/disable

±2.5V, 0.500A power supply

69

TEXAS INSTRUMENTS


The VirtualBench instrument setup is very similar to experiment 1. Make the following changes:

Set the vertical scale of CH1 to 100mV/div. Keep the vertical scale of CH2 at 1V/div.

Set the function generator to a 0.22Vpp, 0V offset, 50% symmetry triangle wave at 1kHz.

Measurement Results – Inverting Amplifier

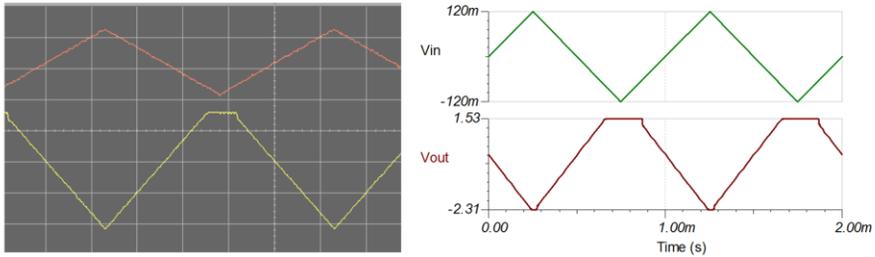1. Compare TINA-TI™ simulation results to measured results.




2. Use the cursors on the VirtualBench and TINA-TI™ tool to measure the voltage where Vout becomes limited (clipped). Compare this to your calculation.

Answer (calculation):	clipped at -2.0V and +1.3V
Answer (simulation):	clipped at -2.31V and +1.53V (it may distort before the clip)
Answer (measurement):	clipped at -2.40V and +1.59V (it may distort before the clip)

70



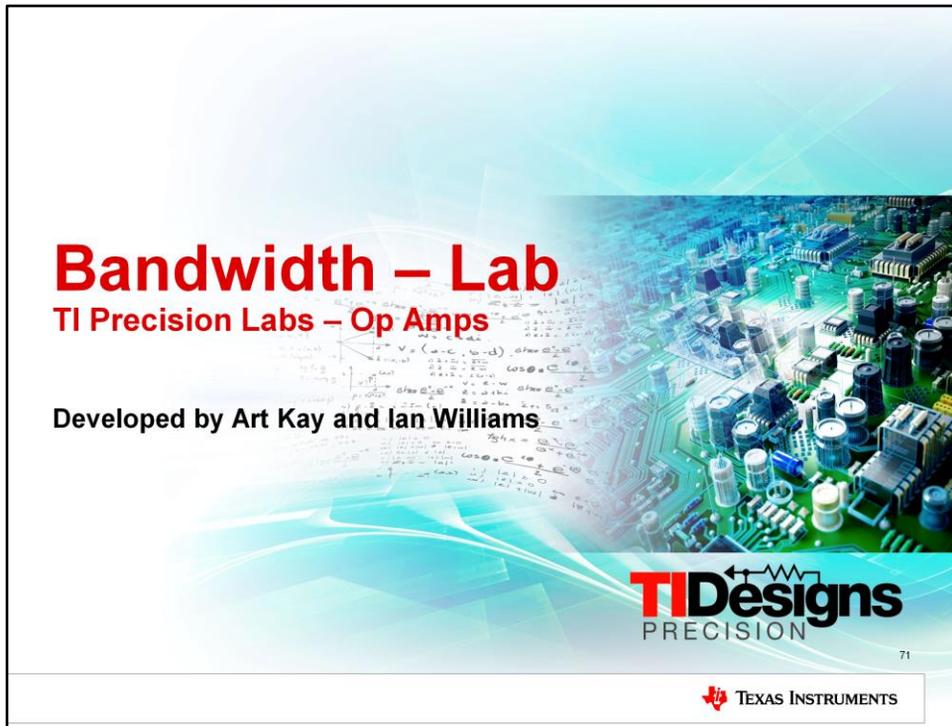Compare the TINA simulation results to your measured results. The shape of the output waveform should look very similar, with hard clipping at the top of the waveform. Your device may or may not clip at the bottom of the waveform.



Bandwidth – Lab

TI Precision Labs – Op Amps

Developed by Art Kay and Ian Williams

TIDesigns
PRECISION

71

 TEXAS INSTRUMENTS

Hello, and welcome to the presentation for the TI Precision Lab supplement for op amp bandwidth. This lab will walk through detailed calculations, SPICE simulations, and real-world measurements that greatly help to reinforce the concepts established in the op amp input and output limitations presentation.

Required/Recommended Equipment

- Calculation
 - Pencil and paper
 - **Recommended:** MathCAD, Excel, or similar
- Simulation
 - SPICE simulation software
 - **Recommended:** TINA-TI™
- Measurement
 - TI Precision Labs PCB from Texas Instruments
 - Bode plotter
 - $\pm 15V$ power supply
 - **Recommended:** National Instruments VirtualBench™


The detailed calculation portion of this lab can be done by hand, but calculation tools such as MathCAD or Excel can help greatly.

The simulation exercises can be performed in any SPICE simulator, since Texas Instruments provides generic SPICE models of the op amps used in this lab. However, the simulations are most conveniently done in TINA-TI, which is a free SPICE simulator available from the Texas Instruments website. TINA simulation schematics are embedded in the presentation.

Finally, the real-world measurements are made using a printed circuit board, or PCB, provided by Texas Instruments. If you have access to standard lab equipment, you can make the necessary measurements with any Bode plotter and $\pm 15V$ power supply. However, we highly recommend the VirtualBench from National Instruments. The VirtualBench is an all-in-one test equipment solution which connects to a computer over USB or Wi-Fi and provides power supply rails, analog signal generator and oscilloscope channels, and a 5 ½ digit multimeter for convenient and accurate measurements. This lab is optimized for use with the VirtualBench.

Calculation – Bandwidth

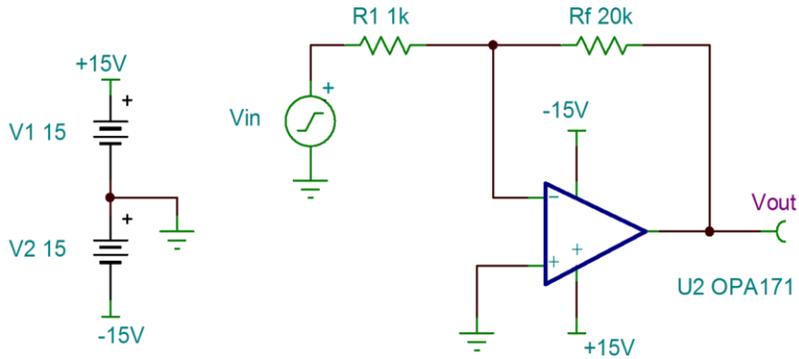Calculate the closed loop bandwidth and DC signal gain for the circuit shown below. Use the data sheet parameters given on the next slide.



73

 TEXAS INSTRUMENTS


First, calculate the closed loop bandwidth and DC signal gain for the circuit shown here, using the techniques and equations given in the bandwidth lecture. Use the data sheet parameters given on the next slide.

Calculation – Bandwidth

1. Use excerpt from data sheet below to fill in the table and AC transfer function:

PARAMETER		OPA171			UNIT
		MIN	TYP	MAX	
Gain bandwidth product	GBP		3.0		MHz
Slew rate	SR		1.5		V/ μ s

Closed Loop Bandwidth:	$GBP/G_n = 3\text{MHz}/21 = 143\text{kHz}$.
Signal Gain at DC	$G_{CL} = -(R_f/R_1) = -(20\text{k}/1\text{k}) = -20\text{V/V}$

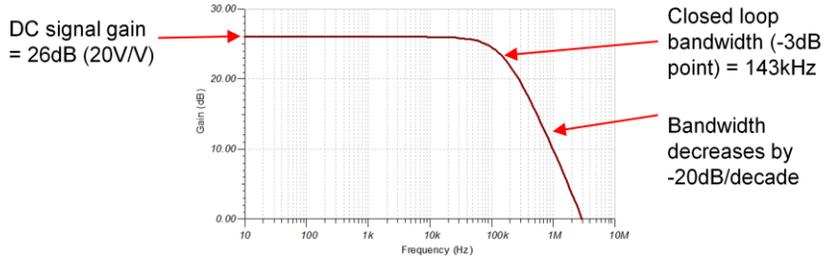

74




This circuit uses the OPA171. In order to perform the calculations, you need to know the gain bandwidth product and for that device. That value is given here.

Enter your answers in the table in the middle of the slide. The solutions are already provided to allow you to check your work.

Also complete the AC transfer function for this circuit. Again, the solution is already provided.

Simulation Setup – Bandwidth

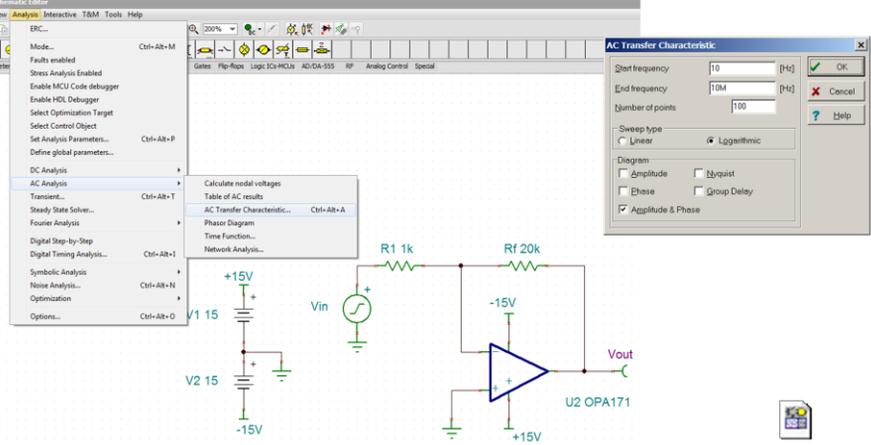Click **Analysis** → **AC Analysis** → **AC Transfer Characteristic** to show the AC response for the OPA171 circuit. Run the analysis from 10Hz to 10MHz.



03 - Bandwidth - OPA171.TSC

75

 **TEXAS INSTRUMENTS**


The next step is to run a SPICE simulation analysis for the AC transfer characteristic. This will allow us to see the op amp's closed loop bandwidth and DC gain in this configuration.

The necessary TINA-TI simulation schematic is embedded in this slide set – simply double-click the icon to open it. To run the analysis, click **Analysis** → **AC Analysis** → **AC Transfer Characteristic**. Run the analysis from 10Hz to 10MHz.

Simulation Results – Bandwidth

The cursor frequency and gain is read in this box.

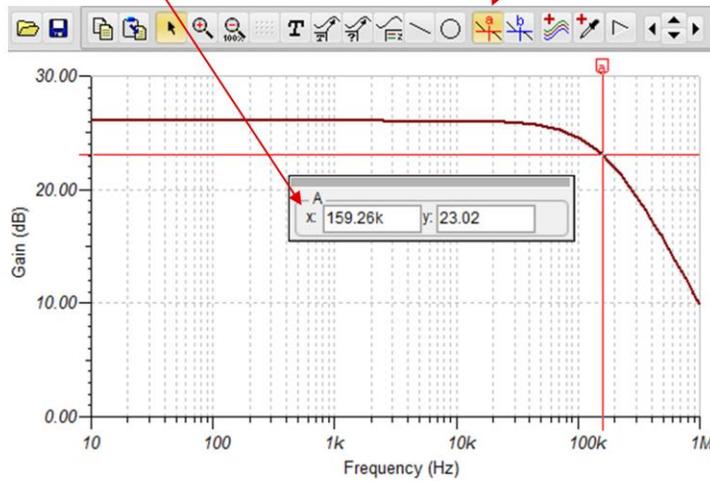Use the cursor to determine the bandwidth (-3dB point)




76

 TEXAS INSTRUMENTS

You should see a result similar to this. Enable the cursor, then check the DC gain, or gain at minimum frequency. The result will be 26dB, or 20V/V. Next, find the -3dB point, or the frequency where gain drops to 23dB. This occurs at 159kHz.

Make All “Not Found” devices are closed

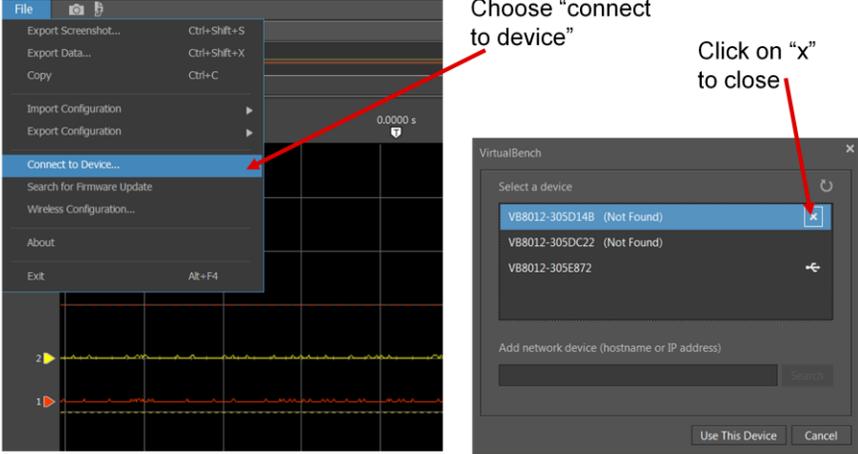

Choose “connect to device”

Click on “x” to close

File

- Export Screenshot... Ctrl+Shift+S
- Export Data... Ctrl+Shift+X
- Copy Ctrl+C
- Import Configuration
- Export Configuration
- Connect to Device...
- Search for Firmware Update
- Wireless Configuration...
- About
- Exit Alt+F4

0.0000 s

VirtualBench

Select a device

- VB8012-305D14B (Not Found)
- VB8012-305DC22 (Not Found)
- VB8012-305E872

Add network device (hostname or IP address)

Search


Use This Device Cancel

TEXAS INSTRUMENTS

We will be using a new software package. To prevent problems, make sure that all “not found” devices are closed.

Disable Function Generator

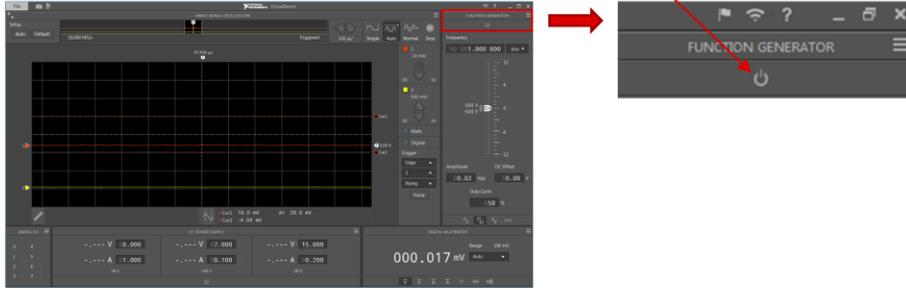Power button GRAY =
Function Generator OFF




78




Also make sure the Function Generator is OFF.

Disable DC Power Supply

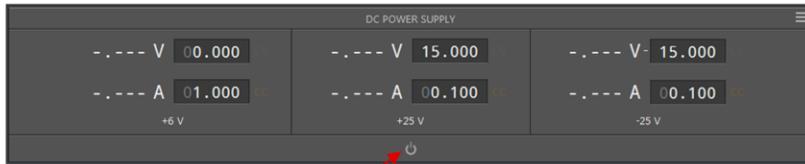

Power button GRAY = DC power supply OFF

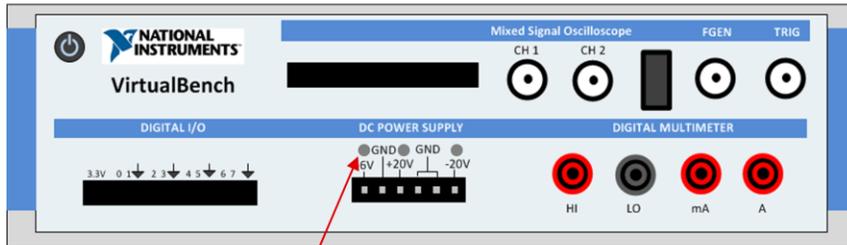


LEDs OFF = DC power supply OFF

79

 TEXAS INSTRUMENTS


Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

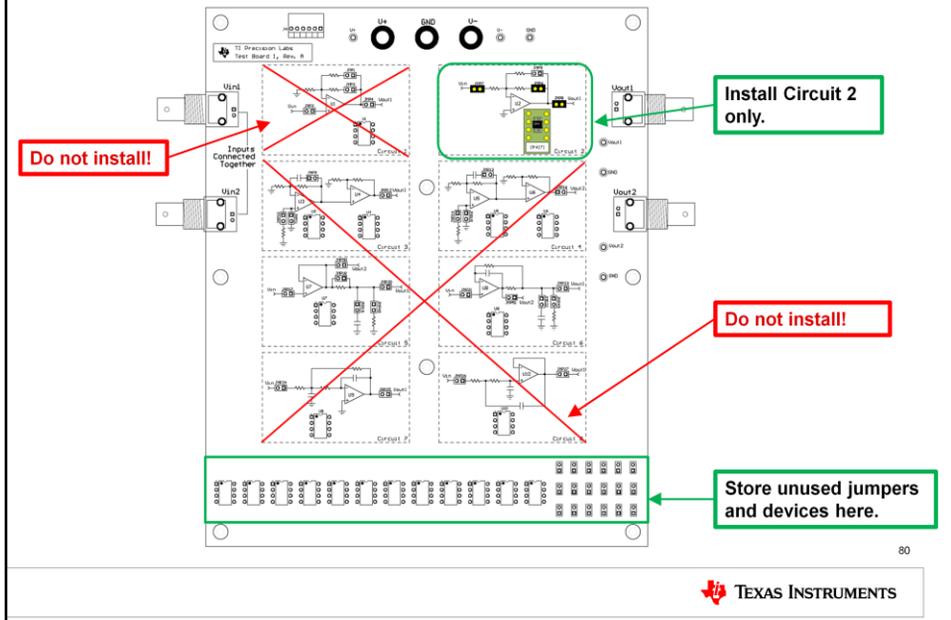

For this measurement, only circuit 2 is used. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup - Jumpers

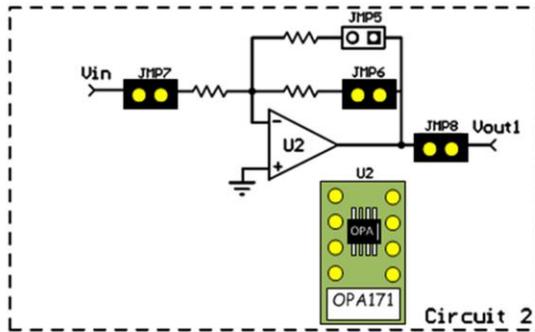

Jumper, Device	Description
JMP6	Select $R_f = 20k\Omega$ for gain = $-20V/V$
JMP7	Connect input to signal source
JMP8	Connect Circuit 2 output to V_{out1}
U2	Install OPA171


81



To prepare the test board for the measurement, install the jumpers and devices on circuit 2 as shown here.

Install JMP6, JMP7, and JMP8, as well as the OPA171 in socket U2.


Hardware Setup – Cables

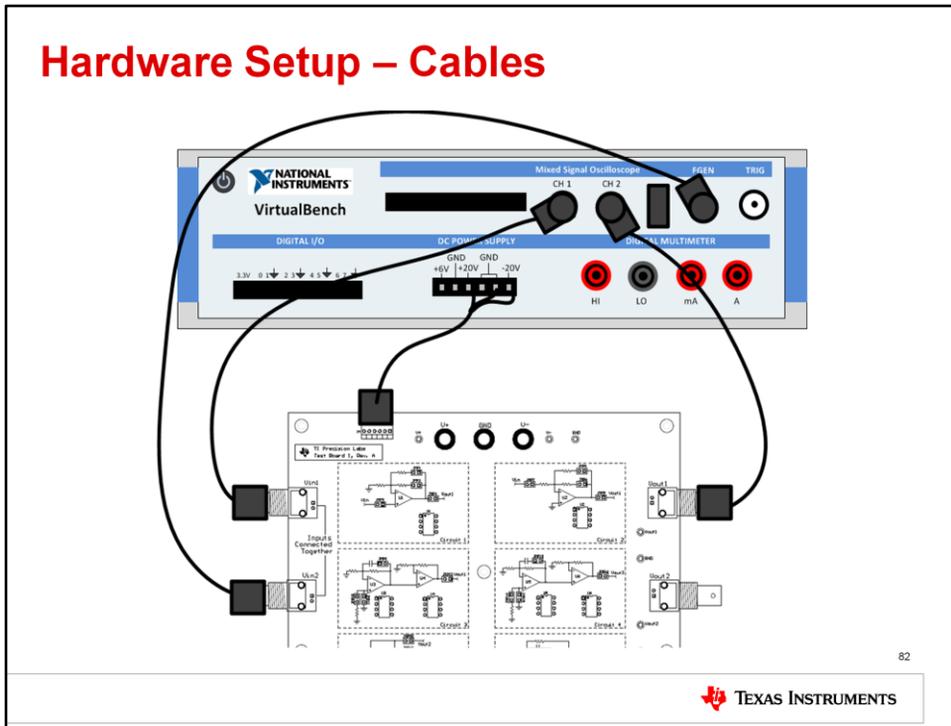

This slide gives the connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board. Connect Vin2 on the test board to VirtualBench channel FGEN, or function generator. Then connect Vin1 on the test board to VirtualBench oscilloscope channel 1, and Vout1 on the test board to VirtualBench oscilloscope channel 2.

Close VirtualBench Software

Click the 'X' to close

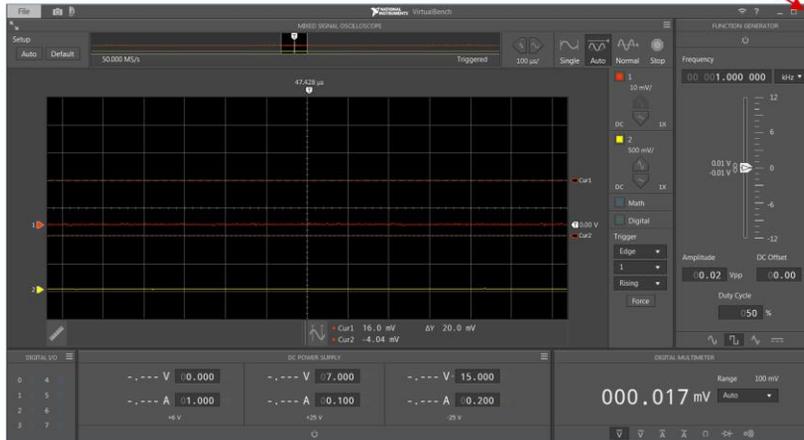


83



The VirtualBench software must be closed before continuing with the lab. Click the 'X' in the top-right corner of the software to close.

Open Bode Analyzer Software

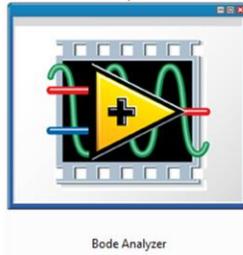Double-click icon on desktop to start **Bode Analyzer** software.



84

 TEXAS INSTRUMENTS

This lab requires additional Bode analyzer software. Install the software, then run it by double-clicking the Bode Analyzer icon on the desktop. You may also run the software by clicking Start → All Programs → Bode Analyzer → Bode Analyzer.

Bode Analyzer Setup

Power Supply

	+6V	+25V	-25V	
Voltage (V)	0	15	15	14.992
Current Limit(A)	0.1	0	0.1	0.001

FGEN

Amplitude (V) 0.05 DC Offset (V) 0

Measurement

Frequency (Hz) 8.9M

Start Frequency (Hz) 10 No. of Points to Average 10

End Frequency (Hz) 10M No. of Points/Decade 20

Start

±15V , 0.100A power supply. Press **GREEN** button to turn on power.

Start Frequency = 10Hz
End Frequency = 10MHz
No. of Points to Average = 10
No. of Points/Decade = 20

Press **Start** to run the analyzer


85

TEXAS INSTRUMENTS

In the configuration panel, set the power supply to $\pm 15V$, 0.1A. Press the green button to turn on the power.

Set the start frequency to 10Hz and the end frequency to 10MHz. Set the number of points to average to 10, and the number of points per decade to 20. Press "Start" to run the Bode analyzer.


Measurement – Bode Analyzer

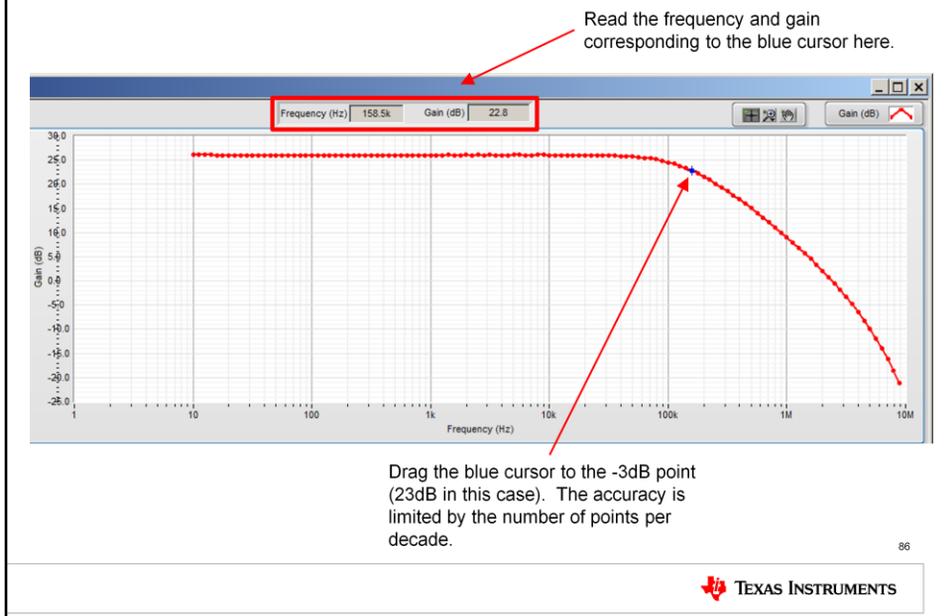

You should see a result similar to this. Enable the cursor, then drag the cursor to the -3dB point, or 23dB in this case. Take note of the frequency – in this case the result is 159kHz, although your results may vary slightly.

Measurement Results – Bandwidth

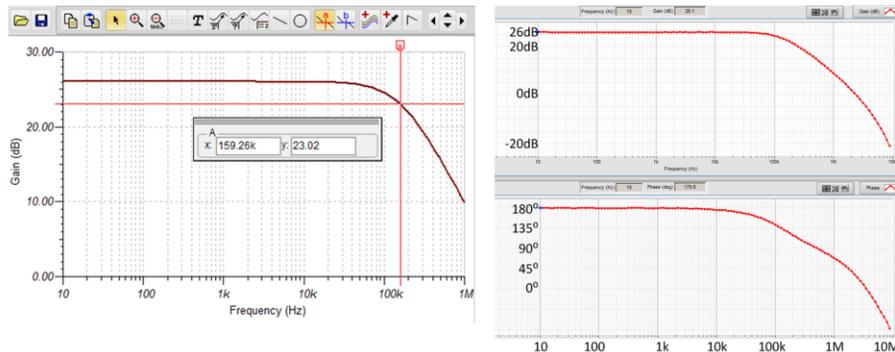1. Compare TINA-TI™ simulation results to measured results.



2. Compare the calculated, simulated, and measured bandwidth for the OPA171.


Device	Calculated	Simulated	Measured
OPA171	143kHz	159kHz	159kHz

87




Compare the bandwidth measurement of the VirtualBench to the simulated results from TINA-TI. Compare this to your calculated results. You should see very good correlation between all three values, although your numbers may vary slightly.

Reset Software

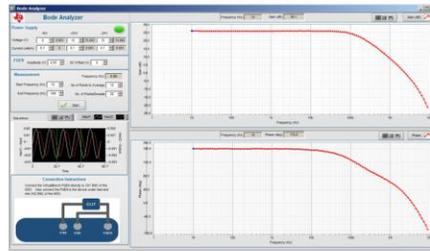

1. Close the Bode Analyzer software

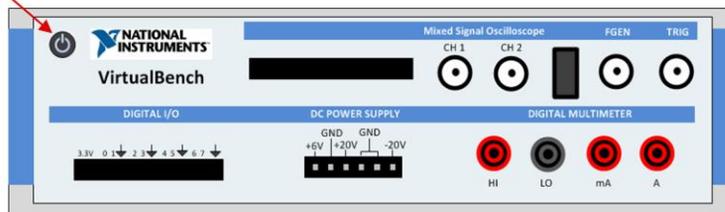2. Cycle power to restart VirtualBench software



88

TEXAS INSTRUMENTS

The bandwidth lab is now complete. Before continuing to the next lab, you must reset the software. First, close the Bode Analyzer software by clicking the 'X' in the top-right corner. Next, cycle power on the VirtualBench by turning power off and on. This will restart the VirtualBench software.



Slew Rate – Lab
TI Precision Labs – Op Amps

Developed by Art Kay and Ian Williams

TIDesigns
PRECISION

89

 TEXAS INSTRUMENTS

Hello, and welcome to the presentation for the TI Precision Lab supplement for op amp slew rate. This lab will walk through detailed calculations, SPICE simulations, and real-world measurements that greatly help to reinforce the concepts established in the slew rate lecture.

Required/Recommended Equipment

- Calculation
 - Pencil and paper
 - **Recommended:** MathCAD, Excel, or similar
- Simulation
 - SPICE simulation software
 - **Recommended:** TINA-TI™
- Measurement
 - TI Precision Labs PCB from Texas Instruments
 - Oscilloscope
 - Function generator
 - $\pm 15\text{V}$ power supply
 - **Recommended:** National Instruments VirtualBench™

The detailed calculation portion of this lab can be done by hand, but calculation tools such as MathCAD or Excel can help greatly.


The simulation exercises can be performed in any SPICE simulator, since Texas Instruments provides generic SPICE models of the op amps used in this lab. However, the simulations are most conveniently done in TINA-TI, which is a free SPICE simulator available from the Texas Instruments website. TINA simulation schematics are embedded in the presentation.

Finally, the real-world measurements are made using a printed circuit board, or PCB, provided by Texas Instruments. If you have access to standard lab equipment, you can make the necessary measurements with any oscilloscope, function generator, and $\pm 15\text{V}$ power supply. However, we highly recommend the VirtualBench from National Instruments. The VirtualBench is an all-in-one test equipment solution which connects to a computer over USB or Wi-Fi and provides power supply rails, analog signal generator and oscilloscope channels, and a 5 ½ digit multimeter for convenient and accurate measurements. This lab is optimized for use with the VirtualBench.

Calculation – Slew Rate

Draw the output voltage waveform of the circuit shown below, based on the data sheet slew rate parameters given in the table.

PARAMETER		OPA277			UNIT
		MIN	TYP	MAX	
Gain-Bandwidth Product	GBW		1.0		MHz
Slew Rate	SR		0.8		V/ μ s

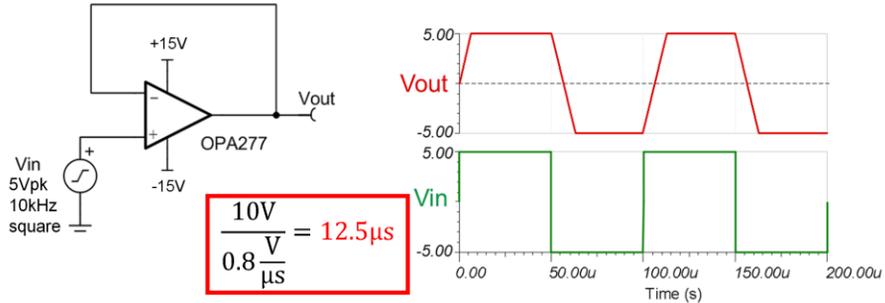


91

 TEXAS INSTRUMENTS

First, draw the output voltage waveform of the circuit shown below. Use the slew rate specifications given in the table and the techniques from the slew rate lecture.

Simulation Setup – Slew Rate

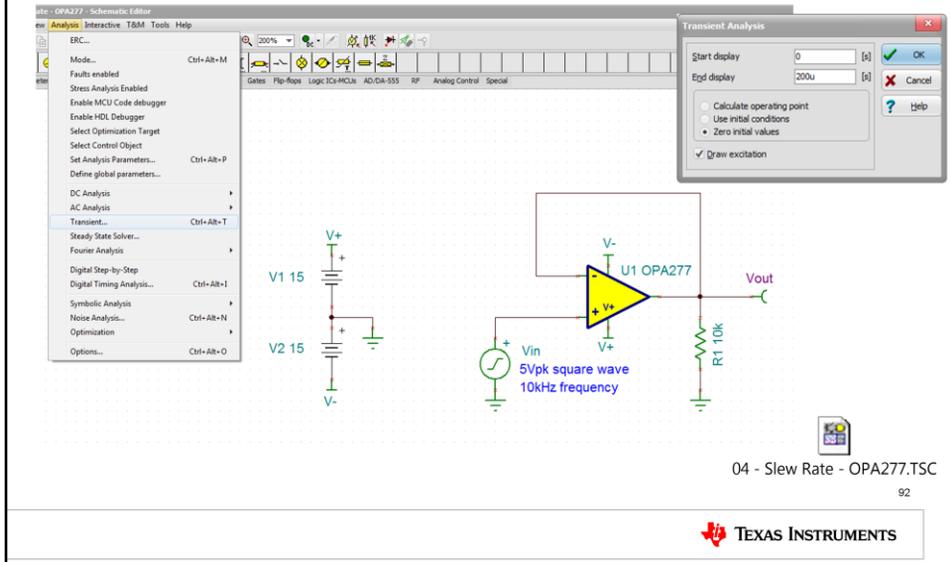
Click **Analysis** → **Transient** to show the slew rate limitations for the OPA277.
Run the analysis from 0 μ s to 200 μ s. The input is a 5Vpk, 10kHz square wave.



The next step is to run a SPICE simulation analysis for the transient output voltage behavior. This will allow us to see the op amp's output voltage response for a specified input signal, which in this case is a 5Vp, 10kHz square wave.

The necessary TINA-TI simulation schematic is embedded in this slide set – simply double-click the icon to open it. To simulate the transient output behavior, click **Analysis** → **Transient**. Run the analysis from 0 μ s to 200 μ s.


Simulation Results – Slew Rate

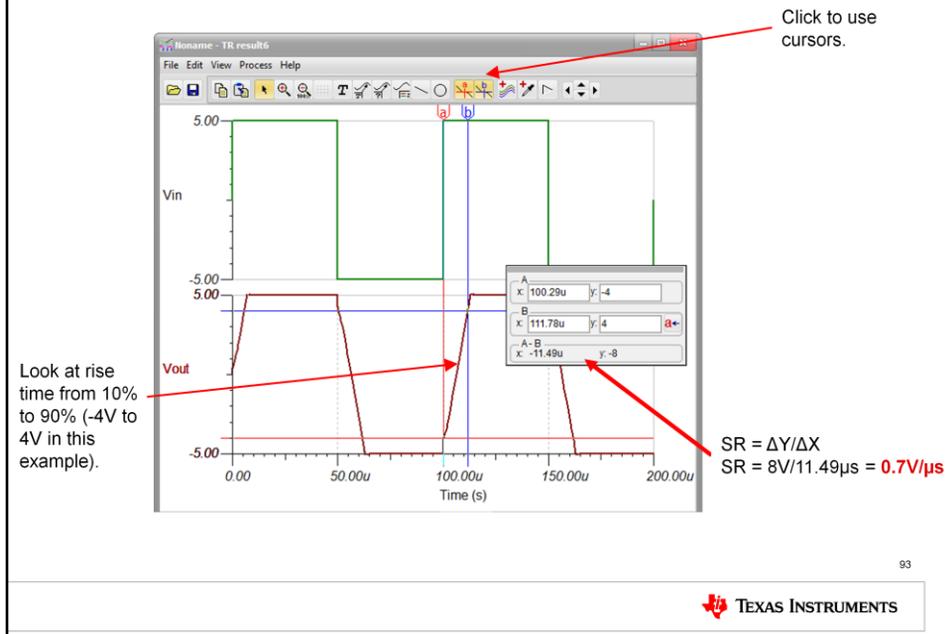

You should see a result similar to this. Vin is a square wave, as expected, but Vout must obey the slew rate limitations of the OPA277. You can see this effect in the rise time from 10% to 90% of the output, or -4V to 4V. Use the cursors to measure the time required to slew from -4V to 4V, and use the equation that slew rate = delta y over delta x to calculate the simulated slew rate of 0.7V/ μ s.

Disable Function Generator

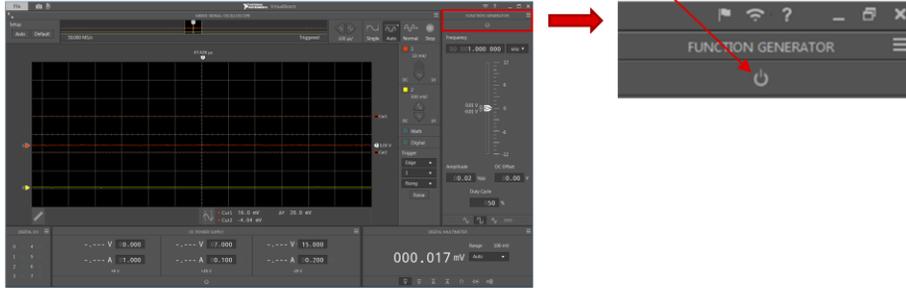
Power button GRAY =
Function Generator OFF




94

Also make sure the Function Generator is OFF.

Disable DC Power Supply

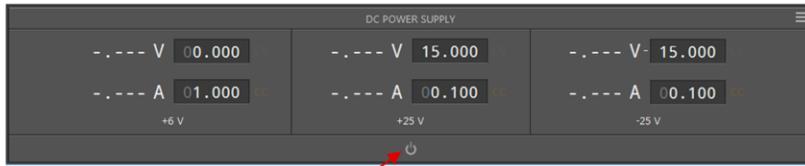

Power button GRAY = DC power supply OFF

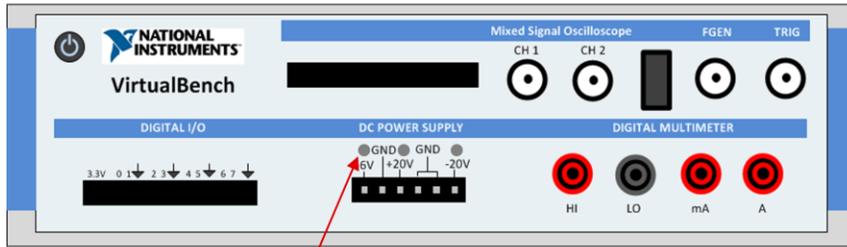


LEDs OFF = DC power supply OFF

95




Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

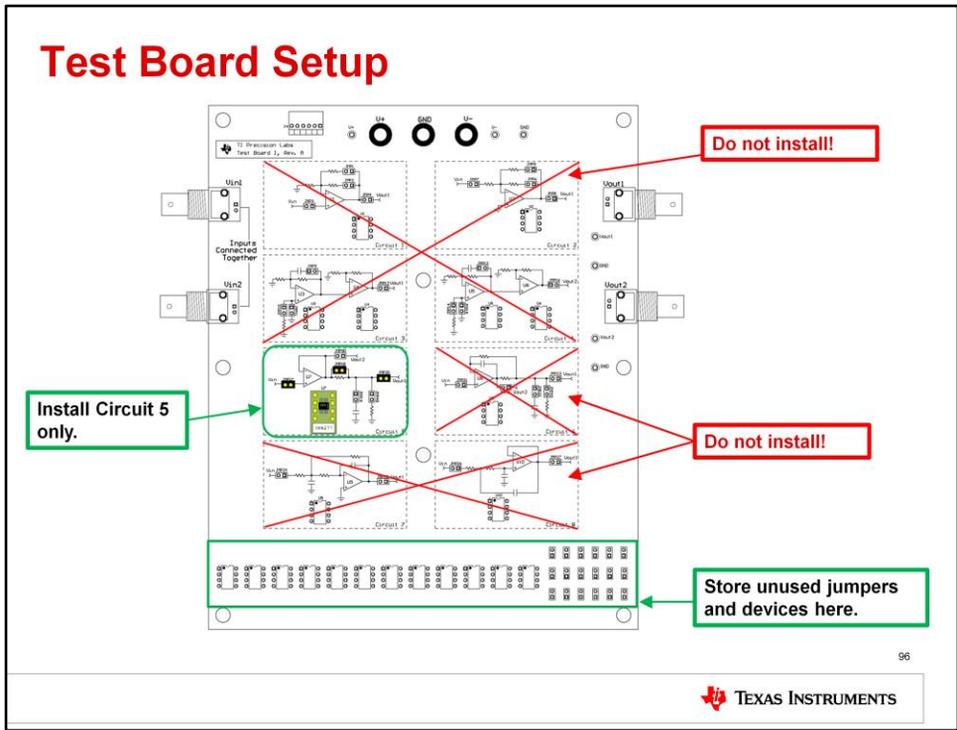

For the test board to function properly, it is important that you only install jumpers and devices in circuit 5. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup – Jumpers

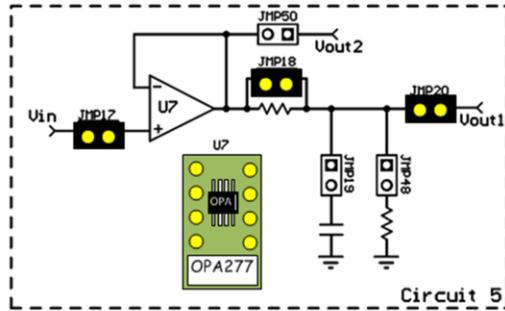

Jumper, Device	Description
JMP17	Connect input to signal source.
JMP18	Short output resistance
JMP20	Connect Circuit 5 output to Vout1
U7	Install OPA277


97



To prepare the test board for the measurement, install the jumpers and devices on circuit 5 as shown here.

Install JMP17, JMP18, and JMP20, as well as the OPA277 in socket U7.

Hardware Setup - Cables

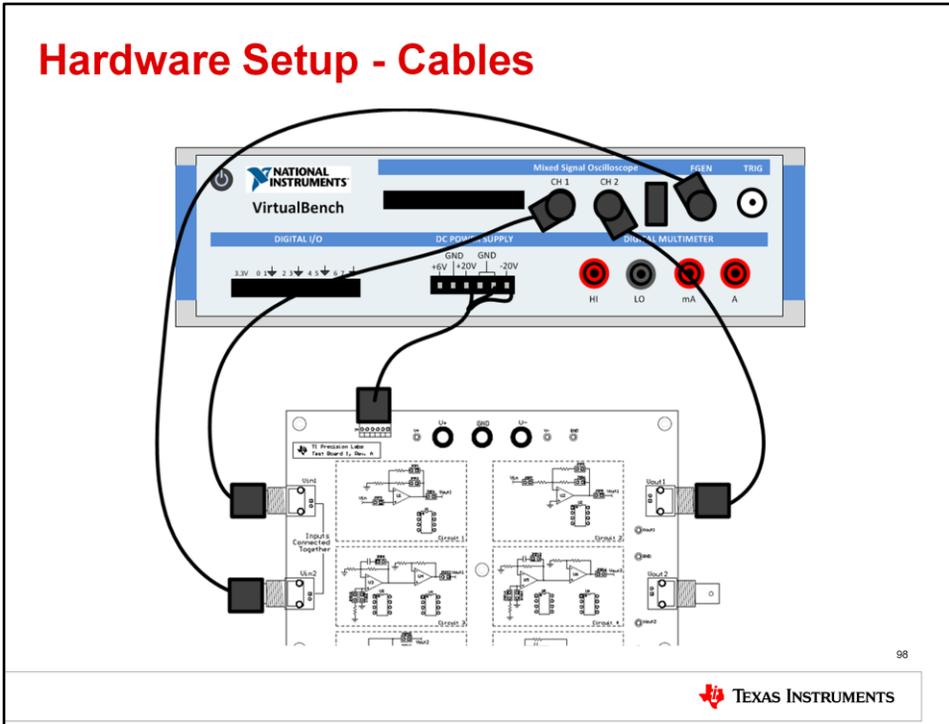

This slide gives the connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board. Connect Vin2 on the test board to VirtualBench channel FGEN, or function generator. Then connect Vin1 on the test board to VirtualBench oscilloscope channel 1, and Vout1 on the test board to VirtualBench oscilloscope channel 2.

VirtualBench™ Instrument Setup

20 μ s/div, "Auto" acquisition

10kHz signal frequency

DC coupled, 1x, 5V/div

10Vpp, 0V offset, 50% duty cycle square wave

First: Power supply enable/disable

± 15 V, 0.500A power supply

99

TEXAS INSTRUMENTS


Next apply power to the National Instruments VirtualBench and connect it to your computer with a USB cable. The hardware should be detected as a virtual CD drive, and you can run the VirtualBench software directly from the drive. Once the software opens, configure the software as follows:

Set the time scale to 20 μ s per division, with the acquisition mode set to "Auto." Enable channels 1 and 2 on the oscilloscope, and set them to 1x, DC-coupled mode, 5V/div. Enable the function generator and setup the signal as follows:

10kHz frequency, 10Vpp, 0V offset, 50% duty cycle square wave.

Set the +25V power supply to +15V, 0.500A. Set the -25V power supply to -15V, 0.500A. Press the power button to turn on the power supply rails.


Measurement Results – Slew Rate

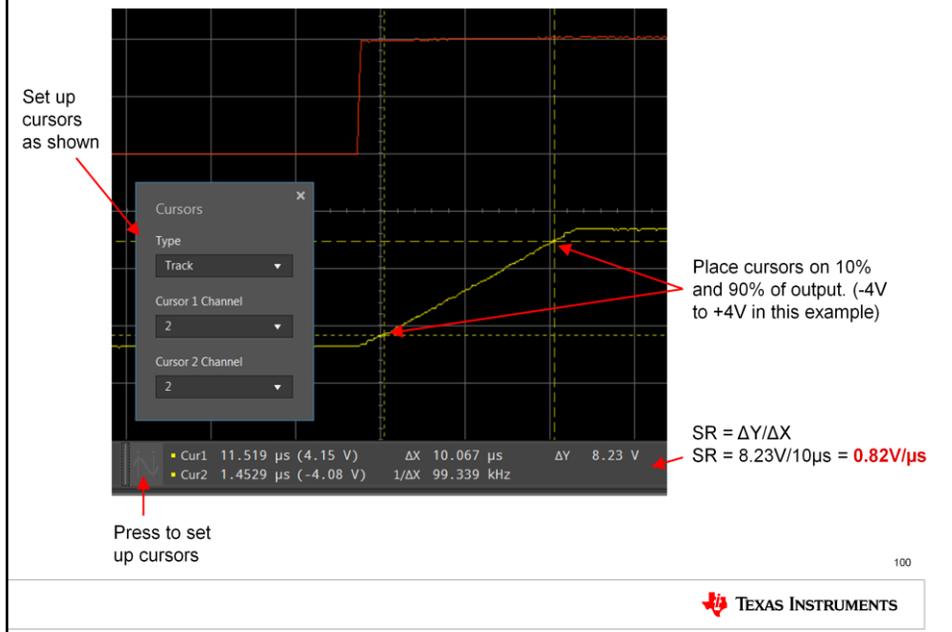

Let's now determine the measured slew rate. Enable cursors, set them up as shown, then place the cursors on 10% and 90% of the output signal. Take note of the time and voltage difference, and then calculate the slew rate using the equation given. In this example, a slew rate of $0.82\text{V}/\mu\text{s}$ was measured. You may have different results in your experiment.

Measurement Results – Slew Rate

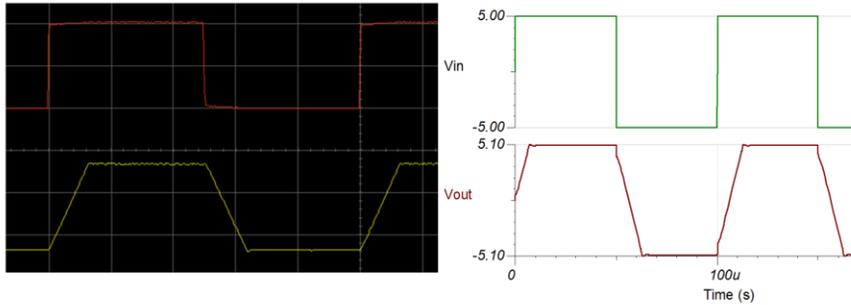1. Compare TINA-TI™ simulation results to measured results.




Slew Rate (data sheet):	0.8V/ μ s
Slew Rate (simulation):	8V / 11.49 μ s = 0.7V/ μ s
Slew Rate (measurement):	8.23V / 10 μ s = 0.82V/ μ s

101



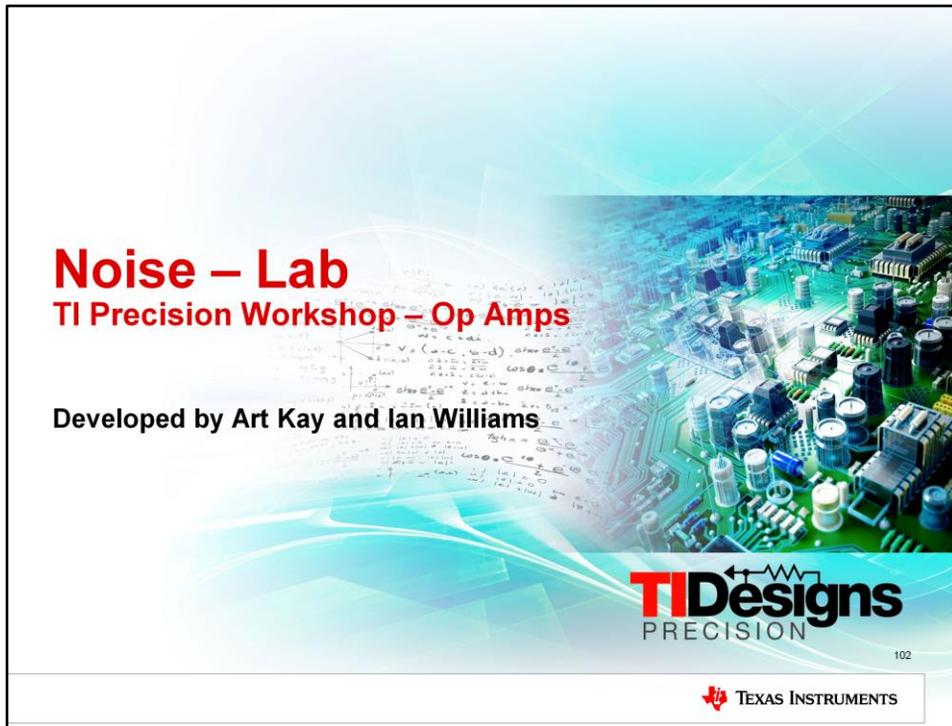Compare the oscilloscope display of the VirtualBench to the simulation results from TINA-TI. Also compare the slew rate values from the data sheet, simulation, and measurement. They should all be similar, although you may get slightly different results.



Noise – Lab
TI Precision Workshop – Op Amps

Developed by Art Kay and Ian Williams

TIDesigns
PRECISION

102

 TEXAS INSTRUMENTS

Hello, and welcome to the presentation for the TI Precision Lab supplement for intrinsic op amp noise. This lab will walk through detailed calculations, SPICE simulations, and real-world measurements that greatly help to reinforce the concepts established in the noise lecture.

Required/Recommended Equipment

- Calculation
 - Pencil and paper
 - **Recommended:** MathCAD, Excel, or similar
- Simulation
 - SPICE simulation software
 - **Recommended:** TINA-TI™
- Measurement
 - TI Precision Labs PCB from Texas Instruments
 - Oscilloscope
 - $\pm 12\text{V}$ power supply
 - **Recommended:** National Instruments VirtualBench™

The detailed calculation portion of this lab can be done by hand, but calculation tools such as MathCAD or Excel can help greatly since noise calculations can involve many steps.

The simulation exercises can be performed in any SPICE simulator, since Texas Instruments provides generic SPICE models of the op amps used in this lab. However, the simulations are most conveniently done in TINA-TI, which is a free SPICE simulator available from the Texas Instruments website. TINA simulation schematics are embedded in the presentation.

Finally, the real-world noise measurements are made using a printed circuit board, or PCB, provided by Texas Instruments. If you have access to standard lab equipment, you can make the necessary measurements with any $\pm 12\text{V}$ power supply and oscilloscope. However, we highly recommend the VirtualBench from National Instruments. The VirtualBench is an all-in-one test equipment solution which connects to a computer over USB or Wi-Fi and provides power supply rails, analog signal generator and oscilloscope channels, and a 5 ½ digit multimeter for convenient and accurate measurements. This lab is optimized for use with the VirtualBench.

Experiment 1

Output Noise – No Filter


104



In experiment 1, we'll determine the total output voltage noise in a circuit with no filtering.

Calculation – No Filter

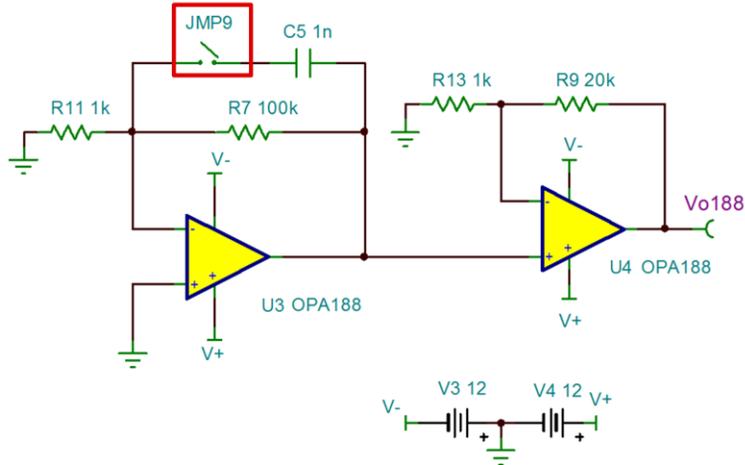Calculate the total RMS and peak-to-peak output noise voltage for the circuit shown below. Note that the switch **JMP9** is **OPEN**, so filter capacitor **C5** is **NOT CONNECTED**.



Calculate the result for both OPA188 and OPA211!

105

 TEXAS INSTRUMENTS

First, calculate the expected total RMS and peak-to-peak output noise voltage for the circuit shown here, using the techniques and equations given in the noise lecture. Note that the switch **JMP9** is open, so filter capacitor **C5** is not connected to the circuit. Make this calculation twice – first with the OPA188 selected for U1 and U2, then with the OPA211. The different parameters of these op amps will give you different noise results.

Calculation – No Filter

1. Use the data sheet parameters given below to calculate output noise.

PARAMETER		CONDITIONS	OPA188			UNIT
			MIN	TYP	MAX	
Input Voltage Noise Density	e_n	$f = 1\text{kHz}$		8.8		$\text{nV} / \sqrt{\text{Hz}}$
Input Current Noise Density	i_n	$f = 1\text{kHz}$		7		$\text{fA} / \sqrt{\text{Hz}}$
Gain Bandwidth	GBW			2		MHz

PARAMETER		CONDITIONS	OPA211			UNIT
			MIN	TYP	MAX	
Input Voltage Noise Density	e_n	$f = 1\text{kHz}$		1.1		$\text{nV} / \sqrt{\text{Hz}}$
Input Current Noise Density	i_n	$f = 1\text{kHz}$		3.2		$\text{pA} / \sqrt{\text{Hz}}$
Gain Bandwidth	GBW			80		MHz

Answers	OPA188	OPA211
Total RMS output noise	$3.6\text{mV}_{\text{RMS}}$	$10.7\text{mV}_{\text{RMS}}$
Total peak-to-peak noise	22mV_{PP}	64mV_{PP}

106



In order to perform the noise calculations, you need to know certain parameters of each op amp. The key parameters are the op amp gain bandwidth product, or GBW, input voltage noise density, or e_n , and input current noise density, or i_n . This slide gives a table of these key specs for both the OPA188 and OPA211.

Enter your answers in the table at the bottom of the slide. The solutions are already provided to allow you to check your work.

Calculation – No Filter, OPA188

OPA188 noise, no filter

Thermal noise calculation

$$k_n := 1.38 \cdot 10^{-23} \quad T_n := 273 + 25 \quad R_n := 1 \cdot 10^3$$

$$e_{n_r} := \sqrt{4k_n \cdot T_n \cdot R_n} = 4.056 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}}$$

op-amp current and voltage noise

$$e_{n_opa} := 8.8 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}} \quad \text{From OPA188 Data sheet}$$

$$i_n := 7 \times 10^{-15} \quad \text{From OPA188 Data sheet}$$

$$e_{n_i} := R_n \cdot i_n = 7 \times 10^{-12}$$

Add thermal noise and voltage noise calculation

$$e_{n_total} := \sqrt{e_{n_r}^2 + e_{n_opa}^2 + e_{n_i}^2} = 9.69 \times 10^{-9}$$

Gain from two stage amp

$$G_{n1} := 101 \quad G_{n2} := 21$$

$$\text{GBW} := 2 \cdot 10^6 \quad \text{From OPA188 Data sheet}$$

Closed loop bandwidth (-3dB)

$$f_c := \frac{\text{GBW}}{G_{n1}} = 19.802 \times 10^3 \text{ Hz}$$

Noise bandwidth (-3dB)

$$\text{BW}_n := 1.57 \cdot f_c = 31.089 \times 10^3 \text{ Hz}$$

$$E_n := e_{n_total} \sqrt{\text{BW}_n} = 1.708 \times 10^{-6} \text{ Vrms}$$

Total rms noise

$$E_{n_out} := G_{n1} \cdot G_{n2} \cdot E_n = 3.624 \times 10^{-3} \text{ Vrms}$$

Peak-to-peak output noise

$$V_{pp_out} := 6E_{n_out} = 0.022 \text{ Vpp}$$

107



I won't go through the entire calculation, but will give an overview of the key steps. First, the resistor thermal noise spectral density is calculated using the circuit resistor values. Next, the total input noise spectral density is computed based on the resistor thermal noise, op amp input voltage noise, and op amp input current noise once it's been converted to voltage. The op amp's GBW and the circuit's closed-loop bandwidth are used to calculate the noise bandwidth, which enables you to determine the total input-referred RMS noise. Finally, the input-referred noise is multiplied by the closed-loop gain in order to compute the total RMS and peak-to-peak output noise. This slide shows the complete calculation for the OPA188.

Calculation – No Filter, OPA211

OPA211 noise, no filter

Thermal noise calculation

$$k_n := 1.38 \cdot 10^{-23} \quad T_n := 273 + 25 \quad R_n := 1 \cdot 10^3$$

$$e_{n_r} := \sqrt{4k_n \cdot T_n \cdot R_n} = 4.056 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}}$$

op-amp current and voltage noise

$$e_{n_opa} := 1.1 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}} \quad \text{From OPA211 Data sheet}$$

$$i_n := 1.7 \times 10^{-12} \quad \text{From OPA211 Data sheet}$$

$$e_{n_i} := R_n \cdot i_n = 1.7 \times 10^{-9}$$

Add thermal noise and voltage noise calculation

$$e_{n_total} := \sqrt{e_{n_r}^2 + e_{n_opa}^2 + e_{n_i}^2} = 4.533 \times 10^{-9}$$

Gain from two stage amp

$$G_{n1} := 101 \quad G_{n2} := 21$$

$$\text{GBW} := 80 \cdot 10^6 \quad \text{From OPA211 Data sheet}$$

Closed loop bandwidth (-3dB)

$$f_c := \frac{\text{GBW}}{G_{n1}} = 792.079 \times 10^3 \text{ Hz}$$

Noise bandwidth (-3dB)

$$\text{BW}_n := 1.57 \cdot f_c = 1.244 \times 10^6 \text{ Hz}$$

$$E_n := e_{n_total} \sqrt{\text{BW}_n} = 5.055 \times 10^{-6} \text{ Vrms}$$

Total rms noise

$$E_{n_out} := G_{n1} \cdot G_{n2} \cdot E_n = 10.72 \times 10^{-3} \text{ Vrms}$$

Peak-to-peak output noise

$$V_{pp_out} := 6E_{n_out} = 0.064 \text{ Vpp}$$

108



This slide shows the calculation for the OPA211. The op amp's input voltage and current spectral density, as well as the op amp gain bandwidth product, are different, but the steps of the calculation are exactly the same. Simply substitute in the new values and take note of the result.

Simulation Setup – No Filter

Click **Analysis** → **Noise Analysis** to compute the total output noise. Run the noise analysis from 1Hz to 100MHz and select the **Total Noise** diagram. The filter capacitor is disconnected.

Note that the capacitor is disconnected.

Run the simulation for both the OPA188 and OPA211!

05 - Noise - OPA188.TSC

05 - Noise - OPA211.TSC


109

TEXAS INSTRUMENTS

The next step is to run a SPICE simulation analysis for the total output noise. Simply open the TINA-TI simulation schematics embedded in the presentation, ensure that filter capacitor jumper is open, then select Analysis, followed by Noise Analysis. Make sure that “total noise” is selected, then run the analysis from 1Hz to 100MHz.

Run the simulation for both the OPA188 and OPA211!

Simulation Results – No Filter

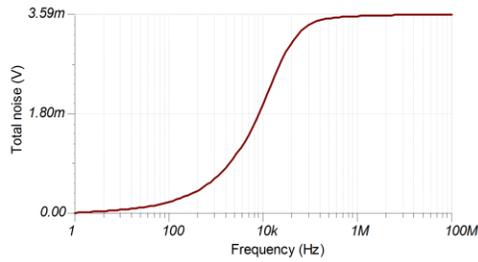


OPA188

$$E_{n-rms} = 3.59mV_{RMS}$$

$$E_{n-pp} = E_{n-rms} * 6$$

$$E_{n-pp} = 21.5mV_{PP}$$

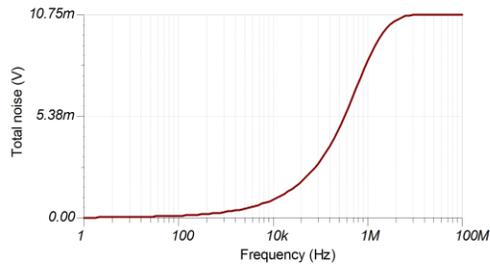

OPA211

$$E_{n-rms} = 10.75mV_{RMS}$$

$$E_{n-pp} = E_{n-rms} * 6$$

$$E_{n-pp} = 64.5mV_{PP}$$


110



Over the 100MHz frequency range, the OPA188 circuit has a total noise of 3.59mVrms, or 21.5mVpp. The OPA211 circuit has a total noise of 10.75mVrms, or 64.5mVpp.

Disable Function Generator

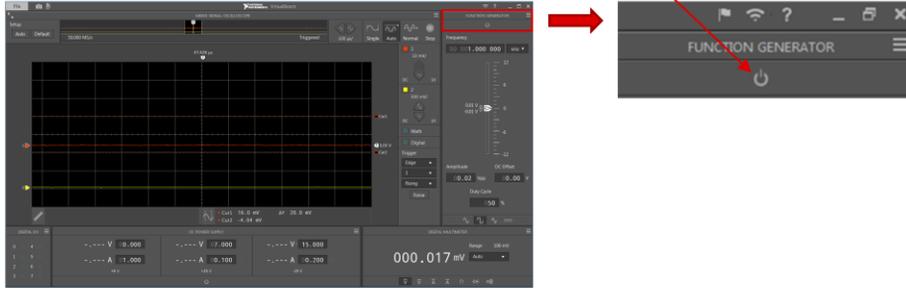Power button GRAY =
Function Generator OFF




111




Also make sure the Function Generator is OFF.

Disable DC Power Supply

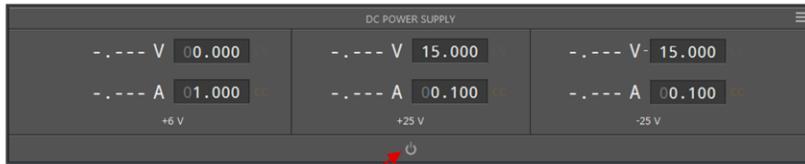

Power button GRAY = DC power supply OFF

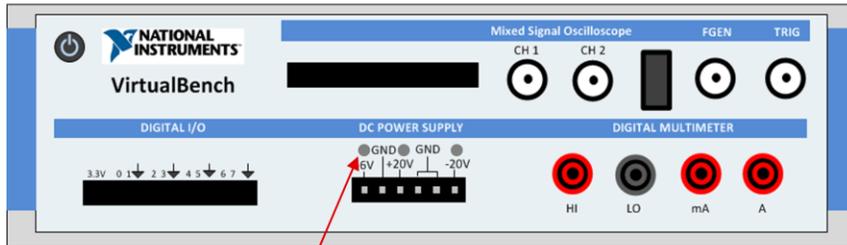


LEDs OFF = DC power supply OFF

112




Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

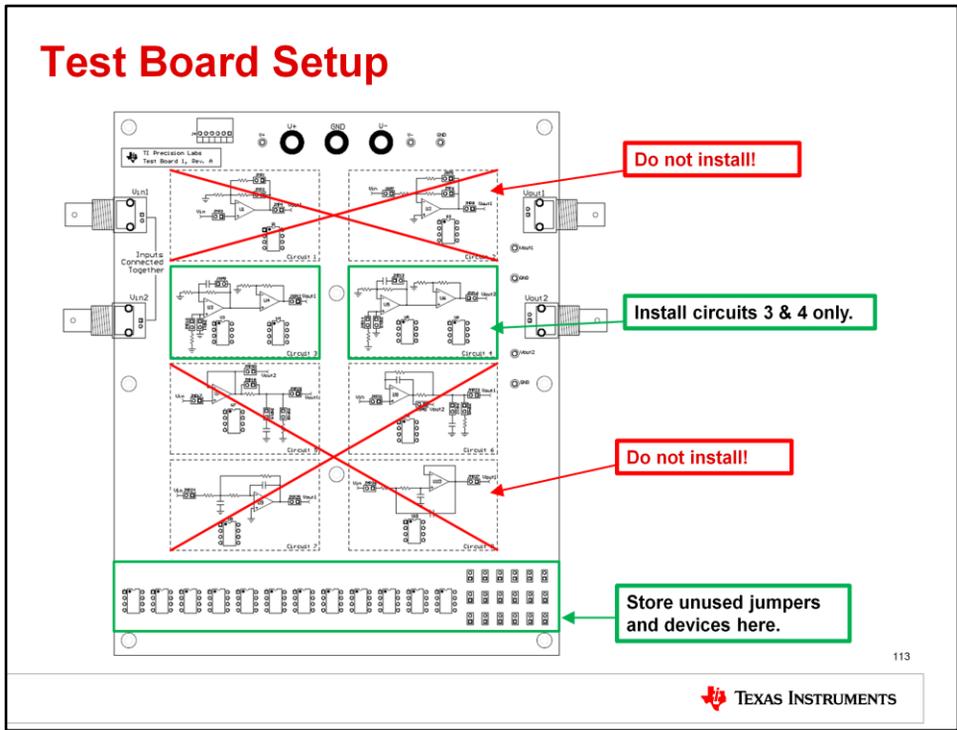

For the test board to function properly, it is important that you only install jumpers and devices in circuits 3 and 4. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup - Jumpers

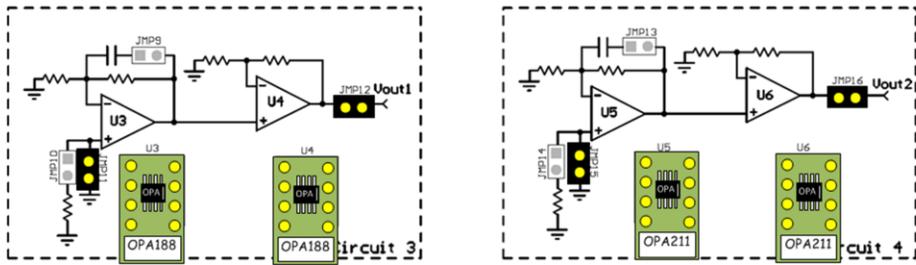

Jumper, Device	Description
JMP11, JMP15	Connect VIN+ to GND
JMP12, JMP16	Connect Circuit 3 to Vout1, connect Circuit 4 to Vout2
U3, U4	Install OPA188
U5, U6	Install OPA211


114

 TEXAS INSTRUMENTS

To prepare the test board for the measurement, install the jumpers and devices on circuit 3 and circuit 4 as shown here.

On circuit 3, install JMP11 and JMP12, as well as the OPA188 in sockets U3 and U4. On circuit 4, install JMP15 and JMP16, as well as the OPA211 in sockets U5 and U6.

Hardware Setup – Cables

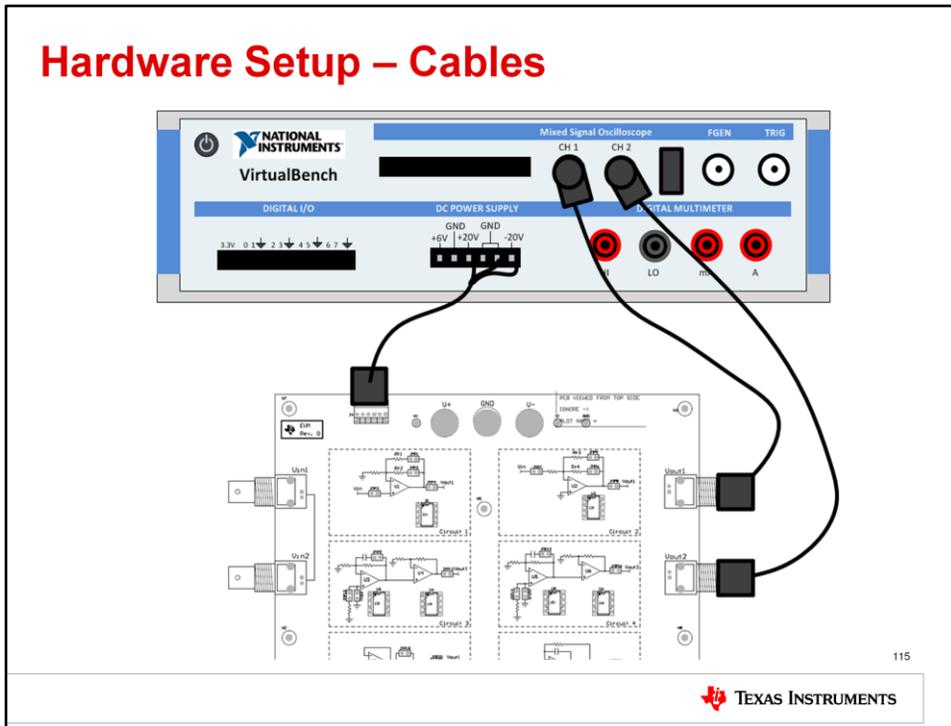

This slide gives the connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board. Connect Vout1 on the test board to VirtualBench oscilloscope channel 1, and Vout2 on the test board to Virtual Bench oscilloscope channel 2, using BNC cables.

VirtualBench™ Instrument Setup

The screenshot shows the VirtualBench software interface. At the top, the title "VirtualBench™ Instrument Setup" is displayed in red. The main window features an oscilloscope with two channels of waveforms (orange and green) and a power supply control panel. Red boxes and arrows highlight the following elements:

- 100ms/div, "Auto" Acquisition:** Points to the acquisition mode and time scale settings.
- AC coupled, 1x, CH1 = 10mV/div, CH2 = 20mV/div:** Points to the channel settings on the right.
- Use Pk-Pk and RMS measurement options. This is where you read output voltage.** Points to the measurement options at the bottom left.
- First: Power supply enable/disable:** Points to the power supply control buttons at the bottom center.
- ±15V, 0.500A power supply:** Points to the power supply output settings at the bottom right.

116


TEXAS INSTRUMENTS

Next apply power to the National Instruments VirtualBench and connect it to your computer with a USB cable. The hardware should be detected as a virtual CD drive, and you can run the VirtualBench software directly from the drive. Once the software opens, configure the software as follows:

Set the time scale to 100ms per division, with the acquisition mode set to "Auto." Enable channels 1 and 2 on the oscilloscope, and set them to 1x, AC-coupled mode. Set the vertical scale on channel 1 to 10mV/div, and on channel 2 to 20mV/div. Set the +25V power supply to +15V, 0.500A. Set the -25V power supply to -15V, 0.500A. Press the power button to turn on the power supply rails.

Enable Peak-to-peak and RMS measurements on both channels in order to read the output voltage of each circuit.

VirtualBench™ Scope Mode

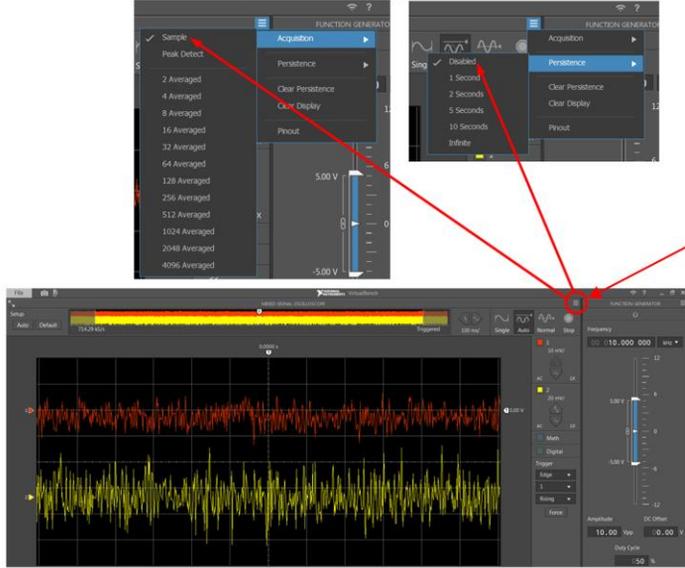

The image displays the VirtualBench software interface. At the top, two inset screenshots show the 'Acquisition' menu. The left inset shows the 'Acquisition' menu with 'Sample' selected. The right inset shows the 'Persistence' menu with 'Disabled' selected. Red arrows point from these insets to a red circle on the main interface, which highlights a button on the front panel. To the right of this circle, text reads: 'Click to set scope mode: Acquisition = Sample Persistence = Disabled'. The main interface shows a waveform display with two traces (red and green) and various control panels on the right.


Click to set scope mode:
Acquisition = Sample
Persistence = Disabled

117

 TEXAS INSTRUMENTS

You must also set the mode of the Virtual Bench oscilloscope. Click the button shown on the front panel, then set Acquisition to “Sample” and Persistence to “Disabled.”

Oscilloscope Settings – Coupling & Probe

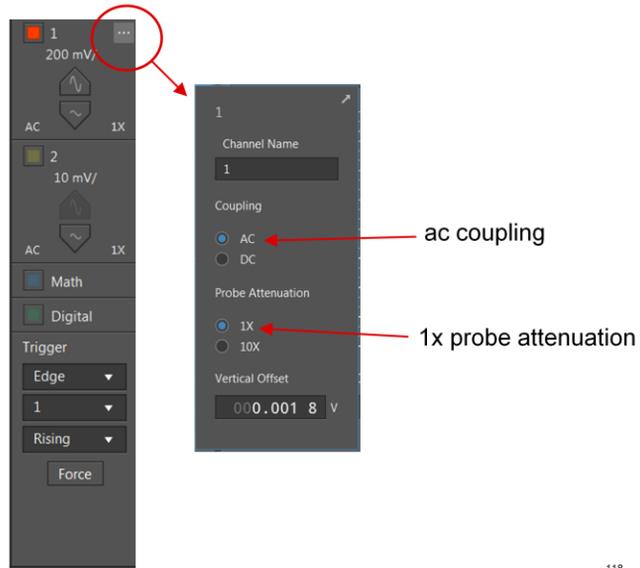



118

 TEXAS INSTRUMENTS

The icon at the top right of the oscilloscope opens a new window with more options for each channel. Each channel can be given a custom name. Set the coupling mode to AC. Set probe attenuation to 1x.

Measurement Results – No Filter

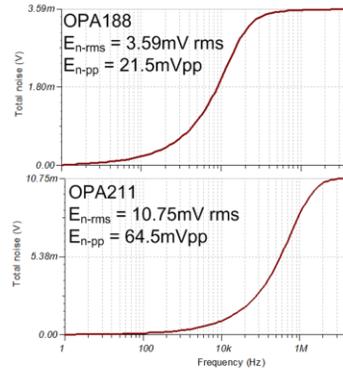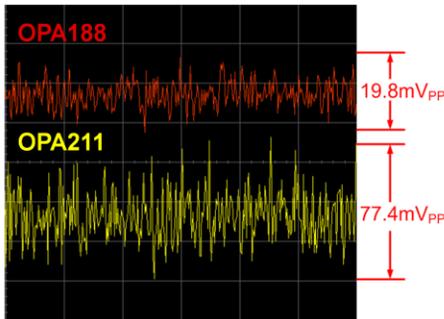1. Compare TINA-TI™ simulation results to measured and calculated results.



Device	Calculated Noise (RMS)	Simulated Noise (RMS)	Measured Noise (RMS)
OPA188	3.62mV _{RMS}	3.59mV _{RMS}	3.3mV _{RMS}
OPA211	10.72mV _{RMS}	10.75mV _{RMS}	12.9mV _{RMS}

Note: Measured RMS noise is determined using measured peak-to-peak noise divided by 6.

119



The expected output voltage noise results from the measurement are shown in the screenshot at the top left. The OPA188 has a measured noise of 19.8mVpp, or 3.3mVrms, and the OPA211 has a measured noise of 77.4mVpp, or 12.9mVrms. As you can see from the table, this agrees extremely well with the results from calculation and simulation!

Experiment 2

Output Noise with Filter


120



In experiment 2, we'll determine the total output voltage noise in a circuit with a filter capacitor in the feedback network.

Calculation – With Filter

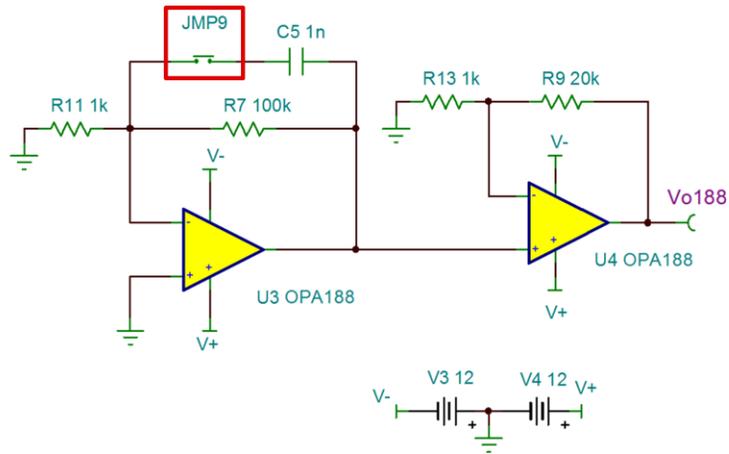Calculate the total RMS and peak-to-peak output noise voltage for the circuit shown below. Note that the switch **JMP9** is **CLOSED**, so filter capacitor **C5** is **CONNECTED**.



Calculate the result for both OPA188 and OPA211!

121



Perform another total noise calculation on the circuit shown. However, this time a filter capacitor is added to the feedback network of the first amplifier stage. This capacitor will reduce the circuit's noise bandwidth, so the overall noise performance will be significantly improved. As before, do the calculations with both the OPA188 and OPA211.

Calculation – With Filter

1. Use the data sheet parameters given below to calculate output noise.

PARAMETER		CONDITIONS	OPA188			UNIT
			MIN	TYP	MAX	
Input Voltage Noise Density	e_n	$f = 1\text{kHz}$		8.8		$\text{nV} / \sqrt{\text{Hz}}$
Input Current Noise Density	i_n	$f = 1\text{kHz}$		7		$\text{fA} / \sqrt{\text{Hz}}$
Gain Bandwidth	GBW			2		MHz

PARAMETER		CONDITIONS	OPA211			UNIT
			MIN	TYP	MAX	
Input Voltage Noise Density	e_n	$f = 1\text{kHz}$		1.1		$\text{nV} / \sqrt{\text{Hz}}$
Input Current Noise Density	i_n	$f = 1\text{kHz}$		3.2		$\text{pA} / \sqrt{\text{Hz}}$
Gain Bandwidth	GBW			80		MHz

Answers	OPA188	OPA211
Total RMS output noise	1mV_{RMS}	$0.48\text{mV}_{\text{RMS}}$
Total peak-to-peak noise	6mV_{PP}	$2.88\text{mV}_{\text{PP}}$

122



The key parameters of op amp gain bandwidth product, or GBW, input voltage noise density, or e_n , and input current noise density, or i_n are given again for your reference.

Enter your answers in the table at the bottom of the slide. The solutions are already provided to allow you to check your work.

Calculation – With Filter, OPA188

OPA188 noise, with filter

Thermal noise calculation

$$k_n := 1.38 \cdot 10^{-23} \quad T_n := 273 + 25 \quad R_n := 1 \cdot 10^3$$

$$e_{n_r} := \sqrt{4k_n \cdot T_n \cdot R_n} = 4.056 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}}$$

op-amp current and voltage noise

$$e_{n_{\text{opa}}} := 8.8 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}} \quad \text{From OPA188 Data sheet}$$

$$i_n := 7 \times 10^{-15} \quad \text{From OPA188 Data sheet}$$

$$e_{n_i} := R_n \cdot i_n = 7 \times 10^{-12}$$

Add thermal noise and voltage noise calculation

$$e_{n_{\text{total}}} := \sqrt{e_{n_r}^2 + e_{n_{\text{opa}}}^2 + e_{n_i}^2} = 9.69 \times 10^{-9}$$

Gain from two stage amp

$$G_{n1} := 101 \quad G_{n2} := 21$$

$$\text{GBW} := 2 \cdot 10^6 \quad \text{From OPA188 Data sheet}$$

Closed loop bandwidth (-3dB)

$$f_c := \frac{1}{2 \cdot \pi \cdot 100 \cdot 10^3 \cdot 1 \cdot 10^{-9}} = 1.592 \times 10^3 \text{ Hz}$$

Noise bandwidth (-3dB)

$$\text{BW}_n := 1.57 \cdot f_c = 2.499 \times 10^3 \text{ Hz}$$

$$E_n := e_{n_{\text{total}}} \sqrt{\text{BW}_n} = 4.844 \times 10^{-7} \text{ V}_{\text{rms}}$$

Total rms noise

$$E_{n_{\text{out}}} := G_{n1} \cdot G_{n2} \cdot E_n = 1.027 \times 10^{-3} \text{ V}_{\text{rms}}$$

Peak-to-peak output noise

$$V_{\text{pp_out}} := 6E_{n_{\text{out}}} = 6.164 \times 10^{-3} \text{ V}_{\text{pp}}$$

123



The steps in the calculation are nearly the same as before. However, this time the filter capacitor must be taken into account when calculating the circuit's closed-loop bandwidth. With the filter capacitor connected, the closed-loop bandwidth is computed to be 1.59kHz. Without the capacitor, the bandwidth was 19.8kHz! As expected, this helps to reduce the total noise.

Calculation – With Filter, OPA211

OPA211 noise, with filter

Thermal noise calculation

$$k_n := 1.38 \cdot 10^{-23} \quad T_n := 273 + 25 \quad R_n := 1 \cdot 10^3$$

$$e_{n_r} := \sqrt{4k_n \cdot T_n \cdot R_n} = 4.056 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}}$$

op-amp current and voltage noise

$$e_{n_opa} := 1.1 \times 10^{-9} \frac{\text{V}}{\sqrt{\text{Hz}}} \quad \text{From OPA211 Data sheet}$$

$$i_n := 1.7 \times 10^{-12} \quad \text{From OPA211 Data sheet}$$

$$e_{n_i} := R_n \cdot i_n = 1.7 \times 10^{-9}$$

Add thermal noise and voltage noise calculation

$$e_{n_total} := \sqrt{e_{n_r}^2 + e_{n_opa}^2 + e_{n_i}^2} = 4.533 \times 10^{-9}$$

Gain from two stage amp

Gain from two stage amp

$$G_{n1} := 101 \quad G_{n2} := 21$$

$$GBW := 80 \cdot 10^6 \quad \text{From OPA211 Data sheet}$$

Closed loop bandwidth (-3dB)

$$f_c := \frac{1}{2 \cdot \pi \cdot 100 \cdot 10^3 \cdot 1 \cdot 10^{-9}} = 1.592 \times 10^3 \text{ Hz}$$

Noise bandwidth (-3dB)

$$BW_n := 1.57 \cdot f_c = 2.499 \times 10^3 \text{ Hz}$$

$$E_n := e_{n_total} \sqrt{BW_n} = 2.266 \times 10^{-7} \text{ Vrms}$$

Total rms noise

$$E_{n_out} := G_{n1} \cdot G_{n2} \cdot E_n = 480.62 \times 10^{-6} \text{ Vrms}$$

Peak-to-peak output noise

$$V_{pp_out} := 6E_{n_out} = 2.884 \times 10^{-3} \text{ Vpp}$$


124



Step through the calculation again for the OPA211, substituting in for the noise and bandwidth parameters of that device.

Simulation Setup – With Filter

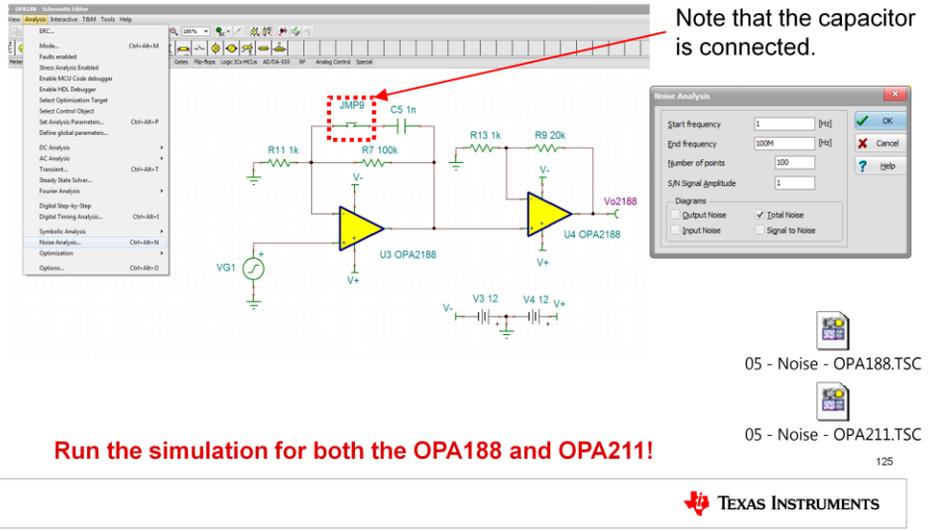Click **Analysis** → **Noise Analysis** to compute the total output noise. Run the noise analysis from 1Hz to 100MHz and select the **Total Noise** diagram. Make sure **JMP9** is closed so the filter capacitor **C5** is connected!



The screenshot shows a SPICE simulation environment with a circuit diagram and a Noise Analysis dialog box. The circuit diagram features two OPA2188 op-amp stages. The first stage, U3, is configured as a voltage follower. Its non-inverting input is connected to a voltage source VG1 through a 1k resistor (R11). The inverting input is connected to a feedback network consisting of a 100k resistor (R7) and a 1nF capacitor (C5) in parallel. A jumper labeled JMP9 is connected across the capacitor C5. The output of U3 is connected to the non-inverting input of the second stage, U4. The inverting input of U4 is connected to a feedback network consisting of a 1k resistor (R13) and a 20k resistor (R9) in parallel. The output of U4 is labeled Vo2188. The circuit also includes a 12V battery (V3) and another 12V battery (V4). The Noise Analysis dialog box is open, showing the following settings: Start frequency: 1 [Hz], End frequency: 100M [Hz], Number of points: 100, S/N Signal Amplitude: 1. The Diagrams section is checked for Total Noise, Input Noise, and Signal to Noise. The OK button is highlighted.

Note that the capacitor is connected.

Run the simulation for both the OPA188 and OPA211!

05 - Noise - OPA188.TSC
05 - Noise - OPA211.TSC


125

TEXAS INSTRUMENTS

Run another SPICE simulation analysis for the total output noise. This time, ensure that the filter capacitor jumper is closed so that the capacitor is connected! As before, select Analysis, followed by Noise Analysis. Make sure that “total noise” is selected, then run the analysis from 1Hz to 100MHz.

Remember, run the simulation for both the OPA188 and OPA211!

Simulation Results – With Filter

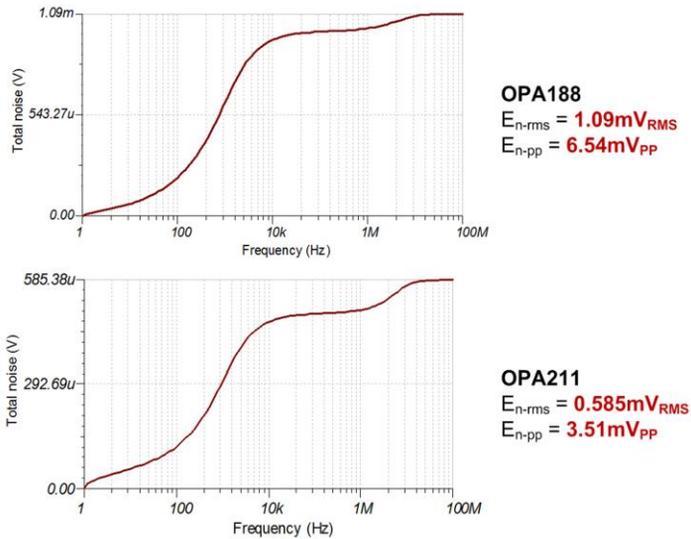


126



With the filter capacitor connected, the OPA188 circuit has a total noise of 1.09mVrms, or 6.54mVpp. The OPA211 circuit has a total noise of 0.585mVrms, or 3.51mVpp.

Test Board Setup – Jumpers

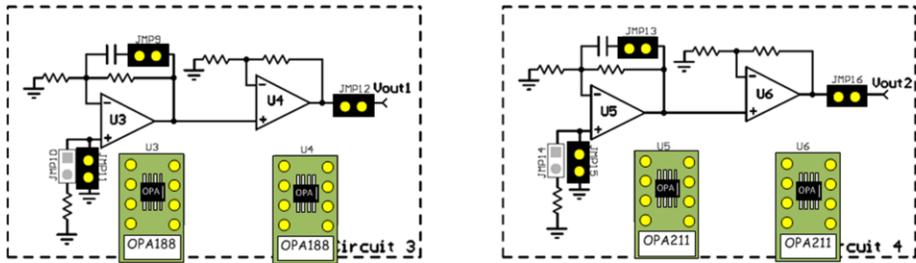

The only change. →
Can be "hot
plugged".

Jumper, Device	Description
JMP9, JMP13	Connect filter capacitor in Circuit 3 and Circuit 4
JMP11, JMP15	Connect VIN+ to GND
JMP12, JMP16	Connect Circuit 3 to Vout1, connect Circuit 4 to Vout2
U3, U4	Install OPA188
U5, U6	Install OPA211


127

 TEXAS INSTRUMENTS

The jumper settings on the test board must be modified before re-running the bench measurement. Simply install jumpers JMP9 and JMP13. All other jumpers and devices remain the same from the previous experiment.


Measurement Results – With Filter

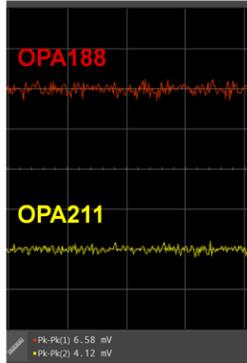1. Compare TINA-TI™ simulation results to measured and calculated results.



6.58mV_{PP}

4.12mV_{PP}

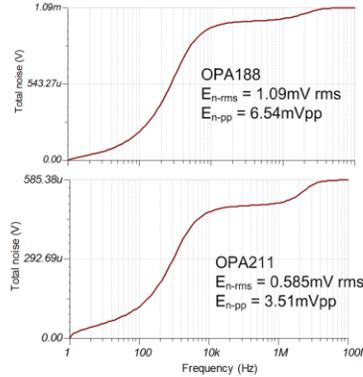

Device	Calculated Noise (RMS)	Simulated Noise (RMS)	Measured Noise (RMS)
OPA188	1mV _{RMS}	1.09mV _{RMS}	1.09mV _{RMS}
OPA211	0.48mV _{RMS}	0.585mV _{RMS}	0.69mV _{RMS}


Note: Measured RMS noise is determined using measured peak-to-peak noise divided by 6.

128



The expected output voltage noise results from the measurement with the filter are shown here. The OPA188 has a measured noise of 6.58mVpp, or 1.09mVrms, and the OPA211 has a measured noise of 4.12mVpp, or 0.69mVrms. Like before, the calculated, simulated, and measured results all match quite closely. The real question is: how much benefit did we get by adding the filter capacitor?

Noise Comparison – Filter vs. No Filter

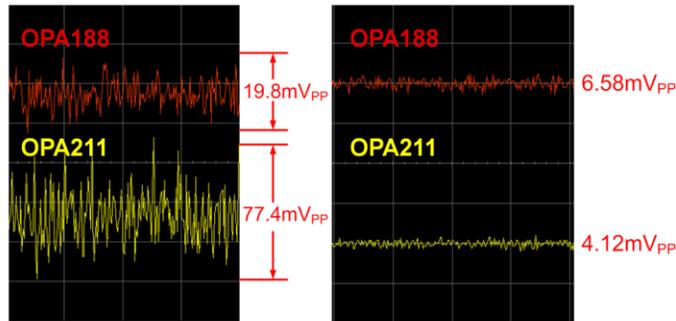

Device	Calculated (no filter)	Calculated (with filter)	Simulated (no filter)	Simulated (with filter)	Measured (no filter)	Measured (with filter)
OPA188	3.62mV _{RMS}	1mV _{RMS}	3.59mV _{RMS}	1.09mV _{RMS}	3.3mV _{RMS}	1.09mV _{RMS}
OPA211	10.72mV _{RMS}	0.48mV _{RMS}	10.75mV _{RMS}	0.59mV _{RMS}	12.9mV _{RMS}	0.69mV _{RMS}

OPA188 → 3x noise improvement!
OPA211 → 19x noise improvement!

129



This slide compares the noise performance of both the OPA188 and OPA211, with and without the filter. It should be clear just from the oscilloscope capture that the filter gave us a massive improvement in noise. If you compare the peak-to-peak noise values in the table, you can see that with the filter, we achieved a 3x improvement with the OPA188 and a 19x improvement with the OPA211!

You may wonder why we didn't see more of a reduction in noise with the OPA188. One key reason is that the gain-bandwidth product of the OPA188 at 2MHz is much lower than that of the OPA211 at 80MHz, so the closed-loop bandwidth of the OPA188 circuit is lower as well. When we added the filter and reduced the closed-loop bandwidth of both circuits to 1.6kHz, this was much more of a percentage reduction for the OPA211 than the OPA188. Therefore, the filter had a bigger effect for the OPA211 circuit. The OPA188 also has higher input voltage noise spectral density than the OPA211.

Stability – Lab
TI Precision Labs – Op Amps

Developed by Art Kay, Collin Wells, and Ian Williams

TIDesigns
PRECISION

130

 TEXAS INSTRUMENTS

Hello, and welcome to the presentation for the TI Precision Lab supplement for op amp stability. This lab will walk through detailed calculations, SPICE simulations, and real-world measurements that greatly help to reinforce the concepts established in the stability lecture.

Required/Recommended Equipment

- Calculation
 - Pencil and paper
 - **Recommended:** MathCAD, Excel, or similar
- Simulation
 - SPICE simulation software
 - **Recommended:** TINA-TI™
- Measurement
 - TI Precision Labs PCB from Texas Instruments
 - Oscilloscope
 - Function generator
 - Bode plotter
 - $\pm 15\text{V}$ power supply
 - **Recommended:** National Instruments VirtualBench™

The detailed calculation portion of this lab can be done by hand, but calculation tools such as MathCAD or Excel can help greatly.

The simulation exercises can be performed in any SPICE simulator, since Texas Instruments provides generic SPICE models of the op amps used in this lab. However, the simulations are most conveniently done in TINA-TI, which is a free SPICE simulator available from the Texas Instruments website. TINA simulation schematics are embedded in the presentation.

Finally, the real-world measurements are made using a printed circuit board, or PCB, provided by Texas Instruments. If you have access to standard lab equipment, you can make the necessary measurements with any oscilloscope, function generator, Bode plotter, and $\pm 15\text{V}$ power supply. However, we highly recommend the VirtualBench from National Instruments. The VirtualBench is an all-in-one test equipment solution which connects to a computer over USB or Wi-Fi and provides power supply rails, analog signal generator and oscilloscope channels, and a 5 ½ digit multimeter for convenient and accurate measurements. This lab is optimized for use with the VirtualBench.

Experiment 1

Buffer with Cap Load


132



In experiment 1, we'll determine the phase margin, and therefore the stability, of a buffer circuit which is being used to drive a large capacitive load. We'll determine the phase margin by observing the transient overshoot as well as the AC transfer characteristic.

Calculation – Capacitive Load

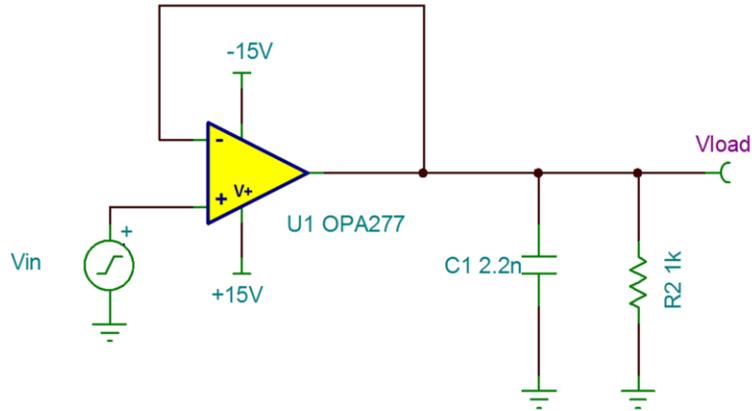Calculate the phase margin and percentage overshoot for the circuit shown below.




133

 TEXAS INSTRUMENTS

First, calculate the phase margin and percentage overshoot for the circuit shown here, using the techniques and equations given in the stability lecture. Use the plots given on the next slide.

Calculation – Capacitive Load

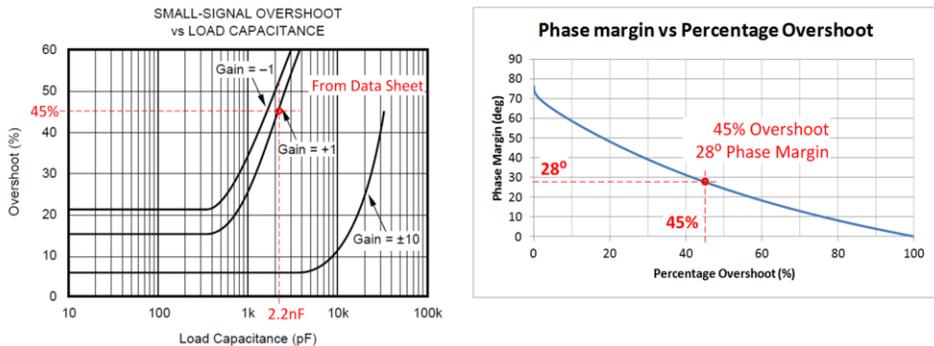

Answers	OPA277
Percent overshoot	45%
Phase margin	28°

134




This circuit uses the OPA277. In order to perform the calculations, you need to know the percent overshoot versus load capacitance for that device, shown on the top left. Then, use the plot on the right to determine the phase margin from that percentage overshoot.

Enter your answers in the table at the bottom of the slide. The solutions are already provided to allow you to check your work.

Simulation Setup – Overshoot

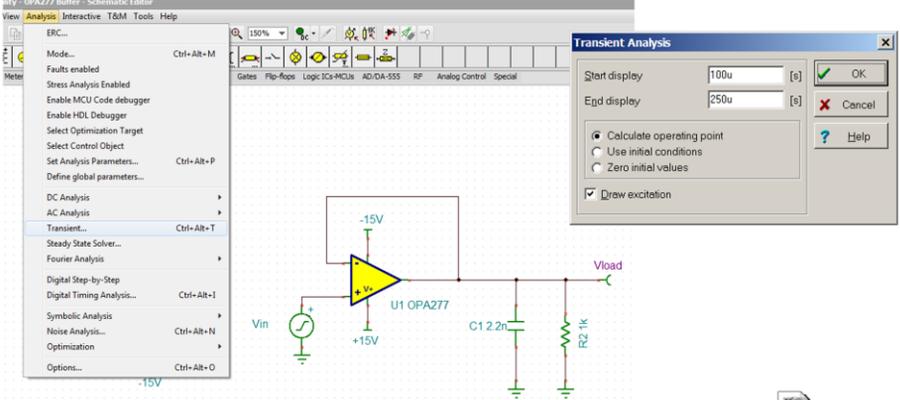Click **Analysis** → **Transient** to run a transient simulation showing overshoot.
Run the analysis from 100 μ s to 250 μ s. The input is a 20mVpk, 10kHz square wave.




The screenshot shows the TINA-TI Schematic Editor interface. On the left, the 'Analysis' menu is open, with 'Transient...' selected. The main workspace displays a circuit schematic for an OPA277 buffer. The op-amp (U1) is configured as a voltage follower. The non-inverting input (+) is connected to an AC voltage source labeled 'Vin'. The inverting input (-) is connected to the output. The op-amp is powered by a +15V supply and a -15V supply. A 2.2nF capacitor (C1) is connected between the output and the inverting input. A 1k Ω resistor is connected between the output and ground. A load resistor labeled 'Vload' is also connected to the output. A 'Transient Analysis' dialog box is open in the top right corner, showing 'Start display' set to 100 μ s and 'End display' set to 250 μ s. The 'Calculate operating point' option is selected, and 'Draw excitation' is checked. The file name '06 - Stability - OPA277 Buffer.TSC' and the number '135' are visible at the bottom of the window.

The next step is to run a SPICE simulation analysis for the transient overshoot.

The necessary TINA-TI simulation schematic is embedded in this slide set – simply double-click the icon to open it. To run the analysis, click **Analysis** → **Transient**, and run the analysis from 0ms to 150 μ s. The input is a 20mVpk, 10kHz square wave.


Simulation Results – Overshoot

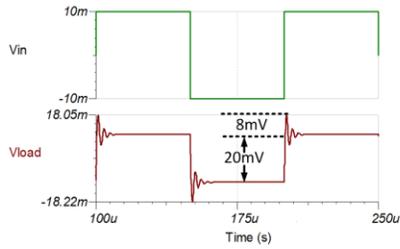

$$\text{Percentage_Overshoot} = \frac{\text{Overshoot}}{\text{Step_Size}} \cdot 100$$

$$\text{Percentage_Overshoot} = \frac{8\text{mV}}{20\text{mV}} \cdot 100 = 40\%$$

Phase Margin = 31°

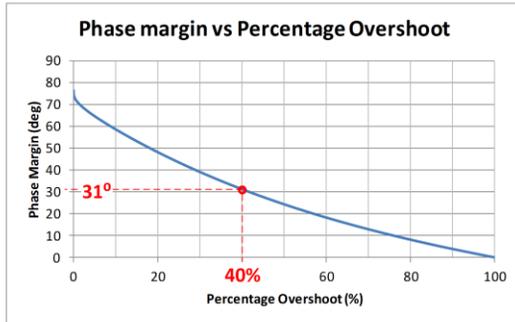

136



You should see a result similar to this. Use the simulated percentage overshoot of 55% to calculate the phase margin, which comes out to 21 degrees.

Simulation Setup – Bode Plot

Click **Analysis** → **AC Analysis** → **AC Transfer Characteristic** to generate the bode plot. Run the AC analysis from 10kHz to 10MHz.

06 - Stability - OPA277 Buffer.TSC


137

TEXAS INSTRUMENTS

Next, run a SPICE simulation analysis for the AC transfer characteristic. This will allow us to see the op amp's AC peaking, which is another indicator of phase margin.


Use the same TINA-TI simulation schematic as before. To run the analysis, click **Analysis** → **AC Analysis** → **AC Transfer Characteristic**. Run the analysis from 10kHz to 10MHz.

Simulation Results – Bode Plot

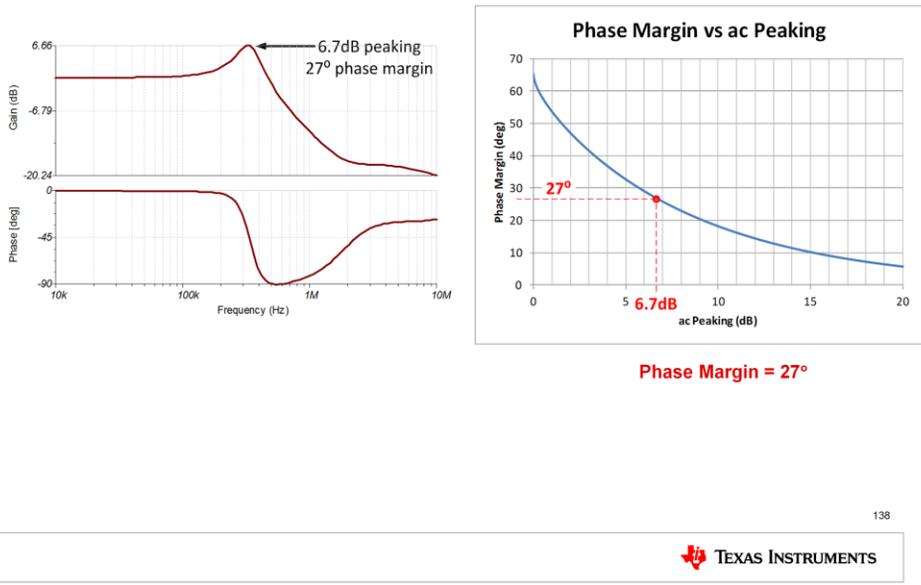

You should see a result similar to this. The 9dB of simulated AC peaking results in a phase margin of approximately 20 degrees.

Make All “Not Found” devices are closed

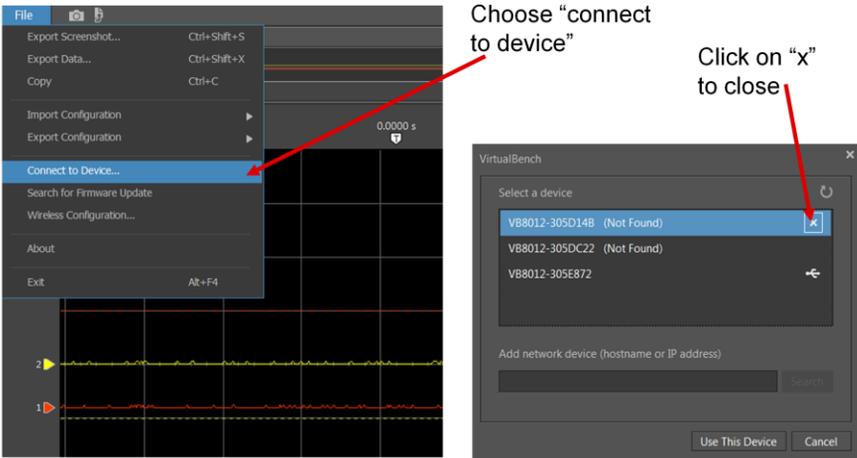

Choose “connect to device”

Click on “x” to close

File

- Export Screenshot... Ctrl+Shift+S
- Export Data... Ctrl+Shift+X
- Copy Ctrl+C
- Import Configuration
- Export Configuration
- Connect to Device...
- Search for Firmware Update
- Wireless Configuration...
- About
- Exit Alt+F4

0.0000 s

VirtualBench

Select a device

- VB8012-305D14B (Not Found)
- VB8012-305DC22 (Not Found)
- VB8012-305E872

Add network device (hostname or IP address)


Use This Device Cancel

TEXAS INSTRUMENTS

We will be using a new software package. To prevent problems, make sure that all “not found” devices are closed.

Disable Function Generator

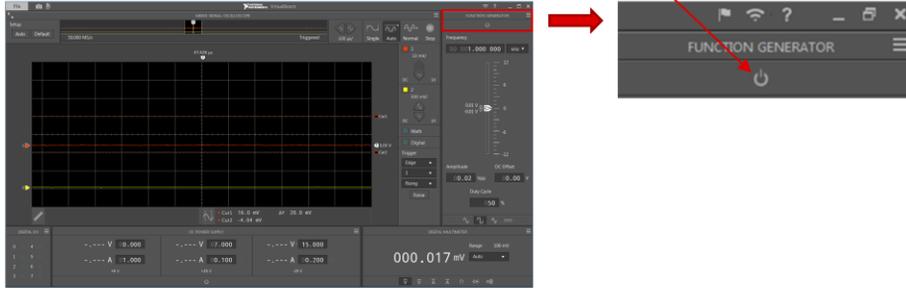Power button GRAY =
Function Generator OFF




140




Also make sure the Function Generator is OFF.

Disable DC Power Supply

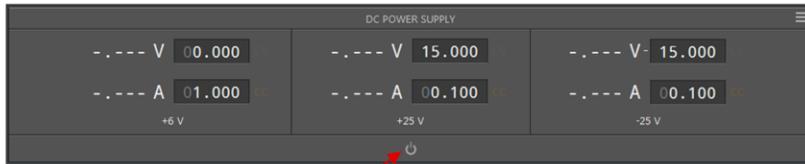

Power button GRAY = DC power supply OFF

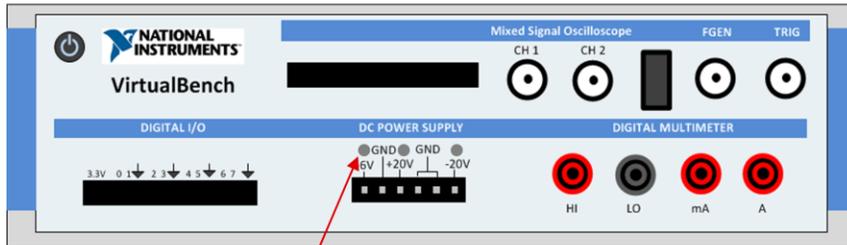


LEDs OFF = DC power supply OFF

141

 TEXAS INSTRUMENTS


Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

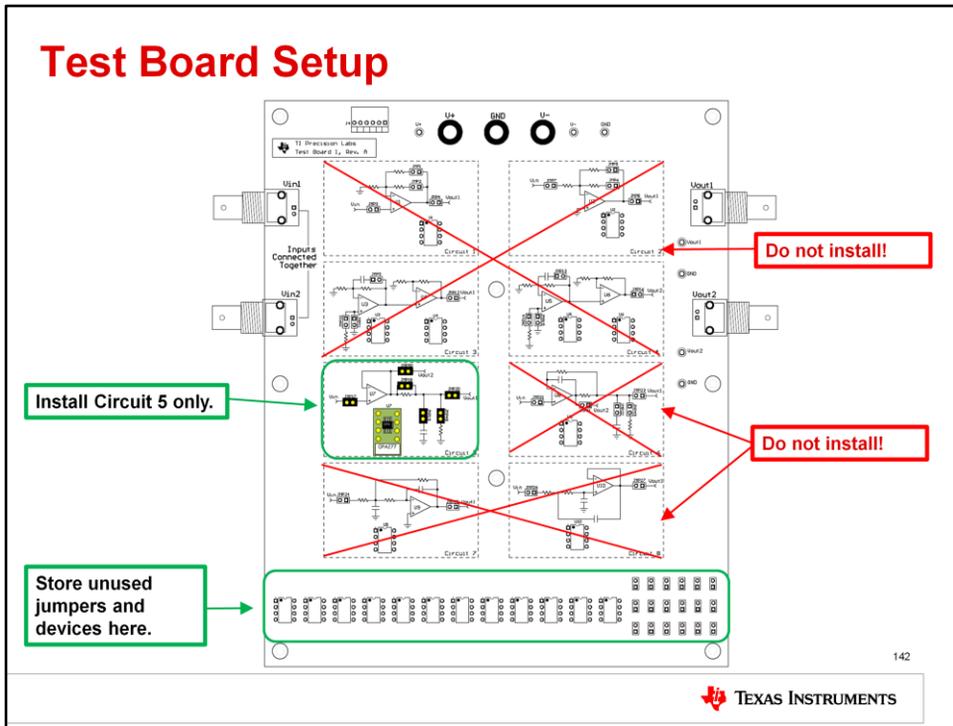

For the test board to function properly, it is important that you only install jumpers and devices in circuit 5. Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup – Jumpers

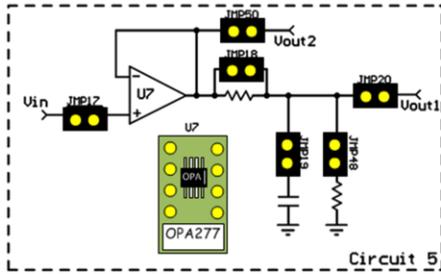

Jumper, Device	Description
JMP17	Connects input to U7
JMP18	Shorts isolation resistor. $R_{iso} = 0\Omega$
JMP19	Connects 2.2nF load capacitance
JMP20	Monitor output across load
JMP48	Connects 1k Ω load resistance
JMP50	Monitor directly at U7 output
U7	Install OPA277


143



To prepare the test board for the measurement, install the jumpers and devices on circuit 5 as shown here.

Install JMP17, JMP18, JMP19, JMP20, JMP48, and JMP50, as well as the OPA277 in socket U7.

Hardware Setup – Cables

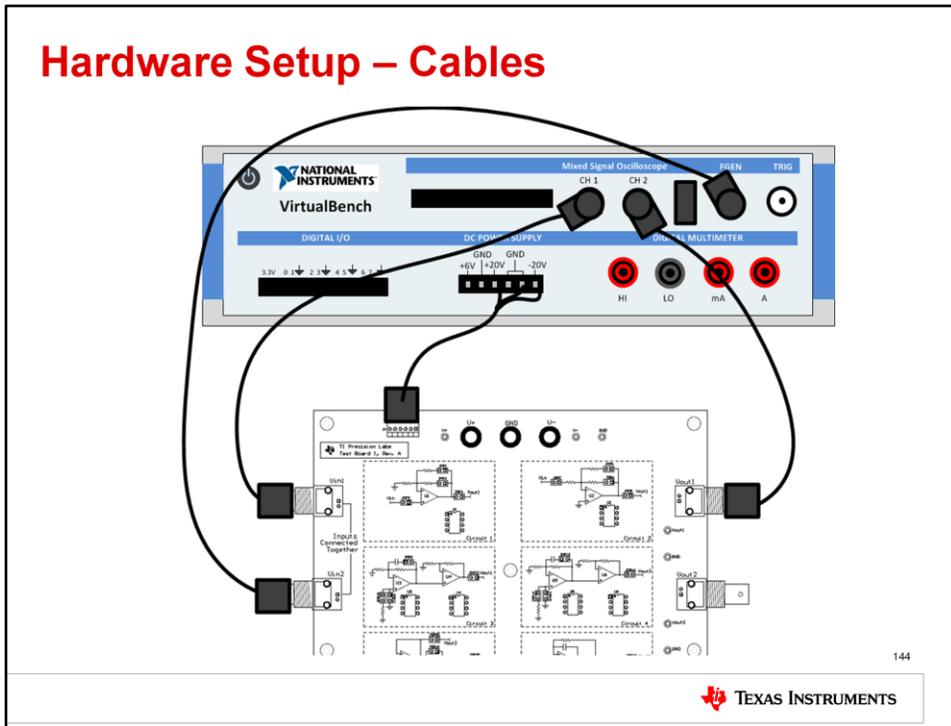


This slide gives the connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board.

Connect Vin1 on the test board to VirtualBench oscilloscope channel 1, and Vin2 on the test board to the VirtualBench FGEN. Connect Vout1 on the test board to VirtualBench oscilloscope channel 2.

Close VirtualBench Software

Click the 'X' to close

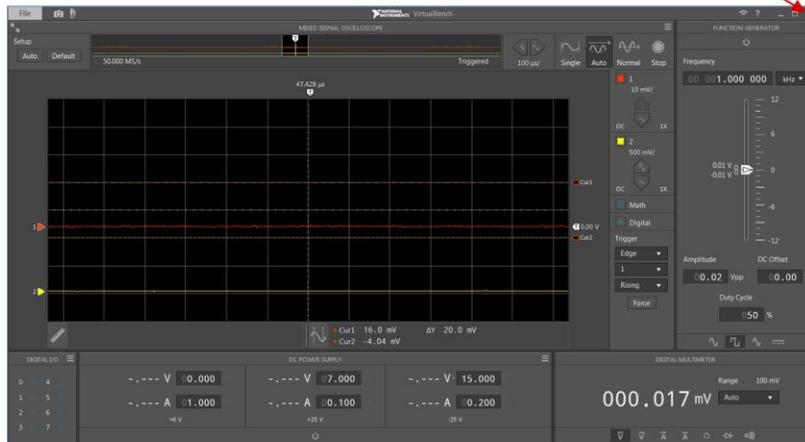


145



The VirtualBench software must be closed before continuing with the lab. Click the 'X' in the top-right corner of the software to close.

Open Bode Analyzer Software

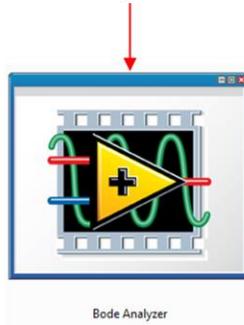Double-click icon on desktop to start **Bode Analyzer** software.



146

 TEXAS INSTRUMENTS

This lab requires additional Bode analyzer software. Install the software, then run it by double-clicking the Bode Analyzer icon on the desktop. You may also run the software by clicking Start → All Programs → Bode Analyzer → Bode Analyzer.

Instrument Setup – Bode Analyzer

The screenshot shows the Bode Analyzer configuration panel. The **Power Supply** section has a green power button and voltage/current settings for +6V, +25V, and -25V rails. The **FGEN** section shows an amplitude of 0.02V and a DC offset of 0V. The **Measurement** section shows a start frequency of 10k Hz, an end frequency of 10M Hz, 10 points to average, and 30 points per decade. A **Start** button is at the bottom. Annotations with red arrows point to the power button, the FGEN amplitude setting, the Start button, and the measurement settings. A smaller inset window shows the resulting Bode plot with magnitude and phase curves.

±15V , 0.100A power supply.
Press **GREEN** button to turn on power.

Amplitude = 0.02V
DC Offset = 0V

Start Frequency = 10kHz
End Frequency = 10MHz
No. of Points to Average = 10
No. of Points/Decade = 30

Press **Start** to run the analyzer

147



TEXAS INSTRUMENTS

In the configuration panel, set the power supply to $\pm 15\text{V}$, 0.1A. Press the green button to turn on the power.

Set the FGEN amplitude to 0.02V, and DC offset to 0V.

Set the start frequency to 10kHz and the end frequency to 10MHz. Set the number of points to average to 10, and the number of points per decade to 30. Press “Start” to run the Bode analyzer.

Measured AC Peaking – Bode Analyzer

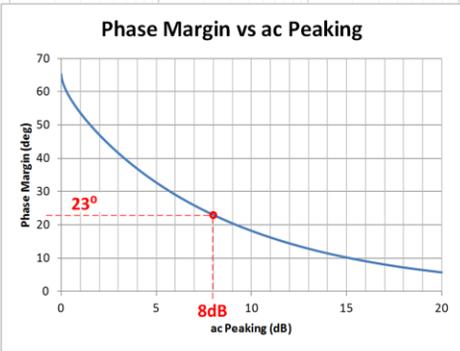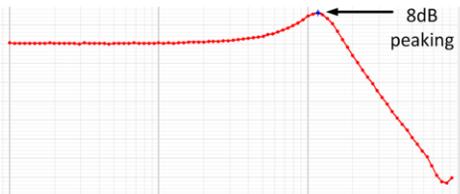


Answers	OPA277
AC Peaking	8dB
Phase margin	23°

148




You should see a result similar to this. Enable the cursor, then drag the cursor to the maximum value to measure the AC peaking. In this measurement, AC peaking of 8dB resulted in a phase margin of 23 degrees. Your results may vary slightly.

Reset Software

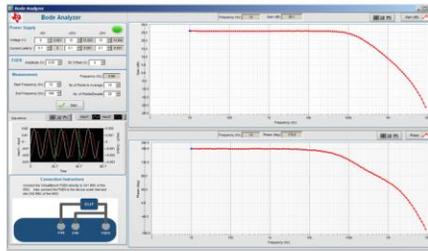

1. Close the Bode Analyzer software

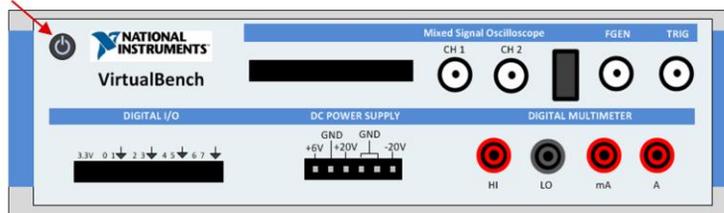
2. Cycle power to restart VirtualBench software



TEXAS INSTRUMENTS

The bandwidth lab is now complete. Before continuing to the next lab, you must reset the software. First, close the Bode Analyzer software by clicking the 'X' in the top-right corner. Next, cycle power on the VirtualBench by turning power off and on. This will restart the VirtualBench software.

VirtualBench™ Instrument Setup

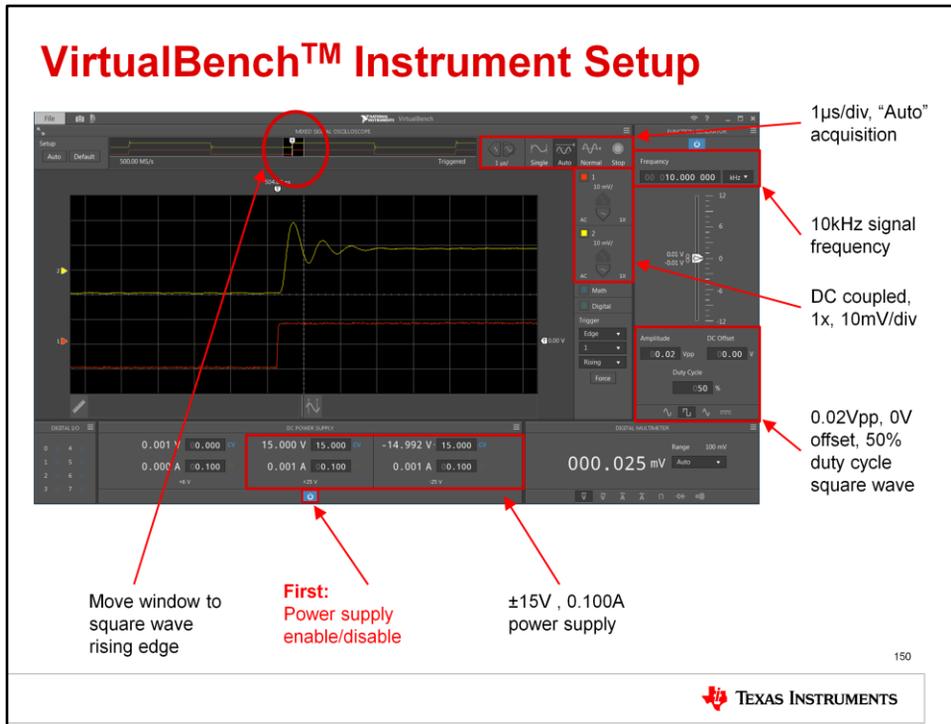

Next apply power to the National Instruments VirtualBench and connect it to your computer with a USB cable. The hardware should be detected as a virtual CD drive, and you can run the VirtualBench software directly from the drive. Once the software opens, configure the software as follows:


Set the time scale to 1µs per division, with the acquisition mode set to "Auto." Enable channels 1 and 2 on the oscilloscope, and set them to 1x, DC-coupled mode, 10mV/div. Enable the function generator and setup the signal as follows:

10kHz frequency, 20mVpp, 0V offset, 50% duty cycle square wave.

Set the +25V power supply to +15V, 0.100A. Set the -25V power supply to -15V, 0.100A. Press the power button to turn on the power supply rails.


Move the display window to the rising edge of the square wave. This allows you to observe the overshoot and ringing of the op amp output.

Measurement Results – Overshoot

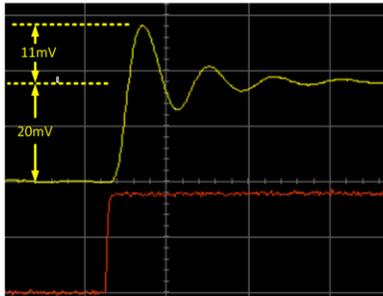

$$\text{Percentage_Overshoot} = \frac{\text{Overshoot}}{\text{Step_Size}} \cdot 100$$
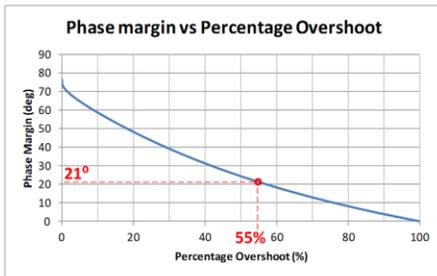
$$\text{Percentage_Overshoot} = \frac{11\text{mV}}{20\text{mV}} \cdot 100 = 55\%$$



Answers	OPA277
Percent overshoot	55%
Phase margin	21°

151

 TEXAS INSTRUMENTS

Use cursors to measure the amount of overshoot. The expected measurement results are shown here. The measured overshoot of 55% results in a phase margin of 21 degrees. Your results may vary slightly.

Results Comparison

1. Compare the phase margin results from calculations, transient and AC response simulations, and transient and AC response measurements.

Test	Phase Margin
Calculated from data sheet	28°
Simulated from transient overshoot	31°
Simulated from AC peaking	27°
Measured from transient overshoot	21°
Measured from AC peaking	23°

152



Now, compare the phase margin results from your hand calculations, transient and AC response simulations, and transient and AC response measurements. While there is some slight variation to the results, the phase margin values compare very well at approximately 23 degrees.

Experiment 2


Stabilizing with R_{ISO}

153



In experiment 2, we'll use an isolation resistor to increase the phase margin of the circuit from Experiment 1 and therefore improve its stability.


Open Loop Simulation – Phase Margin

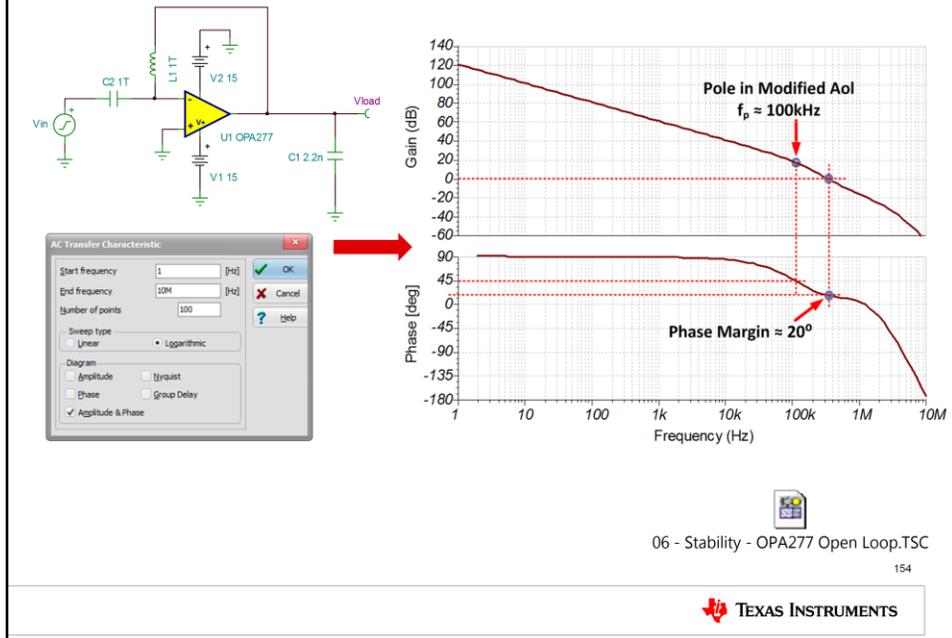

To determine the value of isolation resistor R_{iso} , we must first know the open-loop AC response of the circuit. Here we show the TINA-TI simulation schematic and AC response results, which you can verify using the embedded file.

To measure the phase margin, find the frequency where the gain measures 0dB. Then, measure the phase at that same frequency, which in this example is 20 degrees.

Calculation – R_{ISO}

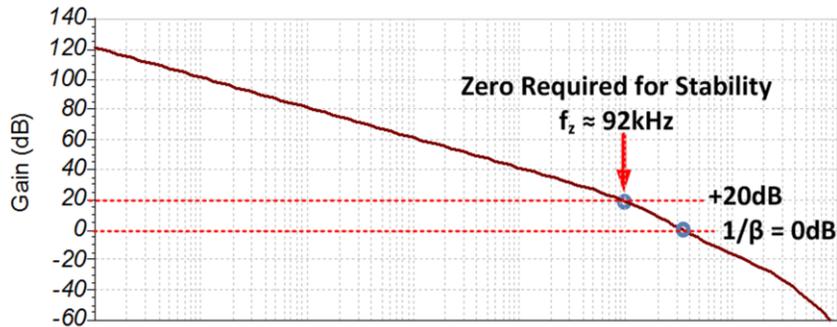

$$R_{iso} = \frac{1}{2 \cdot \pi \cdot f_z \cdot C_L} = \frac{1}{2 \cdot \pi \cdot 92\text{kHz} \cdot 2.2\text{nF}} = 786 \Omega$$

$R_{iso} = 787 \Omega$ (nearest standard value)

155



For best results, R_{iso} should create a zero in the loop response 20dB greater than the frequency where the open-loop gain intersects with the closed-loop gain. This circuit is a buffer with a closed-loop gain of 0dB, so the zero should occur at 20dB. The open-loop gain is equal to 20dB at 92kHz. Use this value and the load capacitance to calculate R_{iso} , which is 786 ohms in this example. 787 ohms is the nearest standard value resistance.

Simulation Setup – R_{ISO} Overshoot

Click **Analysis** → **Transient** to run a transient simulation, showing overshoot.
Run the analysis from 100 μ s to 250 μ s. The input is a 20mVpk, 10kHz square wave.



06 - Stability - OPA277 Riso.TSC

156

TEXAS INSTRUMENTS

Let's now simulate the transient overshoot with Riso included in the circuit. As before, click **Analysis** → **Transient** to run the simulation. Run the analysis from 0ms to 150 μ s. The input is a 20mVpk, 10kHz square wave.

Simulation Results – R_{ISO} Overshoot

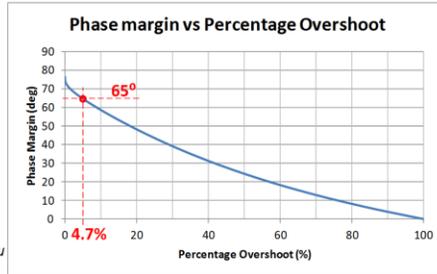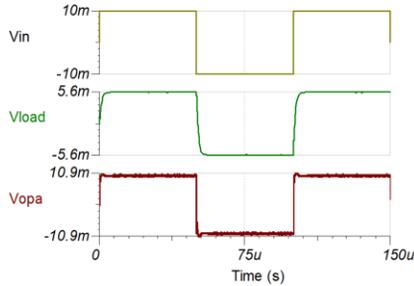

$$\text{Percentage_Overshoot} = \frac{\text{Overshoot}}{\text{Step_Size}} \cdot 100$$

$$\text{Percentage_Overshoot} = \frac{0.93\text{mV}}{20\text{mV}} \cdot 100 = 4.7\%$$


Phase Margin = 65°

157



You should see results similar to this. With R_{ISO} added to the circuit, the overshoot was reduced to only 4.7%. This results in a phase margin of 65 degrees, indicating a stable circuit.

Test Board Setup – Jumpers

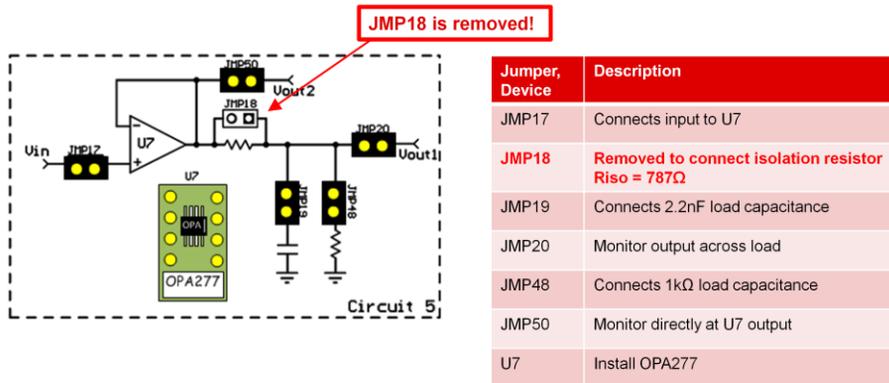


158



Let's now re-run the overshoot measurement, this time with Riso. The jumper setup is almost the same. The only change is to remove JMP18, which connects the isolation resistor of 787 ohms.

Hardware Setup – Cables

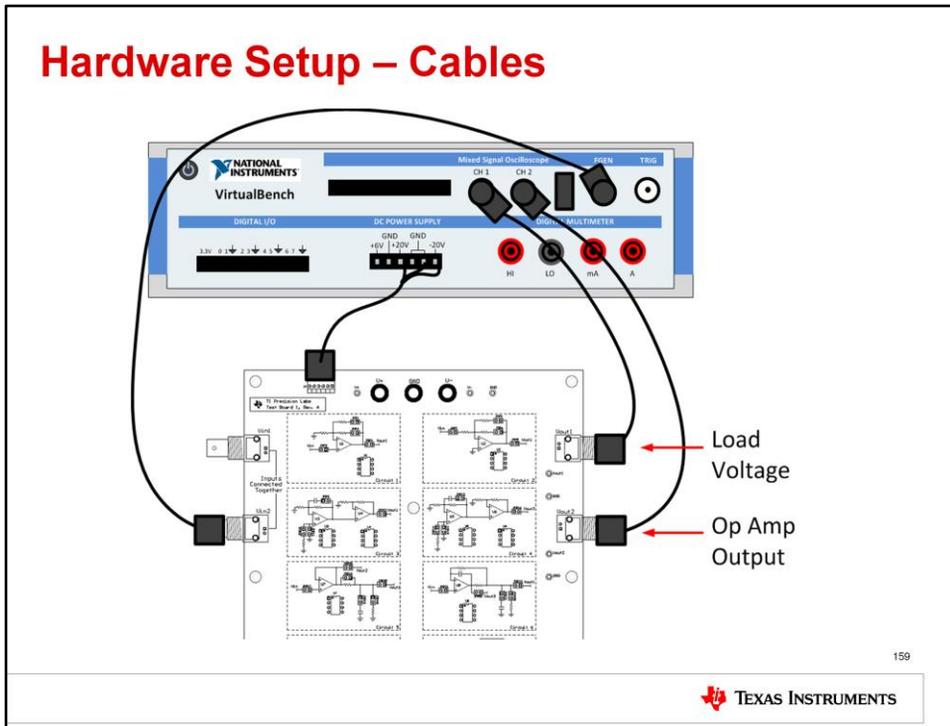

This slide gives the new connection diagram between the TI Precision Labs test board and the National Instruments VirtualBench. Connect the provided power cable to the DC power supply of the Virtual Bench and power connector J4 on the test board.

Connect Vin2 on the test board to the VirtualBench FGEN. Connect Vout1 on the test board to VirtualBench oscilloscope channel 1 to measure the load voltage, and connect Vout2 on the test board to VirtualBench oscilloscope channel 2 to measure the unloaded op amp output voltage.

VirtualBench™ Instrument Setup

The screenshot displays the VirtualBench software interface. The main display shows a square wave signal on a grid. The time scale is set to 500.00 nS. The signal amplitude is 0.02 Vpp and the frequency is 10.000 kHz. The signal is DC coupled with a 10mV/div scale. The duty cycle is 50%. The digital multimeter shows a reading of 000.034 mV. The DC power supply is set to 15.001 V and 0.001 A. The digital multimeter is set to 100 mV range.

Annotations with red arrows point to the following settings:


- 5µs/div, "Auto" acquisition
- 10kHz signal frequency
- DC coupled, 1x, 10mV/div
- 0.02Vpp, 0V offset, 50% duty cycle square wave

160

TEXAS INSTRUMENTS

The VirtualBench setup is almost the same as before. Only change the time scale to 5µs/div. All other settings must remain the same.

Measurement Results – R_{ISO} Overshoot

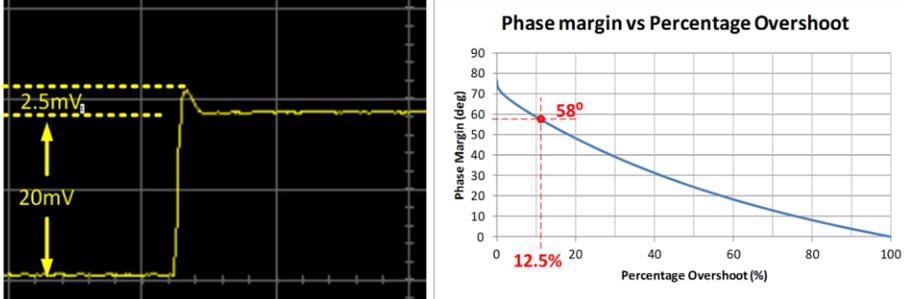

$$\text{Percentage_Overshoot} = \frac{\text{Overshoot}}{\text{Step_Size}} \cdot 100$$

$$\text{Percentage_Overshoot} = \frac{2.5\text{mV}}{20\text{mV}} \cdot 100 = 12.5\%$$


Phase Margin = 58°

161

 TEXAS INSTRUMENTS

Use cursors to measure the amount of overshoot. You should see results similar to this. With Riso, the measured unloaded output overshoot was reduced to 12.5%, resulting in a phase margin of approximately 58 degrees which indicates a stable circuit.

Measurement Setup – Loading Effects

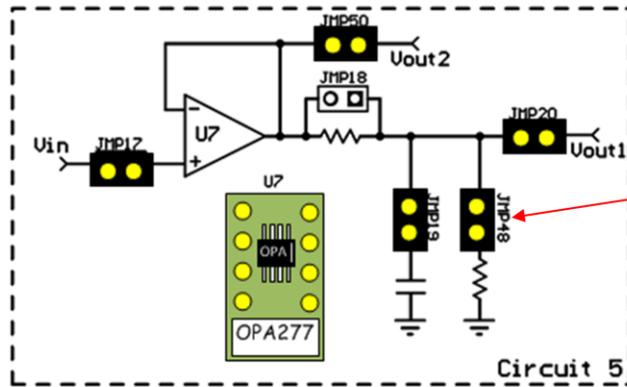


Measure transient response with JMP48 installed and removed.

162

 TEXAS INSTRUMENTS

As an additional experiment, measure the transient response again with JMP48 installed and removed. This will connect and disconnect the 1k load resistor from the circuit.

Measurement Results – Loading Effects

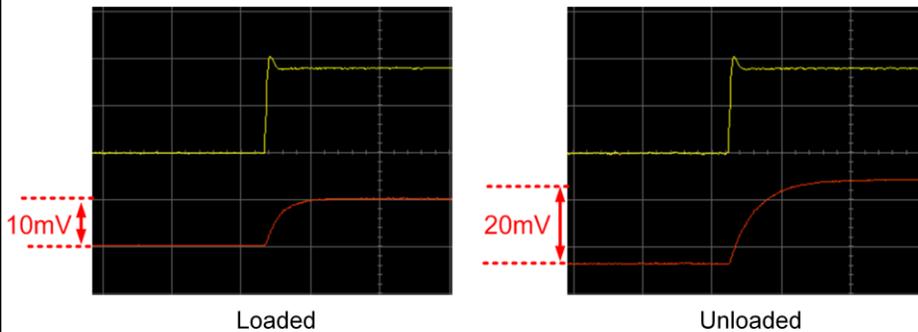

R_{ISO} can cause significant attenuation when under load!

163

 TEXAS INSTRUMENTS

As you can see, the load voltage changes dramatically if the circuit is loaded or unloaded! In fact, when loaded, the circuit with R_{ISO} shows attenuation of approximately 50%! This is simply due to the voltage divider effect of R_{ISO} and the load resistance.

Experiment 3

Dual Feedback

164



For the final experiment, we'll analyze a circuit which uses Riso as well as a dual feedback network to achieve stability as well as output voltage accuracy.

Calculation – Dual Feedback


$$R_F \geq 100 \times R_{iso} = 100 \times 787\Omega = 78.7k\Omega \quad \text{Choose } R_F$$

$$\frac{5 \times R_{iso} \times C_L}{R_F} \leq C_F \leq \frac{10 \times R_{iso} \times C_L}{R_F} \quad \text{Find the range of } C_F$$

$$110pF \leq C_F \leq 220pF$$

$$C_F = 150pF$$

Select standard value of C_F

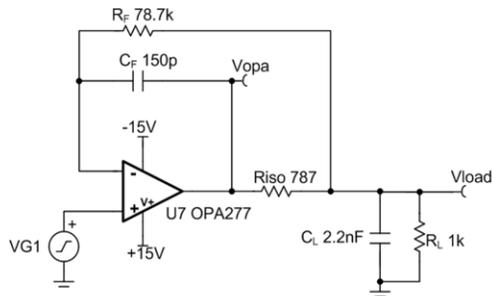

165

 TEXAS INSTRUMENTS

To select the components of the dual feedback network, use the equations given on this slide. For this example, R_F was chosen to be 78.7k, and C_F was chosen to be 150pF.

Simulation Setup – Dual Feedback


Click **Analysis** → **Transient** to run a transient simulation showing overshoot.
Run the analysis from 0ms to 2ms. The input is a 1Vpk, 1kHz square wave.

The screenshot displays the TINA-TI schematic editor for a circuit titled "OPA277 Dual Feedback". The circuit includes an OPA277 operational amplifier (U1) configured with a dual feedback network. The non-inverting input (+) is connected to a +15V supply. The inverting input (-) is connected to a network consisting of a 78.7k resistor (R4) and a 150pF capacitor (C4) in parallel, which is then connected to the output (Vopa). The output (Vopa) is also connected to a 787 resistor (Riso) in series with a 2.2nF capacitor (C1) and a 1k resistor (R2) in parallel, which is connected to a load (Vload). The op-amp is powered by a +15V supply and a -15V supply. A square wave input (Vin) is applied to the non-inverting input. The "Transient Analysis" dialog box is open, showing the start display at 0s and end display at 2ms. The "Calculate operating point" option is selected, and "Draw excitation" is checked. The file name "06 - Stability - OPA277 Dual Feedback.TSC" and the page number "166" are visible at the bottom.

Next, run a SPICE simulation analysis for the transient overshoot with dual feedback.

The necessary TINA-TI simulation schematic is embedded in this slide set – simply double-click the icon to open it. To run the analysis, click **Analysis** → **Transient**, and run the analysis from 0ms to 2ms. The input is a 1Vpk, 1kHz square wave.

Simulation Results – Dual Feedback

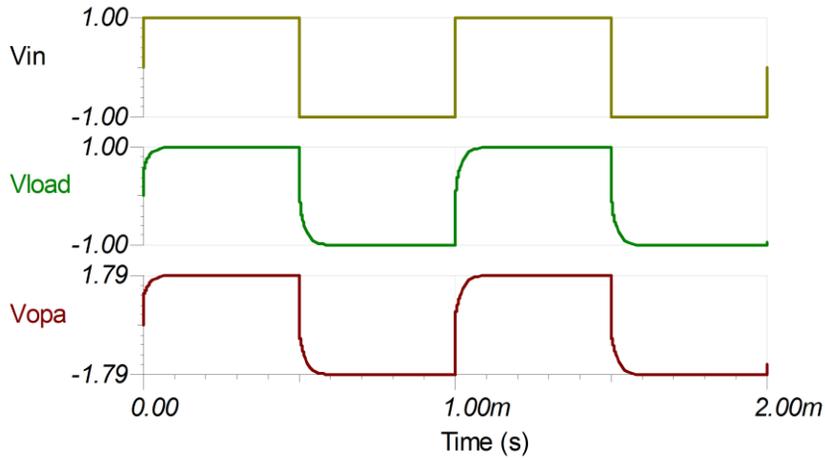


167



You should see results similar to this. As you can observe, in this configuration the loaded output voltage matches very well with the input. To achieve this, the unloaded output voltage V_{opa} must increase to compensate for the attenuation caused by R_{iso} and the load resistance.

Disable Function Generator

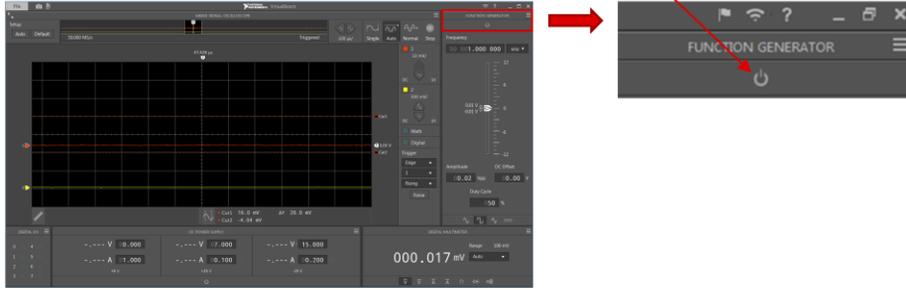Power button GRAY =
Function Generator OFF




168




Also make sure the Function Generator is OFF.

Disable DC Power Supply

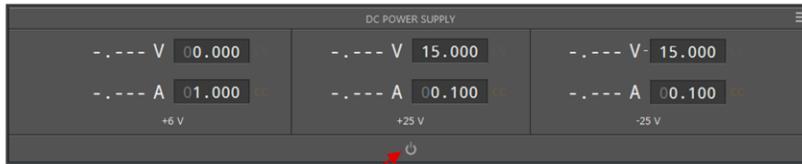

Power button GRAY = DC power supply OFF

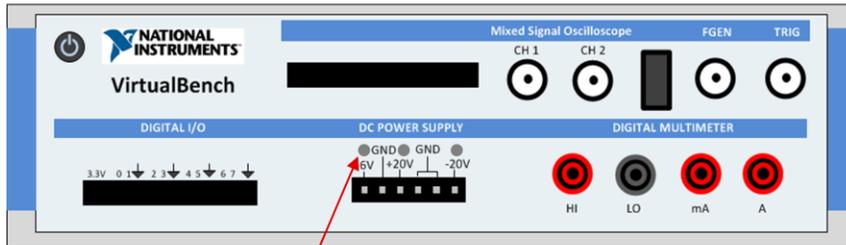


LEDs OFF = DC power supply OFF

169

 TEXAS INSTRUMENTS


Make sure to disable the DC power supply before setting up the test PCB! In the VirtualBench software, click the power button in the DC Power Supply area to turn off the power. Check the front panel of the VirtualBench unit to make sure the LEDs are OFF!

Test Board Setup

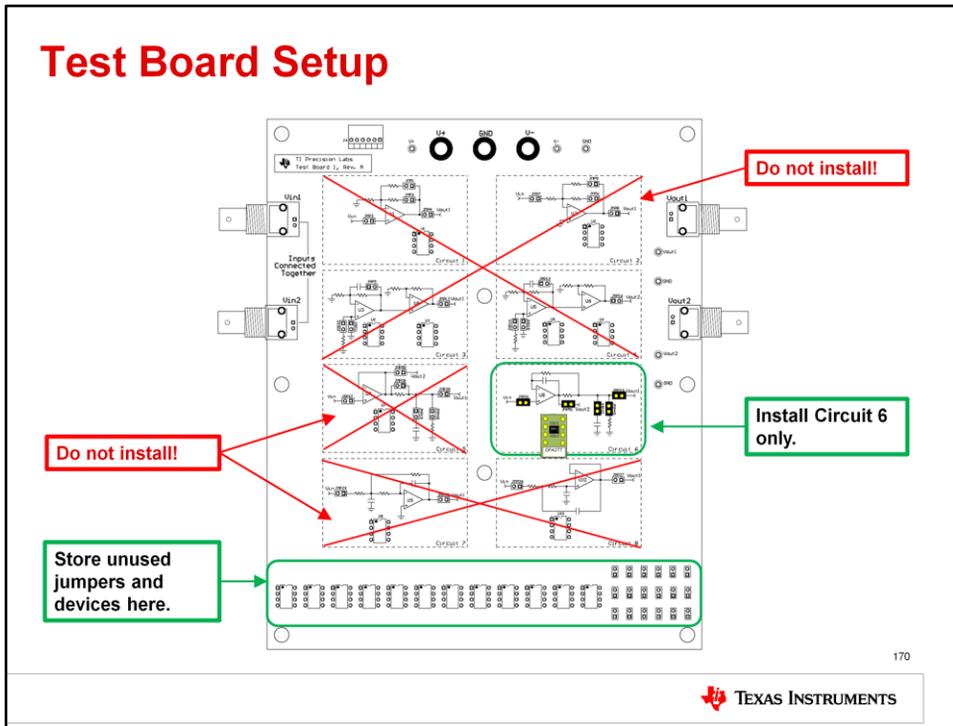

For the test board to function properly, it is important that you only install jumpers and devices in circuit 6! Do not install any jumpers or devices in any other circuits on the PCB! Remove any jumpers or devices from the unused circuits and store them in the storage area at the bottom of the test board.

Test Board Setup – Jumpers

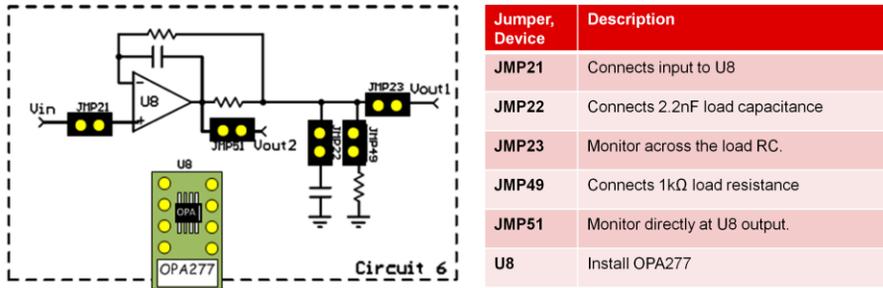

171



To prepare the test board for the measurement, install the jumpers and devices on circuit 6 as shown here.

Install JMP21, JMP22, JMP23, JMP49, and JMP51. Install the OPA277 in socket U8.

VirtualBench™ Instrument Setup


The screenshot displays the VirtualBench software interface. The main window shows a waveform with a time scale of 100 µs/div. The waveform is a square wave with an amplitude of 0.02 Vpp and a 50% duty cycle. The frequency is set to 1 kHz. The coupling is DC, and the vertical scale is 10 mV/div. The power supply settings are shown at the bottom, with a voltage of ±15 V and a current of 0.100 A. The digital multimeter shows a reading of 000.023 mV.

Annotations with red arrows point to the following settings:

- 100µs/div, "Auto" acquisition
- 1kHz signal frequency
- DC coupled, 1x, 10mV/div
- 0.02Vpp, 0V offset, 50% duty cycle square wave
- ±15V, 0.100A power supply
- First: Power supply enable/disable

The VirtualBench setup is almost the same as before. Only change the time scale to 100µs/div. All other settings must remain the same.

Measurement Results – Dual Feedback

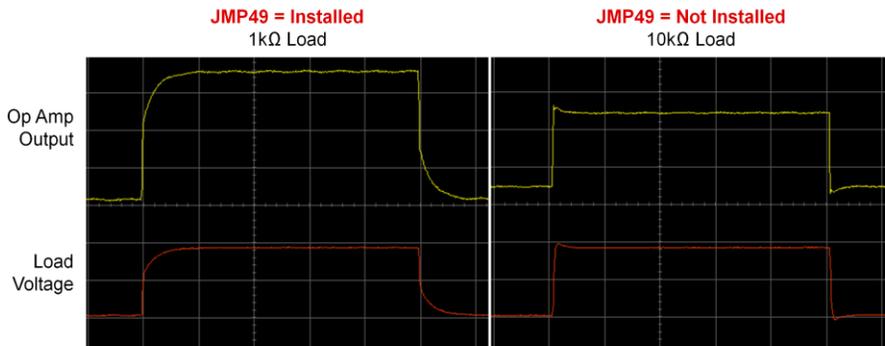

Dual feedback compensates for attenuation from R_{ISO} by increasing the op amp output voltage!

173

 TEXAS INSTRUMENTS

You should see results similar to this. As you can see, the load voltage remains accurate, even with changing load, due to the compensation provided by the dual-feedback network. The unloaded op-amp output voltage must increase as the load resistance decreases to minimize the output voltage divider effect.

Thanks for your time!

174



That concludes the lab – thank you for your time!

Updates

- Changed order of stability lab. Do body plot first to minimize resetting of equipment
- Eliminated redundant hardware setup in noise part 2
- Added animation to IO limit, BW, and Slew Rate hand calculation area
- Corrected slew rate calculation to be 0.8V/us
- Corrected amplifier name in slew rate calculation

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com