# Application Brief Simplify the Design of Isolated CAN with Selective Wake ECUs

### Neel Seshan

In the past, power train and body electronics subsystems in internal combustion engine vehicles used only 12-V battery and hence non-isolated controller area network (CAN) devices were sufficient for invehicle networking. But with the advent of hybrid electric vehicles (HEV) and electric vehicles (EV), more and more non-isolated CAN nodes in these subsystems are going the isolated way.

Depending on the electronic control unit (ECU), signal isolation requirements may vary. Non-isolated CAN may suffice for some while isolated CAN could be necessary for the others. An example of isolated CAN usage is the belt starter generator shown in Figure 1 for a HEV where the micro-controller on the high-voltage side needs to communicate with the 12-V side using CAN communication with isolator providing the protection of the LV side from the HV side.


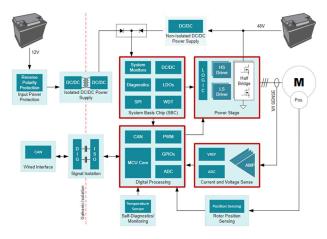


Figure 1. Belt Starter Generator Sub-system

The isolated CAN requirements also differ from system to system. Isolated CAN transceivers such as ISO1042-Q1 meet the requirements of systems that have isolated power supply on both sides of the isolator continuously present. This may be the case in systems like power train where the CAN transceiver needs to be continuously on to monitor safety critical functions and pass this information to the microcontroller. Since the microcontroller (MCU) and the isolated CAN transceiver are on continuously, this leads to increased power consumption.

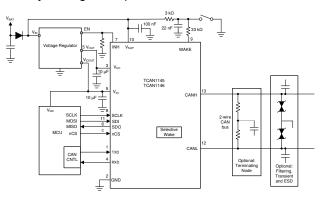

To reduce the overall power consumption in the car, it can be beneficial to turn off the CAN transceiver and the micro-controller not monitoring safety critical signals. Non-isolated CAN transceivers with wake up such as the TCAN1043-Q1 and TCAN1144-Q1 allow for all the CAN transceivers to wake up at the same time while CAN transceivers that support partial networking such as the TCAN1146-Q1, as shown in Figure 2, allow for a single CAN node to wake up thereby saving more power.




 


Figure 3 shows the implementation of the CAN transceiver with selective wake up in an isolated CAN system. To implement the functionality of CAN with wake up or partial networking in an isolated CAN subsystem would require the isolator to have enough channels for communication between the microcontroller and the CAN transceiver.

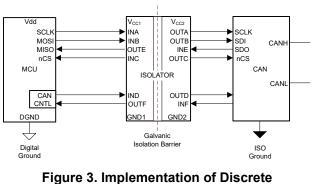

Isolated CAN Solution

1

It is evident from Figure 3 that four channels of isolation are needed for SCLK,SDI, nCS, and TXD signals from MCU to the CAN device while two channels are required for the SDO and RXD signal from CAN transceiver to the MCU. The digital isolator ISO7762-Q1 meets the requirements for the number of channels. Another concern with CAN systems is the timing specifications, namely  $t_{LOOP}$  and  $t_{BIT}$  which need to be compliant with the ISO 11898-2:2016 standard.

Table 1 shows these specifications for the TCAN1146-Q1 over the operating temperature range while Table2 provides the timing specifications of the isolatorISO7762-Q1 over the same temperature range.

	ISO 11898-2:2016		TCAN1146-Q1	
	MIN	MAX	MIN	MAX
t <sub>LOOP</sub>		255 ns		215 ns
t <sub>BIT(BUS)</sub> 2 Mbps CAN FD	435 ns	530 ns	440 ns	525 ns
t <sub>BIT(BUS)</sub> 5 Mbps CAN FD	155 ns	210 ns	160 ns	205 ns
t <sub>BIT(RXD)</sub> 2 Mbps CAN FD	400 ns	550 ns	410 ns	540 ns
t <sub>BIT(RXD)</sub> 5 Mbps CAN FD	120 ns	220 ns	130 ns	210 ns

#### Table 2. Digital Isolator Timing Specifications


		ISO7762-Q1	
		MIN	MAX
t <sub>PLH</sub> , t <sub>PHL</sub>	Propagation delay time	6ns	16 ns
PWD	Pulse width distortion  t <sub>PHL</sub> – t <sub>PLH</sub>		4.9 ns

The resulting timing specifications of the discrete isolator and CAN transceiver are shown in Table 3. It is evident that the discrete solution of ISO7762-Q1 and TCAN1146-Q1 meets the ISO 11898-2:2016 standard up to CAN Flexible Data Rate (FD) speed for 5 Mbps.

Another point to consider while adding the isolator to the systems is the need for the isolated power supply to power the secondary side of the isolator and the microcontroller. A simplified schematic is shown in Figure 4, where the transformer driver SN6505A-Q1 along with an external transformer provides the secondary voltage Viso that is used to power up the secondary side of the isolator as well as the MCU.

The High voltage supply pin of the CAN transceiver (VSUP) is supplied by the battery voltage of 12V that is always present. The power supply of the transformer driver and the 5-V CAN supply voltage (Vcc) are obtained from the LDO that steps the voltage from the battery voltage to 5 V. The enable pin of the LDO is controlled by the inhibit pin (INH)

of the CAN transceiver. In sleep mode, the INH pin is off, going into a high-Z state, thereby disabling the LDO. This allows the node to be placed into the lowest power state with the Isolator, isolated power supply and MCU off. When the INH pin switches high in the wake up mode, the LDO gets enabled and it turns on the isolator, the isolated power supply and MCU, thereby preparing the system to be ready for whatever mode (Normal, Standby, or Listen) the CAN transceiver decided to enter.

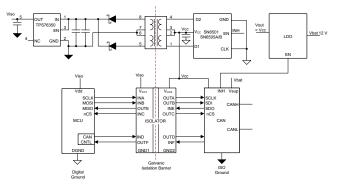

#### Figure 4. Isolated CAN with Wake Up System

In conclusion, discrete implementation of digital isolator along with a suitable CAN transceiver with selective wake features can ensure the low power needs of such systems coupled with the safety feature of isolated systems. Isolation does add complexity to the system design when it comes to the system timing performance and isolated power supply considerations. The ISO7762-Q1 and TCAN1146-Q1 along with an isolated power supply meet the timing and power requirements of isolated CAN FD systems up to 5 Mbps.

Table 3. Discrete Isolated CAN Timing			
Specifications			

	ISO 11898-2:2016		ISO7762-Q1 + TCAN1146-Q1				
	MIN	MAX	MIN	MAX			
t <sub>LOOP</sub>		255 ns		247 ns			
t <sub>BIT(BUS)</sub> 2 Mbps CAN FD	435 ns	530 ns	435.1 ns	529.9 ns			
t <sub>BIT(BUS)</sub> 5 Mbps CAN FD	155 ns	210 ns	160 ns	205 ns			
t <sub>BIT(RXD)</sub> 2 Mbps CAN FD	400 ns	550 ns	400.2 ns	549.8 ns			
t <sub>BIT(RXD)</sub> 5 Mbps CAN FD	120 ns	220 ns	130 ns	210 ns			

2

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated