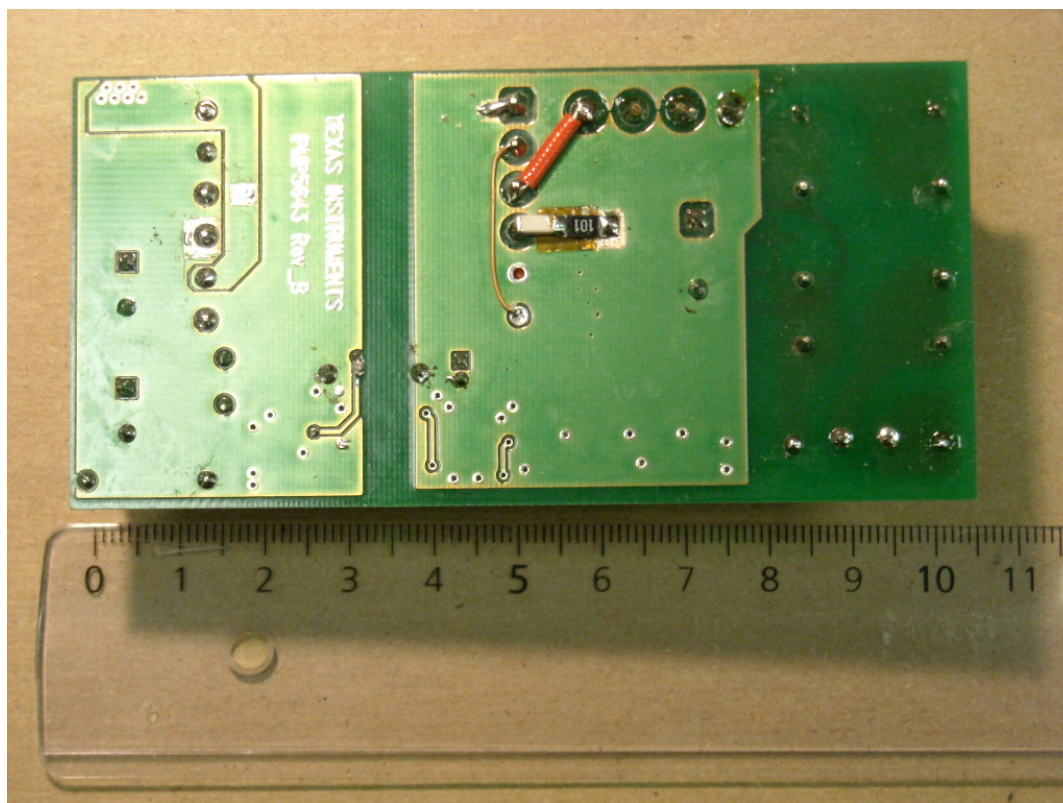
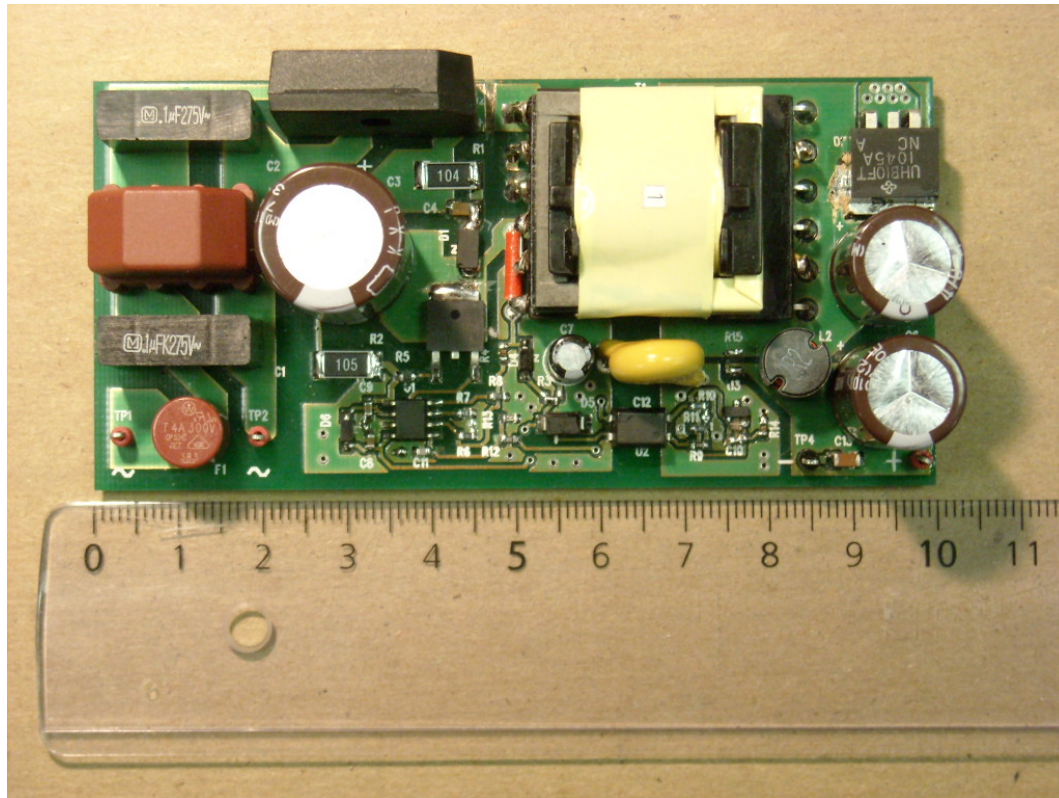


PHOTO OF THE PROTOTYPE:


1 Startup

The input AC voltage, input current and output voltage behavior at startup is shown in the images below. The input voltage was set to 115Vac, 60Hz and 230Vac, 50Hz. The output loaded with a 1A load for the first two pictures and unloaded for the last one.


Ch.4: Input voltage (100V/div, 10ms/div), Ch.1: Output voltage (10V/div)

Ch.3: Input current (2A/div)

Vin = 115Vac, 60Hz, Iout = 1A;

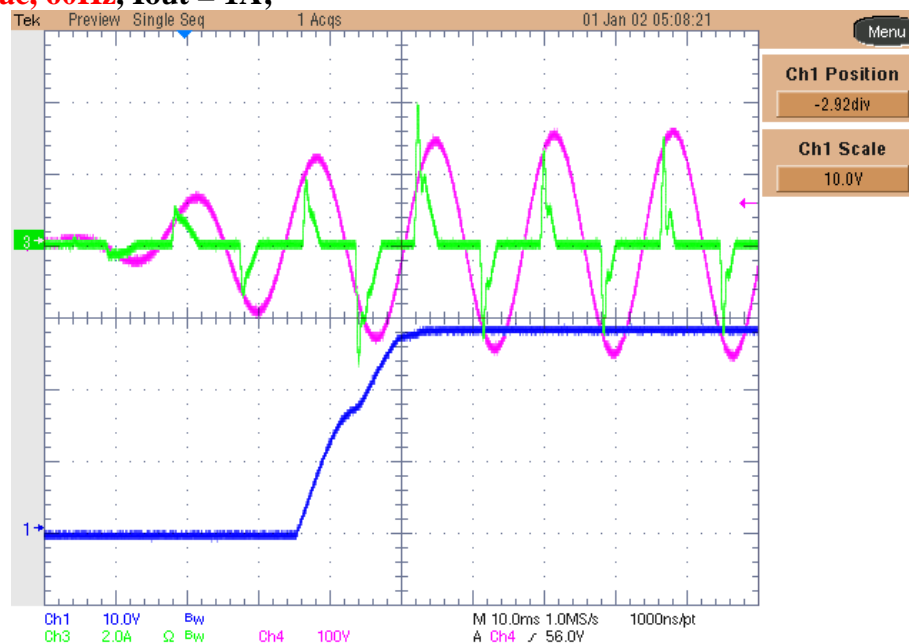


Vin = 230Vac, 50Hz, Iout = 1A;

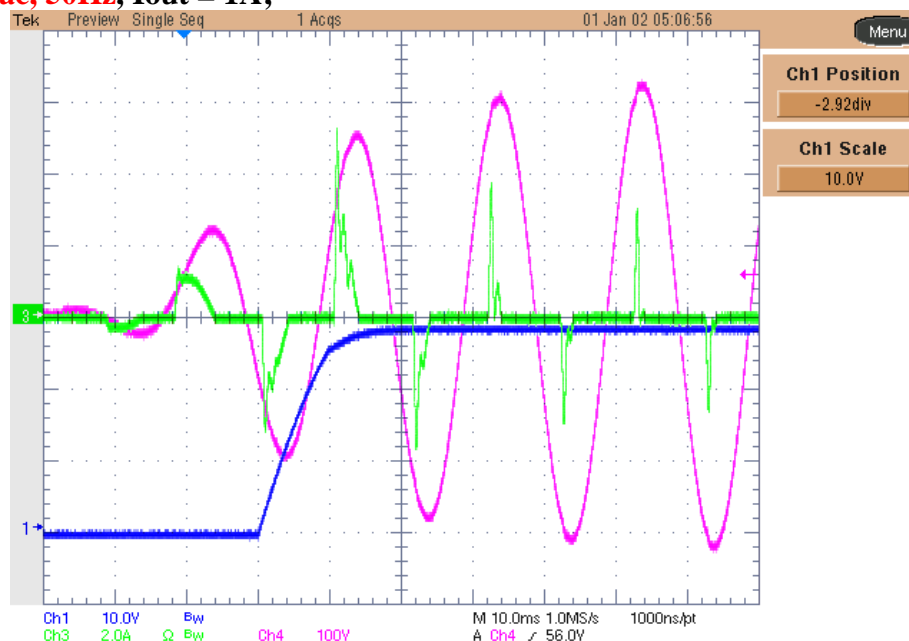

Ch.4: Input voltage (100V/div, 10ms/div), Ch.1: Output voltage (10V/div)


Ch.3: Input current (2A/div)

Vin = 230Vac, 50Hz, No Load;

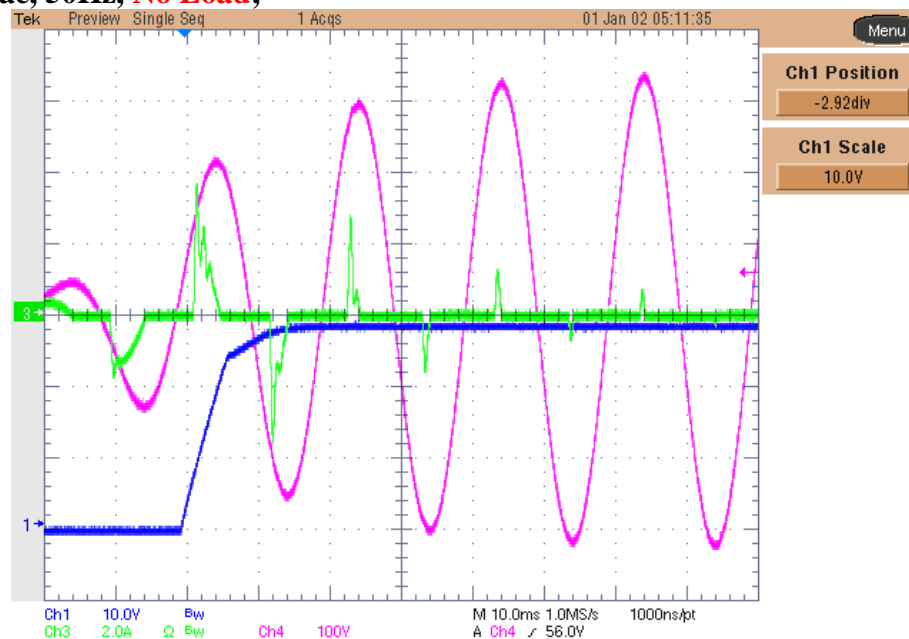

2 Efficiency

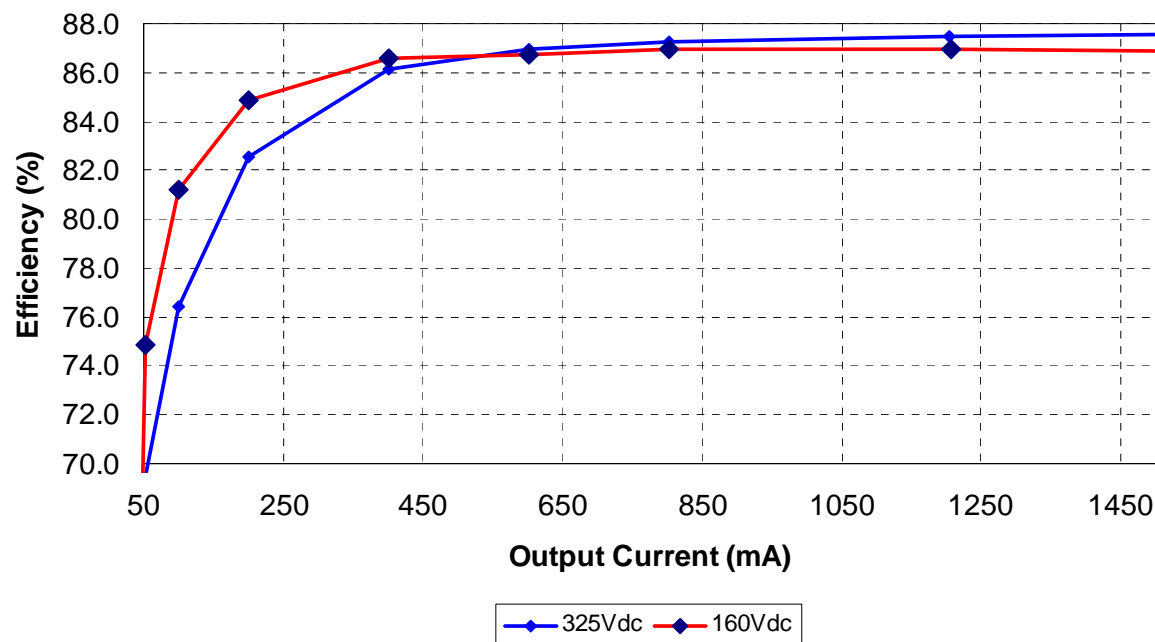The efficiency data are shown in the tables and graph below. In order to get an accurate measure of the input power, a DC voltage source has been employed, set to the peak value of the two nominal input voltages: 115Vac and 230Vac (160Vdc and 325Vdc).




Iout (mA)	Vout (V)	Pout (W)	Iin (mA)	Vin (Vdc)	Pin (W)	Ploss (W)	Eff (%)
0.0	28.60	0.00	1.14	160.0	0.18	0.18	0.00
51.5	28.60	1.47	12.28	160.3	1.97	0.50	74.82
100.2	28.58	2.86	22.0	160.3	3.53	0.66	81.17
200.0	28.58	5.72	42.0	160.3	6.73	1.02	84.90
402.4	28.58	11.50	82.9	160.2	13.28	1.78	86.60
602.3	28.57	17.21	123.8	160.2	19.83	2.63	86.76
802	28.57	22.92	164.6	160.1	26.35	3.44	86.96
1206	28.55	34.43	247.5	160.0	39.60	5.17	86.95
1502	28.55	42.88	308.5	160.0	49.36	6.48	86.88

Iout (mA)	Vout (V)	Pout (W)	Iin (mA)	Vin (Vdc)	Pin (W)	Ploss (W)	Eff (%)
0.0	28.61	0.00	0.945	325.2	0.31	0.31	0.00
51.5	28.61	1.47	6.52	325.1	2.12	0.65	69.51
100.1	28.60	2.86	11.5	325.1	3.75	0.88	76.44
200.0	28.59	5.72	21.3	325.1	6.92	1.21	82.57
402.5	28.59	11.51	41.1	325.1	13.36	1.85	86.12
602.3	28.58	17.21	60.9	325.0	19.79	2.58	86.97
802	28.57	22.92	80.8	325.0	26.26	3.34	87.27
1203	28.56	34.36	120.8	325.0	39.26	4.90	87.51
1502	28.55	42.88	150.7	324.9	48.96	6.08	87.58


3 Output Ripple Voltage

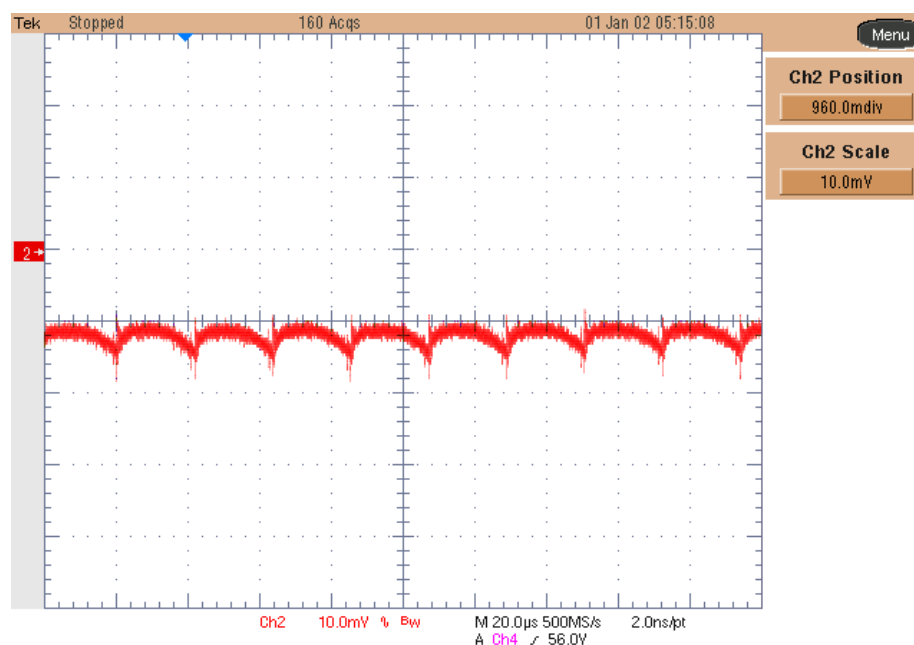The output ripple voltage is shown in the plot below. The input was set to 320Vdc and the output to 1A. **Ch.2: Output Voltage (10mV/div, 20us/div, AC coupling, 20MHz BWL)**



The picture below shows how the output ripple voltage is increased during a burst mode condition. The input was unmodified and the output set to 50mA.

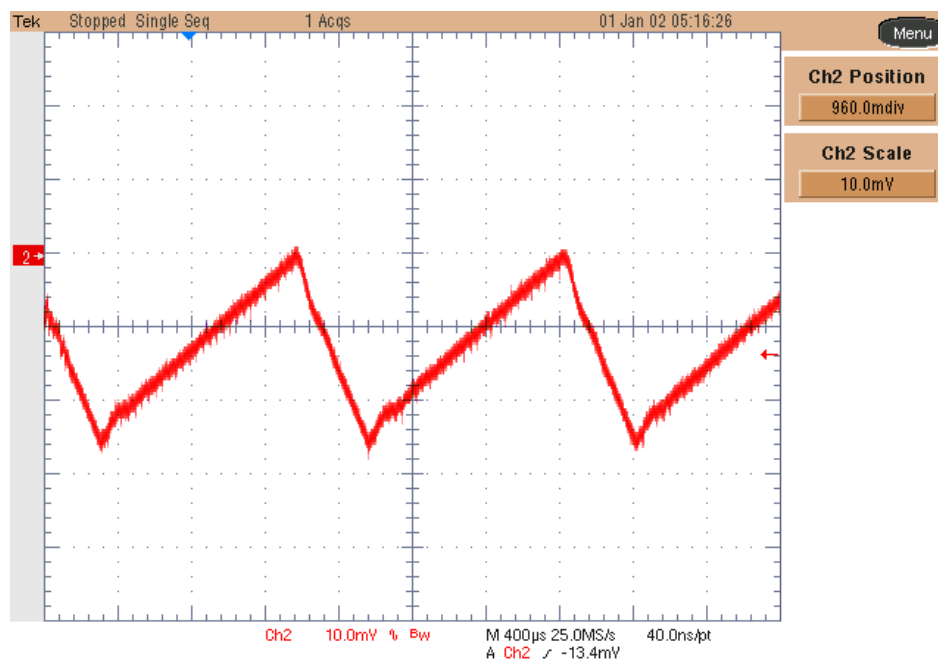
Ch.2: Output Voltage (10mV/div, 400us/div, AC coupling, 20MHz BWL)



4 Switching Node Waveform

The image below shows the peak voltage on the drain of the Mosfet Q1 with a 320Vdc input, and 1A load.

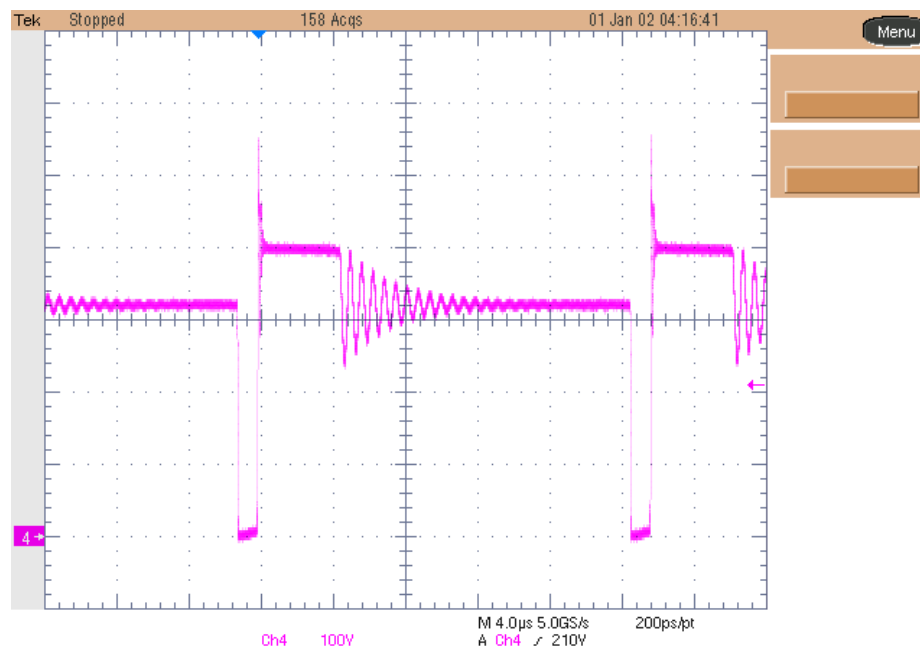
Ch4: Drain voltage (100V/div, 4us/div, No BWL).



By reducing the load, the converter enters the burst mode, as shown in the picture below.


Ch4: Drain voltage (100V/div, 4 μ s/div, No BWL).

V_{in} = 320Vdc, I_{out}=40mA

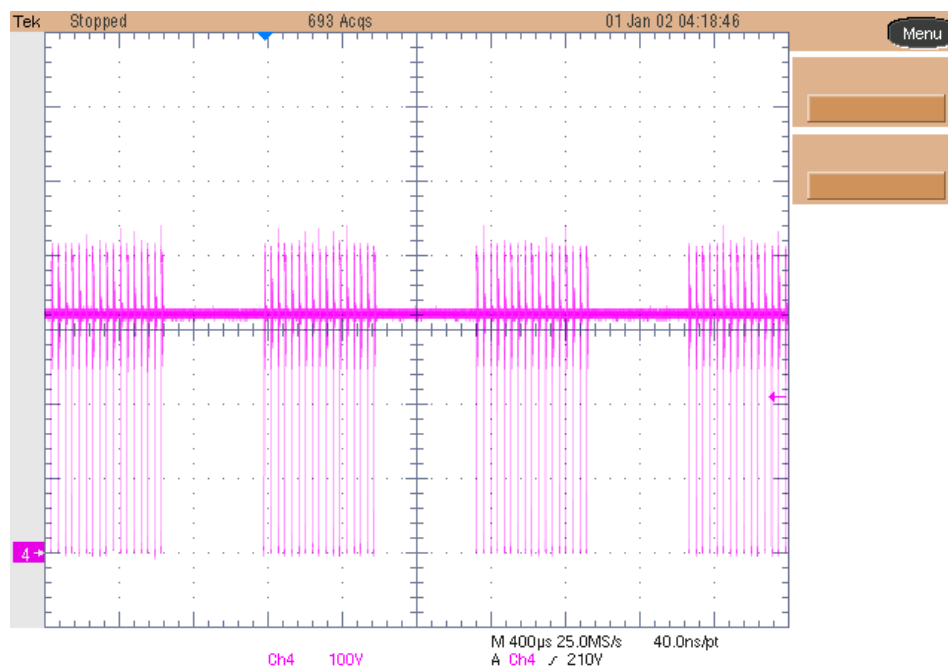

Ch4: Drain voltage (100V/div, 1msec/div, No BWL).

V_{in} = 320Vdc, No Load

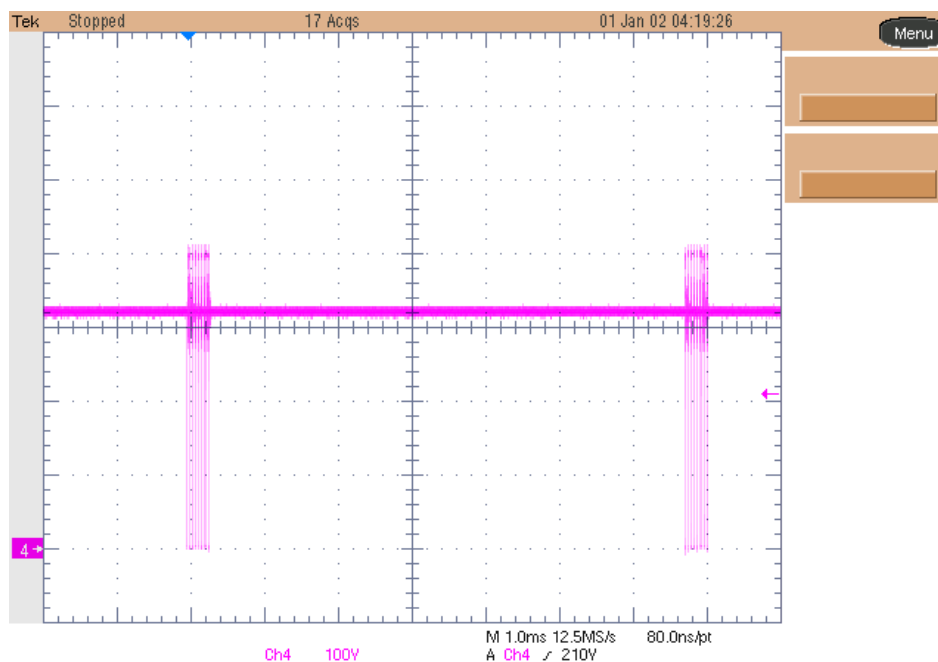


5 Transient Response

The image below shows the transient response of the output voltage when the load has been switched between 0.5A and 1.75A. The input voltage was set to 115Vac, 60Hz. The channel 4 shows the bulk capacitor (C3) voltage.

Ch2: Output Voltage (200mV/div, 20ms/div, AC coupled, 20MHz BWL).

Ch3: Output Current (500mA/div, DC coupled)

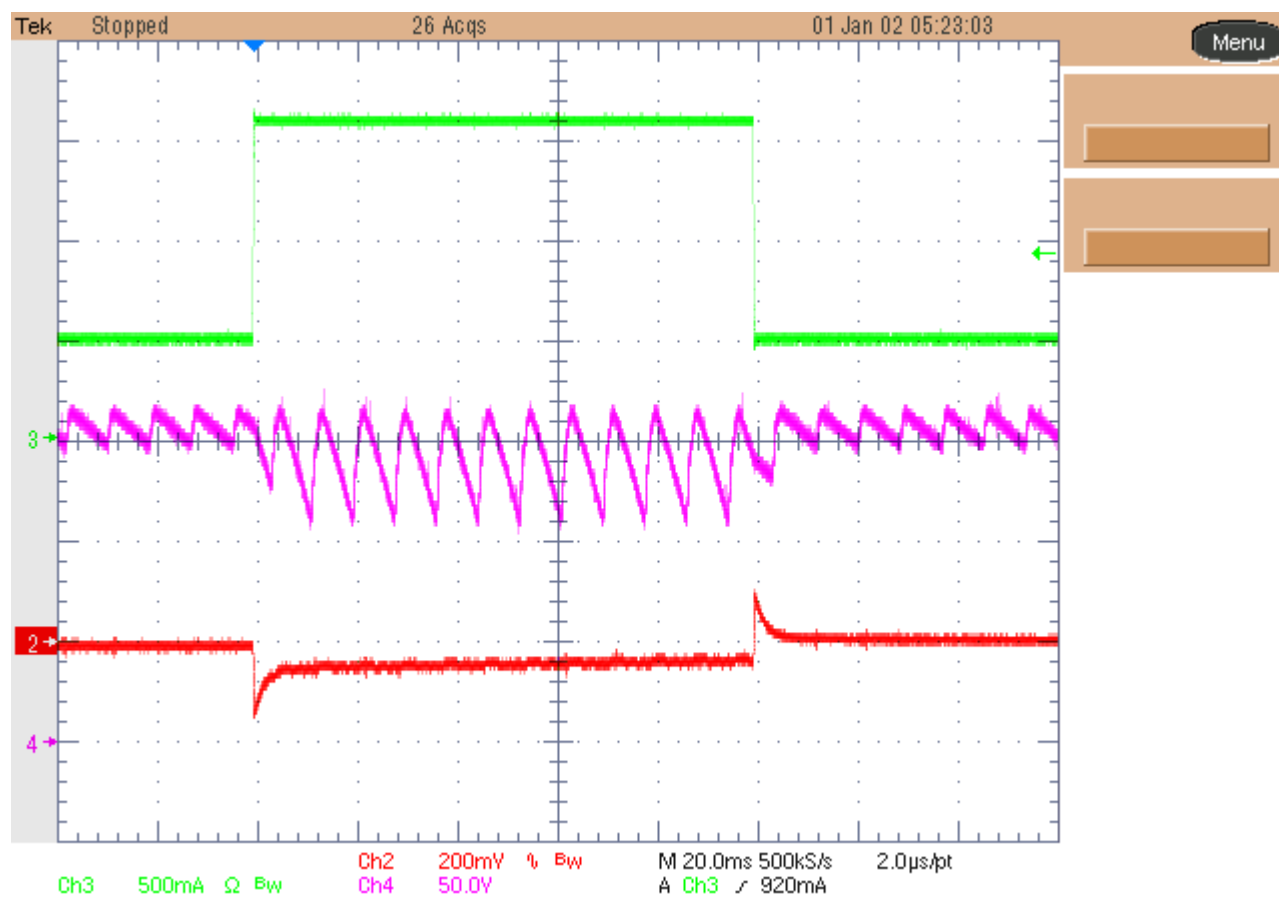Ch4: C3 capacitor voltage (50V/div, DC coupled)




The worst case condition has been measured at 96Vac input. The converters doesn't regulate anymore at 50W peak due to large 120Hz ripple. If full power is needed at these conditions, it is advisable to increase the bulk capacitor C3. The load has not been changed from the previous measurement.

Ch2: Output Voltage (200mV/div, 20ms/div, AC coupled, 20MHz BWL).


Ch3: Output Current (500mA/div, DC coupled)

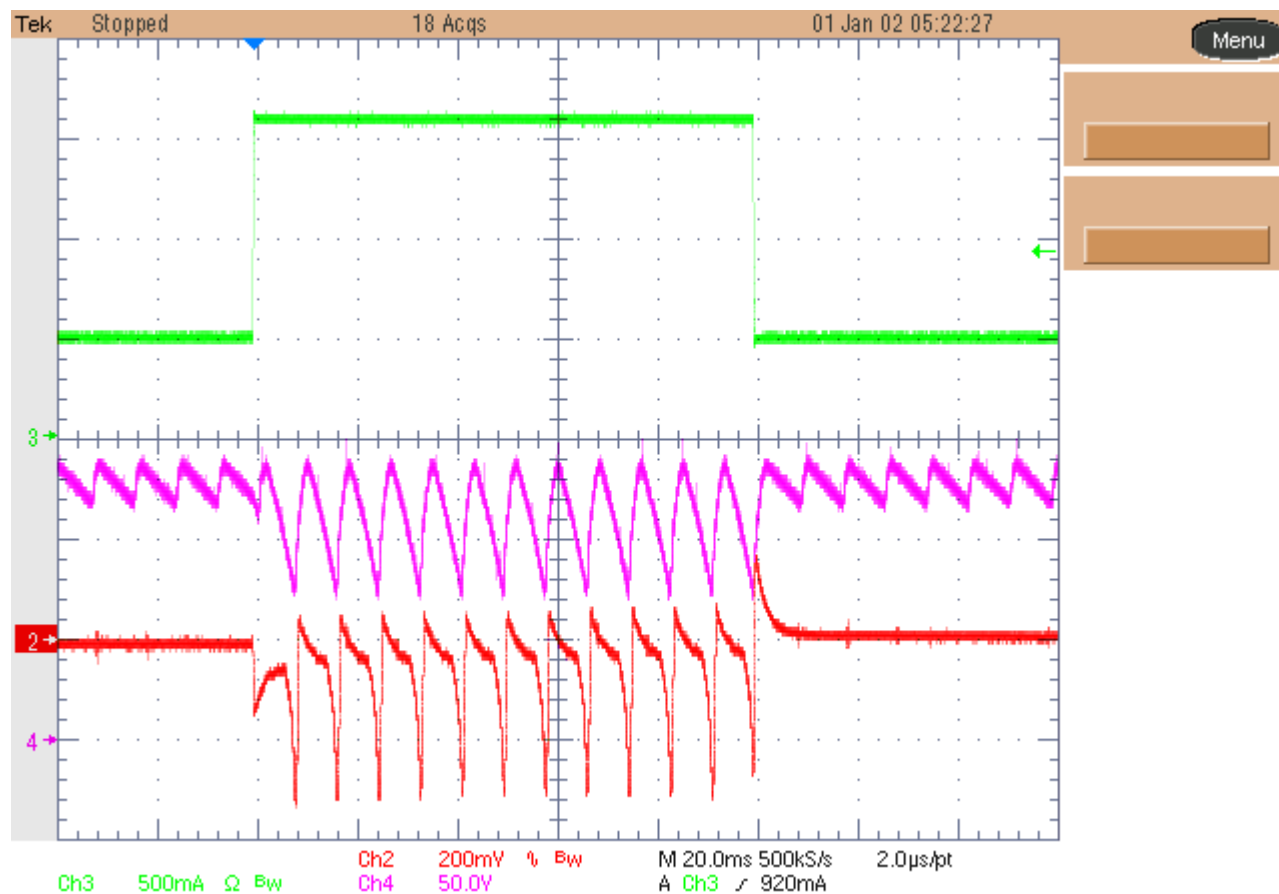Ch4: C3 capacitor voltage (50V/div, DC coupled)




6 Loop Response

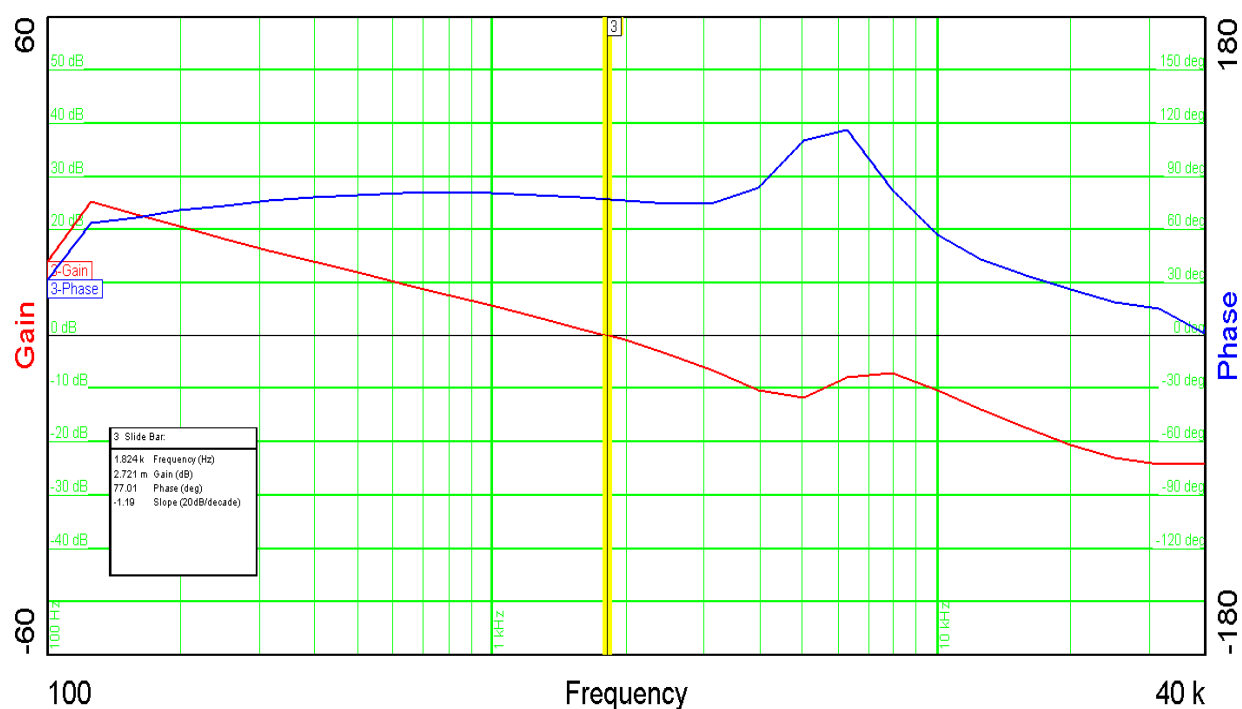The graph below shows the bode-plot analysis. The input voltage was set to 320Vdc and the load to 1A. The crossover frequency was 1.82KHz and the phase margin 77 deg., while the gain margin was 25dB.



7 EMI Measurement

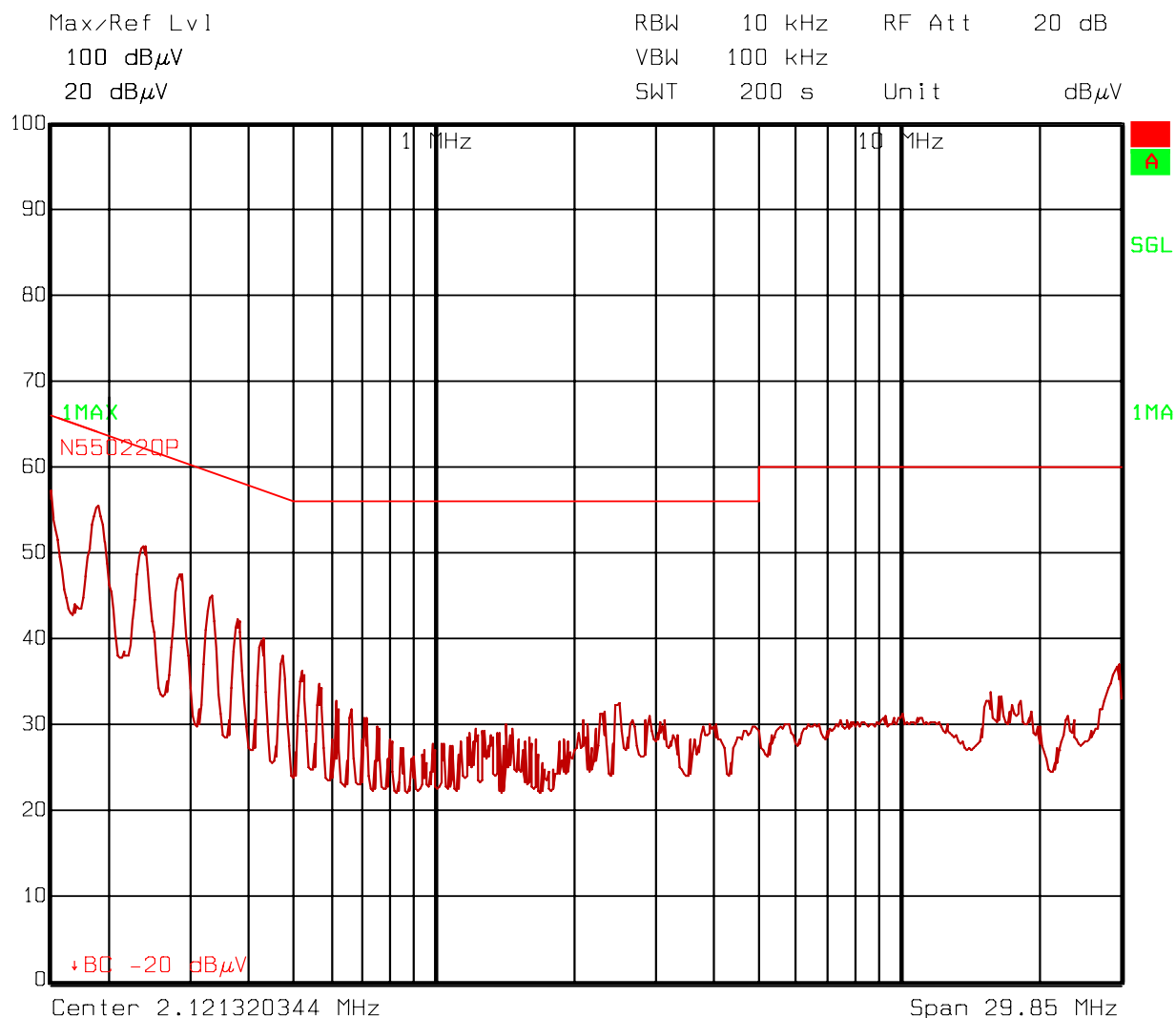The graph below shows the conducted emission EMI noise and the EN55022 Class-B Quasi-Peak limits. The load was connected to a LISN and an isolation transformer; the load was a power resistor and the resistance value set to get a load of 1A, while the input voltage was 230Vac. The receiver was set to Quasi-peak detector, 10 KHz bandwidth.



Title: FFlo1
Date: 30.MAY.2012 15:46:29

EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMER

For Feasibility Evaluation Only, in Laboratory/Development Environments. The EVM is not a complete product. It is intended solely for use for preliminary feasibility evaluation in laboratory / development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical / mechanical components, systems and subsystems. It should not be used as all or part of a production unit.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. Since the EVM is not a completed product, it may not meet all applicable regulatory and safety compliance standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.

Certain Instructions. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output ranges are maintained at nominal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of this agreement. This obligation shall apply whether Claims arise under the law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate TI components for possible use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated