

# Stacked-FET switches enable high-efficiency, high-density solutions

By Tiger Zhou  
Senior Applications Engineer

## Introduction

High-efficiency, high-density power supplies have been a trend for communications equipment due to increasing power consumption and reduced board space. A stacked-FET switch enables high-efficiency and high-density solutions. Two real design examples are examined to illustrate this point. The first is a 30-A design where the benefits of a stacked-FET switch are evaluated relative to size reduction, efficiency gain and thermal budget savings. A second design implements the stacked-FET switch with an integrated driver to further increase system efficiency in a 60-A supply.

As modern electronics equipment advances in speed and performance, the number of power rails keeps increasing in addition to an increase in power consumption. Conversely, the physical area for power supplies keeps shrinking because precious real estate is given to the core ASIC and processors. As such, a high-efficiency, high-density power supply is a challenge for every power designer.

By combining the latest NexFET™ silicon and innovative packaging technologies, a dual FET (Figure 1) consists of two stacked FETs in a SO8 (5 mm x 6 mm) package. This configuration reduces the device footprint by half and doubles the output density.

Using a stacked-FET switch in point-of-load (PoL) applications has many benefits. This article presents a comparative study for a 1.8-V/30-A application using discrete FETs versus stacked FETs.

## Reduced footprint

In the 30-A design example, a dual-phase synchronous buck controller was selected with optimum performance over ripple and transient responses. In the discrete solution layout, the FETs occupy nearly half the area. By replacing two discrete FETs with one stacked FET, the solution size shrinks by 20%. Figure 2 shows two layouts: (a) a discrete solution and (b) the stacked-FET solution. The discrete solution measures 0.75 by 1.3 inches, and the stacked-FET solution measures 0.75 by 1.05 inches.

Figure 1. Stacked-FET switches in a SO8 package


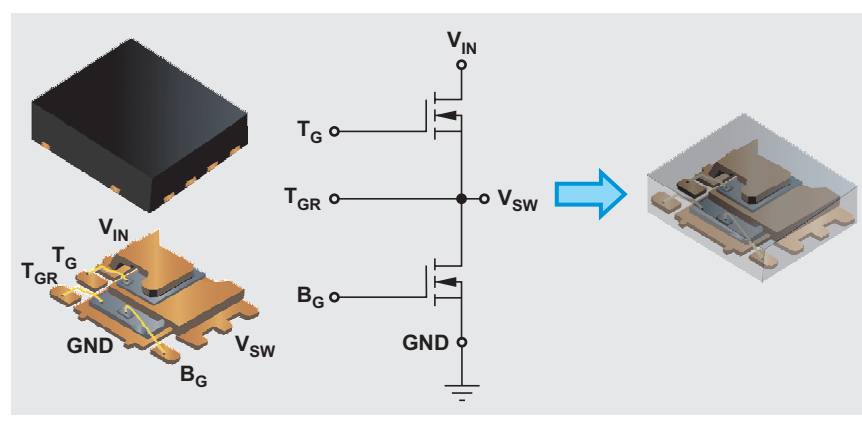


Figure 2. A stacked-FET solution size is 20% smaller than a discrete-FET solution

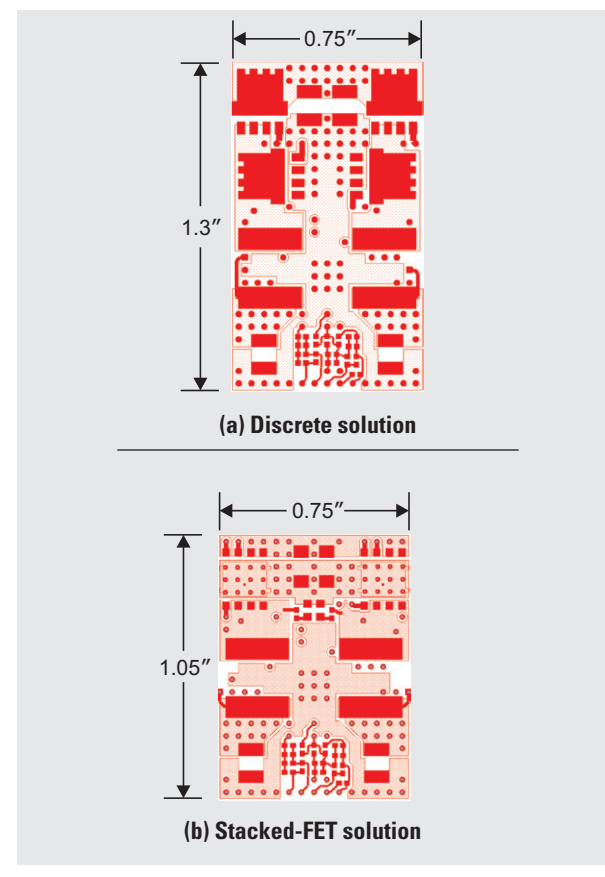

## Increased system efficiency

Compared to other state-of-the-art discrete FETs (Figure 3), the stacked-FET efficiency (red curve) is at least 2.2% higher. A stacked-FET switch, such as the CSD87350, has lower on-state resistance ( $R_{DS(on)}$ ) and lower gate charge due to its unique device structure. Moreover, the stacked-FET packaging technique removes the parasitic inductance associated with traditional wire-bonded technology. Thus, it optimizes the switching speed and increases system efficiency. Both designs use the same inductor, input and output capacitors, and were tested under the same test conditions with a 10-V input, 1.8-V output and 300-kHz switching frequency.


## Cooler operating temperatures

The power loss of stacked FETs is the sum of both the top and bottom FETs, but its thermal resistance is much less than that of discrete FETs. As illustrated in Figure 4, a stacked-FET switch runs 23° cooler than discrete FETs under the same test conditions (10 V<sub>IN</sub>, 1.8-V/30-A output, 300 kHz). When the discrete FET reaches 108.7°C, the stacked-FET dies only reach 85.6°C because it is GND referenced.


The large area of the exposed pad connects to the ground plane of the PCB by 12 thermal vias, which utilizes multiple inner ground layers commonly available with a modern multi-layer PCB. For the discrete FET solution, the heat is concentrated in a small area, known as a switching plane, which prohibits multiple vias for signal integrity concerns.

It was demonstrated that stacked-FET technology enables high-efficiency and high-density solutions. One stacked FET replaces two discrete FETs, thus, reducing the overall solution size by 20%. Its increased efficiency and effective thermal conductivity allows it to run 23° cooler versus a discrete FET under same test conditions.


**Figure 3. A stacked FET excels over other discrete FETs under the same test conditions**

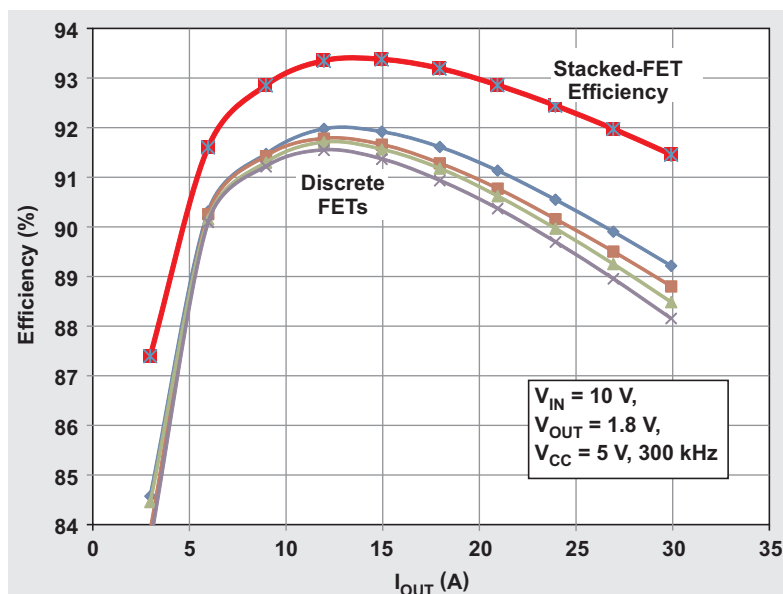

**Figure 4. Operating temperatures of discrete and stacked FETs**

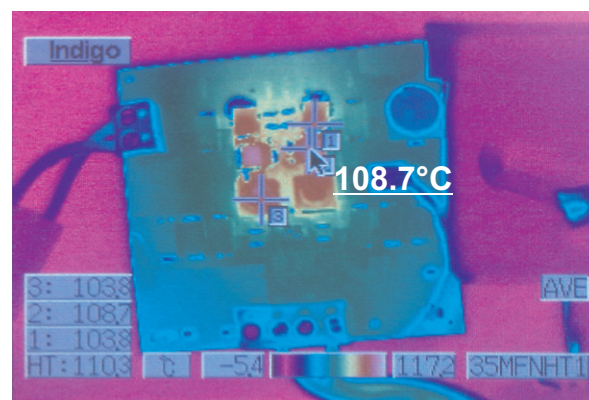

**(a) Thermal image of a discrete FET**

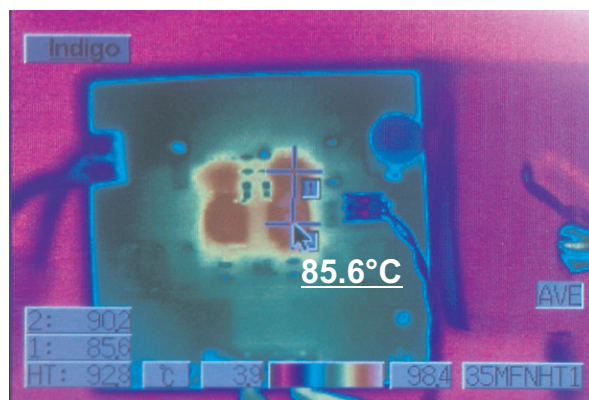

**(b) Thermal image of a stacked FET**

To further push the technology boundary, a new device, the CSD95372B in Figure 5, integrates a stacked-FET switch with an integrated driver. The package maintains the same size as a standard FET, which is SO8 (5 mm x 6 mm) package. By shortening the drive-to-FET distance, it fully optimizes the drive capability by minimizing the driver-related parasitic inductances. It has higher switching speeds, lower conduction loss and requires less PCB real estate. Therefore, it achieves even higher system efficiency.

### Advantages of stacked FET with integrated driver

A 1-V/60-A design solution was used to demonstrate the advantages of a stacked-FET switch with driver. This design was tested with a 12-V input, 1-V output and a 500-kHz switching frequency. The baseline solution used eight discrete FETs to supply the 60-A load current. As shown in Figure 6(a), the solution size is 1.33 by 1.33 inches.

In Figure 6(b), eight discrete FETs were replaced with two stacked FETs. The solution size now shrinks to 1 by 1.075 inches. This now results in a 40% size reduction from the discrete-FET solution.


In Figure 6(c), two stacked-FET switches with driver also replaced eight discrete FETs. This solution size is 1 by 1 inch, or a 43% size reduction.

With the same test conditions applied to each design solution, the stacked-FET with driver solution achieves the highest efficiency of 88.6%. This is 6.6% higher than the discrete-FET efficiency and 2.9% higher at full load (60 A) than the stacked-FET solution without an integrated driver. Figure 7 shows the efficiency of the three different solutions. The green curve represents the stacked-FET with driver solution, the blue curve represents the stacked-FET solution, and the red curve represents a discrete-FET solution.


### Conclusion

The increasing efficiency and density requirements suggests that a high level of package integration is needed. Stacked-FET switches have silicon improvements and innovative packaging technologies that increase system efficiency. Likewise, by replacing a stacked-FET device with one that has an integrated driver, system efficiency further improves due to optimized driver and minimized parasitics.


**Figure 5. A stacked FET with driver**

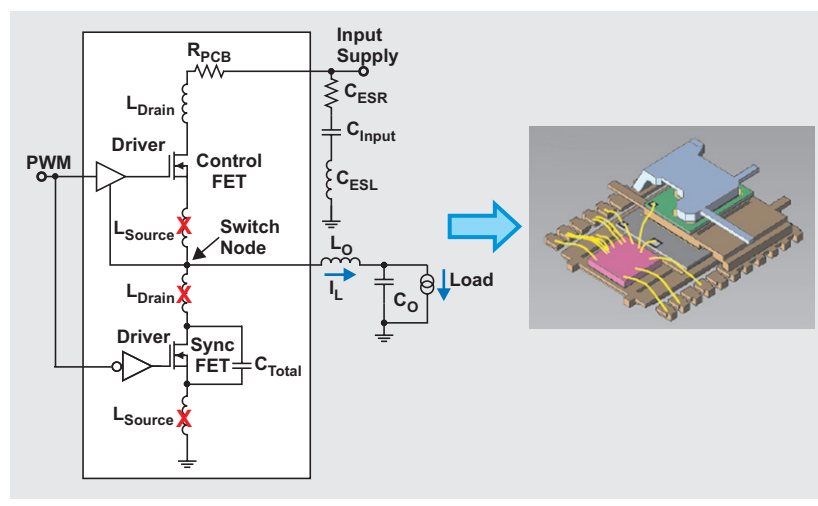

**Figure 6. Three solutions for a 1-V/60-A supply**

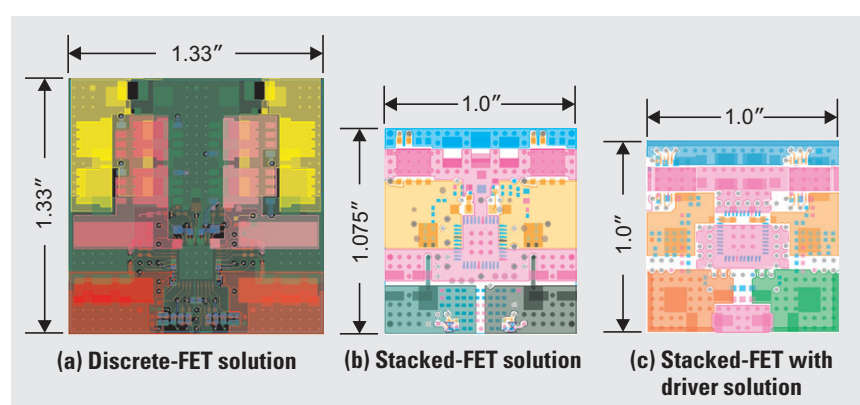

**Figure 7. System efficiency is compared among three designs**

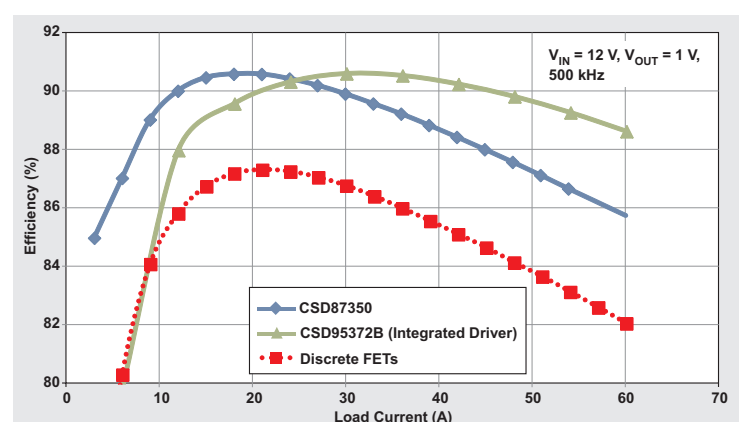

### Related Web sites

[www.ti.com/1q15-CSD87350Q5D](http://www.ti.com/1q15-CSD87350Q5D)

[www.ti.com/1q15-CSD95372BQ5M](http://www.ti.com/1q15-CSD95372BQ5M)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)