CN-5

CN-5 Oscillator Characteristics of COPS Microcontrollers



Literature Number: SNOA629

Oscillator Characteristics of COPS™ Microcontrollers

National Semiconductor COP Note 5 September 1986



Table of Contents

1.0 INTRODUCTION

2.0 RC OSCILLATOR OPTION

3.0 CRYSTAL OR INVERTER OPTION

3.1 COP420/COP402

3.1.1 L, LC, and RLC Networks

3.2 COP420L

3.3 COP410L

3.4 General Notes

4.0 CONCLUSION

1.0 INTRODUCTION

COPS microcontrollers will operate with a wide variety of oscillator circuits. This paper focuses on two of the oscillator options available on COPS microcontrollers: the internal RC oscillator, and the crystal or inverter oscillator. The typical behavior of the RC oscillator with temperature and voltage (and typical values of R and C) is documented. For the crystal or inverter option, circuit configurations (RC, RL, RLC, R, LC, L) are presented which will allow the microcontroller to operate properly without the use of ceramic resonator or crystal.

The passive components used were inexpensive, uncompensated devices: standard carbon resistors, ceramic or foil capacitors, and air core or iron core inductors. To provide reasonably clear data on the characteristics of the microcontroller itself, no attempt at compensation for the external components was made.

2.0 RC OSCILLATOR OPTION

With the RC oscillator option selected, the graphs in Figures 7 through 6 indicate the variation of the instruction cycle time of the microcontroller with temperature and voltage. Typical R and C values, as recommended in the respective device data sheets, were used. The graphs are composite graphs reflecting the worst case variations of the devices tested. Therefore, the graphs show a percentage change of the instruction cycle time from a base or reference value. Where the results are plotted against voltage the reference is the value at $V_{\rm CC}=5V$. Where the results are plotted against temperature, the reference is the value at $T=20^{\circ}{\rm C}$. A positive percent variation indicates a longer instruction cycle time and therefore a slower oscillator frequency. Similarly, a negative percent variation indicates a shorter instruction cycle time and therefore a faster oscillator frequency.

The measurements were taken by holding the RESET pin of the device low and measuring the period of the waveform at pin SK. In this mode the SK period is the instruction cycle time. For divide by 4 the oscillator frequency is given by the following:

$$frequency = \frac{4}{SK period}$$

Measurements were taken at temperatures between $-40^{\circ}\mathrm{C}$ and $+85^{\circ}\mathrm{C}$ and at V_{CC} values between 4.5V and 9.5V. However, the reader must remember that the COP400 series is specified only between $0^{\circ}\mathrm{C}$ and $+70^{\circ}\mathrm{C}$. The reader must also remember that the COP420 is specified at V_{CC} levels between 4.5V and 6.3V only. The data here is usable for the COP300 series, which is specified at the extended temperature range of $-40^{\circ}\mathrm{C}$ to $+85^{\circ}\mathrm{C}$. However, the reader must keep in mind the generally more restricted V_{CC} range for some of the various COP300 series microcontrollers.

The graphs in Figures 1 through θ reflect the variation of the microcontroller only. The resistor and capacitor were not in the temperature chamber with the COPS device. Obviously, the results will be affected by the variation of the R and C with temperature. However, this can vary dramatically with the type of components used. The user will have to combine the data here with the characteristics of the external components used to determine what type of variation may be expected in his system.

3.0 CRYSTAL OR INVERTER OPTION

With the crystal or inverter option selected on the COPS microcontroller there is, effectively, an inverter between the CKI and CKO pins. CKI is the input to the inverter and CKO is the output. Various passive circuits were connected between CKI and CKO and the results documented. Of the operational circuits, a subset was tested over temperature with the microcontroller only in the temperature chamber. A smaller subset was tested over temperature with both the microcontroller and the oscillator network in the temperature chamber.

The data with the oscillator network in the temperature chamber is obviously highly dependent on the particular components used. This data was taken with standard, inexpensive, uncompensated components. Neither high precision nor high stability components were used. This data is included only to provide the user with some very general indication of how the oscillator frequency may vary with temperature in a real system.

3.1 COP420/COP402

Except for the ROM, the COP420 and COP402 are equivalent devices. The internal circuitry of each device is identical. Therefore, data taken for one of the devices is equally

COPS™ is a trademark of National Semiconductor Corporation

applicable to the other. The following discussion will refer to the COP420 but all such references apply equally well to the COP402. Similarly, the graphs for the COP420 apply to the COP402 and vice versa.

With the crystal option selected, the COP420 oscillator circuitry will readily oscillate with almost any circuit configuration between CKI and CKO. What difficulty there is lies in finding the network of the device. With the appropriate divide option selected, oscillator frequencies between 800 kHz and 4 MHz are valid for the COP420. No data was taken for any network that produced an oscillation frequency outside the valid range.

3.1.1 L. LC. and RLC Networks

Various L, LC, and RLC networks were connected with varying results. Certain networks produced results much more stable than the RC networks; others were no better than the RC networks. With a single inductor connected between CKI and CKO, frequencies between 1 MHz and 4 MHz were easily obtained. However, the input gate capacitance at CKI (typically 5 pF to 10 pF) and the series resistance of the inductance become factors that impact the oscillation frequency and its stability over temperature.

The addition of a capacitor between CKI and ground tends to reduce the effects of the internal gate capacitance. For the single L, single C network of this type, the capacitor value should be greater than about 50 pF to begin to effectively swamp out the effects of the input gate capacitance. As might be expected, LC combinations which had their resonant frequencies within the valid COP420 frequency range produced the best results.

The addition of another capacitor(s) to the basic two-component LC network, as shown in Figure III.1, produced very good results. Varying the capacitor values in these networks — especially those capacitors between CKI and ground and CKO and ground — provided a great deal of control over the oscillation frequency. In Figure III.1, varying C1 from 25 pF to 0.01 μF produced oscillation frequencies between about 3 MHz and 1.6 MHz (C2 = 25 pF, L = 56 μH). In Figure III.2, with C1 = 330 pF, L = 56 μH , and C2 = 27 pF, varying C3 between 10 pF and 0.003 μF produced oscillation frequencies between about 2 MHz and 1.1 MHz. Varying C2 in Figure 111.3 produced a similar kind of control.

As the graphs indicate, various types of RLC networks were also tried. The range of possible usable circuits here is limited only by the user's imagination and his favorite type of RLC oscillator circuit. When their resonant frequency is

within the valid frequency range of the COP420, LC and RLC networks can be a very effective substitute for a crystal. The only potential problem is that a good RLC, or even LC, oscillator circuit may not be a cost-effective substitute for a crystal in a COP420 system. The user will have to make that determination.

3.2 COP420L

The valid input frequency range for the COP420L, with the appropriate divide option selected, is between 200 kHz and 2.097 MHz. With the crystal option selected the COP420L oscillated much less readily than the COP420.

The LC networks gave outstanding results with the COP420L. With the simple two-component LC network shown in the graphs, holding C at 50 pF and varying L from 200 μH to 700 μH gave oscillation frequencies from about 2 MHz to 1 MHz. Holding L at 390 μH and varying C from 10 pF to 700 pF gave oscillation frequencies of about 2 MHz to 1.6 MHz. Similar results were obtained when a capacitor was placed in parallel with the inductance.

3.3 COP410L

The COP410L has a valid input frequency range of 200 kHz to 530 kHz.

The LC networks also gave very good results. With the simple LC network shown in the graphs, holding L at 4700 μH and varying C from 25 pF to 0.003 μF gave oscillation frequencies of about 460 kHz to 225 kHz.

3.4 GENERAL NOTES

With the crystal or inverter option selected on COPS microcontrollers, a wide variety of networks may be used in place of the ceramic resonator or crystal.

LC and RLC networks can be used in any of the devices. Appropriately designed, these networks will provide a stable oscillation frequency for the microcontroller. The user will have to allow for the variation of the external components with temperature when using these networks. The problems with networks such as these is that they may not be cost-effective alternatives to the crystal or resonator, especially if high stability, temperature compensated components are used. The user will have to make the determination of cost-effectiveness.


A final note is that all of these networks place a load on the CKO output. If the signal from CKO is needed elsewhere in the system and a circuit similar to one of those discussed in this document is used, it will probably be necessary to buffer the CKO output.


4.0 Conclusion

The networks described are generally simple and inexpensive and have all been observed to be functional.


The results obtained provide greater flexibility in the oscillator selection in a COPs system and gives the user some general indication as to what may be expected with the various circuits described.

COP Microcontroller Pinouts

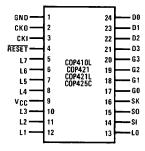

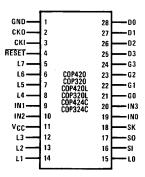

TL/DD/6938-1

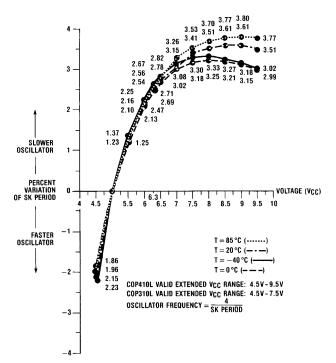


TL/DD/6938-2

Note 1: Base period at $V_{CC} = 5.0V$.

 $\textbf{Note 2:} \ \mathsf{Device} \ \mathsf{variation} \ \mathsf{only.} \ \mathsf{Graph} \ \mathsf{does} \ \mathsf{not} \ \mathsf{include} \ \mathsf{RC} \ \mathsf{variation} \ \mathsf{with} \ \mathsf{temperature}.$

Note 3: SK period = instruction cycle time.


FIGURE 1. COP310L/COP410L RC Oscillator Variation with V_{CC}

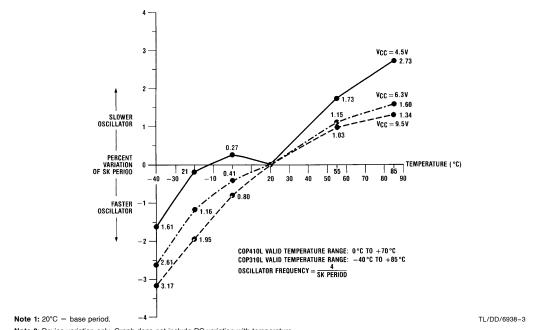

Note 2: Device variation only. Graph does not include RC variation with temperature.

Note 3: SK period = instruction cycle time.

FIGURE 2. COP310L/COP410L RC Oscillator Variation with Temperature

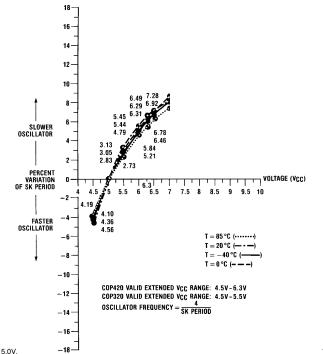


Note 1: Base period at $V_{CC} = 5.0V$.

TL/DD/6938-4


Note 2: Device variation only. Graph does not include RC variation with temperature.

FIGURE 3. COP320/COP420 RC Oscillator Variation with V_{CC}

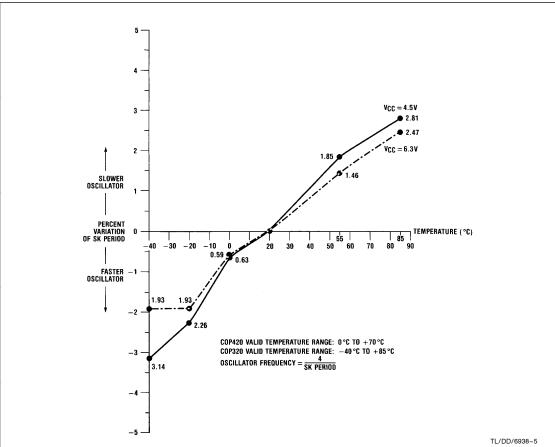

Note 2: Device variation only. Graph does not include RC variation with temperature.

FIGURE 4. COP320/COP420 RC Oscillator Variation with Temperature

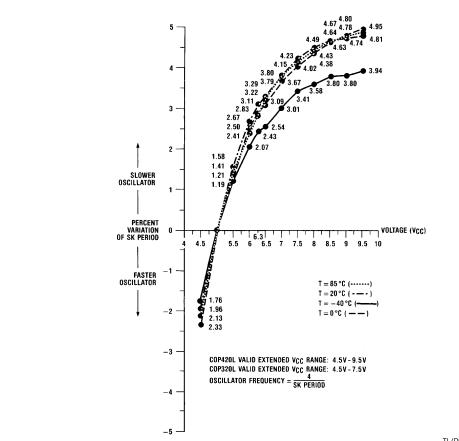


TL/DD/6938-6

Note 1: Base period at $V_{CC}\,=\,5.0V.$


Note 2: Device variation only. Graph does not include RC variation with temperature.


FIGURE 5. COP320L/COP420L RC Oscillator Variation with V_{CC}

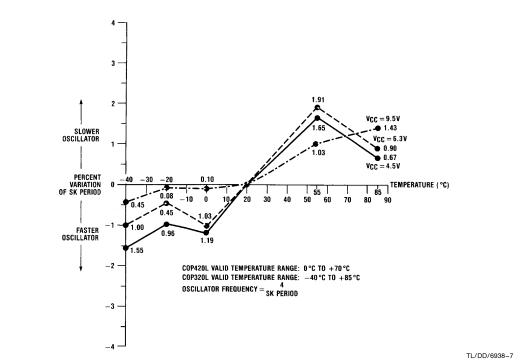

Note 2: Device variation only. Graph does not include RC variation with temperature.


FIGURE 6. COP320L/COP420L RC Oscillator Variation with Temperature

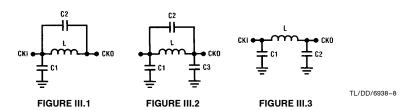

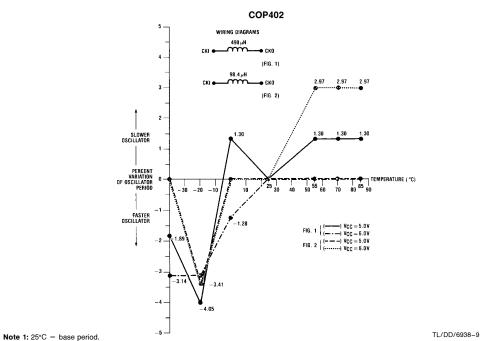


Note 2: Device variation only. Graph does not include "L" variation with temperature.

FIGURE 7

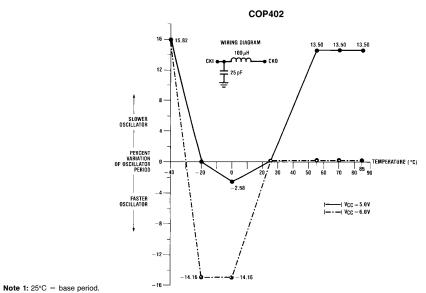

Note 2: Device variation only. Graph does not include LC variation with temperature.

FIGURE 8

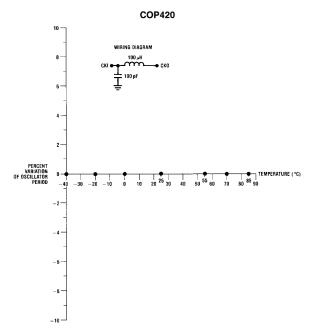

TL/DD/6938-11


Note 1: $25^{\circ}C$ = base period.

Note 2: Device variation only. Graph does not include LC variation with temperature.

No measurable variation over temperature.

FIGURE 9


COP420

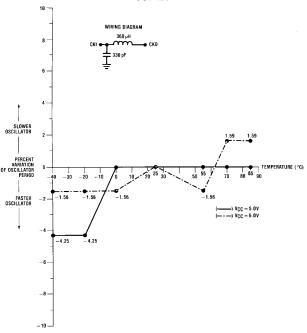

TL/DD/6938-12

Note 1: 25°C = base period.


Note 2: Device variation only. Graph does not include LC variation with temperature.

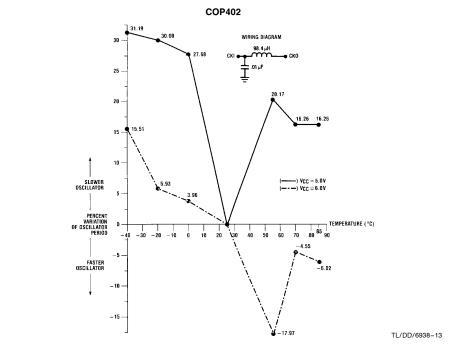

Note 2: Device variation only. Graph does not include LC variation with temperature.

FIGURE 11


COP402

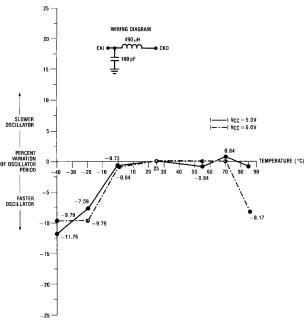

Note 1: $25^{\circ}C = base period$.

Note 2: Device variation only. Graph does not include LC variation with temperature.


FIGURE 12

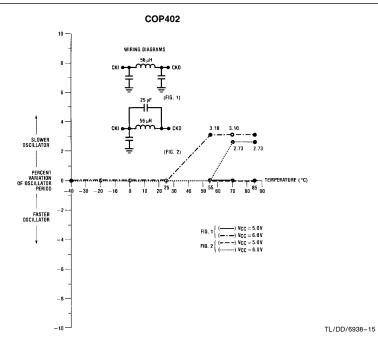

Note 1: $25^{\circ}C$ = base period.

Note 2: Device variation only. Graph does not include LC variation with temperature.


FIGURE 13 COP402

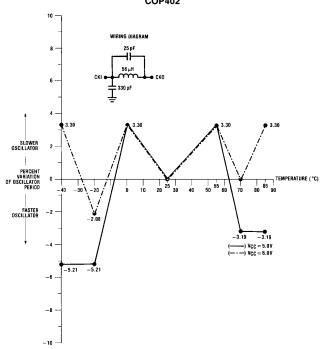

Note 1: 25°C = base period.

Note 2: Device variation only. Graph does not include LC variation with temperature.

FIGURE 14

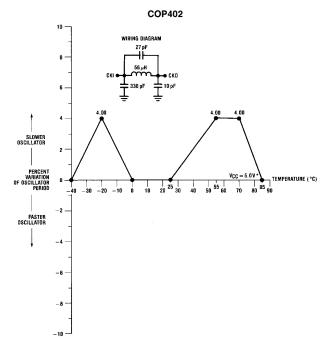


Note 2: Device variation only. Graph does not include LC variation with temperature.

*No variation at 6V.

FIGURE 15


TL/DD/6938-17

TL/DD/6938-18

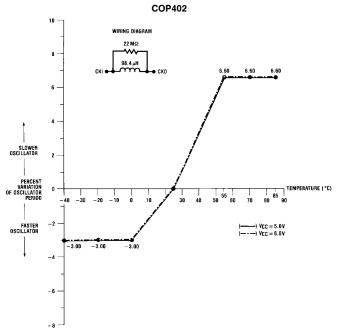

Note 1: 25°C = base period.

Note 2: Device variation only. Graph does not include RL variation with temperature.

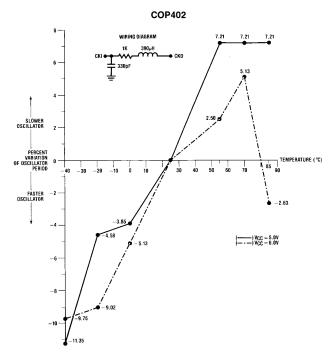


Note 2: Device variation only. Graph does not include RLC variation with temperature.

FIGURE 17

TL/DD/6938-19


TL/DD/6938-20

COP402

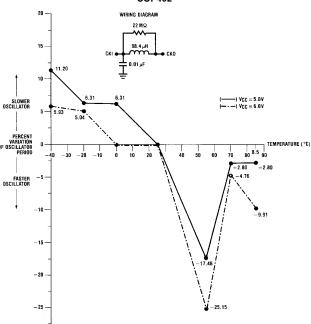

Note 1: 25°C = base period.

Note 2: Device variation only. Graph does not include RLC variation with temperature.

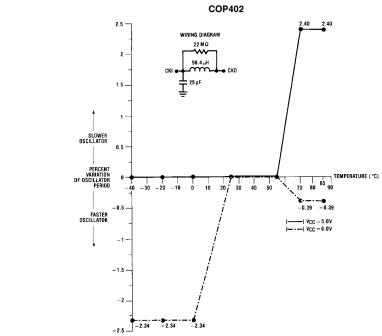


Note 2: Device variation only. Graph does not include RLC variation with temperature.

FIGURE 19

TL/DD/6938-21

TL/DD/6938-22

COP402

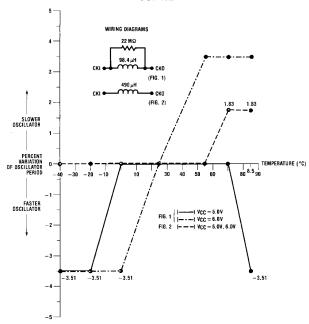

Note 1: 25°C = base period.

Note 2: RL in oven with COP402.


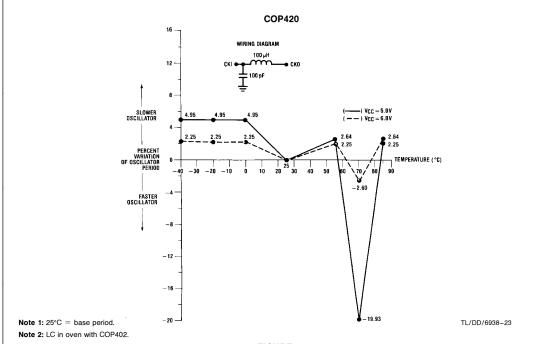



FIGURE 21 COP420L

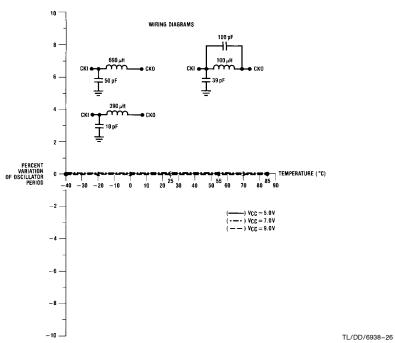

Note 1: No measurable variation for all three circuits above.

Note 2: 25°C = base period.


Note 3: Device variation only. Graph does not include LC variation with temperature.

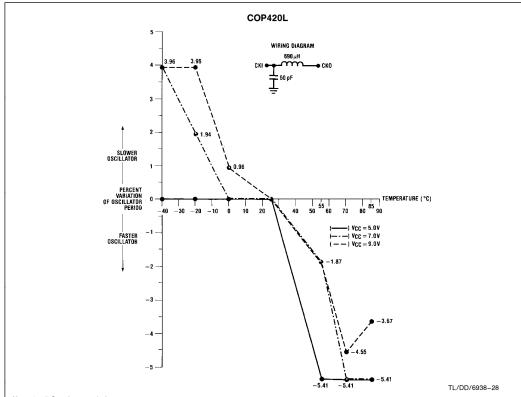

Note 1: 25°C = base period.

Note 2: LC in oven with COP420L.


FIGURE 23

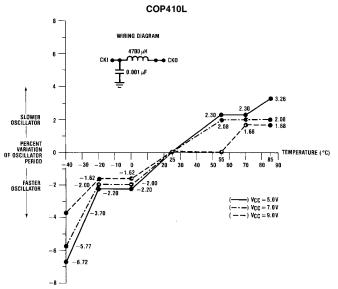

Note 1: 25°C = base period.

Note 2: Device variation only. Graph does not include LC variation with temperature.


FIGURE 24

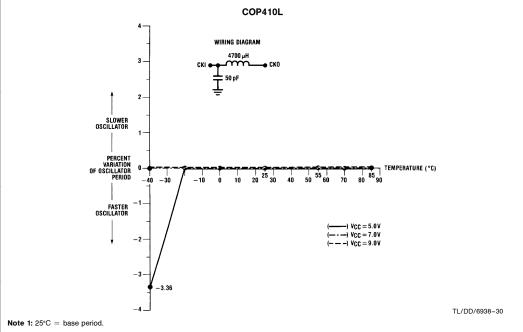

Note 2: Device variation only. Graph does not include LC variation with temperature.

FIGURE 25

COP410L

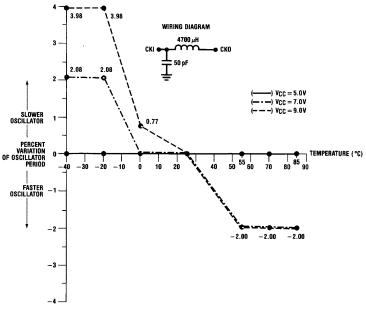

Note 1: 25°C = base period.

Note 2: LC in oven with COP410L.

FIGURE 26

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



CN-5

National Semiconductor Corporation 1111 West Bardin Road Arlington, TX 76017 Tel: 1(800) 272-9959 Fax: 1(800) 737-7018

National Semiconductor Europe

Fax: (+49) 0-180-530 85 86 Email: cnjwge@tevm2.nsc.com
Deutsch Tel: (+49) 0-180-530 85 85 English Tel: (+49) 0-180-532 78 32 Français Tel: (+49) 0-180-532 78 35 Italiano Tel: (+49) 0-180-534 16 80

National Semiconductor Hong Kong Ltd. 13th Floor, Straight Block, Ocean Centre, 5 Canton Rd. Tsimshatsui, Kowloon Hong Kong Tel: (852) 2737-1600 Fax: (852) 2736-9960 National Semiconductor Japan Ltd. Tel: 81-043-299-2309 Fax: 81-043-299-2408

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | Applications |
|----------|--------------|
|----------|--------------|

Audio www.ti.com/audio Communications and Telecom www.ti.com/communications **Amplifiers** amplifier.ti.com Computers and Peripherals www.ti.com/computers dataconverter.ti.com Consumer Electronics www.ti.com/consumer-apps **Data Converters DLP® Products** www.dlp.com **Energy and Lighting** www.ti.com/energy DSP dsp.ti.com Industrial www.ti.com/industrial Clocks and Timers www.ti.com/clocks Medical www.ti.com/medical Interface interface.ti.com Security www.ti.com/security

Logic logic.ti.com Space, Avionics and Defense www.ti.com/space-avionics-defense

Power Mgmt power.ti.com Transportation and Automotive www.ti.com/automotive
Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

RFID <u>www.ti-rfid.com</u>

OMAP Mobile Processors <u>www.ti.com/omap</u>

Wireless Connectivity www.ti.com/wirelessconnectivity

TI E2E Community Home Page e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2011, Texas Instruments Incorporated