

Fast and Furious: Designing Longer-lasting 16S-17S Li-ion Battery Packs for E-motorcycles



Ryan Tan

With the rapid growth in demand for delivery services, electric motorcycles (e-motorcycles) are becoming more popular as a transportation method because the battery capacity is much larger than e-bike/e-scooter batteries. More capacity enables longer ride times, which helps save time and enables longer-distance deliveries.

An e-motorcycle battery pack has several voltage platforms, but the most popular one is 60 V, which requires 17 series (17S) lithium-ion (Li-ion) battery cells in a pack.

Generating longer run times requires addressing three design concerns:

- High cell voltage sensing accuracy for accurate state-of-charge calculations.
- Cell voltage balancing.
- Low system current consumption, especially in standby mode.

The [16S-17S Battery Pack Reference Design with Low Current Consumption](#) addresses each design concern. It uses the [BQ76940](#) battery monitor for the lower 15S of the pack and the [LM2904B](#) dual-channel general-purpose amplifier for accurate voltage sensing of the two upper cells. Adding external metal-oxide semiconductor field-effect transistors (MOSFETs) enables larger cell-balancing capacity. [Figure 1](#) is a block diagram of the battery pack reference design.

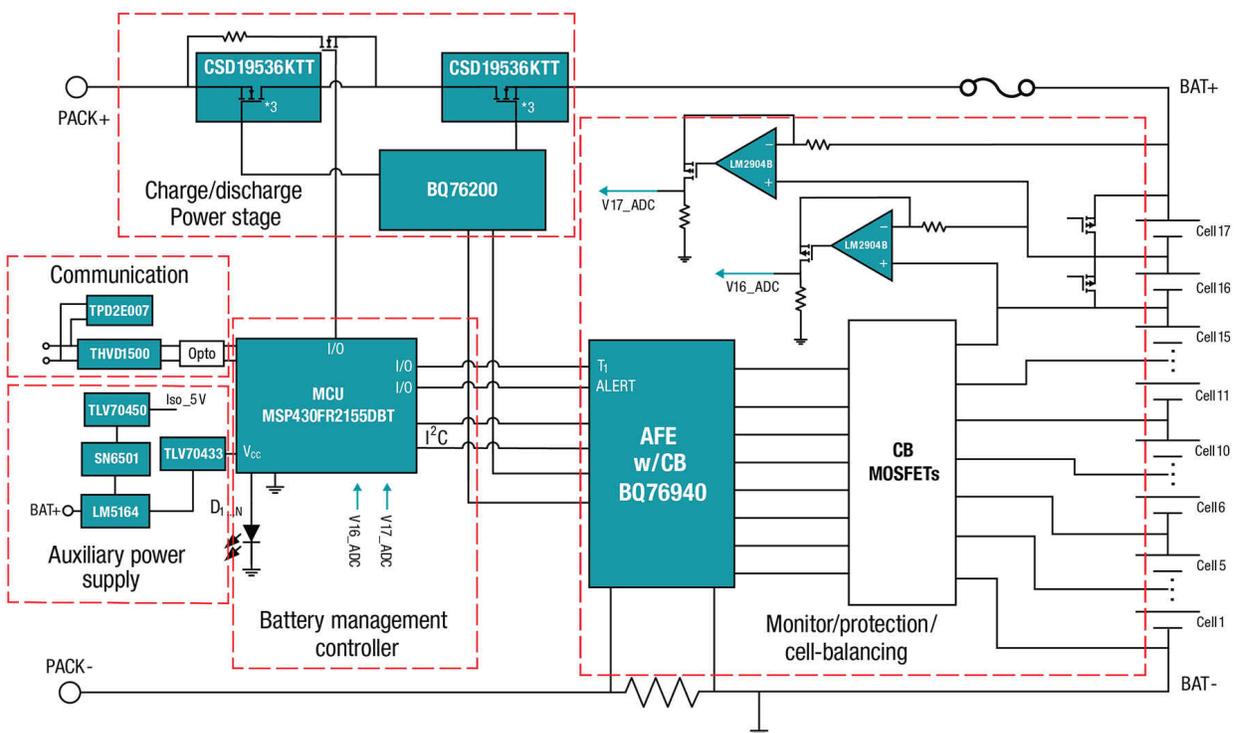


Figure 1. 16S-17S Battery Pack Block Diagram

High Cell Voltage Sensing Accuracy

The [BQ76940](#) monitors the lower 15S battery cells directly and determines the cell voltage accuracy. The typical accuracy is ± 15 mV at 25°C from 3.2 V to 4.6 V. Extra calibration is helpful to improve the accuracy further if necessary. The discrete circuit shown in [Figure 2](#) determines the accuracy of the two upper cells.

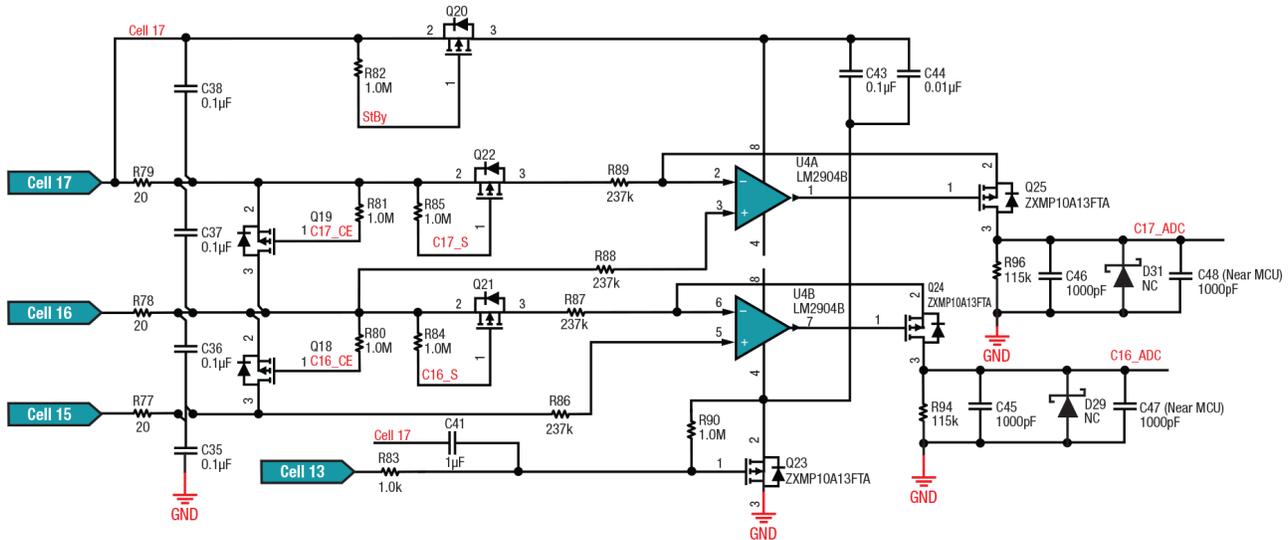


Figure 2. Diagram of the Discrete Circuits for the Two Upper Cells

Let's take the 17th cell as an example. One [LM2904B](#) channel works together with P-channel MOSFET Q25, R89 and R96 as a negative feedback circuit while Q25 works in linear mode. The general-purpose amplifier's negative input voltage is equal to the positive input voltage, which is the voltage of the 16th cell. The 17th cell voltage is across R89 and generates a current that will flow through Q25 and R96 and back to ground, similar to the 16th cell.

The 16th and 17th cell voltages can be monitored by measuring the ADC_16 and ADC_17 voltages with an analog-to-digital converter (ADC). Considering the tolerance of R89, R96, R87, R94 and the ADC reference, two-point calibration is necessary for higher accuracy. [Figure 3](#) shows the two-point calibration process.

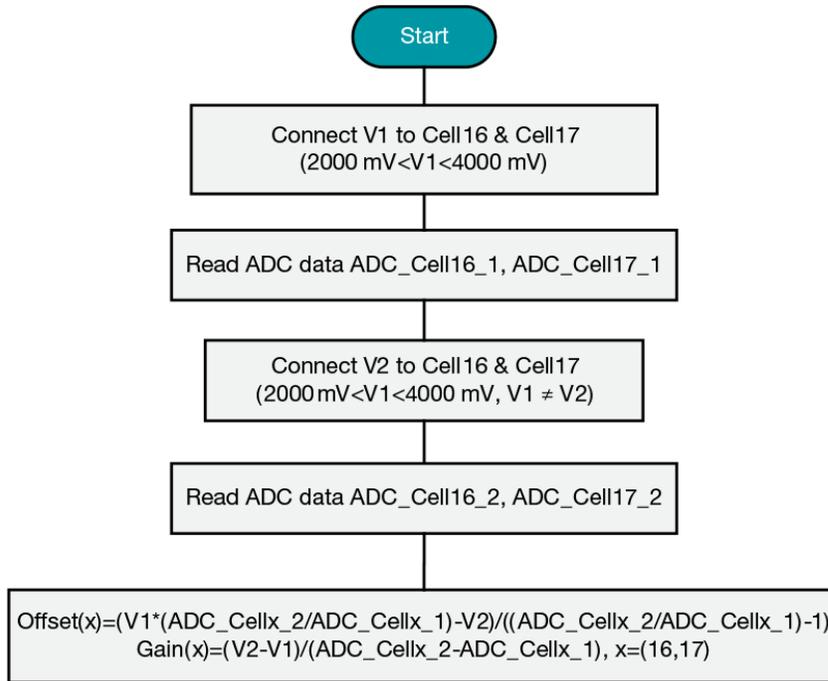


Figure 3. Two-point Calibration Process

In the lab, I tested the 16th and 17th cell voltage accuracy after calibration; the results are shown in [Figure 4](#). The typical accuracy reaches ± 2 mV.

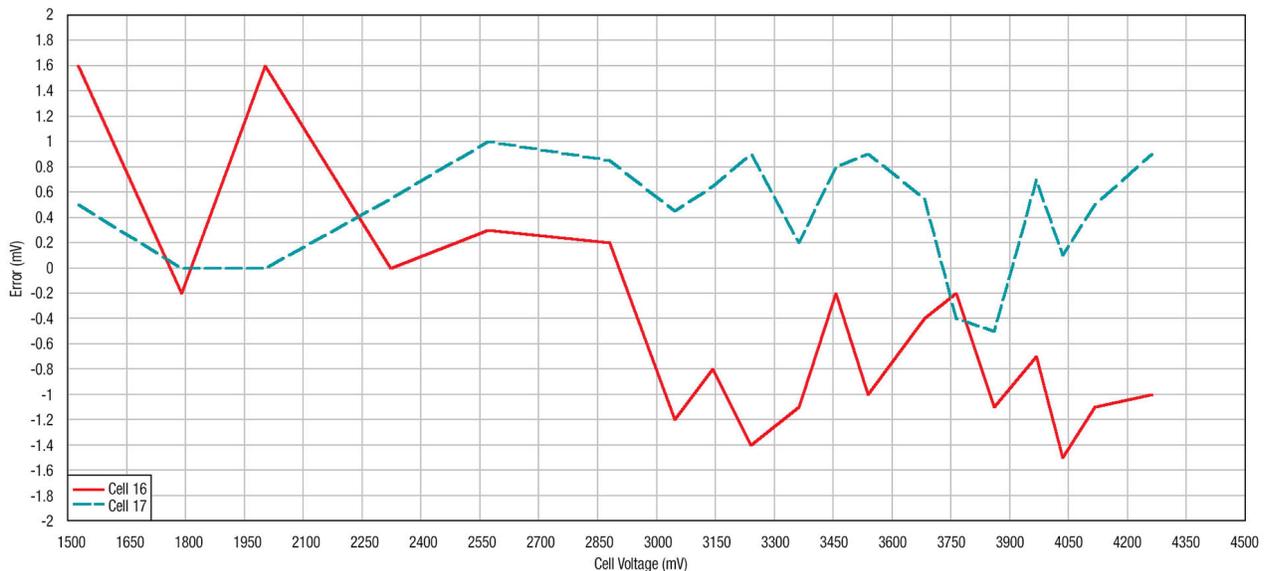


Figure 4. 16th and 17th Cell Voltage Accuracy (at 25°C)

Cell Balancing

Since the 16th and 17th cells are monitored by a discrete circuit and the lower 15 cells are monitored by the BQ76940, you must consider the impact on cell balancing.

Figure 5 shows the main current paths. Red is the general-purpose amplifier power path, green is the 17th cell's sensing path and gray is the 16th cell's sensing path. The general-purpose amplifier power pulls energy from the entire pack and flows back to ground, which discharges the pack and will not cause unbalancing. The 17th cell's sensing path also pulls energy from the entire pack and flows back to ground, which will not cause unbalancing either. But the 16th cell's sensing path pulls energy from the lower 16 series cells only, which will cause a voltage gap between the 17th cell and the lower 16 cells. This unbalancing happens only when sensing the 16th cell voltage.

To reduce unbalancing, turn off Q21 when not sensing the 16th cell – and consider the Q21 control circuit current when calculating the unbalancing effect.

Based on the analysis here and assuming a voltage sensing period of 250 ms, the typical unbalancing current of this battery pack reference design is less than 0.1 μA .

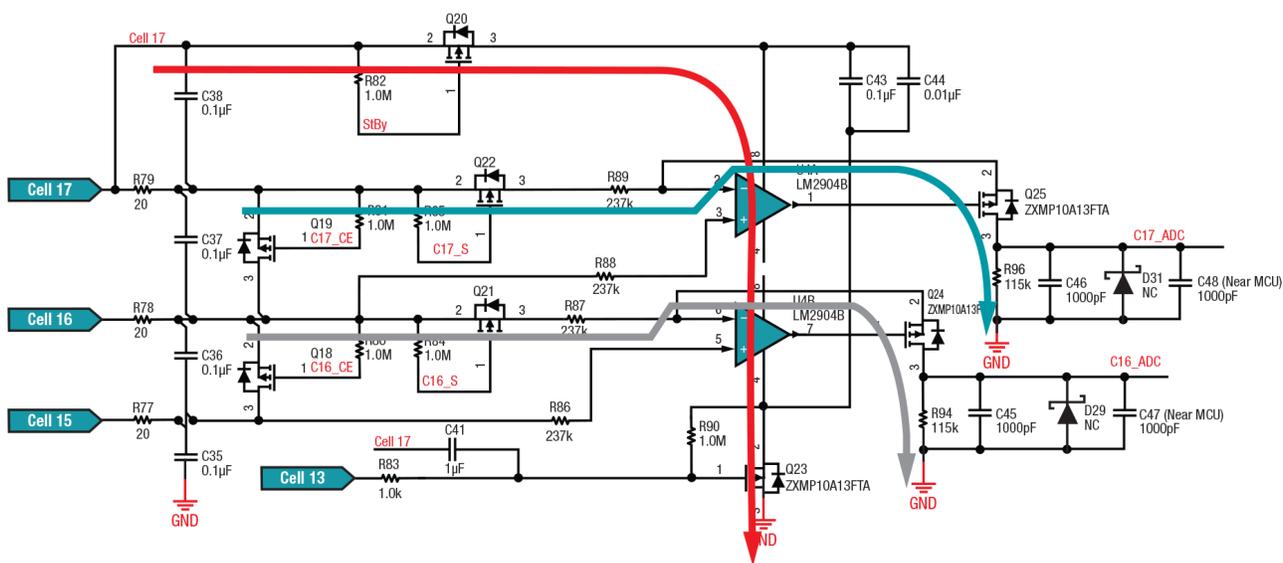


Figure 5. Diagram of the Current Paths of the Discrete Circuit

Low System Standby Current Consumption

In my previous article, “Power to the pedal: Achieving longer-lasting 13S, 48-V lithium-ion battery packs for e-bikes and e-scooters,” I explained how to reduce system-level current consumption in standby mode with the LM5164 and a system-level design. Now, I want to briefly discuss how to reduce current consumption of the discrete circuit in standby mode. There is neither charging nor discharging in standby mode. Cell voltage sensing is for protection and you can normally reduce the frequency by adding idle time. To reduce power consumption in standby mode, you can power off the circuit when voltage sensing is not required.

The solution in Figure 2 uses a P-channel MOSFET Q20 to switch power to the LM2904B and is controlled by a microcontroller. To further reduce current, I added Q22 and Q21 to cut off the cell voltage sensing route and save more energy. Assuming that the voltage sensing period is 250 ms and the idle time is 250 ms, the average current consumption will be quite low in standby. The typical current in the solution shown in Figure 2 is less than 1 μA .

Conclusion

Overall, the reference design offers a cost-competitive battery pack solution that covers cells as high as 17S, which is a good fit for e-motorcycles. The design achieves longer run times by:

- Improving cell voltage sensing accuracy.
- Reducing current consumption in standby mode.
- Eliminating the unbalancing effect.

This design is also suitable for a telecom [battery backup unit](#), which requires a 16S/48-V lithium-iron phosphate battery pack.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated