

Technical Article

The Story of Motor-drive Integration



Wenjia Liu

Just like every MOSFET needs a gate driver to switch it, there's always a driving force behind each motor. Depending on the complexity level and the system's cost, size and performance requirements, there are different ways to drive motors.

The most simple and discrete solution is a totem-pole/push-pull circuit consisting of two transistors. These transistors, which can be different combinations of NPN and PNP transistors, create an amplifier that converts the input logic signal to a high current signal, which in turn switches the MOSFETs and IGBTs on and off. In [Figure 1](#), the emitters are connected to give an amplified output to drive the FET. This kind of solution has been widely used in many different applications including motor drives, mainly due to its low cost and ease of use, but there are still some limitations and drawbacks.

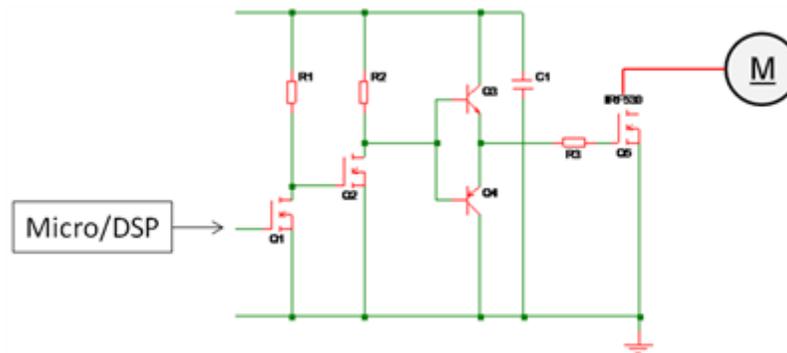


Figure 1. A Typical Push-pull/totem Pole Gate Drive Circuit

For example, the transistors can generate heat, which causes a thermal issue in some systems. Or both transistors can turn on for a short amount of time, which causes circuit shoot-through. For applications with limited PCB space, a totem-pole circuit is not an ideal choice either, as it requires multiple components to realize the gate drive function. For higher output voltages, the solution shown in [Figure 1](#) will require additional level-shift circuitry to achieve the voltage level on the output – and on the input as well, when using a controller that only supplies 5V or less to drive the switch. The transistors and level-shift circuitry increase the bill of materials (BOM) count and required printed circuit board (PCB) space for totem-pole circuit solutions.

A gate-driver integrated circuit (IC) can resolve these issues. Gate-driver ICs implement the same functions as a totem-pole circuit but have many extra benefits:

- A gate-driver IC saves space and resources because it integrates all of the components into a single package. Thus, the physical size is smaller, the design is more straightforward and assembly is easier.
- A gate-driver IC simplifies board layout and reduces design uncertainty, as the data sheet has all of the specifications.
- The drive current is not limited to input base current and gain, so the drive capability is stronger, thus reducing switching losses and increasing efficiency.
- Protection features like under voltage-lockout (UVLO) and “anti-shoot-through” increase system robustness.

Although the totem-pole circuit is a mature solution that has been popular for many years, modern and future systems require higher integration and higher performance. With advances in semiconductor technology, the cost of gate-driver ICs is already comparable to discrete circuits, which makes the IC solution even more attractive and feasible for most applications.

TI offers a broad gate-driver portfolio that can fit in almost all markets and applications. TI's gate drivers support voltages up to 620V for non-isolated solutions and 5kV for isolated solutions. The [LM5109B](#) is a popular solution for motor solutions below 100V. For more details, see the [TI gate driver page](#).

If you prefer an even more integrated solution, there are system-level solutions available that offer not only gate-driving capability but also have MOSFETs, on-chip communication, and different levels of protection and control, all integrated into one chip. These solutions further reduce physical size and design uncertainty. TI's [DRV8xxx series](#), for example, is a popular solution for brushed-DC, brushless-DC and stepper motors. For more information, see the [TI motor driver page](#).

All options have their pros and cons, and you need to choose the one that's the best for your system. Start your design with the various solutions provided by TI and you will find the right one.

Additional Resources

- Check out these motor drive reference designs:
 - [230-V, 3.5-kW PFC with >98% Efficiency, Optimized for BOM and Size Reference Design](#).
 - [18-V/400-W 98% Efficient Compact Brushless DC Motor Drive with Stall Current Limit Reference Design](#).
 - [24V, 100W/30W Dual Sensorless Brushless DC Motor Drive Reference Design](#).
- Download the white paper, "[Power electronics in motor drives: Where is it?](#)"

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated