

# Power Tips: Don't Let a Drooping USB Voltage Slow Down Your Charger



John Betten

Portable devices such as cellphones and tablets are capable of charging their batteries faster than ever. To obtain a fast charge time, the voltage at the charging device must be at the proper level. If it is not, the charger may reduce the charging current to a lower- (but still acceptable) level, ultimately extending the total charge time. Voltage droop across the charging cable can also cause inadequate voltage. Let's take a look at how this might affect a universal serial bus (USB) cable and how to address potential problems.

A typical USB cable interface contact resistance is approximately 30mΩ. Since there are four connections (two on each cable end), this represents 0.12Ω. Assuming a standard 24AWG wire for each power line and a 1m cable length, the total wire resistance is 0.166Ω. The total expected cable and contact resistance is 0.286Ω. If the 5V converter is designed to provide a maximum output current of 2.1A, the expected voltage drop across the cable would be 0.6V. The voltage at the end of the cable would drop to 4.4V for a fixed-converter voltage of 5.0V. This is at the lower voltage limit for USB devices, so it's easy to see how a high-current load can create potential issues. USB cables with heavier gauge wire may help, while extra-long USB cables, with smaller gauge wire, will charge below the maximum rate. Something must be done to increase charging currents further.

A common solution is to raise the output set voltage at no load, typically 5.0V, as high as possible, to 5.15V or 5.20V (5.25V maximum for USB 3.0). This solution provides adequate (although still minimal) headroom at a maximum 2.1A current. But for higher-load currents, this approach quickly runs out of steam.

Another method involves using a dedicated charging port controller such as the [TPS2511](#). This device monitors the USB data lines and automatically provides the correct electrical signatures to charge compliant devices; it also has a current-limiting function. Its current sense (/CS) pin pulls low when the output current is one-half the maximum set by a current-limiting threshold resistor. Connecting this pin through a resistor to the 5V power source's feedback resistors (see [Figure 33 in the TPS2511 data sheet](#)) increases the output voltage, as shown in [Figure 1](#). This reduces the voltage droop by about 50%. See the [Dual-Port Automotive USB Charger Reference Design](#) for an example design.


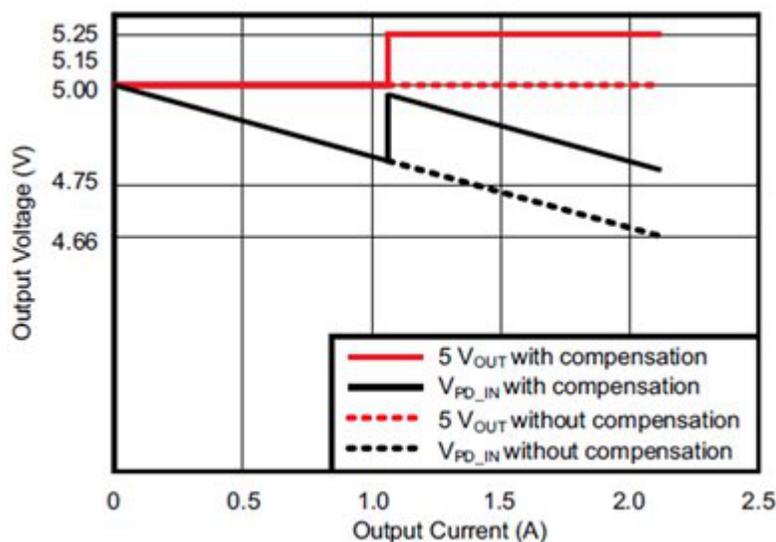


Figure 1. Current Sensing Increases the Output Voltage at 50% Load, Fighting Voltage Droop

The block diagram in [Figure 2](#) details a method to linearly increase the converter's output voltage to compensate for the cable losses, keeping the voltage at the end of the cable constant. This solution adds a sense resistor to monitor the output current. A differential amplifier increases the voltage across the sense resistor and uses this voltage to inject a current into the controller's feedback (FB) pin. For more detail on this approach, see "[Power Tips: Compensate for cable voltage droop](#)".

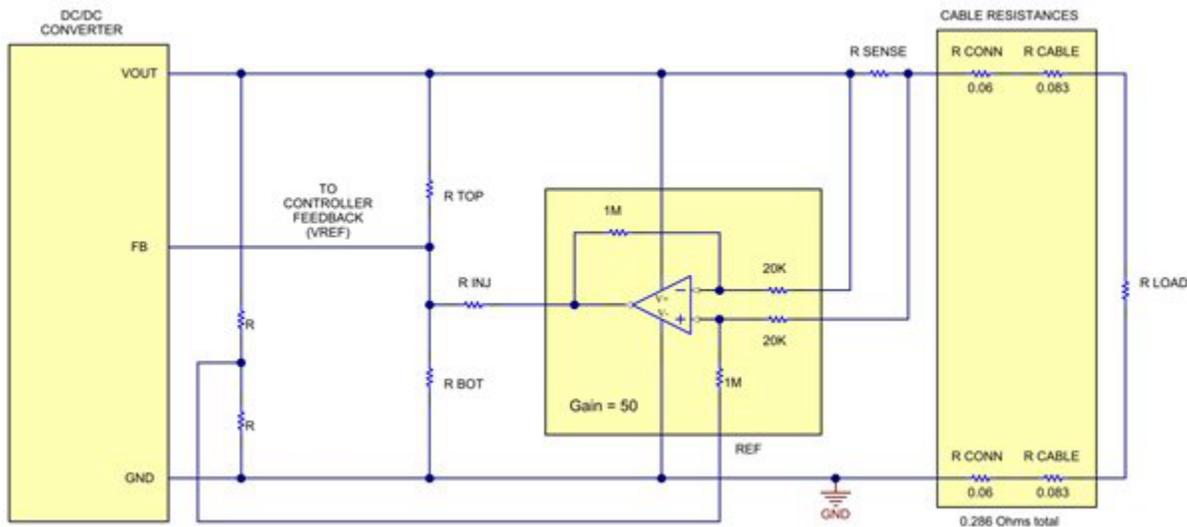

**Figure 2. Current Sensing Continuously Adjusts the Feedback to Hold a Steady Voltage at the Load**

These techniques are just a few ways to fight voltage droop and get the fastest charge time possible.

#### Additional Resources

- Check out TI's [Power Tips blog series](#) on Power House.
- For similar example designs, see [Automotive USB Charger with Linear Droop Compensation Reference Design](#) and [Automotive USB Battery Charging Reference Design](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated