



LM27403 Synchronous Buck Converter

TI reference design number: PMP10691

Input: 12V Output: 3.3V @ 35A

DC – DC Test Results



Table of Contents

1	Circuit Description	3					
2	Photos						
3	Efficiency	5					
4	Thermal Tests	7					
	4.1 Test Setup	7					
	4.2 30A Load, No Airflow						
5	Startup and Shutdown Behavior	9					
	5.1 Turn-on and Turn-off from Vin	9					
	5.2 Turn-on and Turn-off from EN	10					
6	Switching and Ripple	11					
	6.1 Switching and Ripple	11					
7	Load Transient Response	12					
	7.1 Load Transient Response	12					




1 Circuit Description

PMP10691 is a single-phase synchronous buck converter rated for 3.3V output at 35A from an input voltage of 12V. This design uses the LM27403 synchronous buck controller at a switching frequency of 500 kHz. CSD87350Q5D power block MOSFETs provide maximum efficiency when combined with a 250nH ferrite output inductor. The design solution uses all ceramic capacitors to fit into a minimum board area.

All tests were performed at room temperature on an open bench. A 470μ F, 25V aluminum electrolytic input capacitor was used for input filter damping.


2 Photos

The photographs below show the PMP10691 Rev A assembly as built on PMP7935-A printed circuit board. This is a 4 layer board using 2 ounce copper on external layers and 1 ounce copper on internal layers. Power components are mounted on the top side of the board, with the control circuit on the bottom. The overall board dimensions are 2.5" x 2.5". The solution size component area is 1.1" x 0.65". The maximum component height is set by the inductor at 9.4 mm. RevA board requires jumper for NT3 connection which is included in the RevB documentation.

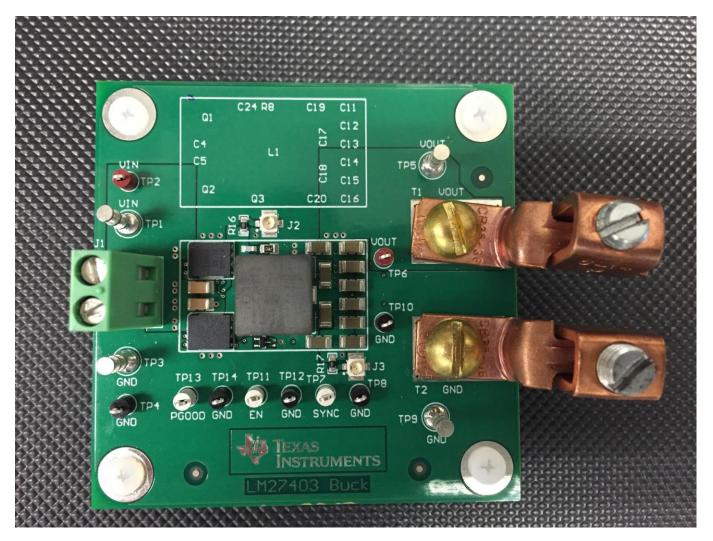

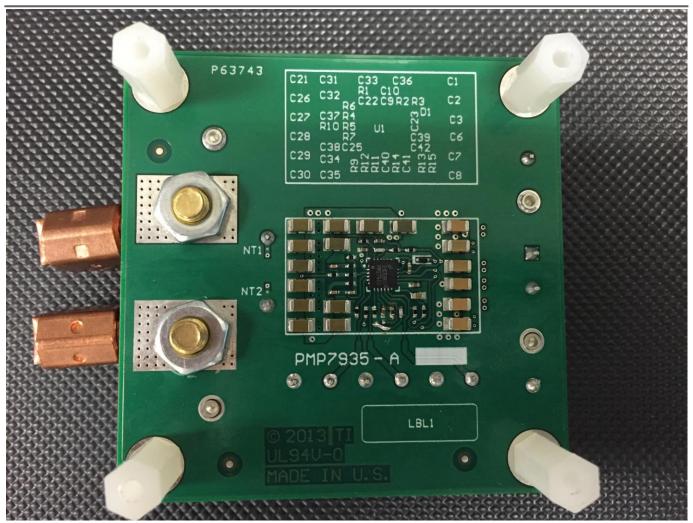Created on: 5/18/2015 Revised on: 5/19/2015 PMP10691 Test Results








3 Efficiency

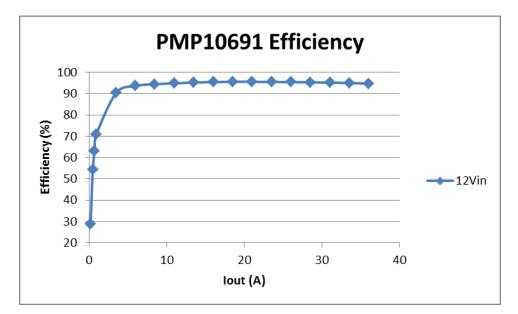The efficiency data is shown in the tables and graph below. Load is incremented above full load to show current limit set point.



Vin(V)	lin(A)	Pin (W)	Vout(V)	lout(A)	Pout (W)	Losses (W)	Efficiency(%)
12.00	0.11	1.26	3.33	0.00	0.00	1.26	0.00
12.00	0.16	1.86	3.33	0.16	0.53	1.33	28.68
12.00	0.23	2.70	3.34	0.44	1.47	1.23	54.34
12.00	0.30	3.60	3.34	0.68	2.27	1.33	62.98
12.00	0.36	4.32	3.34	0.92	3.07	1.25	71.01
12.00	1.07	12.78	3.34	3.46	11.55	1.24	90.33
12.00	1.77	21.24	3.34	5.96	19.89	1.36	93.62
12.00	2.49	29.82	3.34	8.44	28.17	1.65	94.47
12.00	3.21	38.52	3.34	10.94	36.54	1.98	94.85
12.00	3.94	47.28	3.34	13.48	45.04	2.25	95.25
12.00	4.67	55.98	3.34	15.98	53.42	2.56	95.42
12.00	5.39	64.68	3.34	18.48	61.80	2.88	95.54
12.00	6.12	73.44	3.35	20.98	70.18	3.26	95.56
12.00	6.87	82.44	3.35	23.52	78.72	3.72	95.49
12.00	7.61	91.31	3.35	26.02	87.14	4.17	95.43
12.00	8.36	100.31	3.35	28.52	95.57	4.74	95.27
12.00	9.11	109.30	3.35	31.02	104.04	5.26	95.19
12.00	9.87	118.42	3.36	33.52	112.49	5.93	95.00
12.00	10.65	127.72	3.36	36.04	121.02	6.70	94.76
12.00	11.42	136.95	3.36	38.56	129.56	7.38	94.61
12.00	12.19	146.24	3.36	41.04	137.94	8.31	94.32

Created on: 5/18/2015 Revised on: 5/19/2015 PMP10691 Test Results



12.00	12.97	155.54	3.36	43.56	146.45	9.09	94.15
12.00	13.76	165.06	3.36	46.08	154.92	10.14	93.86
12.00	14.55	174.48	3.36	48.58	163.33	11.16	93.61
12.00	15.34	184.00	3.36	51.08	171.78	12.22	93.36
12.00	16.15	193.66	3.36	53.58	180.24	13.42	93.07
11.99	16.98	203.66	3.36	56.12	188.79	14.87	92.70
12.00	0.11	1.26	0.00	2.02	0.01	1.25	0.64




4 Thermal Tests

All tests were performed at room temperature on an open bench.

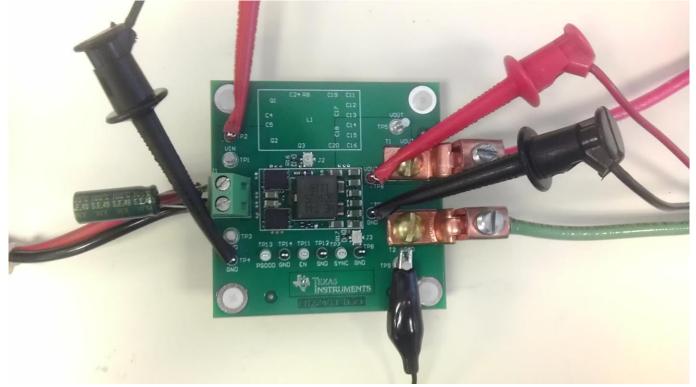
4.1 Test Setup

Thermal data was taken with a Fluke handheld thermal camera.





4.2 35A Load, No Airflow

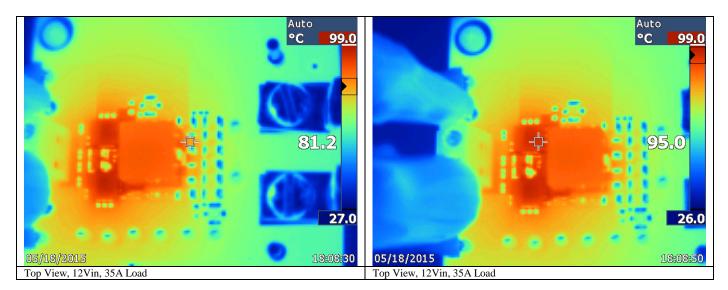




5 Startup and Shutdown Behavior

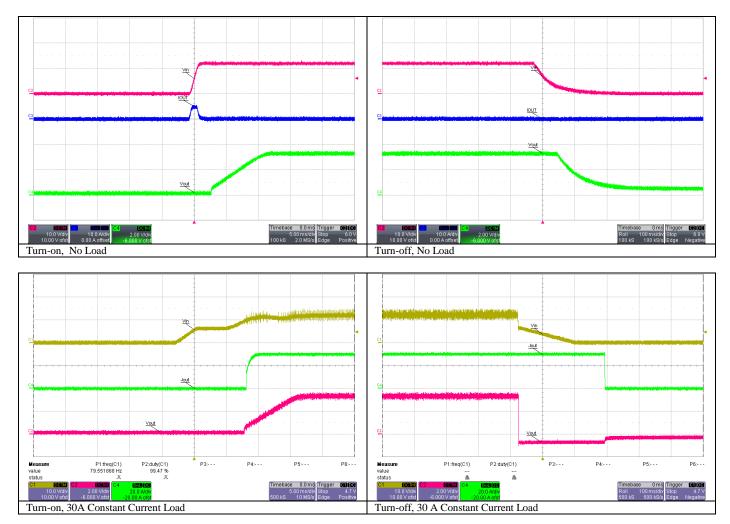5.1 Turn-on and Turn-off from Vin


The output voltage is well controlled at turn-on, showing no evidence of over-shoot.






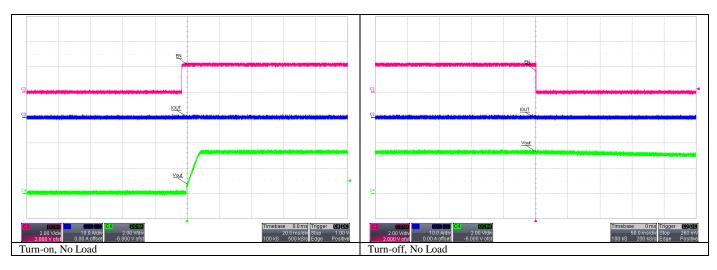5.2 Turn-on and Turn-off from EN

The output voltage is well controlled at turn-on, showing no evidence of over-shoot.



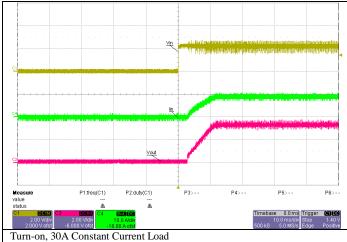




6 Switching and Ripple

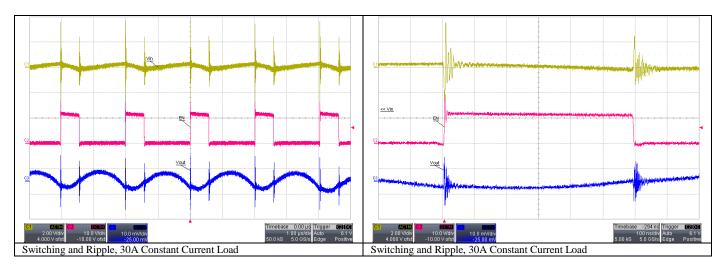6.1 Switching and Ripple

Switching and ripple tests were made with a 470µF, 25V aluminum electrolytic input capacitor for input filter damping.






7 Load Transient Response

Load transient response for each condition was taken at two points to represent the minimum and maximum deviation. This difference occurs when the transient step coincides with either the converter off-time or on-time interval.

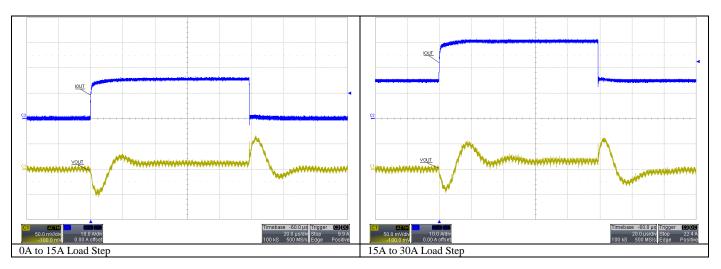7.1 Load Transient Response

The output voltage transient is within 60mV for a 15A load step.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated