

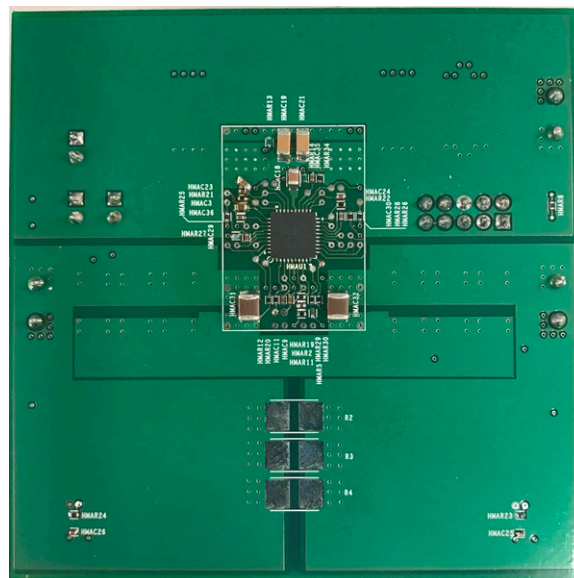
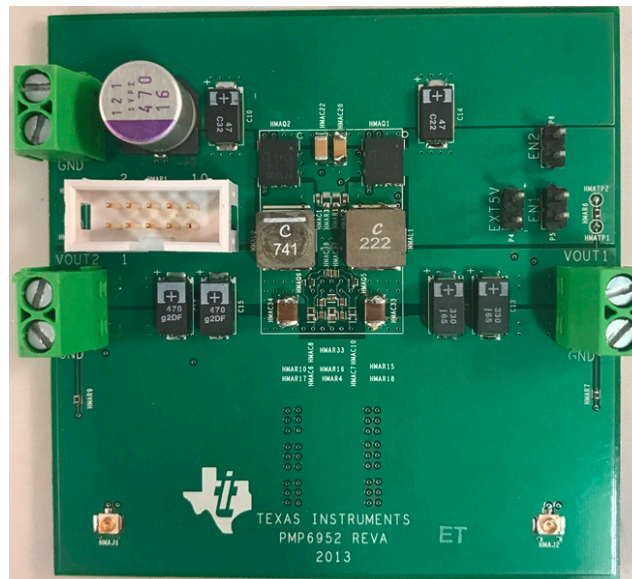
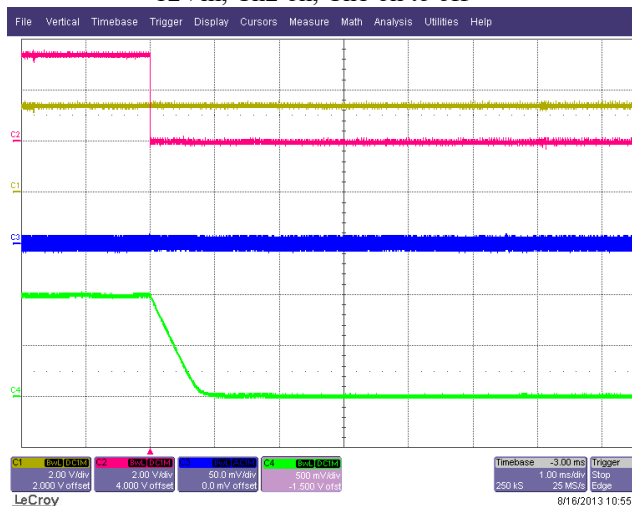
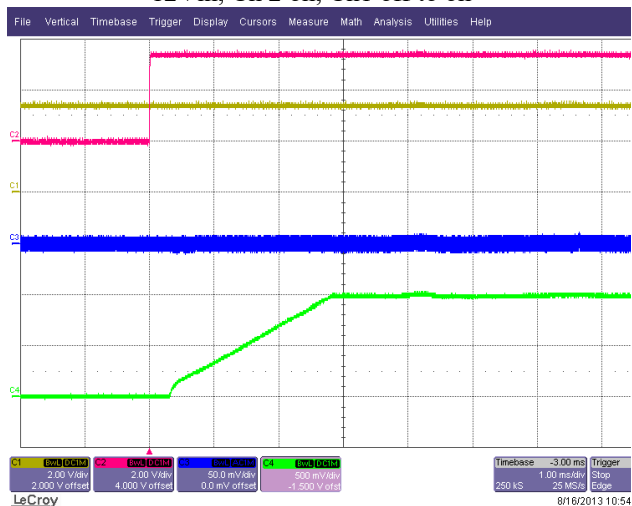


Photo of the prototype

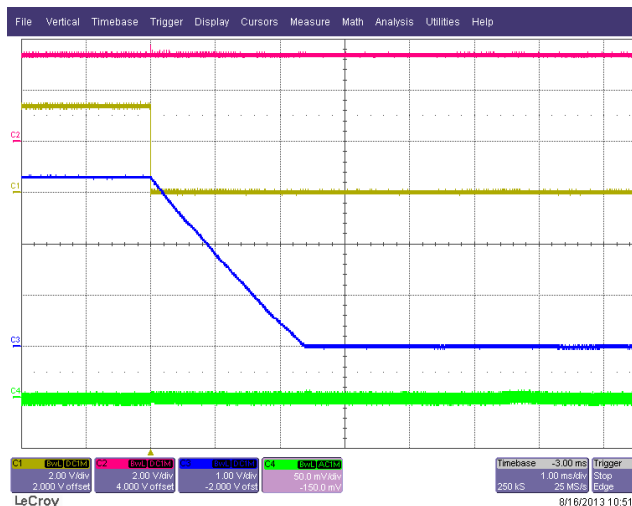


1 Startup and shutdown

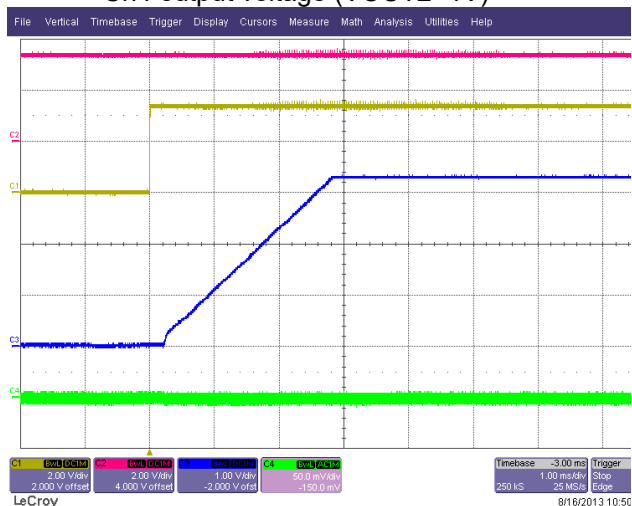- Ch1 enable signal EN1
- Ch2 enable signal EN2
- Ch3 output voltage (VOUT1=3.3V)
- Ch4 output voltage (VOUT2=1V)




2 Output Ripple

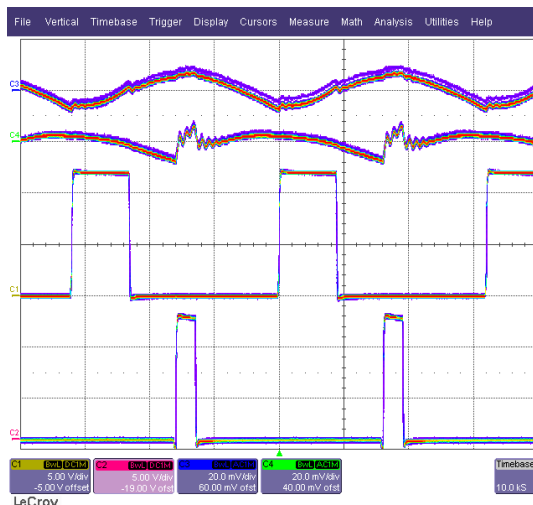- Ch1 Switch-node (3.3V)
- Ch3 Output voltage (AC coupling)
- Ch2 Switch-node (1V)
- Ch4 Output voltage (AC coupling)



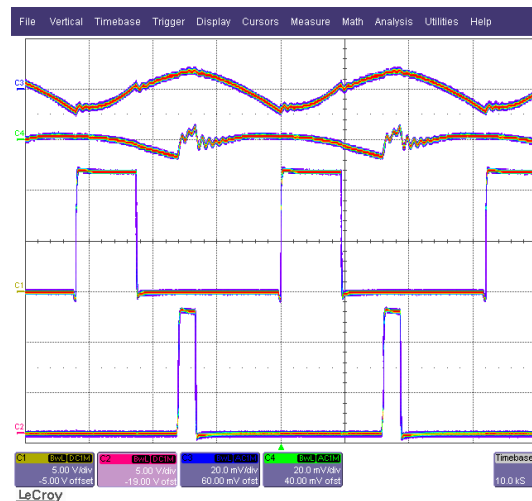
12Vin, Ch1 at 3.3V/1.2A, Ch2 at 1V/15A (Cout2=2x 100uF, 6.3V, 1210+2x470uF, 4V, 10mohm, 7343), VOUT2=16mVpp




12Vin, Ch1 at 3.3V/12A, Ch2 at 1V/1.5A (Cout1=2x 100uF, 6.3V, 1210+2x330uF, 6.3V, 45mohm, 7343), VOUT1=20mVpp

3 Transient

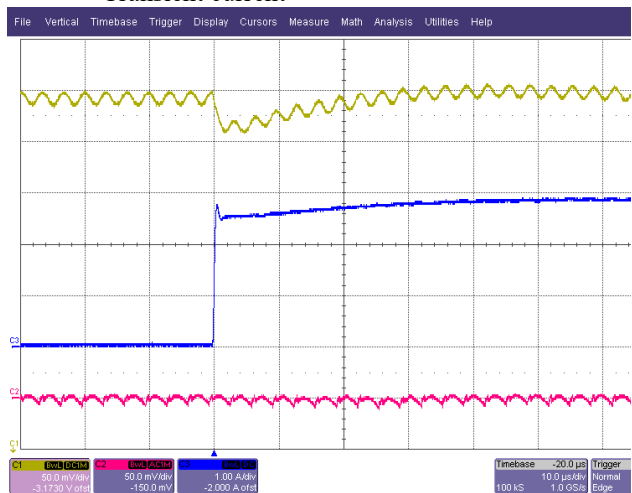
- Output voltage of channel undergoing transient test (DC coupling)
- Output voltage of channel with static load (AC coupling)
- Transient current



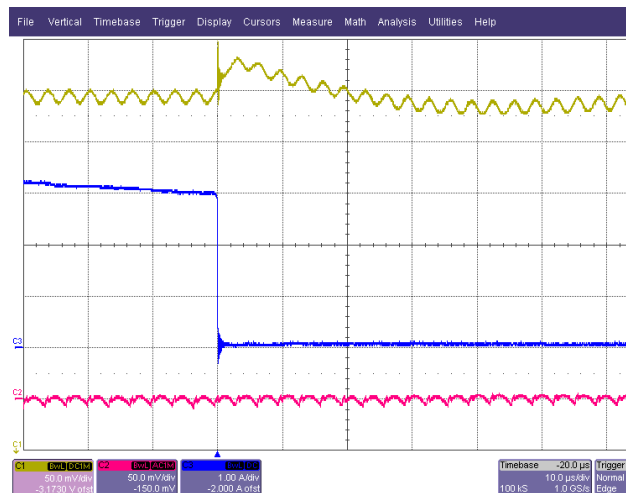12Vin, Ch1 3.3V/9A to 12A Load Step, Ch2 1V/7.5A static load (-30mV)





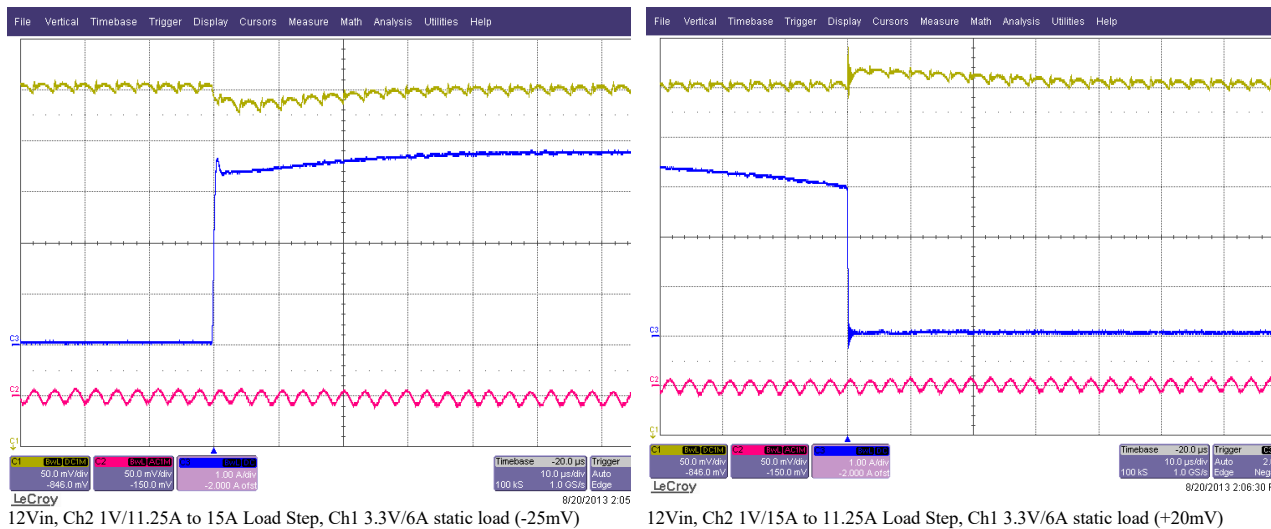12Vin, Ch1 3.3V/12A to 9A Load Step, Ch2 1V/7.5A static load (+30mV)




4 Over-Current protection

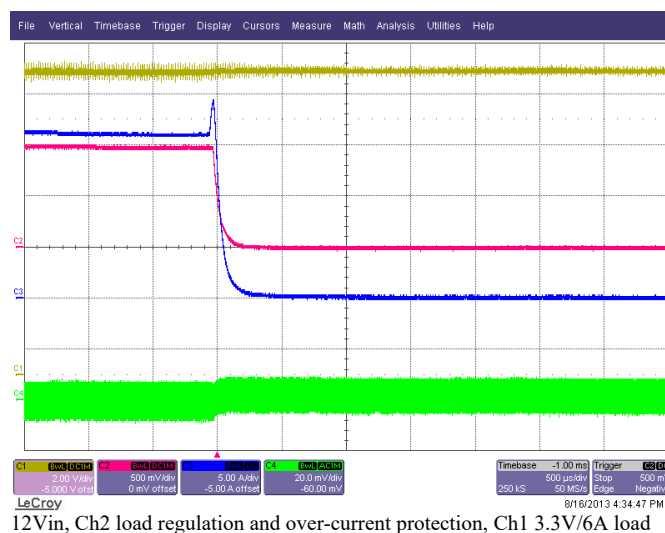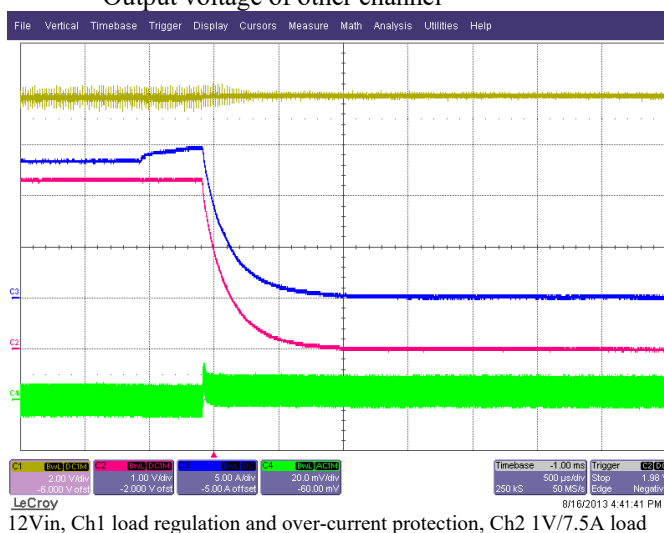- Input voltage
- Output voltage of channel under test
- Load current
- Output voltage of other channel




5 Short-Circuit Protection

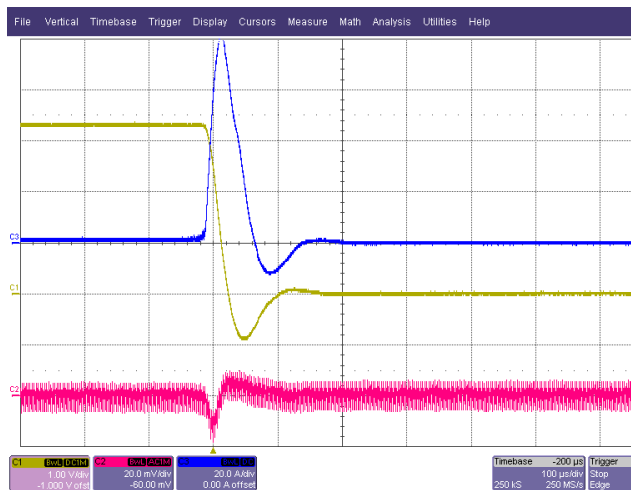
- Output voltage of channel being shorted
- Output voltage of other channel
- Short-circuit current




12Vin, Ch1, Short circuit applied

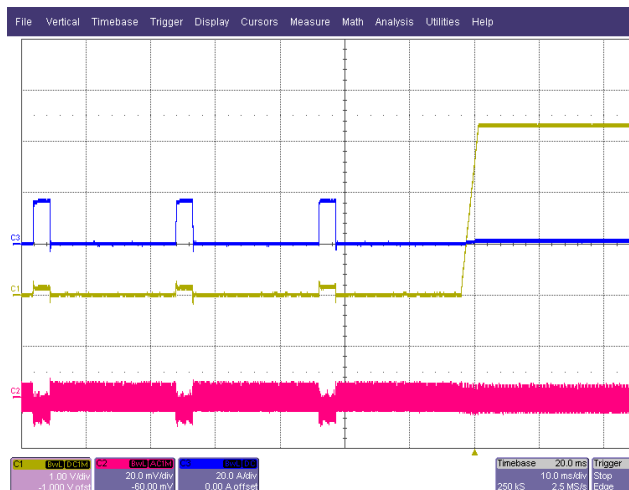

12Vin, Ch1, Short circuit released


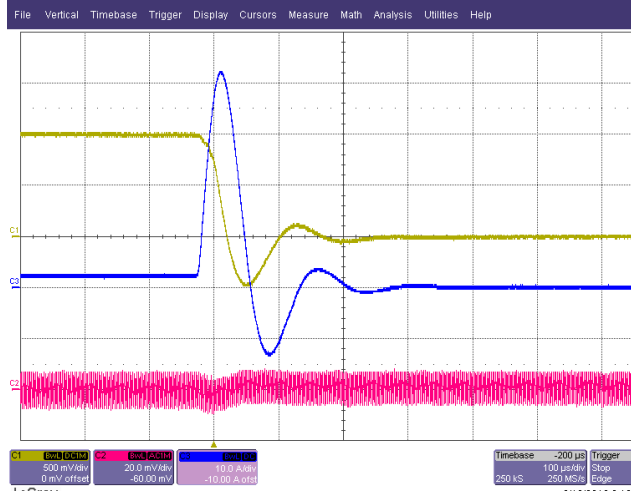




12Vin, Ch2, Short circuit applied

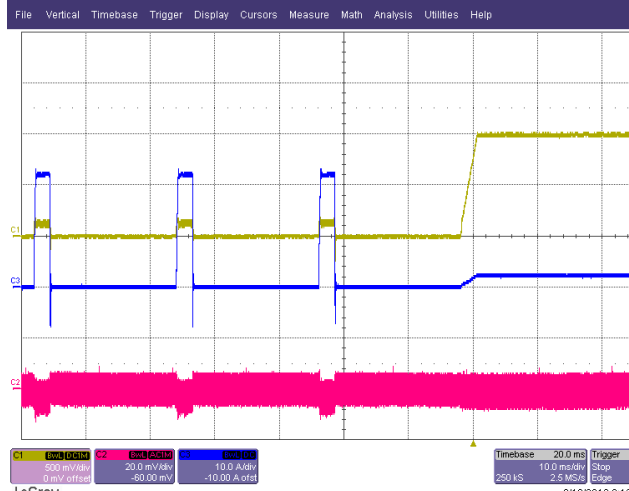


12Vin, Ch2, Short circuit released

6 Bode Plot

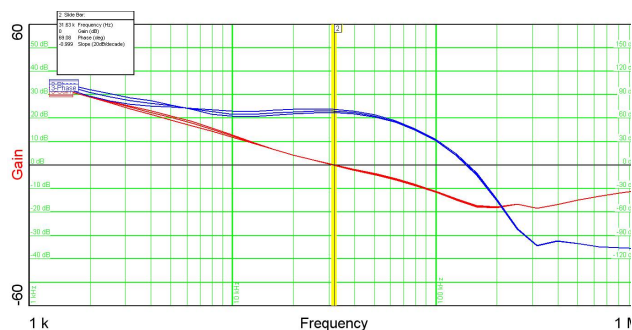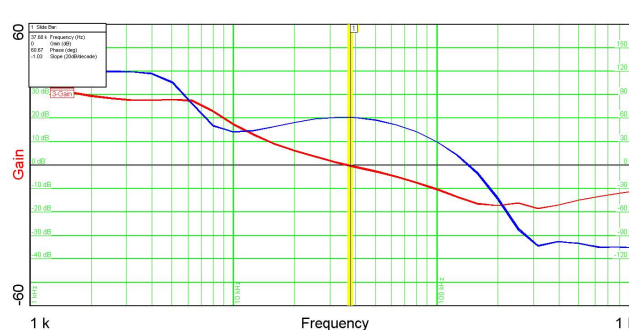
8, 10, 12Vin, 1.0Vout, 10% Load($f_c=31.6k$, $pm=69$, $gm=16db$)8, 10, 12Vin, 1.0Vout, 100% Load($f_c=37.7k$, $pm=60.7$, $gm=15db$)

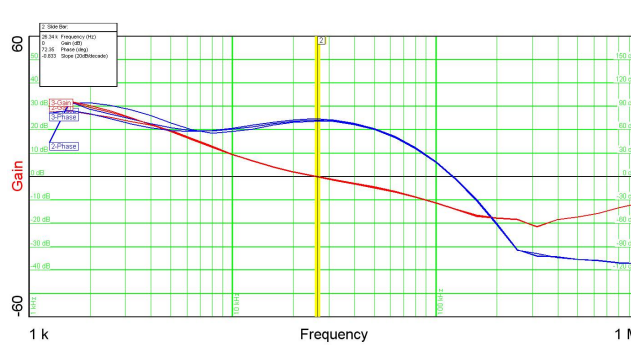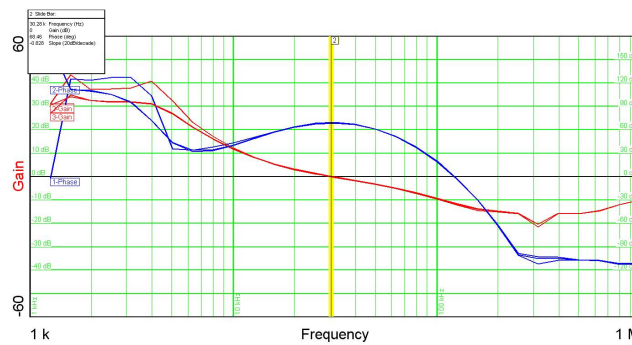8,10,12Vin, 3.3Vout, 10% Load($f_c=26.3k$, $pm=72.4$, $gm=13db$)8,10,12Vin, 3.3Vout, 100% Load($f_c=30.3k$, $pm=68.5$, $gm=12db$)

7 Efficiency

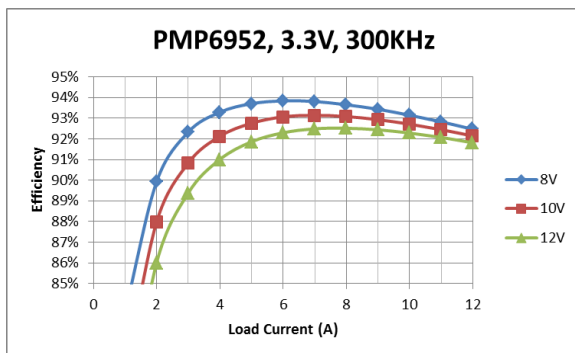

3.3V efficiency @300kHz

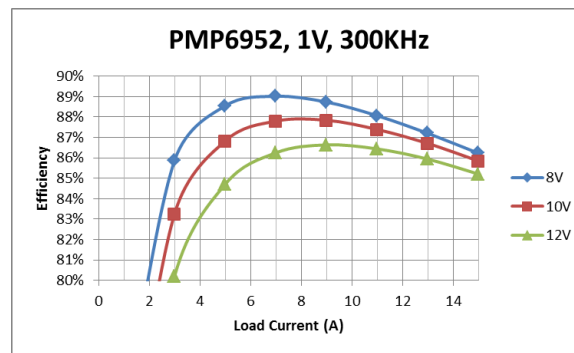

1.0V efficiency @300kHz

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated