

An Improved Line Regulation Solution Used In LM3444/ LM3445 Nonisolated LED Lighting Application

Richard Yang

China Power FAE

ABSTRACT

This paper details the full operation principle based on the traditional nonisolated solution with LM3445. The targeted line regulation formula is derived and analyzed. The result has been verified from the results of a practical experiment, and they matched very closely. To evaluate the feasibility in mass production, the output current tolerance is fully investigated and analyzed. The result proves that it is difficult for the traditional solution to meet the total mass production current tolerance, especially in the higher output application as required by the current market tendency.

To solve this problem, a simple line regulation compensation circuit is proposed. This proposed solution is verified both from theoretical calculation and experiment measurement results. Based on the formula of output current and line regulation rate derived, the final total current tolerance is analyzed for the practical mass production requirement. From the result, we find there is a great improvement toward meeting the practical requirement. Finally, the test result and calculation result are compared based on the prototype; it is proven that they matched well.

Contents

1	Introduction	3
2	The Principle of Traditional Nonisolated LM3444/LM3445 Solution	3
3	Analysis of LED Current Line Regulation Based On the Traditional Solution	5
	3.1 The Delta LED Current Variation Analysis During Mass Production	6
	3.2 The LED Current Tolerance Analysis During Mass Production	7
4	Design Example Verification On the Line Regulation and Mass Production Current Tolerance Based On the Traditional Solution	8
5	Principle of Improved Nonisolated LM3444/LM3445 Solution	13
	Conclusion	19
	References	20

Figures

Figure 1.	Traditional Proposed Nonisolated Solution With High PF	4
Figure 2.	Frequency of No Improved Solution With Less Than 90 Vac and 140 Vac	8
Figure 3.	Output Current of No Improved Solution Less Than 90 Vac and 140 Vac	9
Figure 4.	Simulation Result of Inductor Current and Output Current Less Than 90 Vac	9
Figure 5.	Test Result of Inductor Current and Output Current Less Than 90 Vac	9
Figure 6.	Simulation Result of Inductor Current and Output Current Less Than 140 Vac	10
Figure 7.	Test Result of Inductor Current and Output Current Less Than 140 Vac	10
Figure 8.	Output Current of No Improved Solution Less Than 90 Vac and 140 Vac	11

Figure 9.	LED Output Current Variation Influenced by the Components Tolerance of No Improved Solution Less Than 90 Vac to 140 Vac	11
Figure 10.	Total LED Current Tolerance of No Improved Solution Less Than 90 Vac to 140 Vac When Mass Production.....	12
Figure 11.	Improved Line Compensation Circuit	13
Figure 12.	Temperature Sweep Simulation Result Less Than 0°C, 25°C, 50°C, 85°C	13
Figure 13.	Frequency Less Than 90 Vac and 140 Vac	15
Figure 14.	Inductor Current Less Than 90 Vac and 140 Vac	15
Figure 15.	Test Result of Inductor Current and Output Current Less Than 90 Vac.....	15
Figure 16.	Test Result of Inductor Current and Output Current Less Than 140 Vac.....	16
Figure 17.	Line Regulation Calculation Has Been Improved to Less Than $\pm 1\%$	16
Figure 18.	Calculation of worst-case Current Tolerance Has Been Improved to $\pm 6.6\%$	17
Figure 19.	Circuit to Improve Line Regulation Less Than 120 Vac to 140 Vac	18
Figure 20.	Voltage of Pin 5 on LM3445/LM3444 When Figure 20 Circuit is Added	18
Figure 21.	Line Regulation Has Been Improved More After Using Figure 19 circuit.	18
Figure 22.	Total Solution With the Optional way to Improve the Line Regulation Greatly	19

1 Introduction

With the increasing growth in LED indoor lighting, the nonisolated scheme, along with the isolated scheme, has become more popular. Specifically, the scheme of higher PF and precise constant current mode with high line regulation has become the dominant issue on the market. However, with output voltage becoming higher and wider, the traditional LM3444/L3445 nonisolated application cannot achieve this requirement with enough margin, which may further limit the application of LM3445/LM3445.

In view of the above-mentioned issue, the major objective of this paper focuses on the higher output application with precise line regulation requirement. In this paper, the general operation principle is illustrated through the formulas in Chapter 2, with which the final output current can be solved. To evaluate the result, Chapter 3 provides the uniform formula into which the output current is simplified; Chapter 3 also gives and further detailed current tolerance analysis. Chapter 4 gives the design example based on the prototype. The calculation result, together with simulation result, is provided to make the contrast with the experiment result; it is proven they match very well. However, with further investigation, it is still difficult to meet the current tolerance for mass production.

To solve this problem, the proposed compensation circuit is presented in chapter 5. This compensation circuit is verified both through calculation and simulation and experimentation. Ultimately, experiments demonstrate that the circuit greatly improves the line regulation and current tolerance performance, with which the improved line regulation will become more competitive in the practical application, especially in the LED R30/PAR30/A19/E27 LED lighting applications.

2 The Principle of Traditional Nonisolated LM3444/LM3445 Solution

Figure 1 is presented as the traditional nonisolated solution with higher PF achievement. To convenient the operation principle, the parameters are defined as follows:

- V_{out} : Output voltage of LED
- I : Equivalent value of time within a single period
- K_{feed} : Feed ward coefficient of input AC voltage
- R_s : Resistor for current sense
- R_{up} : Charge resistor for t_{off}
- C_{char} : Charge capacitor for t_{off}
- V_{inmin} : Minimum of AC input voltage
- V_{inmax} : Maximum of AC input voltage
- V_{inac} : AC input voltage
- $_noimp$: Functions with no improved line regulation circuit

_imp: Functions with improved line regulation circuit

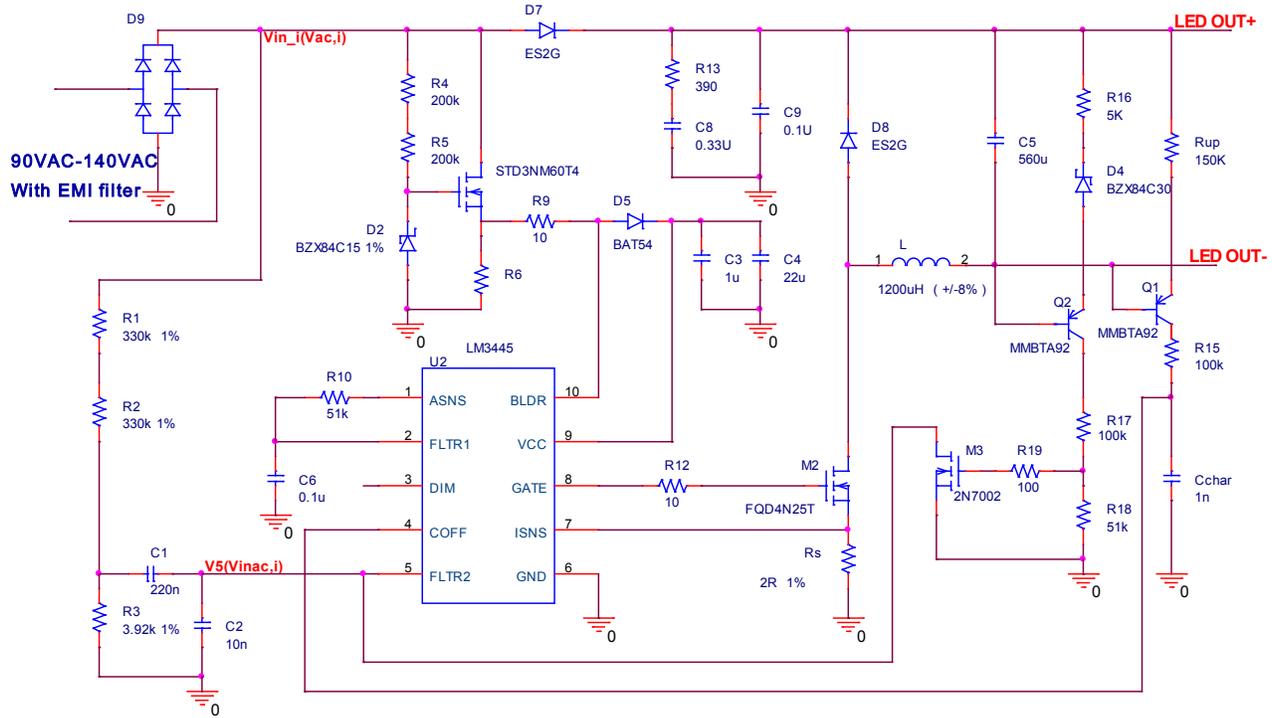


Figure 1. Traditional Proposed Nonisolated Solution With High PF

This is typically the application without feedback loop, but it can achieve the following characteristic:

1. Higher PF. This is achieved through input feed forward circuit.
2. Constant current. This is achieved through the t_{off} circuit sensed through LED output voltage.

The AC input voltage can be expressed as follows:

$$V_{in}(t) = \sqrt{2} \cdot V_{inac} \cdot |\sin(\omega t)| \tag{1}$$

As shown as Figure 1, C1 is bigger than C2 in order to achieve higher PF value, for example: C1/C2 = 220n/10n. The voltage for pin 5 on the LM3444 or LM3445 can be expressed as:

$$V_s(t) = \sqrt{2} \cdot V_{inac} \cdot |\sin(\omega t)| \cdot k_{feed} - \frac{2\sqrt{2} \cdot V_{inac} \cdot k_{feed}}{\pi} + 0.75 \tag{2}$$

$$k_{feed} = \frac{R3}{R1 + R2 + R3}$$

The charge current for t_{off} can be obtained as follows:

$$I_{char_noimp}(t) = \frac{V_{out} - V_{eb_Q1}}{R_{up}} \tag{3}$$

On practical calculation, V_{be_Q1} can choose 0.6 as the reference design.

So, t_{off} can be written as:

$$T_{off_noimp}(t) = \frac{C_{char} \cdot 1.276}{I_{char_noimp}(t)} \quad (4)$$

The frequency can be expressed as follows

$$F_{sw_noimp}(t) = \frac{1 - \frac{V_{out}}{V_{in}(t)}}{T_{off_noimp}(t)} \quad (5)$$

$(V_{out} \leq V_{in}(t))$

The ripple current through the inductor is obtained as:

$$\Delta i_{noimp}(t) = \frac{T_{off_noimp}(t) \cdot V_{out}}{L} \quad (6)$$

So, the maximum current and average inductor current formula can be written as:

$$I_{L_max}(t) = \frac{V_5(t)}{R_s} \quad (7)$$

$(V_{out} \leq V_{in}(t))$

$$I_{avg_noimp}(t) = \frac{V_5(t)}{R_s} - 0.5 \cdot \Delta i_{noimp}(t) \quad (8)$$

$(V_{out} \leq V_{in}(t))$

Then the LED output current can be obtained as follows:

$$\Delta I_{out_noimp}(t) = \frac{1}{T_{rec}} \cdot \int_0^{T_{rec}} I_{avg_noimp}(t) \cdot dt \quad (9)$$

3 Analysis of LED Current Line Regulation Based On the Traditional Solution

As the LED current is derived above, we can write the total formula as follows:

$$I_{out_noimp}(V_{inac}) = \left(0.75 - \frac{2\sqrt{2} \cdot V_{inac} \cdot k_{feed}}{\pi} - \frac{0.5V_{out} \cdot C_{char} \cdot 1.276 \cdot R_s}{L} \cdot \frac{\pi - 2 \arcsin\left(\frac{V_{out}}{\sqrt{2}V_{inac}}\right)}{\pi \cdot R_s} + \frac{V_{out} - V_{be_Q1}}{R_{up}} \right)$$

$$2\sqrt{2} \cdot V_{inac} \cdot \frac{k_{feed}}{\pi \cdot R_s} \cdot \sqrt{1 - \frac{V_{out}^2}{2 \cdot V_{inac}^2}} \quad (10)$$

To derive the LED current variation per input voltage, formula (10) will be simplified because V_{out} is normally much smaller than V_{inac} , and V_{out} is much higher than V_{be_Q2} . The simplification is obtained as follows:

$$I_{out_noimp}(V_{inac}) = \left(0.75 - \frac{2\sqrt{2} \cdot V_{inac} \cdot k_{feed}}{\pi} - \frac{0.5C_{char} \cdot 1.276 \cdot R_s \cdot R_{up}}{L} \right) \cdot \frac{\pi - \frac{\sqrt{2}V_{out}}{V_{inac}}}{\pi \cdot R_s} + 2\sqrt{2} \cdot V_{inac} \cdot \frac{k_{feed}}{\pi \cdot R_s} \quad (11)$$

Then the LED current variation within the whole input range can be derived from formula (11).

$$\Delta I_{out_noimp} = \left(0.75 - \frac{0.5C_{char} \cdot 1.276 \cdot R_s \cdot R_{up}}{L} \right) \cdot \frac{\sqrt{2}V_{out}}{\pi \cdot R_s} \cdot \left(\frac{1}{V_{acmin}} - \frac{1}{V_{acmax}} \right) \quad (12)$$

It can be seen that the LED current variation depends greatly on the V_{out} , which means that it can be with the higher line regulation when the LED voltage is low, in which case it is very suitable for GU10 application.

3.1 The Delta LED Current Variation Analysis During Mass Production

Because the LED current variation is derived as shown in formula (11) however, this variation is influenced by the tolerance of R_s , L , C_{char} , and R_{up} during the whole input range. It has been investigated per the mass production requirement as follows:

1. The Delta LED current variation influenced by R_s (for example: 2% tolerance) when mass production is as follows:

$$\Delta(\Delta I_{out_Rs}) = \frac{-\sqrt{2} \cdot 0.75 \cdot V_{out} \cdot \Delta R_s}{\pi \cdot R_s^2} \cdot \left(\frac{1}{V_{acmin}} - \frac{1}{V_{acmax}} \right) \quad (13)$$

2. The Delta LED current variation influenced by R_{up} (for example: 2% tolerance) when mass production is as follows:

$$\Delta(\Delta I_{out_R_{up}}) = \frac{-0.5 \cdot C_{char} \cdot 1.276 \cdot \Delta R_{up}}{L} \cdot \frac{\sqrt{2} \cdot V_{out}}{\pi} \cdot \left(\frac{1}{V_{acmin}} - \frac{1}{V_{acmax}} \right) \quad (14)$$

3. The Delta LED current variation influenced by C_{char} (for example: 10% tolerance) when mass production is as follows:

$$\Delta(\Delta I_{out_C_{char}}) = \frac{-0.5 \cdot \Delta C_{char} \cdot 1.276 \cdot R_{up}}{L} \cdot \frac{\sqrt{2} \cdot V_{out}}{\pi} \cdot \left(\frac{1}{V_{acmin}} - \frac{1}{V_{acmax}} \right) \quad (15)$$

4. The Delta LED current variation by L (for example: 16% tolerance) when mass production is as follows:

$$\Delta(\Delta I_{out_L}) = \frac{0.5 \cdot C_{char} \cdot \Delta L \cdot 1.276 \cdot R_{up}}{L^2} \cdot \frac{\sqrt{2} \cdot V_{out}}{\pi} \cdot \left(\frac{1}{V_{acmin}} - \frac{1}{V_{acmax}} \right) \quad (16)$$

5. The worst case Delta LED current variation under a certain Vled when mass production is as follows:

$$\Delta(\Delta I_{out_total}) = \left| \Delta(\Delta I_{out_Rs}) \right| + \left| \Delta(\Delta I_{out_Rup}) \right| + \left| \Delta(\Delta I_{out_Cchar}) \right| + \left| \Delta(\Delta I_{out_L}) \right| \quad (17)$$

Normally, this total variation is very small compared to the LED current variation.

3.2 The LED Current Tolerance Analysis During Mass Production

In mass production, the LED current is specified. It is normally required to be within $\pm 5\%$ regardless of the tolerance of Vled, kfeed, L, Cchar, and Rup during the whole input range.

From formula (9), we can see that the LED current variation is influenced by these parameters. The following details this analysis.

1. The LED current variation influenced by Rs (for example: 2% tolerance) when mass production is as follows:

$$\Delta I_{out_Rs_noimp}(Vinac) = \left(0.75 - \frac{2\sqrt{2} \cdot Vinac \cdot k_{feed}}{\pi} \right) \cdot \frac{0.02 \left(\pi - 2 \arcsin \left(\frac{V_{out}}{\sqrt{2} Vinac} \right) \right)}{\pi \cdot Rs} + 2\sqrt{2} \cdot Vinac \cdot \frac{0.02 \cdot k_{feed}}{\pi \cdot Rs} \quad (18)$$

2. The LED current variation influenced by Rup (for example: 2% tolerance) when mass production is as follows:

$$\Delta I_{out_Rup_noimp}(Vinac) = \frac{0.5 C_{char} \cdot 1.276 R_s \cdot R_{up}}{L} \cdot \frac{0.02 \left(\pi - 2 \arcsin \left(\frac{V_{out}}{\sqrt{2} Vinac} \right) \right)}{\pi \cdot R_s} \quad (19)$$

3. The LED current variation influenced by Cchar (for example: 10% tolerance) when mass production is as follows:

$$\Delta I_{out_Cchar_noimp}(Vinac) = \frac{0.5 C_{char} \cdot 1.276 R_s \cdot R_{up}}{L} \cdot \frac{0.1 \left(\pi - 2 \arcsin \left(\frac{V_{out}}{\sqrt{2} Vinac} \right) \right)}{\pi \cdot R_s} \quad (20)$$

4. The total LED current variation by L (for example: 16% tolerance) when mass production is as follows:

$$\Delta I_{out_L_noimp}(Vinac) = \frac{0.5 C_{char} \cdot 1.276 R_s \cdot R_{up}}{L} \cdot \frac{0.16 \left(\pi - 2 \arcsin \left(\frac{V_{out}}{\sqrt{2} Vinac} \right) \right)}{\pi \cdot R_s} \quad (21)$$

5. The total LED current variation by kfeed (for example: 2% tolerance) when mass production is as follows:

$$\Delta I_{out_kfeed_noimp}(Vinac) = \frac{-2\sqrt{2} \cdot Vinac \cdot k_{feed}}{\pi} \cdot \frac{0.02 \left(\pi - 2 \arcsin \left(\frac{Vout}{\sqrt{2} Vinac} \right) \right)}{\pi \cdot Rs} + 2\sqrt{2} \cdot Vinac \cdot \frac{0.02 \cdot k_{feed} \cdot \sqrt{1 - \frac{Vout^2}{2 \cdot Vinac^2}}}{\pi \cdot Rs} \tag{22}$$

6. The worst-case LED current variation under a certain Vled when mass production is as follows:

$$\Delta I_{out_total_noimp} = \Delta I_{out_Rs_noimp}(Vinac) + \Delta I_{out_Rup_noimp}(Vinac) + \Delta I_{out_Cchar_noimp}(Vinac) + \Delta I_{out_L_noimp}(Vinac) + \Delta I_{out_kfeed_noimp}(Vinac) \tag{23}$$

Then the total LED current tolerance can be expressed as follows as mass production requirement:

$$\Delta I\%_{out_noimp}(Vinac) = \frac{\Delta I_{out_total_noimp} + \Delta I_{out_noimp} + \Delta(\Delta I_{out_total})}{I_{out_noimp}(Vinac)} \tag{24}$$

4 Design Example Verification On the Line Regulation and Mass Production Current Tolerance Based On the Traditional Solution

To verify the validation of above derived calculation result, a prototype is made as the parameters listed in Table 1.

Parameters	Value	Parameters	Value
Rs	2.2	k1	0.098
L	1.1 mh	Kfeed	3.939 m
Rup	270K	Cchar	470 p
Vled	30	R1 comp	600 K

Table 1. Parameters for the Prototype

Using formula (5) in Chapter 2, obtain the frequency curve as shown in Figure 2:

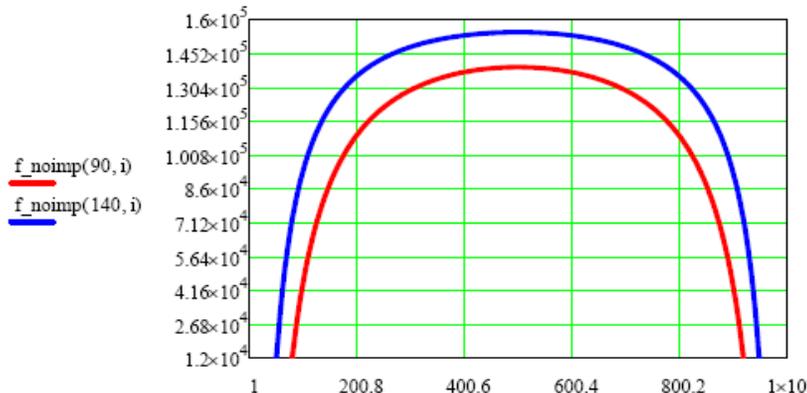


Figure 2. Frequency of No Improved Solution With Less Than 90 Vac and 140 Vac

Using formulas (7) and (8) in Chapter 2, obtain the maximum current and average current through the inductor (see Figure 3):

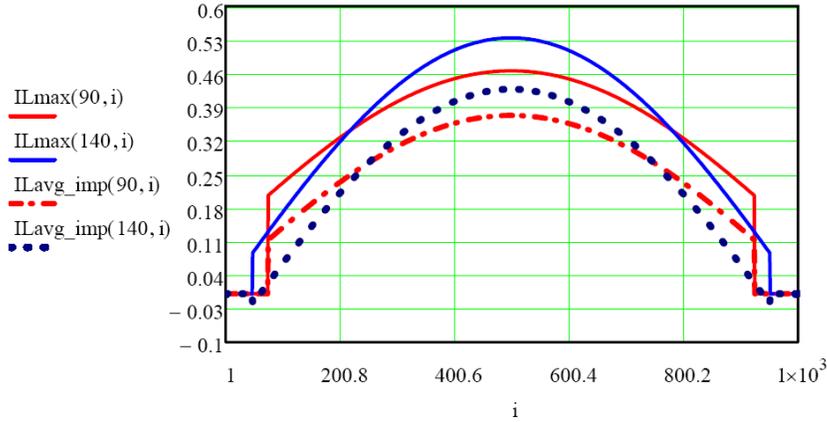


Figure 3. Output Current of No Improved Solution Less Than 90 Vac and 140 Vac

Figure 4 and Figure 5 show the simulation and experiment results less than 90 Vac and 140 Vac.

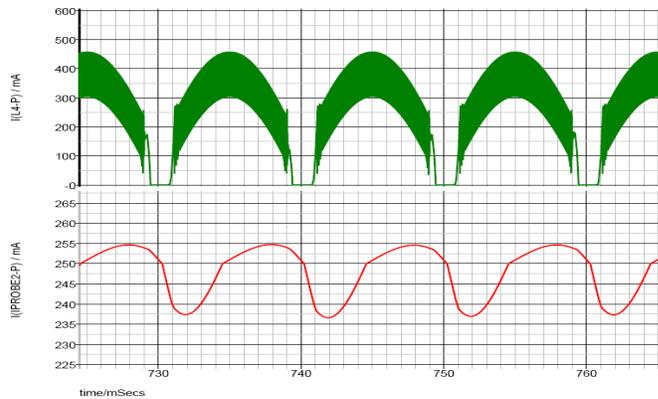


Figure 4. Simulation Result of Inductor Current and Output Current Less Than 90 Vac

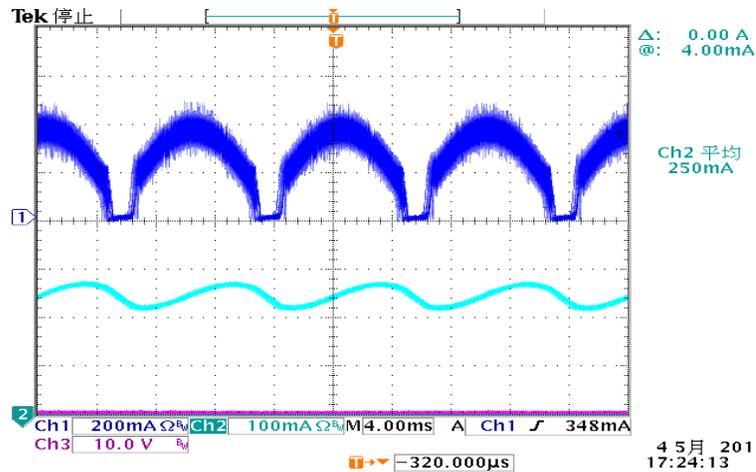


Figure 5. Test Result of Inductor Current and Output Current Less Than 90 Vac

The measured and simulated current waveforms (see Figure 4 and Figure 5) are nearly identical; the output ripple has shown a small difference due to the difference between LED simulation model and practical testing LED load.

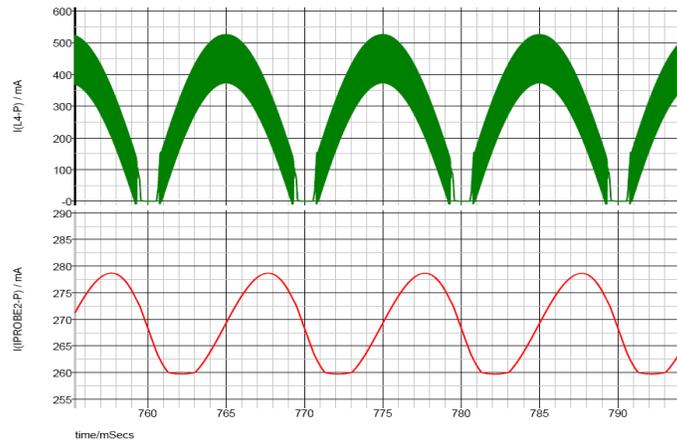


Figure 6. Simulation Result of Inductor Current and Output Current Less Than 140 Vac

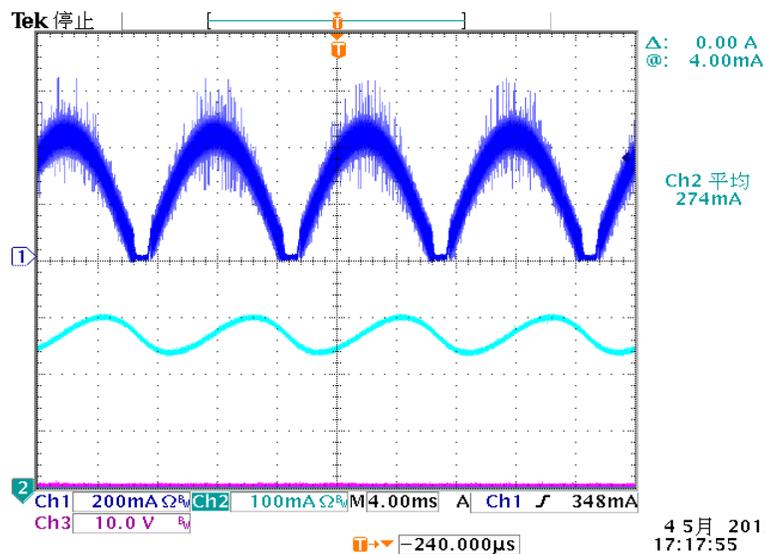


Figure 7. Test Result of Inductor Current and Output Current Less Than 140 Vac

From the results in Figure 6 and Figure 7, it seems that the calculation results closely match the simulation results and practical measured results. This finding provides the strong theoretical support for the following tolerance analysis.

Using formula 9 in Chapter 2, calculate the normal output current; obtain the maximum and the minimum output current, after considering the parameters tolerance, during mass production as follows:

$$\Delta I_{o_noimp_max}(Vinac) = I_{out_noimp}(Vinac) + 0.5\Delta I_{out_total_noimp}(Vinac) \tag{25}$$

$$\Delta I_{o_noimp_min}(Vinac) = I_{out_noimp}(Vinac) - 0.5\Delta I_{out_total_noimp}(Vinac) \tag{26}$$

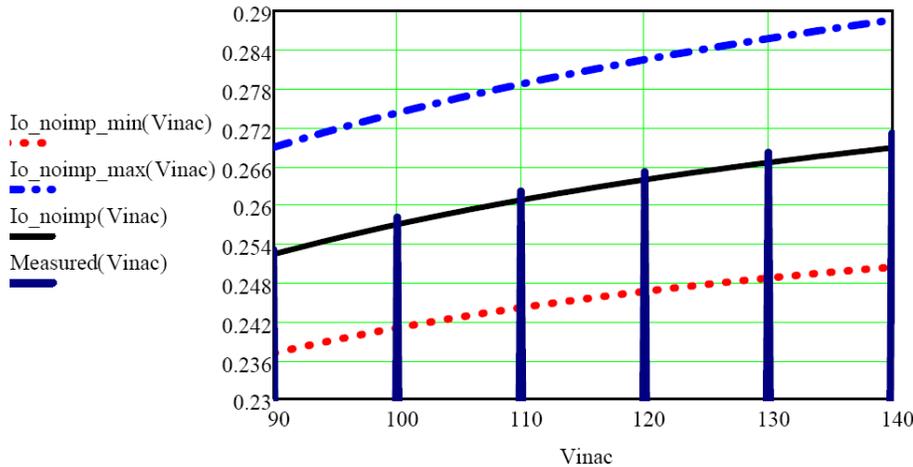


Figure 8. Output Current of No Improved Solution Less Than 90 Vac and 140 Vac

Using formula (23) in Section 3.2, obtain the worst-case LED current variation after considering the parameters tolerance during mass production (see Figure 9).

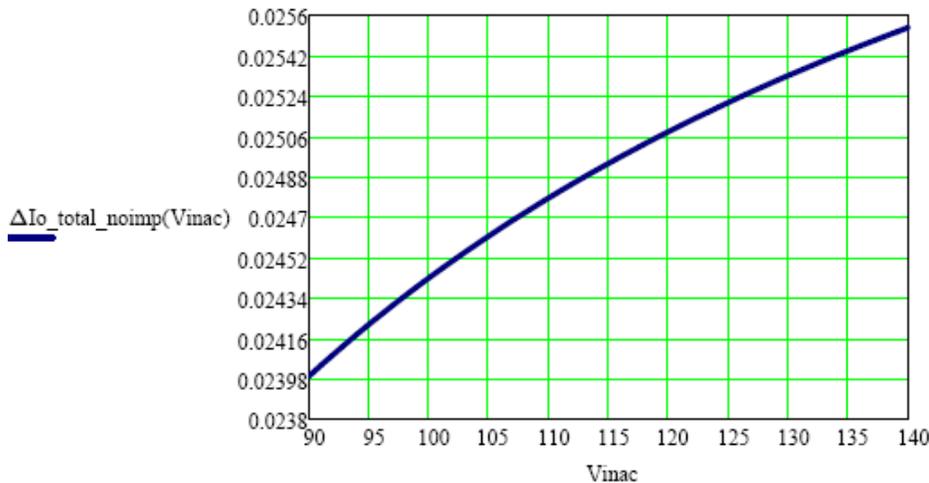


Figure 9. LED Output Current Variation Influenced by the Components Tolerance of No Improved Solution Less Than 90 Vac to 140 Vac

Using formula (24) of 3.2, obtain the total LED current tolerance during mass production (see Figure 10):

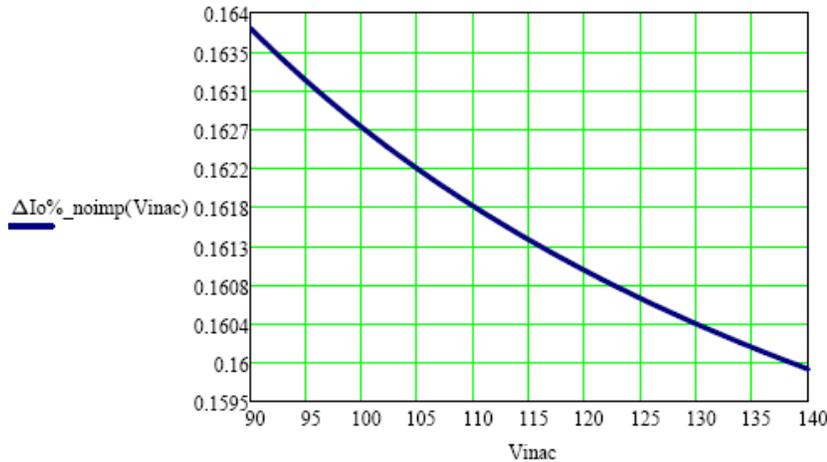


Figure 10. Total LED Current Tolerance of No Improved Solution Less Than 90 Vac to 140 Vac When Mass Production

From formula (24), we can see the normal LED current variation above 90 Vac to 140 Vac is 17 mA, the line regulation is $\pm 3.3\%$, it is acceptable for the single unit. The primary concern in practical engineering, however, is the total regulation feasibility, namely the total LED current tolerance after the component tolerance is considered. From Figure 8, it can be seen that the output current variation influenced by the components tolerance is about 32 mA. So the total LED current tolerance when mass production is above $\pm 8\%$, as shown as Figure 10. This is also hard to implement in practical production. From above analysis, we know the line regulation is the key to improve the total tolerance during the input range.

5 Principle of Improved Nonisolated LM3444/LM3445 Solution

To improve the line regulation, the line compensation shown in Figure 11 is proposed.

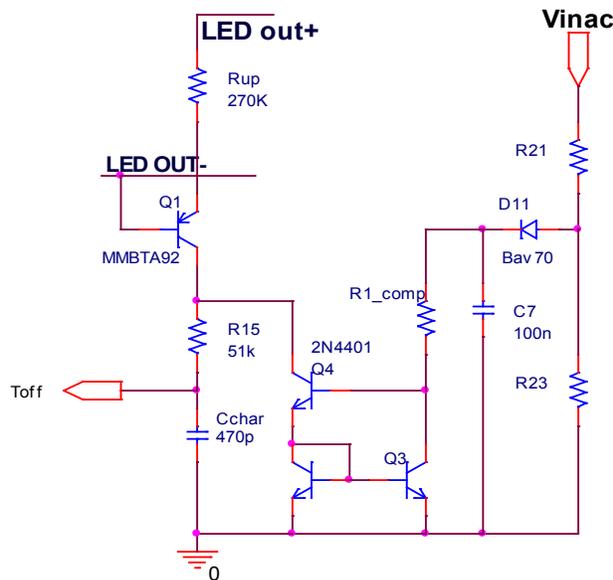


Figure 11. Improved Line Compensation Circuit

To reduce the latched current tolerance as the circuit shown in Figure 11, the higher precise resistors R21, R23, and R1_comp are used. To reduce the effect of forward voltage of D11, Q3, and Q4, the voltage on C7 is proposed to be a little high (for example, 20 Vdc). To know the current tolerance under a different temperature, the spice-based temperature sweep simulation is conducted when defining V_C7 as 20 V, V_c of Q4 as 20 V, and R_comp as 300K. Figure 12 shows the result.

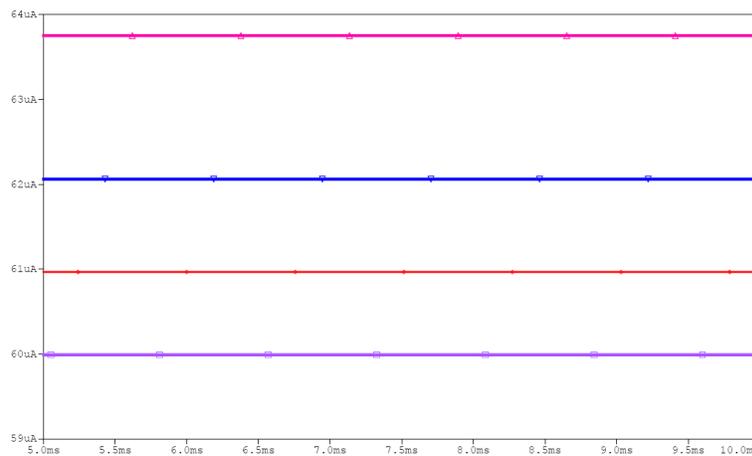


Figure 12. Temperature Sweep Simulation Result Less Than 0°C, 25°C, 50°C, 85°C

From the result, the temperature tolerance is seen as $\pm 3\%$, so it is feasible to put it into the practical design.

After incorporating the compensation circuit (see Figure 11), the charge current for the improved t_{off} can be obtained as follows:

$$I_{char_imp}(t) = \frac{V_{out} - V_{eb_Q1}}{R_{up}} - \frac{\sqrt{2} \cdot k \cdot Vinac - 2V_{be}}{R_{1_comp}} \quad (27)$$

To decrease the effect of V_{be} of Q3 and Q4 (shown in Figure 11), it is advised that the coefficient k in formula (27) is as high as possible so that we can ignore the V_{be} in the design.

The maximum current and average inductor current formulas are the same as formulas (7) and (8) in Chapter 2. The final LED current formula can be obtained as follows:

If no other component tolerance is considered, the normalized formula for the output LED current can be expressed as follows:

$$I_{out_imp}(Vinac) = \left(0.75 - \frac{2\sqrt{2} \cdot Vinac \cdot k_{feed}}{\pi} - \frac{\frac{0.5V_{out} \cdot C_{char} \cdot 1.276 \cdot Rs}{L}}{\frac{V_{out} - V_{eb_Q1}}{R_{up}} - \frac{\sqrt{2} \cdot k \cdot Vinac}{R_{1_comp}}} \right) \cdot \frac{\pi - 2 \arcsin\left(\frac{V_{out}}{\sqrt{2}Vinac}\right)}{\pi \cdot Rs} + 2\sqrt{2} \cdot Vinac \cdot \frac{k_{feed}}{\pi \cdot Rs} \cdot \sqrt{1 - \frac{V_{out}^2}{2 \cdot Vinac^2}} \quad (28)$$

In practical calculation, we can define the 0.95 Char, 0.99 Rs, 0.99 Rup, 1.08 L, 0.99 kfeed to obtain the maxim LED output current. The formula is as follows:

$$I_{out_imp_max}(Vinac) = \left(0.75 - \frac{2\sqrt{2} \cdot Vinac \cdot 0.99 \cdot k_{feed}}{\pi} - \frac{\frac{0.5V_{out} \cdot C_{char} \cdot 0.95 \cdot 0.99 \cdot 1.276 \cdot Rs}{1.08L}}{\frac{V_{out} - 0.6}{0.99R_{up}} - \frac{\sqrt{2} \cdot k \cdot 0.99Vinac}{R_{1_comp}}} \right) \cdot \frac{\pi - 2 \arcsin\left(\frac{V_{out}}{\sqrt{2}Vinac}\right)}{\pi \cdot 0.99Rs} + 2\sqrt{2} \cdot Vinac \cdot \frac{k_{feed}}{\pi \cdot Rs} \cdot \sqrt{1 - \frac{V_{out}^2}{2 \cdot Vinac^2}} \quad (29)$$

Using the same analysis, we can define the 1.05 Char, 1.01 Rs, 1.01 Rup, 0.92 L, 1.01 kfeed to obtain the minim LED output current. The formula is as follows:

$$I_{out_imp_min}(Vinac) = \left(0.75 - \frac{2\sqrt{2} \cdot Vinac \cdot 1.01 \cdot k_{feed}}{\pi} - \frac{\frac{0.5V_{out} \cdot C_{char} \cdot 1.05 \cdot 1.01 \cdot 1.276 \cdot Rs}{0.92L}}{\frac{V_{out} - 0.6}{1.01R_{up}} - \frac{\sqrt{2} \cdot k \cdot 1.01Vinac}{R_{1_comp}}} \right) \cdot \frac{\pi - 2 \arcsin\left(\frac{V_{out}}{\sqrt{2}Vinac}\right)}{\pi \cdot 1.01Rs} + 2\sqrt{2} \cdot Vinac \cdot \frac{k_{feed}}{\pi \cdot Rs} \cdot \sqrt{1 - \frac{V_{out}^2}{2 \cdot Vinac^2}} \quad (30)$$

Then we can obtain the following calculation regarding the frequency range and inductor current waveform.

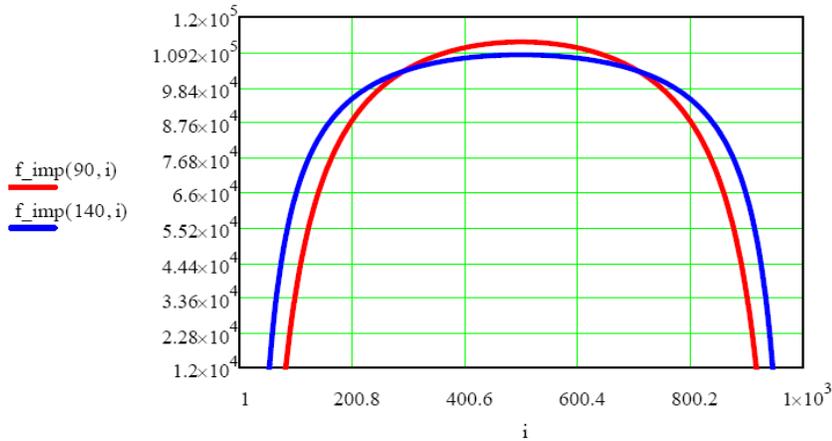


Figure 13. Frequency Less Than 90 Vac and 140 Vac

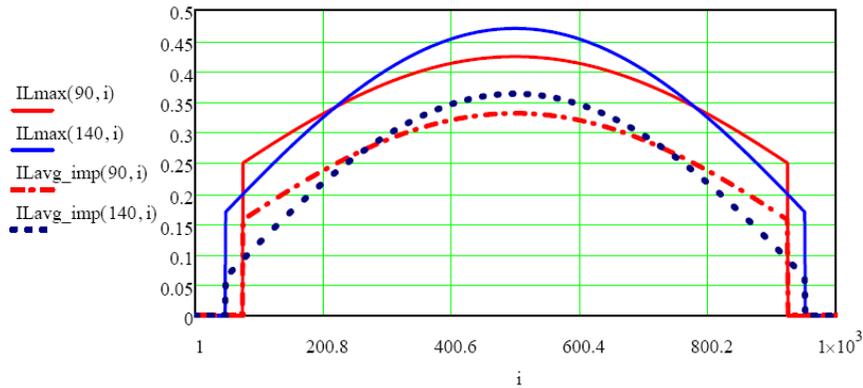


Figure 14. Inductor Current Less Than 90 Vac and 140 Vac

Figure 15 and Figure 16 show the experiment results less than 90 Vac and 140 Vac

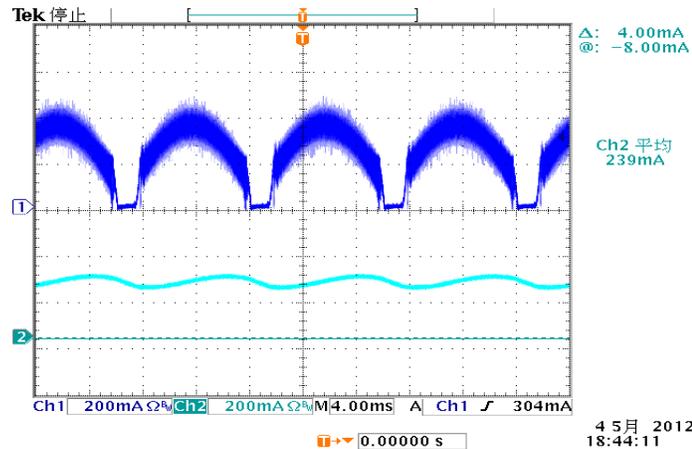


Figure 15. Test Result of Inductor Current and Output Current Less Than 90 Vac

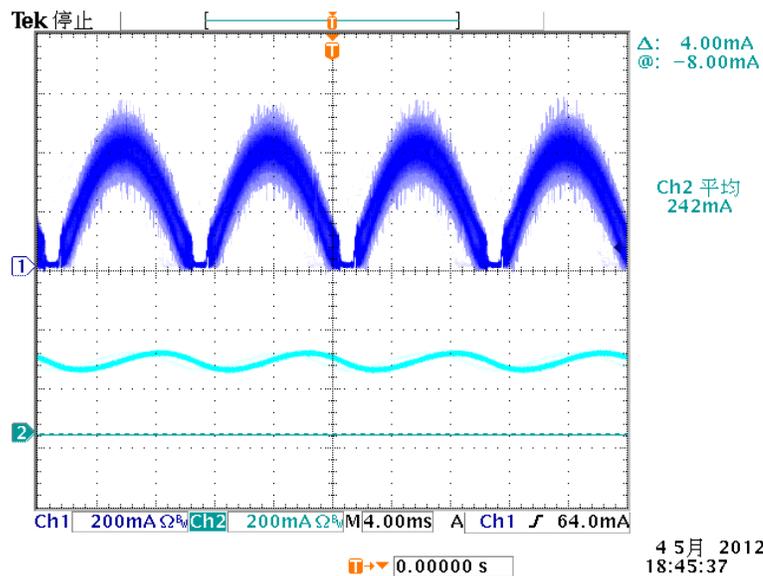


Figure 16. Test Result of Inductor Current and Output Current Less Than 140 Vac

Figure 17 shows the line regulation calculation result:


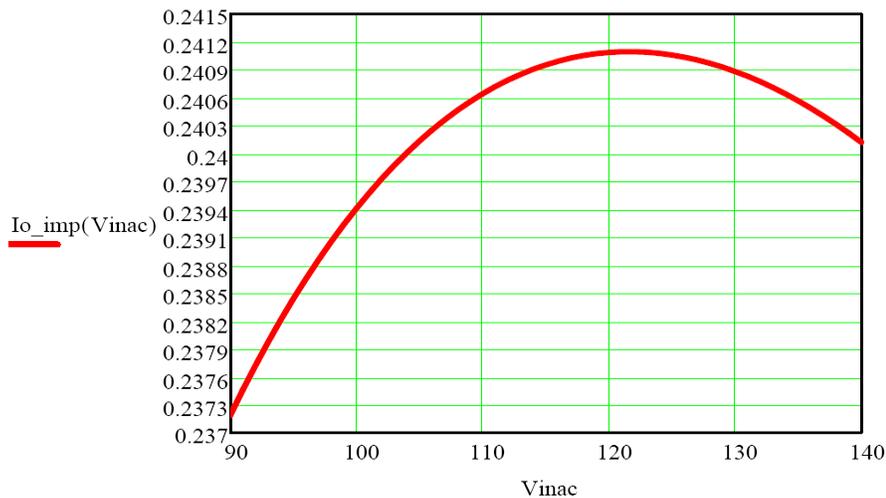


Figure 17. Line Regulation Calculation Has Been Improved to Less Than $\pm 1\%$

The output current is a nonlinear curve with the input voltage, not a linear curve. The compensation parameters greatly influence the curve. In practical design, engineers can optimize the curve by adjusting the line compensation parameters.

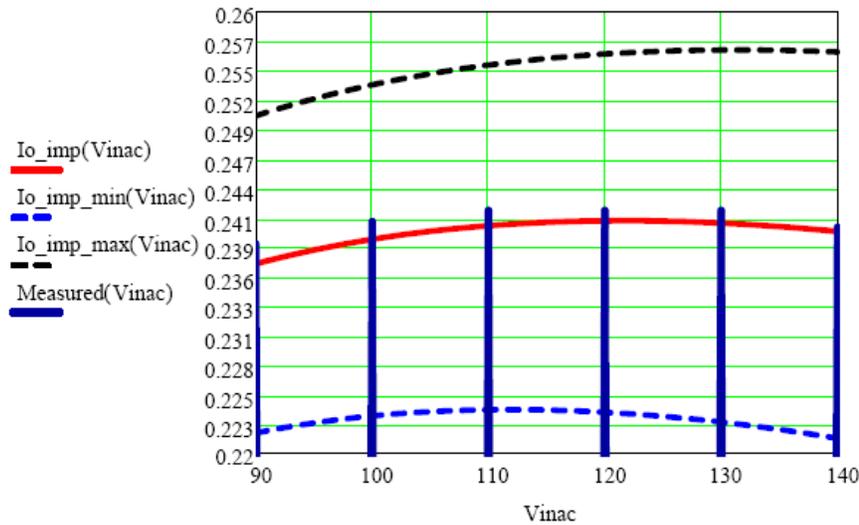To verify the result, use the measurement results shown in Figure 18 make the contrast with the calculation results.



current tolerance:

$$\Delta Io\%_{imp} := \frac{Io_imp_max(130) - Io_imp_min(90)}{Io_noimp(120) \cdot 2}$$

$$\Delta Io\%_{imp} = 0.066$$

Figure 18. Calculation of worst-case Current Tolerance Has Been Improved to ± 6.6%

From Figure 18, it is seen that the worst-case current tolerance has also been improved due to the improved line regulation circuit. To meet the very stringent worst-case current tolerance, our solution must be improved more for some special users.

If the current tolerance under 90 Vac is considered, the following is obtained:

$$\Delta Io\%_{imp90} = \frac{Io_imp_max(90) - Io_imp_min(90)}{Io_noimp(120) \cdot 2}$$

$$\Delta Io\%_{imp90} = 0.056$$

This target is attainable if the tolerance above 90 Vac is nearly the same; therefore, an optional method is proposed in Figure 19.

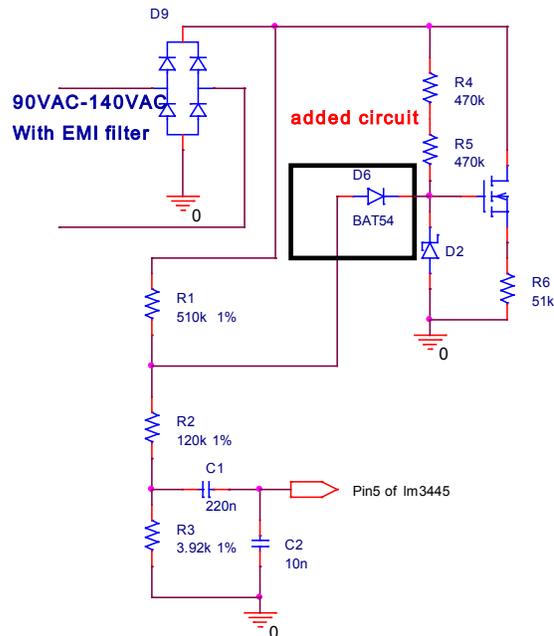


Figure 19. Circuit to Improve Line Regulation Less Than 120 Vac to 140 Vac

Then the pin 5 voltage of LM3445/LM3444 is calculated as shown in Figure 20 and Figure 21:

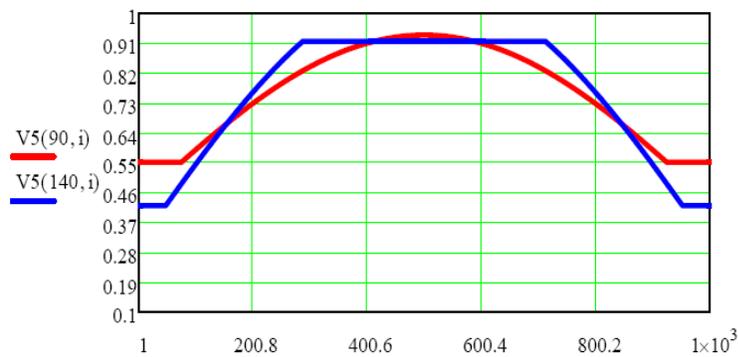


Figure 20. Voltage of Pin 5 on LM3445/LM3444 When Figure 20 Circuit is Added

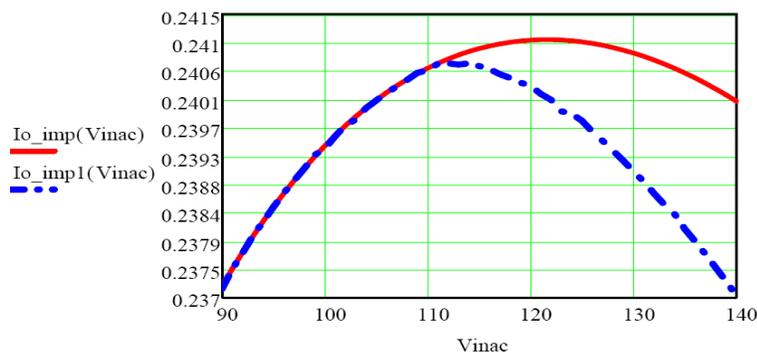


Figure 21. Line Regulation Has Been Improved More After Using Figure 19 circuit.

From the preceding analysis, it can be concluded that this circuit helps improve the line regulation. However, if the current tolerance using the line compensation circuit can meet the requirement during mass production, then the added diode circuit cannot be used. But TI still recommends using the added diode in the practical design schematic if there is room for PCB layout.

Finally, Figure 22 shows the total improved solution with the optional way.

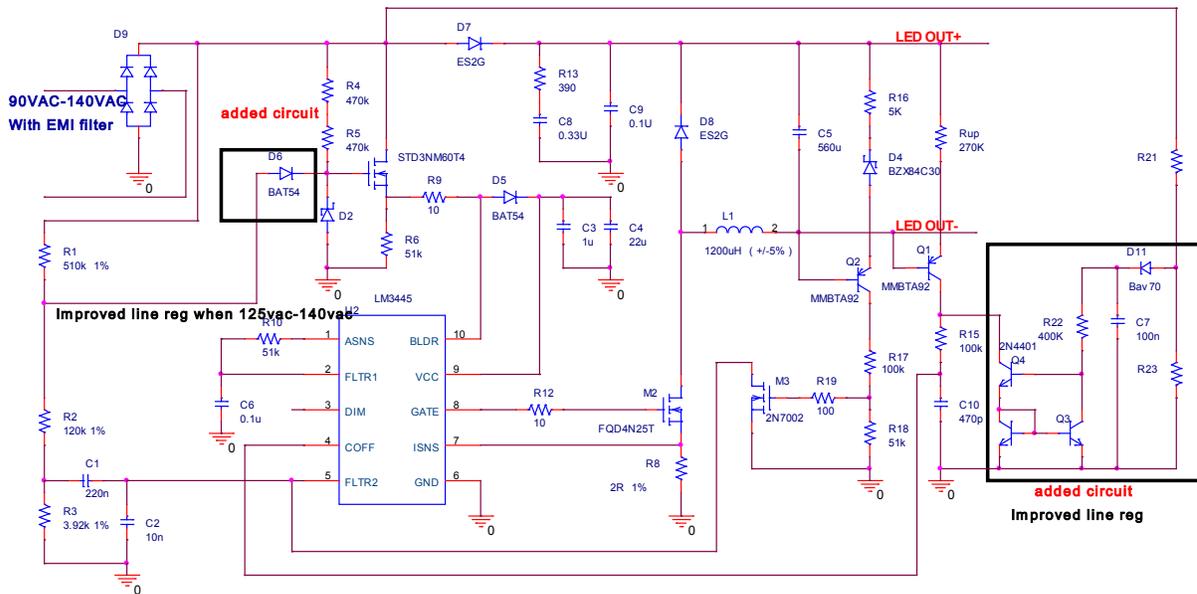


Figure 22. Total Solution With the Optional way to Improve the Line Regulation Greatly

Conclusion

This paper thoroughly analyzes the line regulation of output current and current tolerance based on the traditional nonisolated LM3444/LM3445. It is determined that the line regulation is not good. To solve this problem, an improved solution is proposed. The line regulation and total current tolerance are also illustrated. The viability of the proposed solution is proved both from theoretical analysis and practical experimentation.

References

- [1] LM3445 Triac Dimmable Offline LED Driver Literature Number: SNVS570K.
- [2] Application Note 2069 LM3445 - 230VAC, 6W- 15W Isolated Flyback LED Driver
- [3] [Application Note 2034 LM3445 -120VAC, 8W Isolated Flyback LED Driver \(Rev. B\)](#)
- [4] [Application Note 2082 LM3444 -120VAC, 8W Isolated Flyback LED Driver \(Rev. B\)](#)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com