

1	Startup .....	2
2	Shutdown .....	4
3	Efficiency .....	6
4	Load Regulation .....	7
5	Line Regulation .....	8
6	Output Ripple Voltage .....	9
7	Input Ripple Voltage .....	10
8	Load Transients .....	11
9	Control Loop Frequency Response .....	13
10	Miscellaneous Waveforms .....	17
10.1	Input Voltage = 36V .....	17
10.2	Input Voltage = 48V .....	20
10.3	Input Voltage = 60V .....	23
11	Thermal Image .....	28
12	Addendum .....	30

Topology: Active Clamp Forward

Device: UCC2897A

Unless otherwise mentioned the measurements were done with about 2A output current.

*This design is dedicated to a RF application – design topic is low reflected ripple and low output ripple. So the converter itself is powered across a differential input filter, the output filter uses ceramics only. Due to constant load the output capacitance is pretty low, but fully sufficient for constant current. A minimum load >100mA is required to ensure BIAS power.*



## 1 Startup

The startup waveform is shown in the Figure 1. The input voltage was set to 36V.

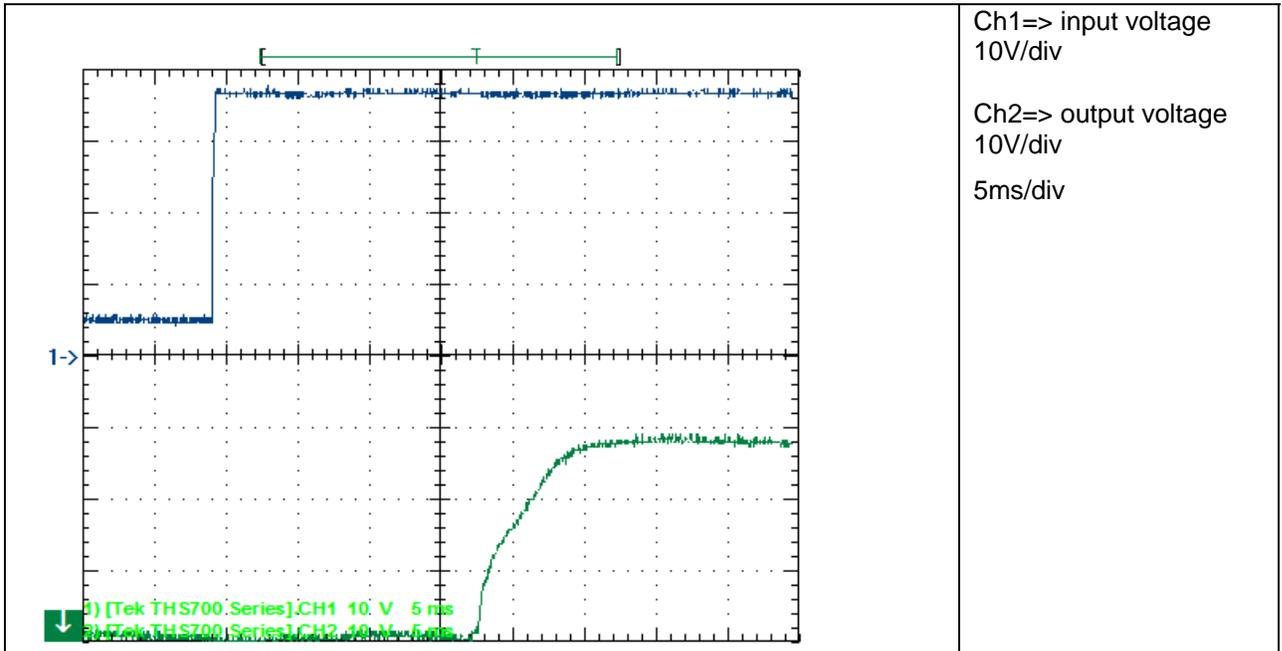


Figure 1

The startup waveform is shown in the Figure 2. The input voltage was set to 48V.

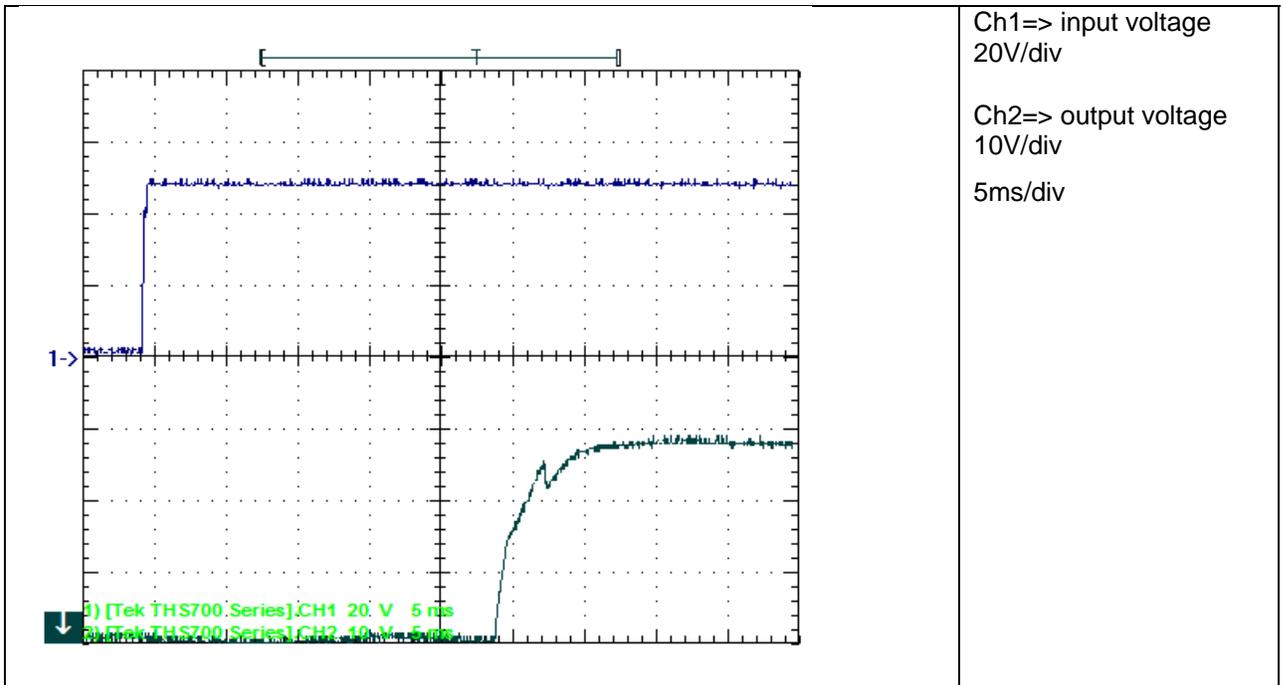


Figure 2

The startup waveform is shown in the Figure 3. The input voltage was set to 60V.

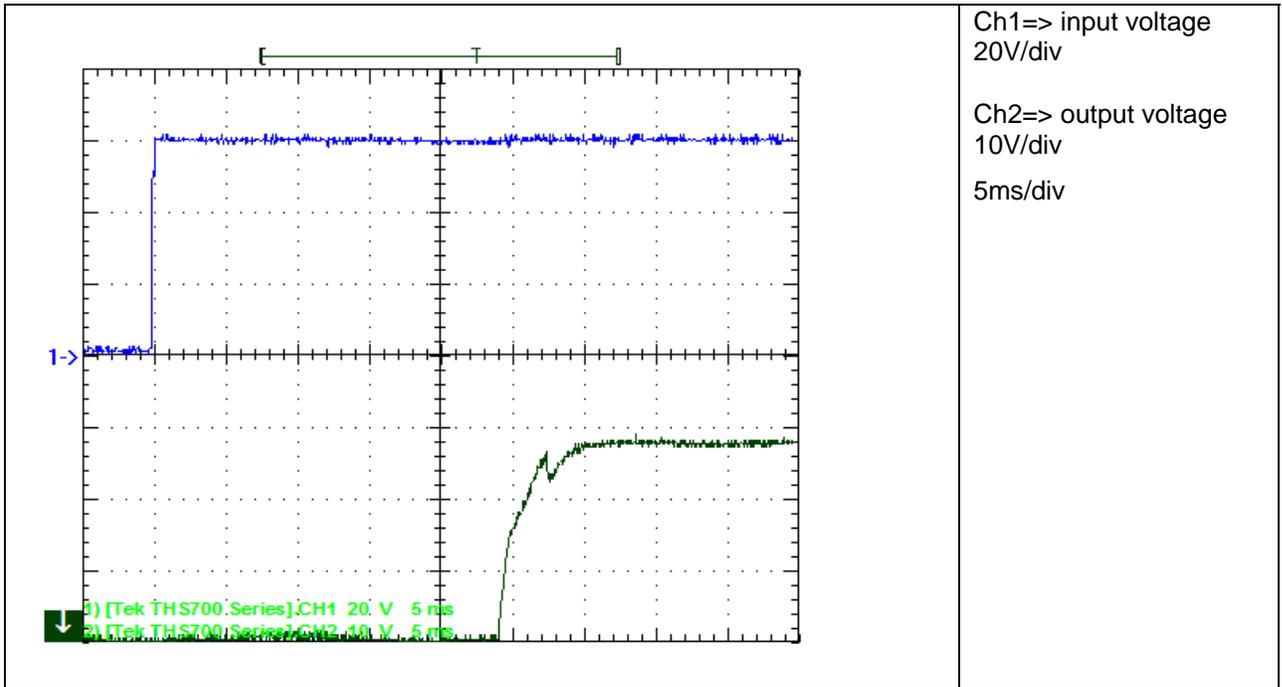


Figure 3

## 2 Shutdown

The shutdown waveform is shown in the Figure 4. The input voltage was set to 36V. The power supply was disconnected.

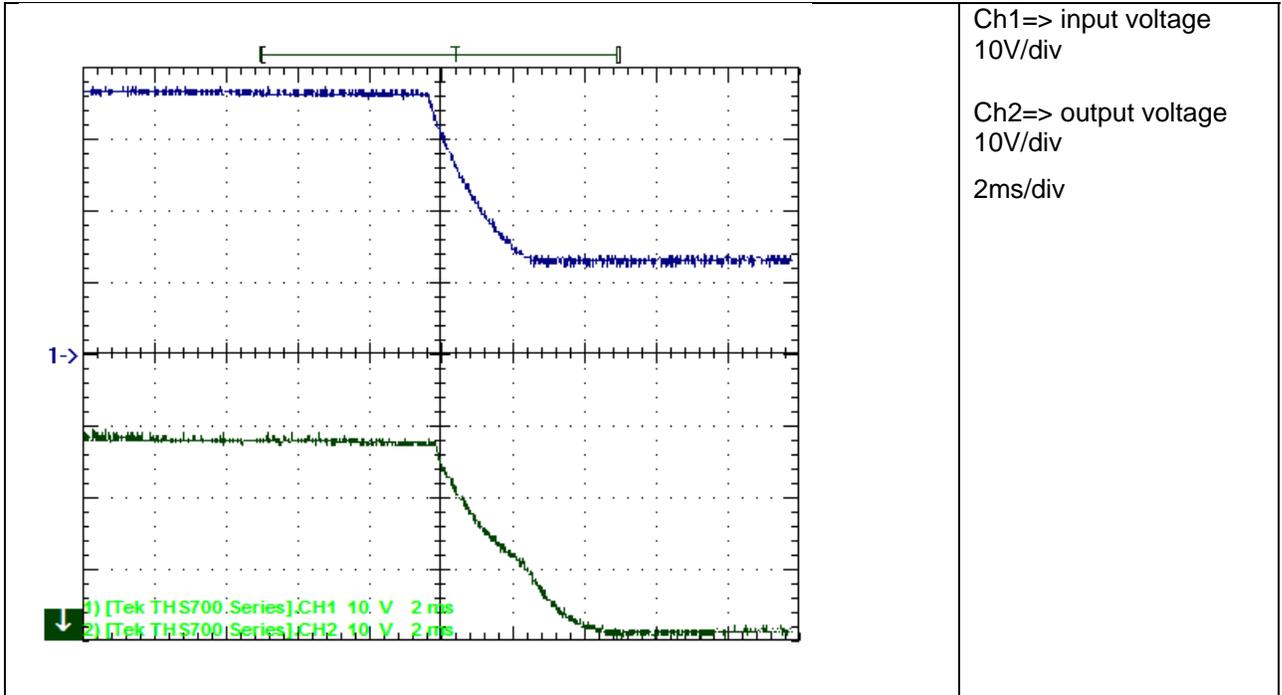


Figure 4

The shutdown waveform is shown in the Figure 5. The input voltage was set to 48V. The power supply was disconnected.

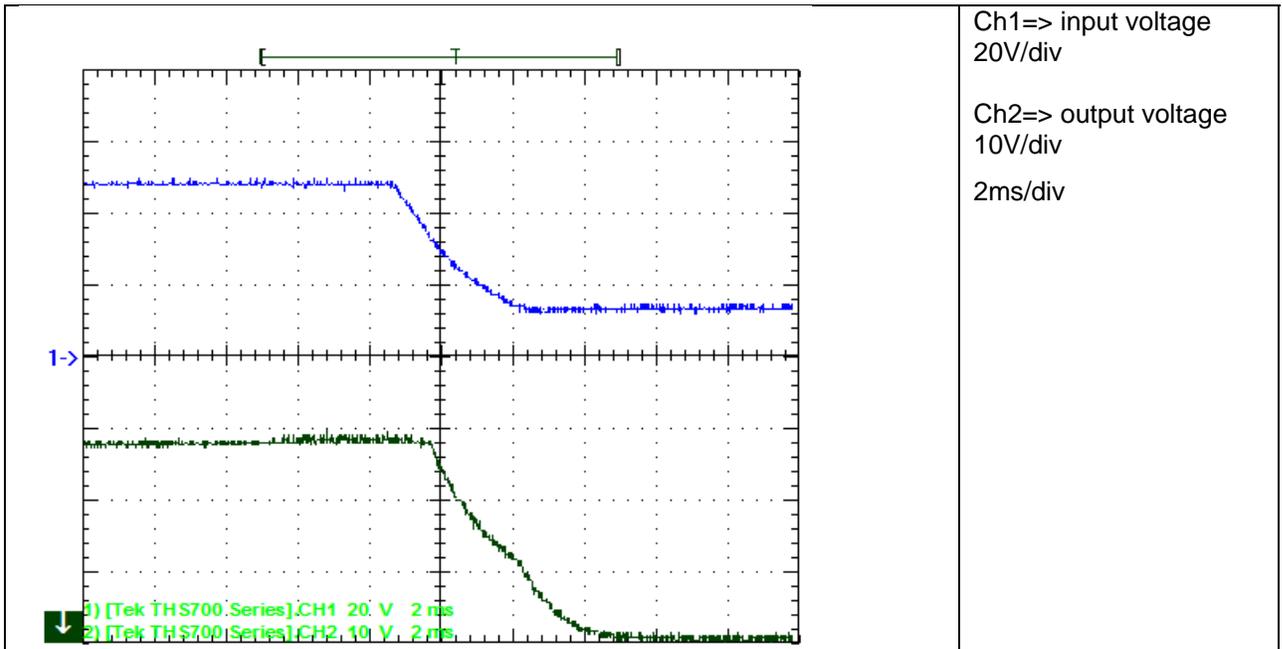


Figure 5

The shutdown waveform is shown in the Figure 6. The input voltage was set to 60V. The power supply was disconnected.

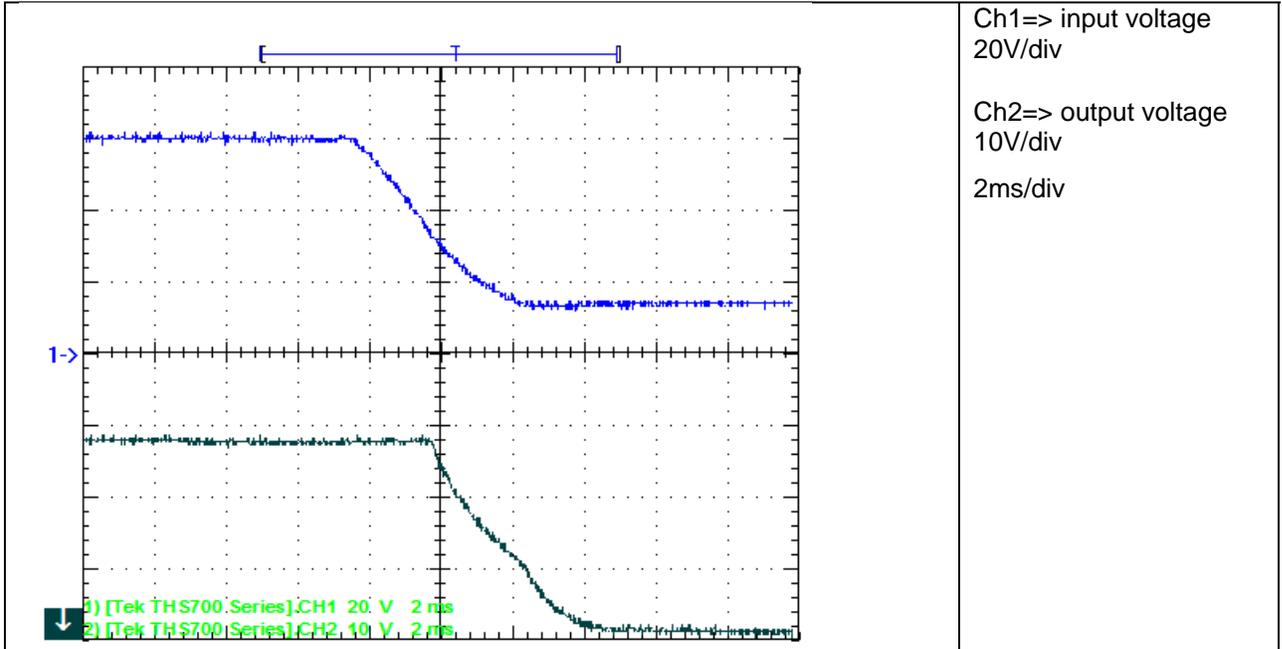


Figure 6

### 3 Efficiency

The efficiency curves are shown in the Figure 7 below. Measurements were done with resistor load. Inductor is MSS1210-224KE, suited up to 1.6Amps load.

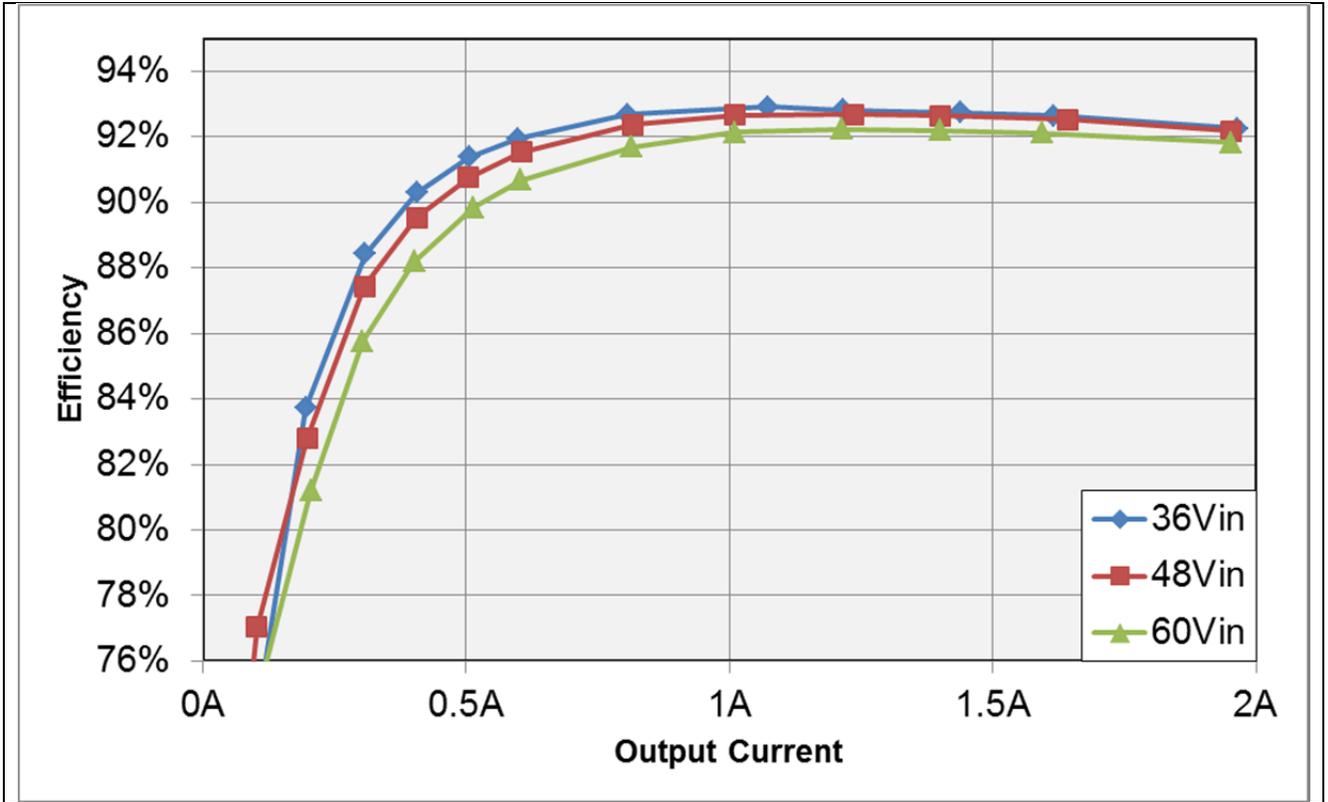


Figure 7

## 4 Load Regulation

The load regulation of the output is shown in the Figure 8 below. Measurements were done with resistor load.

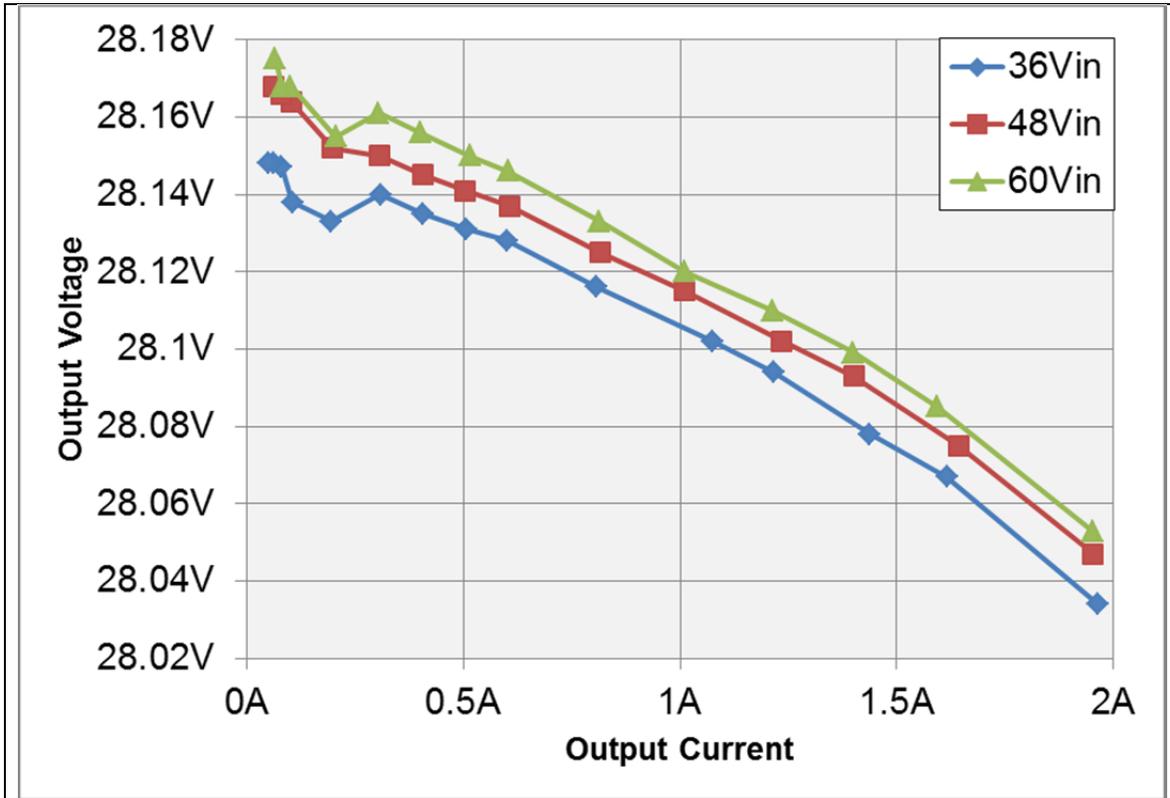


Figure 8

### 5 Line Regulation

The line regulation is shown in Figure 9. Measurements were done with electronic EL 100.

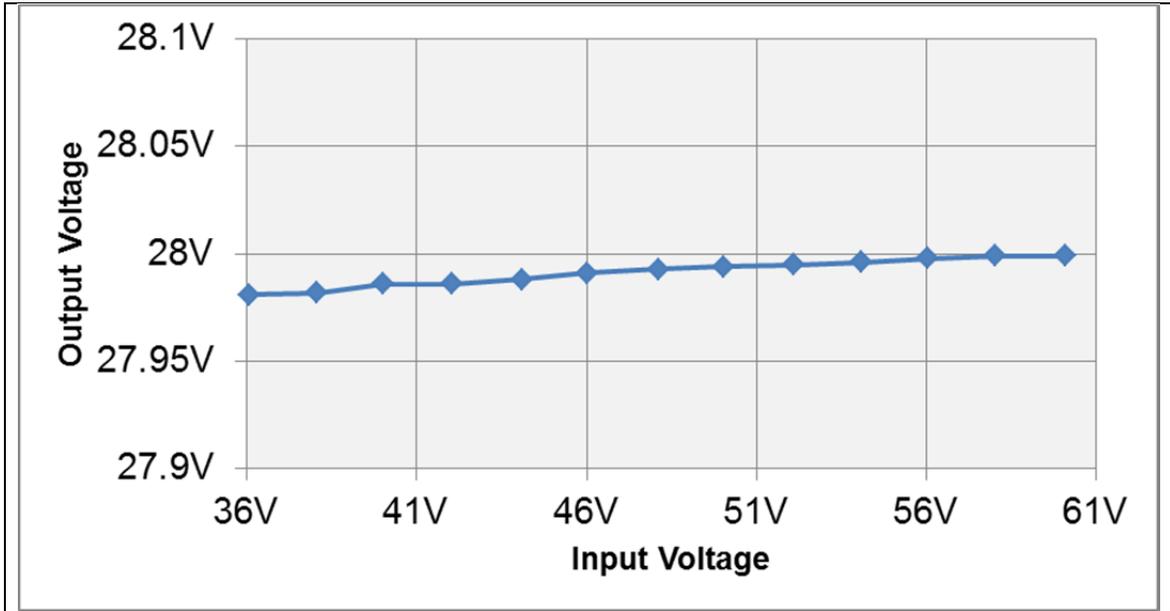


Figure 9

With the same setup the efficiencies are shown in Figure 10.

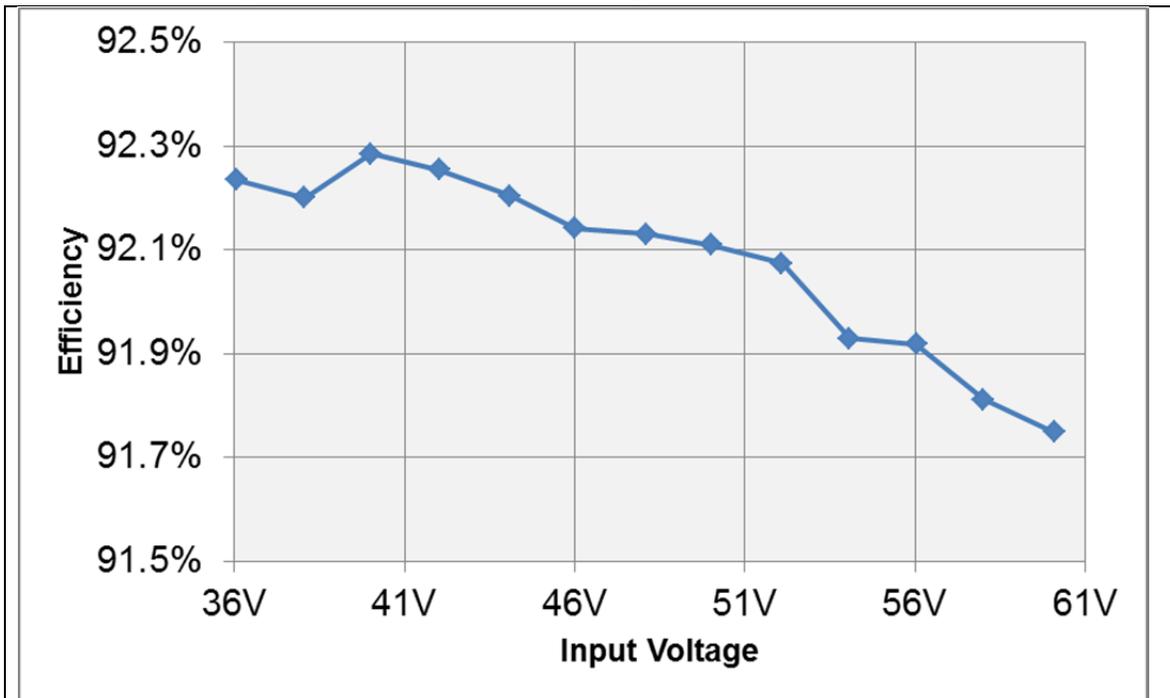


Figure 10

## 6 Output Ripple Voltage

The output ripple voltage (measured at J2 bottom side) is shown in Figure 11

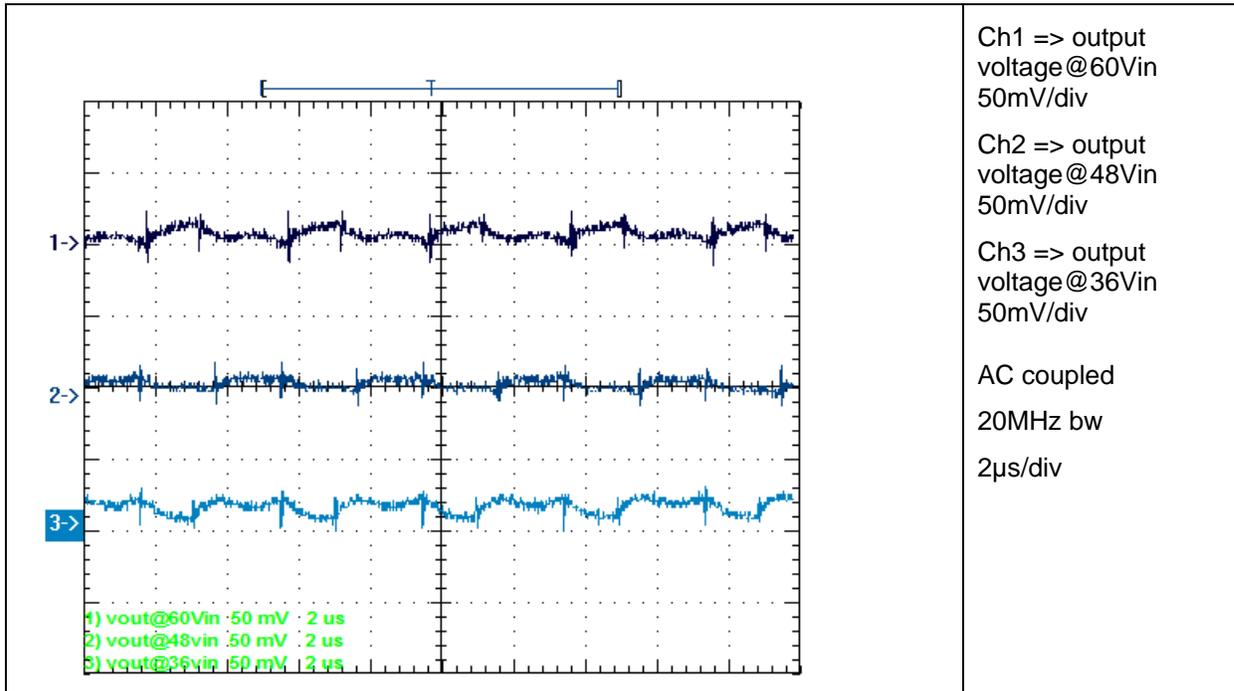


Figure 11

The output voltage ripple voltage is well below specified 100mVpp, here 40mVpp, **means only 0.14% for a 28V output.**

The filtered reflected input voltage ripple is around 40mVpp, at the converter input close to 1Vpp; This, differential filter provides roughly an attenuation of 40mV/880mV, means -27dB.

## 7 Input Ripple Voltage

The input ripple voltage is shown in Figure 12 (measured at J1 bottom side).

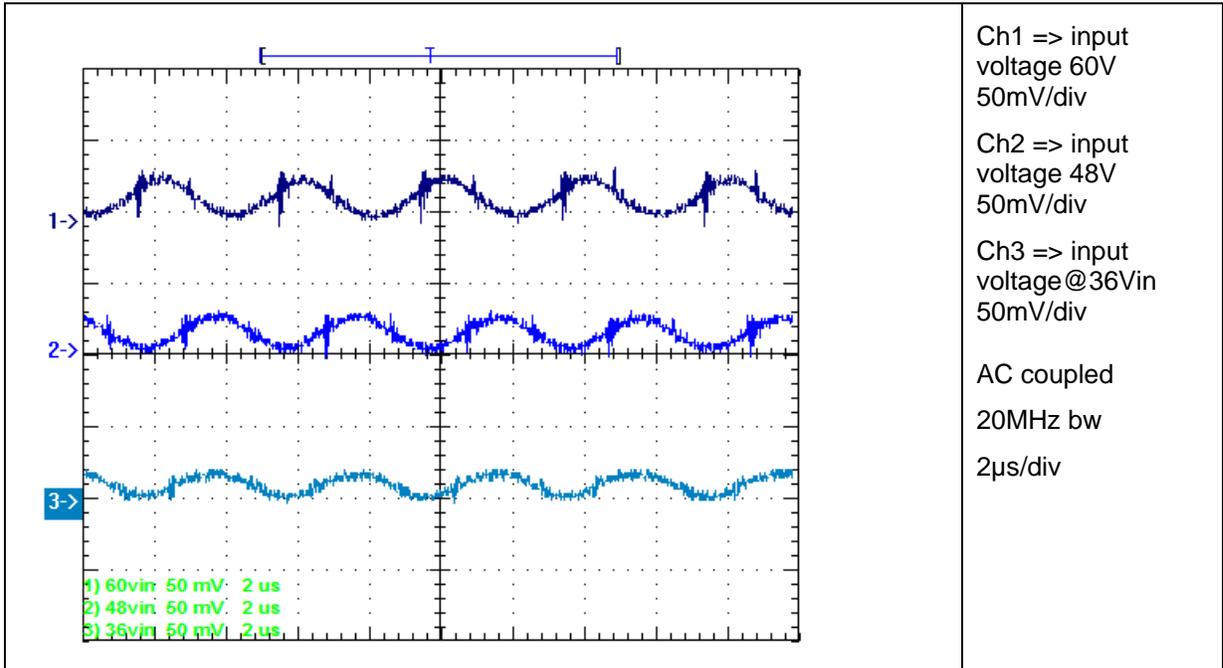


Figure 12

The input ripple voltage is shown in Figure 13 (measured near C9).

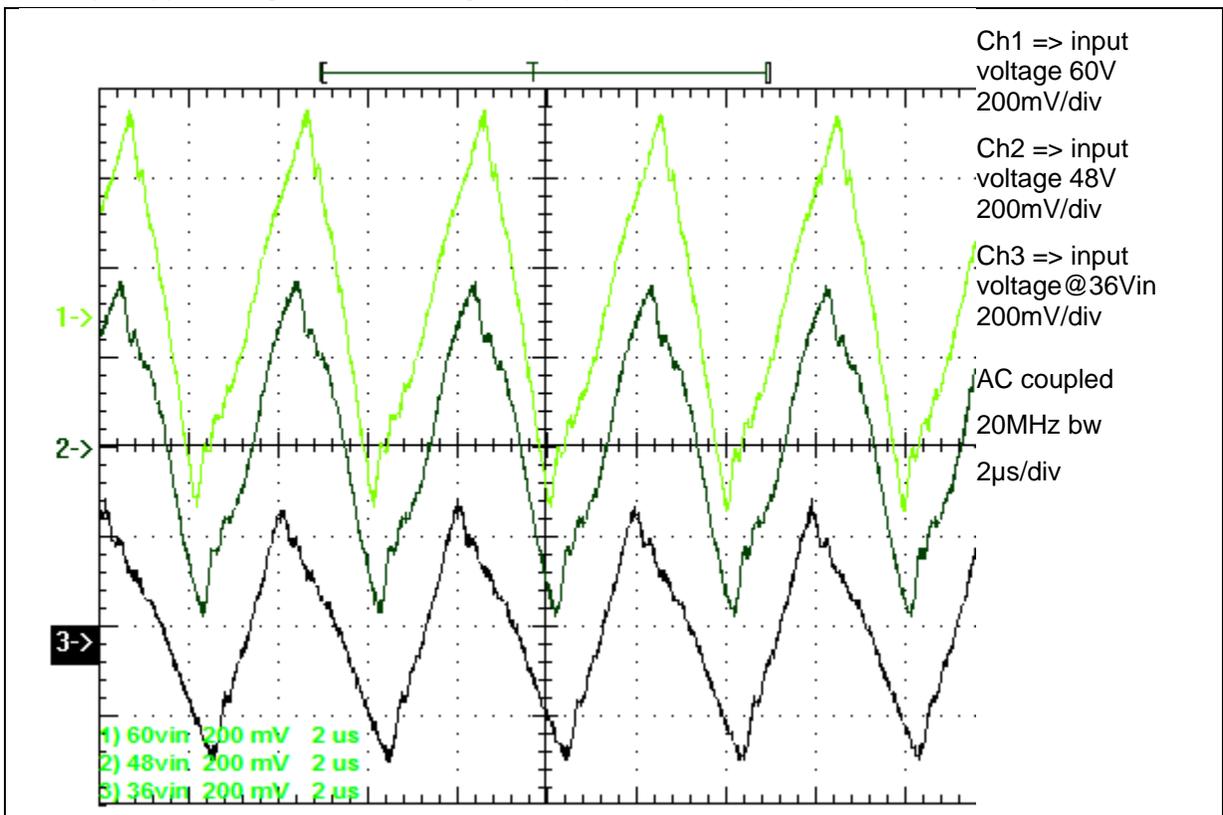


Figure 13

## 8 Load Transients

The Figure 14 shows the response to load transients. The load is switching from 1A to 2A with a frequency of 75Hz. The input voltage was set to 36V

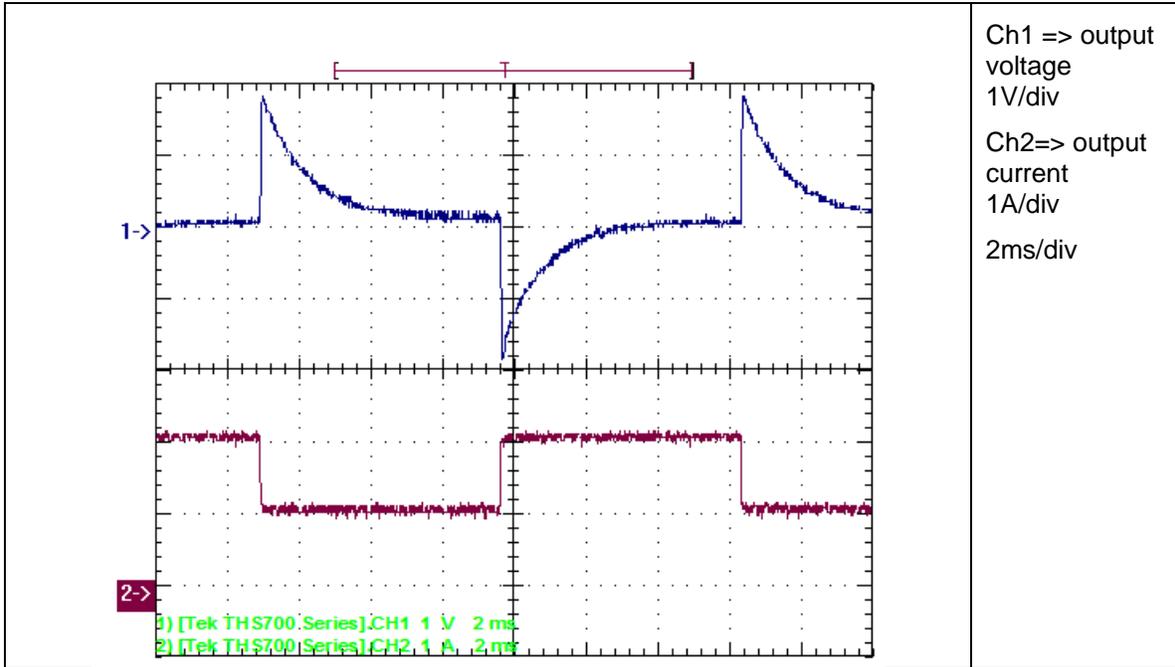


Figure 14

The Figure 15 shows the response to load transients. The load is switching from 1A to 2A with a frequency of 75Hz. The input voltage was set to 48V

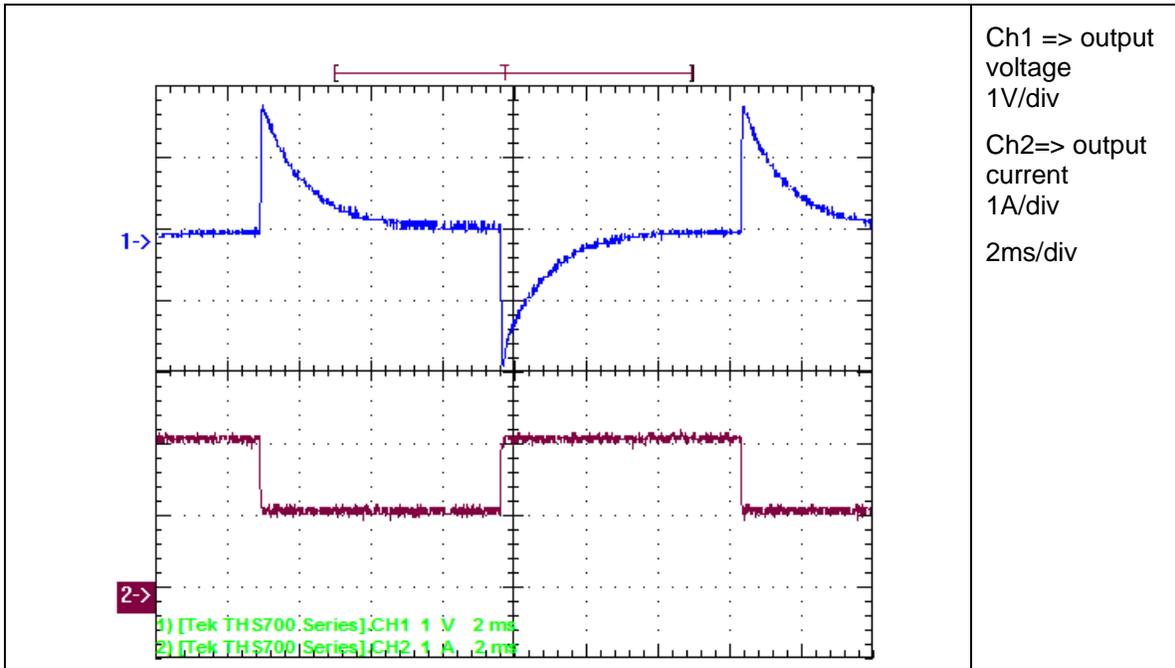


Figure 15

The Figure 16 shows the response to load transients. The load is switching from 1A to 2A with a frequency of 75Hz. The input voltage was set to 60V

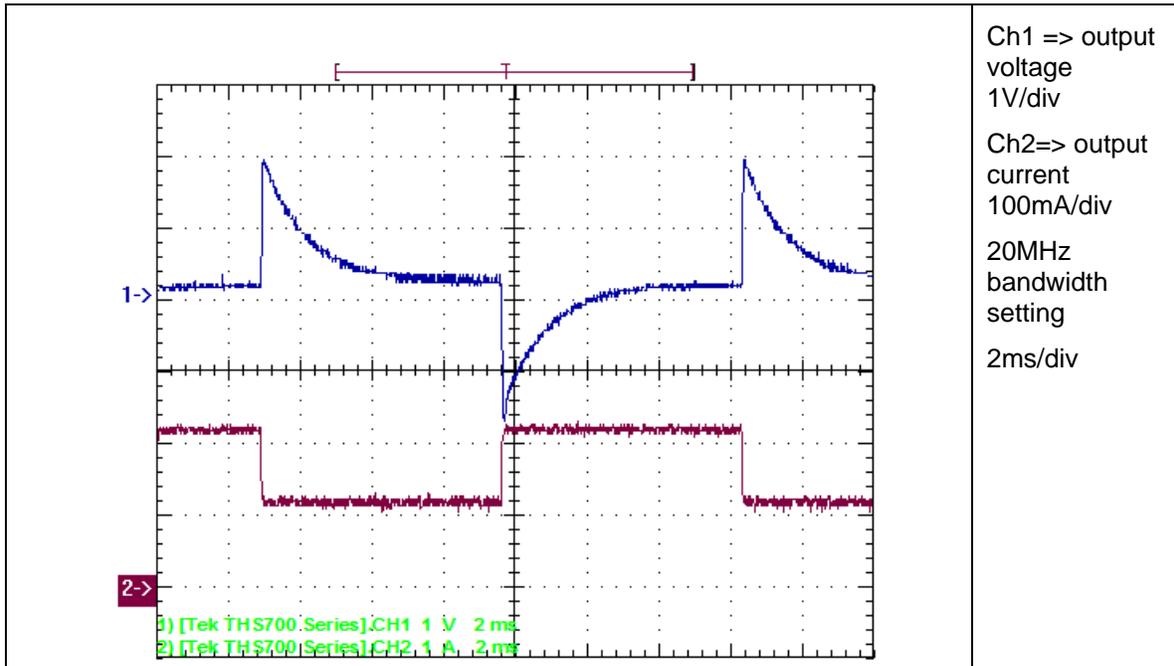


Figure 16

The converter itself is designed for CONSTANT load, transient response around du 2V for a transient di of 1A; this means a deviation of 7%.

For dynamic loads output capacitance needs to be increased and loop to be adjusted.

For loads <100mA BIAS needs to be changed from buck to peak detection or additional auxiliary power via diode ORing.

For continuous load >1.5A the output inductor needs a custom design (220uH, 2.5Arms, 3.0Asat, shielded, ferrite)

## 9 Control Loop Frequency Response

Figure 17 shows the loop response. 2A-load applied. The input voltage was set to 36V (Electronic load).

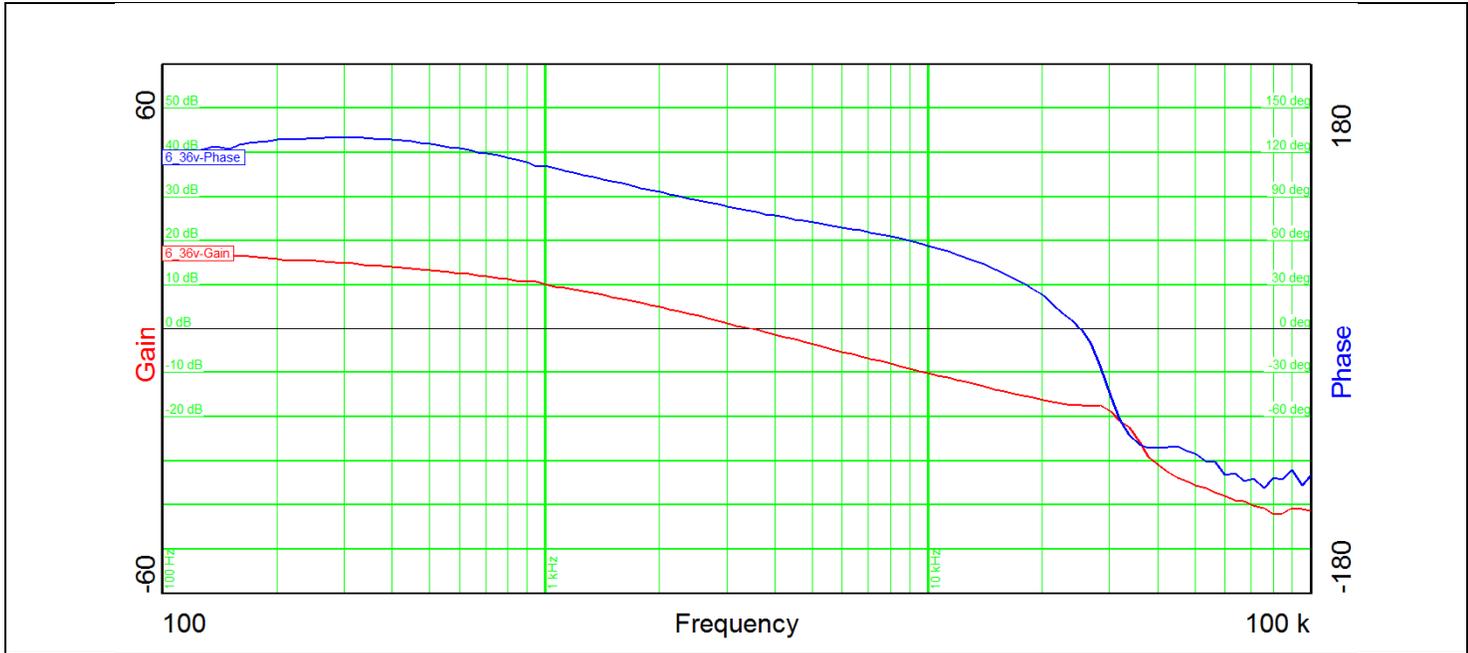


Figure 17

Figure 18 shows the loop response. 2A-load applied. The input voltage was set to 36V (resistor load)


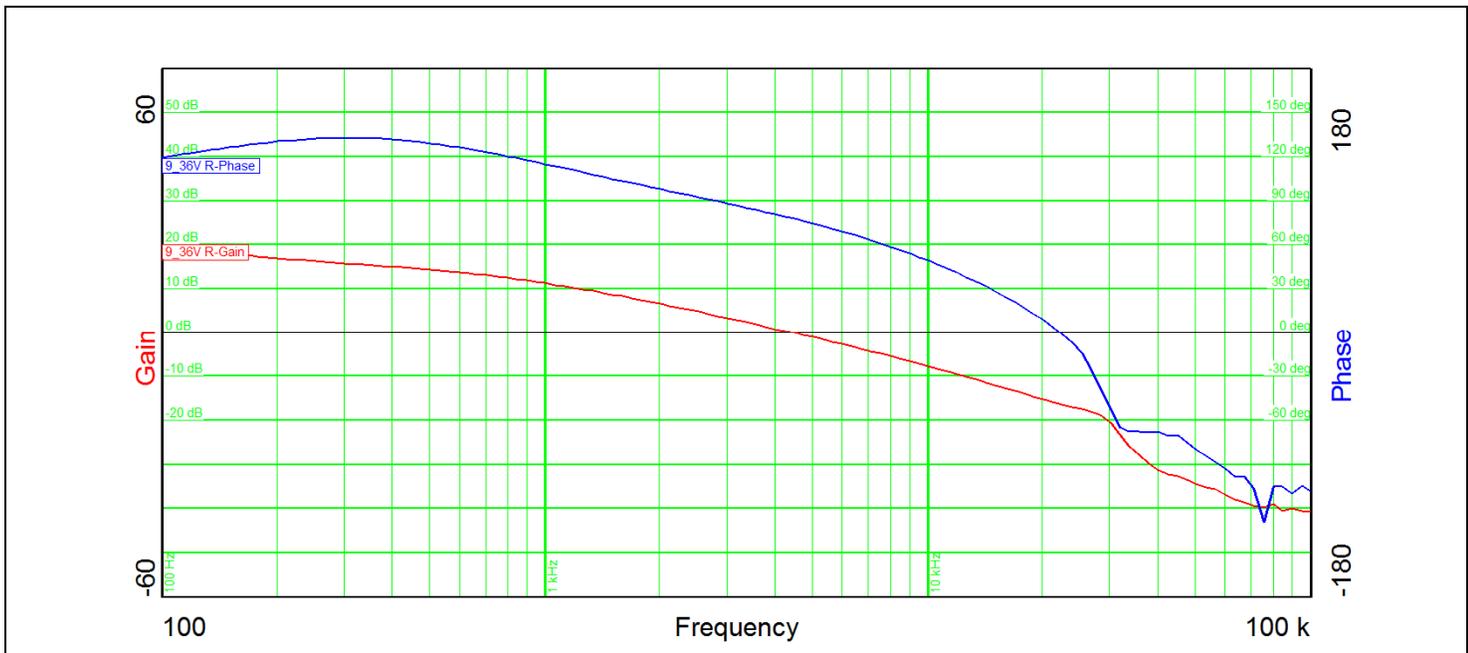



Figure 18

Figure 19 shows the loop response. 2A-load applied. The input voltage was set to 48V (Electronic load)

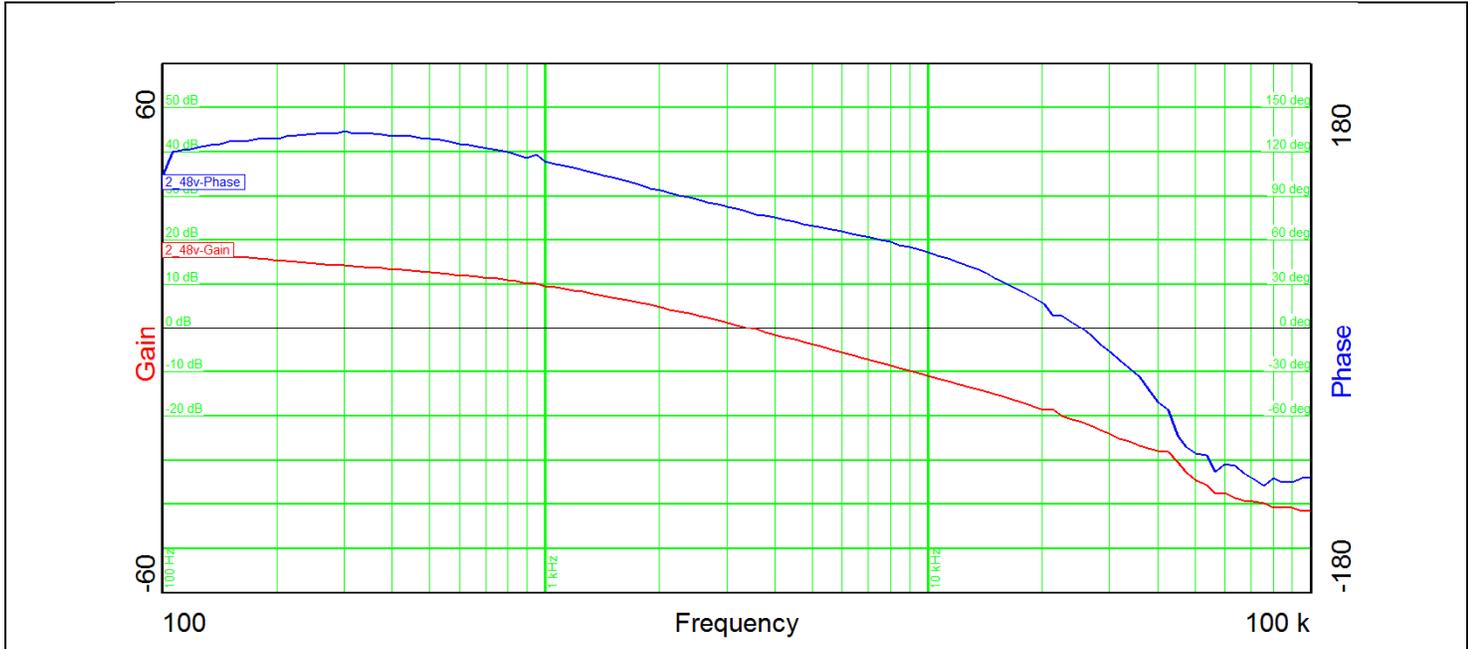

**Figure 19**

Figure 20 shows the loop response. 2A-load applied. The input voltage was set to 48V (resistor load).

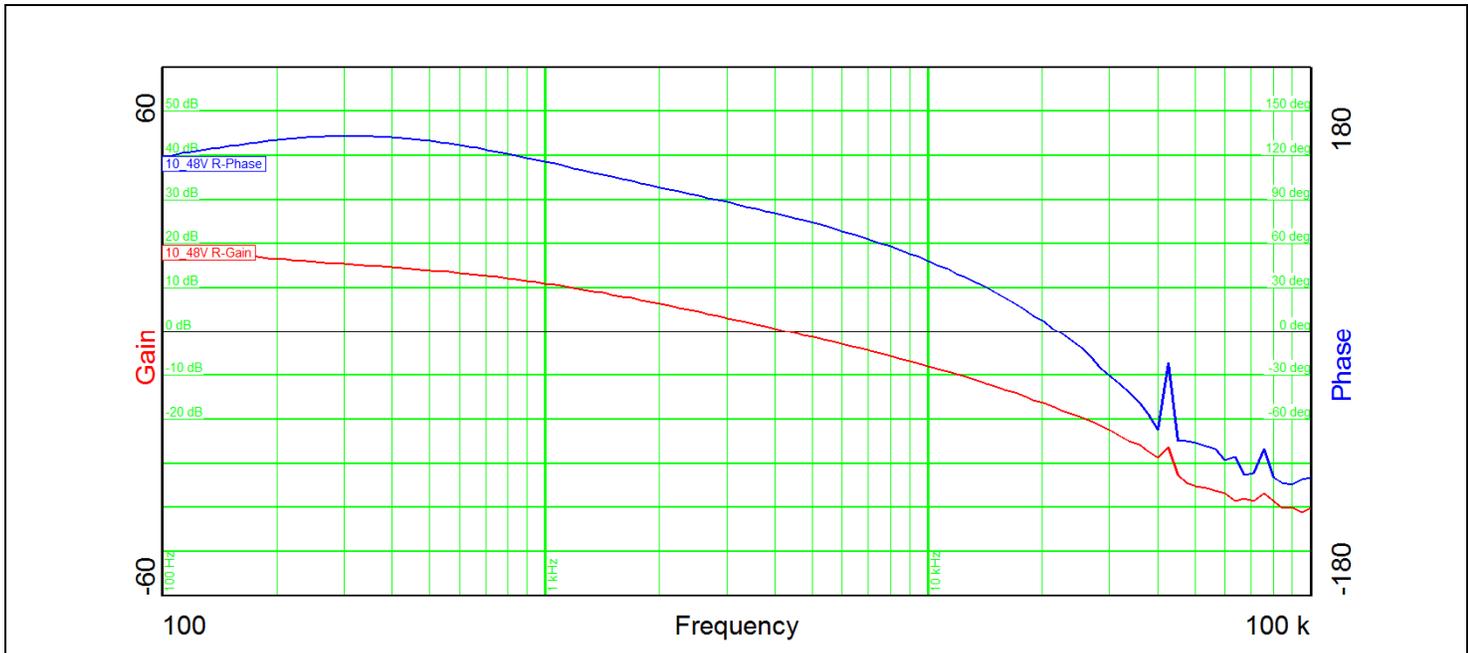

**Figure 20**

Figure 21 shows the loop response. 2A-load applied. The input voltage was set to 60V (Electronic load).

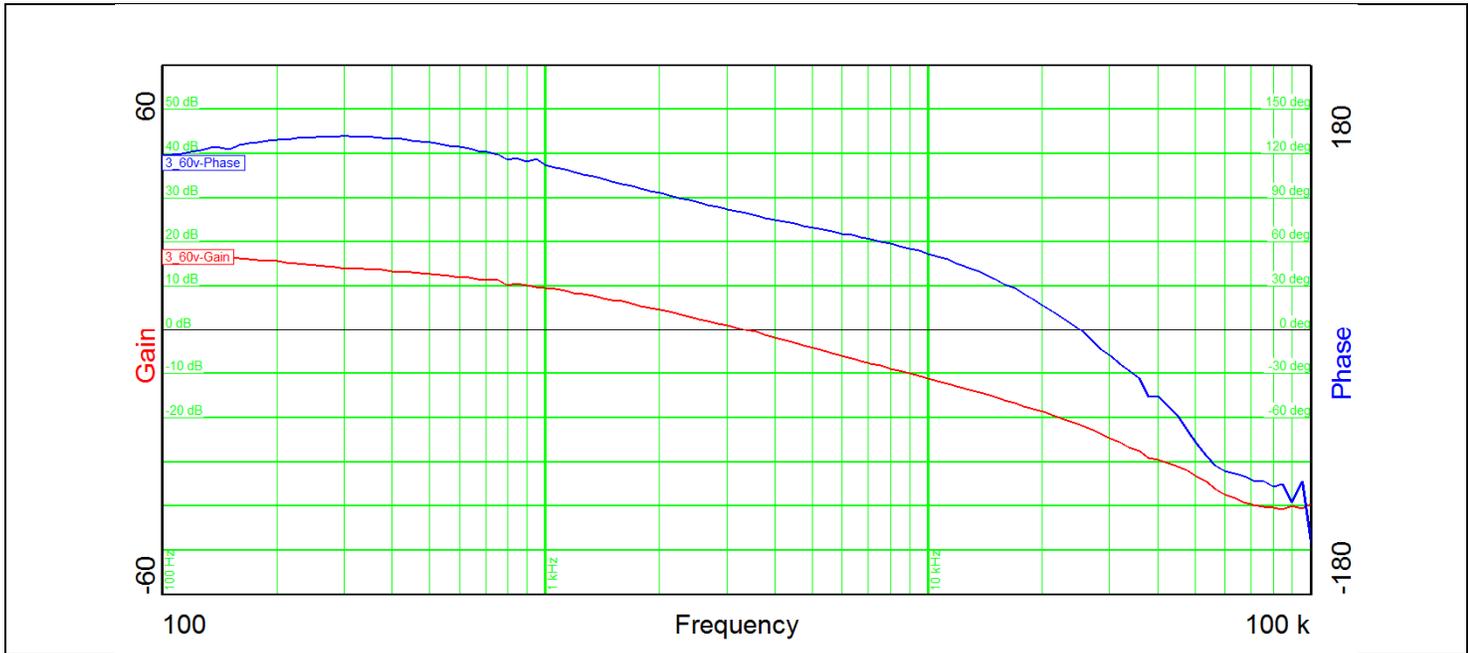


Figure 21

Figure 22 shows the loop response. 2A-load applied. The input voltage was set to 60V(resistor load).

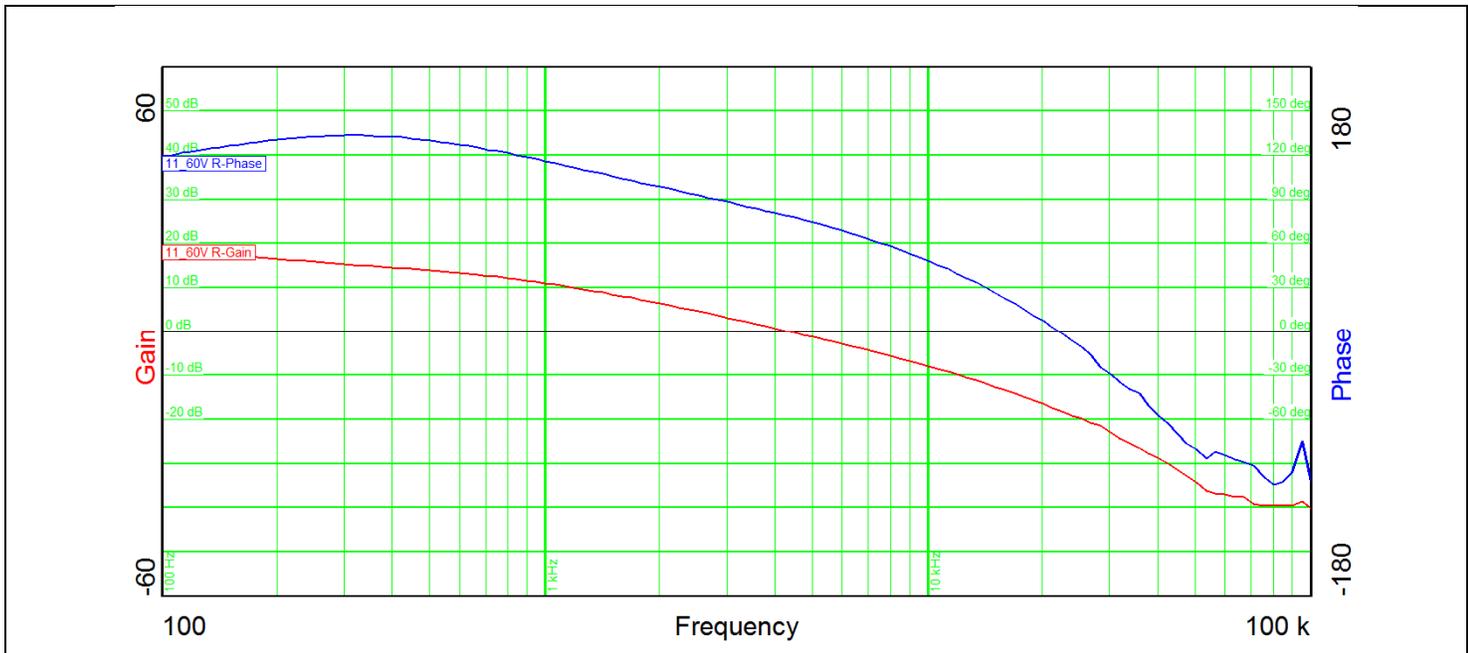


Figure 22

Table 1 summarizes the results from the frequency response measurements with electronic load.

<b>Vin</b>	36V	48V	60V
<b>Bandwidth (kHz)</b>	3.49	3.46	3.34
<b>Phase margin</b>	80°	79°	80°
<b>slope (20dB/decade)</b>	-1.15	-0.97	-1.17
<b>gain margin (dB)</b>	-17.5	-21.5	-21.7
<b>slope (20dB/decade)</b>	-0.35	-1.56	-1.54
<b>freq (kHz)</b>	24.9	25.2	25

**Table 1**

Table 2 summarizes the results from the frequency response measurements with resistor load.

<b>Vin</b>	36V	48V	60V
<b>Bandwidth (kHz)</b>	4.43	4.36	4.36
<b>Phase margin</b>	78°	78°	78°
<b>slope (20dB/decade)</b>	-1.02	-1.02	-1.01
<b>gain margin (dB)</b>	-16.4	-17.6	-17.9
<b>slope (20dB/decade)</b>	-1.13	-1.7	-1.75
<b>freq (kHz)</b>	22.3	22	22

**Table 2**

## 10 Miscellaneous Waveforms

### 10.1 Input Voltage = 36V

The waveform of the voltage on switchnode Q2 (drain-source) is shown in Figure 23.

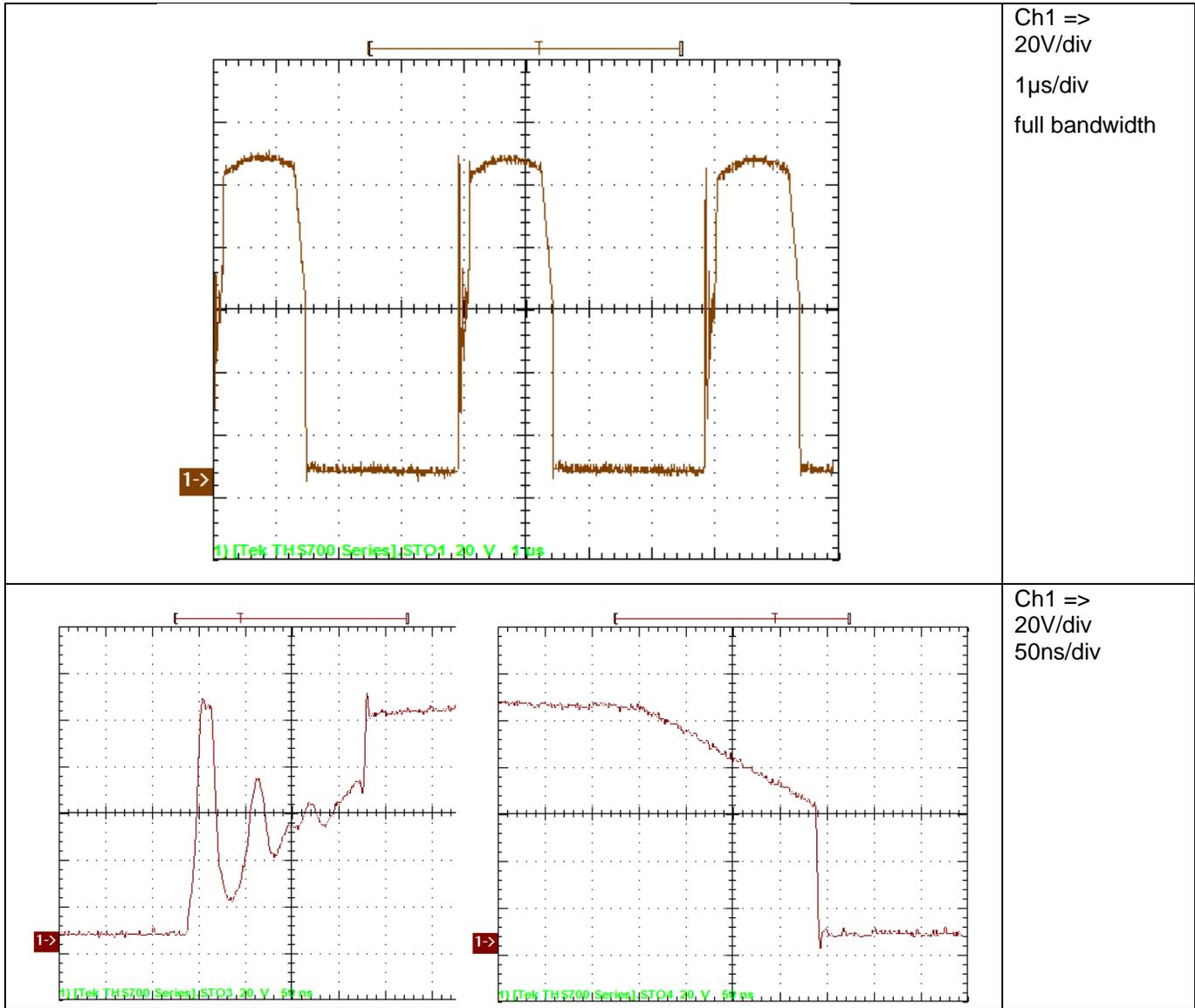


Figure 23

*Delay resistor  $R_T$  of 2.2kOhm offers a shiny drain waveform – but less QR switching and less efficiency; screenshots are taken w/  $R_T$  of 16kOhm. Placing 2k55 to 16k in parallel and switching 2k55 shows the difference; 2k2 means hard switching.*

The waveform of the voltage on Q1 (PMOS) drain-source is shown in Figure 24.

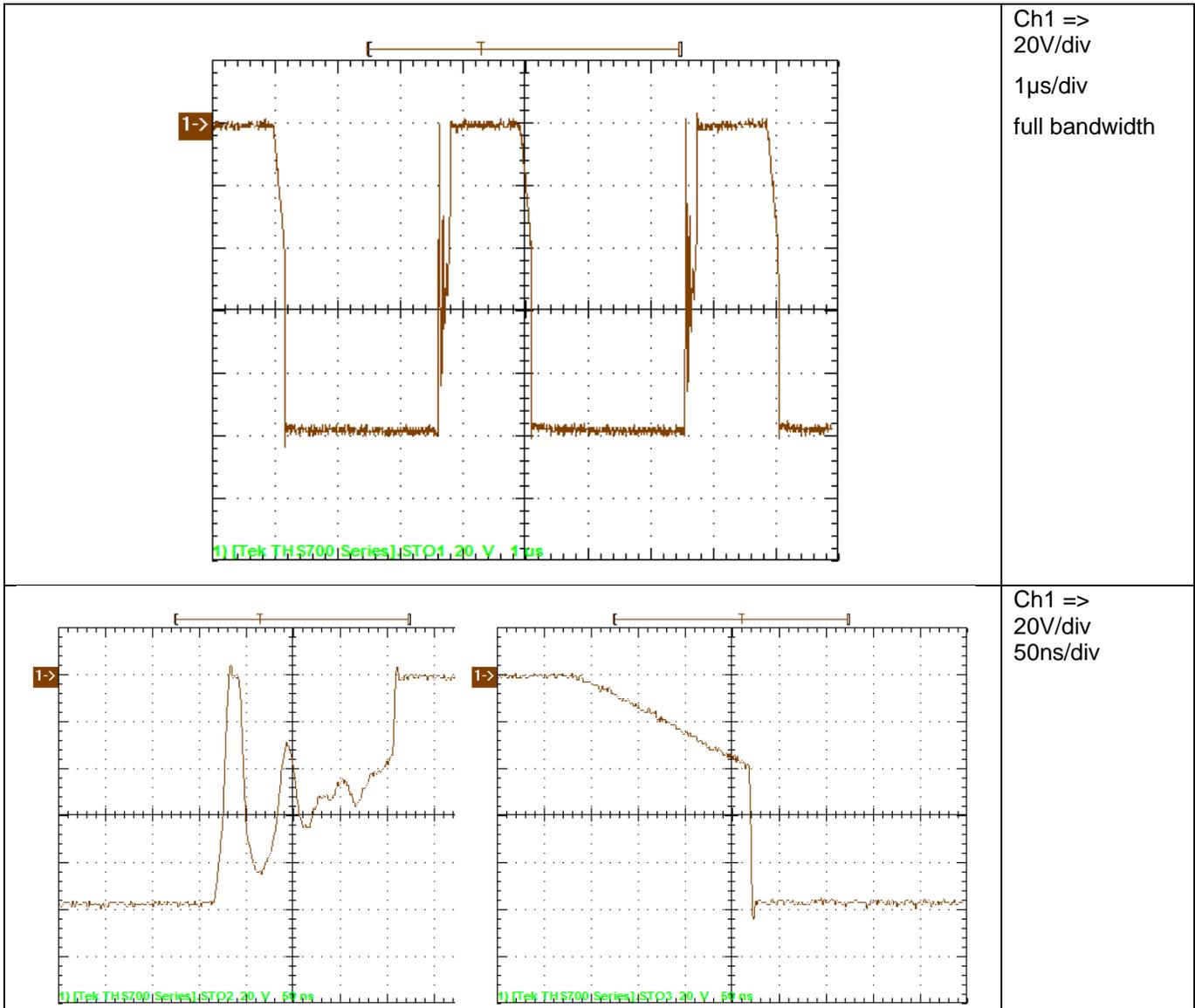


Figure 24

The waveform of the voltage at the transformer output is shown in Figure 25.

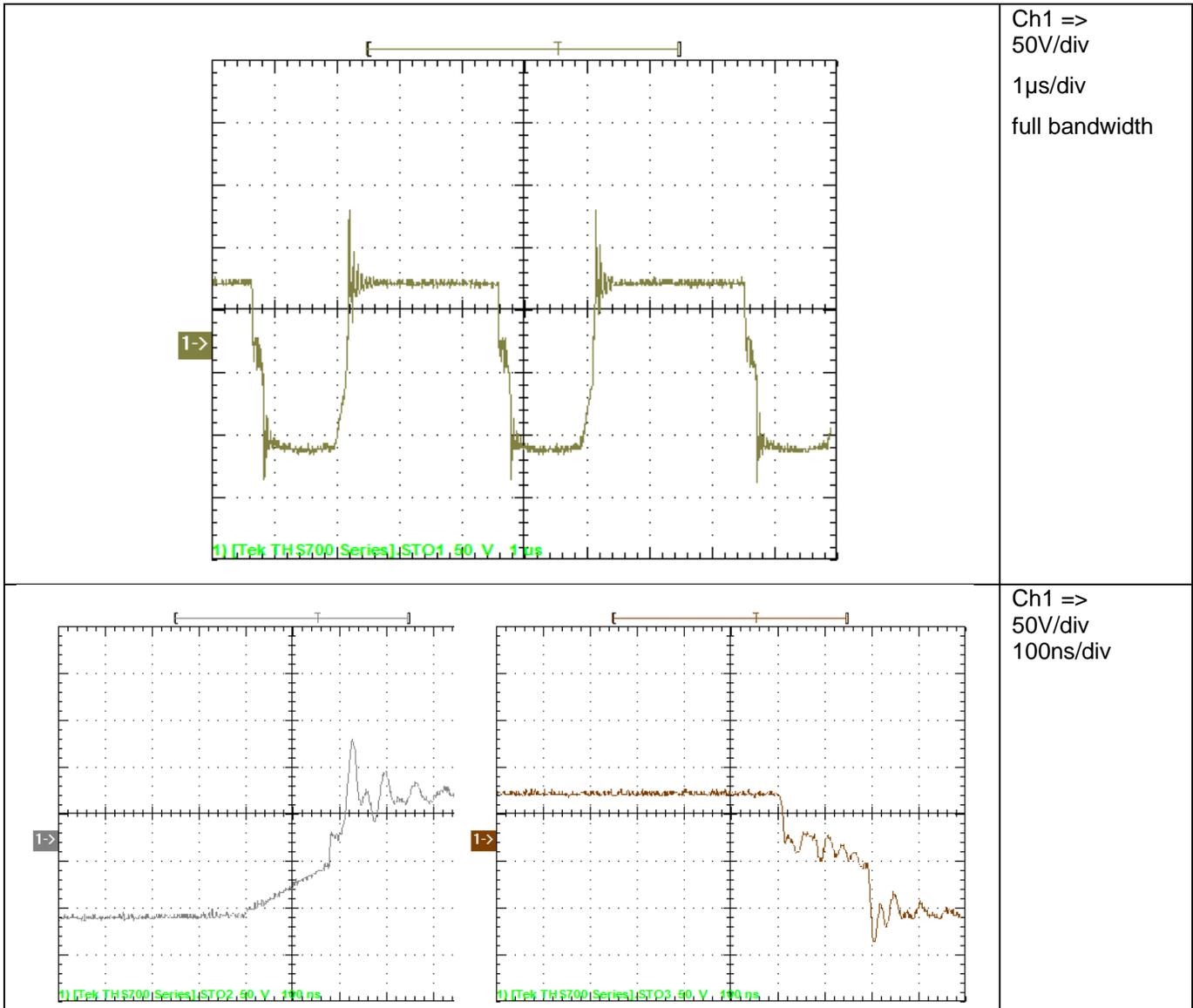


Figure 25

## 10.2 Input Voltage = 48V

The waveform of the voltage on switchnode Q2 (drain-source) is shown in Figure 26.

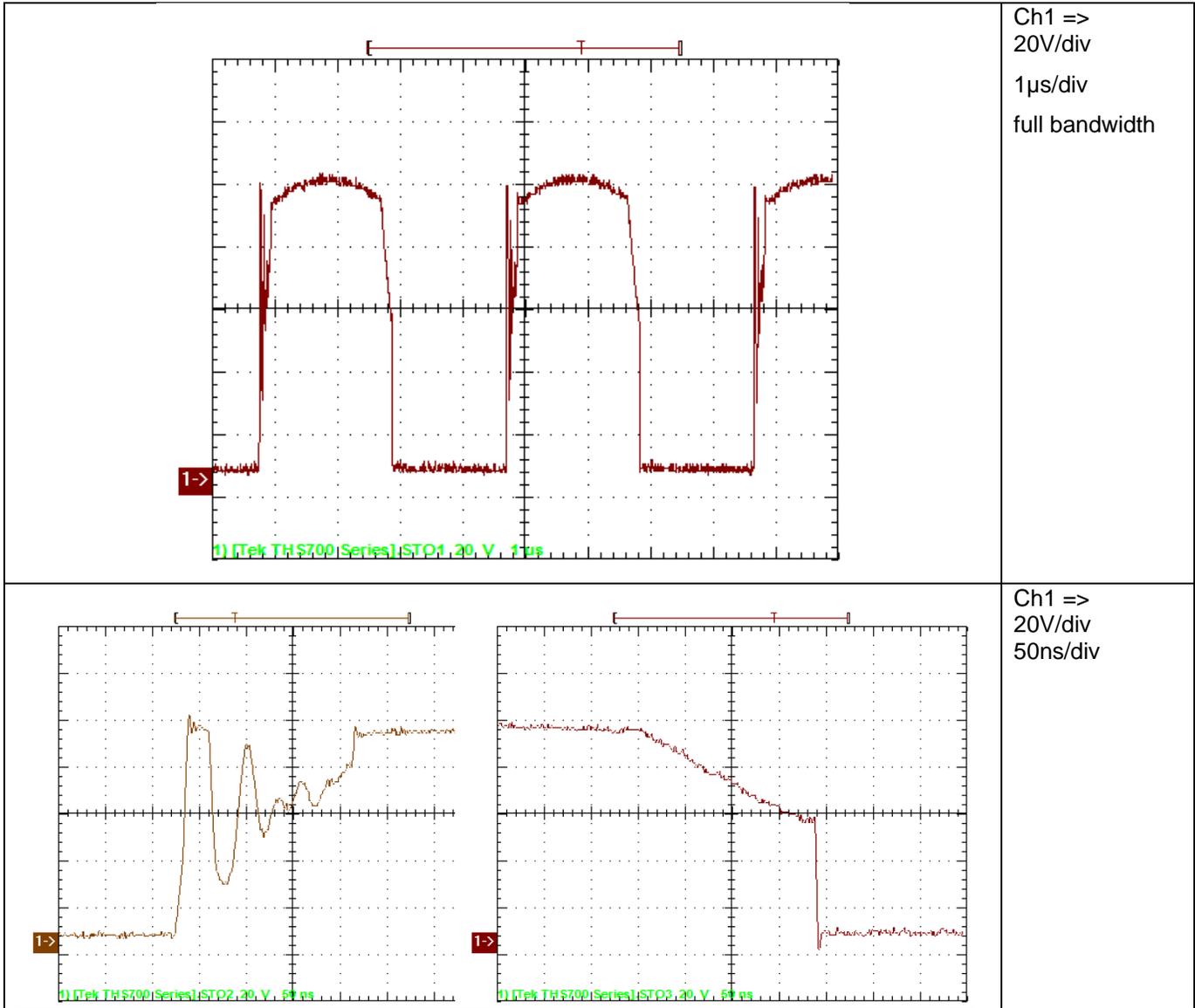


Figure 26

The waveform of the voltage on Q1 (PMOS) drain-source is shown in Figure 27.

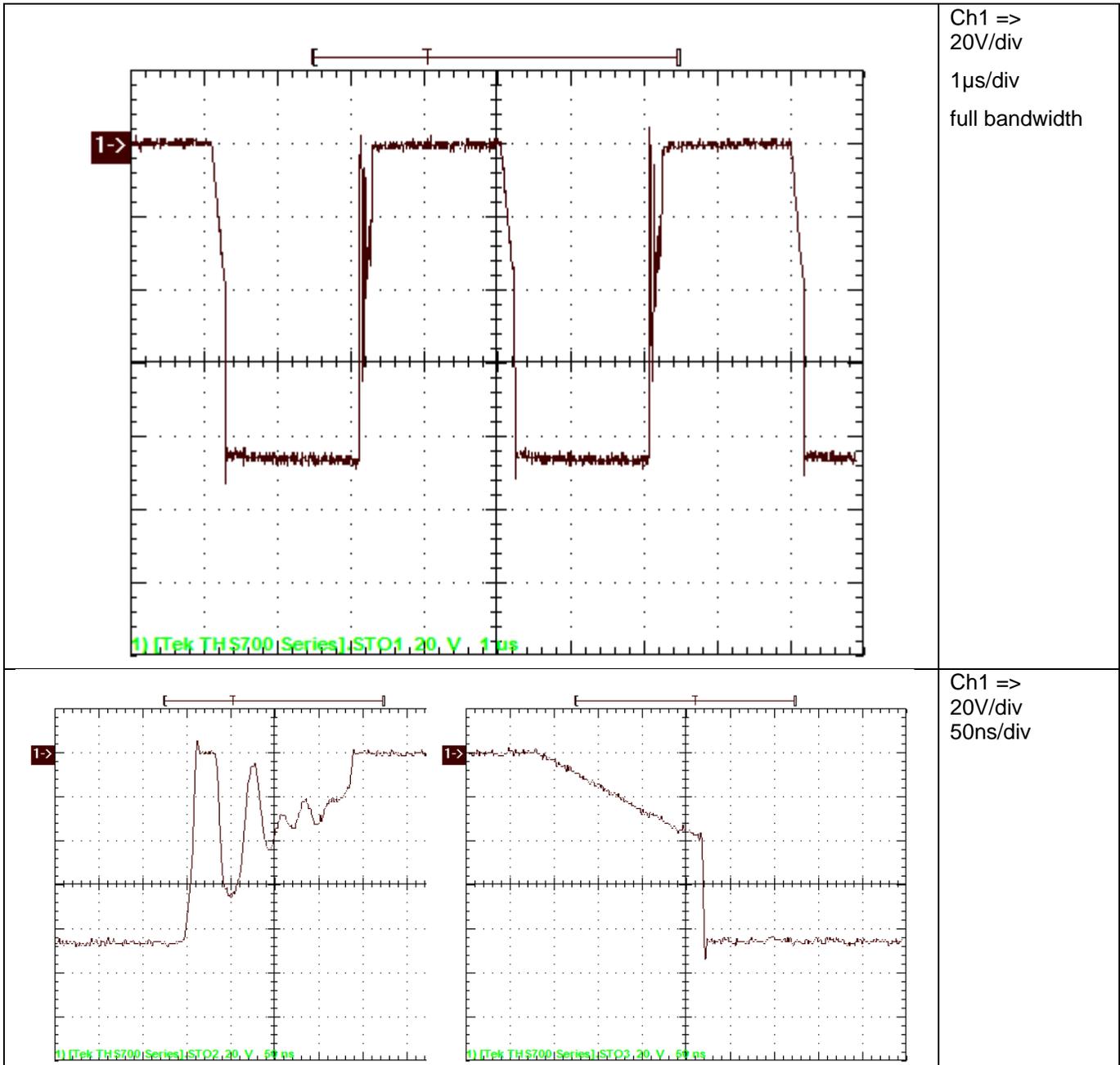


Figure 27

The waveform of the voltage at the transformer output is shown in Figure 28.

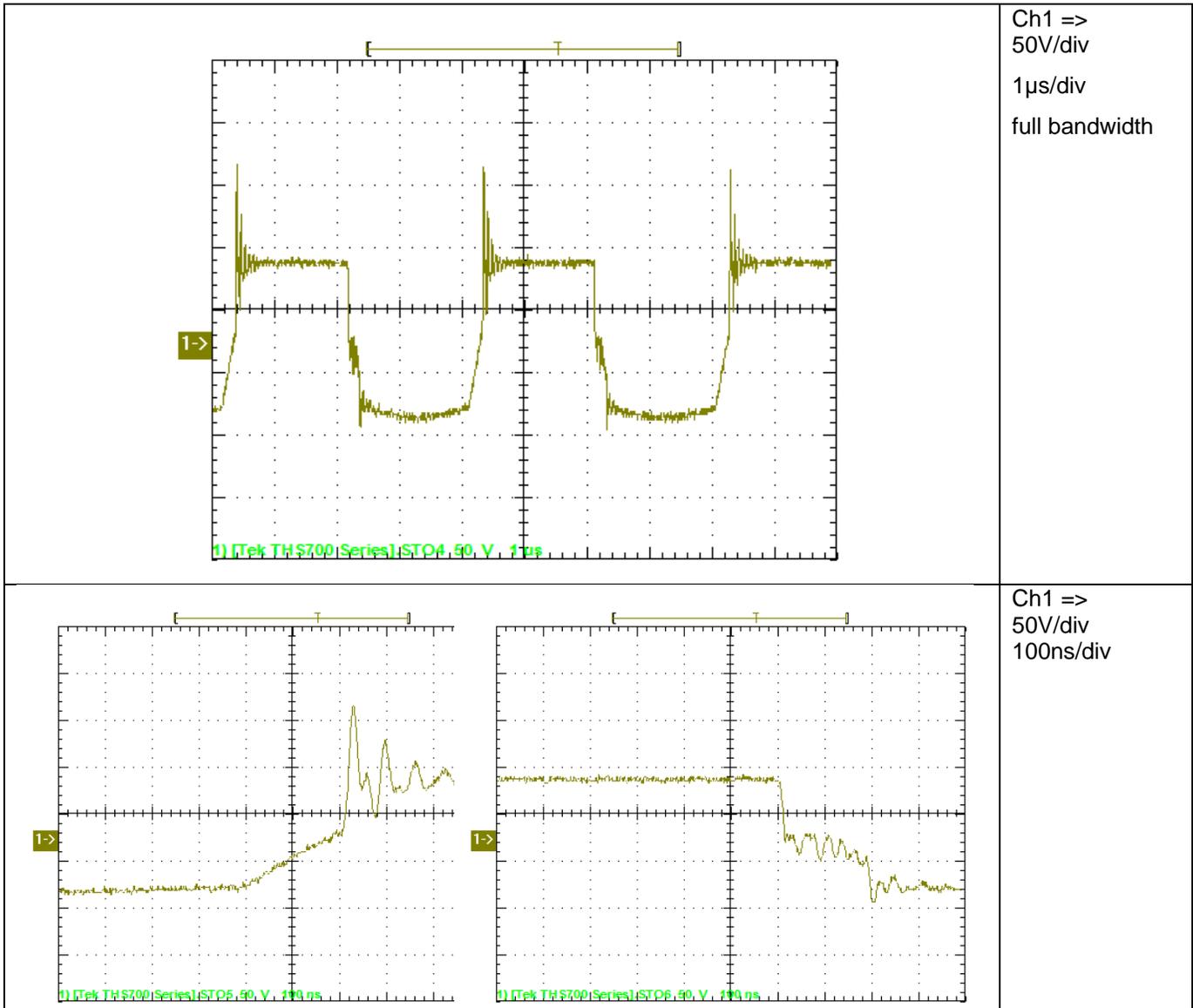


Figure 28

## 10.3 Input Voltage = 60V

The waveform of the voltage on switchnode Q2 (drain-source) is shown in Figure 29.

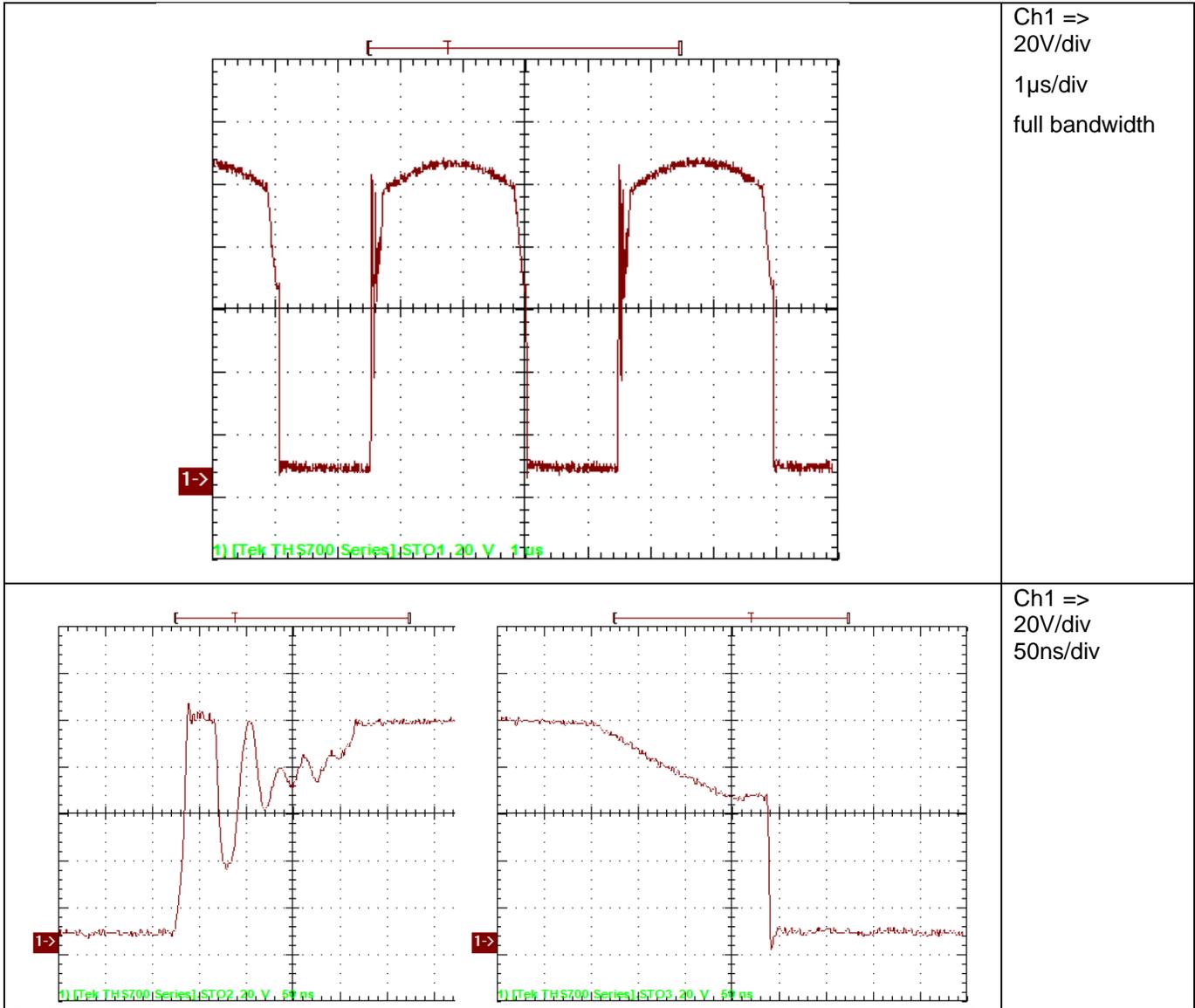


Figure 29

The waveform at Q2 gate-source is shown in Figure 30

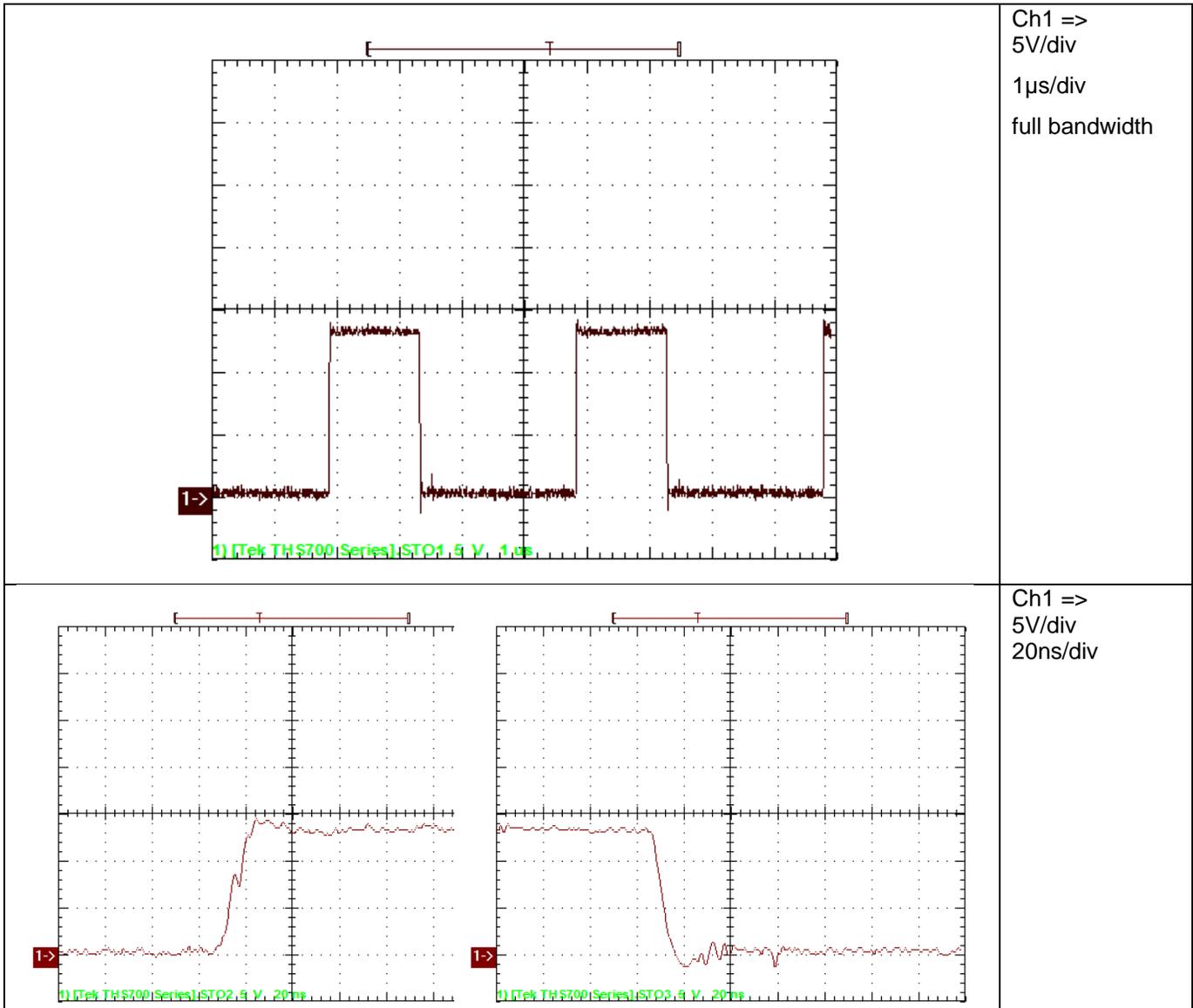


Figure 30

The waveform of the voltage on Q1 (PMOS) drain-source is shown in Figure 31.

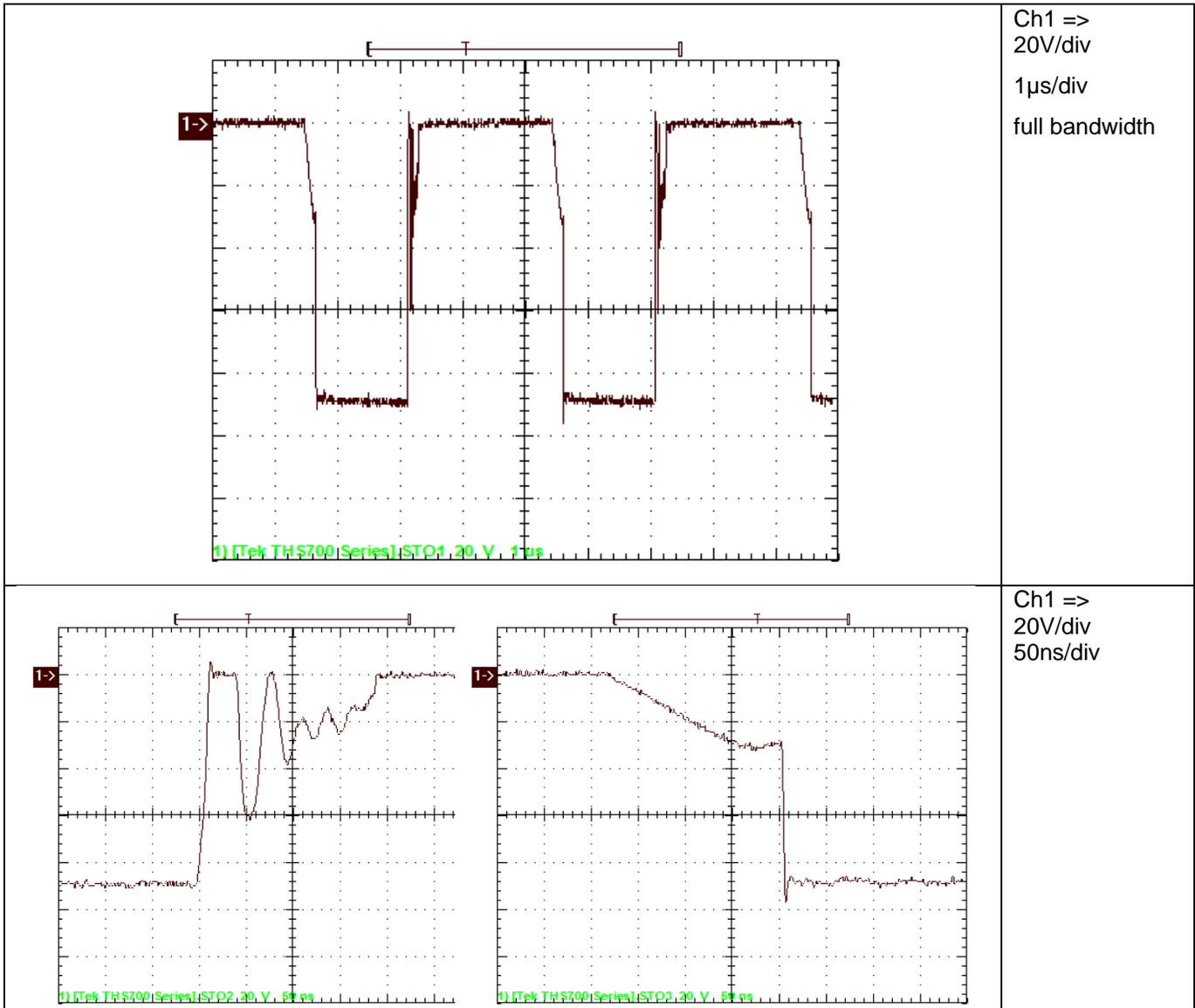


Figure 31

The waveform of the voltage on Q1 (PMOS) gate-source is shown in Figure 32.

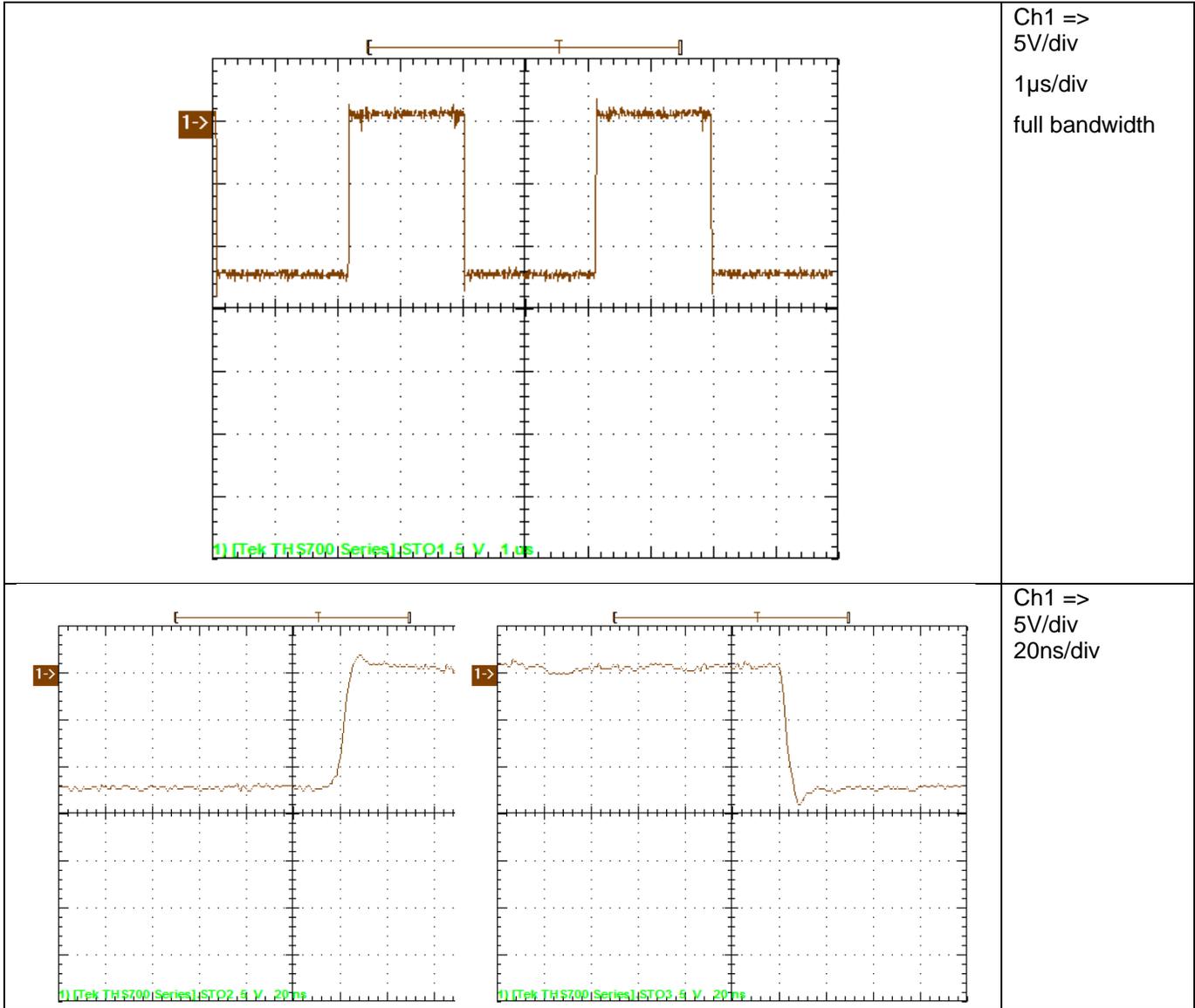


Figure 32

The waveform of the voltage at the transformer output is shown in Figure 33.

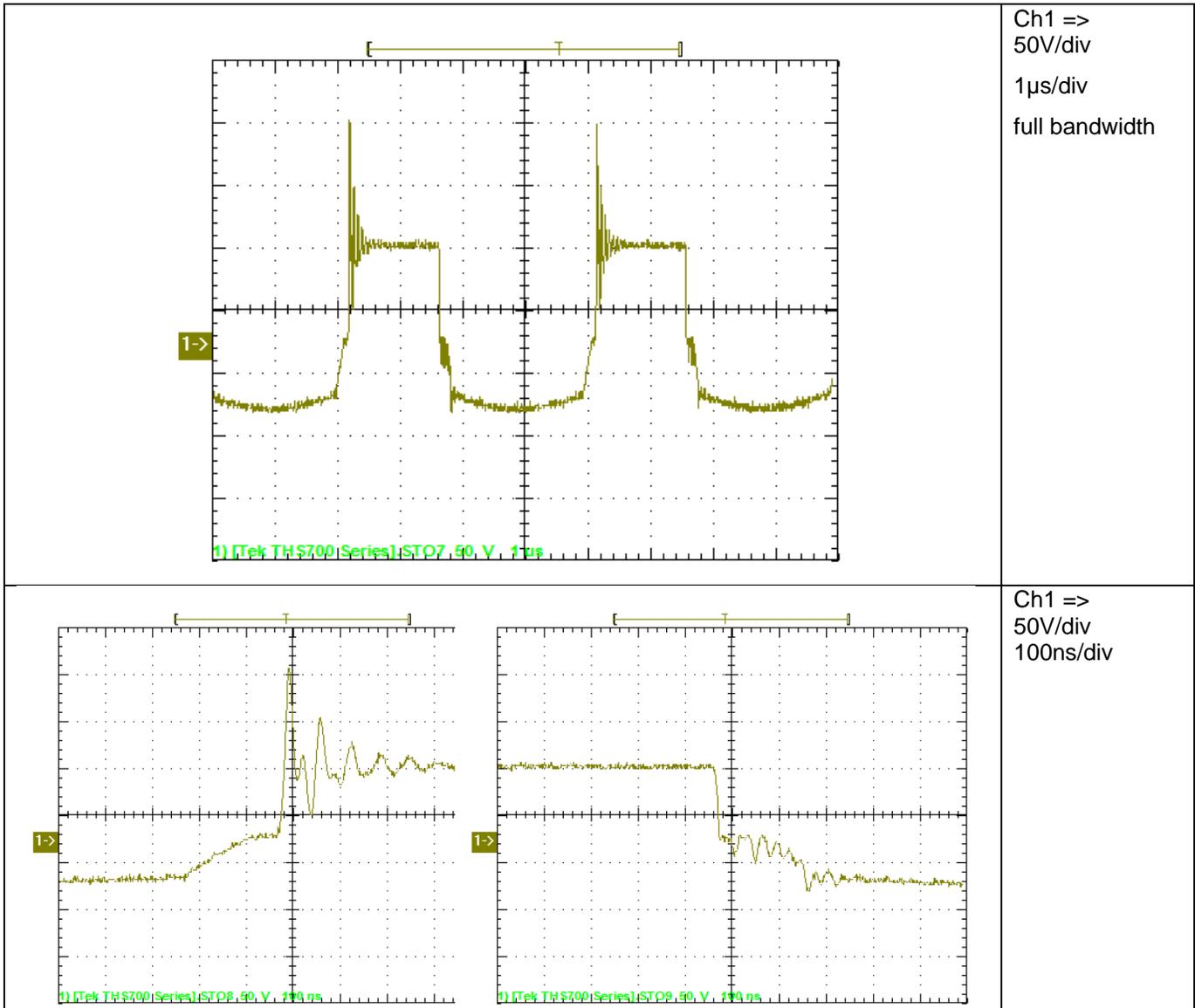


Figure 33

## 11 Thermal Image

Figure 34 shows the thermal image at 48V input voltage and 1A output current.

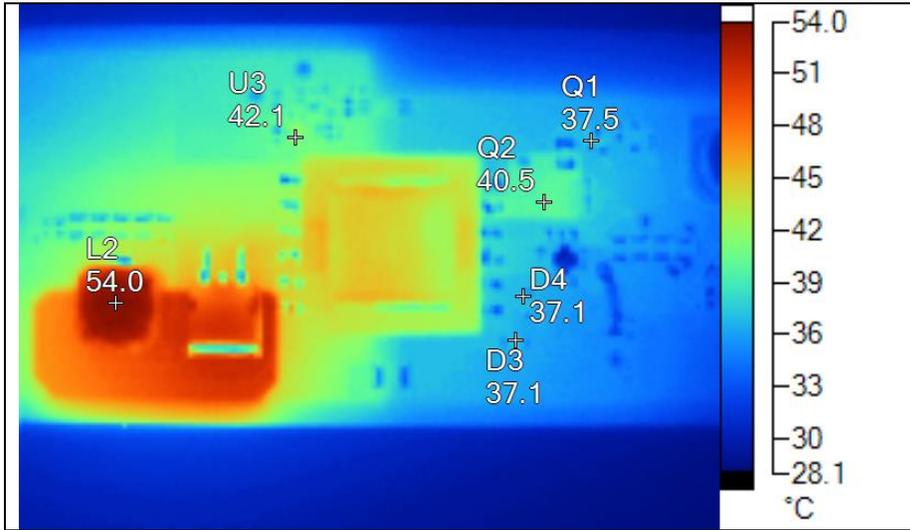


Figure 34

Figure 35 shows the thermal image at 48V input voltage and 1.5A output current.

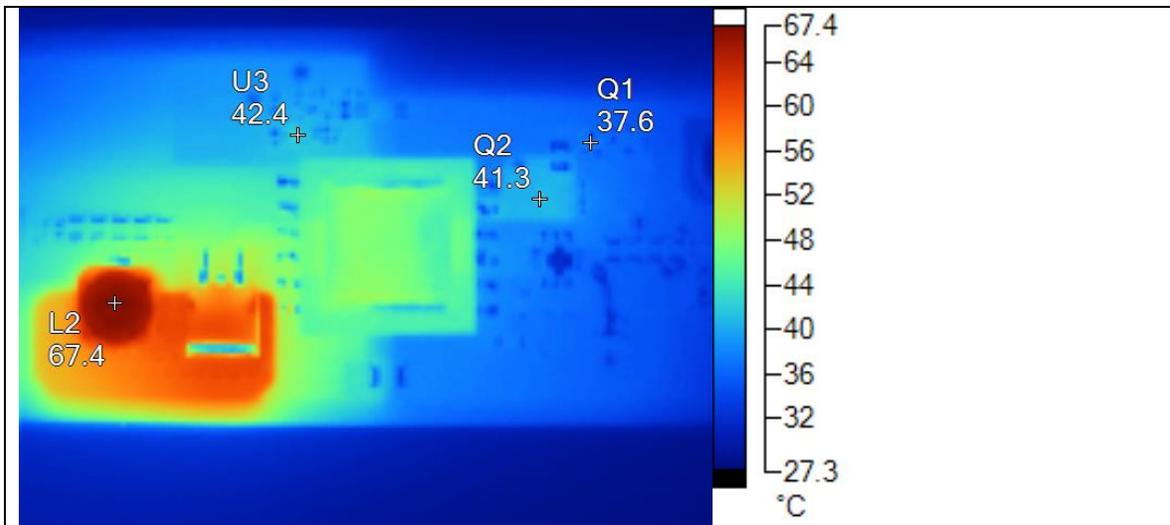


Figure 35

Figure 36 shows the thermal image at 48V input voltage and 2A output current.

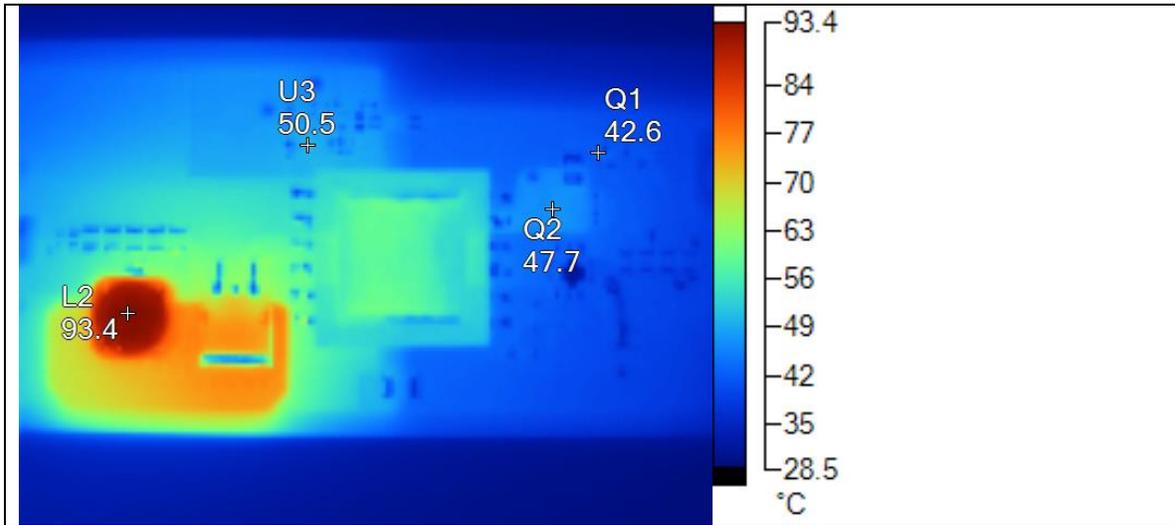



Figure 36

Table 3 summarizes the last three figures.

Name	1A	1.5A	2A
L2	54.0°C	67.4°C	<b>93.4°C</b>
Q2	40.5°C	41.3°C	47.7°C
U3	42.1°C	42.4°C	50.5°C
Q1	37.5°C	37.6°C	42.6°C
D3	37.1°C		
D4	37.1°C		

Table 3

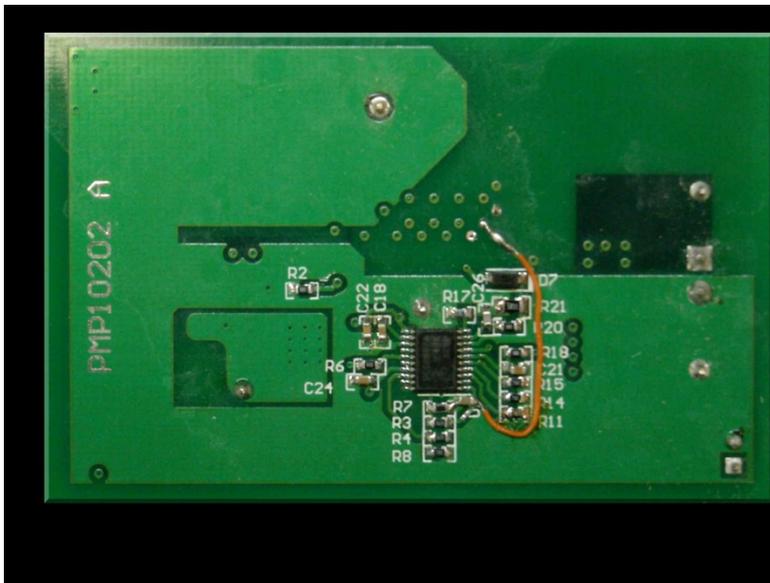For continuous output current >1.5A the output inductor needs a custom design (220uH, 2.5A<sub>rms</sub>, 3.0A<sub>sat</sub>, shielded, ferrite)



## 12 Addendum

Added RC-snubber on switchnode (secondary side) to GND2 across lowside Schottky.  
 Figure 37 is the waveform of the switchnode without snubber circuit.

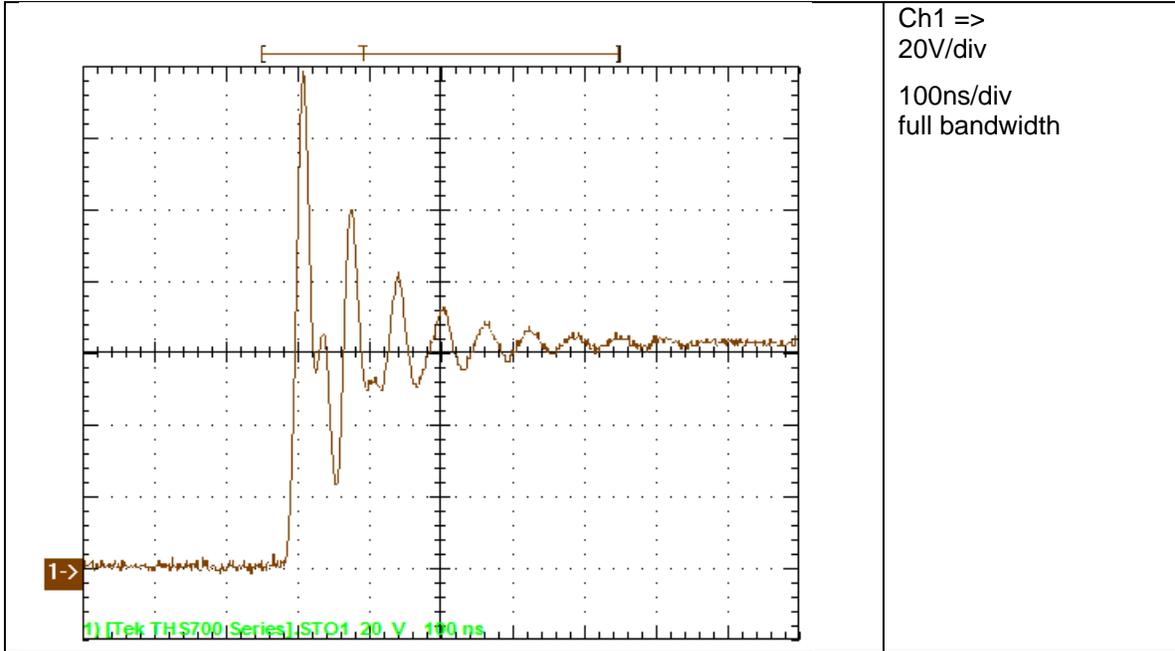


Figure 37

Figure 38 is the waveform of the switchnode with snubber (here used 430pF+270hms)

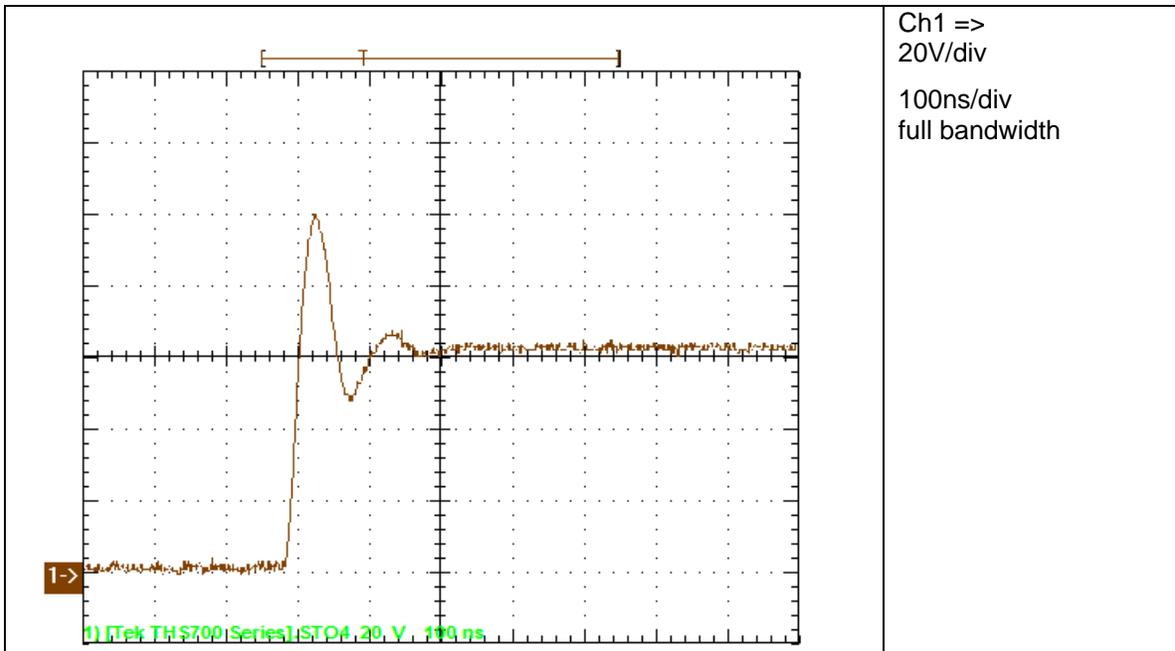


Figure 38

RF noise and overshoot could be reduced simply by adding 470pF (E6) / 33 Ohms (E6) or similar.

Figure 38 is the waveform of the transformer output (with snubber). See Figure 28 to compare the waveform with the waveform without snubber

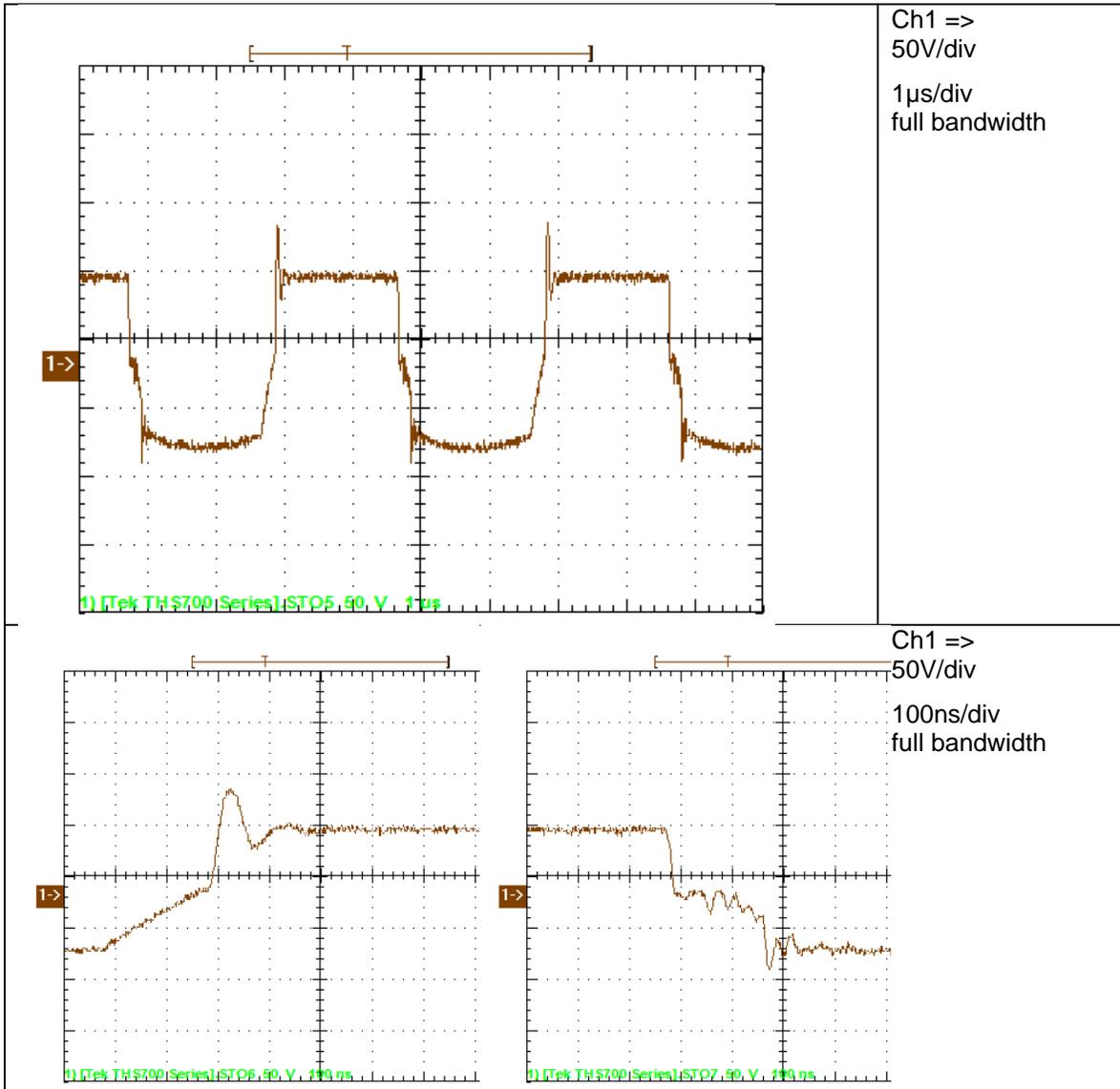


Figure 39

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated