


1 Photo

The photographs below show the top and bottom views of the PMP5411 Rev B demo board. The circuit is built on a PMP5411 Rev A PWB.



2 Active Mode Efficiency – Flyback Supply

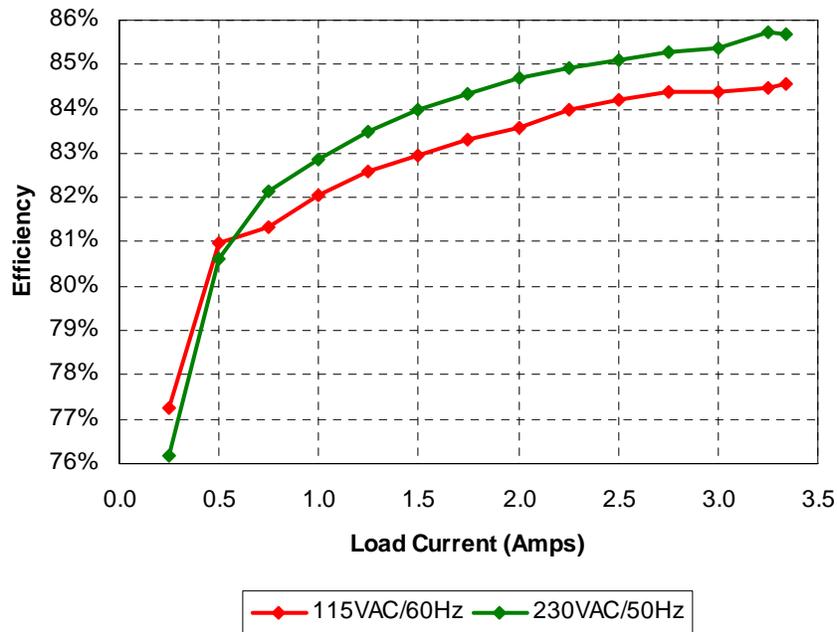The efficiency of the 12V flyback supply is shown in the tables and graph below.



115VAC/60Hz

Iout	Vout	Vin	Iin	Pin	PF	Pout	Losses	Efficiency
0.250	12.08	115.3	0.076	3.91	0.45	3.02	0.89	77.2%
0.500	12.08	115.3	0.132	7.46	0.49	6.04	1.42	81.0%
0.750	12.08	115.2	0.188	11.14	0.52	9.06	2.08	81.3%
1.000	12.08	115.1	0.240	14.72	0.53	12.08	2.64	82.1%
1.250	12.08	114.9	0.289	18.28	0.55	15.10	3.18	82.6%
1.500	12.08	114.9	0.340	21.84	0.56	18.12	3.72	83.0%
1.749	12.08	115.1	0.389	25.36	0.57	21.13	4.23	83.3%
2.000	12.08	115.0	0.438	28.90	0.58	24.16	4.74	83.6%
2.250	12.09	114.9	0.486	32.39	0.58	27.20	5.19	84.0%
2.500	12.09	114.8	0.534	35.89	0.59	30.23	5.67	84.2%
2.750	12.09	115.1	0.581	39.40	0.59	33.25	6.15	84.4%
3.000	12.09	115.0	0.631	42.98	0.59	36.27	6.71	84.4%
3.250	12.09	115.0	0.680	46.51	0.60	39.29	7.22	84.5%
3.338	12.09	114.9	0.686	47.72	0.60	40.36	7.36	84.6%

230VAC/50Hz

Iout	Vout	Vin	Iin	Pin	PF	Pout	Losses	Efficiency
0.250	12.10	230.0	0.047	3.97	0.36	3.03	0.95	76.2%
0.500	12.09	229.9	0.080	7.50	0.41	6.05	1.46	80.6%
0.750	12.09	229.9	0.112	11.04	0.43	9.07	1.97	82.1%
1.000	12.09	229.8	0.143	14.59	0.45	12.09	2.50	82.9%
1.250	12.09	229.8	0.173	18.10	0.46	15.11	2.99	83.5%
1.500	12.09	229.8	0.201	21.59	0.47	18.14	3.46	84.0%
1.749	12.09	229.8	0.229	25.07	0.48	21.15	3.92	84.3%
2.001	12.09	229.7	0.257	28.56	0.48	24.19	4.37	84.7%
2.250	12.09	229.7	0.285	32.04	0.49	27.20	4.84	84.9%
2.500	12.09	229.6	0.312	35.52	0.50	30.23	5.30	85.1%
2.750	12.09	229.6	0.340	38.99	0.50	33.25	5.74	85.3%
3.000	12.09	229.5	0.367	42.48	0.51	36.27	6.21	85.4%
3.250	12.09	229.5	0.394	45.84	0.51	39.29	6.55	85.7%
3.338	12.09	229.5	0.404	47.09	0.51	40.36	6.73	85.7%

3 Active Mode Energy Star Compliance – Flyback Supply

The table below shows the calculations and compliance for “ENERGY STAR® Program Requirements for Single Voltage External Ac-Dc and Ac-Ac Power Supplies” version 2 based on the measured efficiency.

Name Plate Power Rating	Measured Efficiency				Avg. Eff.	Energy Star Req.	Compliant
	25% Load	50% Load	75% Load	100% Load			
30	0.81	0.83	0.83	0.84	0.83	0.83	YES
35	0.81	0.83	0.84	0.84	0.83	0.84	NO
40	0.82	0.83	0.84	0.85	0.84	0.85	NO

4 Light Load Power Consumption – Flyback Supply

The tables below show the input power and efficiency during light load operation of the 12V flyback supply. The No-Load mode requirements of “ENERGY STAR® Program Requirements for Single Voltage External Ac-Dc and Ac-Ac Power Supplies” version 2 require less than 300mW of power dissipation during no load operation.

115VAC/60Hz

Iout	Vout	Vin	Iin (mA)	Pin	PF	Pout	Losses	Efficiency
0.000	12.09	115.0	9.1	0.14	0.13	0.00	0.14	0.0%
0.050	12.08	115.0	24.7	1.06	0.37	0.60	0.46	57.0%
0.100	12.08	114.9	38.7	1.82	0.41	1.21	0.61	66.4%
0.150	12.08	114.9	50.7	2.51	0.43	1.81	0.70	72.2%
0.200	12.08	114.9	62.5	3.21	0.45	2.42	0.79	75.3%


230VAC/50Hz

Iout	Vout	Vin	Iin (mA)	Pin	PF	Pout	Losses	Efficiency
0.000	12.10	230.2	14.1	0.19	0.06	0.00	0.19	0.0%
0.050	12.09	230.2	19.8	1.10	0.24	0.60	0.50	55.0%
0.100	12.09	230.1	27.7	1.94	0.30	1.21	0.73	62.3%
0.150	12.09	230.1	34.4	2.62	0.33	1.81	0.81	69.2%
0.200	12.08	230.1	41.1	3.32	0.31	2.42	0.90	72.8%


5 Efficiency – Point of Load Converters

The efficiency of the point of load converters is shown in the plots below. Efficiency was measured using the TPS54325 and TPS54326 (light load efficient).

TPS54325

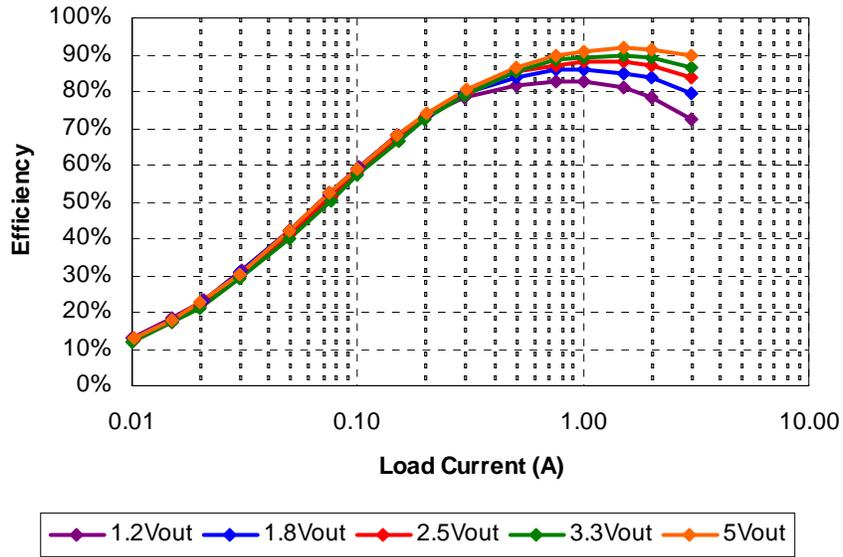


TPS54326

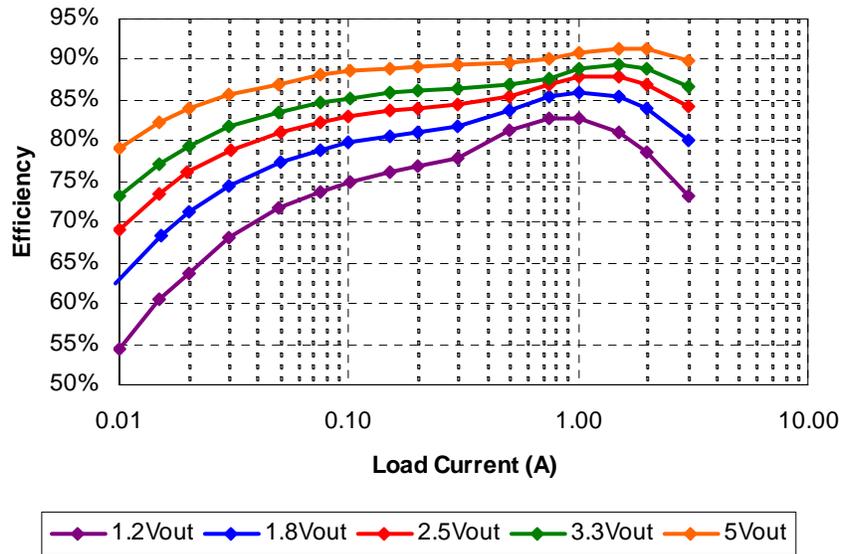


6 Thermal Images

The thermal images below show a top view (left) and bottom view (right) of the board. The ambient temperature was 26°C with no forced air flow. Only the flyback supply was loaded with 3.4A. The point of load converters were not active.

6.1 115VAC, 60Hz Input


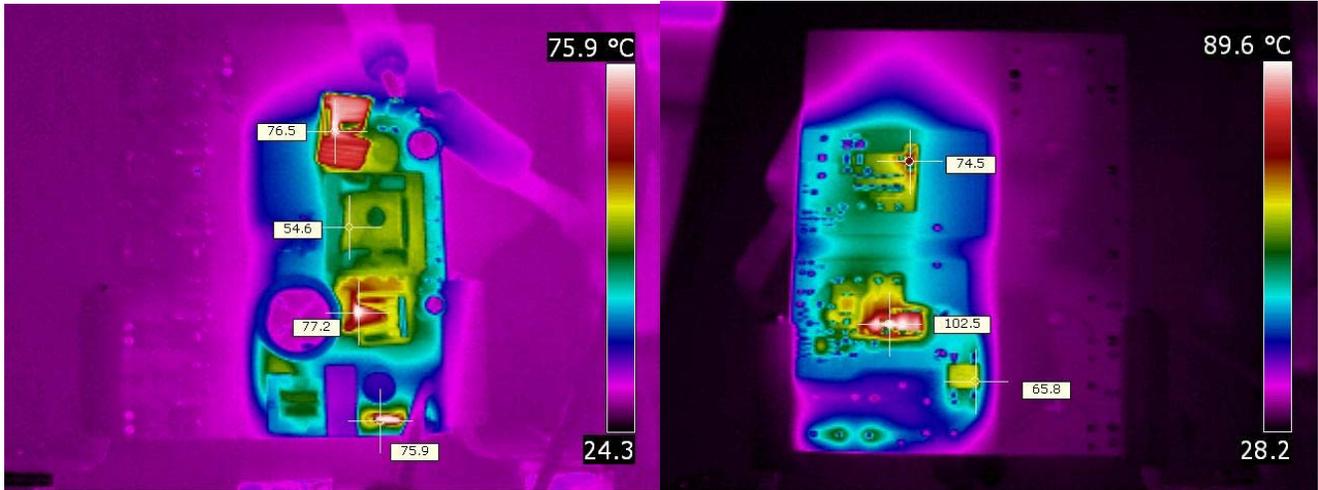


6.2 230VAC, 50Hz Input

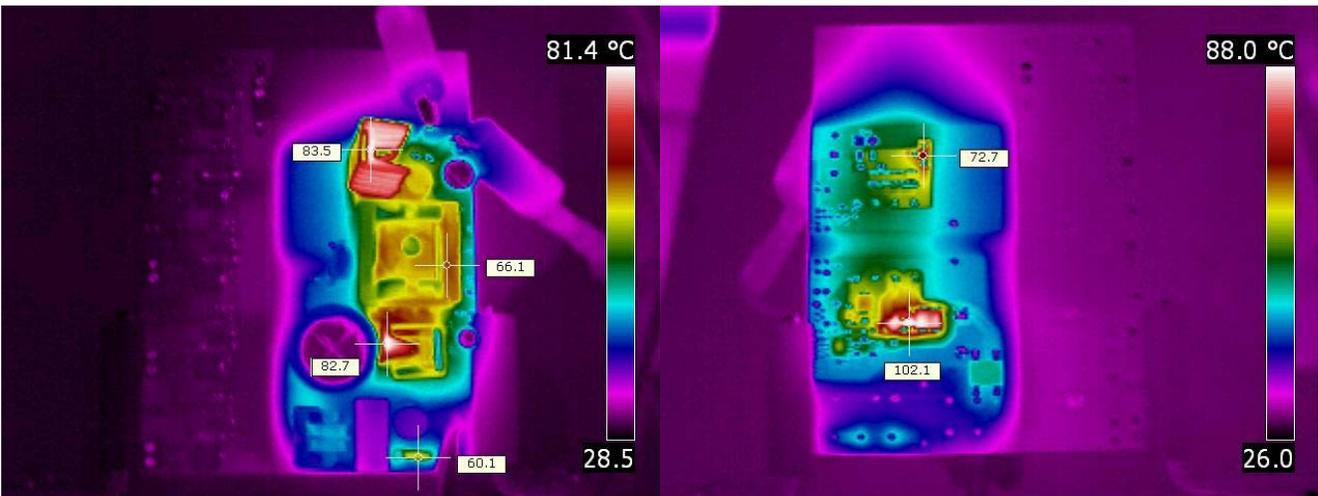



7 Startup – Flyback Supply – No Load

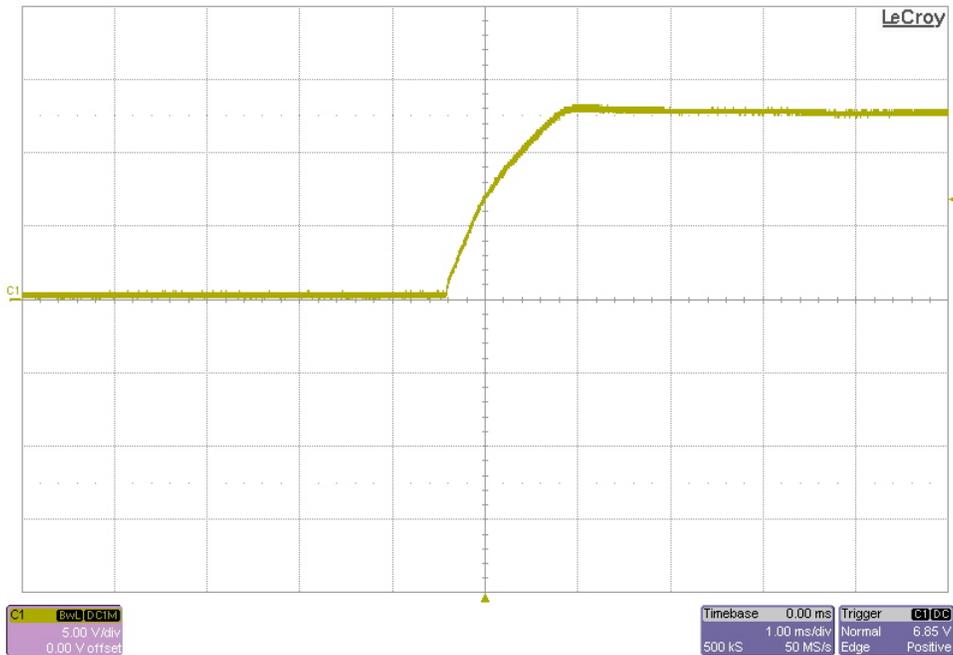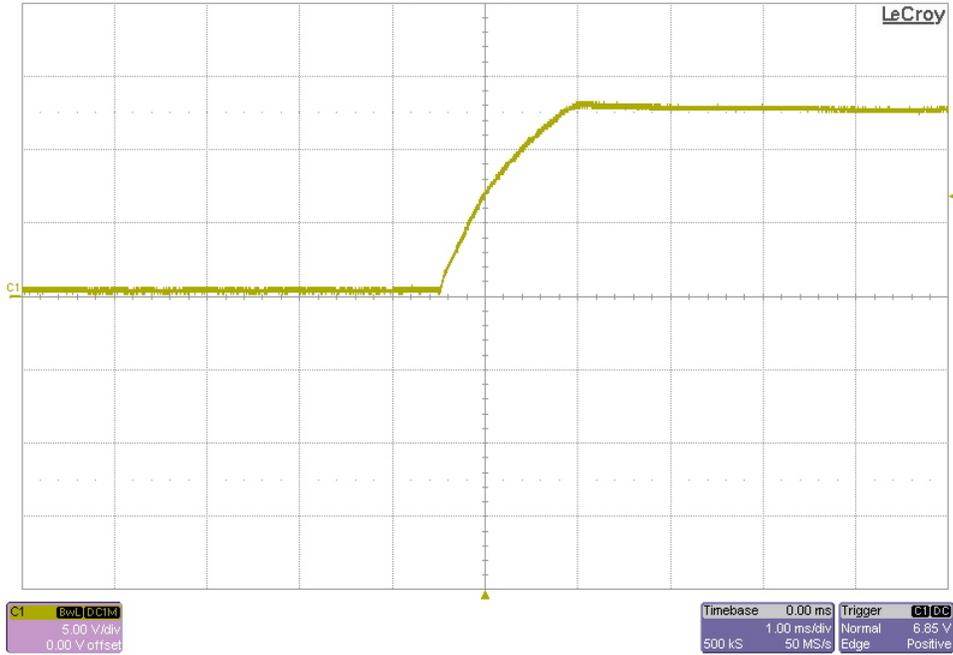The output voltage of the 12V flyback supply at startup is shown in the images below. The output was unloaded. For the top image, the input was 115VAC. For the bottom image, the input was 230VAC.



8 Startup – Flyback Supply – Full Load

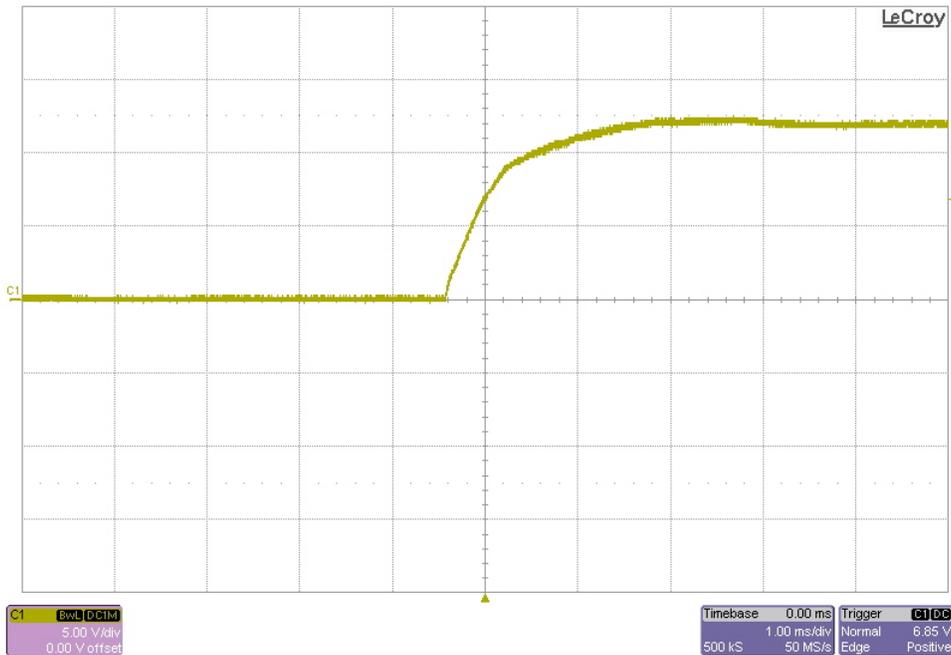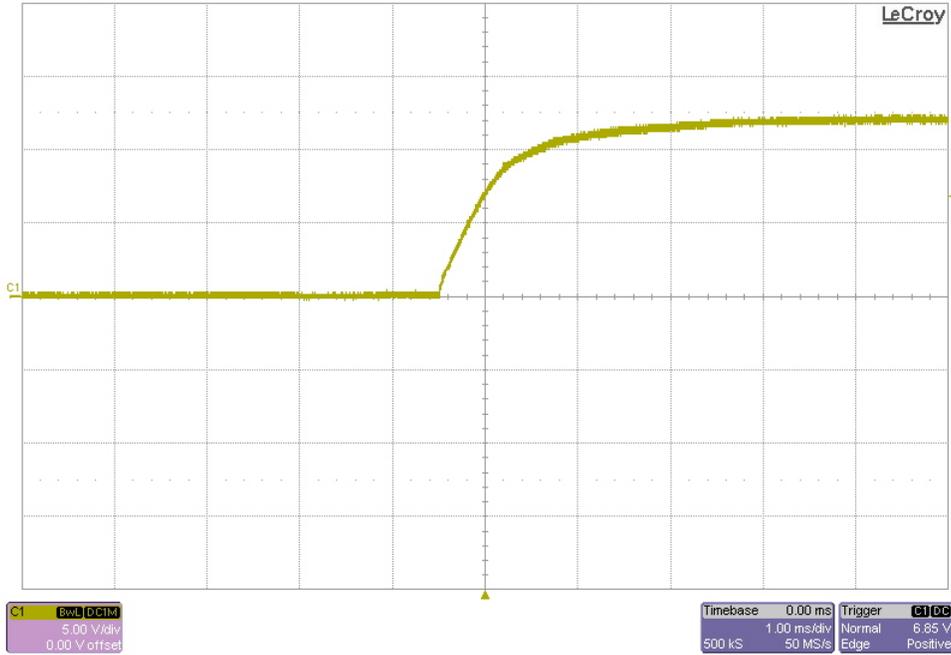
The output voltage of the 12V flyback supply at startup is shown in the images below. The output was loaded with 3.4A. For the top image, the input was 115VAC. For the bottom image, the input was 230VAC.




9 Startup – Point of Load Converters

The output voltage at startup is shown in the images below. The input was 12VDC. The startup waveform is not dependent on load current.


9.1 1.8Vout

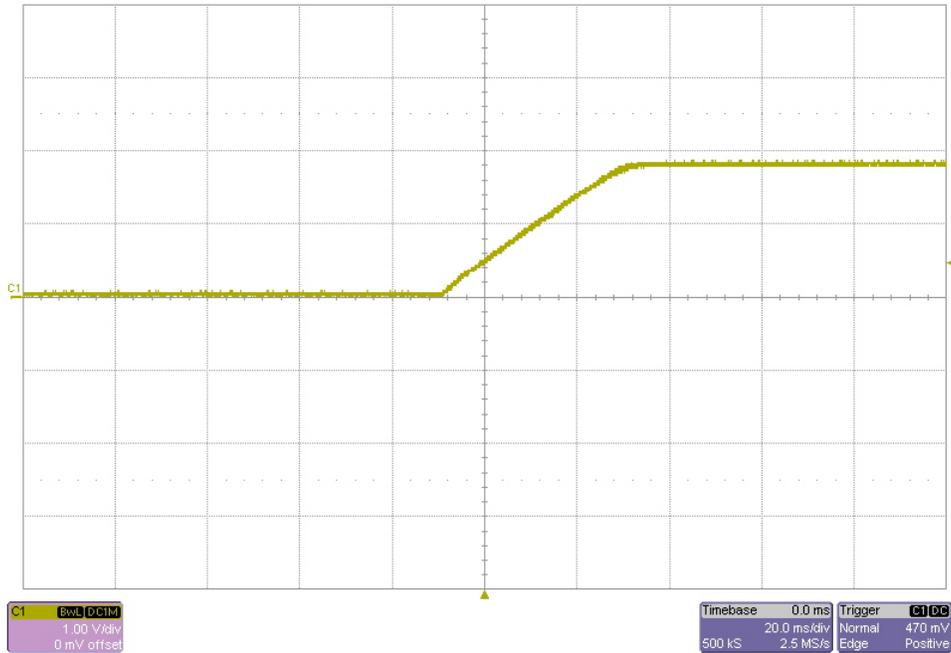


9.2 2.5Vout

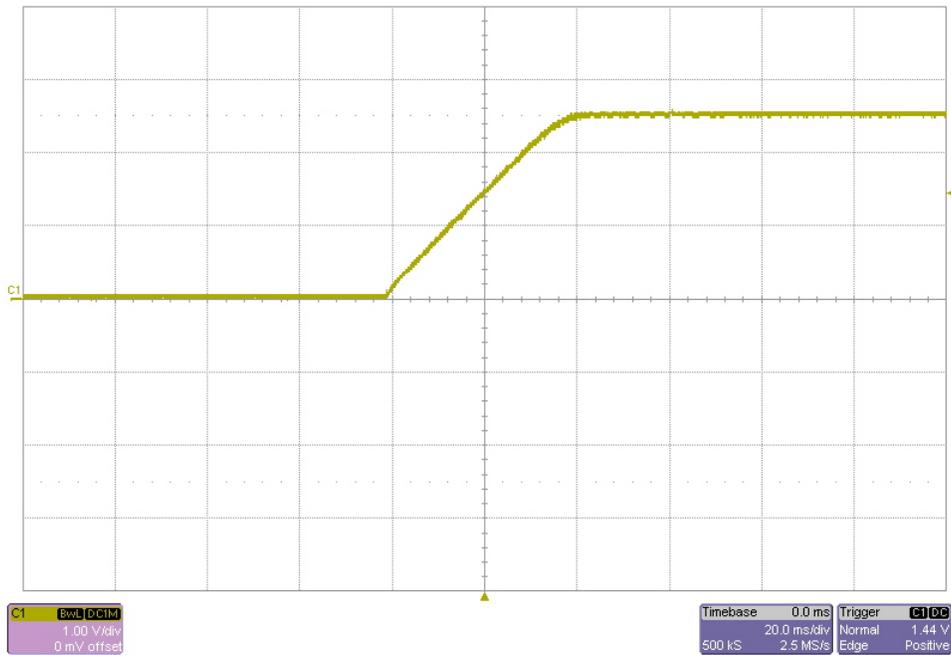

9.3 3.3Vout


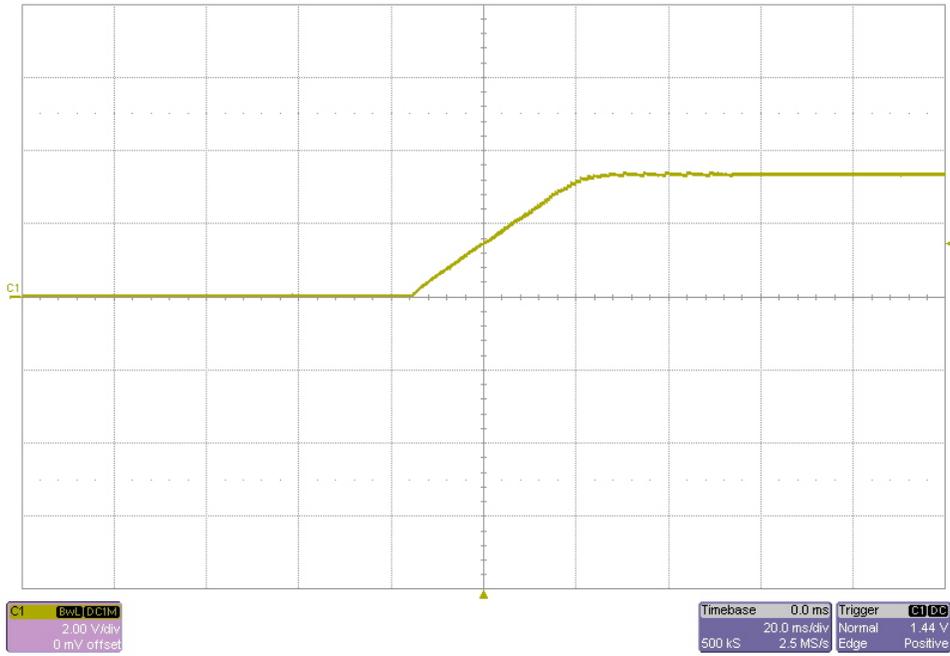


9.4 5Vout

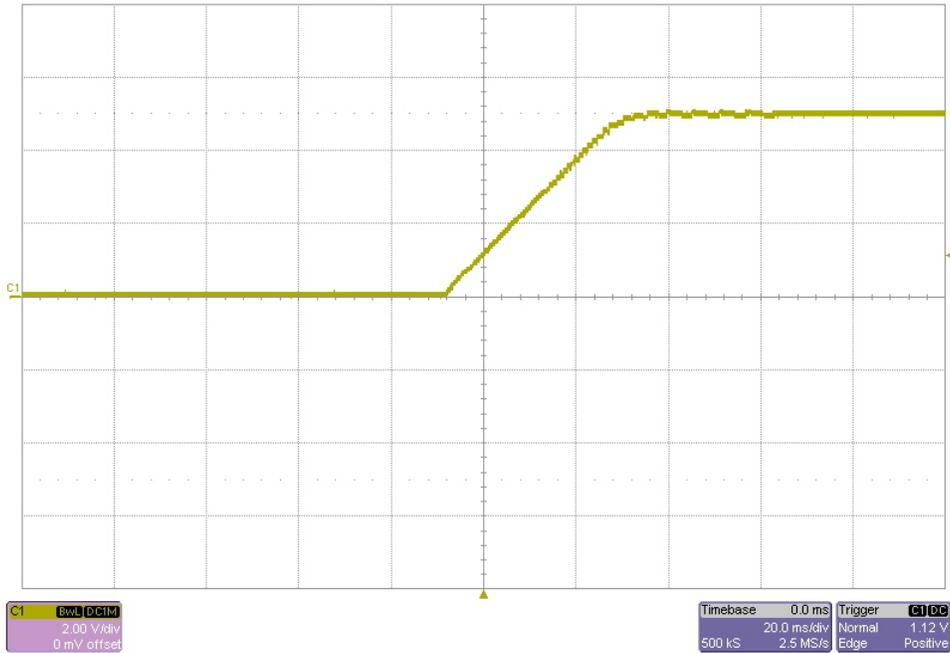



10 Output Ripple Voltage – Flyback Supply – Full Load

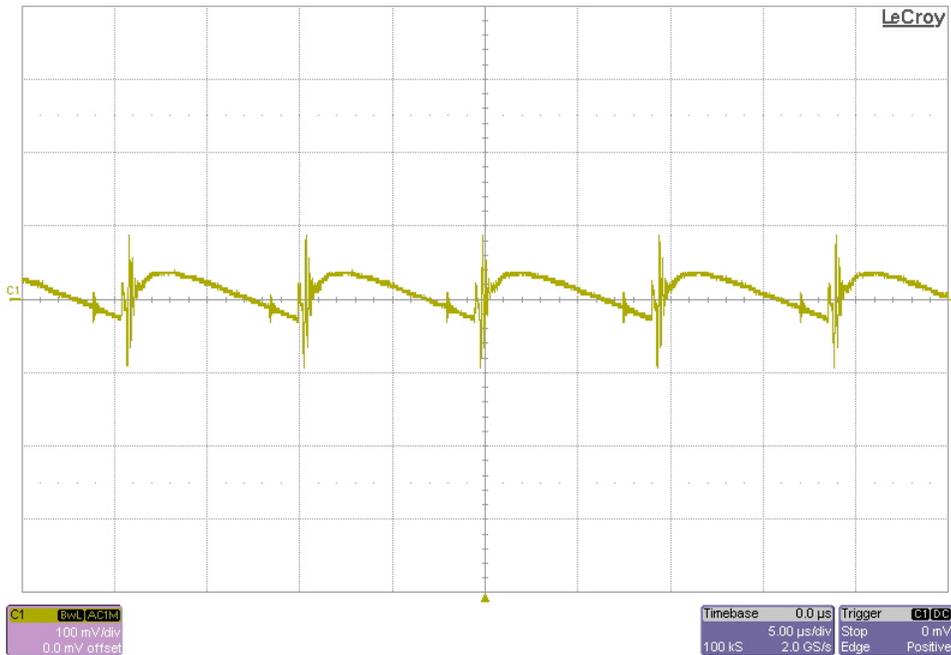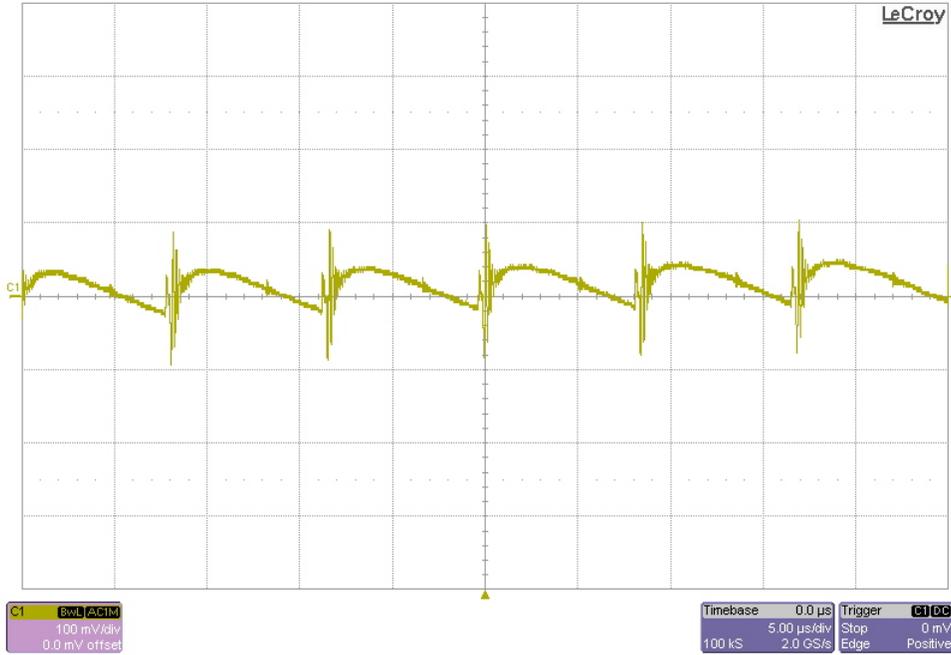The output ripple voltage of the 12V flyback supply during full load (3.4A) operation is shown in the plots below. The top image shows the ripple with an 115VAC input. The bottom image shows the ripple with a 230VAC input.



11 Output Ripple Voltage – Flyback Supply – No Load

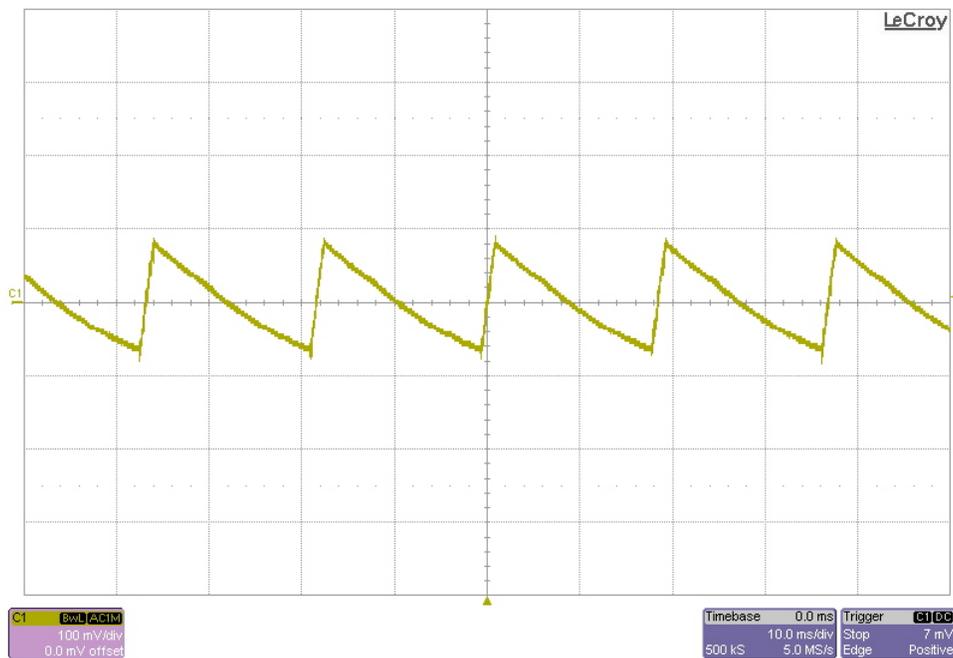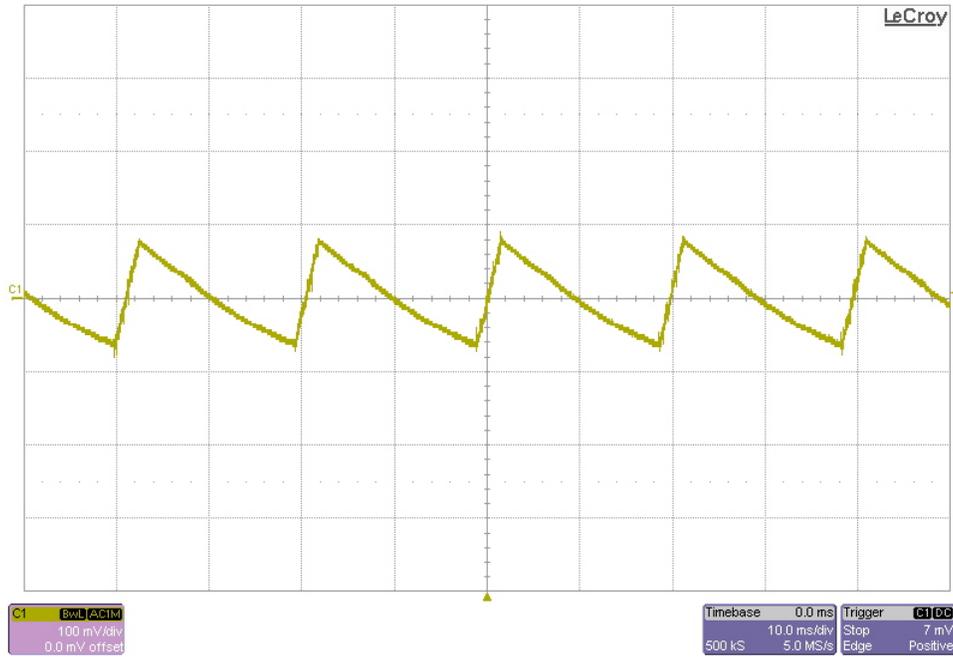
The output ripple voltage of the 12V flyback supply during no load operation is shown in the plots below. The top image shows the ripple with a 115VAC input. The bottom image shows the ripple with a 230VAC input.




12 Output Ripple Voltage – Point of Load Converters

The output ripple voltage is shown in the plots below. The input voltage was 12V, and the output was loaded with 3A.


12.1 1.8Vout

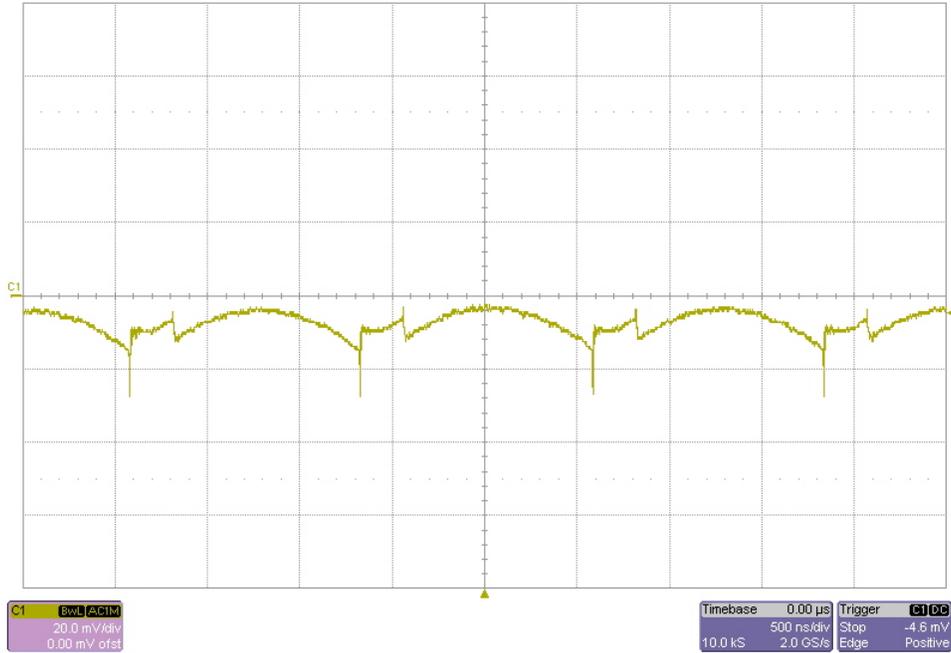


12.2 2.5Vout

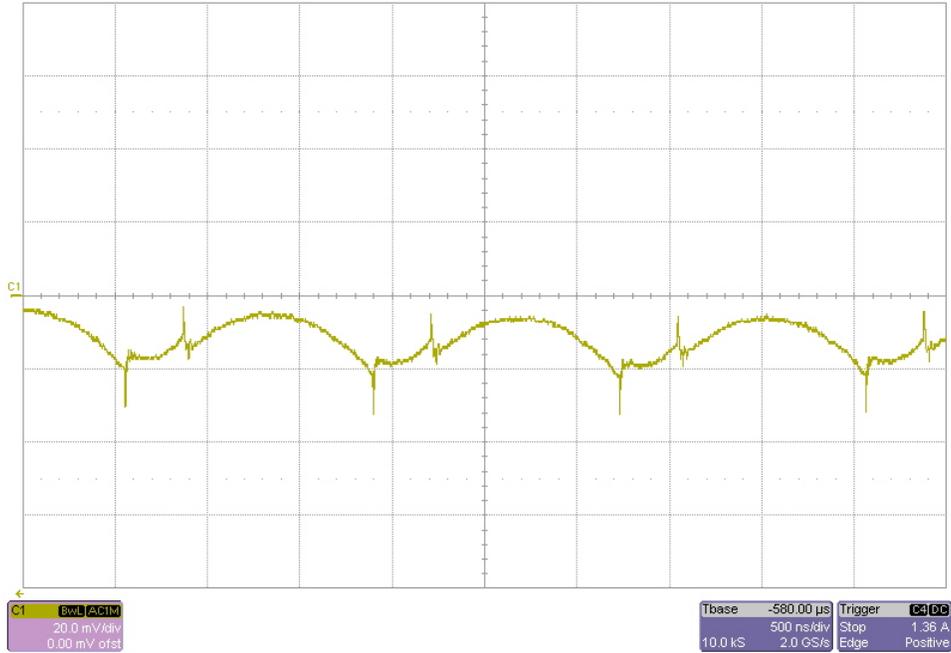

12.3 3.3Vout

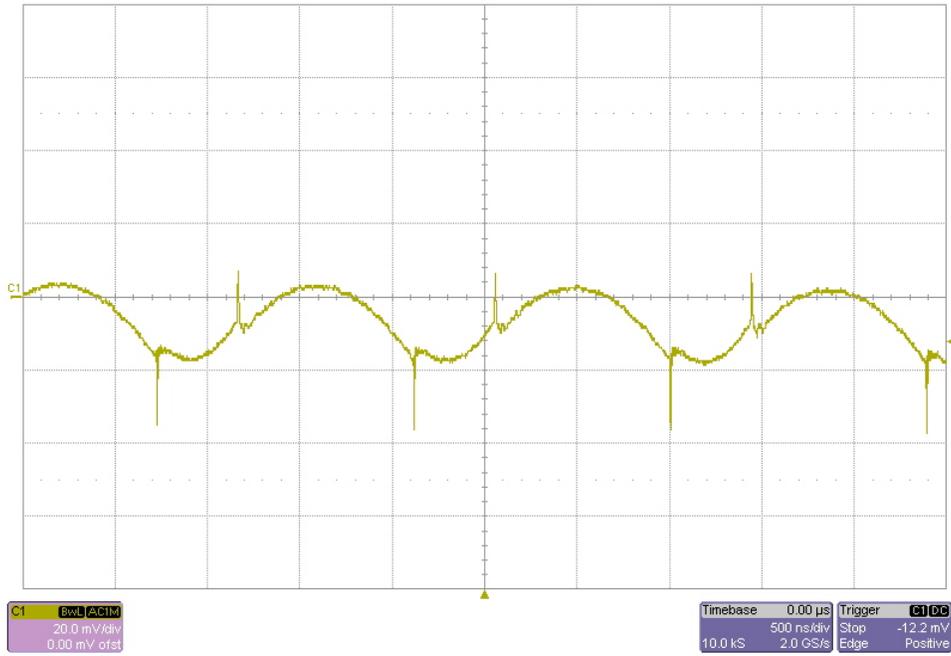

12.4 5Vout


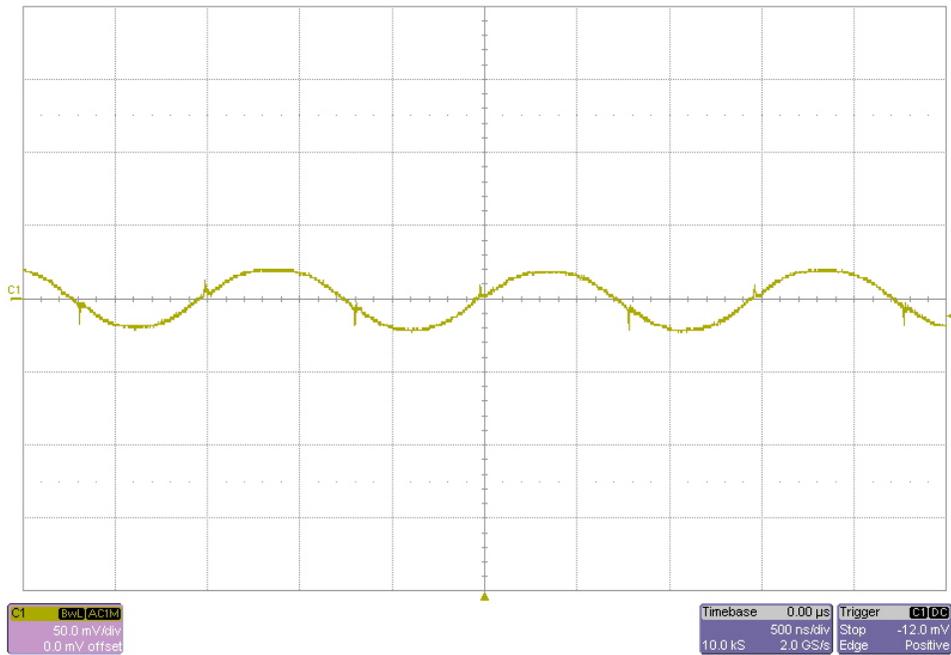


13 Load Transients – Flyback Supply

The images below show the response to a 1.5A to 3A load transient on the 12V flyback supply. For the top image, the input voltage was set to 115VAC. For the bottom image, the input was set to 230VAC.

Channel 1: Vout (ac coupled) 500mV/div


Channel 4: Iout 1A/div

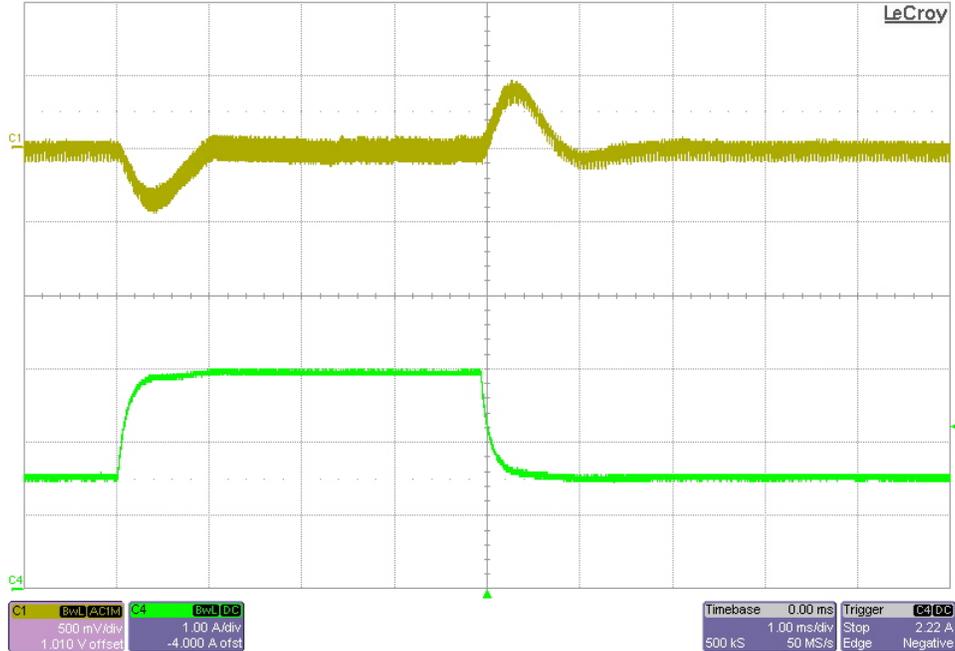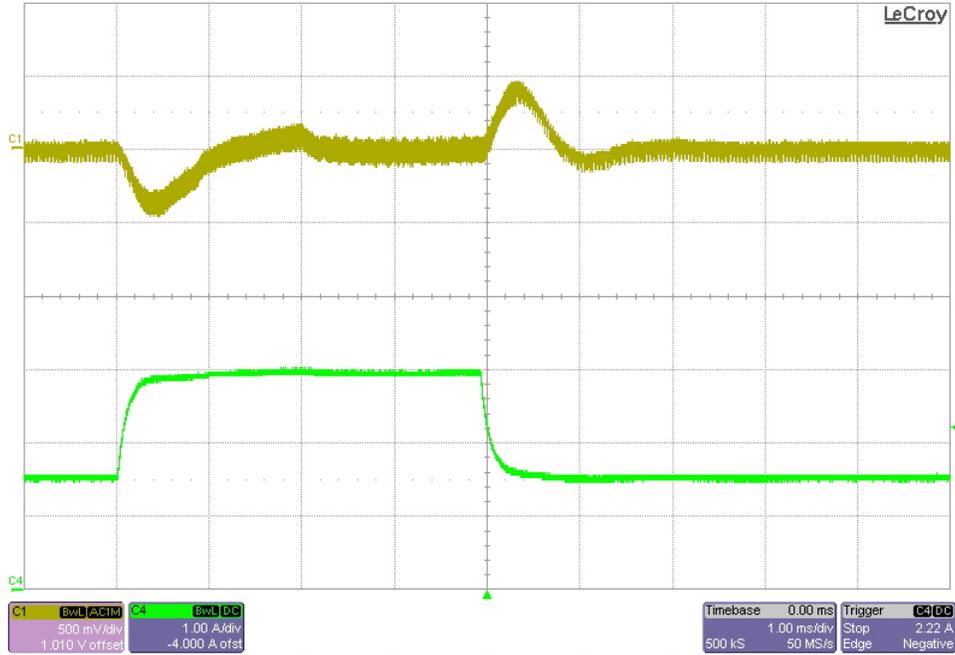


14 Load Transients – Point of Load Converters

The image below shows the response to a 1A to 2A pulsed load. Channel 1 is the AC-coupled output voltage, and channel 4 is the load current. The input voltage was 12V.


14.1 1.8Vout

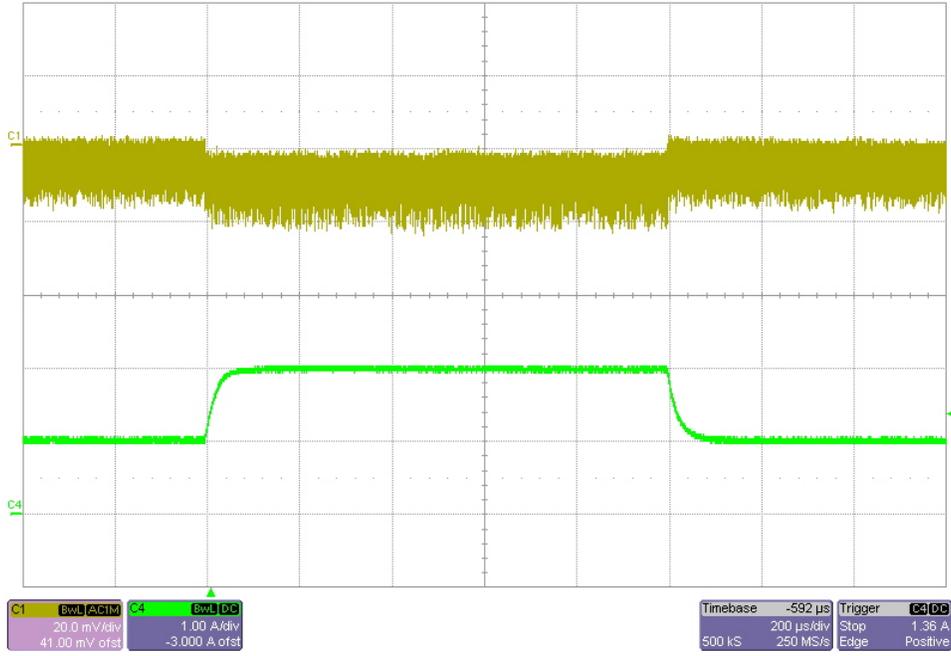


14.2 2.5Vout

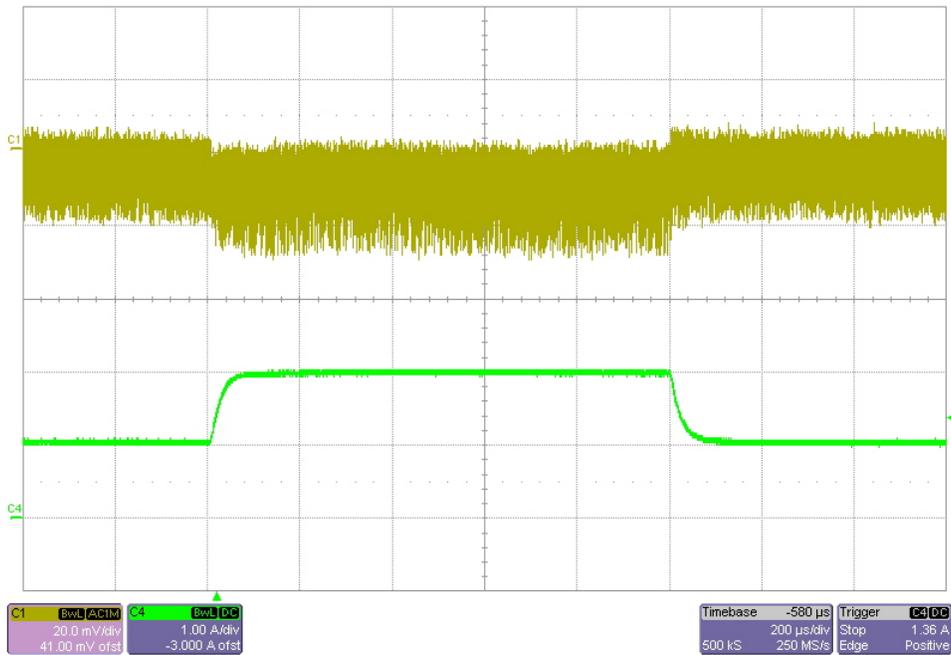

14.3 3.3Vout

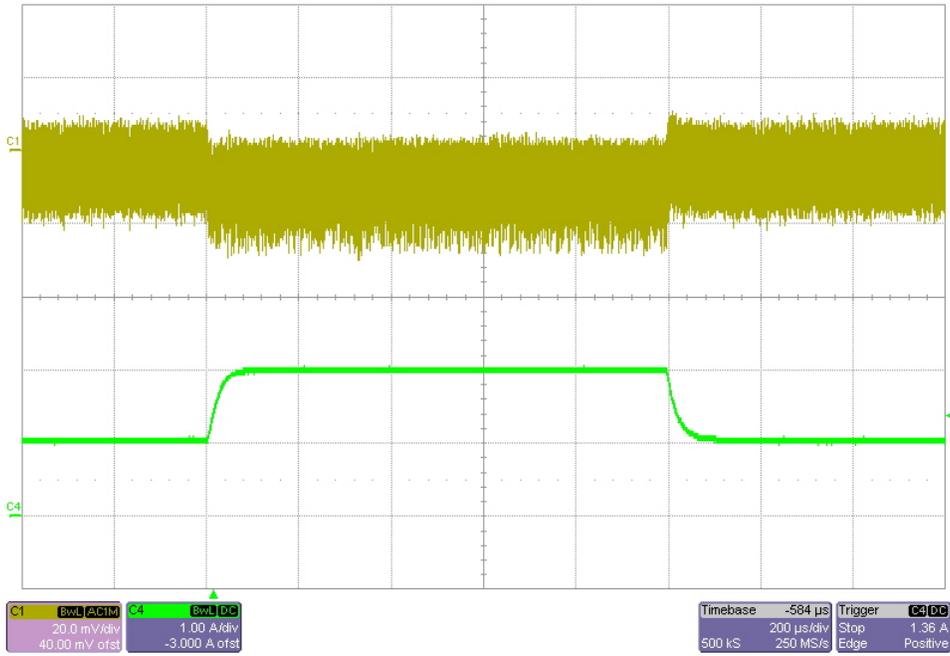


14.4 5Vout

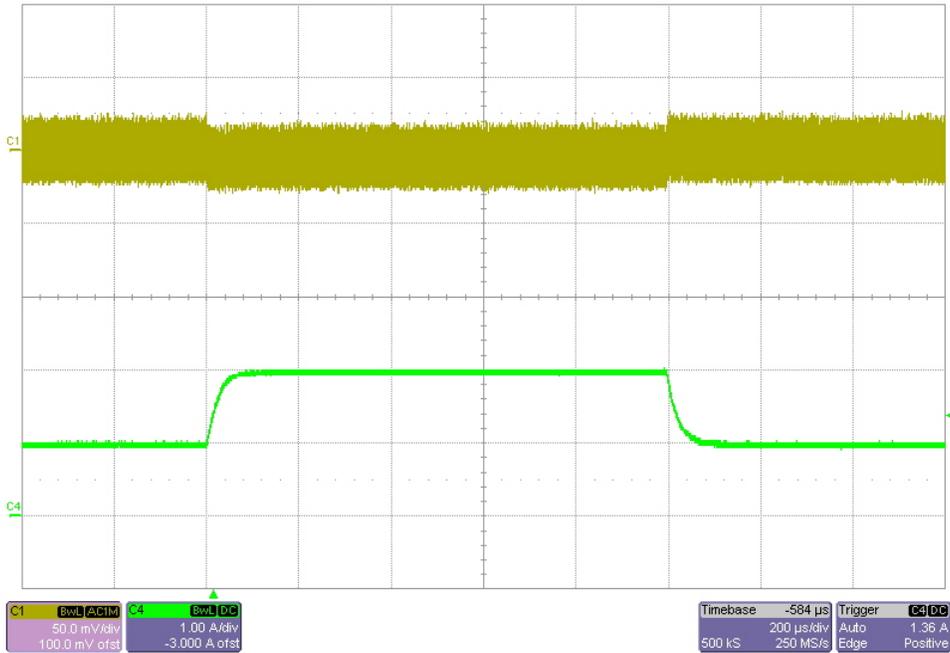

15 Switching Waveforms – Flyback Supply

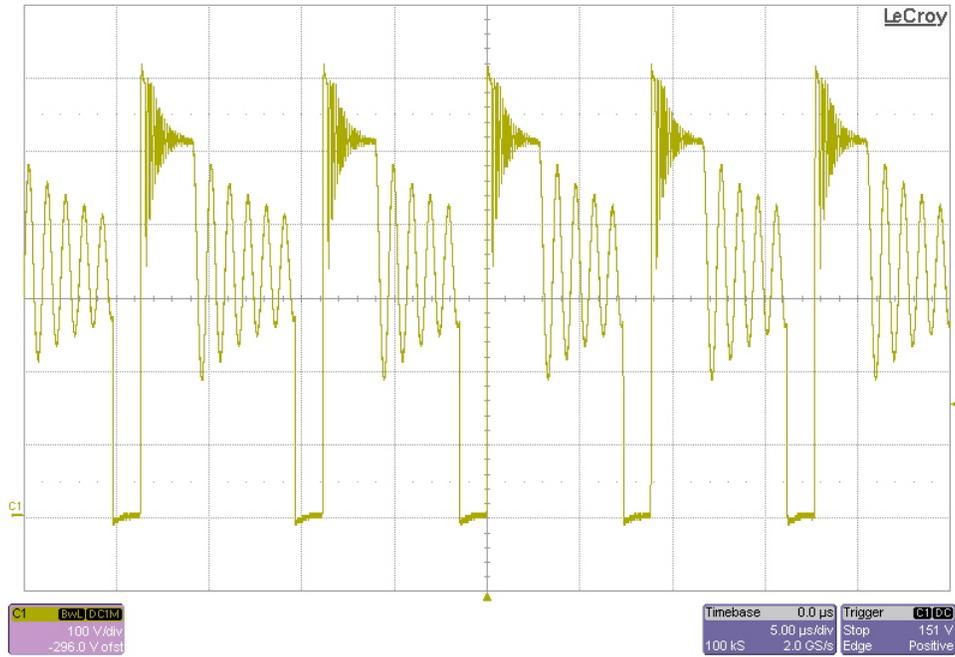The image below shows the drain-to-source voltage waveform on the primary MOSFET (Q1) of the 12V flyback supply. The load was 3.4A. The input was 230VAC.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated