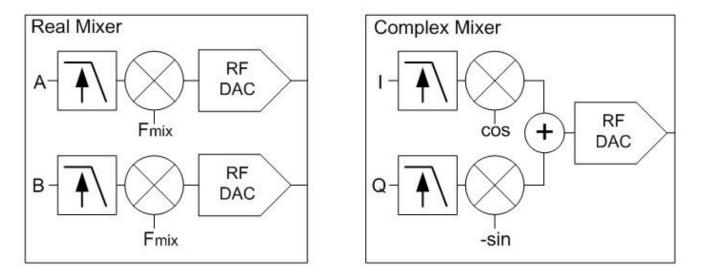
Technical Article **RF Sampling: Digital Mixers Make Mixing Fun**



Russell Hopper

** This is the sixth post in a new RF-sampling blog series that'll appear monthly on Analog Wire **

In a communication system the digital processor feeds or receives digital data at baseband frequencies; this keeps data rates at reasonable speeds for processing. With traditional transceiver architectures the data converter operates with low frequency analog signals. An additional analog mixer is elsewhere in the line-up to convert to or from a higher frequency. With an RF Sampling data converter, the analog signals are directly generated or received at high frequencies. These data converters are equipped with digital mixers to move the baseband signal to or from the desired high frequency location. For simplicity, I will focus on the digital-to-analog converters (DACs), although the concepts are equivalent in analog-to-digital converters (ADCs) with the signal flow in the opposite direction. There are two primary options for digital mixers: real-in to real-out or complex-in to real-out. Figure 1 illustrates the two options in a DAC.





The complex mixer is more advantageous because the input I and Q data occupies half the bandwidth of the output signal and the image and carrier components are naturally suppressed. Unlike its analog equivalent, the digital mixer is near perfect, so the impairments that translate to imperfect sideband suppression or carrier feed-through are not present.

The digital mixer, like its analog equivalent, needs an oscillator source for the mixing operation. An easy implementation is to use a fixed frequency based on the data converter's sample clock. A coarse mixer using a fixed oscillator frequency at the sampling rate divided by four (Fs/4) is very easy to implement. The complex mixer multiplies the I and Q input data by quadrature tones: cosine and sine. When using Fs/4 mixing, the multiplication factors simplify to either 1, 0 or -1: no actual multiplication is required. You can derive the output by extracting the proper data point within the I/Q data stream, which is a simple approach that minimizes current consumption. Figure 2 illustrates the operation for Fs/4 mixing and the pattern for the output.

1



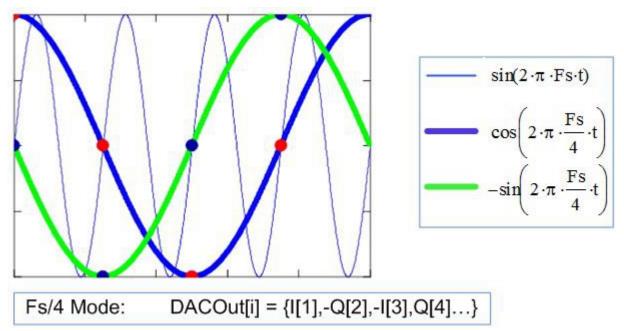


Figure 2. Output Pattern for Complex Fs/4 Mixing

When you need more flexibility, a numerically controlled oscillator (NCO) provides the oscillator function. The NCO is programmed to any arbitrary frequency within the device's Nyquist zone. This allows the signal to be moved via software to any RF band. The NCO uses a fast look-up table to create the oscillator signal. A common implementation utilizes a 32-bit to 48-bit NCO that can provide sub-hertz frequency resolution. In addition, the mixer incorporates phase-adjustment capabilities. Figure 3 is a block diagram of the NCO.

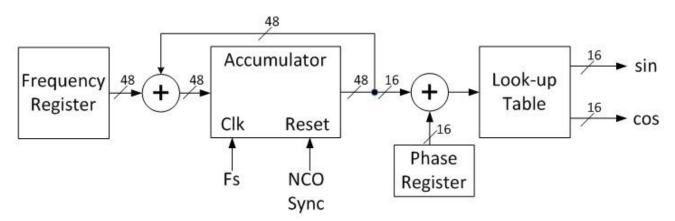


Figure 3. 48-Bit NCO Block Diagram

The digital mixer provides superior performance compared to its analog counterpart. Users can program the exact frequency output on the fly. No hardware modifications are needed. DACs like the DAC38J84 employ a full complement of coarse and fine mixer options for the transmitter. An ADC like the ADC12J4000 incorporates a complex mixer for use on the receiver.

For added flexibility in software-defined architectures, the converter can employ multiple digital mixers so that multiple signals can be independently moved in frequency. This opens up opportunities to support multiband applications very easily and change frequency bands in real time as needed.

In next month's post, I will discuss interleaving to achieve high-sampling-rate RF sampling ADCs.

TEXAS INSTRUMENTS www.ti.com

Additional Resources

- Learn more about designing with data converters in TI's Data Converter Learning Center.
- Watch and learn more about digital mixer usage in the RF sampling series video: Managing data rates.
- Read other blog posts in the RF sampling series.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated