# LMX1501A

AN-935 Upgrading from the MB150X to the National LMX1501A: Replacement

Issues



Literature Number: SNOA317

# Upgrading from the **MB150X to National** LMX1501A: Replacement Issues

### ABSTRACT

Compatibility of the LMX1501AM with the MB1501(std. and options H, and L) and MB1502 (in the FPT-16P-M06 package option) is inspected with emphasis on issues related to dual sourcing, or replacement of the MB150X parts with the LMX1501A. The devices are fundamentally similar, with identical (1501) or compatible (1502) pin outs, and identical programming specifications. Some key differences are found, however, which require attention. These include, package size and footprint, charge pump characteristics, loop filter configuration, and programming timing. In many cases the LMX1501A will easily replace MB150X components with few or no changes at all. This will not be true in all cases, however, particularly when data sheet programming specifications of the MB150X or LMX1501A have not been followed, or when high charge pump tuning voltages are required

#### SIMILARITIES

- Architecture
- Pinout
- Operating voltage (V<sub>CC</sub>)
- · Programming content, format, and levels
- Temperature range
- · RF fin sensitivity and impedance

#### DIFFERENCES


- Package Size/Footprint
- Charge pump magnitude, balance, deadband
- Charge pump maximum supply voltage
- · Loop filter configuration
- Programming timing. (Faster, t<sub>ES</sub>)
- I<sub>CC</sub> vs V<sub>CC</sub> dependency

National Semiconductor **Application Note 935** July 1994


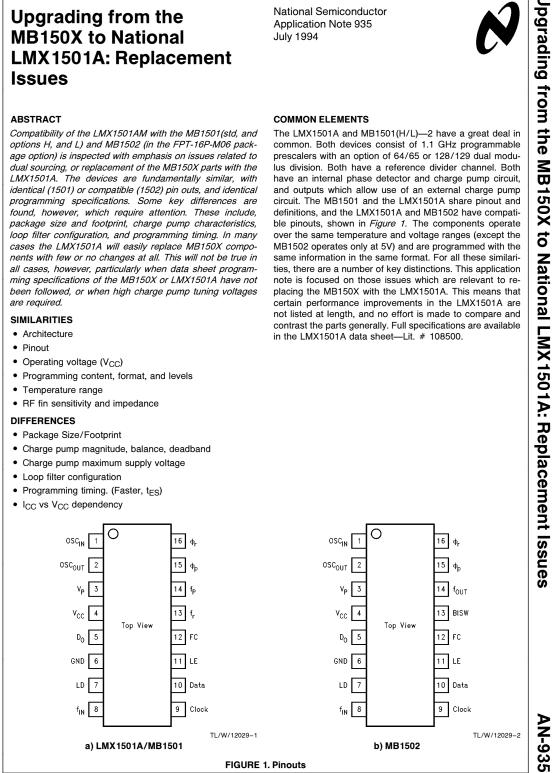
# COMMON ELEMENTS


The LMX1501A and MB1501(H/L)-2 have a great deal in common. Both devices consist of 1.1 GHz programmable prescalers with an option of 64/65 or 128/129 dual modulus division. Both have a reference divider channel. Both have an internal phase detector and charge pump circuit, and outputs which allow use of an external charge pump circuit. The MB1501 and the LMX1501A share pinout and definitions, and the LMX1501A and MB1502 have compatible pinouts, shown in Figure 1. The components operate over the same temperature and voltage ranges (except the MB1502 operates only at 5V) and are programmed with the same information in the same format. For all these similarities, there are a number of key distinctions. This application note is focused on those issues which are relevant to replacing the MB150X with the LMX1501A. This means that certain performance improvements in the LMX1501A are not listed at length, and no effort is made to compare and contrast the parts generally. Full specifications are available in the LMX1501A data sheet-Lit. # 108500.




© 1995 National Semiconductor Corporation TL/W/12029 RRD-B30M115/Printed in U.S.A
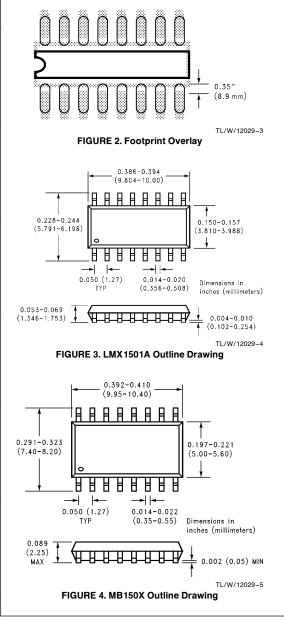
#### PHYSICAL DIFFERENCES

**Footprint.** The MB1501 and MB1502 are packaged in a EIAJ standard SO 16. This package has a pin to pin pitch of 0.050 in. with a **body width of 0.209**". The NSC LMX1501A is packaged in a standard JEDEC SO 16, which has the same pin to pin pitch, but a **body width of 0.153**". *Figure 2* shows an overlay of the JEDEC package on a PCB showing (typical) EIAJ solder pads. *Figures 3* and 4 show the dimensions of the two packages. Re-layout of the PCB is advisable, but probably not mandatory. Although not optimal, lengthening the solder pads by 0.35" will accommodate both package types. *Corrective action: re-design the PCB using a smaller footprint.* 




Loop Filter Configuration. Figure 5 shows a loop filter topology which is often found with MB150X components. It is unusual in its placement of a series resistor before the integrating capacitor. This resistor effectively causes the voltage at the charge pump (CP) output to increase instantaneously as the CP delivers large current pulses. For the MB150X, since the sink current is much higher than the source current, the delivered pump up current is limited by this resistor, which makes the negative frequency lock time increase. Because of the low output of the MB150X charge pump source current, the series R does not noticeably degrade performance, and it allows an additional lowpass filter function to cope with the large spurious response caused by time and current imbalance. The LMX1501A, however, with a balanced CP design, is sensitive to this resistance. It causes current limiting in the CP output,  $D_O$ , which decreases the phase detector gain. This effect is most noticeable in large frequency steps or steps towards the high end of the tuning range. Fortunately, this resistance can be removed with no ill effect. The dramatically lower spurious content of the LMX1501A eases the filter requirement substantially. Corrective Action: remove and short the series resistor at D<sub>O</sub>.

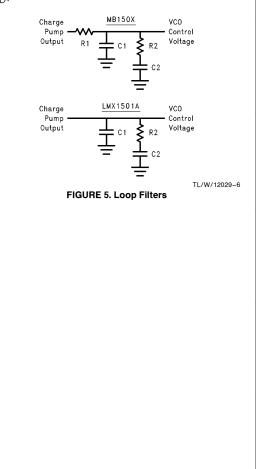
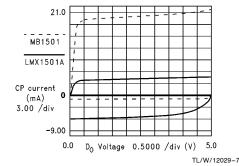
#### ELECTRICAL DIFFERENCES

Charge pump output magnitude and balance of the source and sink currents can be seen in *Figure 6.* Laboratory measurements of the LMX1501A/MB1501 sink and source currents using an HP4145A Semiconductor Parameter Analyzer are shown for  $V_{CC} = V_{PP} = 5V$ .



#### FIGURE 6. Charge Pump Magnitude and Balance


Clearly, from the sample tested, the LMX1501A has better balance between the sink and source currents. The positive and negative lock times are therefore nearly equivalent, and the spurious energy is greatly reduced. Since the overall magnitude of the charge pump currents are markedly different, the PLL dynamics will change due to the change in the closed loop gain. In order to take full advantage of the superior performance of the LMX1501A charge pump, loop filter component values should be optimized corresponding to the LMX1501A phase detector gain. If an external charge pump implementation is used, no modification is necessary. **Corrective Action:** Optimize component values for appropriate loop gain. **Max voltage** on the internal (D<sub>O</sub>), and external ( $\phi_r$ ,  $\phi_p$ ) charge pump of the MB150X is 10V, and 6V for the LMX1501A. Although the bulk of applications, do not require VCO tuning voltages above 5V, certain systems use higher V<sub>CC</sub>'s. The LMX1501A cannot attain voltages higher than 6V because of the N-channel breakdown voltage. For the charge pump of the LMX1501A to drive voltages greater than 6V one may use an active loop filter to provide the DC gain needed. Unfortunately, this is a redesign, and reduces the tuning sensitivity of the PLL. *Corrective Action: If Vp* < 6V. *No Action needed.* 

#### SOFTWARE COMPATIBILITY

If the specifications for the MB150X for the data timing are met, the LMX1501A will also program correctly, since the programming protocol is identical. If t<sub>ES</sub>, the clock to enable set-up time, equals 0 ns, then the LMX1501A will not program correctly, while the MB15XX will continue to function out of spec. The data input timing of the LMX1501A is more than fast enough to accept MB150X programming, since the specification for setup and hold times are  $\geq$ 50 ns, and the MB15XX specification calls for setup and hold times of  $\geq$ 1 µs. **Corrective Action**: Make sure Clock returns to a low state before the rising edge of Load Enable.
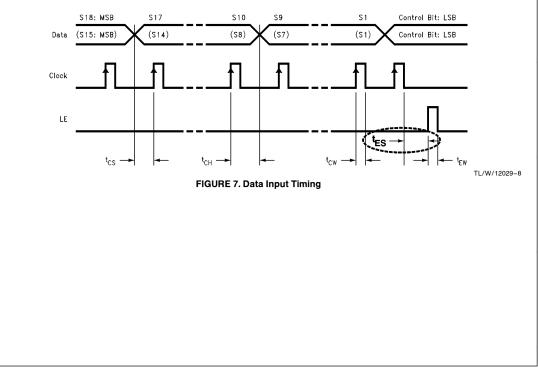
#### ADDITIONAL NOTES

The major differences between the LMX1501AM and the MB150X that merit attention when replacing or dual sourcing have been discussed. Although the user may realize additional performance advantages from the LMX1501A, such as power dissipation, phase noise, lock time, and spurious performance, these are not discussed in depth, with the emphasis put on fundamental similarities and differences in the functional operation of the parts. With attention to the package size, loop filter, and programming, the LMX1501A will easily replace the MB150X series for many applications.



# LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

National Semiconductor Corporation 1111 West Bardin Road Arlington, TX 76017 Tel: 1(800) 272-9959 Fax: 1(800) 737-7018	National Semiconductor   Europe Fax: (+49) 0-180-530 85 86   Email: cnjwge@tevm2.nsc.com   Deutsch Tei: (+49) 0-180-530 85 85   English Tei: (+49) 0-180-532 78 32   Français Tei: (+49) 0-180-532 93 58   Italiano Tei: (+49) 0-180-534 16 80	National Semiconductor Hong Kong Ltd. 13th Floor, Straight Block, Ocean Centre, 5 Canton Rd. Tsimshatsui, Kowloon Hong Kong Tei: (852) 2737-1600 Fax: (852) 2736-9960	National Semiconductor Japan Ltd. Tei: 81-043-299-2309 Fax: 81-043-299-2408
---	--	--	--

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

# **IMPORTANT NOTICE**

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

	Products		Applications	
	Audio	www.ti.com/audio	Communications and Telecom	www.ti.com/communications
	Amplifiers	amplifier.ti.com	Computers and Peripherals	www.ti.com/computers
	Data Converters	dataconverter.ti.com	Consumer Electronics	www.ti.com/consumer-apps
	DLP® Products	www.dlp.com	Energy and Lighting	www.ti.com/energy
	DSP	dsp.ti.com	Industrial	www.ti.com/industrial
	Clocks and Timers	www.ti.com/clocks	Medical	www.ti.com/medical
	Interface	interface.ti.com	Security	www.ti.com/security
	Logic	logic.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
	Power Mgmt	power.ti.com	Transportation and Automotive	www.ti.com/automotive
	Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
	RFID	www.ti-rfid.com		
	OMAP Mobile Processors	www.ti.com/omap		
	Wireless Connectivity	www.ti.com/wirelessconnectivity		
		u Hama Dawa	a O a Al a a m	

**TI E2E Community Home Page** 

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2011, Texas Instruments Incorporated