Filename: BOM-Altera_Cyclone_V_SoC_RevB.xls

Variant: None

Generated: 7/3/2014 1:30:50 PM

Altera Cyclone V SoC

Designator	Description	Manufacturer	PartNumber	Quantity
C1	CAP, CERM, 0.1uF, 25V, +/-10%, X5R, 0603	MuRata	GRM188R61E104KA01D	1
C1, C3,	CAP, TA, 68uF, 16V, +/-20%, 0.05 ohm, SMD	Panasonic	16TQC68MYF	8
C16, C18,				
C30, C32,				
C44, C46				
C2, C4,	CAP, CERM, 47uF, 16V, +/-20%, X5R, 1210	MuRata	GRM32ER61C476ME15L	8
C17, C19,				
C31, C33,				
C45, C47				
C5, C11,	CAP, TA, 220uF, 6.3V, +/-20%, 0.009 ohm, SMD	Kemet	T520D227M006ATE009	8
C20, C25,				
C34, C39,				
C48, C53				
C6, C7, C8,	CAP, CERM, 47uF, 6.3V, +/-20%, X5R, 1210	MuRata	GRM32ER60J476ME20L	32
C9, C12,				
C13, C14,				
C15, C21,				
C22, C23,				
C24, C26,				
C27, C28,				
C29, C35,				
C36, C37,				
C38, C40,				
C41, C42,				
C43, C49,				
C50, C51,				
C52, C54,				
C55, C56,				
C57				
C58, C59,	CAP, CERM, 0.01uF, 50V, +/-5%, X7R, 0603	Kemet	C0603C103J5RACTU	7
C60, C64,				
C65, C66,				
C67				
C61, C62,	CAP, CERM, 0.1uF, 50V, +/-10%, X7R, 0603	MuRata	GCM188R71H104KA57B	3
C72				
	CAP, CERM, 100pF, 50V, +/-5%, C0G/NP0, 0603	AVX	06035A101JAT2A	1
C68, C70,	CAP, CERM, 10uF, 6.3V, +/-20%, X5R, 0603	Kemet	C0603C106M9PACTU	6
C71, C74,				
C75, C76				
C69	CAP, CERM, 1000pF, 100V, +/-5%, X7R, 0603	AVX	06031C102JAT2A	1
C73	CAP, CERM, 10pF, 50V, +/-5%, C0G/NP0, 0603	AVX	06035A100JAT2A	1
C77, C85	CAP, CERM, 47uF, 10V, +/-20%, X5R, 0805	MuRata	GRM21BR61A476ME15	2
C78, C79,	CAP, CERM, 10uF, 10V, +/-10%, X5R, 0805	MuRata	GRM21BR61A106KE19L	12
C80, C81,				
C82, C83,				
C86, C87,				
C88, C89,				
C90, C91				
	CAP, CERM, 1uF, 50V, +/-10%, X7R, 0805	MuRata	GRM21BR71H105KA12L	2
C203	CAP, CERM, 100pF, 100V, +/-5%, C0G/NP0, 0603	MuRata	GRM1885C2A101JA01D	1
D2	Diode, Zener, 5.1V, 300mW, SOD-523	Diodes Inc.	BZT52C5V1T-7	1

Designator	Description	Manufacturer	PartNumber	Quantity
	Diode, Schottky, 30V, 0.2A, SOT-23	Diodes Inc.	BAT54-7-F	9
D5, D6, D7,				
D8, D9, D10				
				
	TERMINAL BLOCK 5.08MM VERT 2POS, TH	On-Shore Technology	ED120/2DS	12
J4, J5, J6,				
J7, J8, J9,				
J10, J11, J12				
	DES 100k ohm 59/ 0.1M/ 0602	Vichay Dala	CDCW0602100KINEA	2
	RES, 100k ohm, 5%, 0.1W, 0603 RES, 49.9 ohm, 1%, 0.1W, 0603	Vishay-Dale Vishay-Dale	CRCW0603100KJNEA CRCW060349R9FKEA	3 8
R10, R2, R9,	RES, 49.9 01111, 1%, 0.100, 0003	VISHAy-Dale	CRCW000349R9FREA	0
R16, R13,				
R22				
R3, R12,	RES, 453 ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603453RFKEA	4
R17, R24	TCES, 400 OHIII, 170, 0.177, 0000	Violity Baic	ONOVOCCO-CON NEX	
	RES, 1.74k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW06031K74FKEA	2
	RES, 158k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603158KFKEA	2
	RES, 261k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603261KFKEA	2
	RES, 1.62k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW06031K62FKEA	2
R13, R25	RES, 324k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603324KFKEA	2
R14, R26	RES, 165k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603165KFKEA	2
R27, R28,	RES, 1.0k ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW06031K00JNEA	8
R29, R30,				
R33, R34,				
R35, R36				
	RES, 10k ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW060310K0JNEA	2
	RES, 10.0k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW060310K0FKEA	2
R39	RES, 100k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603100KFKEA	1
R40	RES, 10 ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW060310R0JNEA	1
R128	RES, 68.1k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW060368K1FKEA	1
R130	RES, 12.1k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW060312K1FKEA	1
TP1, TP3,	Test Point, Multipurpose, Orange, TH	Keystone	5013	8
TP5, TP7, TP9, TP11,				
TP13, TP15				
TP2, TP4,	Test Point, Multipurpose, Red, TH	Keystone	5010	8
TP6, TP8,	Test Folint, Multipurpose, Rea, 111	Reyslone	3010	0
TP10,				
TP12,				
TP14, TP16				
U1	Power Sequencer, 6-pin SOT-23	National Semiconductor	LM3880MF-1AA	1
	6A SIMPLE SWITCHER Power Module with 2.95V-	Texas Instruments	LMZ31506RUQ	4
U7	14.5V Input and Current Sharing in QFN Package,	, , , , , , , , , , , , , , , , , , , ,		
	RUQ0047A			
U2, U4, U6,	3A SIMPLE SWITCHER Power Module with 4.5V-14.5V	Texas Instruments	LMZ31503RUQ	4
Ú8 .	Input in QFN Package, RUQ0047A			1
U9	IC, Single Schmitt-Trigger Inverter	TI	SN74LVC1G14DCK	1
U10, U11	36-V, 1-A, 4.17-μVRMS, RF LDO Voltage Regulator,	Texas Instruments	TPS7A4700RGW	2
	RGW0020A			
U12	IC, Sink/Source DDR Termination Regulator	TI	TPS51200DRC	1

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.