

# Universal and Fast Charging – a Future Trend for Battery-powered Applications




Upal Patel

Today's "always-on" consumer wants to charge their portable electronics wherever they are. For example, it's common to see travelers charging their cellphones, laptops and headphones while waiting to board a flight or hop on a train. But when there are different charging methods for each device, these consumers must carry different adapters, and it can become quite a hassle to remember each adapter for each device (see [Figure 1](#)). For engineers to help minimize this hassle, their battery charging system designs must support charging from various input sources.


## Why consider USB Type-C PD charging?

Designing a single-chip charger integrated circuit (IC) to charge multiple battery-powered devices with different configurations and different input-voltage ranges can be a complicated process, since classic adapters are not compatible with all battery-powered devices and traditional USB adapters are limited to 5-15 W, limiting the portable battery-powered devices they will support.

USB Type-C™ Power Delivery (USB PD) offers a useful alternative for fast and efficient charging of a wide range of applications, as illustrated in [Figure 2](#). The output voltage range of USB PD is adjustable for different battery-powered devices with different battery configurations to utilize 5 W to 100 W (20 V / 5 A) power spectrum of USB PD.

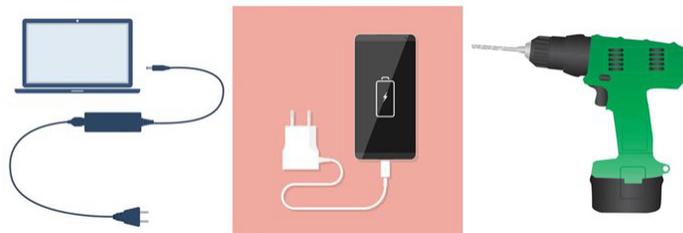

**Figure 1. Charging with different input sources and adapters**

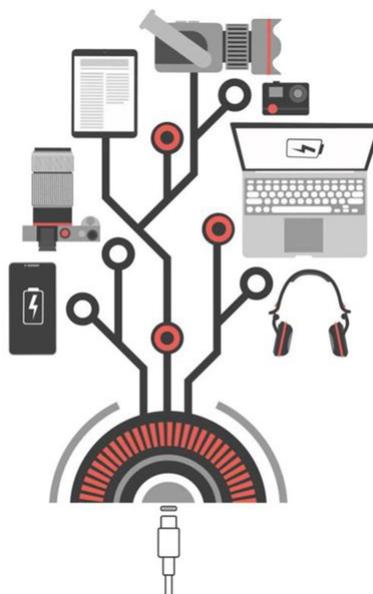

**Figure 2. Universal and fast charging enabled by USB PD**

Expanding on the above example of a traveler charging one or more devices, the best-case situation given their potentially limited access to a power supply is that their devices will quickly charge to full battery capacity, and that the battery will last for an extended period of time once charged. Even if they only have a quick 15-minute layover to recharge a device, that should be enough to extend battery operation for hours.

Thus, to meet consumer expectations, design engineers are looking for solutions that can:

- Simplify their designs while enabling universal charging – the ability to charge multiple battery-powered devices with different configurations (1 cell in series [s] to 4s) and different input voltages.
- Extend battery run times and use the maximum battery capacity to enable the best consumer experience.
- Charge efficiently while reducing thermal dissipation to minimize power loss within the charger IC.
- Protect the input adapter, battery and system from a cascade failure.

TI's new family of integrated buck-boost battery-charger ICs, including the BQ25790 and BQ25792, leverage USB PD input for improved flexibility in charging 1S – 4S batteries across an input-voltage range of 3.6 V to 24 V. With integrated components, these buck-boost chargers give you the freedom to choose whether a single-charger IC is a better design choice for compact, size-constrained battery-powered devices like cell phones, laptops, Bluetooth headsets or medical equipment vs. designing with multiple power stages that need either boosting up or bucking down to keep the application within a safe operating voltage range.

The BQ25790 and BQ25792 leverage an ultra-low power consumption charger IC to extend the battery's run time during operation and to conserve as much battery power as possible when the application is not in use. In addition to ultra-low power consumption, the chargers come with a top-off timer that enables extra charging on top of a normal charge cycle, ensuring that the battery can charge to its maximum capacity (see [Table 1](#)).

**Table 1. Included programmable features on the BQ25790 and BQ25792**

Parameter	Programmability	Resolution	Default
Charge voltage	3 V-18.8 V	10 mV	4.2 V (1 cell in series [s]), 8.4 V (2s), 12.6 V (3s), 16.8 V (4s)
Charge current	50 mA-5 A	10 mA	2 A (1s), 2 A (2s), 1 A (3s), 1 A (4s)
On-the-go (OTG) voltage	2.8 V-22 V	10 mV	5 V
OTG current	120 mA-3.32 A	40 mA	3 A
Pre-charge current	40 mA-2 A	40 mA	120 mA
Termination current	40 mA-1 A	40 mA	200 mA
Top-off timer	Disabled, 15 minutes, 30 minutes, 45 minutes		

For power designs that require a long run time, short and efficient charging, and a compact design, USB PD charging offers flexibility to charge a wide range of applications while keeping bill of materials low and shrinking total solution size. To learn more about designing with power density and low quiescent current in mind, check out the additional resources below.

**Additional resources**

- Read the technical article, [Small chargers pack a powerful punch: combining buck-boost and USB Type C™ power delivery for maximum power delivery.](#)
- Read the technical article, [Transform the way you charge your devices with USB Type-C and PD.](#)
- Watch the video, [What could you achieve with universal and fast charging?](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated