

Russell Crane

In my [last post](#), I discussed the future of factory automation and how IO-Link is an enabling interface for Industry 4.0. You can use the IO-Link bidirectional, manufacturer-independent communication protocol to develop highly efficient and scalable “smart factories.”

TI's TIOL111 IO-Link transceiver and TIOS101 digital output switch will enable the next generation of sensors and actuators in factories, while providing features that further optimize product offerings and simplify bill of materials.

You can take advantage of the pin compatibility between the TIOL111 and TIOS101 devices to develop a complete portfolio of both IO-Link and standard input/output (SIO) enabled sensors without using two separate printed circuit boards (PCBs) for each offering. Each device supports the interfaces intended while also supporting a high level of integrated protection, including:

- 16kV International Electrotechnical Commission (IEC) 61000-4-2 electrostatic discharge (ESD).
- 4kV IEC 61000-4-4 electrical fast transient (EFT) Criterion A.
- 1.2kV/500Ω IEC 61000-4-5 (surge).
- ±65V transient tolerance.
- Reverse polarity up to ±55V.
- Overcurrent/overvoltage/overtemperature.

This level of protection can simplify designs by eliminating or greatly reducing the size of external transient voltage suppression (TVS) diode components that originally provided protection, thus reducing the overall bill of materials and associated costs when compared to previous-generation or competitive solutions.

The physical size of sensors continues to shrink. The smallest of these sensors is likely the cylindrical sensor, as shown in [Figure 1](#).

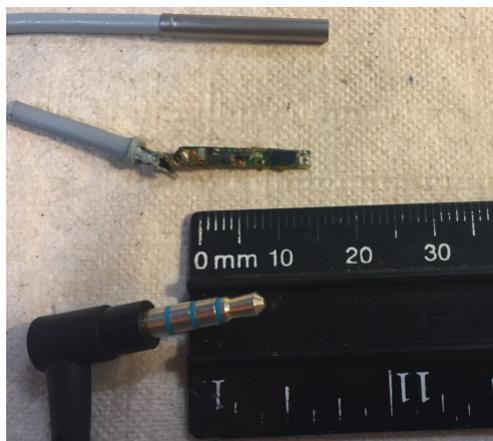


Figure 1. IO-Link Cylindrical Sensor

The sensor at the top of [Figure 1](#) is the finished product with a cylindrical enclosure. The middle wire is the sensor's internal printed circuit board (PCB). This PCB measures 17.5mm by 2.5mm. In order to fit in these small form factors, an equally small device is required to implement either IO-Link or SIO output. Knowing these system requirements drove a new package development for TIOL111 and TIOS101 solutions. The DMW package is one of the smallest, thermally enhanced IO-Link packages available today. Measuring 3.0mm by 2.5mm, the DMW package also supports a thermal pad for heat conduction and a flow-through pinout. The

flow-through pinout (Figure 2) further aides in PCB layout and device placement by supporting the logic interface to the microcontroller on one X-axis and the 24V IO-Link interface on the other.

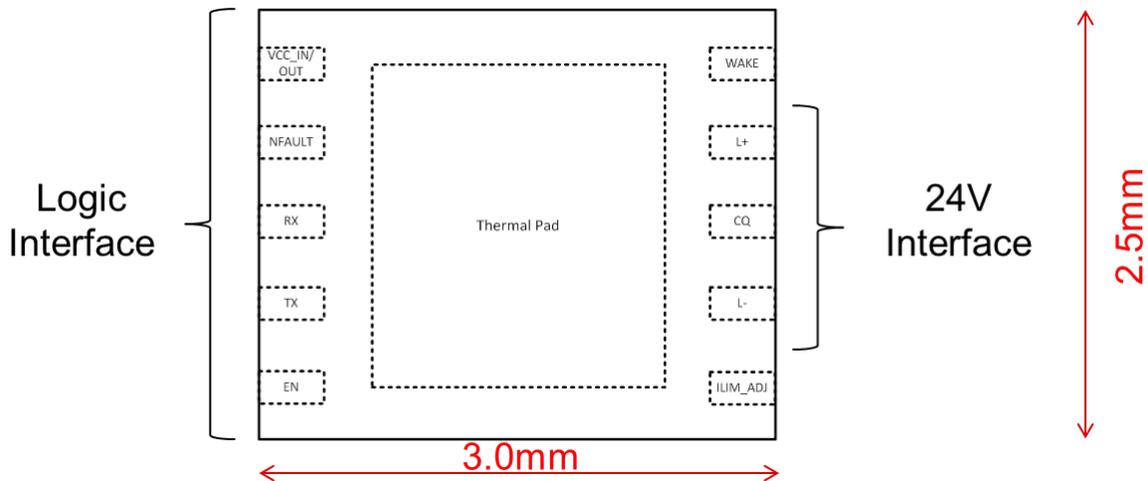


Figure 2. TIOL111/TIOS101 flow-through package

The TIOL111 and TIOS101 have a low residual voltage of just 1.75V – the size of sensors that use IO-Link and SIO are rugged, sealed and often very small. This small, enclosed form factor introduces numerous design challenges, with thermal performance one of the most challenging. By supporting an ultra-low residual voltage of 1.75V at 250mA, the TIOL111 and TIOS101 provide a superior base for power dissipation and related system thermal management.

Table 1. Power Dissipation = Residual Voltage × 10

	Driver current output	Residual voltage
High Side	100mA	1.1V
	200mA	1.5V
	250mA	1.75V
Low Side	100mA	1.1V
	200mA	1.5V
	250mA	1.75V

Configurable current limit is an additional protection feature that can protect the sensor and possibly prevent the network from shutting down. Through a 0-100kΩ resistor, the TIOL111 and TIOS101 can support a 50-350mA current limit. This limiter can notify the programmable logic controller (PLC) of an overcurrent condition and shut down the device's output, with periodic monitoring of the overcurrent condition.

The configurable current-limit resistor is placed on the ILIM_ADJ pin (see Figure 3).

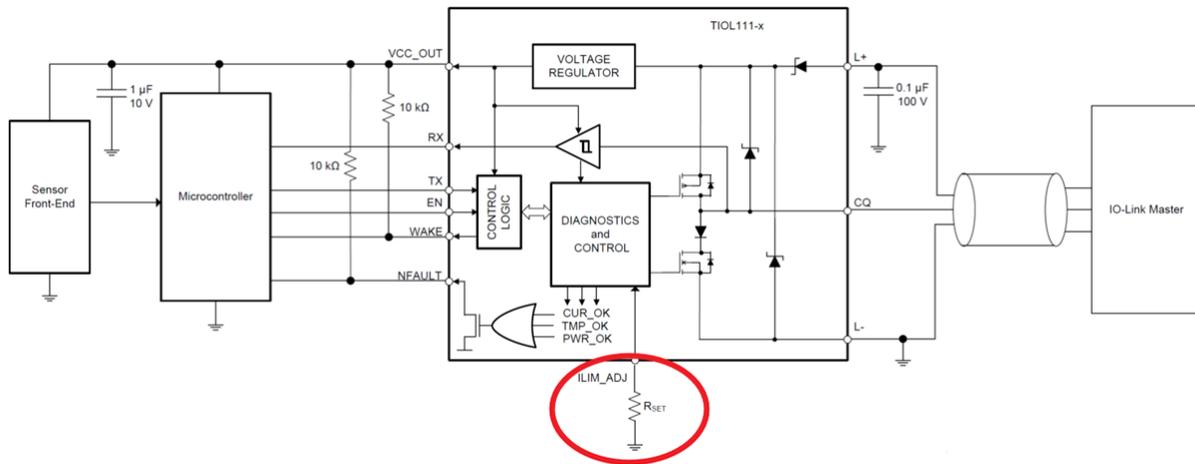


Figure 3. TIOL111 application schematic

As [Figure 4](#) indicates, using a 0Ω resistor on the ILIM_ADJ pin will default to the maximum current limit of 350mA (see [Figure 4](#))

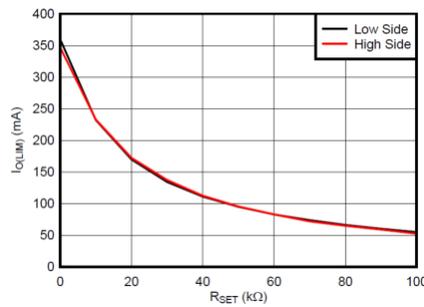


Figure 4. Current limit vs. R_{SET}

These and other features and benefits of the TIOL111 and TIOS101 can enable the smallest sensor form factors, while providing the flexibility to support multiple platforms and current configuration requirements.

Additional Resources

- Learn more about TI's line of [IO-Link and digital output switches](#).
- Evaluate your device today with the [TIOL1115](#) and [TIOS1015](#) evaluation modules.
- Download the [Smart Solenoid Driver with Predictive Maintenance Reference Design](#) featuring the TIOL111.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated