

Bill of Materials

TI DESIGNS TIDA-00368 Reference Design for Interfacing current output Hall sensors and CTs with Differential ADC/MCU

		output nam sensors and CTS with Differential AD				
Qty	Reference	Part Description	Manufacturer	Manufacturer Part Number	PCB Footprint	Note
1	!PCB1	Printed Circuit Board	Any	TIDA-00368		Fitted
1	C1	CAP, CERM, 10 μF, 35 V, +/- 20%, X7R, 1206_190	TDK	C3216X7R1V106M160AC	1206_190	Fitted
1	C2	CAP, CERM, 3300 pF, 50 V, +/- 10%, X7R, 0805	Kemet	C0805C332K5RACTU	0805	Fitted
2	C4, C11	CAP, CERM, 100 pF, 100 V, +/- 5%, COG/NPO, 0603	TDK	C1608C0G2A101J	0603	Fitted
9	C6, C8, C20, C21, C29, C36, C38, C54, C56	CAP, CERM, 10 μF, 25 V, +/- 10%, X5R, 0805_140	MuRata	GRM21BR61E106KA73L	0805_140	Fitted
8	C13, C30, C31, C33, C34, C35, C53, C55	CAP, CERM, 0.1 μF, 50 V, +/- 10%, X7R, 0603	MuRata	GRM188R71H104KA93D	0603	Fitted
2	C9, C12	CAP, CERM, 22 μF, 16 V, +/- 10%, X5R, 0805	TDK	C2012X5R1C226K125AC	0805	Fitted
4	C15, C16, C58, C59	CAP, CERM, 0.01 μF, 25 V, +/- 5%, COG/NP0, 0603	TDK	C1608C0G1E103J	0603	Fitted
8	C17, C24, C47, C48, C49, C50, C51, C52	CAP, CERM, 1uF, 10V, +/-10%, X7R, 0805	Kemet	C0805C105K8RACTU	0805	Fitted
1	C26	CAP, CERM, 200 pF, 100 V, +/- 5%, C0G/NP0, 0603	MuRata	GRM1885C2A201JA01D	0603	Fitted
2	C27, C28	CAP, CERM, 9100 pF, 50 V, +/- 5%, COG, 0603	MuRata	GRM2195C1H912JA01D	0603	Fitted
2	C42, C43	CAP, CERM, 4.7 μF, 10 V, +/- 10%, X5R, 0603	AVX	0603ZD475KAT2A	0603	Fitted
2	C46, C61	CAP, CERM, 330 pF, 50 V, +/- 1%, COG/NPO, 0603	TDK	C1608C0G1H331F080AA	0603	Fitted
1	C60	CAP, CERM, 0.01 μF, 50 V, +/- 5%, X7R, 0402	Kemet	C0402C103J5RACTU	0402	Fitted
3	D5, D6, D9	Diode, Schottky, 40 V, 0.015 A, SOD-123	Diodes Inc.	SD101CW-7-F	SOD-123	Fitted
2	D3, D4	Diode, Schottky, 60V, 1A, SMA	ON Semiconductor	MBRA160T3G	SMA	Fitted
2	D11, D12				SOD-123	
	011, 012	Diode, Zener, 3.6V, 500mW, SOD-123	Diodes Inc.	MMSZ5227B-7-F	SUD-123	Fitted
4	H1, H2, H3, H4	Machine Screw, Round, #4-40 x 1/4, Nylon, Philips panhead	B&F Fastener Supply	NY PMS 440 0025 PH	Screw	Fitted
4	H9, H10, H11, H12	Standoff, Hex, 0.5"L #4-40 Nylon	Keystone	1902C	Standoff	Fitted
1	J1	Conn Term Block, 2POS, 5.08mm, TH	Phoenix Contact	1715721	2POS Terminal Block	Fitted
1	J2	Terminal Block, 3.5 mm, 2x1, Tin, TH	Molex	39357-0002	Terminal Block, 3.5 mm, 2x1, TH	Fitted
1	13	Terminal Block, 3.5 mm, 3x1, Tin, TH	Molex	39357-0003	Terminal Block, 3.5 mm, 3x1, TH	Fitted
2	J4, J12	Header, 2.54 mm, 6x1, Gold, TH	Wurth Elektronik	61300611121	Header, 2.54mm, 6x1, TH	Fitted
2	J6, J7	Connector, TH, SMA	Emerson Network Power	142-0701-201	SMA	Fitted
1	J9	Header, 100mil, 2x1, Tin, TH	Molex	90120-0122	Header 2x1	Fitted
1	J10	CONN HIGH SPD CARD EDGE 60 POS	3M	SPD08-060-RB-TR	28.6x7mm	Fitted
1	J11	CONN HIGH SPD CARD EDGE 120 POS	3M	SPD08-120-L-RB	7x56mm	Fitted
1	L1	Inductor, Shielded, Composite, 2.2 µH, 3.7 A, 0.02 ohm, SMD	Coilcraft	XFL4020-222MEB	4x2x4mm	Fitted
2	LD1, LD2	LED SmartLED Green 570NM	OSRAM	LG L29K-G2J1-24-Z	0603	Fitted
32	R1, R2, R9, R25, R47, R50, R62, R63, R65, R66, R67, R68, R69, R70, R71, R72, R73, R74, R75, R76, R77, R78, R79, R80, R81, R82, R83, R84, R95, R96, R97,	RES, 0, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06030000Z0EA	0603	Fitted
		DEC 4541 40/ 0.4 W 0000	V6.1	CDC14/0502454V5V54	0000	en l
1	R5	RES, 154 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603154KFKEA	0603	Fitted
1	R6	RES, 42.2, 1%, 0.125 W, 0805	Vishay-Dale	CRCW080542R2FKEA	0805	Fitted
1	R8	RES, 1.00 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06031K00FKEA	0603	Fitted
5	R15, R19, R20, R21, R23	RES, 2.00 k, 1%, 0.1 W, 0603	Yageo America	RC0603FR-072KL	0603	Fitted
1	R13	RES, 1.0 M, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06031M00JNEA	0603	Fitted
2	R28, R29	RES, 2.00 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06032K00FKEA	0603	Fitted
2	R30, R32	RES, 18.2 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060318K2FKEA	0603	Fitted
4	R31, R33, R37, R40	RES, 2.00 k, 0.1%, 0.1 W, 0603	Susumu Co Ltd	RG1608P-202-B-T5	0603	Fitted
2	R38, R39	RES, 255, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603255RFKEA	0603	Fitted
2	R43, R45	RES, 43.2 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060343K2FKEA	0603	Fitted
1	R44	RES, 20.0 k, 1%, 0.1 W, 0603	Yageo America	RC0603FR-0720KL	0603	Fitted
2	R48, R49	RES, 24.9, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060324R9FKEA	0603	Fitted
1	R52	RES, 10.0 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060310K0FKEA	0603	Fitted
2	R55, R93	RES, 511, 0.5%, 0.1 W, 0603	Yageo America	RT0603DRE07511RL	0603	Fitted
1	R56	RES, 2.49 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06032K49FKEA	0603	Fitted
2	R58, R59	RES, 22, 5%, 0.1 W, 0603	Vishay-Dale Vishay-Dale	CRCW06032R49FREA CRCW060322R0JNEA	0603	Fitted
	,		•			
6	R85, R86, R87, R88, R89, R90	RES, 0, 5%, 0.25 W, 1206	Yageo America	RC1206JR-070RL	1206	Fitted
1	U1	Buck Step Down Regulator with 3 to 17 V Input and 0.9 to 6 V Output, -40 to 85 degC, 16-Pin QFN (RGT), Green	Texas Instruments	TPS62150RGTT	RGT0016C	Fitted
	113	(RoHS & no Sb/Br)	1584	LAH 25 ND	14.03,23.3	F:++ ¹
1	U2 U3	Current Transducer, 25A, TH 20 MHz, Low Noise, RRIO, CMOS Operational Amplifier with Shutdown, 1.8 to 5.5 V, -40 to 125 degC, 5-pin SOT23 (DBV0005A), Green (RoHS & no Sb/Br)	LEM Texas Instruments	LAH 25-NP OPA322AIDBVR	14.93x33.3mm DBV0005A	Fitted Fitted
1	U4	Single Output High PSRR LDO, 200 mA, Adjustable -1.18 to -33 V Output, -3 to -36 V Input, with Ultra-Low Noise, 8-pin MSOP (DGN), -40 to 125 degC, Green (RoHS & no Sb/Br)	Texas Instruments	TPS7A3001DGNR	DGN0008D	Fitted

Qty	Reference	Part Description	Manufacturer	Manufacturer Part Number	PCB Footprint	Note
1	U5	Single Output High PSRR LDO, 150 mA, Adjustable 1.2 to 33 V Output, 3 to 36 V Input, with Ultra-Low Noise, 8- pin MSOP (DGN), -40 to 125 degC, Green (RoHS & no Sb/Br)	Texas Instruments	TPS7A4901DGNR	DGN0008D	Fitted
1	U8	Ultra Low Power, Rail-to-Rail Output, Fully-Differential Amplifier, DGK0008A	Texas Instruments	THS4531AIDGK	DGK0008A	Fitted
1	U9	2.2-V to 36-V, microPower Comparator, DGK0008A	Texas Instruments	TLV1702AIDGK	DGK0008A	Fitted
1	U10	Micropower 250 mA Low-Noise Ultra Low-Dropout Regulator, 6-pin LLP, Pb-Free	Texas Instruments	LP2992AILD-5.0/NOPB	LDE06A	Fitted
1	U12	DUAL OUTPUT VOLTAGE REFERENCE 2.5V, DBV0005A	Texas Instruments	REF2025DBV	DBV0005A	Fitted
0	C40	CAP, CERM, 330 pF, 50 V, +/- 1%, COG/NPO, 0603	TDK	C1608C0G1H331F080AA	0603	Not Fitted
0	FID1, FID2, FID3, FID4, FID5, FID6	Fiducial mark. There is nothing to buy or mount.	N/A	N/A	Fiducial	Not Fitted
0	R24, R54	RES, 0 ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW06030000Z0EA	0603	Not Fitted

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.