

Engineering Bill of Materials



Project Name:	PMP10725
Project File:	PMP10725_LM3481 Rev_B.PrjPcb
Base ID:	PMP10725_LM3481
PCB Rev:	X1
Schematic Rev:	X1
Assembly Variant:	Secondary Control
Generated:	3/18/2016 10:19:43 AM

Date opened: 4/13/2016
Time opened: 3:10:35 PM

Item	Designator	Description	Manufacturer	PartNumber	Quantity
					50
1	C1	CAP, CERM, 10 uF, 25 V, +/- 10%, X7R, 1206	MuRata	GRM31CR71E106KA12L	1
2	C2, C11	CAP, AL, 47 uF, 50 V, +/- 20%, 0.68 ohm, SMD	Panasonic	EEE-FK1H470XP	2
3	C3	CAP, CERM, 0.1 uF, 100 V, +/- 10%, X7R, 0603	MuRata	GRM188R72A104KA35D	1
4	C4	CAP, CERM, 1 uF, 50 V, +/- 10%, X5R, 0603	MuRata	GRM188R61H105KAALD	1
5	C5	CAP, CERM, 4.7 uF, 25 V, +/- 10%, X5R, 0603	MuRata	GRM188R61E105KA12D	1
6	C6	CAP, CERM, 1 uF, 25 V, +/- 10%, X7R, 0603	MuRata	GRM188R71E105KA12D	1
7	C7	CAP, CERM, 1000 pF, 50 V, +/- 10%, X5R, 0603	MuRata	GRM188R61H102KA01D	1
8	C8	CAP, CERM, 100 pF, 25 V, +/- 5%, C0G/NP0, 0201	MuRata	GRM033R71E101JA01D	1
9	C10	CAP, CERM, 150 pF, 50 V, +/- 5%, C0G/NP0, 0603	MuRata	GRM1885C1H151JA01D	1
10	C12	CAP, CERM, 10 uF, 35 V, +/- 10%, X7R, 1206	Taiyo Yuden	GMK316AB7106KL	1
11	C13	CAP, CERM, 0.1 uF, 50 V, +/- 10%, X7R, 0603	MuRata	GCM188R71H104KA57D	1
12	C14, C15, C21, C22	CAP, CERM, 10 uF, 16 V, +/- 10%, X5R, 1206	MuRata	GRM319R61C106KE15D	4
13	C16	CAP, CERM, 0.47uF, 10V, +/-10%, X5R, 0603	MuRata	GRM188R61A474KA61D	1
14	C17	CAP, CERM, 1000 pF, 500 V, +/- 10%, X7R, 1210	Vishay-Vitramon	VJ1210Y102KXEAT5Z	1
15	C20	CAP, CERM, 0.1 uF, 6.3 V, +/- 10%, X7R, 0603	MuRata	GRM188R70J104KA01D	1
16	D1	Diode, Schottky, 100 V, 1 A, PowerDI123	Diodes Inc.	DFLS1100-7	1
17	D3	Diode, Schottky, 60 V, 2 A, SMB	Vishay-Semiconductor	SS26-E3/52T	1
18	D4, D5	Diode, Schottky, 20 V, 1 A, SMA	Diodes Inc.	B120-13-F	2
19	Q1	MOSFET, N-CH, 100 V, 17 A, SON 5x6mm	Texas Instruments	CSD19532Q5B	1
20	R1	RES, 69.8 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060369K8FKEA	1

21	R2	RES, 14.3 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060314K3FKEA	1
22	R3	RES, 100 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603100KFKEA	1
23	R4	RES, 100, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603100RFKEA	1
24	R5	RES, 332, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603332RFKEA	1
25	R6	RES, 5.11 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06035K11FKEA	1
26	R7, R22	RES, 0.01, 1%, 0.5 W, 1206	Stackpole Electronics Inc	CSR1206FK10L0	2
27	R10	RES, 200, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603200RFKEA	1
28	R12	RES, 8.06 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06038K06FKEA	1
29	R13, R16	RES, 1.00k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW06031K00FKEA	2
30	R14	RES, 21.5 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060321K5FKEA	1
31	R15	RES, 2.49 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06032K49FKEA	1
32	R18	RES, 5.11 k, 1%, 0.125 W, 0805	Vishay-Dale	CRCW08055K11FKEA	1
33	R19	RES, 511, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603511RFKEA	1
34	R20	RES, 0, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06030000Z0EA	1
35	T1	Transformer, 30 uH, Isat 2.6A, EP13, 16Pin, 0.54:0.54:0.135:1:0.135, SMT	Würth Elektronik	750342985	1
36	TP1	Terminal, Turret, TH, Double	Keystone	1503-2	1
37	TP2	Terminal, Turret, TH, Double	Keystone	1503-2	1
38	TP3	Terminal, Turret, TH, Double	Keystone	1503-2	1
39	TP4	Terminal, Turret, TH, Double	Keystone	1503-2	1
40	U1	High Efficiency Low-Side N-Channel Controller for Switching Regulators	Texas Instruments	LM3481MM/NOPB	1
41	U2	Optocoupler, 2.5 kV, 100-200% CTR, SMD-4	California Eastern Laboratories	PS2811-1-M-A	1
42	U3	Adjustable Precision Zener Shunt Regulator, 3-pin SOT-23	Texas Instruments	LM431ACM3	1
43	Z1	Diode, Zenor, 40V, 1A, SOD-123	Diodes Inc.	1N5819HW-7-F	1

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

TI's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equipment includes, without limitation, all medical devices identified by the U.S. Food and Drug Administration as Class III devices and equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

TI's standard terms of sale for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's non-compliance with the terms and provisions of this Notice.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2016, Texas Instruments Incorporated