

PMP20021 REV A Bill of Materials

Designator	Quantity	Value	PartNumber	Manufacturer	Description	PackageReference
C1, C2, C3, C4	4	10uF	C3225X5R1H106M250AB	TDK	CAP, CERM, 10uF, 50V, +/-20%, X5R, 1210	1210
C5, C24, C25,	8	10uF		TDK	CAP, CERM, open, 1210	1210
C28, C29, C32,						
C35, C36						
C6, C7, C18, C19	4	1uF	C1608X7R1E105K080AB	TDK	CAP, CERM, 1uF, 25V, +/-10%, X7R, 0603	0603
C8, C20, C21,	5	1000pF	C1608C0G1H102J	TDK	CAP, CERM, 1000pF, 50V, +/-5%, C0G/NP0, 0603	0603
C30, C31					, , , , , , , , , , , , , , , , , , , ,	
C9	1	0.1uF	06035C104KAT2A	AVX	CAP, CERM, 0.1uF, 50V, +/-10%, X7R, 0603	0603
C10	1	100pF	C1608C0G1H101J	TDK	CAP, CERM, 100pF, 50V, +/-5%, C0G/NP0, 0603	0603
C11	1	0.47uF	C0603C474K4RACTU	Kemet	CAP, CERM, 0.47uF, 16V, +/-10%, X7R, 0603	0603
C12, C13	2	0.1uF	C1608X7R1H104K	TDK	CAP, CERM, 0.1uF, 50V, +/-10%, X7R, 0603	0603
C16	1	220pF	C1608C0G1H221J	TDK	CAP, CERM, 220pF, 50V, +/-5%, C0G/NP0, 0603	0603
C17	1	0.033uF	GRM188R71H333KA61D	MuRata	CAP, CERM, 0.033uF, 50V, +/-10%, X7R, 0603	0603
C22, C26	2	390uF	20SVPF390M	Sanvo	CAP, OS-CON, 390uF, 20V, +/-20%, 0.014 ohm, 8x10 SMD	8x10
C23, C27	2	10uF	GMK325AB7106MM-T	Taiyo Yuden	CAP, CERM, 10uF, 35V, +/-20%, X7R, 1206	1206
C33, C34	2	2200pF	C0603C222K5RAC	Kemet	CAP, CERM, 2200pF, 50V, +/-10%, X7R, 0603	0603
C100		82uF	COCCOCCECTION	Sanyo	CAP, OS-CON, open	8x10
D1, D2		60V	PMEG6010CEH	NXP Semiconductor	Diode, Schottky, 60V, 1A, SOD-123F	SOD-123F
J1, J2	2	00 V	ED120/2DS	On Shore Technology	TERMINAL BLOCK 5.08MM VERT 2POS	TERM_BLK, 2pos,
			LD120/2D3	On Shore reclinology	TERMINAL BEOOK 5.00MW VERT 21 00	5.08mm
L1, L2	2	5.6uH	XAL1010-562MEB	Coilcraft	Inductor, Shielded, Composite, 5.6uH, 21.2A, 0.01 ohm, SMD	Inductor,
L1, LZ		3.0ui i	XALIO10-30ZWLD	Colician	inductor, officiaed, composite, 5.0dr i, 21.2A, 6.01 offin, one	11.3x10x10mm
Q1, Q2, Q3, Q4	4	40V	CSD18503Q5A	Texas Instruments	MOSFET, N-CH, 40V, 3.4 milliohm, SON 5x6mm	SON 5x6mm
R1	1	1.00	CRCW08051R00FKEA	Vishay-Dale	RES, 1.00 ohm, 1%, 0.125W, 0805	0805
R2	1	1.00 100k	CRCW06031R00FREA	Vishay-Dale Vishay-Dale	RES, 100k ohm, 1%, 0.1W, 0603	0603L
R3	•	6.65k	CRCW0603160KI KEA	Vishay-Dale Vishay-Dale	RES, 6.65k ohm, 1%, 0.1W, 0603	0603L
R4	1	16.2k	CRCW060316K2FKEA	Vishay-Dale Vishay-Dale	RES, 16.2k ohm, 1%, 0.1W, 0603	0603
R7	1	20.0k	CRCW060310K2FKEA	Vishay-Dale Vishay-Dale	RES, 20.0k ohm, 1%, 0.1W, 0603	0603
R8	1	100	CRCW060320R0FREA	Vishay-Dale Vishay-Dale	RES, 100 ohm, 1%, 0.1W, 0603	0603
R10	1	20.0k	CRCW0603100KFKEA	Vishay-Dale Vishay-Dale	RES, 20.0k ohm, 1%, 0.1W, 0603	0603L
R11	1	1.43k	CRCW060320K0FKEA	Vishay-Dale Vishay-Dale	RES, 1.43 k, 1%, 0.1 W, 0603	0603
R14, R15						
		66.5k 0	CRCW060366K5FKEA	Vishay-Dale	RES, 66.5k ohm, 1%, 0.1W, 0603	0603 0603L
R16, R21, R22	3	_	CRCW06030000Z0EA	Vishay-Dale	RES, 0 ohm, 5%, 0.1W, 0603	
R17		0	CRCW06030000Z0EA	Vishay-Dale	RES, 0 ohm, 5%, 0.1W, 0603	0603
R18, R20	2	0.003	WSL20103L000FEA	Vishay-Dale	RES, 0.003 ohm, 1%, 0.5W, 2010	2010
R23, R24, R31,	4	100	RC0603FR-07100RL	Yageo America	RES, 100 ohm, 1%, 0.1W, 0603	0603L
R32				Ne i Si	DEC 10 1 50/ 11/ 0010	2010
R25, R26	2	10	CRCW201010R0JNEFHP	Vishay-Dale	RES, 10 ohm, 5%, 1W, 2010	2010
R27, R28, R29,	4	2.2	CRCW06032R20JNEA	Vishay-Dale	RES, 2.2 ohm, 5%, 0.1W, 0603	0603
R30	_					
TP1, TP2, TP5,	7	Red	5010	Keystone	Test Point, Multipurpose, Red, TH	Keystone5010
TP6, TP100,						
TP102, TP103						
TP101		Black	5011	Keystone	Test Point, Multipurpose, Black, TH	Keystone5011
U1	1		LM25119PSQ/NOPB	Texas Instruments	LM25119/LM25119Q Wide Input Range Dual Synchronous Buck	RTV0032A
					Controller, RTV0032A	

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ('TI") reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

Tl's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter Tl's applicable published warranties or warranty disclaimers for Tl products, and no additional obligations or liabilities arise from Tl providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equipment includes, without limitation, all medical devices identified by the U.S. Food and Drug Administration as Class III devices and equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

Tl's standard terms of sale for semiconductor products (http://www.ti.com/sc/docs/stdterms.htm) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's non-compliance with the terms and provisions of this Notice.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2016, Texas Instruments Incorporated