Test Report: PMP31248 Universal AC Input, 12-V, 25-W PSR Reference Design



Description

This reference design is a quasi-resonant flyback power supply based on the UCC28730 primary side regulation (PSR) controller and UCC24650 (wake-up monitor). Using PSR topology eliminates the need of an optocoupler, increases reliability, and optimizes system cost. The design achieves less than 6-mW standby power (at 230 V_{AC}) and over 85% efficiency at 25-W load.



Top Photo

Features

- 185-V_{AC} to 265-V_{AC} input, 50 Hz and 60 Hz; 12-V, 2.1-A output
- Over 85% average 4-point efficiency
- Over 82% efficiency at 2% load (0.4 W)
- Less than 6-mW standby power losses
- Protected against output short circuits

Applications

• Dishwasher



Bottom Photo



Angled Photo

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements				
Parameter	Specifications			
Input Voltage	185 V _{AC} – 265 V _{AC}			
Frequency	47 Hz – 63 Hz			
Output Voltage	12 V _{DC}			
Output Current	1.67 A (average), 2.1 A (peak)			

1.2 Required Equipment

- 0 V_{AC} 265 V_{AC}, 45 Hz 65 Hz (minimum current limit 1 A_{RMS}), AC constant voltage source (VS1)
- Electronic load, (constant current range 0 A 3 A)
- Oscilloscope (minimum 100-MHz bandwidth)
- Current probe (minimum 100-kHz bandwidth)
- Optional: infrared camera
- Spectrum analyzer (typical frequency range 9 kHz 3.5 GHz)
- AC Line Impedance Stabilization Network (LISN)
- Variable isolation transformer (100 W minimum)

1.3 Testing Conditions

- 1. Connect the source VS1 to J1-1 and J1-2.
- 2. Connect the load to J2-1 (positive) and J2-2 (negative).
- 3. Attach a current probe in series to the output to take load transient response behavior.
- 4. Turn on VS1 (accepted range: $185 V_{AC} 265 V_{AC}$).
- 5. Increase the load on the output.
- 6. After turn off, discharge the capacitors C1 and C2 by means of an external resistor (warning: HIGH VOLTAGE)

1.4 Considerations

The reference design PMP31248 Rev_C was built on PMP31248 Rev_A PCB.

1.5 Dimensions

The board dimensions are 114.30 mm × 41.91 mm, the height is 24 mm (transformer T1).

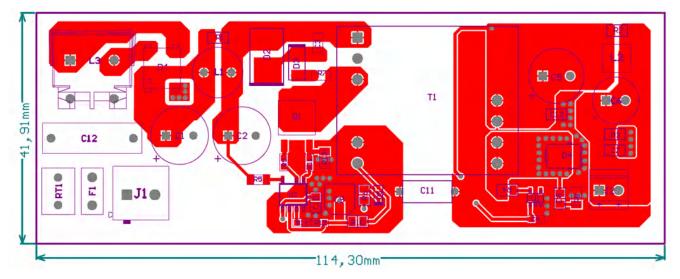


Figure 1-1. Outline



2 Testing and Results

2.1 Efficiency Graphs and Data

2.1.1 Efficiency Graph: Light Load Performance

The efficiency graph in Figure 2-1 shows the converter efficiency, versus output current, during light load.

The input voltage was set to 185 V_{AC} , 230 V_{AC} , and 265 V_{AC} , and the load current range restricted between zero and 70 mA.

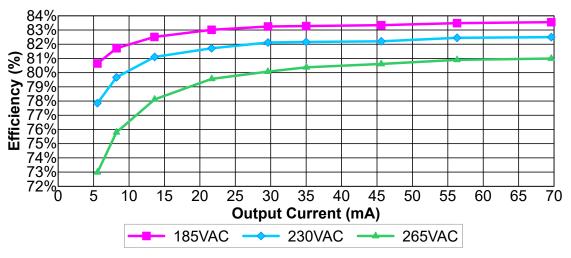


Figure 2-1. Light Load Efficiency

2.1.2 Efficiency Graph: Available Output Power Versus Input Power

The graph in Figure 2-2 shows the available output power versus input power at 230 V_{AC}.

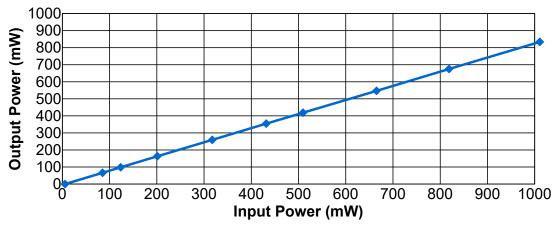


Figure 2-2. Output Power vs Input Power



2.1.3 Efficiency Graph: Full Load Performance

The efficiency graph in Figure 2-3 shows the converter efficiency, versus output current, from light to full load.

The input voltage was set to 185 V_{AC} , 230 V_{AC} , and 265 V_{AC} .

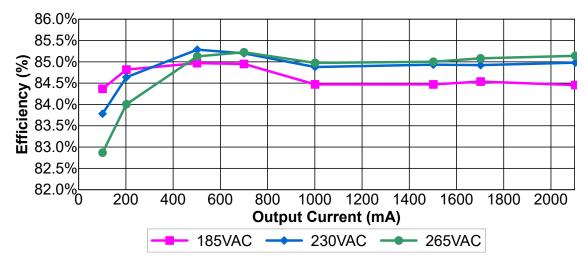


Figure 2-3. Full Load Efficiency

2.1.4 Efficiency Data

The efficiency graphs (Figure 2-1, Figure 2-2, and Figure 2-3) report the data from the tables shown below at 185 V_{AC} , 230 V_{AC} , and 265 V_{AC} .

P _{IN} (mW)	V _{OUT} (V)	I _{OUT} (mA)	P _{OUT} (mW)	Efficiency (%)
3.7	12.13	0.0	0.00	0.00%
82.3	11.98	5.54	66.37	80.64%
120.7	11.97	8.24	98.63	81.72%
197.5	12.00	13.58	162.96	82.51%
312.7	11.99	21.65	259.58	83.01%
425.9	11.97	29.62	354.55	83.25%
502.8	11.96	35.01	418.72	83.28%
656.6	12.00	45.6	547.20	83.34%
808.6	11.99	56.3	675.04	83.48%
998.8	11.99	69.6	834.50	83.55%

Гаble 2-1. V_{IN} = 185 V_{AC}, f = 50 Hz

Table 2-2. V_{IN} = 230 V_{AC}, f = 50 Hz

P _{IN} (mW)	V _{OUT} (V)	I _{OUT} (mA)	P _{OUT} (mW)	Efficiency (%)	
5.6	12.15	0.0	0.00	0.00%	
85.1	11.98	5.53	66.25	77.85%	
123.4	11.96	8.22	98.31	79.67%	
201.2	11.99	13.61	163.18	81.11%	
317.4	11.98	21.65	259.37	81.72%	
431.6	11.97	29.61	354.43	82.12%	
509.5	11.96	35.00	418.60	82.16%	
665.1	11.99	45.6	546.74	82.20%	
818.7	11.99	56.3	675.04	82.45%	
1010.7	11.98	69.6	833.81	82.50%	

P _{IN} (mW)	V _{OUT} (V)	I _{OUT} (mA)	P _{OUT} (mW)	Efficiency (%)
11.3	12.15	0.0	0.00	0.00%
91.1	11.98	5.55	66.49	72.98%
129.7	11.96	8.22	98.31	75.80%
208.9	11.99	13.61	163.18	78.12%
326.3	11.98	21.67	259.61	79.56%
442.5	11.97	29.60	354.31	80.07%
523.0	12.00	35.03	420.36	80.37%
678.8	12.00	45.6	547.20	80.61%
834.4	11.99	56.3	675.04	80.90%
1029.5	11.98	69.6	833.81	80.99%

Table 2-3. V_{IN} = 265, V_{AC}, f = 50 Hz

2.2 Thermal Images

Figure 2-4 and Table 2-4 show the thermal picture of the converter supplied at 230 V_{AC} and 50 Hz, taken after 30 minutes soak time, at 25.5°C ambient temperature, and placed horizontally to the bench.

The board runs at 1.7 A under still air conditions.

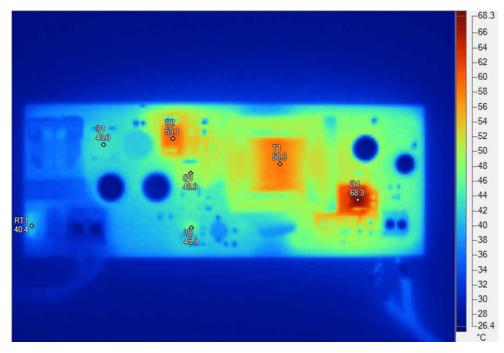


Figure 2-4. Thermal Image	Figure	2-4.	Thermal	Image
---------------------------	--------	------	---------	-------

	iain iniaye wan	
Temperature	Emissivity	Background
59.1°C	0.96	25.5°C
43.0°C	0.96	25.5°C
40.4°C	0.96	25.5°C
45.9°C	0.96	25.5°C
48.9°C	0.96	25.5°C
58.3°C	0.96	25.5°C
68.3°C	0.96	25.5°C
	59.1°C 43.0°C 40.4°C 45.9°C 48.9°C 58.3°C	59.1°C 0.96 43.0°C 0.96 40.4°C 0.96 45.9°C 0.96 48.9°C 0.96 58.3°C 0.96

Table 2-4. Main Image Markers



2.3 Static Output Voltage Variation versus Load

The output voltage versus load current is shown in Figure 2-5 and Figure 2-6.

2.3.1 Light Load Range


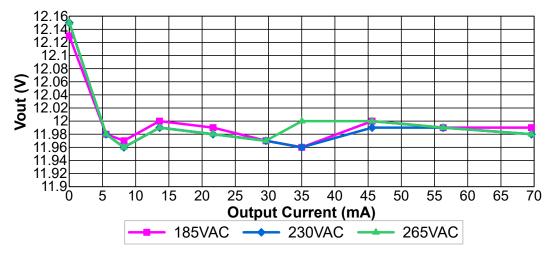


Figure 2-5. Output Voltage vs Output Current (Light Load)

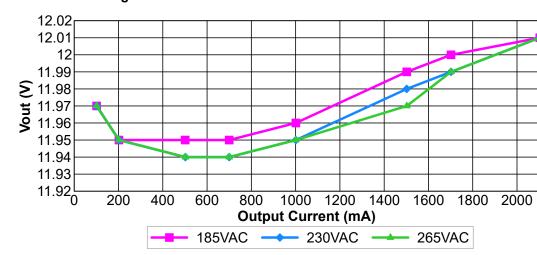

2.3.2 Light to Full Load Range

Figure 2-6. Output Voltage vs Output Current (whole load range)



2.4 EMI Measurement According to EN55022 Class-B Quasi-Peak Limits

The EMI signature of this converter was measured by using the following devices:

- Spectrum Analyzer
 - Manufacturer: Rohde & Schwarz
 - Part number: 1065.6000.20
 - Freq. range: 9 kHz 3.5 GHz
- LISN
 - Manufacturer: Hameg
 - Model: HM6050-2
- Load resistor 7.06 Ω
- Variable isolation transformer
 - Manufacturer: Block TE
 - Model: BR350

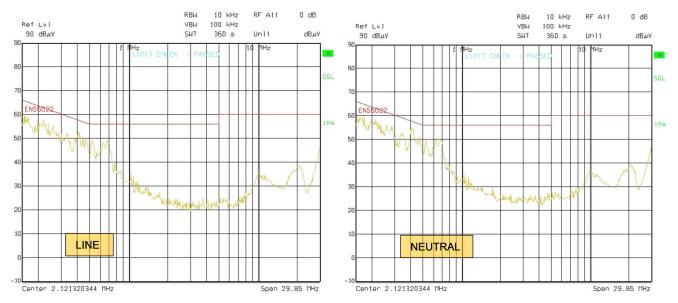


Figure 2-7. EMI: V_{IN} = 230 V_{AC}, R_{LOAD} = 7.06 Ω, Negative Output Terminal Connected to LISN Ground



3 Waveforms

3.1 Switching on Q1 (V_{DS} Voltage) at Full Load

The switching waveforms were measured by supplying the converter at maximum V_{IN} of 265 V_{AC} with 1.7-A load current.

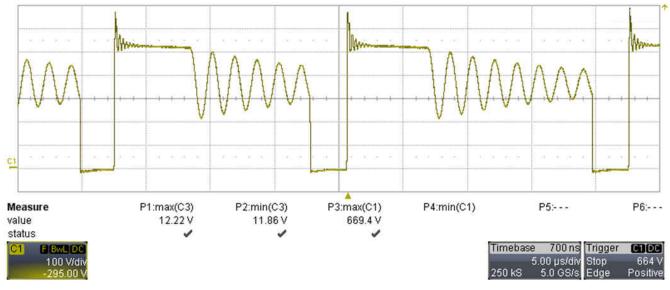


Figure 3-1. Waveform Q1-V_{DS} (100 V/div, 5 µs/div, 200 MHz BWL)

The image in Figure 3-2 is the same measurement as in Figure 3-1 but with time base of 1 μ s/div to enlarge the overshoot.

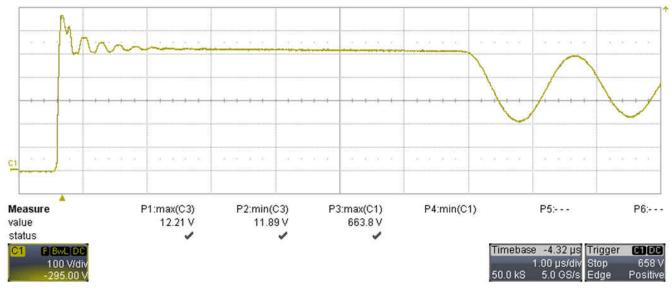


Figure 3-2. Waveform Q1-V_{DS} (100 V/div, 1 µs/div, 200 MHz BWL)



3.2 Output Voltage Ripple

The output voltage ripple was measured by supplying the converter at 230 V_{AC} , while loaded at 1.7 A; the bandwidth limit of oscilloscope (BWL) was set to 20 MHz.

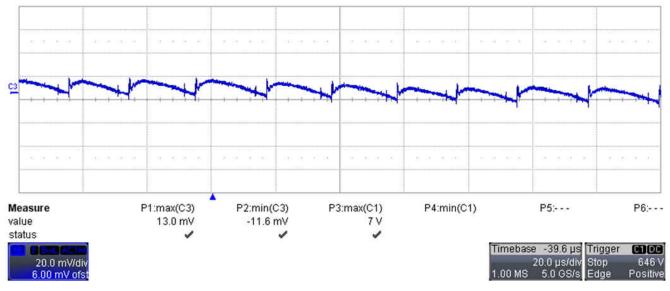


Figure 3-3. Output Voltage (20 mV/div, 20 µs/div, AC coupling)

Figure 3-4 is the same measurement as in Figure 3-3 but with longer time division, showing details about low frequency ripple.

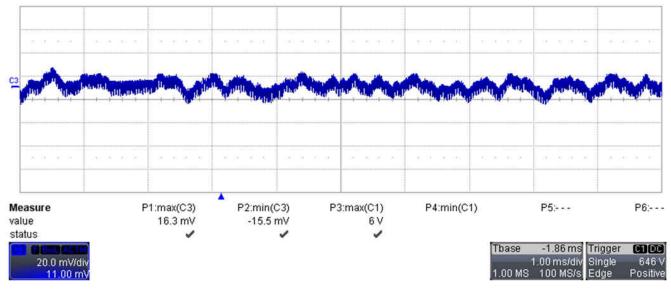



Figure 3-4. Output Voltage (20 mV/div, 1 ms/div, AC coupling)



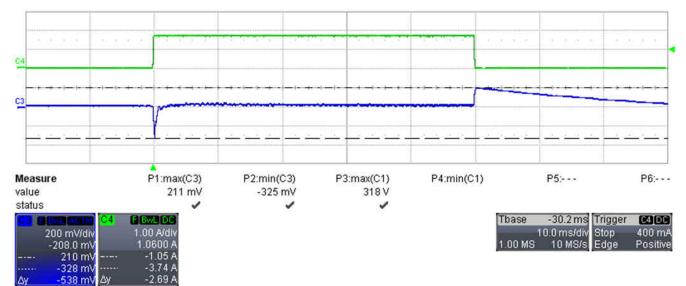3.3 Load Transients

The output voltage variation, during load transients, was measured by supplying the converter at 230 V_{AC} . The load was switched between 0 A and 1.7 A. For voltage and current measurement, the bandwidth limit of oscilloscope was set to 20 MHz.

- C3: Output voltage (200 mV/div, 10 ms/div, AC coupling)
- C4: Output current (1 A/div, DC coupling)







3.4 Start-Up and Shutdown Sequence

During these tests, the AC source was turned on and off. The input (230 V_{AC}) and output voltages were measured (BWL limited to 20 MHz).

3.4.1 Start-Up Sequence

3.4.1.1 Load Current 0 A

- C1: Input AC voltage (200 V/div, 100 ms/div, DC coupling)
- C3: Output voltage (5 V/div, DC coupling)

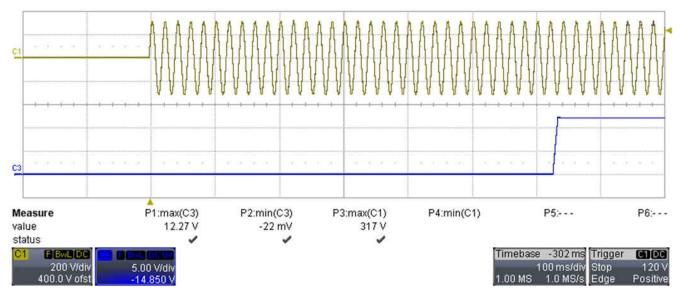


Figure 3-6. Start-Up With 0-A Load (100 ms/div)

Figure 3-7 is the same measurement as in Figure 3-6 but with smaller time division (20 ms/div).

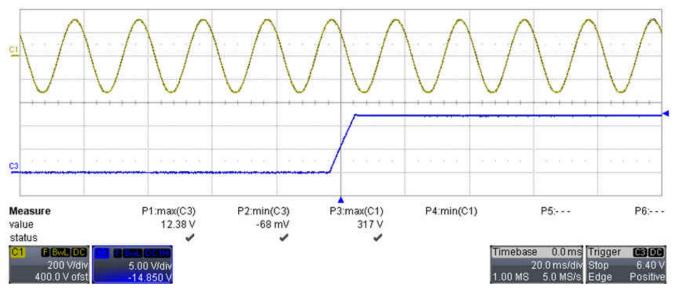


Figure 3-7. Start-Up With 0-A Load (20 ms/div)

3.4.1.2 Load Current 1.7 A

- C1: Input AC voltage (200 V/div, 100 ms/div, DC coupling)
- C3: Output voltage (5 V/div, DC coupling)

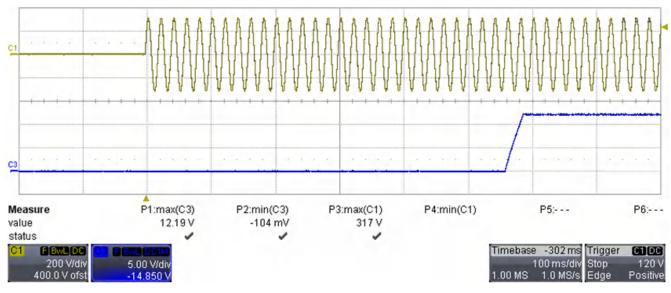


Figure 3-8. Start-Up With 1.7-A Load (100 ms/div)

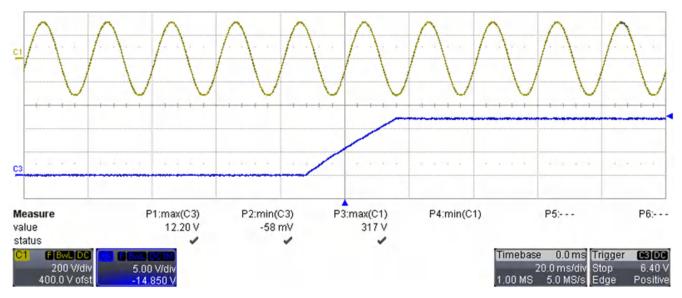


Figure 3-9 is the same measurement as in Figure 3-8 but with smaller time division (20 ms/div).

Figure 3-9. Start-Up With 1.7-A Load (20 ms/div)



3.4.2 Shutdown Sequence

The output voltage was measured by switching off the AC voltage source while the load was set to 1.7 A and V_{IN} to 230 V_{AC} .

- C1: Input AC voltage (200 V/div, 20 ms/div, DC coupling)
- C3: Output voltage (5 V/div, DC coupling)

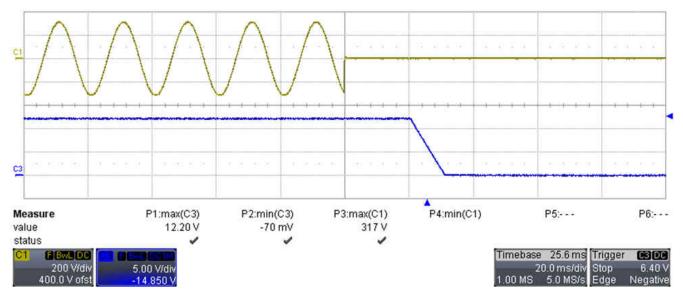


Figure 3-10. Shutdown Sequence With 1.7-A Load Current

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated